

Biasing circuit determines VGS
at VD, and ID setpoint

