EE3C11 Team exercise 7

Create a small-signal model for the TLV4111

This model must include:

- 1. Frequency behavior of the voltage gain
- 2. Frequency behavior of the input impedance
- 3. Frequency behavior of the output impedance (needs chapter 11)
- 4. Input voltage noise spectral density
- 5. Input current noise spectral density

https://www.ti.com/lit/ds/symlink/tlv4111.pdf

