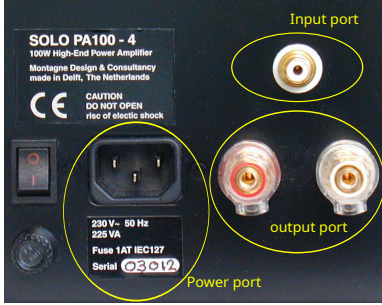


**Definition**  
**Amplifier object**  
 Three electrical ports  
 - input port:  
 connection to signal source  
 - output port:  
 connection to load  
 - power port:  
 connection to power supply  
**Amplification function**  
 - provide load with accurate copy of source signal  
**Characteristic property**  
 - Available power gain exceeds unity




**Functional model**  
 - Two-port input and output port only  
 - Active (delivers power)  
 - Linear, instantaneous, and time-invariant:

$$y(t) = Ax(t)$$


$$A = \text{constant}$$

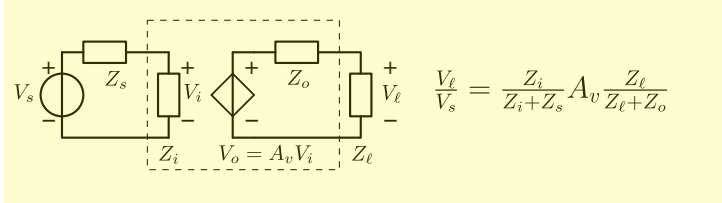**Example voltage amplifier**


- Source**  
 - Information accurately related to open-circuit voltage  
 - Source impedance inaccurately known
- Load**  
 - Information accurately related to driving voltage  
 - Load impedance inaccurately known



**Ideal characteristics**

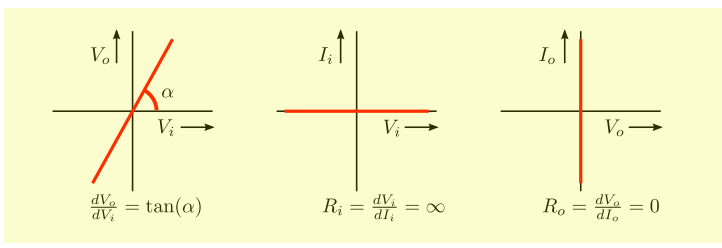

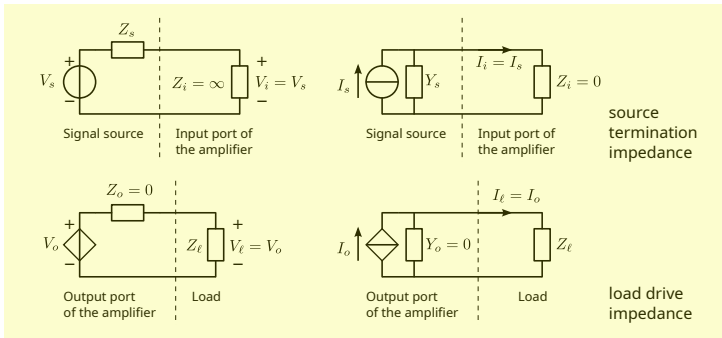**Source termination impedance and load drive impedance**



**Amplifier types**

Follow from best source termination and load drive conditions for accurate signal transfer


transfer	Type	Z <sub>i</sub>	Z <sub>o</sub>	A	B	C	D
voltage amplifier		infinite	0	A	0	0	0
transadmittance		infinite	infinite	0	B	0	0
transimpedance		0	0	0	0	C	0
current amplifier		0	infinite	0	0	0	D
voltage to voltage / current		infinite	R <sub>o</sub>	A	B	0	0
current to voltage / current		0	R <sub>o</sub>	0	0	C	D
voltage / current to voltage		R <sub>i</sub>	0	A	0	C	0
voltage / current to current		R <sub>i</sub>	infinite	0	B	0	D
voltage / current to voltage /current		R <sub>i</sub>	R <sub>o</sub>	A	B	C	D

**Amplifiers, concept, types and ideal behavioral models**

**Port isolation properties**



input-output	input-power	output-power	configuration
non-isolated	non-isolated	non-isolated	common-ground
non-isolated	non-isolated	isolated	x
non-isolated	isolated	non-isolated	differential receiver
non-isolated	isolated	isolated	floating supply
isolated	non-isolated	non-isolated	x
isolated	non-isolated	isolated	differential driver
isolated	isolated	non-isolated	x
isolated	isolated	isolated	differential receiver / driver

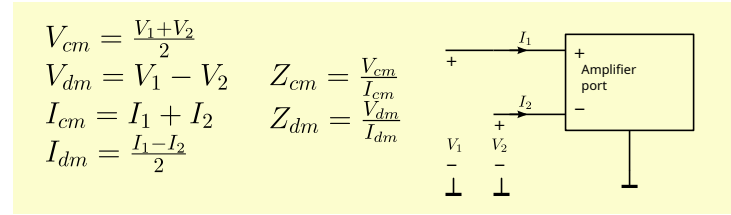**Floating port modeling and characterization**




**Modeling of ideal behavior (natural two-port)**


**Transmission-1 matrix representation**

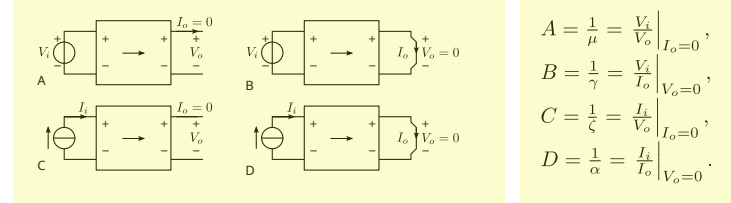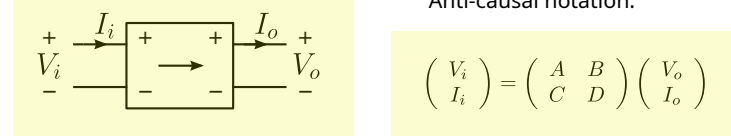

**Source-to-load transfer**

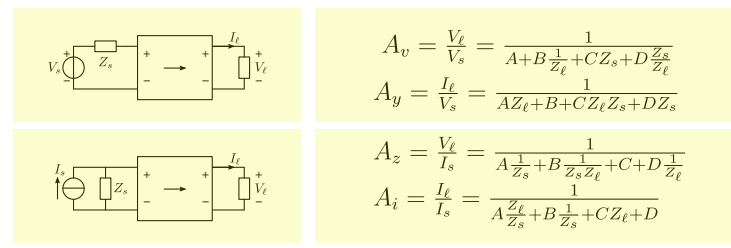

**Port impedances**

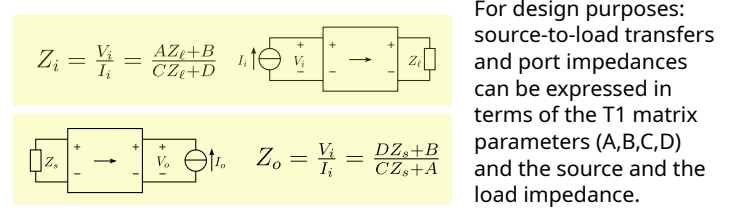


**Unilateral amplifier types**

**Zero reverse transfer**

$$AC = BD$$

Nullor and six non-unilateral types not listed in the table


**Network model**

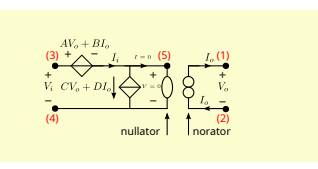

**MNA matrix stamp**

$$\begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} = \begin{pmatrix} 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ C & -C & 0 & 0 & 0 & 0 & D & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 \\ 0 & 0 & 0 & 0 & 1 & -1 & 0 & 0 \\ -A & A & 1 & 0 & -1 & -B & 0 & 0 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ I_o \\ I_i \end{pmatrix}$$

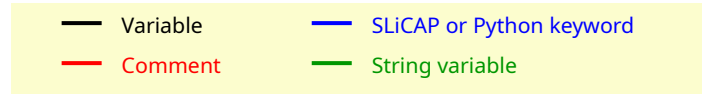**SLiCAP test bench for determination of the T1 matrix parameters**



```
#!/usr/bin/env python3
# -*- coding: utf-8 -*-

import SLiCAP as sl
import sympy as sp

sl.initProject('Circuit T1 matrix solutions')

files = ['cir-1']

# In all circuit files, use:

# Signal source: V1
# Load resistor: R1; model = 'r', value = 'R_ell'
# The name of the input node of the circuit: 'i'
# The name of the output node of the circuit: 'o'

# Define the symbolic variables
# The load resistance:
R_s, R_ell = sp.symbols('R_s, R_ell')

# The input vector:
ViIi = sp.Matrix([[sp.Symbol('V_i')], [sp.Symbol('I_i')]])

# The output vector:
VoIo = sp.Matrix([[sp.Symbol('V_o')], [sp.Symbol('I_o')]])

# Calculate and display the T1 matrix equation of the circuit(s):
for fileName in files:
    kicadFile = 'kicad/' + fileName + '/' + fileName + '.kicad_sch'
    cir = sl.makeCircuit(kicadFile)

    V_i = sl.doLaplace(cir, source='V1', detector='V_i').laplace
    I_i = -sl.doLaplace(cir, source='V1', detector='I_V1').laplace
    V_o = sl.doLaplace(cir, source='V1', detector='V_o').laplace
    I_o = sl.doLaplace(cir, source='V1', detector='I_R1').laplace

    # Calculate the T1 parameters
    A = sp.simplify(sp.limit(V_i/V_o, R_ell, 'oo'))
    B = sp.simplify(sp.limit(V_i/I_o, R_ell, 0))
    C = sp.simplify(sp.limit(I_i/V_o, R_ell, 'oo'))
    D = sp.simplify(sp.limit(I_i/I_o, R_ell, 0))

    # Create the T1 matrix
    T = sp.Matrix([[A, B], [C, D]])


    # Store the matrices in a result object for displaying on an HTML page
    result = sl.doMatrix(cir)
    result.M = T
    result.Iv = ViIi
    result.Dv = VoIo

    # Calculate all six transfers
    Z_i = sp.simplify((A*R_ell+B)/(C*R_ell+D)) # Input impedance
    Z_o = sp.simplify((D*R_s+B)/(C*R_s+A)) # Output impedance
    A_v = sp.simplify(1/(A+B/R_ell+C*R_s+D*R_s/R_ell)) # Voltage gain
    A_y = sp.simplify(1/(A*R_ell+B+C*R_s*R_ell+D*R_s)) # Transadmittance
    A_z = sp.simplify(1/(A/R_s+B/R_ell/R_s+C+D/R_ell)) # Transimpedance
    A_i = sp.simplify(1/(A*R_ell/R_s+B/R_s+C*R_ell+D)) # Current gain

    # HTML Report #####
    sl.htmlPage('Determination of T1 matrix parameters')
    sl.head2html('Circuit diagram')
    sl.img2html(fileName + '.svg', 500)
    sl.head2html('T1 matrix ')
    sl.text2html('The T1 matrix of the device under test is found as:')
    sl.eqn2html('T', T)
    sl.text2html('The matrix equation for the two-port (DUT) is found as:')
    sl.matrices2html(result)
    sl.head2html("Input and output impedances")
    sl.eqn2html("Z_i", Z_i)
    sl.eqn2html("Z_o", Z_o)
    sl.head2html("Transfers")
    sl.eqn2html("A_v", A_v)
    sl.eqn2html("A_y", A_y)
    sl.text2html("For $A_z$ and $A_i$, the voltage source V1 in series with " +
    "R4 is replaced with a current source in parallel with R4.")
    sl.eqn2html("A_z", A_z)
    sl.eqn2html("A_i", A_i)
```

**Determination of T1 matrix parameters**

**Circuit diagram**

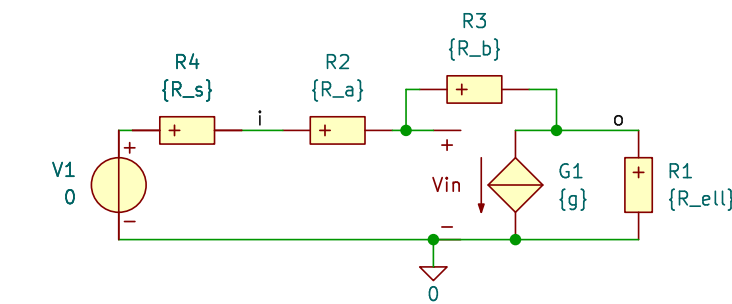

**T1 matrix**

The T1 matrix of the device under test is found as:

$$T = \begin{bmatrix} \frac{-R_a g - 1}{R_b g - 1} & \frac{-R_a - R_b}{R_b g - 1} \\ -\frac{g}{R_b g - 1} & -\frac{1}{R_b g - 1} \end{bmatrix} \quad (1)$$

The matrix equation for the two-port (DUT) is found as:

**Matrix equation:**

$$\begin{bmatrix} V_i \\ I_i \end{bmatrix} = \begin{bmatrix} \frac{-R_a g - 1}{R_b g - 1} & \frac{-R_a - R_b}{R_b g - 1} \\ -\frac{g}{R_b g - 1} & -\frac{1}{R_b g - 1} \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix} \quad (2)$$

**Input and output impedances**

$$Z_i = \frac{R_a + R_b + R_\ell (R_a g + 1)}{R_\ell g + 1} \quad (3)$$

$$Z_o = \frac{R_a + R_b + R_s}{R_a g + R_s g + 1} \quad (4)$$

**Transfers**

$$A_v = -\frac{R_\ell (R_b g - 1)}{R_a + R_b + R_\ell (R_a g + R_s g + 1) + R_s} \quad (5)$$

$$A_y = \frac{-R_b g + 1}{R_a + R_b + R_\ell R_s g + R_\ell (R_a g + 1) + R_s} \quad (6)$$

For  $A_z$  and  $A_i$ , the voltage source V1 in series with R4 is replaced with a current source in parallel with R4.

$$A_z = \frac{R_\ell R_s (-R_b g + 1)}{R_a R_\ell g + R_a + R_b + R_\ell R_s g + R_\ell + R_s} \quad (7)$$

$$A_i = \frac{R_s (-R_b g + 1)}{R_a R_\ell g + R_a + R_b + R_\ell R_s g + R_\ell + R_s} \quad (8)$$

Go to [cir-1\\_index](#)  
 SLiCAP: Symbolic Linear Circuit Analysis Program, Version 2.0.1 © 2009-2024 SLiCAP development team  
 For documentation, examples, support, updates and courses please visit: [analog-electronics.tudelft.nl](#)  
 Last project update: 2024-10-22 11:36:22