

Design of application-specific amplifiers in CMOS technology

1. Application Description

The design starts with a study of the application description. The result of this study is the designer's interpretation of this description in the form of a performance and test specification

2. Performance and Test Specification

The performance specification gives measurable quantities for

- Performance aspects of the amplifier, such as,
 - Noise performance
 - Drive capability
 - Bandwidth and frequency response
 - Weak nonlinearity
- Environmental conditions under which this performance must be achieved
 - Signal source specification
 - Load specification
 - Temperature range
 - EMI and ESD conditions
- Available resources for the amplifier
 - Power supply specification
 - Chip area and available packages
 - PCB area and external components
- More:
 - Interaction with environment (emitted radiation, temperature rise)
 - Safety
 - Reliability

The test specification describes the test methods and tools, or applicable standards for the quantities described above.

3. Feedback configuration and biasing concept of the amplifier

- Which electrical quantities can be used at the input and at the output of the amplifier?
- Which combinations of (zero, non-zero) transmission-1 matrix parameters can be used?
- In which way can these parameters be fixed with negative feedback?
- Is there, on grounds of the performance requirements a preference for a specific solution?

4. Technology noise (offset) performance

The equivalent input noise sources and the equivalent-input offset and offset drift of a negative feedback amplifier can at best equal those of its controller. If the feedback networks are not non-energetic, these equivalent input sources of the feedback amplifier will be larger than those of the controller. This effect can be studied with simple models. If the controller is designed with cascaded nullor-like stages (CS or balanced CS) these equivalent input sources can at best equal those of the input stage of the controller. Application of transformers or noise matching networks may be considered. Considering noise and offset, the technology may introduce show stoppers and set limits to the device geometry, the operating conditions, and the use of transformers or matching networks.

5. Technology drive capability

The drive capability of a feedback amplifier at best equals that of its controller. If the feedback networks are not non-energetic, the drive capability of the feedback amplifier will be lower than that of its controller. This effect can be studied with simple models. If the controller is designed with cascaded nullor-like stages (CS or balanced CS) the drive capability of the controller at best equals that of its output stage. Application of transformers or power matching networks may be considered. Considering the drive capability, the technology may introduce show stoppers and set limits to the device geometry, the operating conditions, and the use of transformers or matching networks.

6. Number of controller stages

In negative feedback amplifiers:

- The mid-band gain accuracy can be increased by increasing the mid-band value of the loop gain
 - The bandwidth can be increased by increasing the product of the mid-band loop gain and the dominant poles
 - The weak nonlinearity can be decreased by decreasing the differential-error-to-gain ratio
- This all can be done by increasing the number of stages and by:
- Maximizing the contribution of each stage to the mid-band value of the loop gain
 - Maximizing the contribution of each stage to the product of the mid-band loop gain and the poles
 - Minimizing the contribution of each stage to the differential-error-to-gain ratio of the loop gain

This all can be achieved by:

- Not inserting impedances in series or in parallel with the signal path
 - Use cascoded CS or balanced cascoded CS stages.
- If the bandwidth is too close to the process cut-off frequency, a feedback amplifier is not feasible.
- If the number of dominant poles exceeds four, frequency compensation may become too difficult and the amplifier may be designed as two cascaded feedback amplifiers

7. Structure of controller and feedback network

The stages in the controller must be cascaded properly:

- The input of subsequent stages is connected to the output port of preceding stages.
- Four-terminal controllers can be connected in two different ways to their environment.

8. Frequency compensation of the amplifier

The following frequency compensation techniques can be applied (order of preference)

- Phantom zero compensation
- Pole-splitting by increasing the interaction between two poles
- Pole-splitting by pole-zero canceling
- Resistive broadbanding
- Manipulate dominant pole(s) out of the dominant group (bandwidth reduction)
 - Reduction of the mid-band loop gain (resistive broadbanding or local feedback)
 - Excessive pole-splitting
 - Increasing the time constant of a more dominant pole

9. Biasing concept of the controller

- Add ideal bias sources (LTSpice) to the signal path of the controller and use the over-all biasing concept from step (3).
- Optimize the concept: minimize the number of floating voltage sources, and combine current sources.
- Check the performance and compare it with that of the signal path (SLiCAP, step (8))
- Make adjustments if necessary.

10. Weak nonlinearity check

Check the weak nonlinearity (differential-gain, differential phase, IMD, THD) if not within spec:

- Check signal excursions and if necessary, adjust bias voltages and currents.
- If the above does not give the desired results:
 - Try to compensate for nonlinearity
 - Increase the loop gain, it may be necessary to add another stage (see step(6))


11. Step-by step implementation of bias sources

For all bias sources:

- Find budgets for biasing parasitics, biasing errors and added noise of bias sources (SLiCAP)
- Find budgets for requires voltage swing across current sources and current excursions through bias voltage sources (LTSpice, step (10))
- Performance specification of bias source
- Design voltage or current bias source according to this specification
- Verify the behavior of the bias source
- Add it to the controller
- Verify the amplifier performance, and if necessary, make adjustments.

Design Active Antenna for radio astronomy in CMOS18 technology


1. Application Description

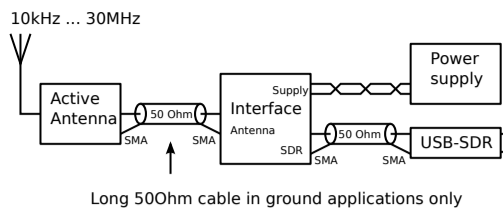


2. Performance specification

Antenna length: max 0.5m	IM distortion: -50dB: 10kHz-30MHz	Power supply: 1.8V
E-field antenna-referred noise: 10kHz : 100n [V/m√Hz]	Output 1dB compression level: 0dBm in 50ohm	Power dissipation: < 30mW
100kHz : 10n	Temperature range: -25 ... +70 deg Celsius	ESD discharge protected
1MHz : 5n		
30MHz : 5n		
Antenna gain (-3dB: 10kHz-30MHz) 0dB		

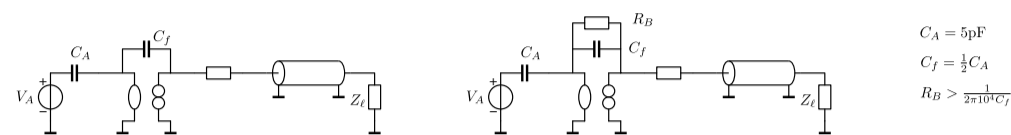
3. Feedback configuration and biasing concept of the amplifier



4. Technology noise (offset) performance

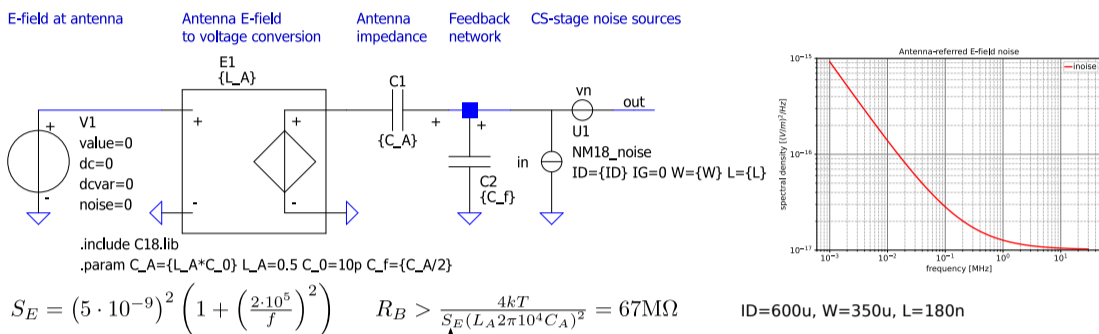

5. Technology drive capability

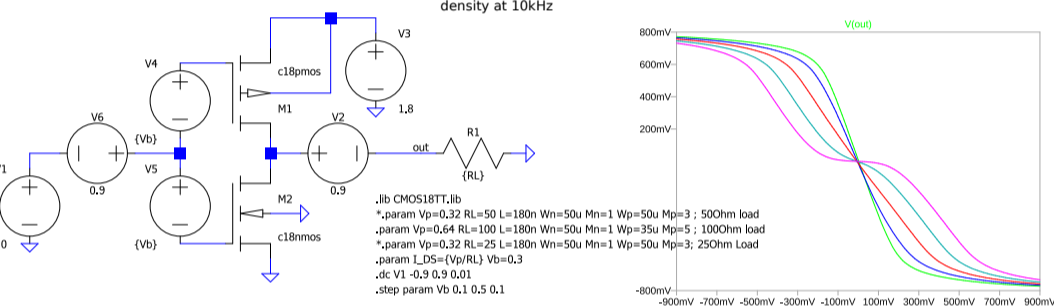


6. Number of controller stages

- Single-stage controller, push-pull stage (complementary parallel CS stage)
 - Noise: OK
 - Drive capability: OK
 - Bandwidth: OK
 - Weak nonlinearity NOT OK
- Two-stage controller with larger mid-band loop gain for improved accuracy and linearity

7. Structure of controller and feedback network


- CS input stage
- Complementary parallel CS output stage
- Unity gain inverting current amplifier intermediate stage (not counted as stage because it does not contribute a dominant pole and not increase the mid-band loop gain)

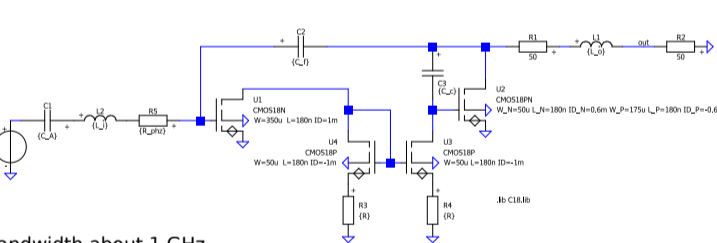8. Frequency compensation of the amplifier



- Bandwidth about 1 GHz
- Input and output phantom zeros
- Pole splitting in output stage

9. Biasing concept of the controller

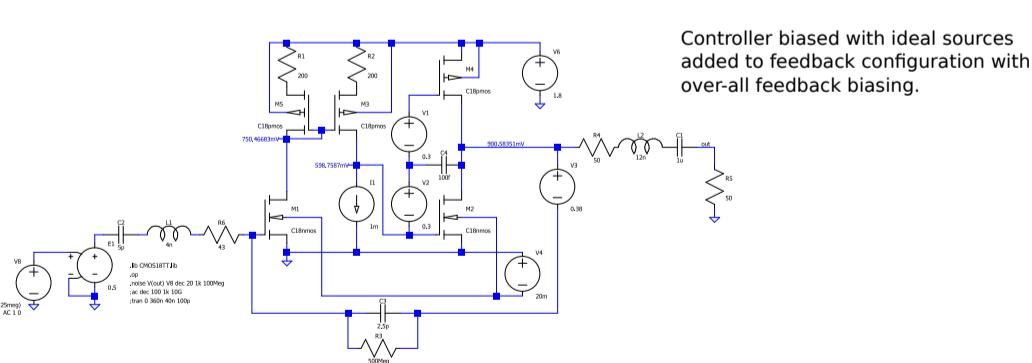

10. Weak nonlinearity check

In-band IMD of the above configuration OK!

11. Step-by step implementation of bias sources

