

# **Structured Electronic Design**

## Application of Negative Feedback in Amplifier Design

*Anton J.M. Montagne*

# Application of negative feedback


1. Amplification mechanism found in biased amplifying devices suffers from numerous imperfections
2. We need error reduction techniques to improve the performance-to-cost ratio

## Negative 🙄 feedback?


Negative (corrective 😊) feedback can be regarded as an error reduction technique that:

- Makes the properties of the amplifier less dependent on those of the biased amplifying devices
- Uses an accurate feedback network as reference for the transfer
- Allows the use of a feedback network with an available power gain equal or less than unity
  - Accurate (passive) components available for the feedback network
- Strongly facilitates **orthogonal** design of performance aspects

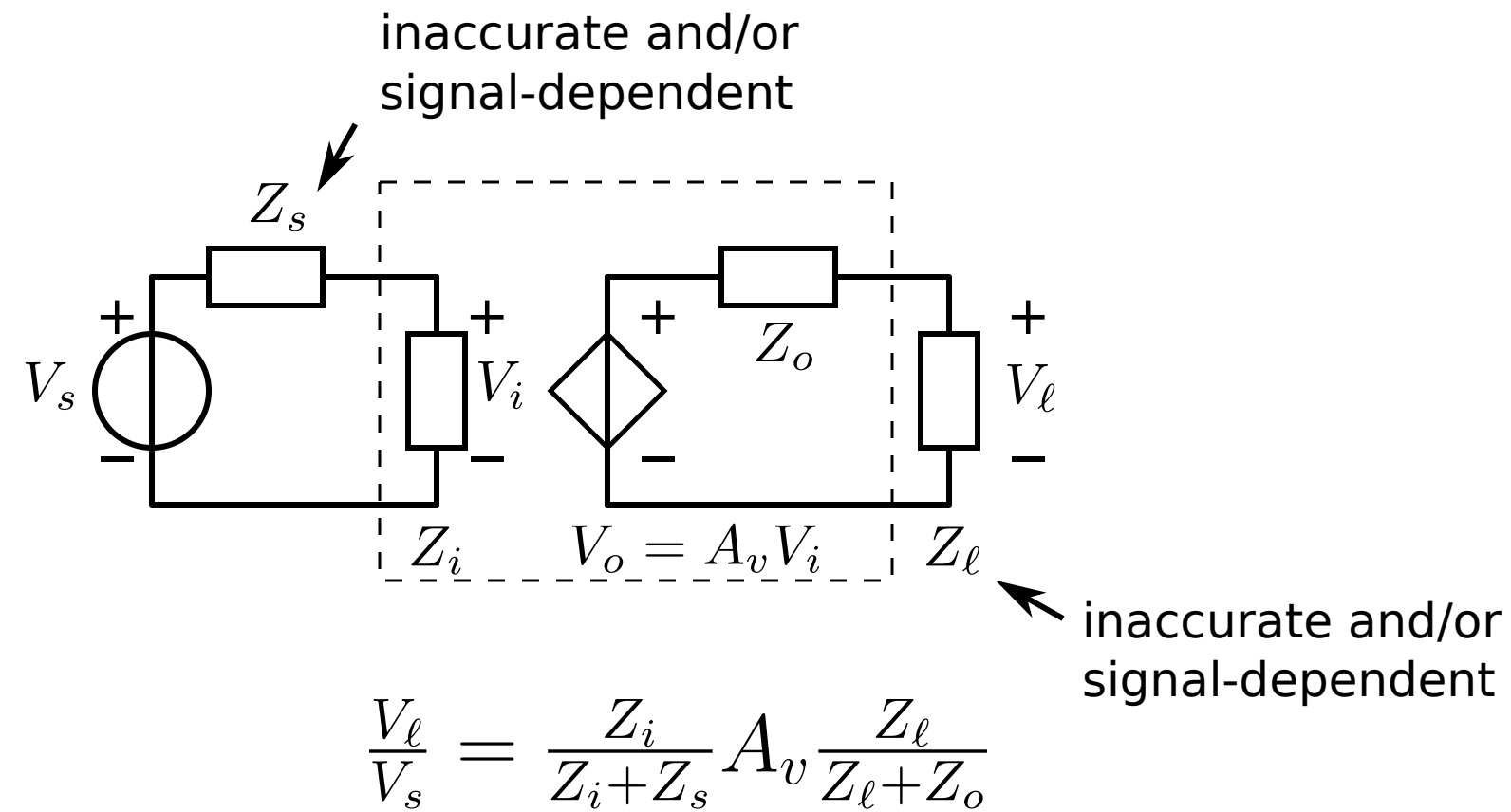**Example:** **Brute-force** reduction of the influence of source and load impedance variations on the accuracy of the transfer of a voltage amplifier



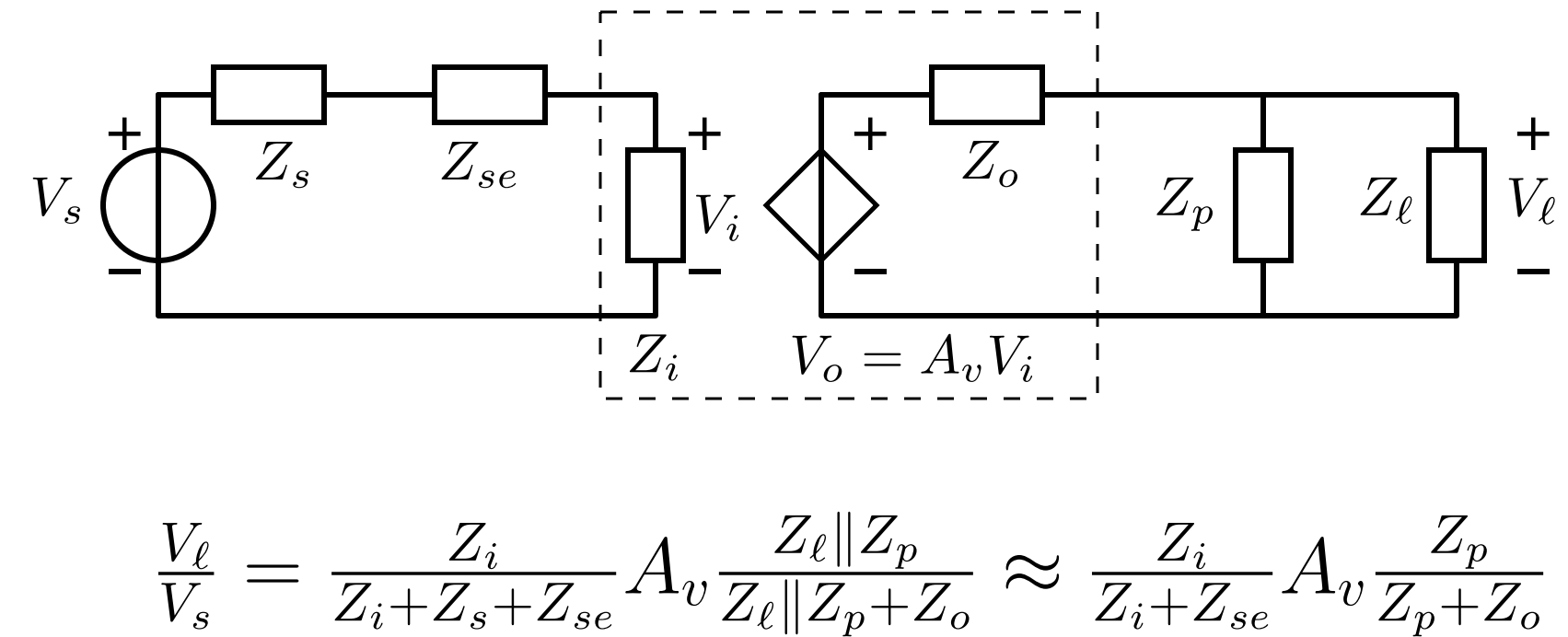**Brute-force:** Insert **dominant**, high-accuracy and linear impedances in the signal path:



**Remember:** **Thou shalt not insert impedances in series or in parallel with the signal path**

**Conclusion:** Strong interaction between:

- accuracy and noise addition
- accuracy and power inefficiency
- accuracy and source-to-load transfer

**Orthogonality:** See: "orthogonalDesignNegativeFeedbackAmplifiers.svg"

- ☹️ At the source:  
**reduction of the signal to noise ratio**
- ☹️ At the load:  
**decrease of power efficiency**
- ☹️ Source-to-load transfer:  
**reduced as a result of attenuation**