

# **Structured Electronic Design**


EE3C11

Amplifiers: Modeling of Ideal Behavior


*Anton J.M. Montagne*
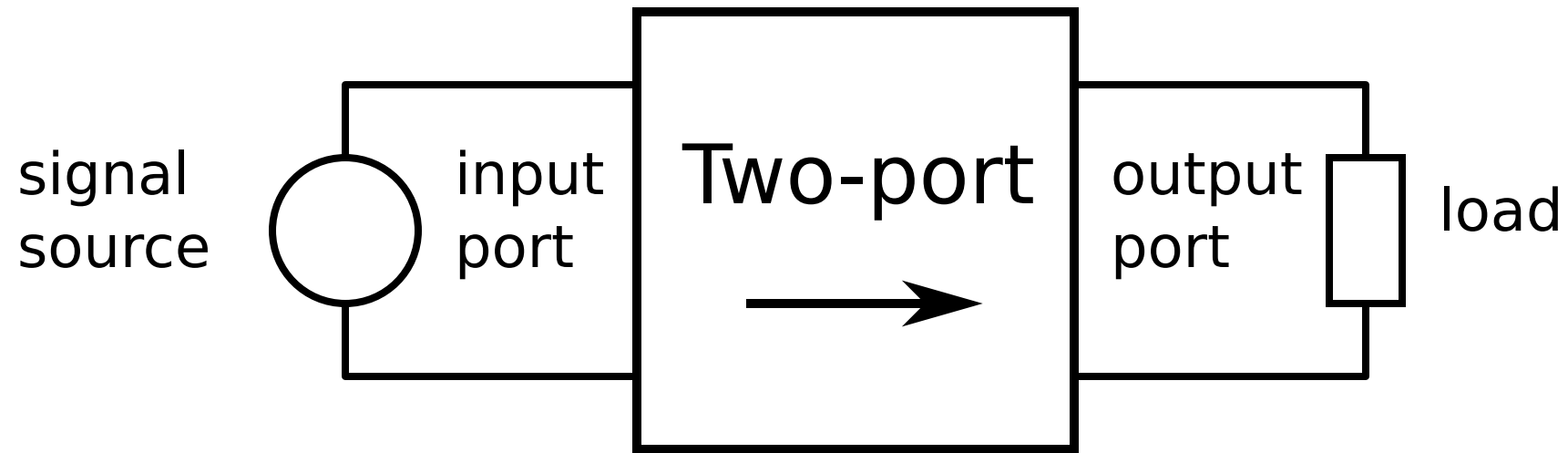
# Two-port model

Functional model:  
the power port will be omitted



Two-port modeling: Chapter 18.6

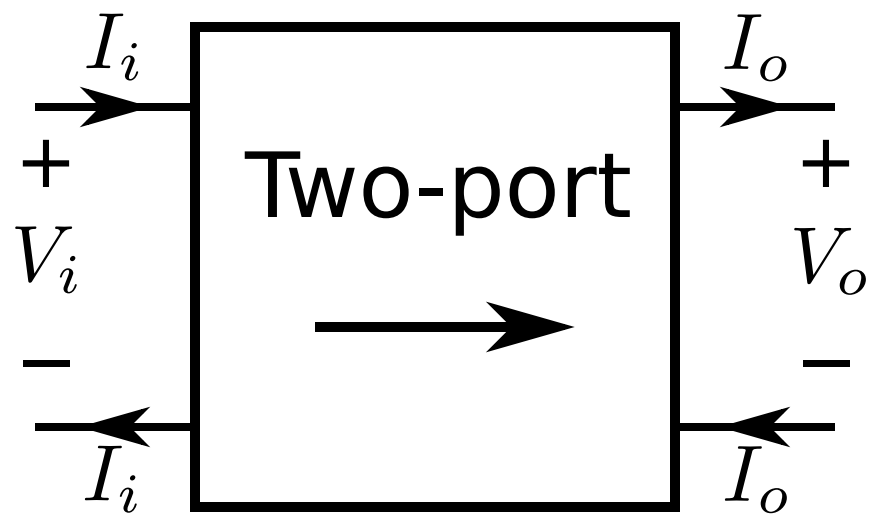

Two-port  
conditions  
Two-port  
representations

Transmission-1 (anti-causal)  
representation

$$\begin{pmatrix} V_i \\ I_i \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_o \\ I_o \end{pmatrix}$$


$$A = \frac{1}{\mu} = \left. \frac{V_i}{V_o} \right|_{I_o=0}, \quad \text{Open output}$$

$$B = \frac{1}{\gamma} = \left. \frac{V_i}{I_o} \right|_{V_o=0}, \quad \text{Shorted output}$$

$$C = \frac{1}{\zeta} = \left. \frac{I_i}{V_o} \right|_{I_o=0}, \quad \text{Open output}$$

$$D = \frac{1}{\alpha} = \left. \frac{I_i}{I_o} \right|_{V_o=0}, \quad \text{Shorted output}$$

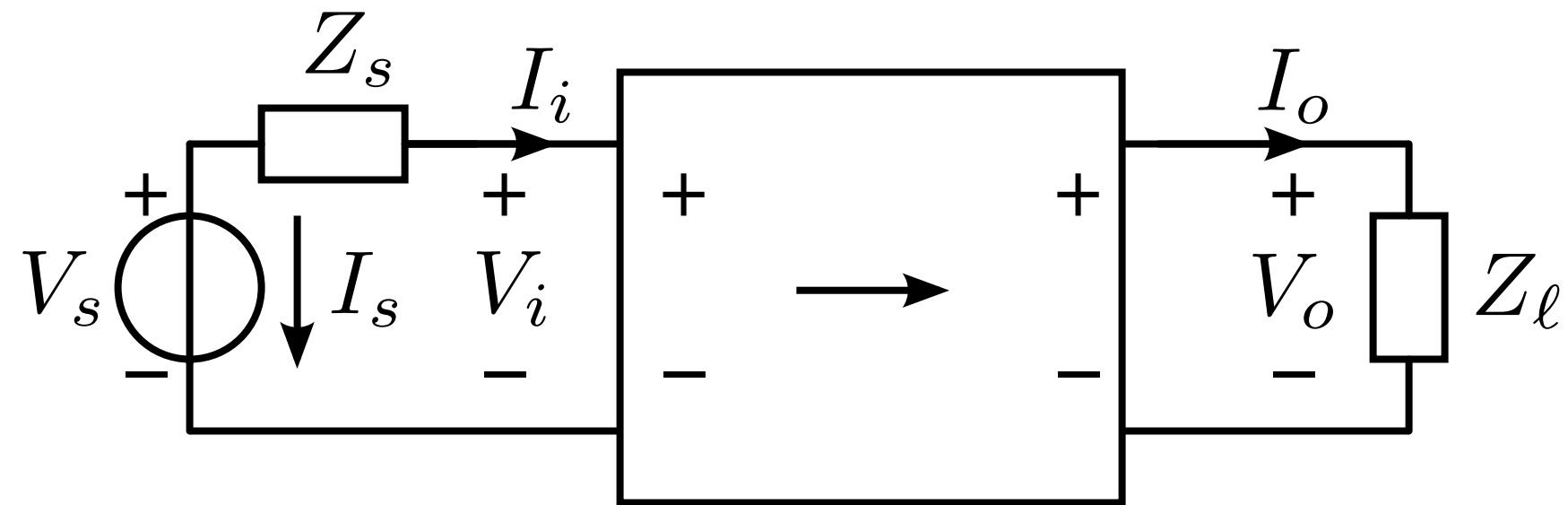
# Determination of the transmission-1 two-port parameters



$$\mu = \frac{1}{A} = \frac{V_o}{V_i} \Big|_{I_o=0} \quad A = \lim_{Z_\ell \rightarrow \infty} \left( \frac{V_i}{V_o} \right) \quad \zeta = \frac{1}{C} = \frac{V_o}{I_i} \Big|_{I_o=0} \quad C = \lim_{Z_\ell \rightarrow \infty} \left( \frac{I_i}{V_o} \right)$$


$$\gamma = \frac{1}{B} = \frac{I_o}{V_i} \Big|_{V_o=0} \quad B = \lim_{Z_\ell \rightarrow 0} \left( \frac{V_i}{I_o} \right) \quad \alpha = \frac{1}{D} = \frac{I_o}{I_i} \Big|_{V_o=0} \quad D = \lim_{Z_\ell \rightarrow 0} \left( \frac{I_i}{I_o} \right)$$

# Source to load transfer

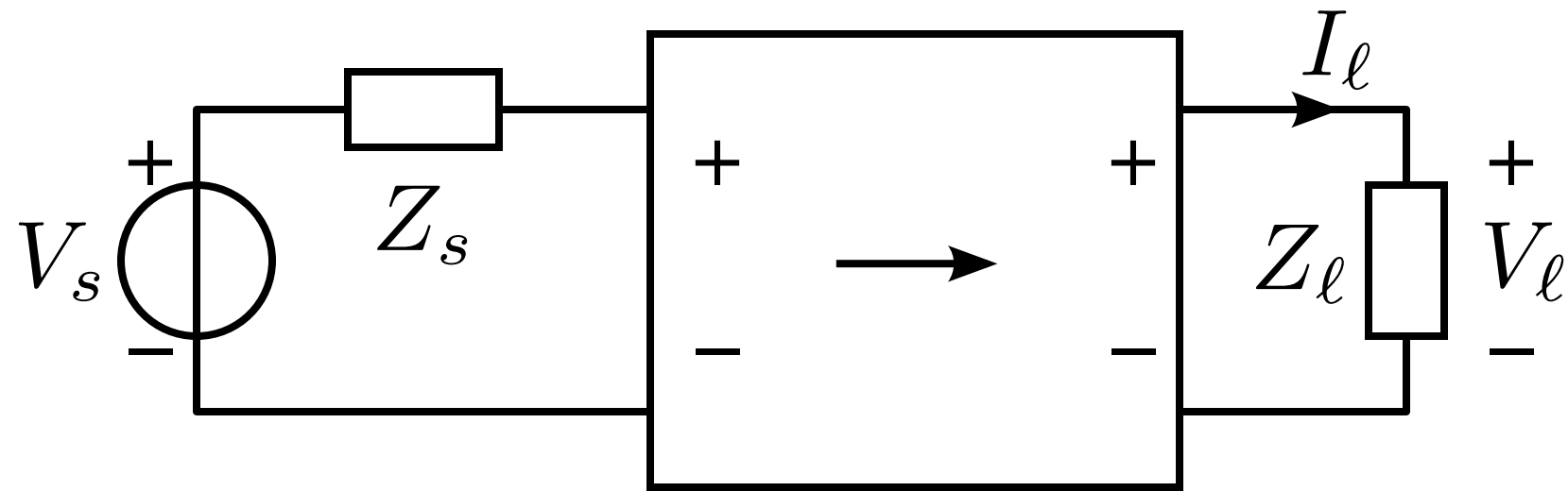

$$A_v = \frac{V_l}{V_s} = \frac{1}{A + B \frac{1}{Z_l} + C Z_s + D \frac{Z_s}{Z_l}}$$

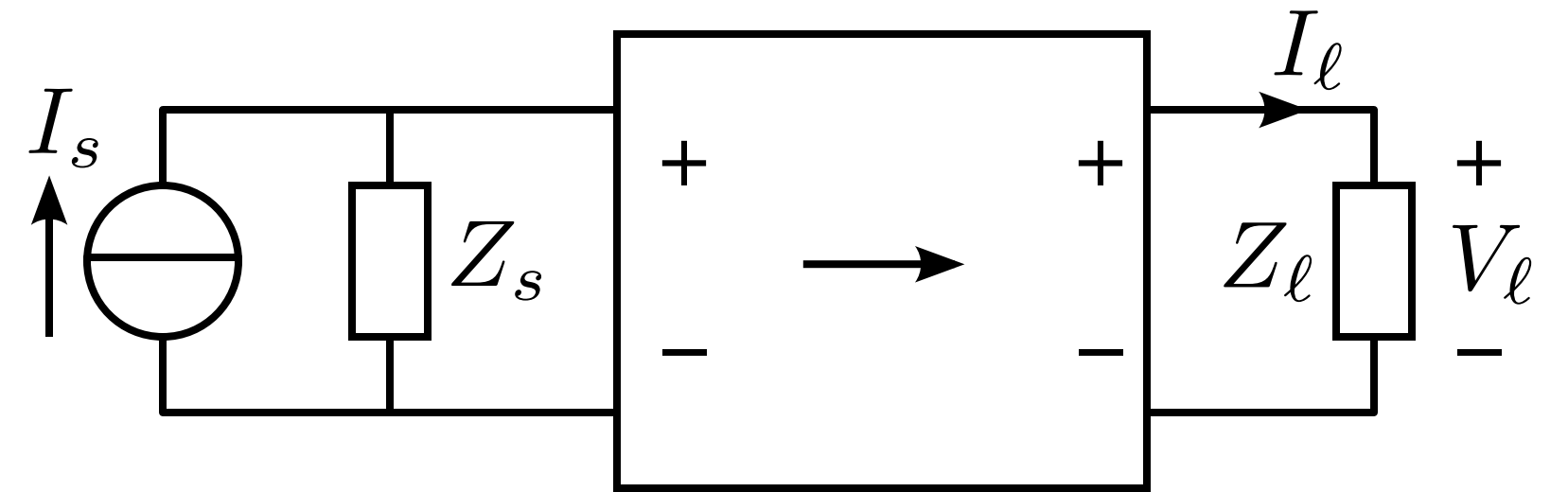
$$A_y = \frac{I_l}{V_s} = \frac{1}{A Z_l + B + C Z_l Z_s + D Z_s}$$



$$A_z = \frac{V_l}{I_s} = \frac{1}{A \frac{1}{Z_s} + B \frac{1}{Z_s Z_l} + C + D \frac{1}{Z_l}}$$


$$A_i = \frac{I_l}{I_s} = \frac{1}{A \frac{Z_l}{Z_s} + B \frac{1}{Z_s} + C Z_l + D}$$

## Available power gain

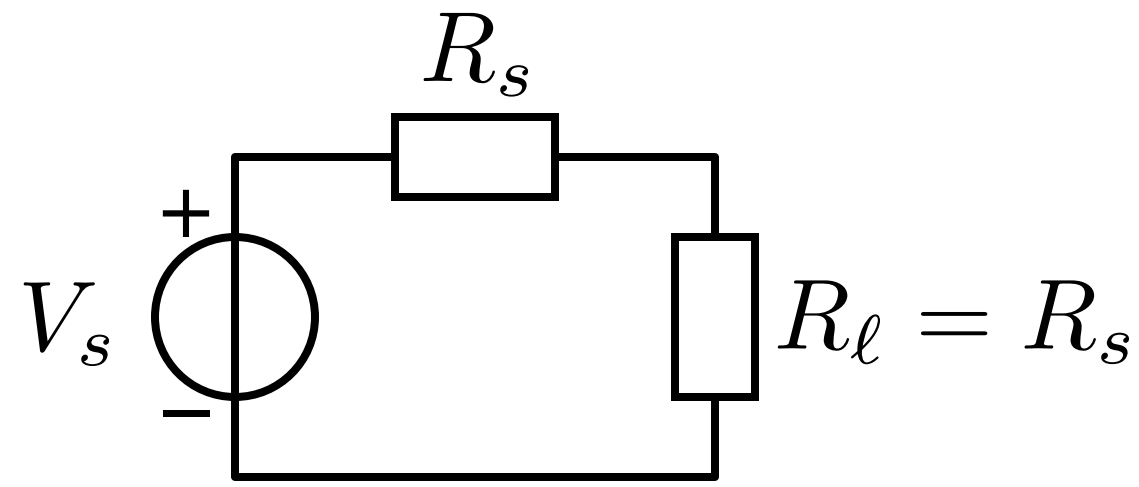

Available power of the source

$$P_s = \frac{V_s^2}{4R_s}$$

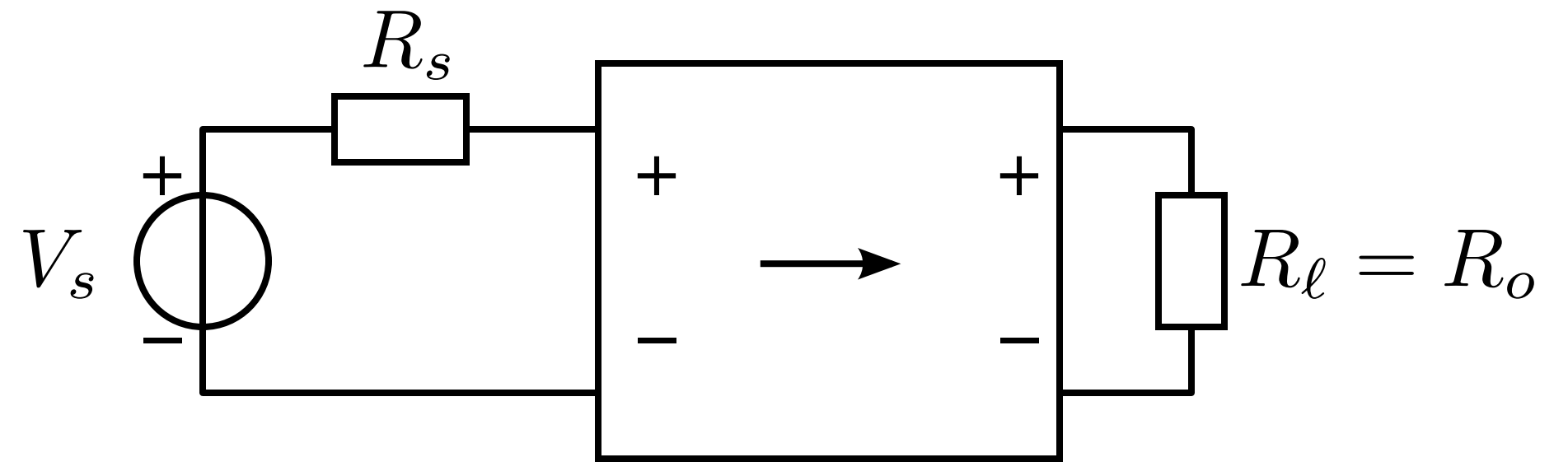


Available power of the amplifier  
connected to the source

$$P_a = \frac{V_s^2}{4(DR_s + B)(CR_s + A)}$$


Available power gain

$$G_p = \frac{P_a}{P_s} = \frac{1}{AD + AB/R_s + BC + CDR_s}$$

# Port impedances

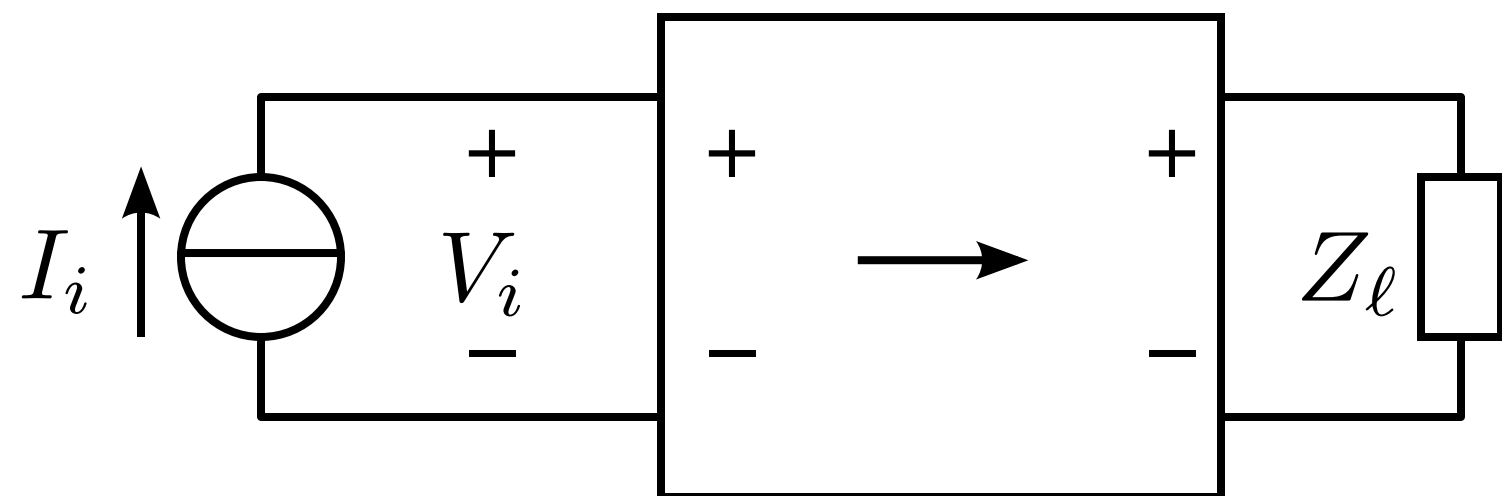
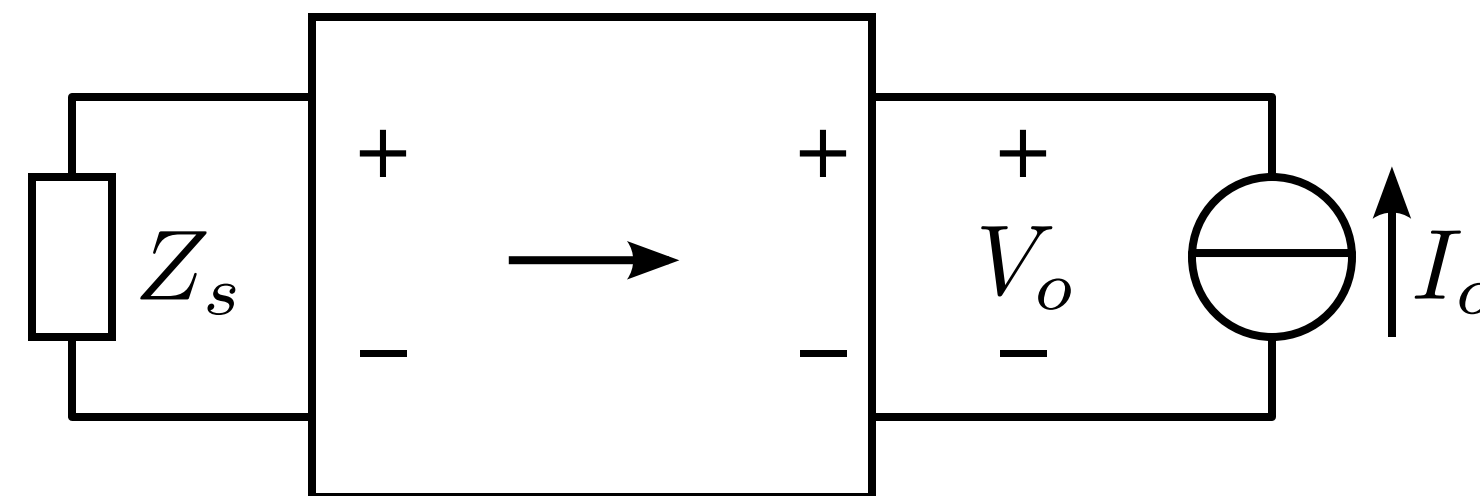
$$Z_i = \frac{V_i}{I_i} = \frac{AZ_l + B}{CZ_l + D}$$



$$Z_o = \frac{V_o}{I_o} = \frac{DZ_s + B}{CZ_s + A}$$


Unilateral if:

$$AD = BC$$

# Amplifier types

no	amplifier type	$Z_i$	$Z_o$	A	B	C	D
1	Voltage amplifier	$\infty$	0	A	0	0	0
2	Transadmittance amplifier	$\infty$	$\infty$	0	B	0	0
3	Voltage input, finite nonzero output impedance	$\infty$	$Z_o$	A	B	0	0
4	Transimpedance amplifier	0	0	0	0	C	0
5	Current amplifier	0	$\infty$	0	0	0	D
6	Current input, finite nonzero output impedance	0	$Z_o$	0	0	C	D
7	Finite nonzero input impedance, voltage output	$Z_i$	0	A	0	C	0
8	Finite nonzero input impedance, current output	$Z_i$	$\infty$	0	B	0	D
9	Finite nonzero input and output impedance	$Z_i$	$Z_o$	A	B	C	D

# Generalized two-port model

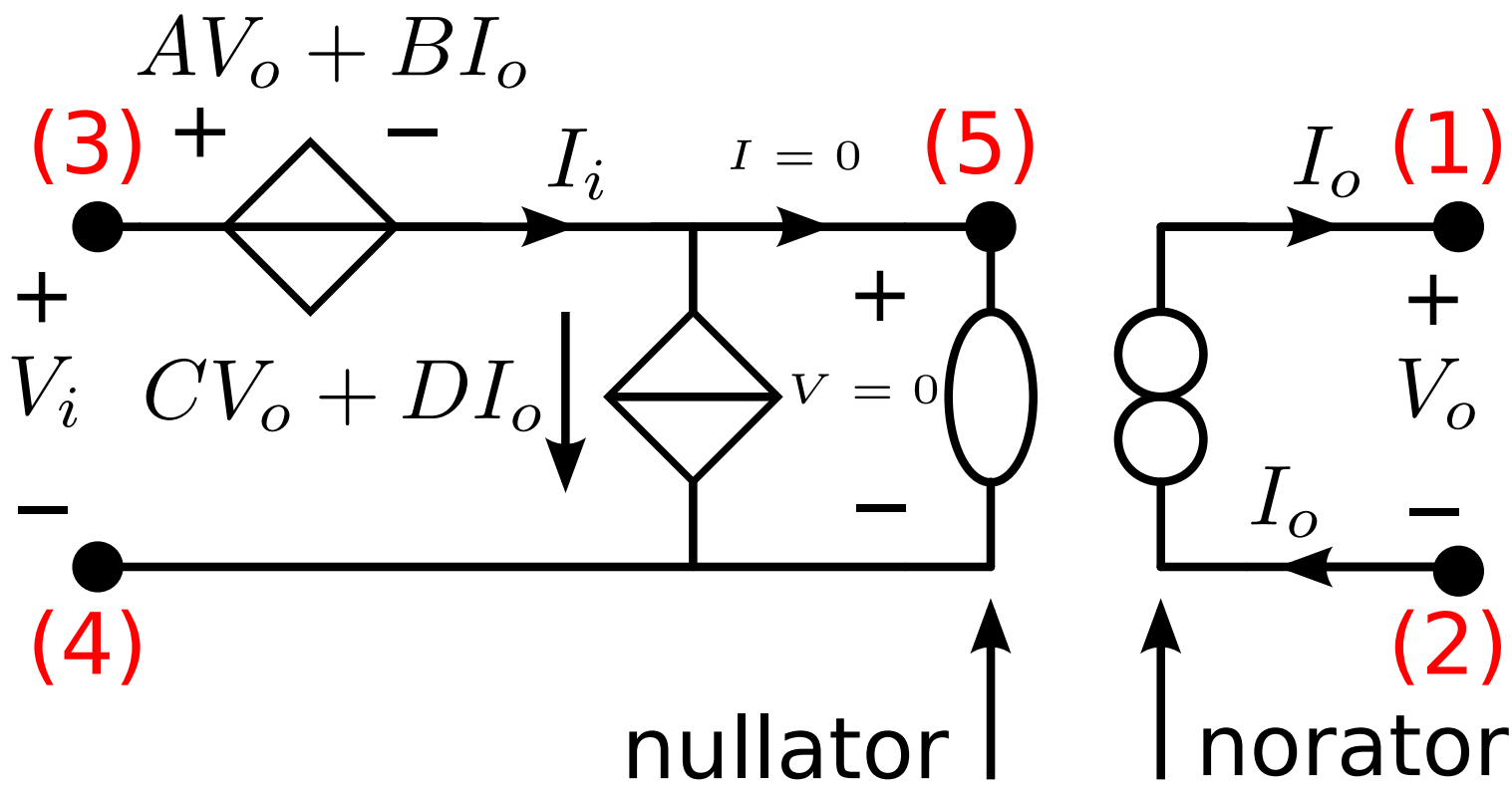

Nullator and norator always in pairs in a network  
See section 18.3.3

Nullator sets network condition  
Norator adds variable

Subcircuit included in SLiCAP: symbol SLABCD in LTspice.

Can only be used with A,B,C,D = Real