Structured Electronic Design

Negative Feedback Amplifiers Ideal Gain and Controller

Anton J.M. Montagne

1. The ideal gain is the source-to-load transfer in the case of a nullor as controller

1. The ideal gain is the source-to-load transfer in the case of a nullor as controller

2. Practical controllers have a finite gain and bandwidth

ne case of a nullor as controller width

- 1. The ideal gain is the source-to-load transfer in the case of a nullor as controller
- 2. Practical controllers have a finite gain and bandwidth
 - a. Negative (corrective) feedback if transfer from the positive output of the controller to its positive input is inverting:

- 1. The ideal gain is the source-to-load transfer in the case of a nullor as controller
- 2. Practical controllers have a finite gain and bandwidth
 - a. Negative (corrective) feedback if transfer from the positive output of the controller to its positive input is inverting:





- 1. The ideal gain is the source-to-load transfer in the case of a nullor as controller
- 2. Practical controllers have a finite gain and bandwidth
 - a. Negative (corrective) feedback if transfer from the positive output of the controller to its positive input is inverting:





- 1. The ideal gain is the source-to-load transfer in the case of a nullor as controller
- 2. Practical controllers have a finite gain and bandwidth
 - a. Negative (corrective) feedback if transfer from the positive output of the controller to its positive input is inverting:



- 1. The ideal gain is the source-to-load transfer in the case of a nullor as controller
- 2. Practical controllers have a finite gain and bandwidth
 - a. Negative (corrective) feedback if transfer from the positive output of the controller to its positive input is inverting:



1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

2. If the feedback network is not a natural two-port: a. Source and load are electrically connected

1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

- a. Source and load are electrically connected
- b. Sign of transfer depends on amplifier type

1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

- a. Source and load are electrically connected
- b. Sign of transfer depends on amplifier type
- c. Port isolation and/or sign inversion requires:

1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

2. If the feedback network is not a natural two-port:

- a. Source and load are electrically connected
- b. Sign of transfer depends on amplifier type
- c. Port isolation and/or sign inversion requires:

- Active feedback

1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

- a. Source and load are electrically connected
- b. Sign of transfer depends on amplifier type
- c. Port isolation and/or sign inversion requires:
 - Active feedback
 - Balanced feedback

1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

- a. Source and load are electrically connected
- b. Sign of transfer depends on amplifier type
- c. Port isolation and/or sign inversion requires:
 - Active feedback
 - Balanced feedback
 - Indirect feedback

1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

- a. Source and load are electrically connected
- b. Sign of transfer depends on amplifier type
- c. Port isolation and/or sign inversion requires:
 - Active feedback
 - Balanced feedback
 - Indirect feedback
 - Transformers

1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

- a. Source and load are electrically connected
- b. Sign of transfer depends on amplifier type
- c. Port isolation and/or sign inversion requires:
 - Active feedback
 - Balanced feedback **Not in BSc course**
- - Indirect feedback
 - Transformers

1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

- a. Source and load are electrically connected
- b. Sign of transfer depends on amplifier type
- c. Port isolation and/or sign inversion requires:
 - Active feedback
 - Balanced feedback 🚽 Not in BSc course 🔀
 - Indirect feedback
 - Transformers



1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

- a. Source and load are electrically connected
- b. Sign of transfer depends on amplifier type
- c. Port isolation and/or sign inversion requires:



1. All port (isolation) configurations can be realized using nonenergic feedback with natural two-ports (gyrator, transformer)

- a. Source and load are electrically connected
- b. Sign of transfer depends on amplifier type
- c. Port isolation and/or sign inversion requires:

