


# **Structured Electronic Design**

Negative Feedback Amplifiers  
Ideal Gain and Controller

*Anton J.M. Montagne*

# Negative feedback and ideal gain

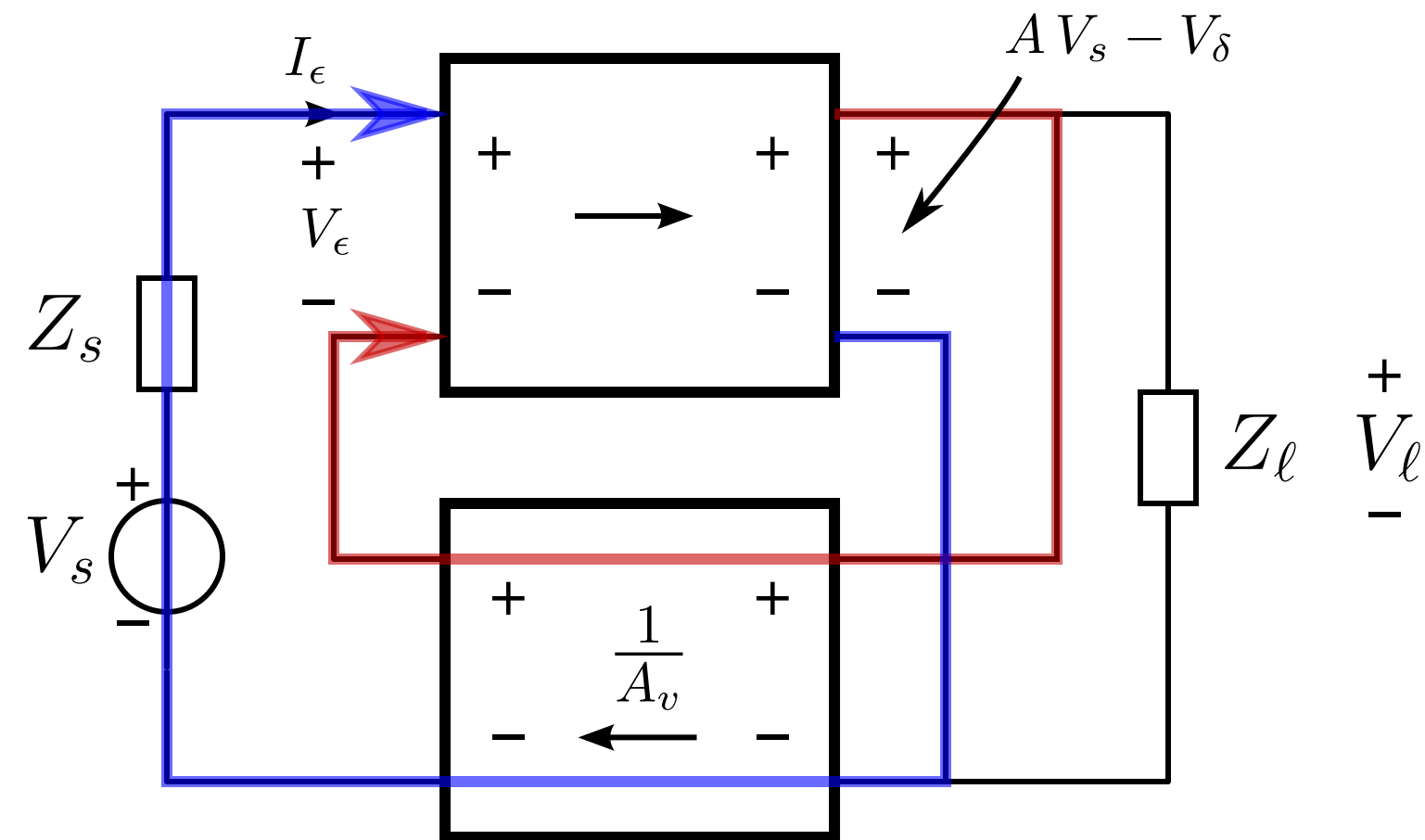1. The ideal gain is the source-to-load transfer in the case of a nullor as controller
2. Practical controllers have a finite gain and bandwidth
  - a. Negative (corrective) feedback if transfer from the positive output of the controller to its positive input is inverting:




# Conclusions single-loop feedback configurations

1. All port (isolation) configurations can be realized using nonenergetic feedback with natural two-ports (gyrator, transformer)
2. If the feedback network is not a natural two-port:
  - a. Source and load are electrically connected
  - b. Sign of transfer depends on amplifier type
  - c. Port isolation and/or sign inversion requires:
    - Active feedback
    - Balanced feedback
    - Indirect feedback
    - Transformers



Read:

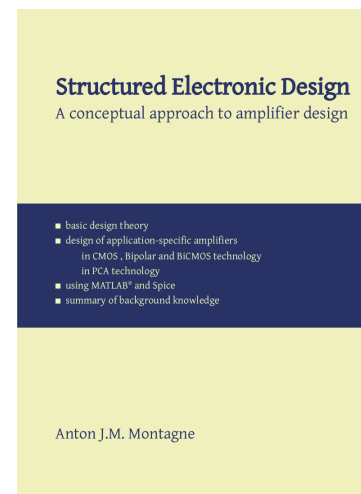

Chapter 7

