

# **Structured Electronic Design**

Design of Multi-loop Negative Feedback Amplifier Configurations

*Anton J.M. Montagne*

# Multiple-loop feedback configurations

# Multiple-loop feedback configurations

1. Each transmission parameter can be fixed to a nonzero value with a single feedback loop

# Multiple-loop feedback configurations

1. Each transmission parameter can be fixed to a nonzero value with a single feedback loop
2. Multiple transmission parameters can be fixed with multiple loops, hence all 15 amplifier types can be realized with negative feedback

# Multiple-loop feedback configurations

1. Each transmission parameter can be fixed to a nonzero value with a single feedback loop
2. Multiple transmission parameters can be fixed with multiple loops, hence all 15 amplifier types can be realized with negative feedback
3. Transmission parameters can be fixed independently if:

# Multiple-loop feedback configurations

1. Each transmission parameter can be fixed to a nonzero value with a single feedback loop
2. Multiple transmission parameters can be fixed with multiple loops, hence all 15 amplifier types can be realized with negative feedback
3. Transmission parameters can be fixed independently if:
  - a. Current through voltage sensing elements equals zero

# Multiple-loop feedback configurations

1. Each transmission parameter can be fixed to a nonzero value with a single feedback loop
2. Multiple transmission parameters can be fixed with multiple loops, hence all 15 amplifier types can be realized with negative feedback
3. Transmission parameters can be fixed independently if:
  - a. Current through voltage sensing elements equals zero
  - b. Voltage across current sensing elements equals zero

# Multiple-loop feedback configurations

1. Each transmission parameter can be fixed to a nonzero value with a single feedback loop
2. Multiple transmission parameters can be fixed with multiple loops, hence all 15 amplifier types can be realized with negative feedback
3. Transmission parameters can be fixed independently if:
  - a. Current through voltage sensing elements equals zero
  - b. Voltage across current sensing elements equals zero
  - c. Output impedance of feedback network is ideal

# Multiple-loop feedback configurations

1. Each transmission parameter can be fixed to a nonzero value with a single feedback loop
2. Multiple transmission parameters can be fixed with multiple loops, hence all 15 amplifier types can be realized with negative feedback
3. Transmission parameters can be fixed independently if:
  - a. Current through voltage sensing elements equals zero
  - b. Voltage across current sensing elements equals zero
  - c. Output impedance of feedback network is ideal
    - Zero in case of voltage comparison

# Multiple-loop feedback configurations


1. Each transmission parameter can be fixed to a nonzero value with a single feedback loop
2. Multiple transmission parameters can be fixed with multiple loops, hence all 15 amplifier types can be realized with negative feedback
3. Transmission parameters can be fixed independently if:
  - a. Current through voltage sensing elements equals zero
  - b. Voltage across current sensing elements equals zero
  - c. Output impedance of feedback network is ideal
    - Zero in case of voltage comparison
    - Infinite in case of current comparison

# Multiple-loop feedback configurations


1. Each transmission parameter can be fixed to a nonzero value with a single feedback loop
2. Multiple transmission parameters can be fixed with multiple loops, hence all 15 amplifier types can be realized with negative feedback
3. Transmission parameters can be fixed independently if:
  - a. Current through voltage sensing elements equals zero
  - b. Voltage across current sensing elements equals zero
  - c. Output impedance of feedback network is ideal
    - Zero in case of voltage comparison
    - Infinite in case of current comparison

# Quadruple-loop feedback configuration


# Quadruple-loop feedback configuration

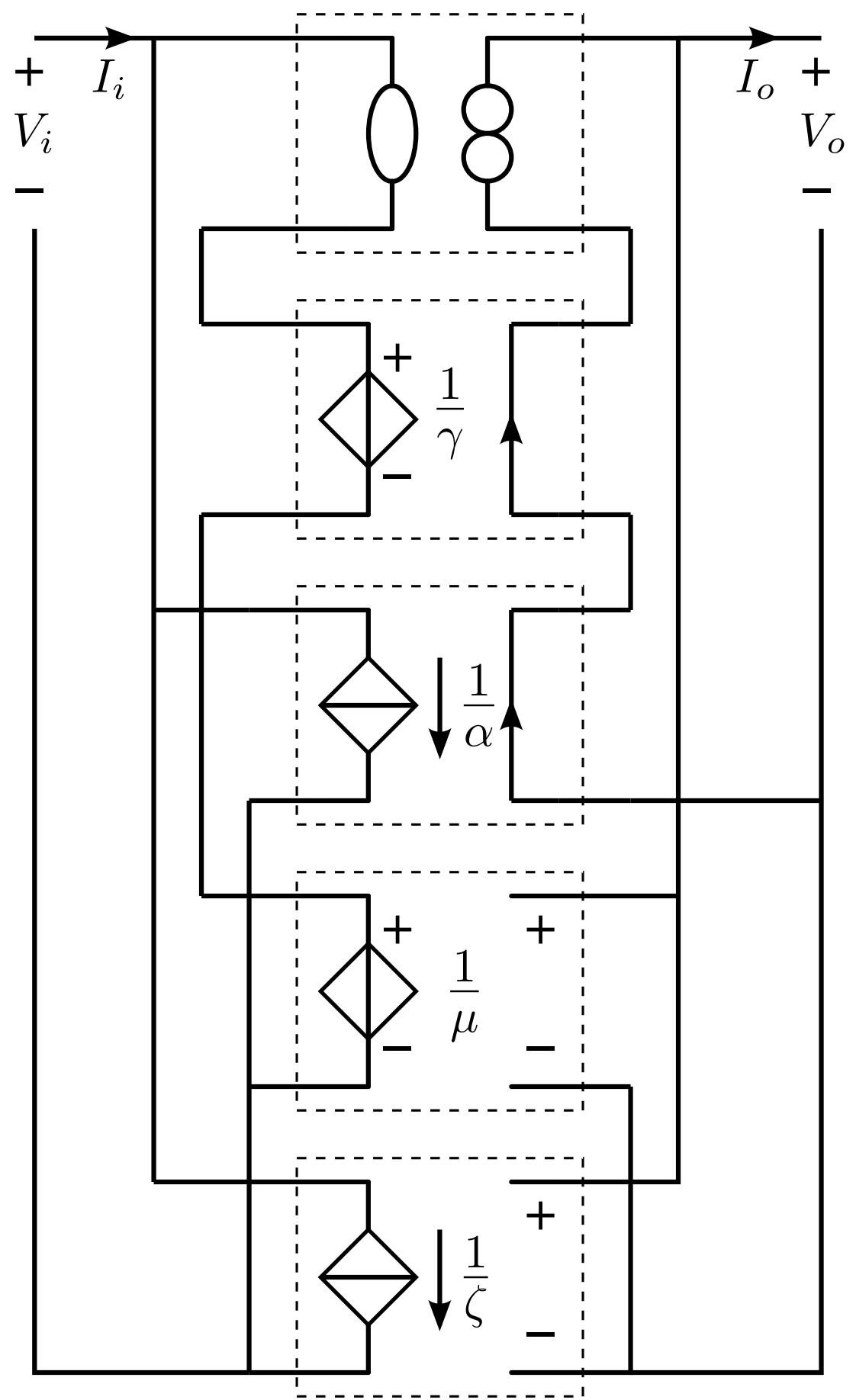


# Quadruple-loop feedback configuration

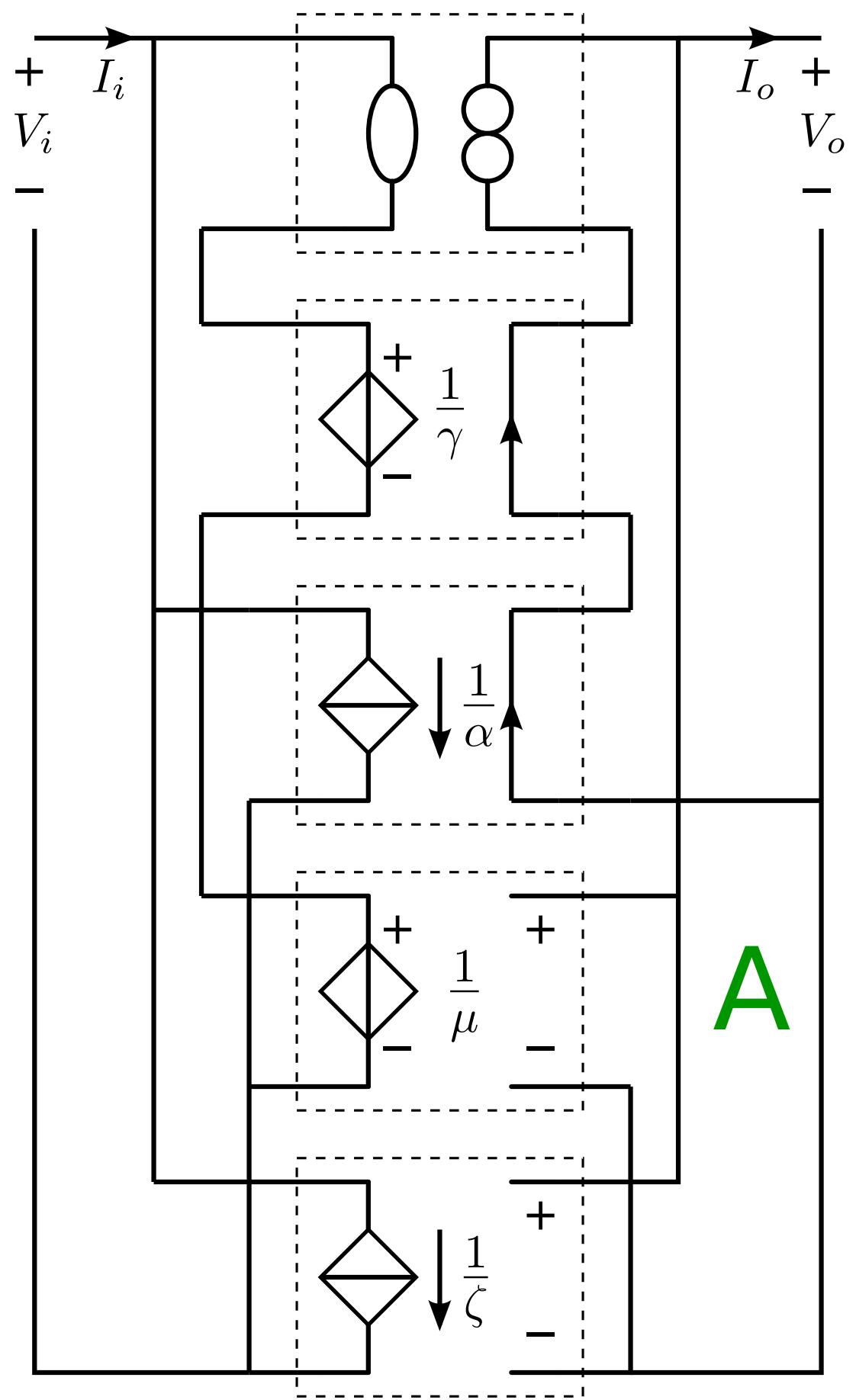


# Quadruple-loop feedback configuration

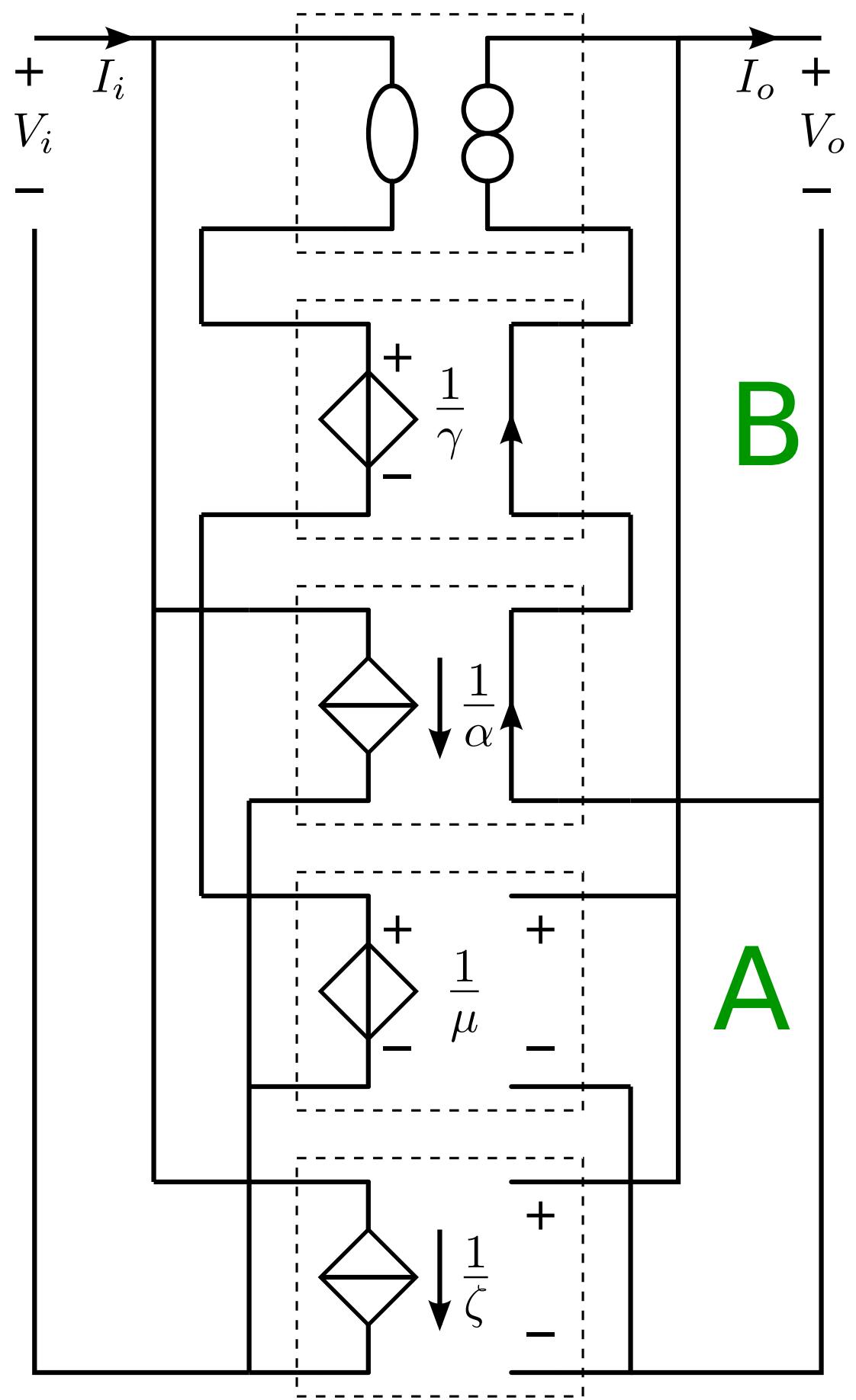


# Quadruple-loop feedback configuration

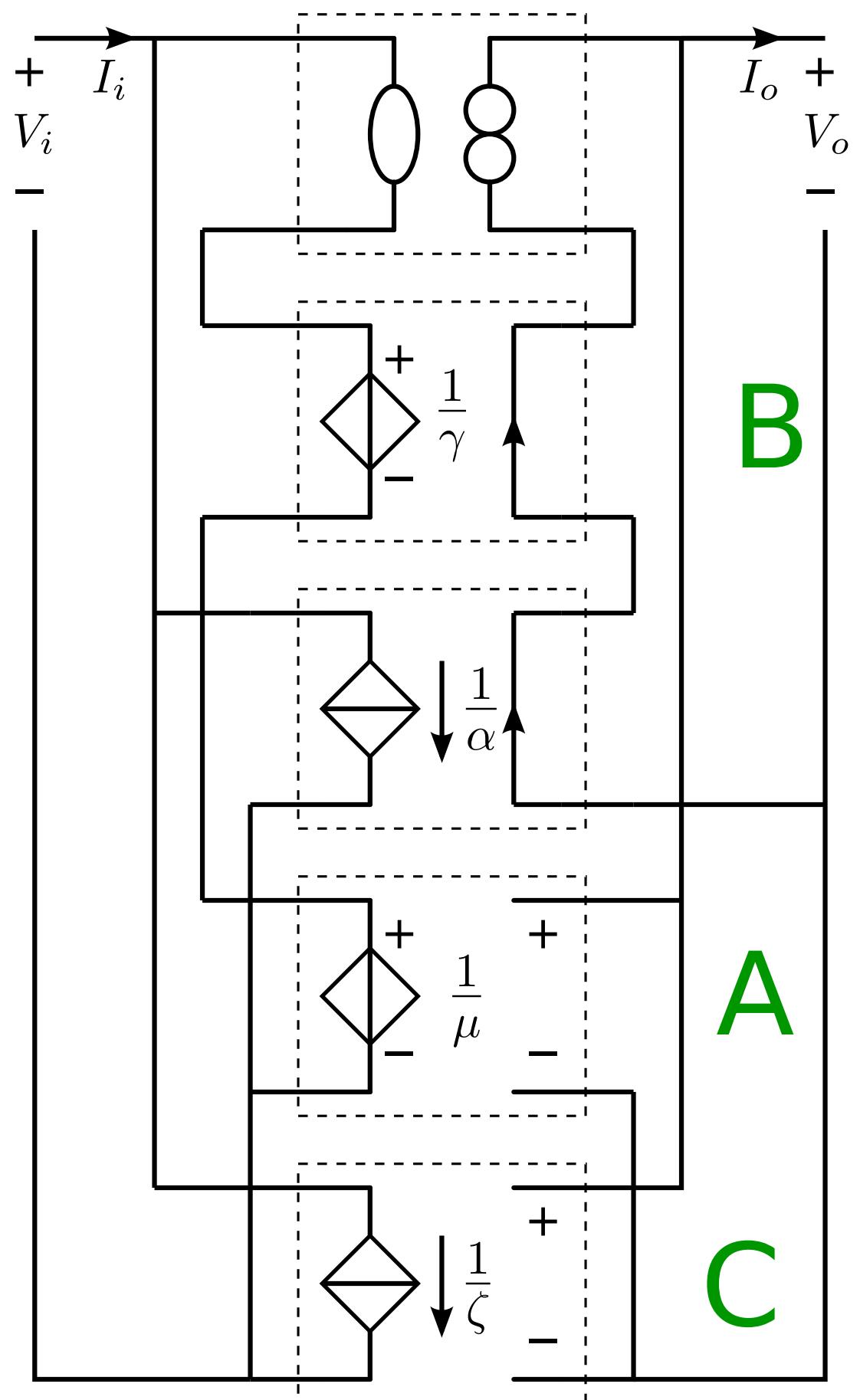

# Quadruple-loop feedback configuration

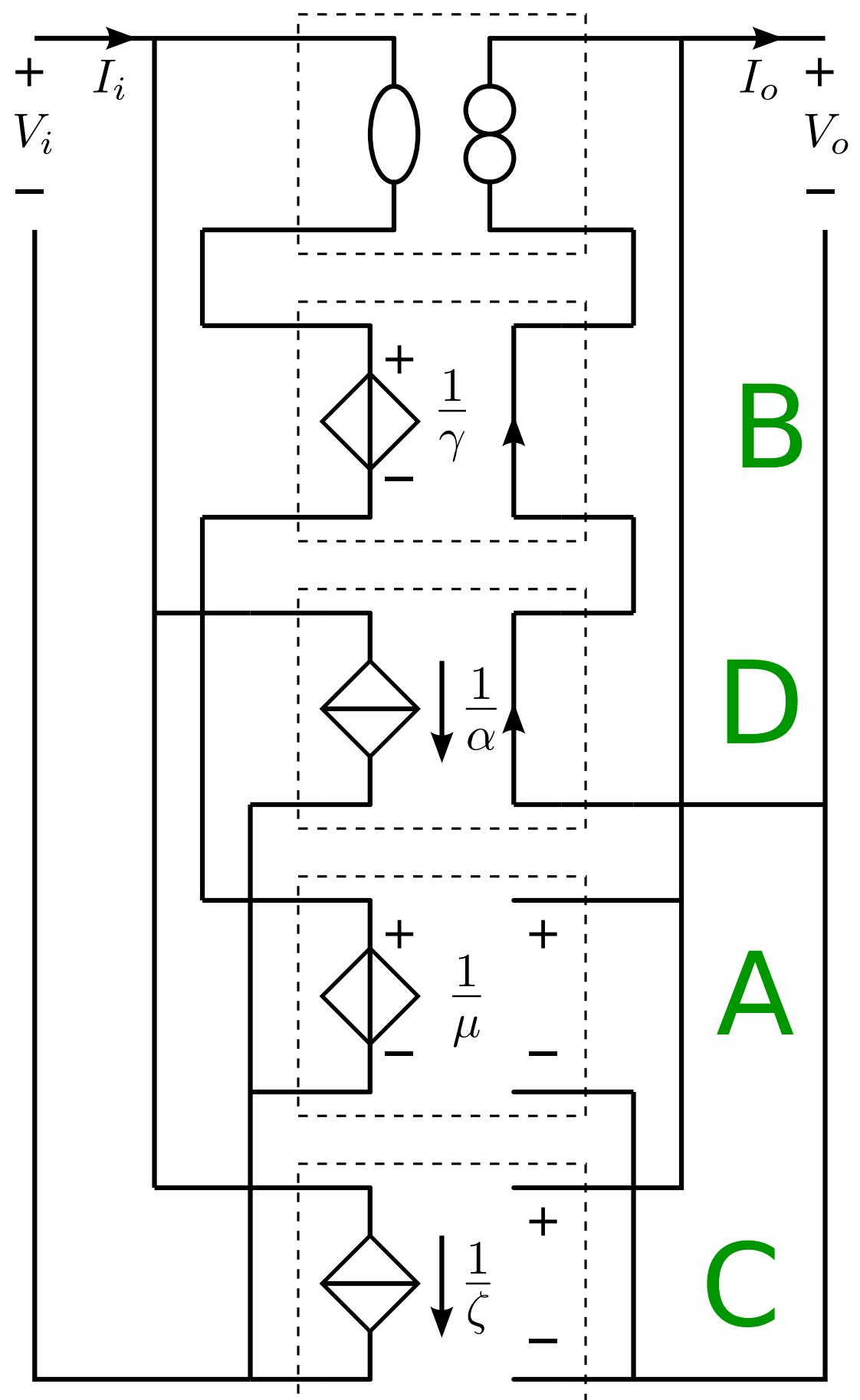

# Quadruple-loop feedback configuration

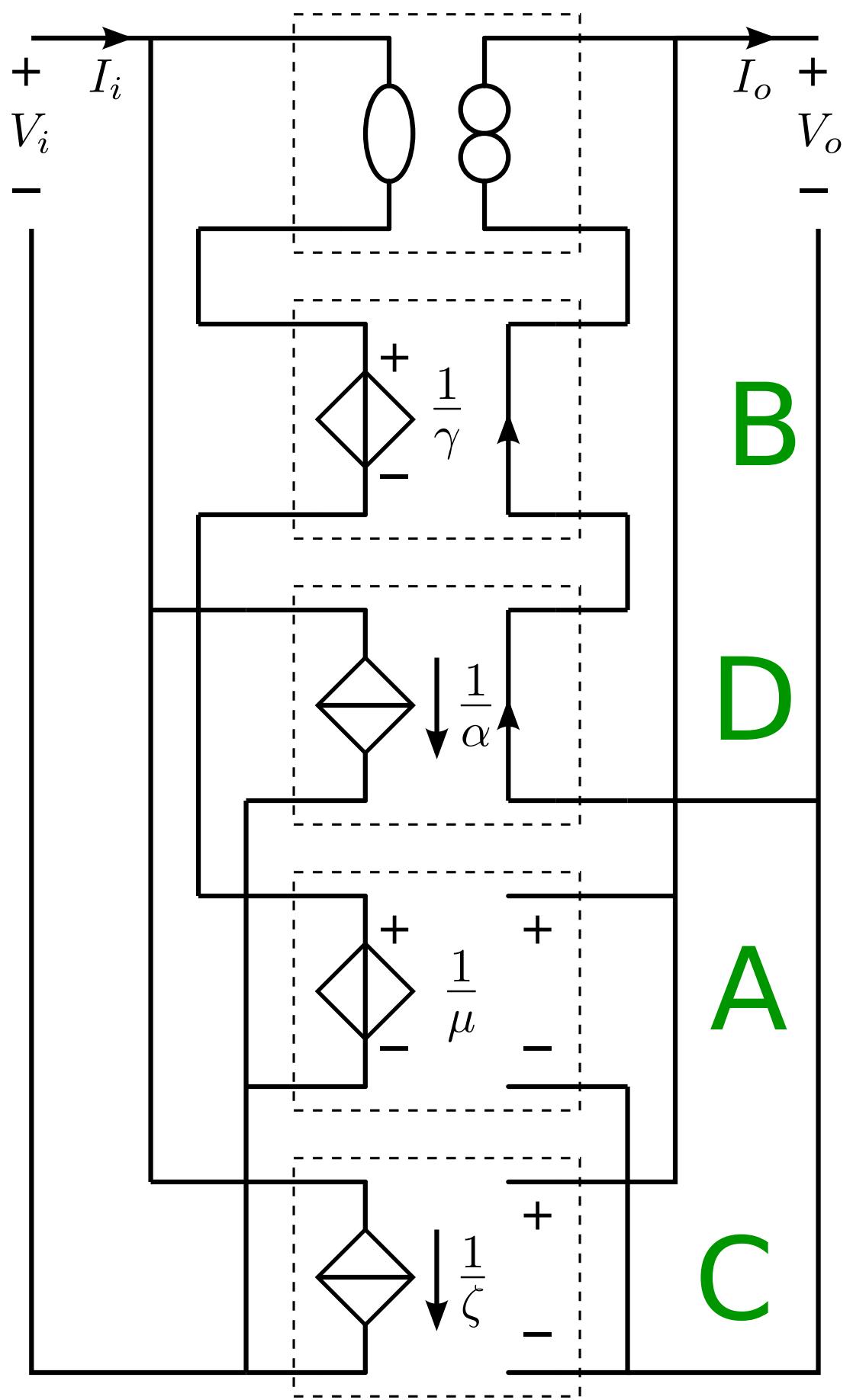

Multiple-loop not in BSc course