Structured Electronic Design

EE3C11 Amplifiers: modeling nonideal port isolation Anton J.M. Montagne

George P. Box (1987): all models are wrong, but some are useful

George P. Box (1987): all models are wrong, but some are useful

Two-port model



George P. Box (1987): all models are wrong, but some are useful

Two-port model



Useful functional model with two independent and two dependent variables

George P. Box (1987): all models are wrong, but some are useful

Two-port model

Complete network model



Useful functional model with two independent and two dependent variables



George P. Box (1987): all models are wrong, but some are useful

Two-port model

Complete network model



Useful functional model with two independent and two dependent variables



Complete network description with three dependent and three independent variables

George P. Box (1987): all models are wrong, but some are useful

Two-port model

Complete network model



Useful functional model with two independent and two dependent variables



Complete network description with three dependent and three independent variables

Commonly used description methods are incomplete:

Commonly used description methods are incomplete:



Commonly used description methods are incomplete:



6 nodes (incl. reference node)

Commonly used description methods are incomplete:



6 nodes (incl. reference node) 5 independent and 5 dependent variables

Commonly used description methods are incomplete:



6 nodes (incl. reference node)

5 independent and 5 dependent variables

Commonly used description methods are incomplete:

Four two-port matrix coefficients



6 nodes (incl. reference node)

5 independent and 5 dependent variables

Commonly used description methods are incomplete:

Four two-port matrix coefficients

Common-mode input impedance (floating input port)



6 nodes (incl. reference node)

5 independent and 5 dependent variables

Commonly used description methods are incomplete:

Four two-port matrix coefficients

Common-mode input impedance (floating input port)

Common-mode (voltage) rejection ratio



6 nodes (incl. reference node)

5 independent and 5 dependent variables

Commonly used description methods are incomplete:

Four two-port matrix coefficients

Common-mode input impedance (floating input port)

Common-mode (voltage) rejection ratio

Common-mode (voltage) gain (floating input port and floating output port)



6 nodes (incl. reference node)

5 independent and 5 dependent variables

Commonly used description methods are incomplete:

Four two-port matrix coefficients

Common-mode input impedance (floating input port)

Common-mode (voltage) rejection ratio

Common-mode (voltage) gain (floating input port and floating output port)

Common-mode (voltage) rejection factor (floating input port and floating output port)



6 nodes (incl. reference node)

5 independent and 5 dependent variables

Commonly used description methods are incomplete:

Four two-port matrix coefficients

Common-mode input impedance (floating input port)

Common-mode (voltage) rejection ratio

Common-mode (voltage) gain (floating input port and floating output port)

Common-mode (voltage) rejection factor (floating input port and floating output port)

Power supply rejection ratio (voltage)



6 nodes (incl. reference node)

5 independent and 5 dependent variables

Commonly used description methods are incomplete:

Four two-port matrix coefficients

Common-mode input impedance (floating input port)

Common-mode (voltage) rejection ratio

Common-mode (voltage) gain (floating input port and floating output port)

Common-mode (voltage) rejection factor (floating input port and floating output port)

Power supply rejection ratio (voltage)

Network theory: section 18.6.1



6 nodes (incl. reference node)

5 independent and 5 dependent variables

Commonly used description methods are incomplete:

Four two-port matrix coefficients

Common-mode input impedance (floating input port)

Common-mode (voltage) rejection ratio

Common-mode (voltage) gain (floating input port and floating output port)

Common-mode (voltage) rejection factor (floating input port and floating output port)

Power supply rejection ratio (voltage)

Network theory: section 18.6.1 Specification of amplifiers: sections 2.4.1 and 2.4.1



6 nodes (incl. reference node)

5 independent and 5 dependent variables

Commonly used description methods are incomplete:

Four two-port matrix coefficients

Common-mode input impedance (floating input port)

Common-mode (voltage) rejection ratio

Common-mode (voltage) gain (floating input port and floating output port)

Common-mode (voltage) rejection factor (floating input port and floating output port)

Power supply rejection ratio (voltage)

Network theory: section 18.6.1 Specification of amplifiers: sections 2.4.1 and 2.4.1



6 nodes (incl. reference node)

5 independent and 5 dependent variables