Structured Electronic Design Principle of amplification





Modulation of power transfer from power source to the load by the signal source



Modulation mechanism found in some passive elements

Modulation of power transfer from power source to the load by the signal source



Modulation mechanism found in some passive elements











1. Find an operating mechanism that provides an available power gain > 1

1. Find an operating mechanism that provides an available power gain > 1

a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point

1. Find an operating mechanism that provides an available power gain > 1

- a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
- b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

1. Find an operating mechanism that provides an available power gain > 1

- a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
- b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

AD = BC

1. Find an operating mechanism that provides an available power gain > 1

- a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
- b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

$$AD = BC \qquad \frac{1}{4AD} > 1$$

- 1. Find an operating mechanism that provides an available power gain > 1
 - a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
 - b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

$$AD = BC \qquad \frac{1}{4AD} > 1$$

2. Study performance versus costs of basic solution

- 1. Find an operating mechanism that provides an available power gain > 1
 - a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
 - b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

$$AD = BC \qquad \frac{1}{4AD} > 1$$

2. Study performance versus costs of basic solution Biased single-device (transistor) amplifier stage suffers from:

- 1. Find an operating mechanism that provides an available power gain > 1
 - a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
 - b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

$$AD = BC \qquad \frac{1}{4AD} > 1$$

2. Study performance versus costs of basic solution Biased single-device (transistor) amplifier stage suffers from: - noise addition

- 1. Find an operating mechanism that provides an available power gain > 1
 - a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
 - b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

$$AD = BC \qquad \frac{1}{4AD} > 1$$

2. Study performance versus costs of basic solution

- noise addition
- inaccuracy

- 1. Find an operating mechanism that provides an available power gain > 1
 - a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
 - b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

$$AD = BC \qquad \frac{1}{4AD} > 1$$

2. Study performance versus costs of basic solution

- noise addition
- inaccuracy
- nonlinearity

1. Find an operating mechanism that provides an available power gain > 1

- a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
- b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

$$AD = BC \qquad \frac{1}{4AD} > 1$$

2. Study performance versus costs of basic solution

- noise addition
- inaccuracy
- nonlinearity
- bandwidth limitation

1. Find an operating mechanism that provides an available power gain > 1

- a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
- b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

$$AD = BC \qquad \frac{1}{4AD} > 1$$

2. Study performance versus costs of basic solution

- noise addition
- inaccuracy
- nonlinearity
- bandwidth limitation
- device tolerances

1. Find an operating mechanism that provides an available power gain > 1

- a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
- b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

$$AD = BC \qquad \frac{1}{4AD} > 1$$

2. Study performance versus costs of basic solution

- noise addition
- inaccuracy
- nonlinearity
- bandwidth limitation
- device tolerances
- temperature dependency

1. Find an operating mechanism that provides an available power gain > 1

- a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
- b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

$$AD = BC \qquad \frac{1}{4AD} > 1$$

2. Study performance versus costs of basic solution

Biased single-device (transistor) amplifier stage suffers from:

- noise addition
- inaccuracy
- nonlinearity
- bandwidth limitation
- device tolerances
- temperature dependency

3. Apply error-reduction techniques for improvement of performance-to-costs ratio

1. Find an operating mechanism that provides an available power gain > 1

- a. Biased passive two-terminal devices: Negative small-signal resistance in the operating point
- b. Biased passive three-terminal or four-terminal devices: Unilateral transfer with available power gain in operating point exceeding unity:

$$AD = BC \qquad \frac{1}{4AD} > 1$$

2. Study performance versus costs of basic solution

Biased single-device (transistor) amplifier stage suffers from:

- noise addition
- inaccuracy
- nonlinearity
- bandwidth limitation
- device tolerances
- temperature dependency

3. Apply error-reduction techniques for improvement of performance-to-costs ratio