

# **Structured Electronic Design**

Design of Single-loop Negative Feedback Amplifier Configurations


*Anton J.M. Montagne*

# Negative Feedback Amplifier Configurations

Source type	Load type	Amplifier type	A, B, C, D	Feedback configuration
V	V	Voltage amplifier	A, 0, 0, 0	Output voltage sensing / parallel feedback
				Input voltage comparison / series feedback
V	I	Transadmittance	0, B, 0, 0	Output current sensing / series feedback
				Input voltage comparison / series feedback
I	V	Transimpedance	0, 0, C, 0	Output voltage sensing / parallel feedback
				Input current comparison / parallel feedback
I	I	Current amplifier	0, 0, 0, D	Output current sensing / series feedback
				Input current comparison / parallel feedback


# Negative Feedback Voltage Amplifier Configurations

$$\frac{V_\ell}{V_s} = n$$

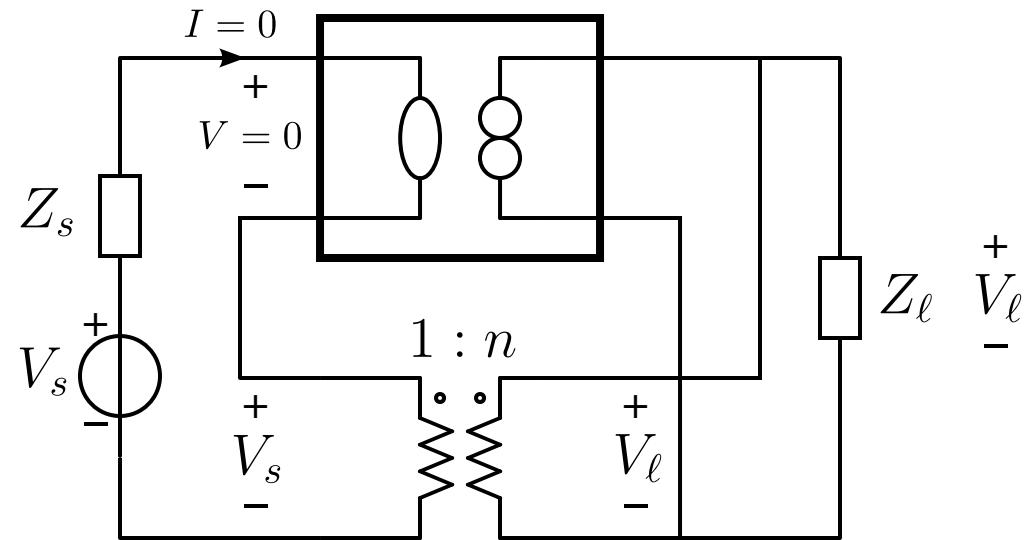

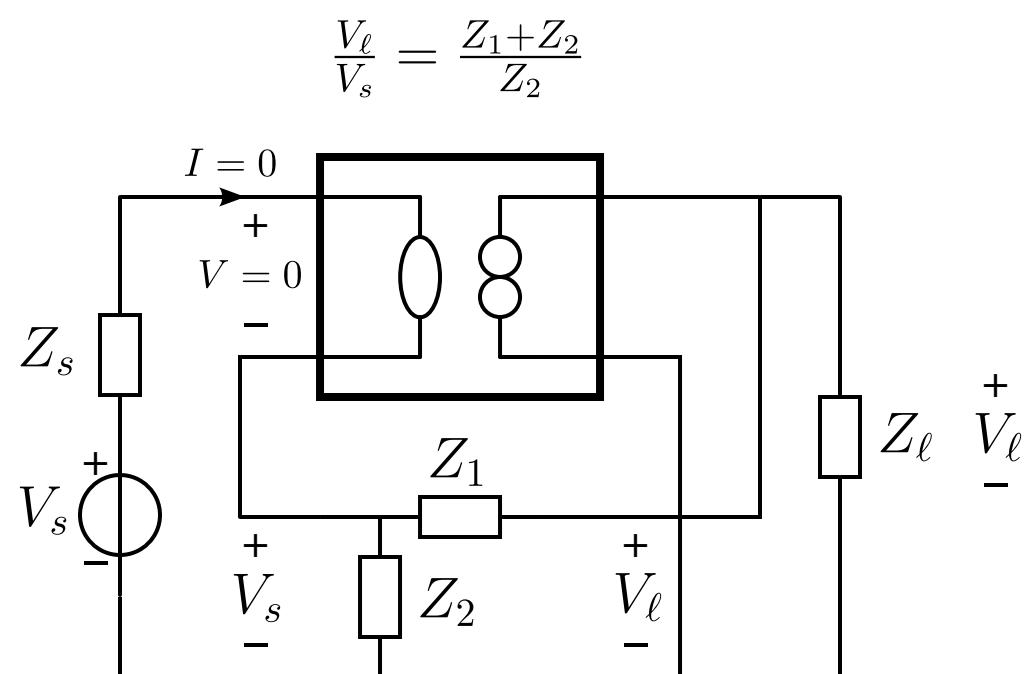
## Nonenergic feedback amplifier

- port isolation
- inverting or noninverting
- gain less, equal or larger than unity


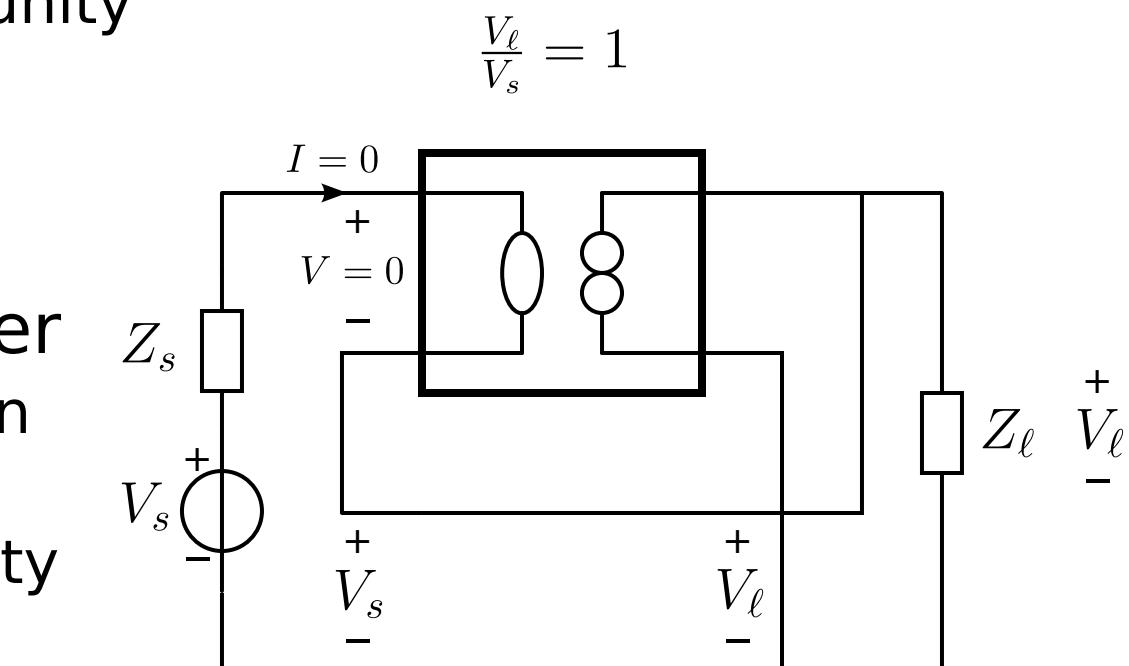
## Nonenergic feedback follower

- no port isolation
- noninverting
- gain equals unity




## Passive feedback amplifier

- no port isolation
- noninverting
- gain larger than unity

# Negative Feedback Transadmittance Configurations


$$\frac{I_\ell}{V_s} = \frac{1}{R}$$

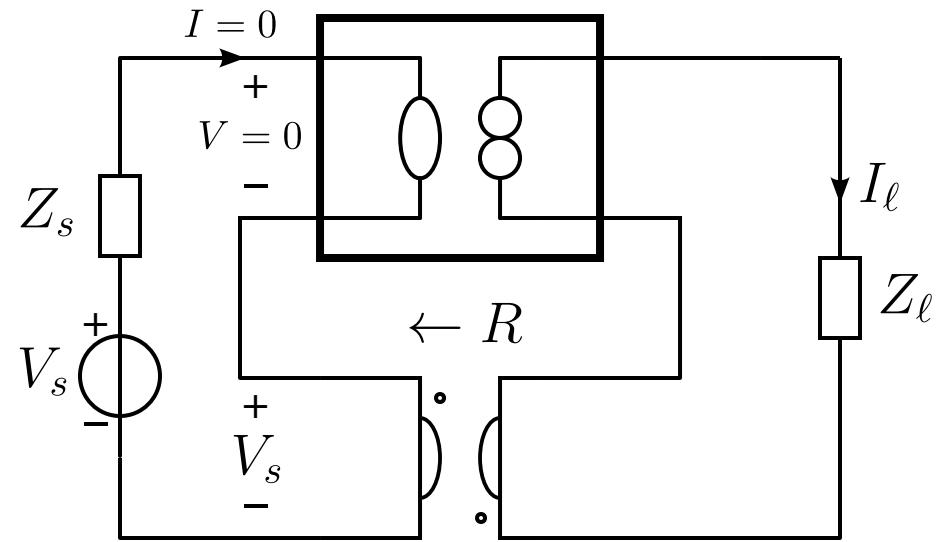

**Nonenergetic feedback amplifier**

- port isolation
- inverting or noninverting

$$\frac{I_\ell}{V_s} = -\frac{1}{Z}$$

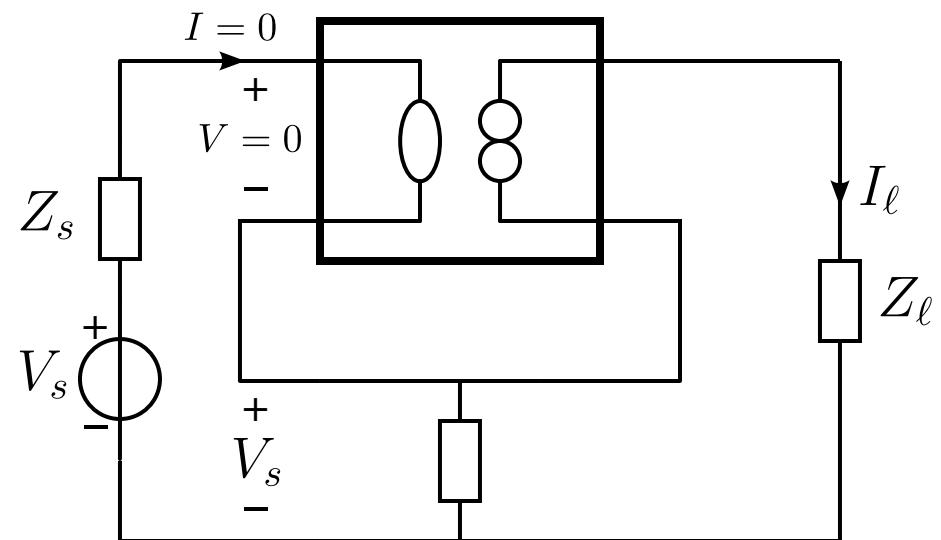


**Passive feedback amplifier**

- no port isolation
- inverting

# Negative Feedback Transimpedance Configurations


$$\frac{V_\ell}{I_s} = \frac{1}{G}$$

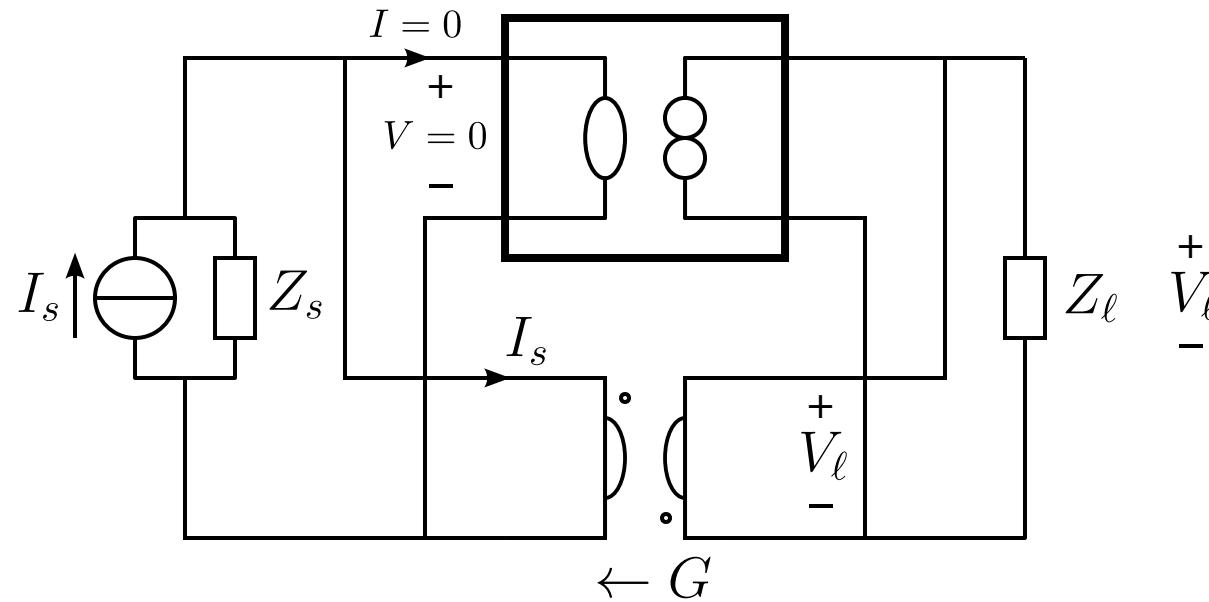

**Nonenergetic feedback amplifier**

- port isolation
- inverting or noninverting

$$\frac{V_\ell}{I_s} = -Z$$

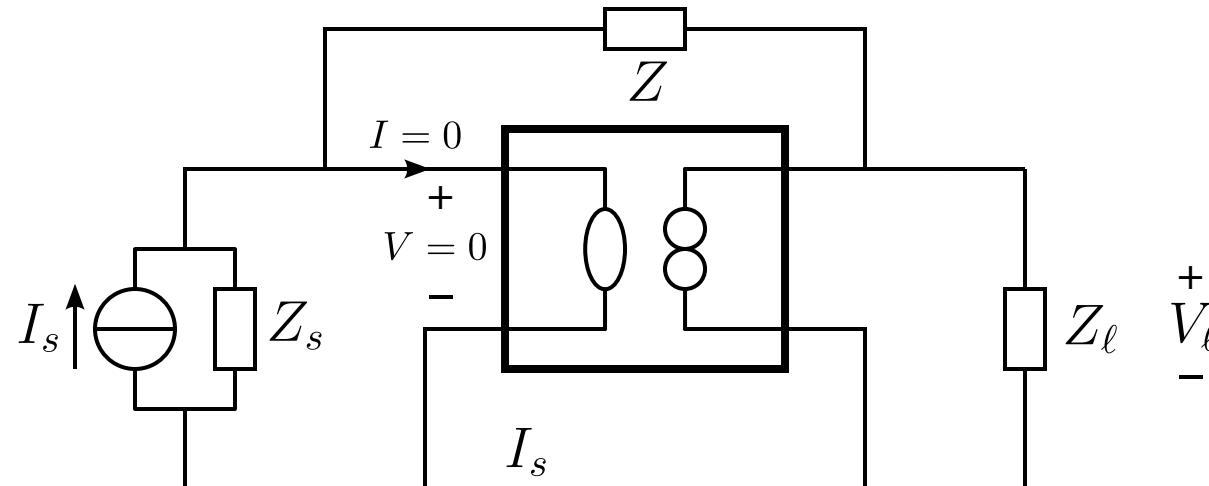


**Passive feedback amplifier**

- no port isolation
- inverting

# Negative Feedback Current Amplifier Configurations


$$\frac{I_\ell}{I_s} = n$$

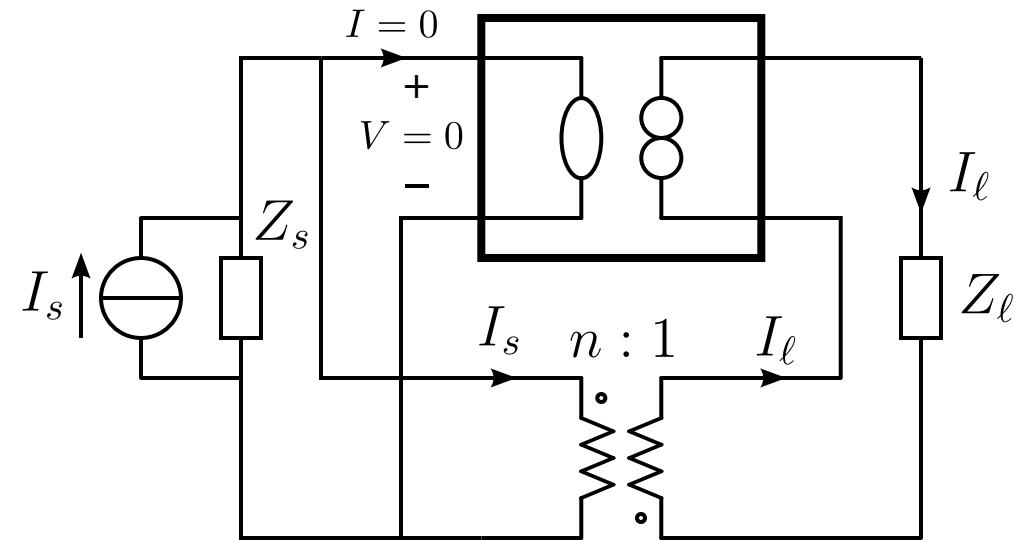

## Nonenergetic feedback amplifier


- port isolation
- inverting or noninverting
- gain less, equal or larger than unity

$$\frac{I_\ell}{I_s} = 1$$

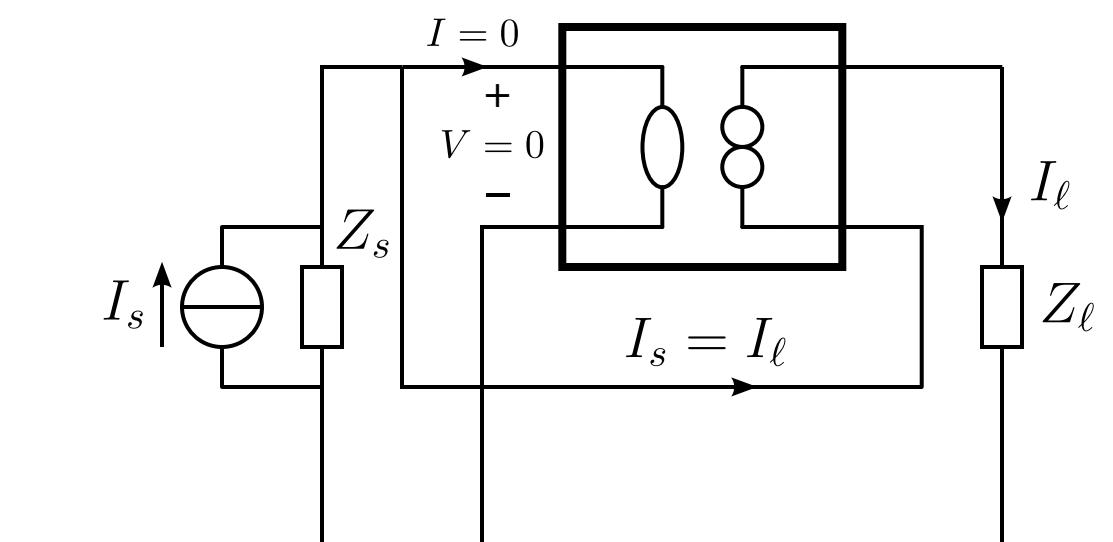
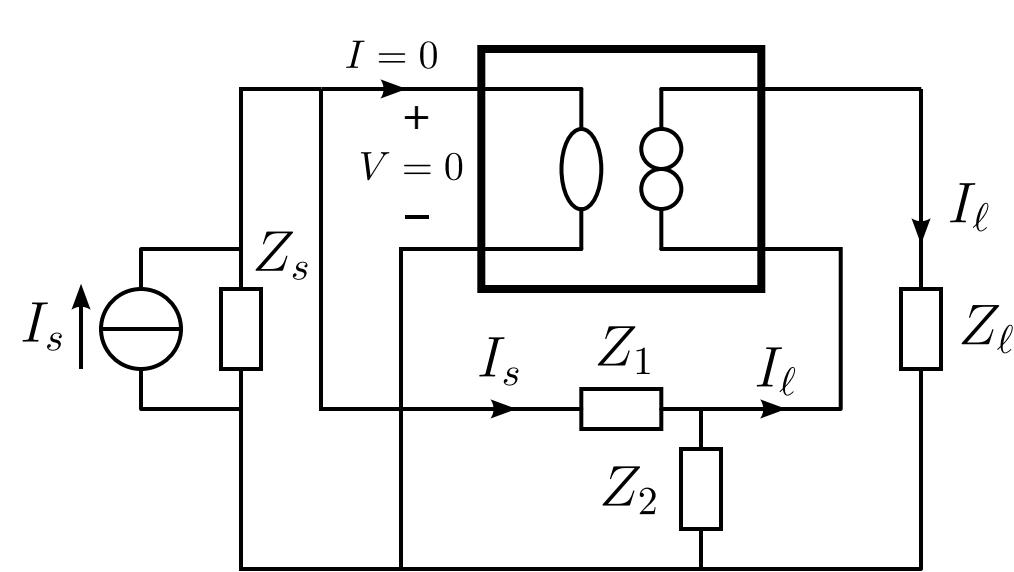
## Nonenergetic feedback follower

- no port isolation
- noninverting
- gain equals unity



## Passive feedback amplifier

- no port isolation
- noninverting
- gain larger than unity