

# **Structured Electronic Design**

EE3C11

Amplifiers: voltage and current drive capability

*Anton J.M. Montagne*

# Static (DC) voltage and current drive capability

# Static (DC) voltage and current drive capability

Signal excursions limited by:

# Static (DC) voltage and current drive capability

Signal excursions limited by

Power supply voltages

# Static (DC) voltage and current drive capability

Signal excursions limited by

Power supply voltages

Breakdown mechanism

# Static (DC) voltage and current drive capability

Signal excursions limited by

Power supply voltages

Breakdown mechanism

Circuit protection mechanism


# Static (DC) voltage and current drive capability

Signal excursions limited by

Power supply voltages

Breakdown mechanism

Circuit protection mechanism

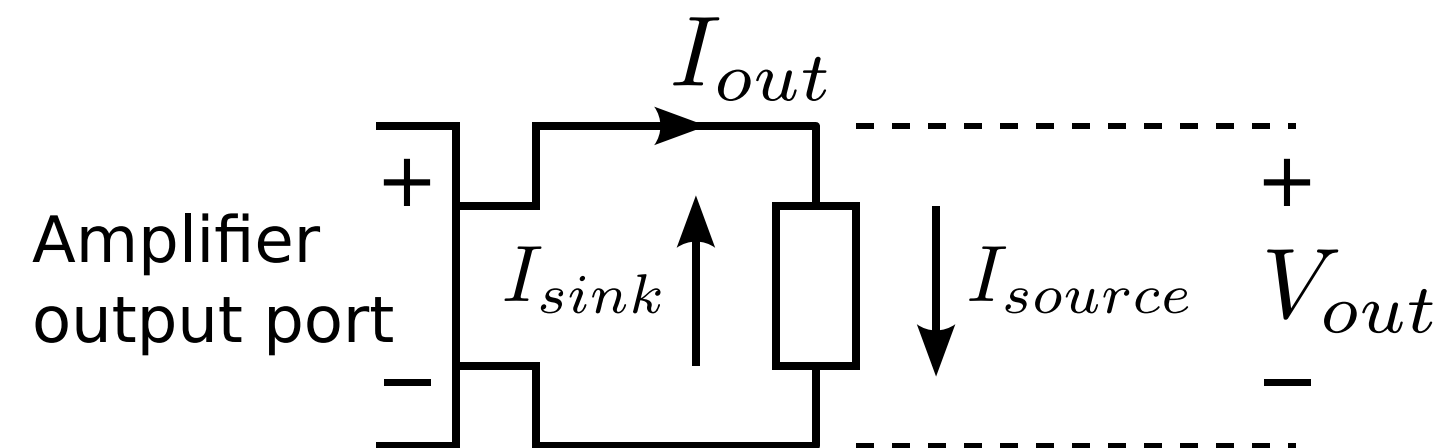



# Static (DC) voltage and current drive capability

Signal excursions limited by

Power supply voltages

Breakdown mechanism

Circuit protection mechanism

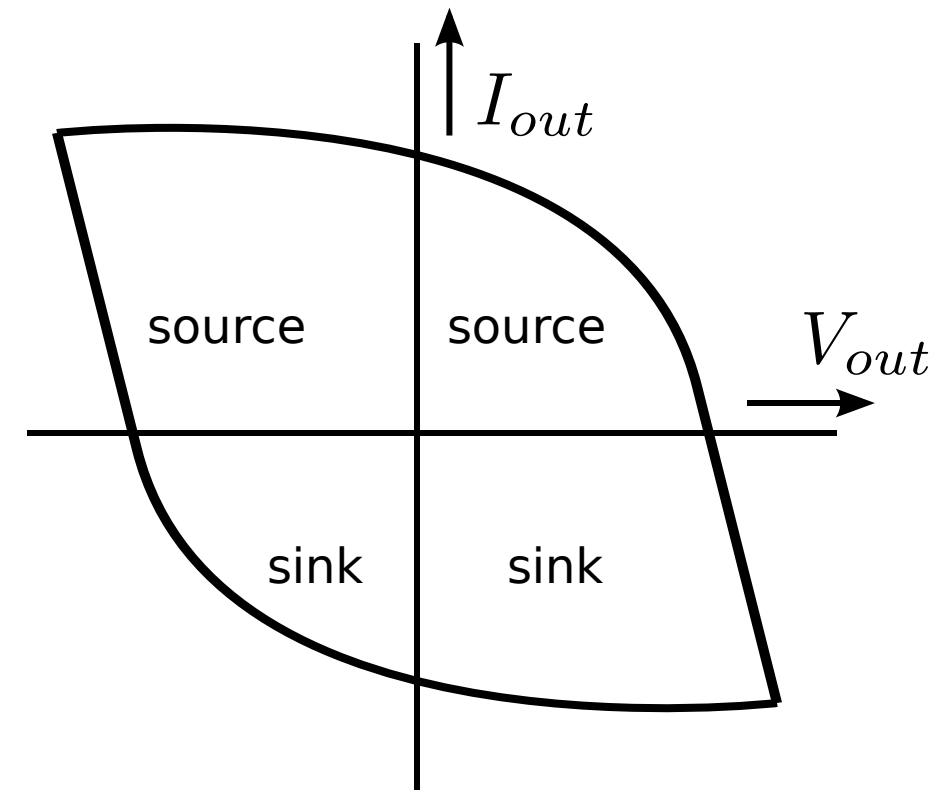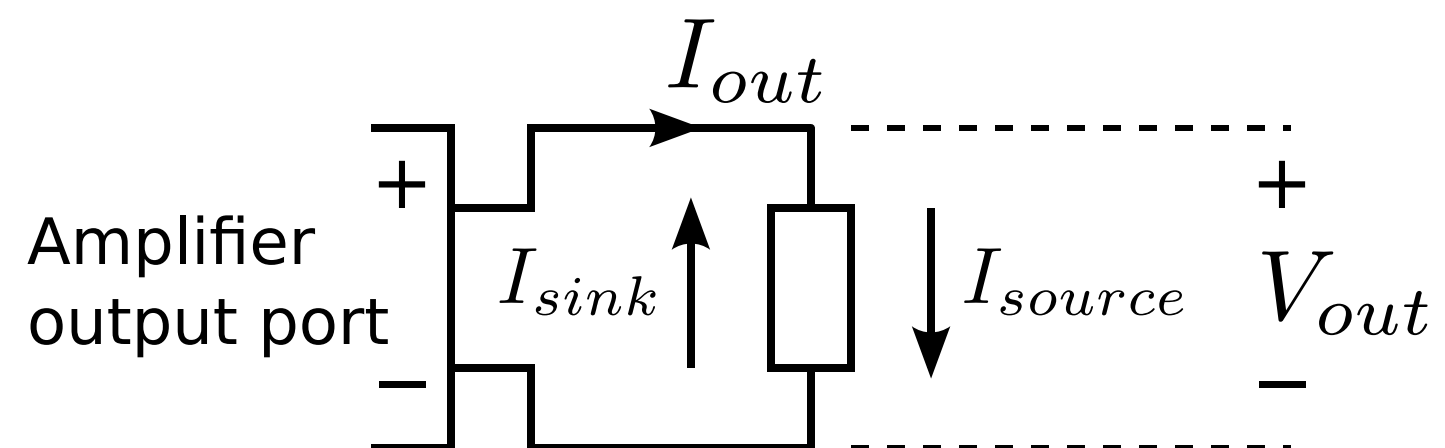



# Dynamic voltage and current drive capability

# Dynamic voltage and current drive capability


Limitation of the rate of change of the signal

# Dynamic voltage and current drive capability

Limitation of the rate of change of the signal

Signal current limitation and  
capacitance in parallel with the signal path

$$\left. \frac{dV}{dt} \right|_{\max} = \frac{I_{\max}}{C}$$

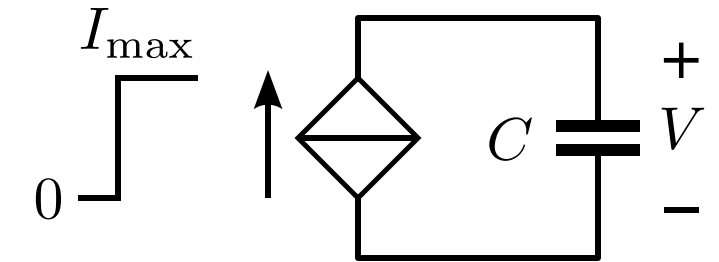


# Dynamic voltage and current drive capability

## Limitation of the rate of change of the signal


Signal current limitation and capacitance in parallel with the signal path

$$\left. \frac{dV}{dt} \right|_{\max} = \frac{I_{\max}}{C}$$

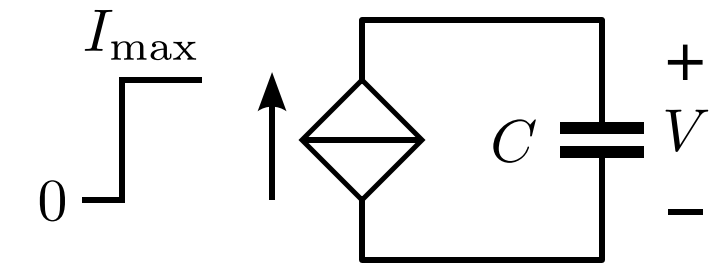

Signal voltage limitation and inductance in series with the signal path

$$\left. \frac{dI}{dt} \right|_{\max} = \frac{V_{\max}}{L}$$

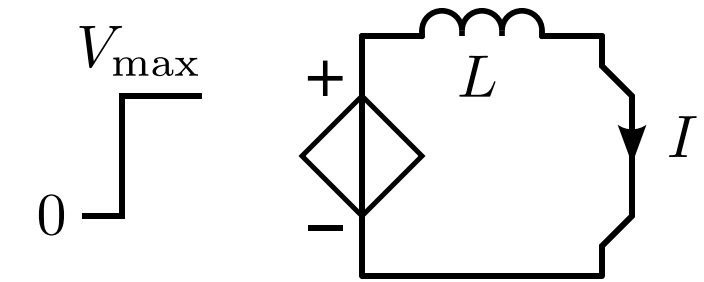


# Dynamic voltage and current drive capability

## Limitation of the rate of change of the signal


Signal current limitation and capacitance in parallel with the signal path

$$\left. \frac{dV}{dt} \right|_{\max} = \frac{I_{\max}}{C}$$

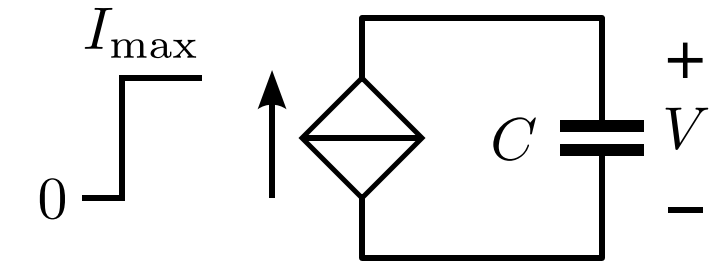

Signal voltage limitation and inductance in series with the signal path

$$\left. \frac{dI}{dt} \right|_{\max} = \frac{V_{\max}}{L}$$

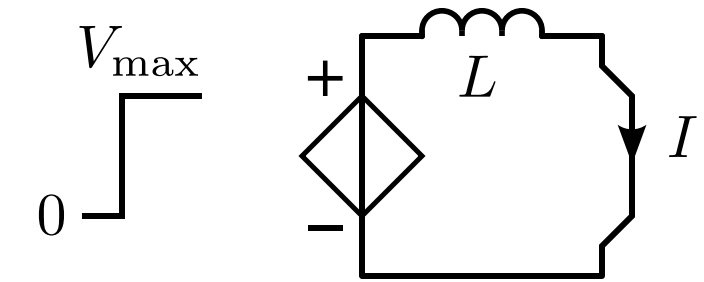


## Limitation of the full-power bandwidth

# Dynamic voltage and current drive capability

## Limitation of the rate of change of the signal


Signal current limitation and capacitance in parallel with the signal path

$$\left. \frac{dV}{dt} \right|_{\max} = \frac{I_{\max}}{C}$$

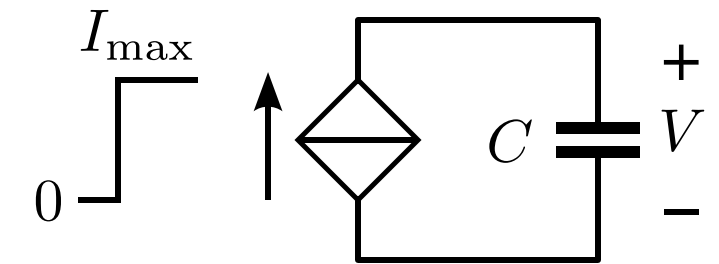

Signal voltage limitation and inductance in series with the signal path

$$\left. \frac{dI}{dt} \right|_{\max} = \frac{V_{\max}}{L}$$

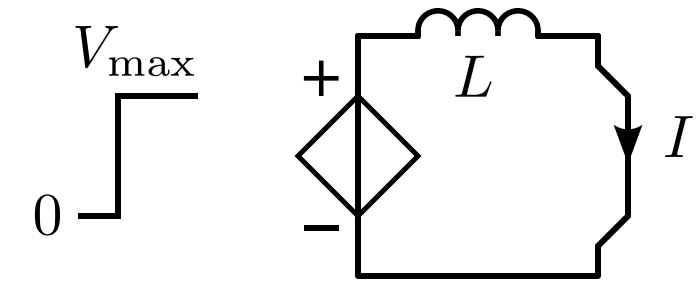

## Limitation of the full-power bandwidth


Maximum frequency of a sinusoidal signal of which:

# Dynamic voltage and current drive capability

## Limitation of the rate of change of the signal


Signal current limitation and capacitance in parallel with the signal path

$$\left. \frac{dV}{dt} \right|_{\max} = \frac{I_{\max}}{C}$$

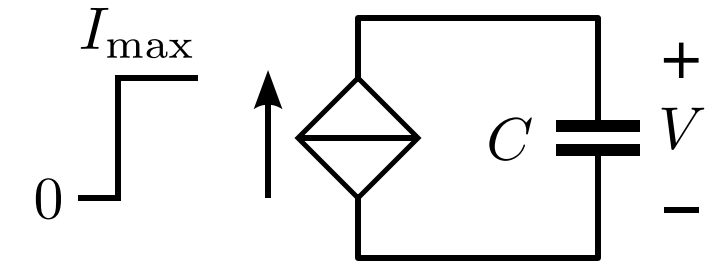

Signal voltage limitation and inductance in series with the signal path

$$\left. \frac{dI}{dt} \right|_{\max} = \frac{V_{\max}}{L}$$

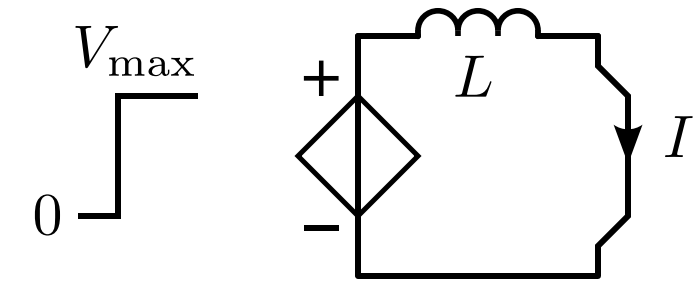

## Limitation of the full-power bandwidth

Maximum frequency of a sinusoidal signal of which:


peak-to-peak value equals maximum static signal swing

# Dynamic voltage and current drive capability

## Limitation of the rate of change of the signal


Signal current limitation and capacitance in parallel with the signal path

$$\left. \frac{dV}{dt} \right|_{\max} = \frac{I_{\max}}{C}$$

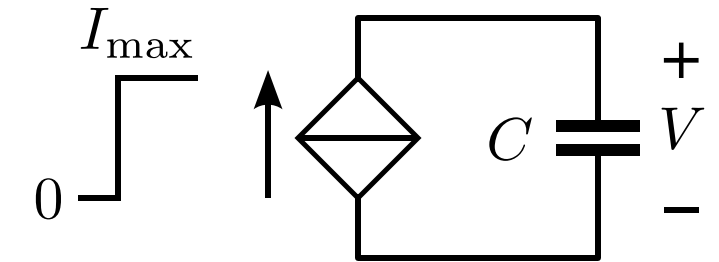

Signal voltage limitation and inductance in series with the signal path

$$\left. \frac{dI}{dt} \right|_{\max} = \frac{V_{\max}}{L}$$

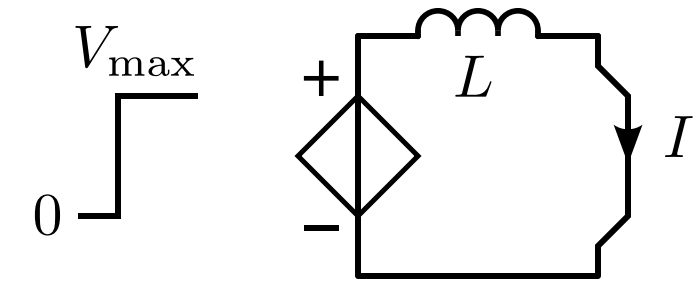

## Limitation of the full-power bandwidth

Maximum frequency of a sinusoidal signal of which:

peak-to-peak value equals maximum static signal swing

maximum of time derivative equals slew-rate limitation




# Dynamic voltage and current drive capability

## Limitation of the rate of change of the signal


Signal current limitation and capacitance in parallel with the signal path

$$\left. \frac{dV}{dt} \right|_{\max} = \frac{I_{\max}}{C}$$

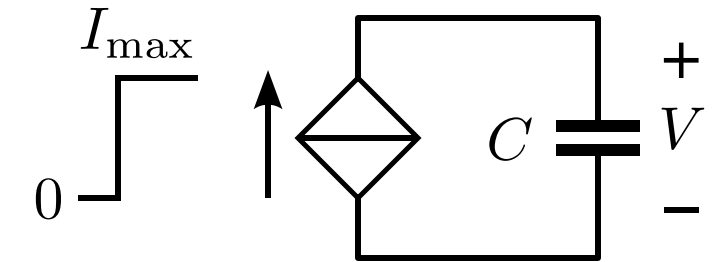

Signal voltage limitation and inductance in series with the signal path

$$\left. \frac{dI}{dt} \right|_{\max} = \frac{V_{\max}}{L}$$

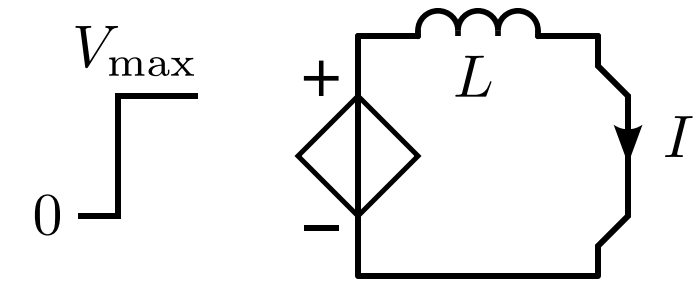

## Limitation of the full-power bandwidth

Maximum frequency of a sinusoidal signal of which:

peak-to-peak value equals maximum static signal swing

maximum of time derivative equals slew-rate limitation

$$f_{\text{fullPower}} = \frac{\text{SR}}{\pi A_{\max}}$$


← Maximum peak-to-peak signal swing  
← Slew-rate limitation

# Dynamic voltage and current drive capability

## Limitation of the rate of change of the signal


Signal current limitation and capacitance in parallel with the signal path

$$\left. \frac{dV}{dt} \right|_{\max} = \frac{I_{\max}}{C}$$

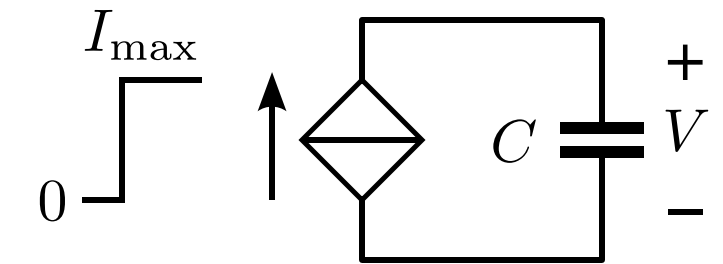

Signal voltage limitation and inductance in series with the signal path

$$\left. \frac{dI}{dt} \right|_{\max} = \frac{V_{\max}}{L}$$

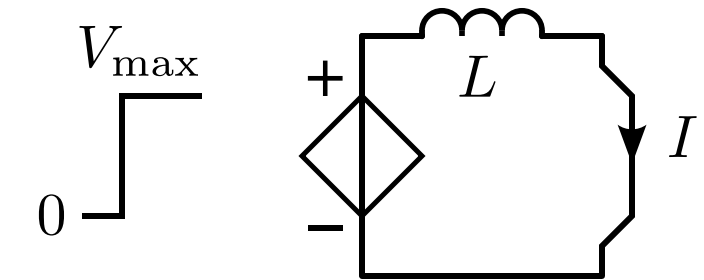

## Limitation of the full-power bandwidth

Maximum frequency of a sinusoidal signal of which:

peak-to-peak value equals maximum static signal swing

maximum of time derivative equals slew-rate limitation

$$f_{\text{fullPower}} = \frac{\text{SR}}{\pi A_{\max}}$$

← Maximum peak-to-peak signal swing  
← Slew-rate limitation

