


Structured Electronic Design

Balancing of two-terminal elements

Anton J.M. Montagne


Anti-series and complementary-series connections

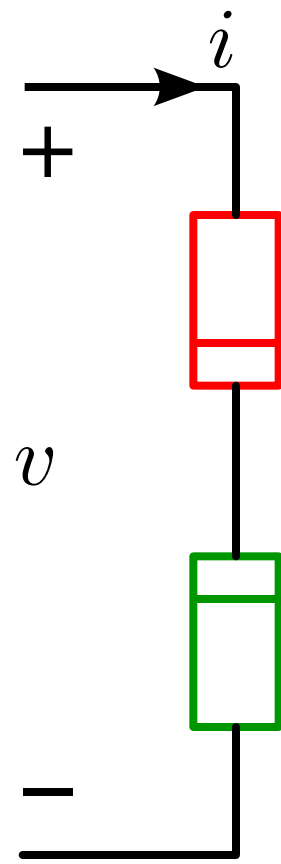Anti-series and complementary-series connections




Anti-series
connection of
equal elements

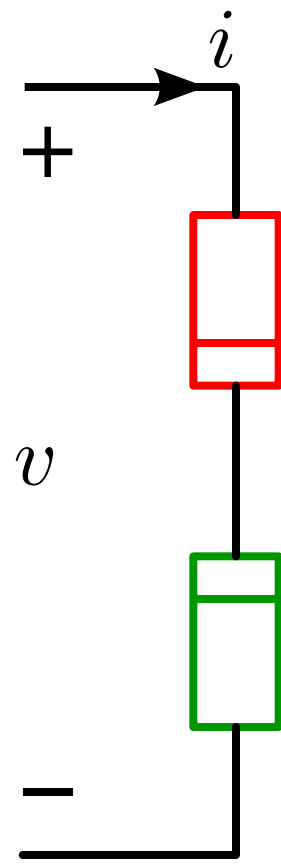Anti-series and complementary-series connections




Anti-series
connection of
equal elements

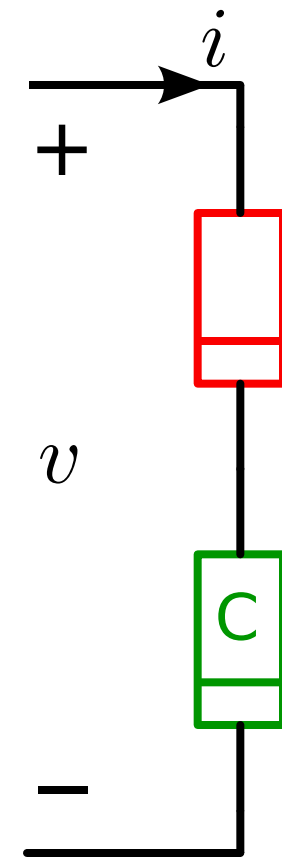


Series
connection of
complementary
elements

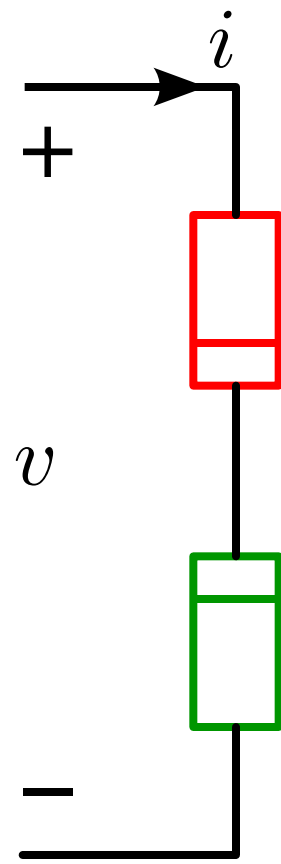
Anti-series and complementary-series connections




Anti-series
connection of
equal elements

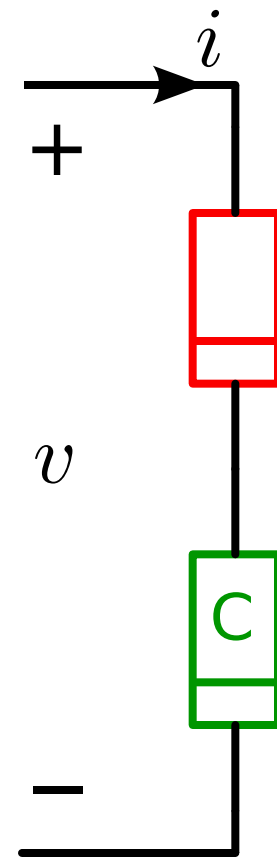

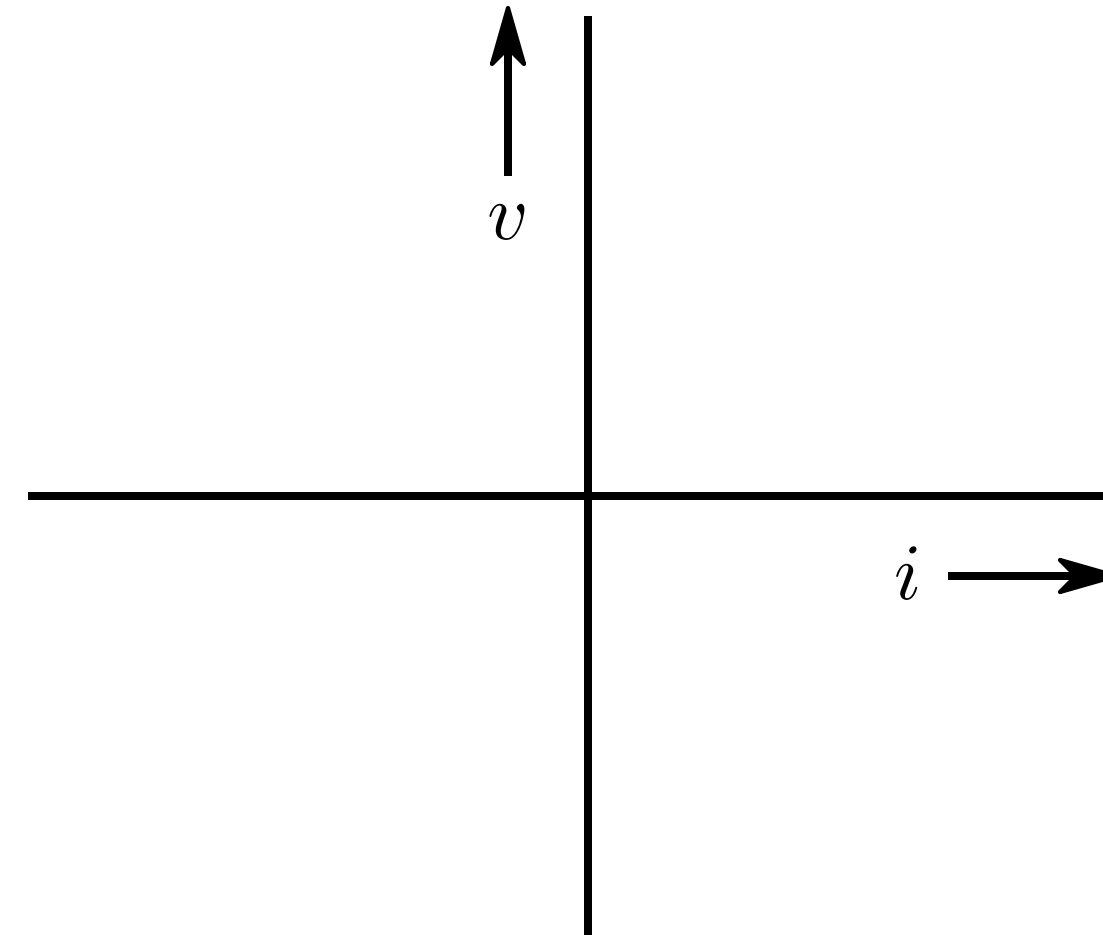
Series
connection of
complementary
elements



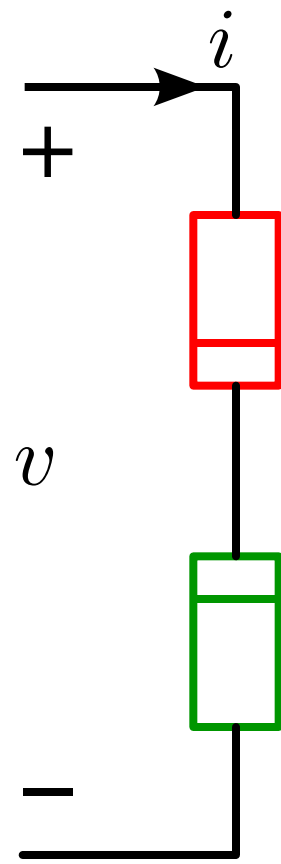
Anti-series and complementary-series connections




Anti-series
connection of
equal elements

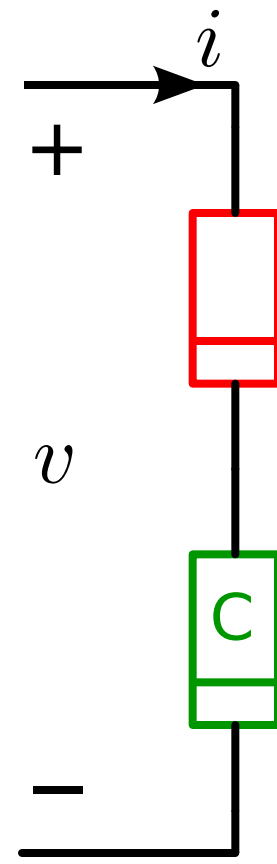

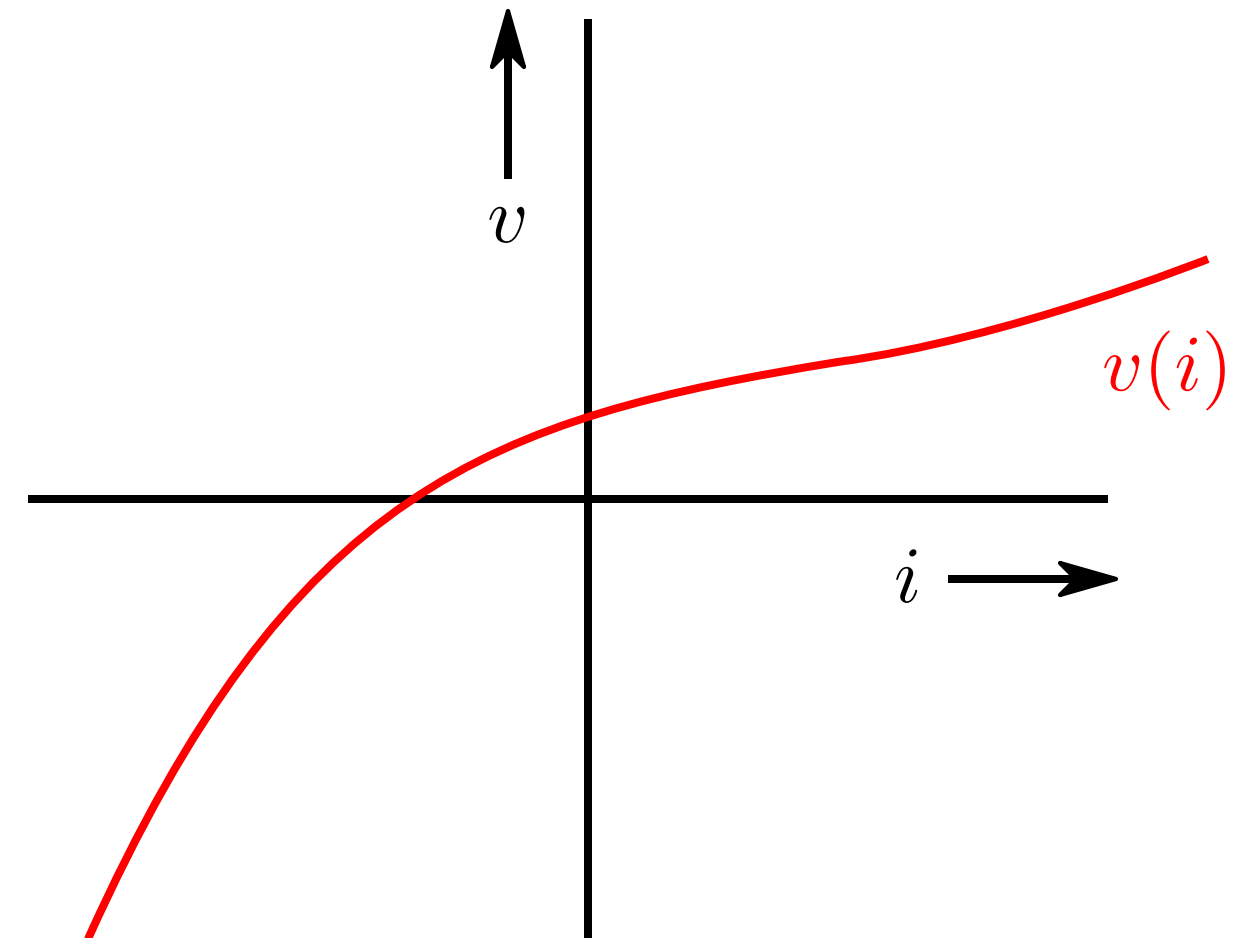
Series
connection of
complementary
elements



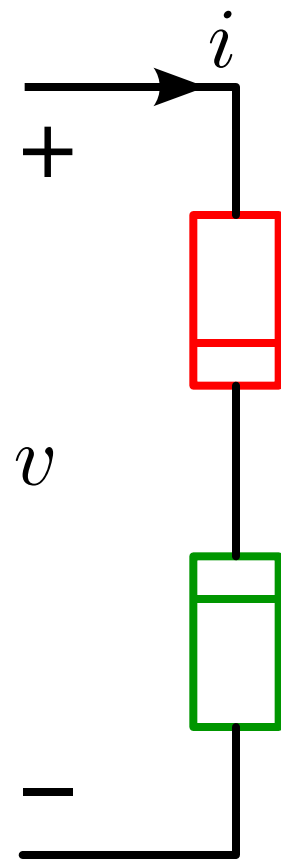
Anti-series and complementary-series connections




Anti-series
connection of
equal elements

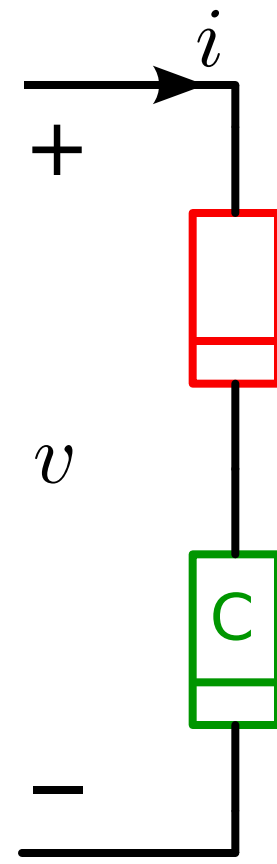

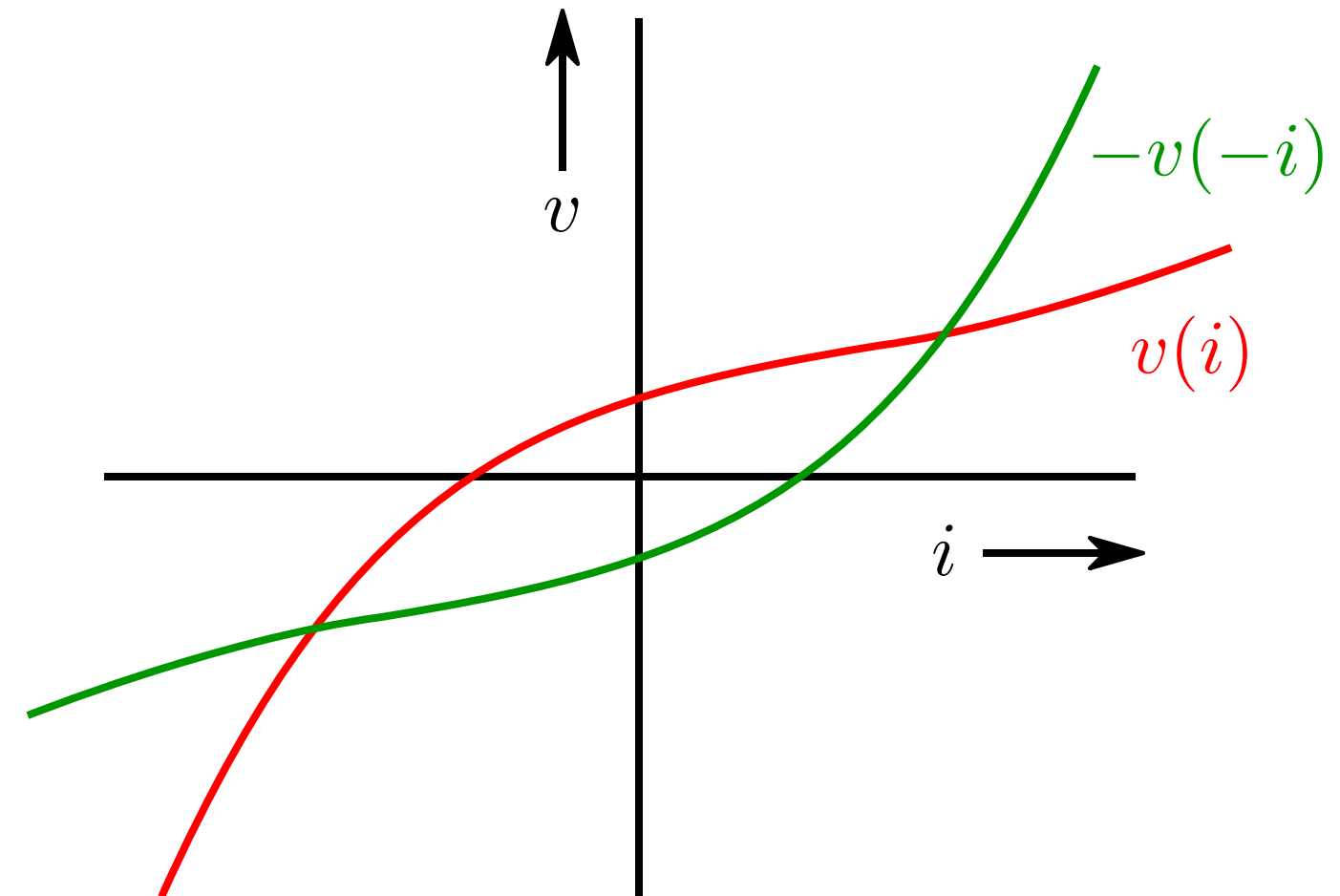
Series
connection of
complementary
elements



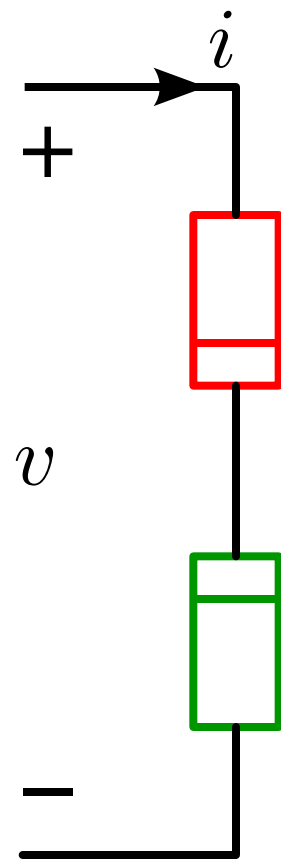
Anti-series and complementary-series connections



Anti-series connection of equal elements

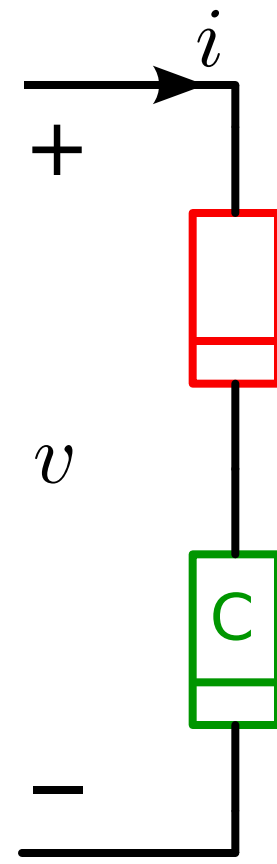


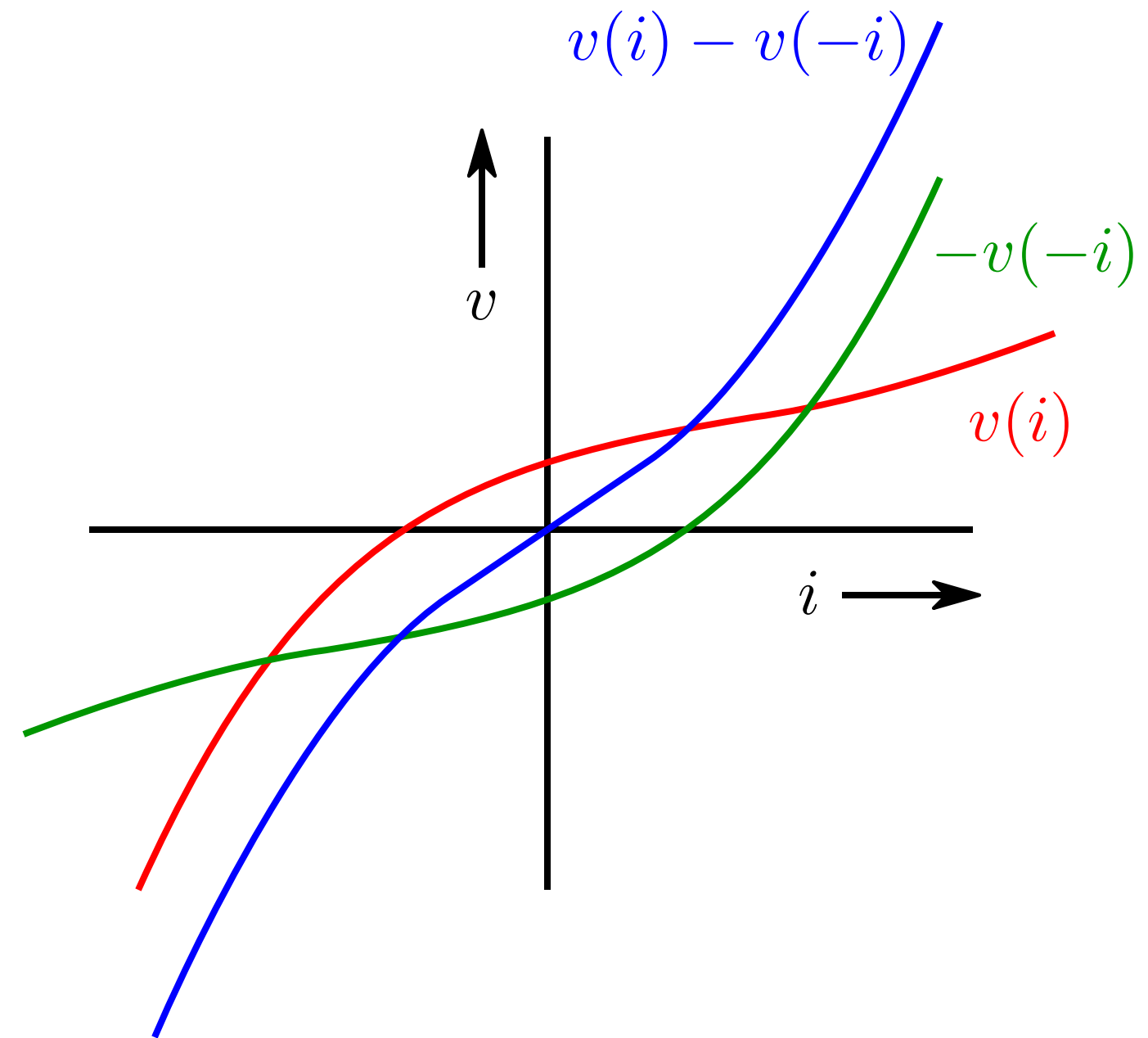Series connection of complementary elements





Anti-series and complementary-series connections


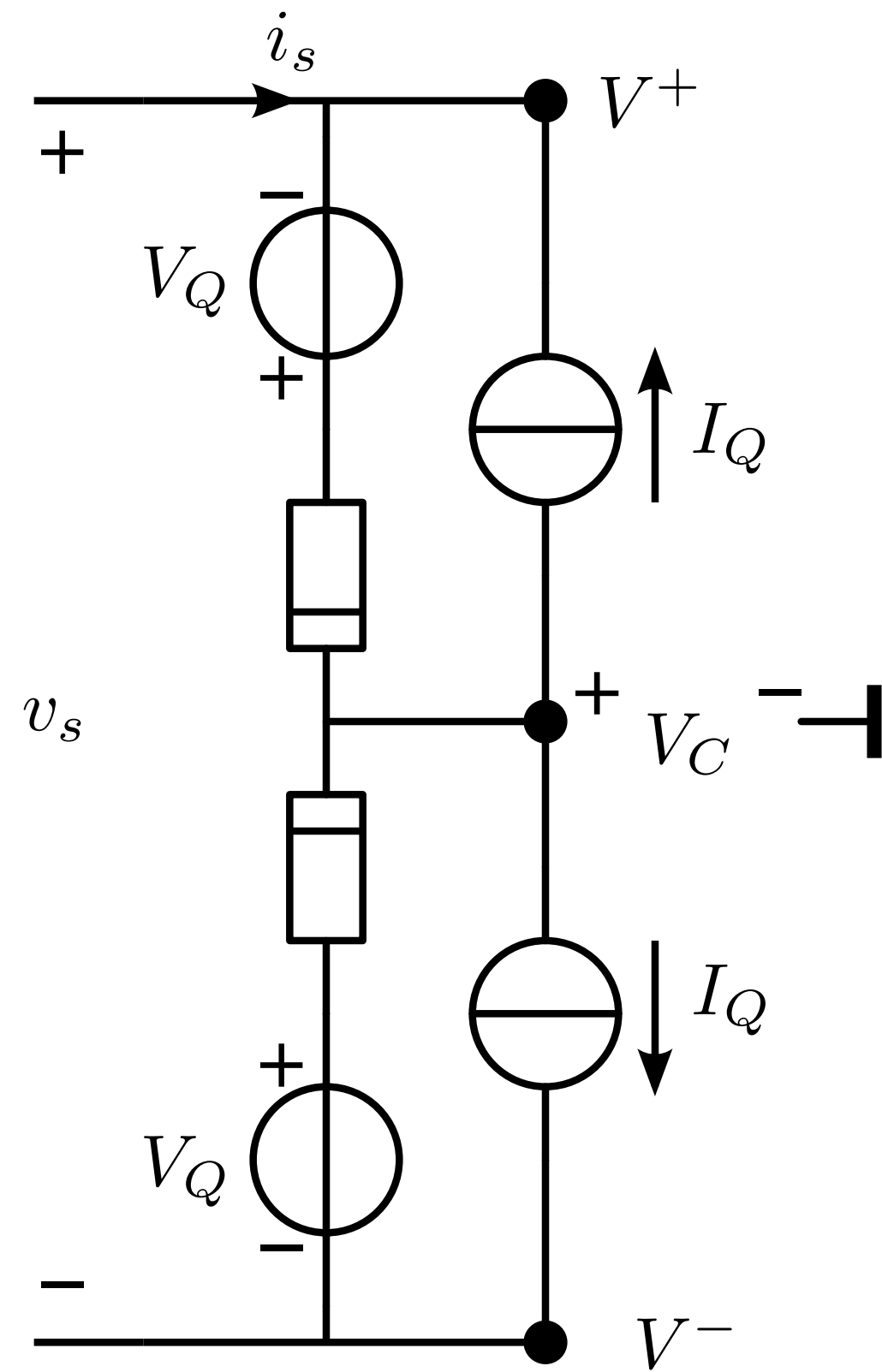
Anti-series and complementary-series connections



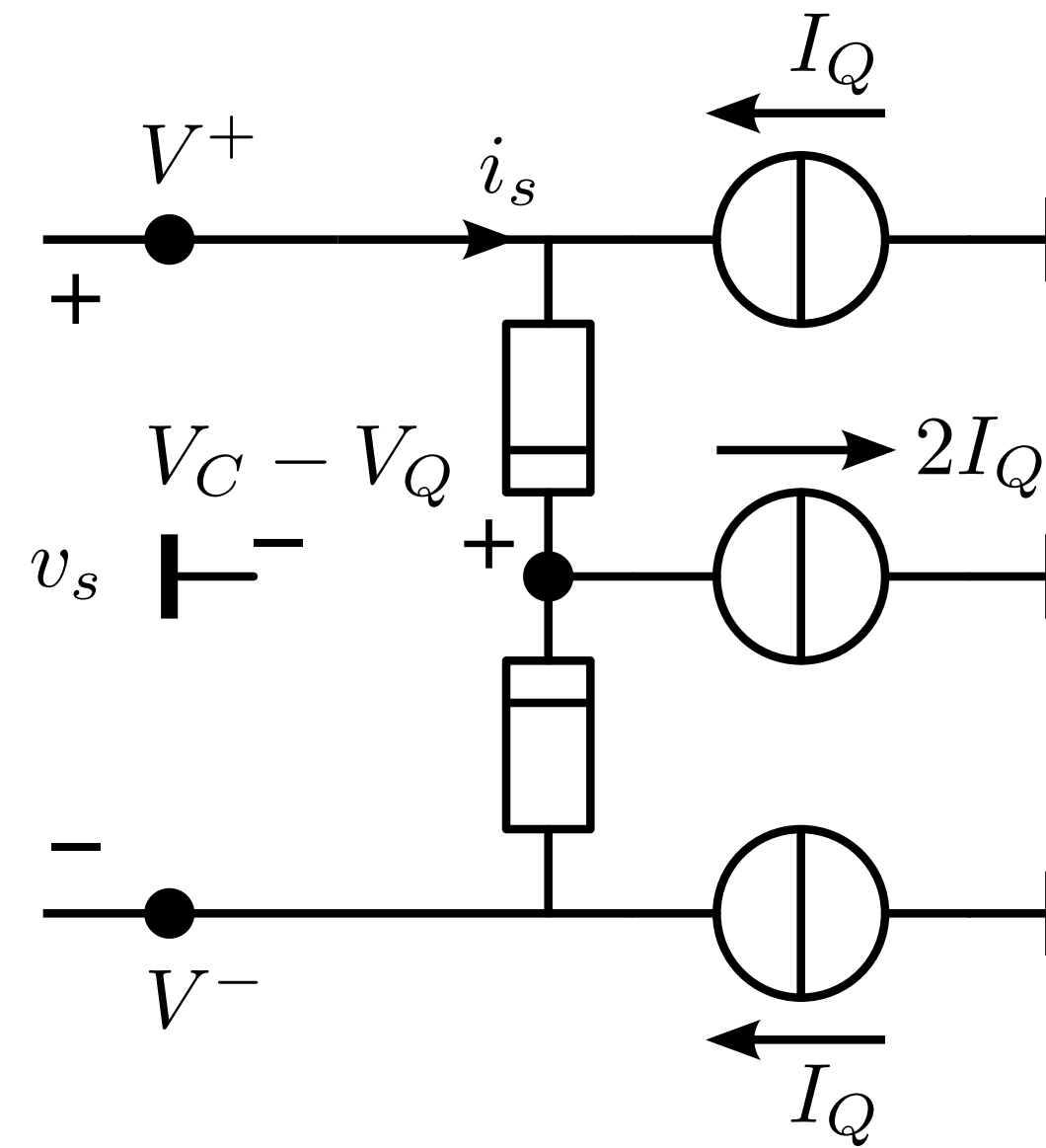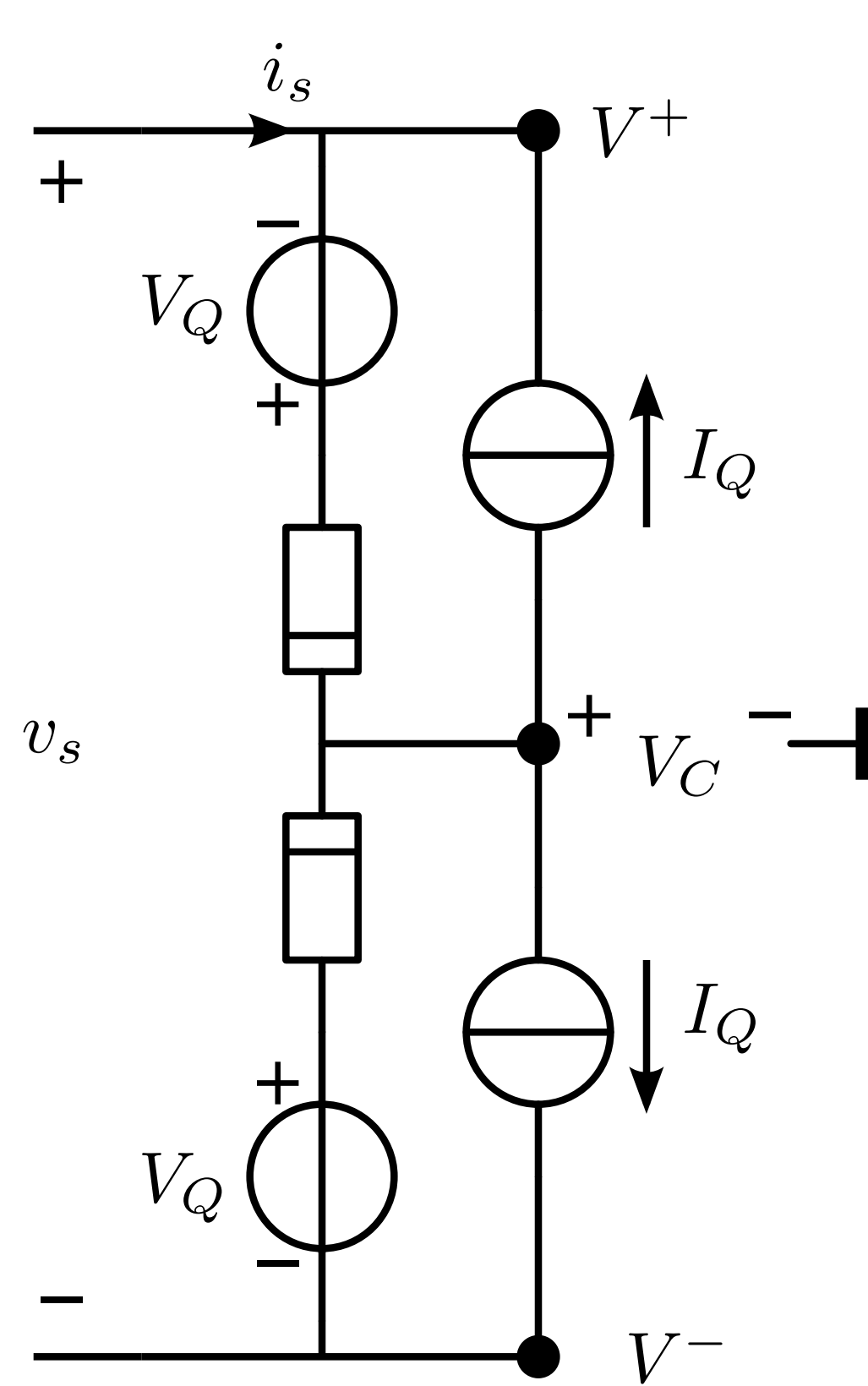Anti-series and complementary-series connections





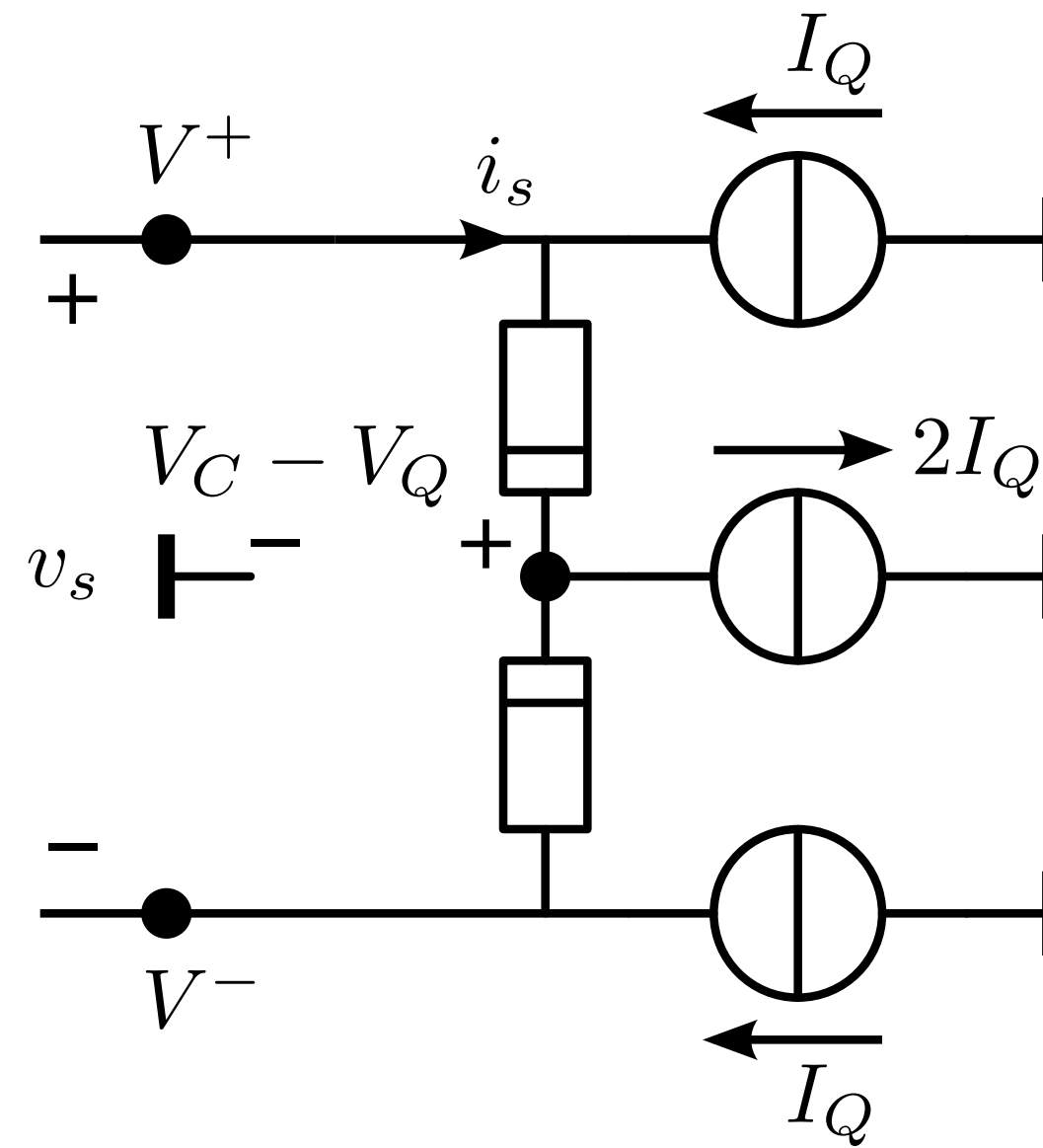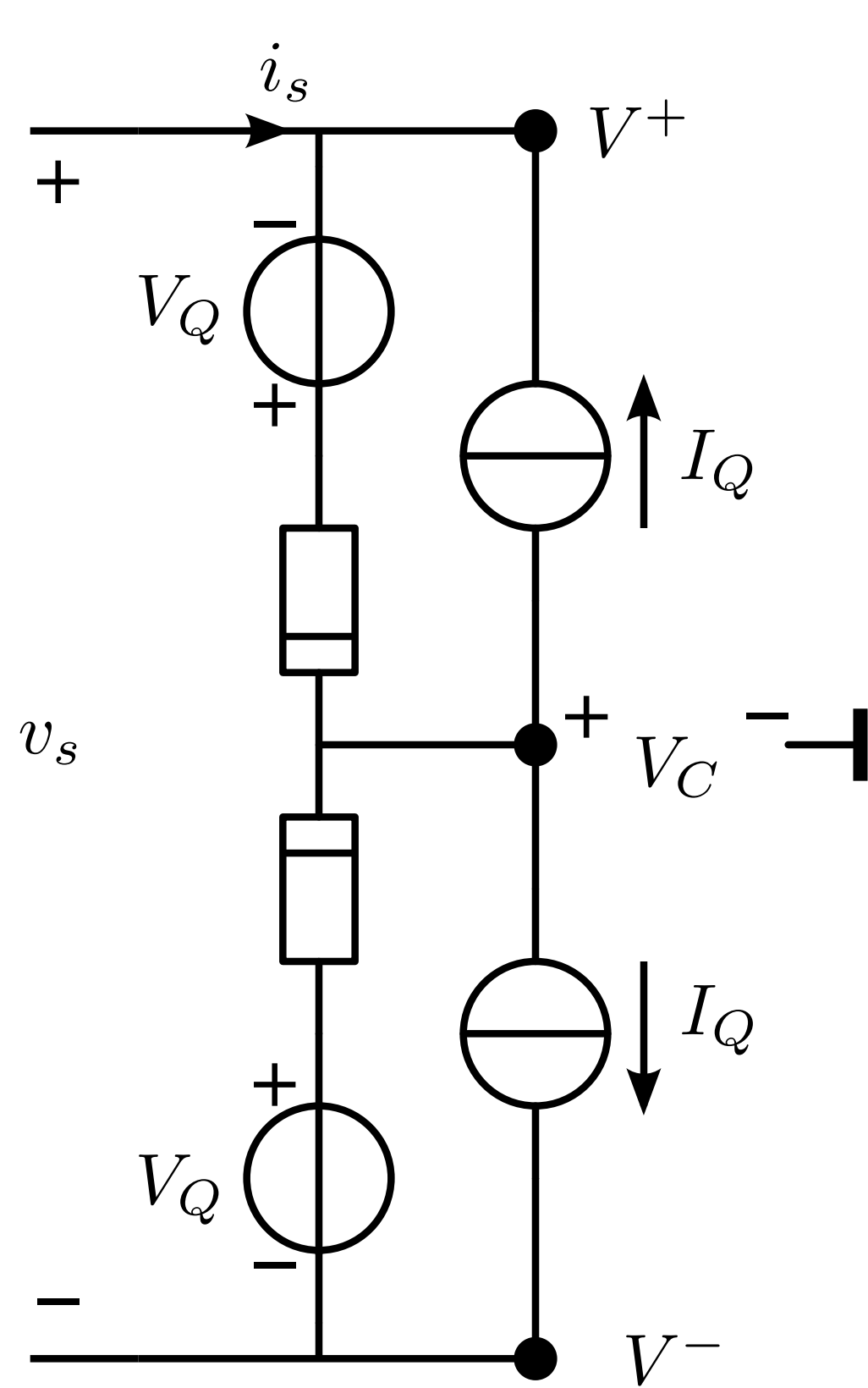Anti-series and complementary-series connections





Elements can be biased with common-mode current sources

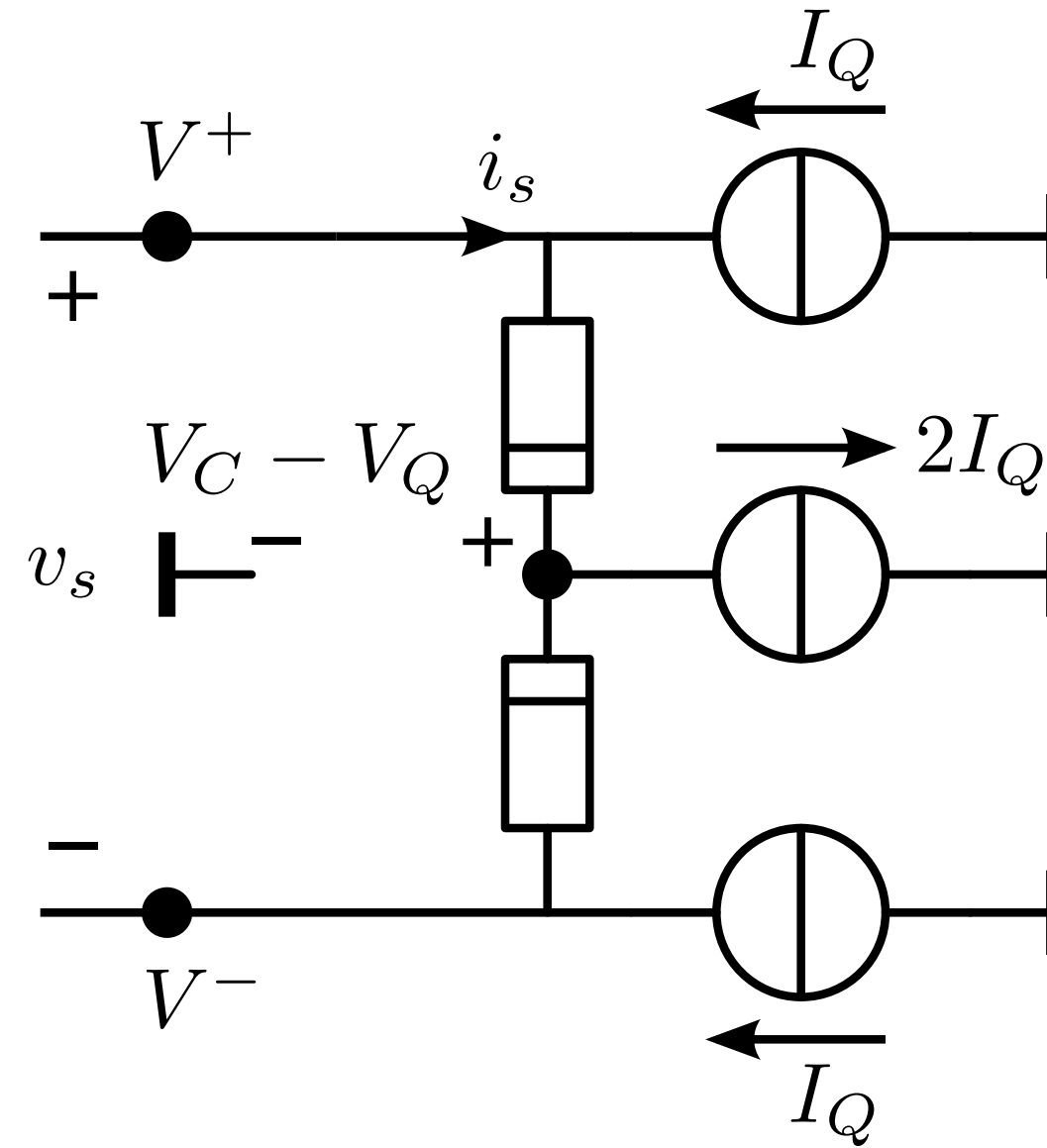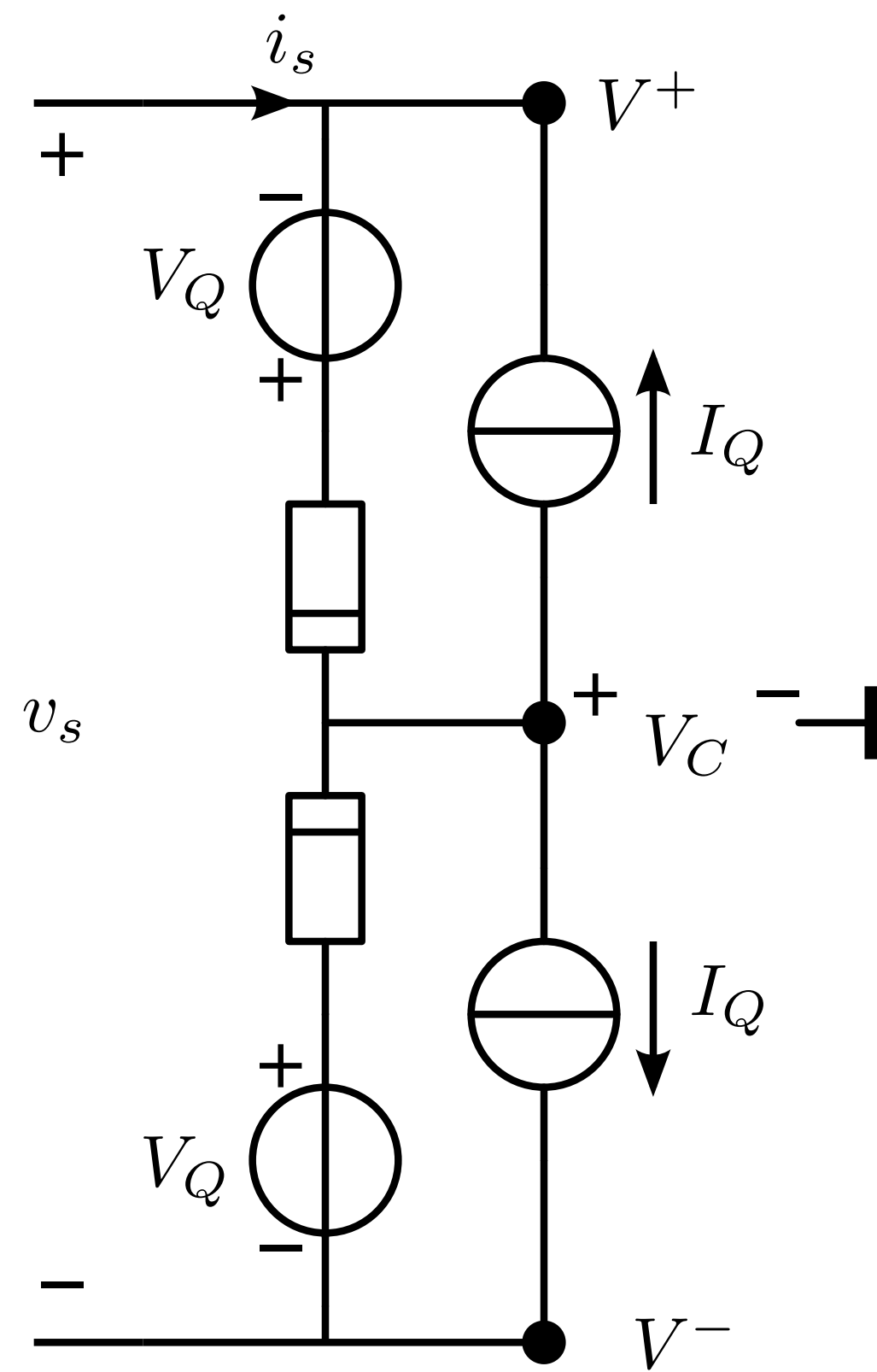Anti-series and complementary-series connections



Elements can be biased with common-mode current sources
 Bias voltage appears as common-mode voltage in the circuit

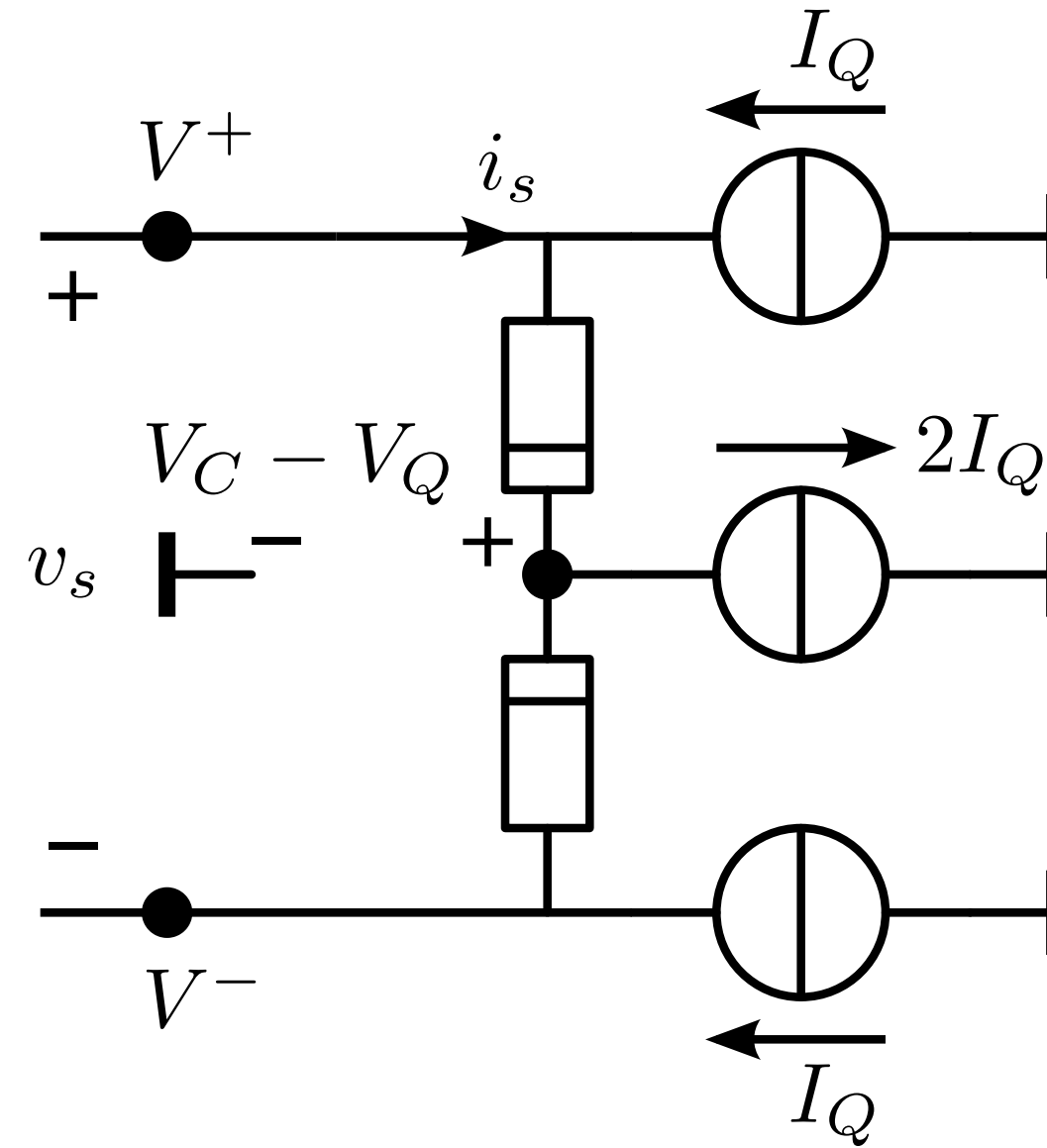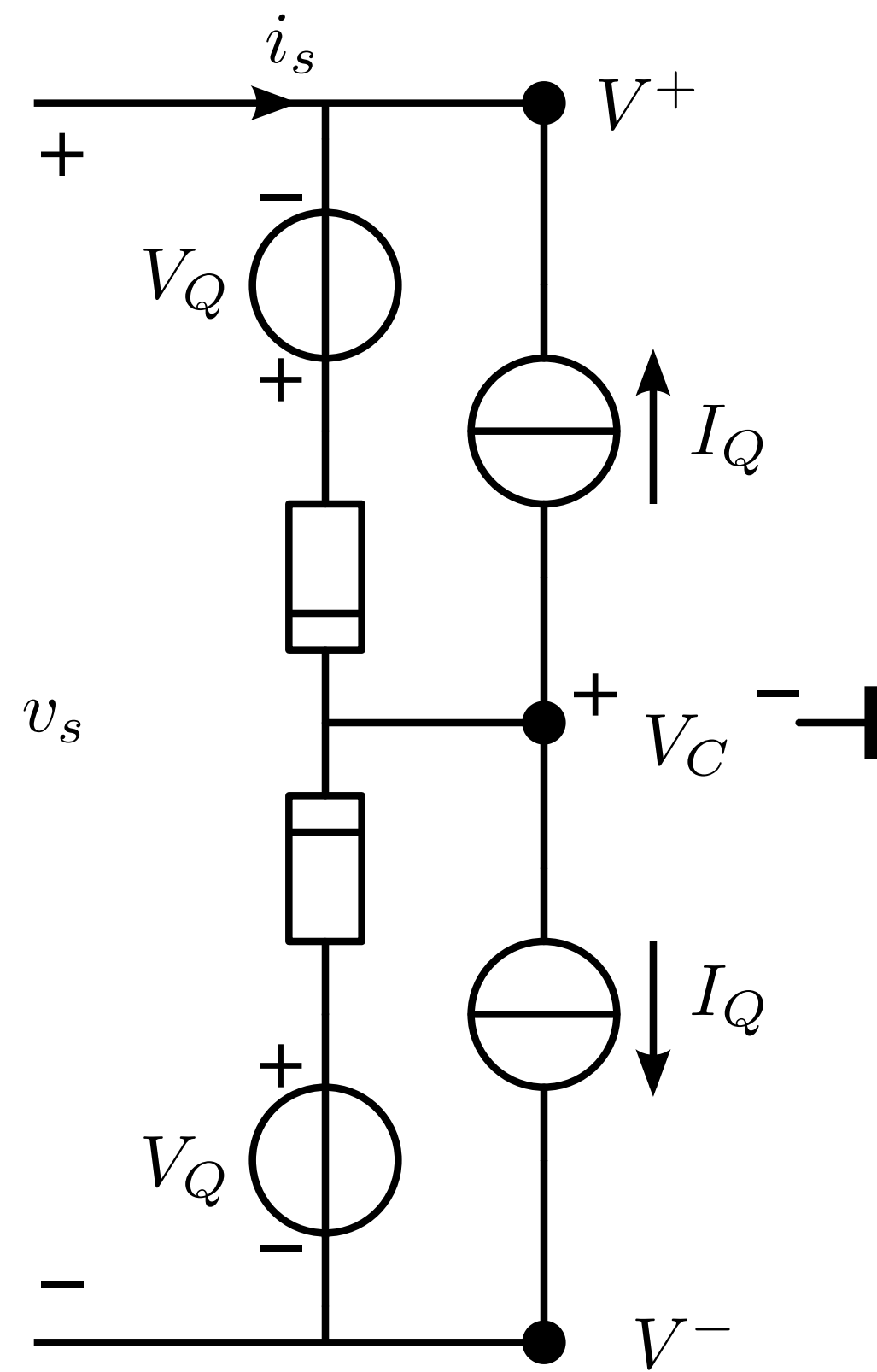Anti-series and complementary-series connections




Elements can be biased with common-mode current sources
 Bias voltage appears as common-mode voltage in the circuit

Anti-series and complementary-series connections

Small-signal model


Anti-series and complementary-series connections

Small-signal model

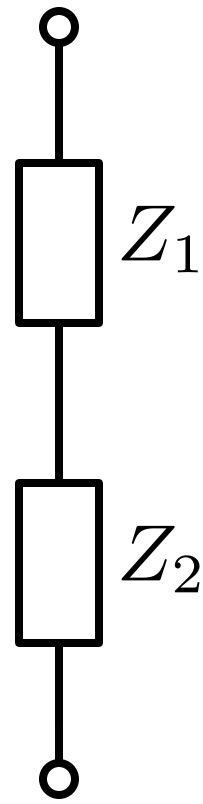


Anti-series and complementary-series connections

Small-signal model


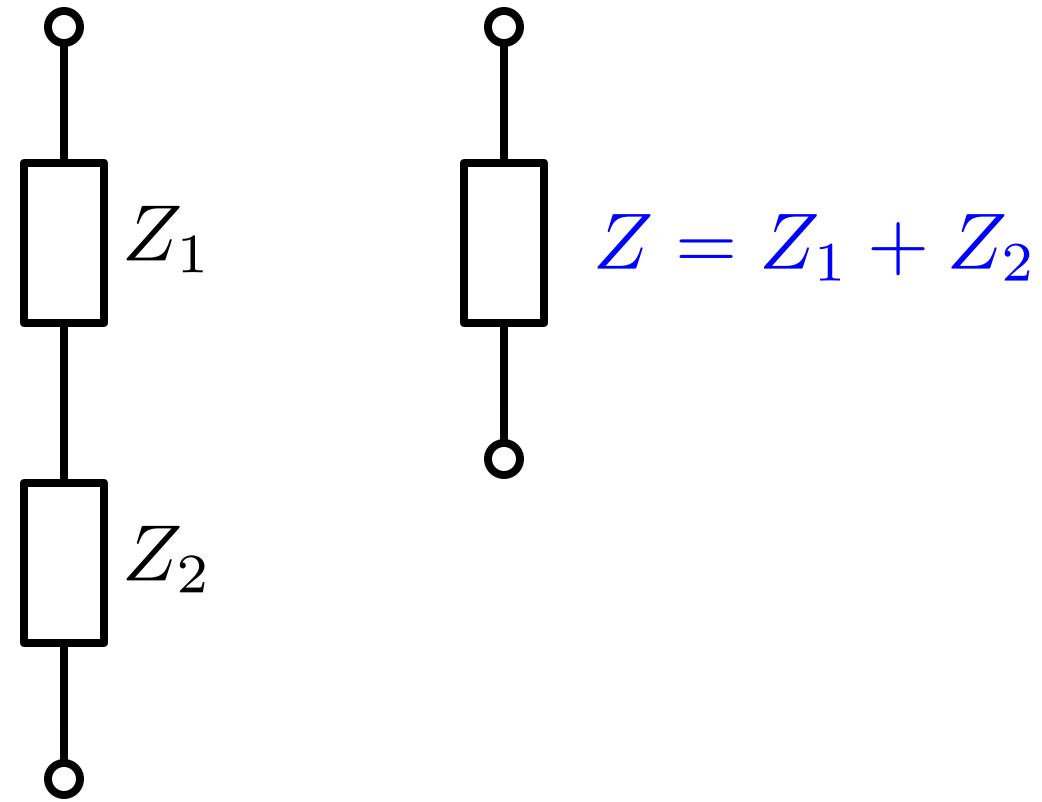


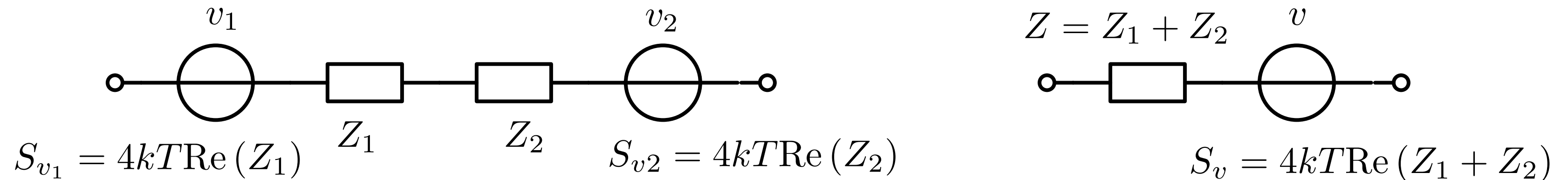Voltage noise spectral density is the sum of the voltage noise spectral densities of the constituting elements



Anti-series and complementary-series connections

Small-signal model

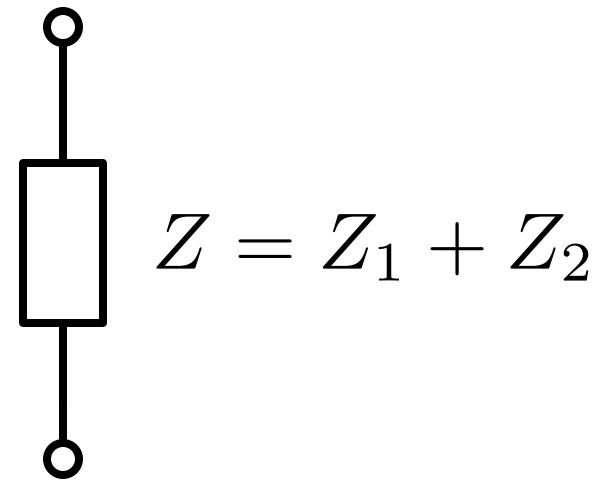
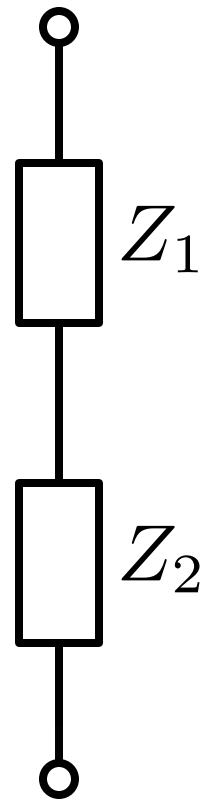


$$Z = Z_1 + Z_2$$

Small-signal impedance is
sum of small-signal
impedances of
constituting elements

Anti-series and complementary-series connections

Small-signal model

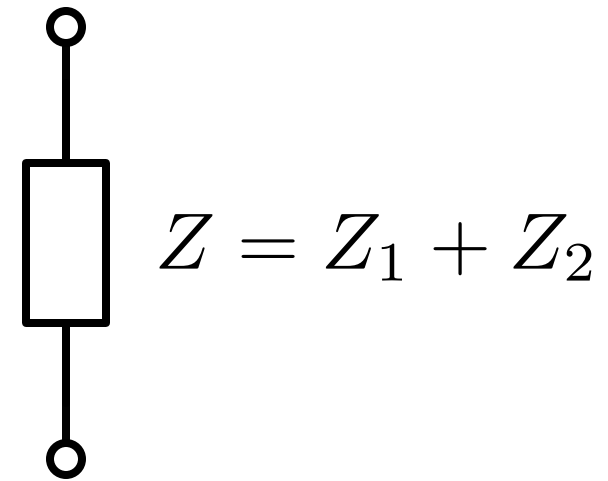
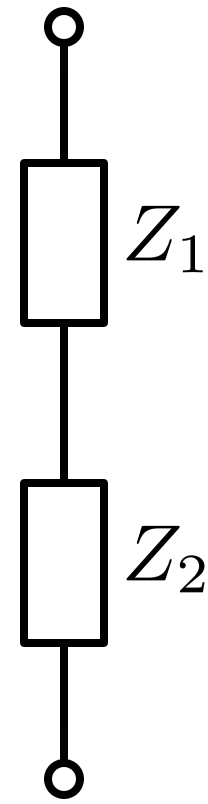


$$Z = 2Z_1 = 2Z_2$$

Small-signal impedance is sum of small-signal impedances of constituting elements

Anti-series and complementary-series connections

Small-signal model

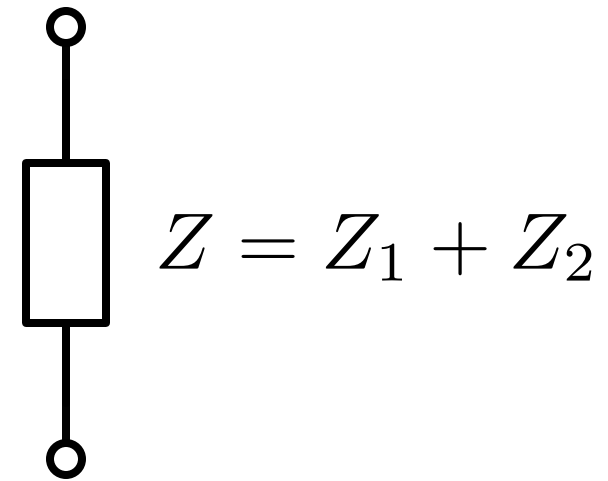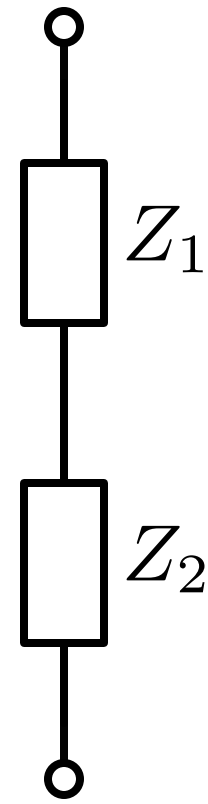



$$Z = 2Z_1 = 2Z_2$$

Small-signal impedance is sum of small-signal impedances of constituting elements

Twice the impedance in the quiescent operating point

Anti-series and complementary-series connections

Small-signal model

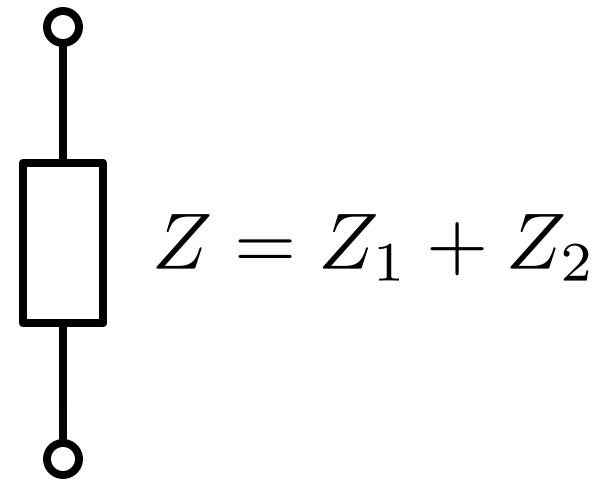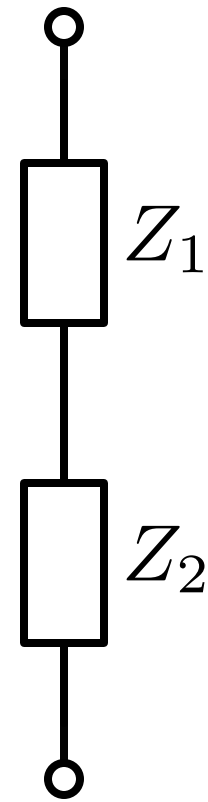

$$Z = 2Z_1 = 2Z_2$$



Small-signal impedance is sum of small-signal impedances of constituting elements

Twice the impedance in the quiescent operating point

Voltage noise spectral density is the sum of the voltage noise spectral densities of the constituting elements

Anti-series and complementary-series connections

Small-signal model

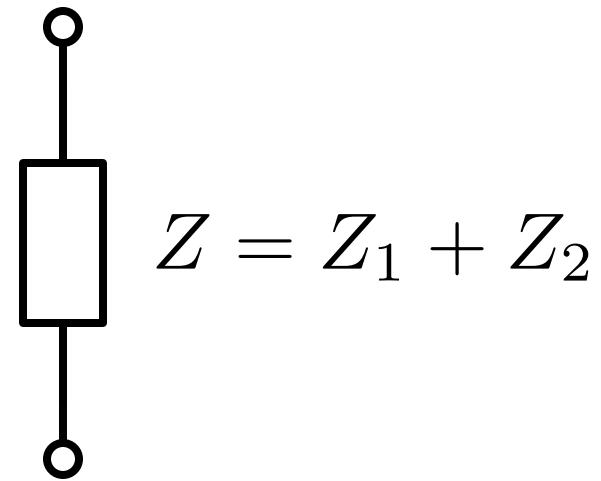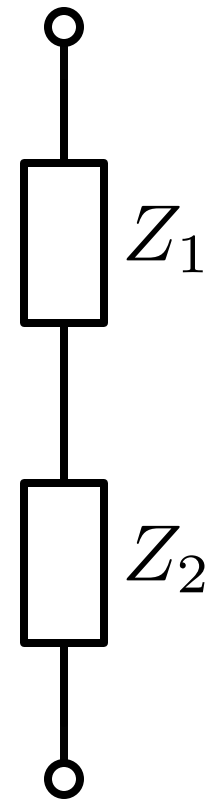


Small-signal impedance is sum of small-signal impedances of constituting elements

$$Z = Z_1 + Z_2$$

Twice the impedance in the quiescent operating point



$$Z = 2Z_1 = 2Z_2$$

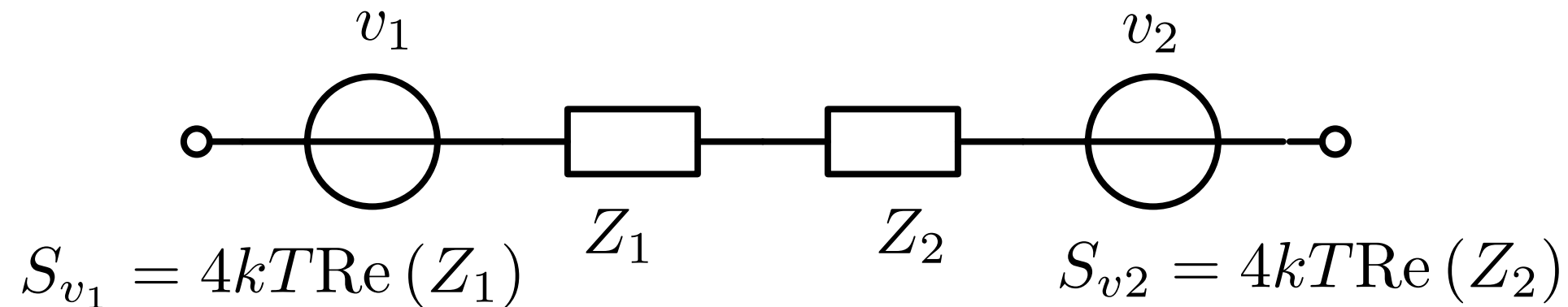Voltage noise spectral density is the sum of the voltage noise spectral densities of the constituting elements



Anti-series and complementary-series connections

Small-signal model

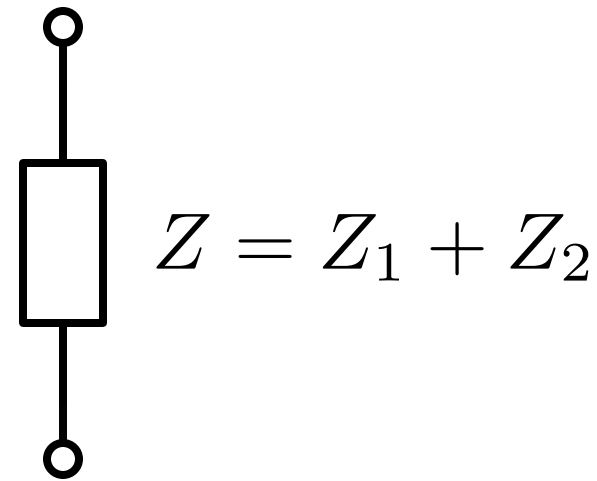
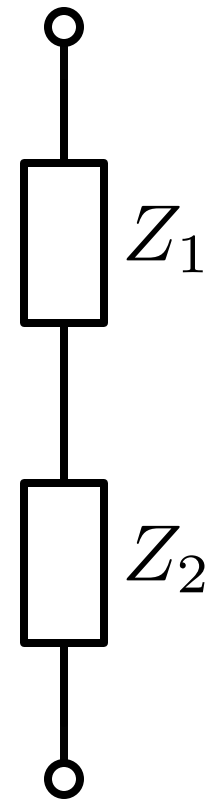


Small-signal impedance is sum of small-signal impedances of constituting elements

$$Z = 2Z_1 = 2Z_2$$



Twice the impedance in the quiescent operating point

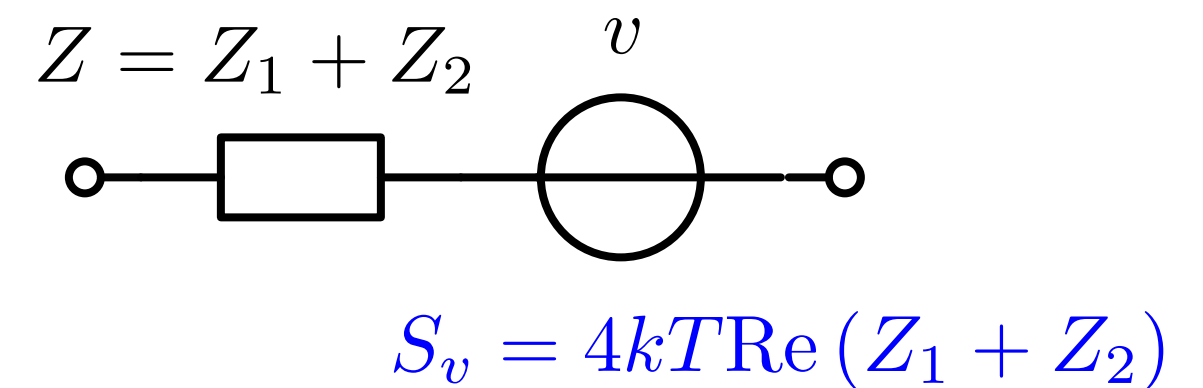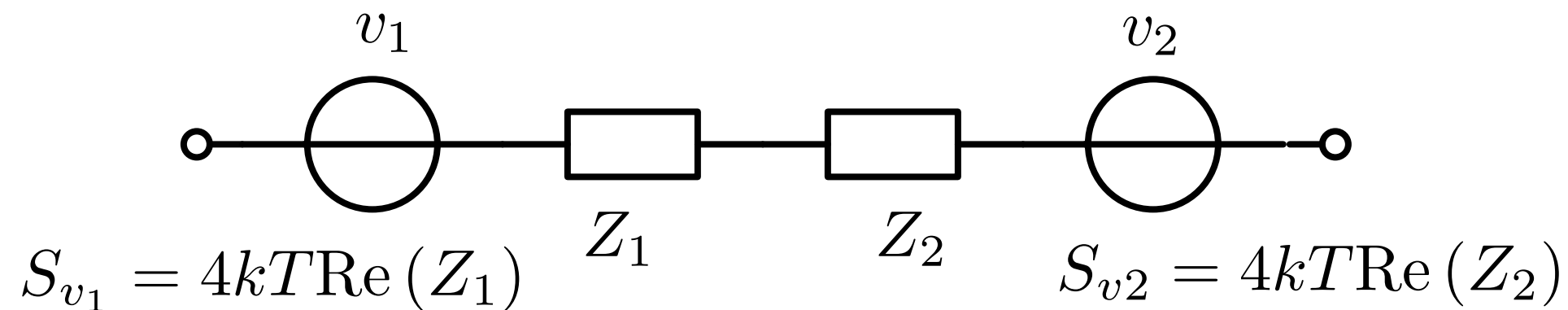Voltage noise spectral density is the sum of the voltage noise spectral densities of the constituting elements



Anti-series and complementary-series connections

Small-signal model

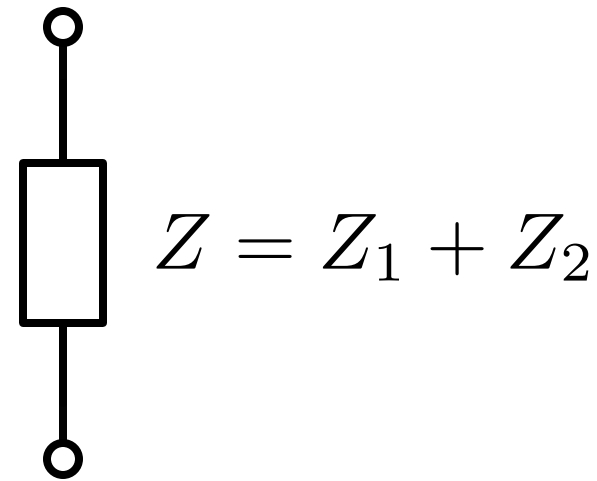
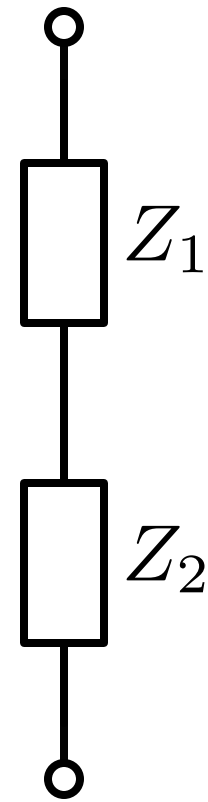


Small-signal impedance is sum of small-signal impedances of constituting elements

$$Z = 2Z_1 = 2Z_2$$


Twice the impedance in the quiescent operating point

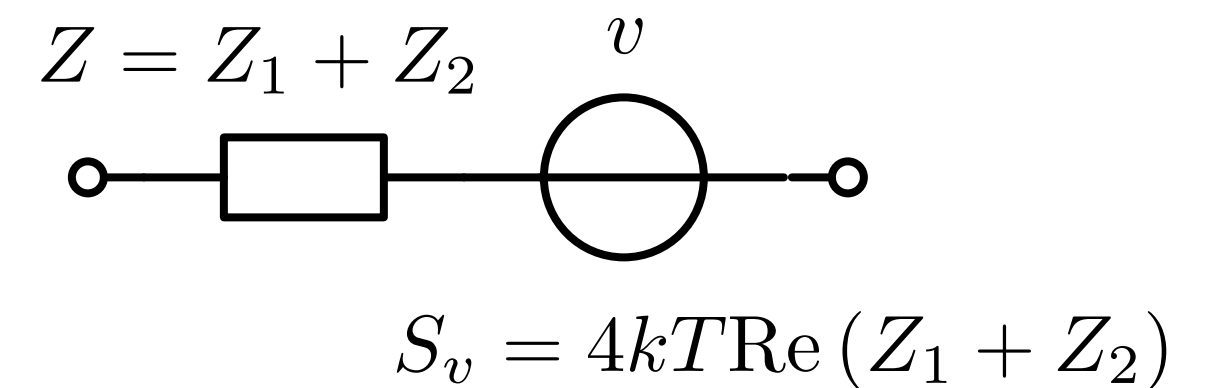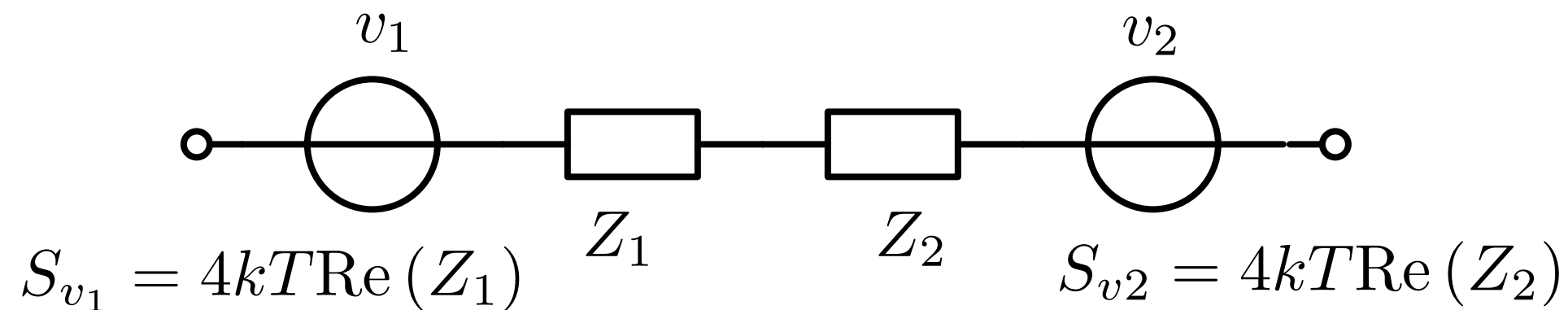Voltage noise spectral density is the sum of the voltage noise spectral densities of the constituting elements




Anti-parallel and complementary-parallel connections

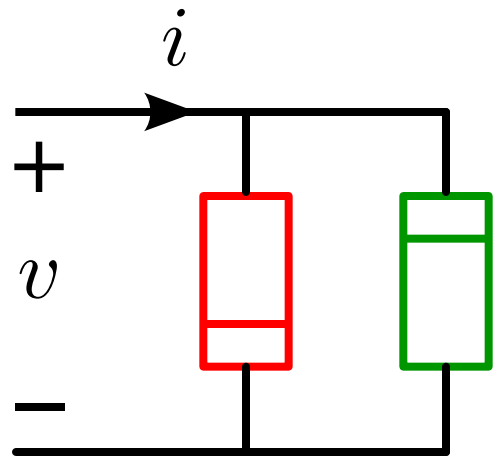Anti-parallel and complementary-parallel connections




Anti-parallel
connection of
equal elements

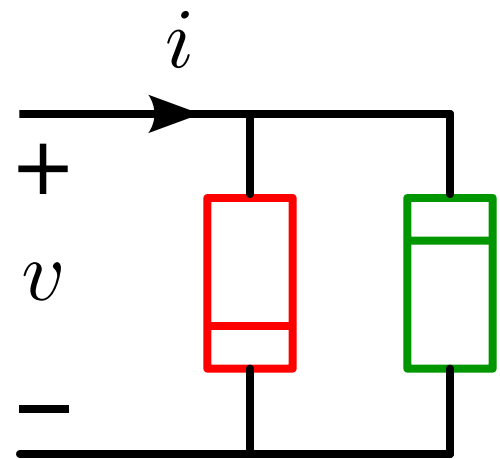Anti-parallel and complementary-parallel connections




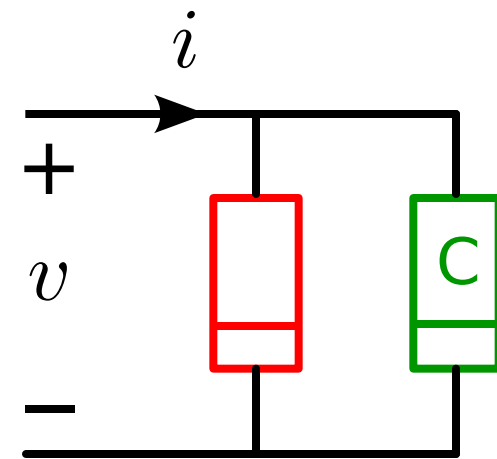Anti-parallel
connection of
equal elements




Parallel
connection of
complementary
elements

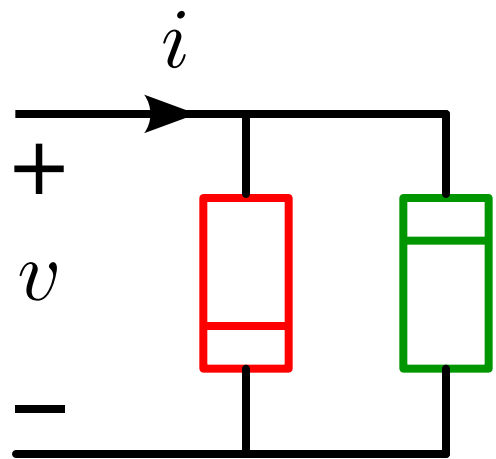
Anti-parallel and complementary-parallel connections



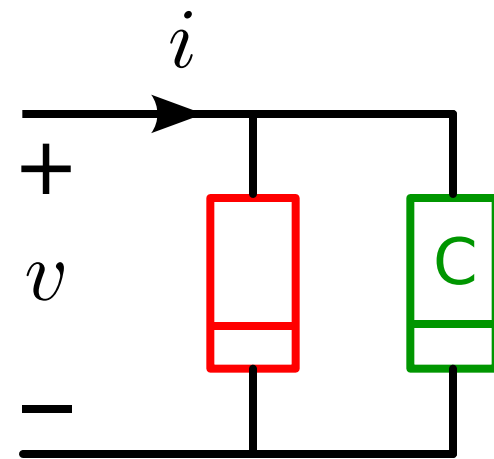
Anti-parallel connection of equal elements



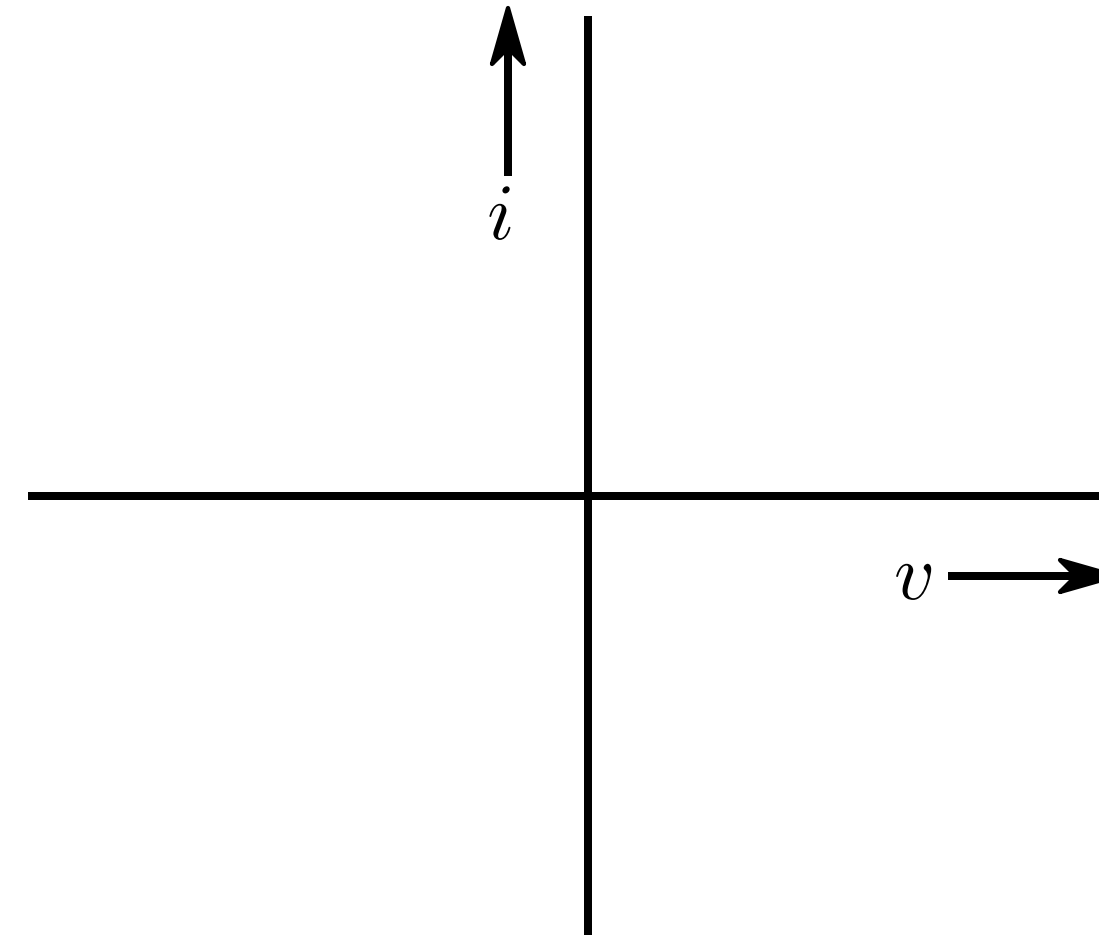
Parallel connection of complementary elements



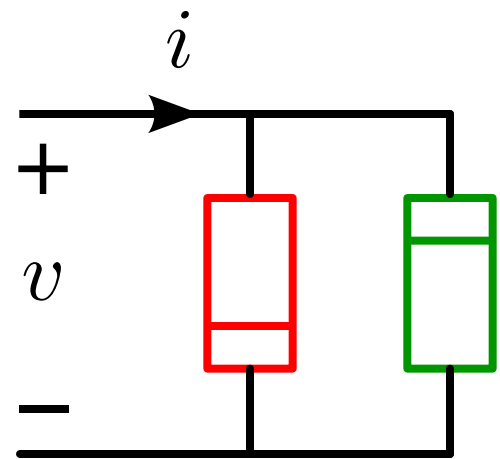
Anti-parallel and complementary-parallel connections



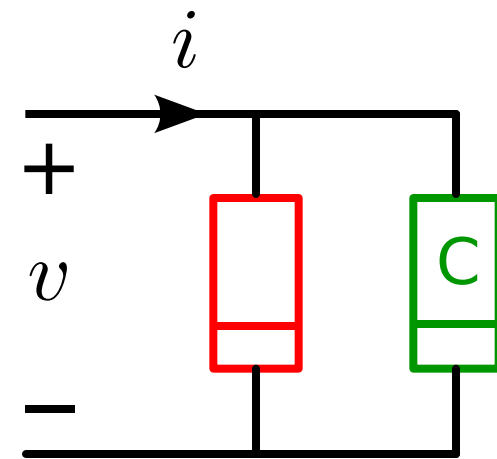
Anti-parallel connection of equal elements



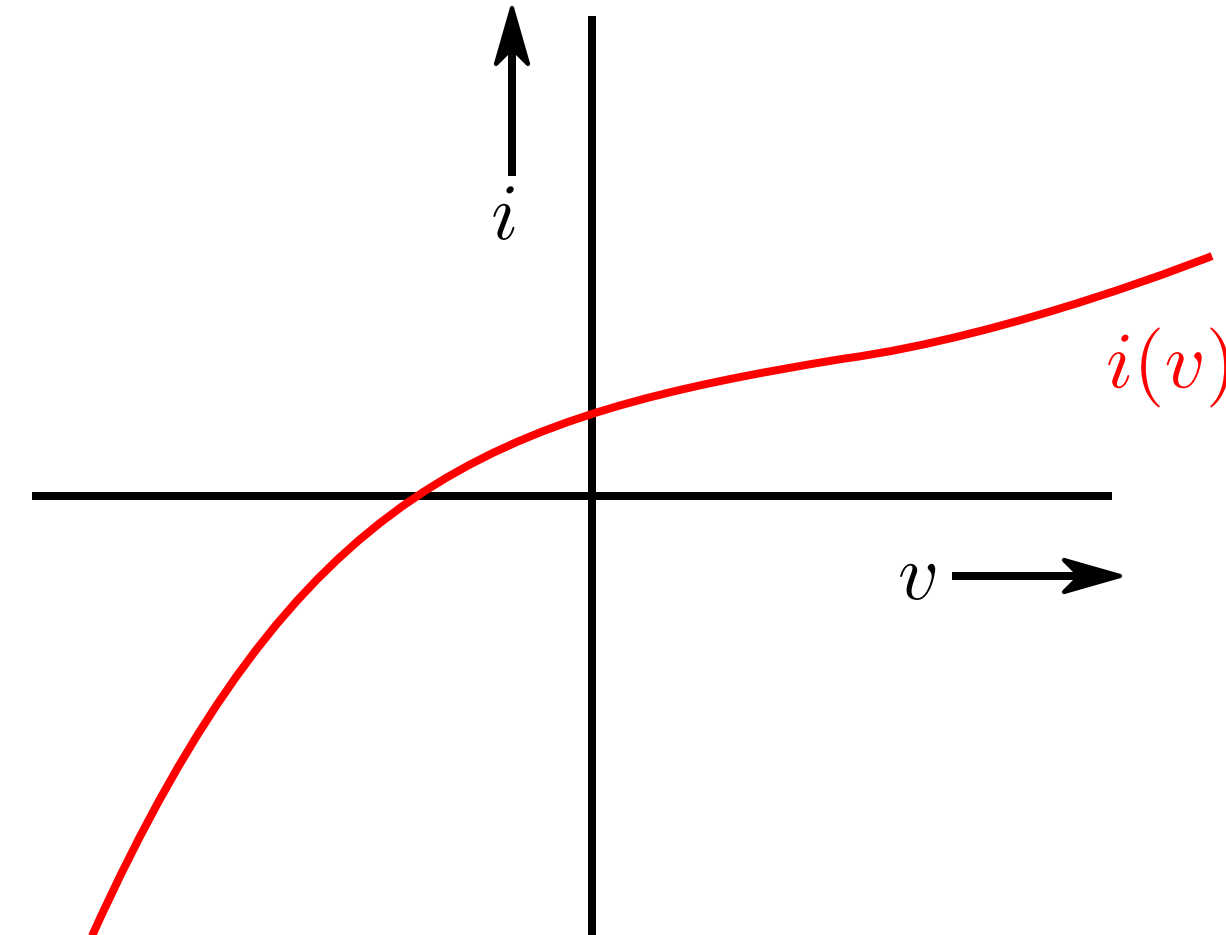
Parallel connection of complementary elements



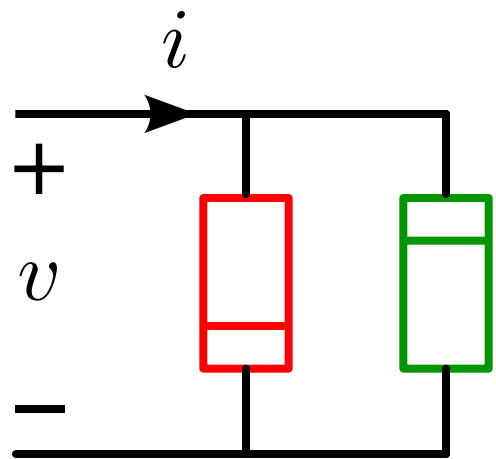
Anti-parallel and complementary-parallel connections



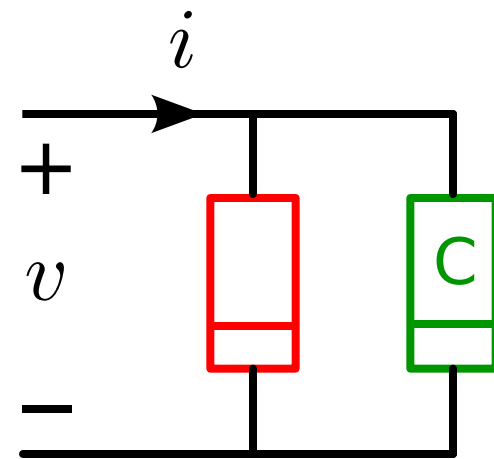
Anti-parallel connection of equal elements



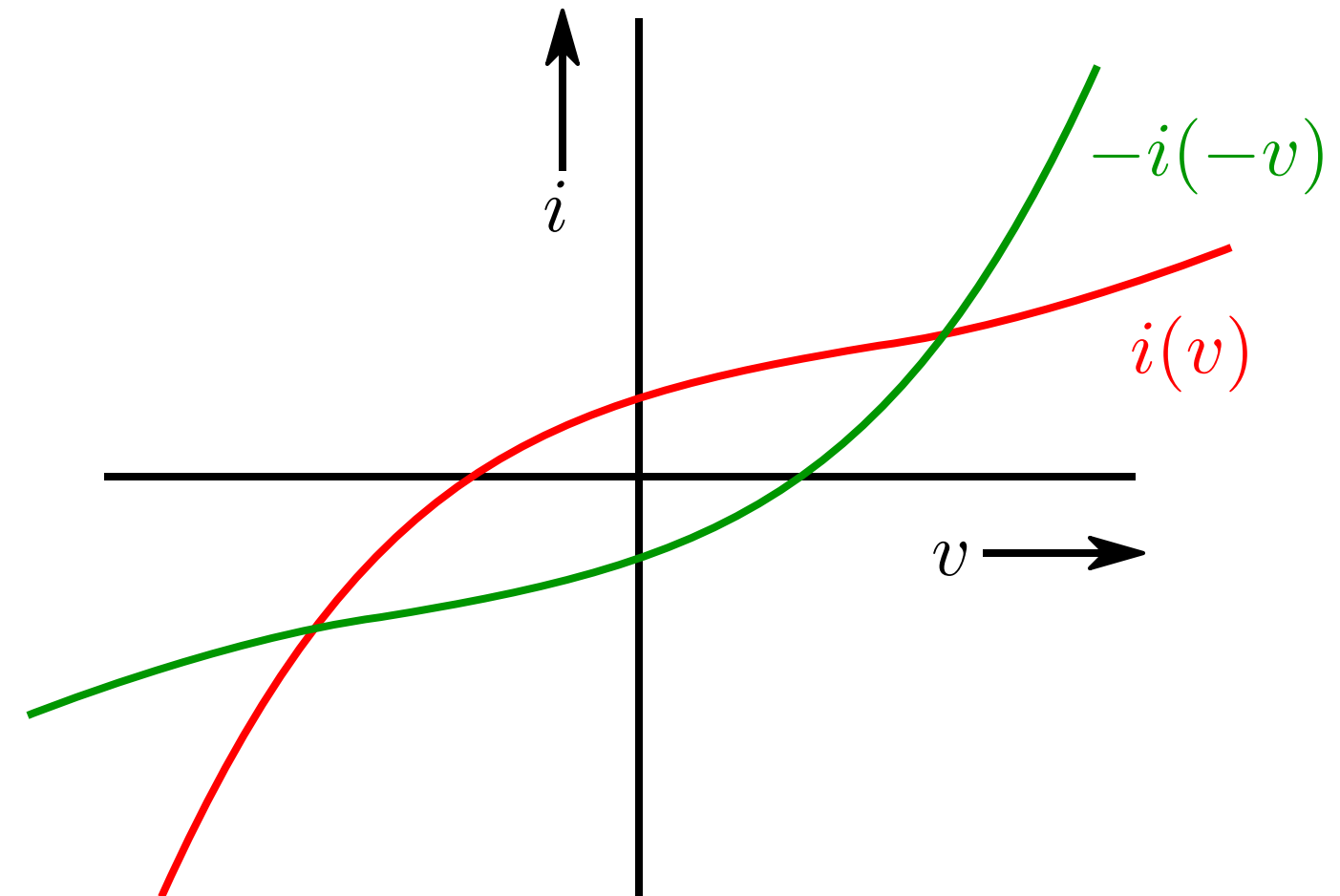
Parallel connection of complementary elements



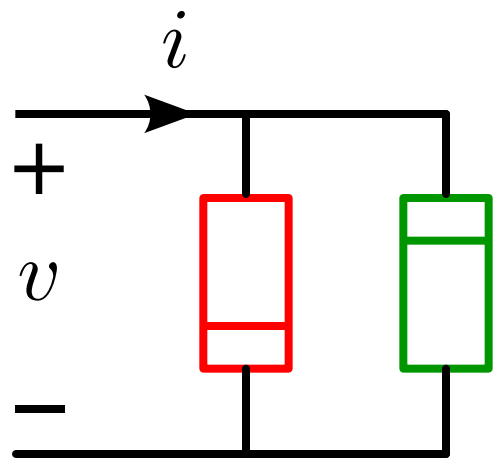
Anti-parallel and complementary-parallel connections



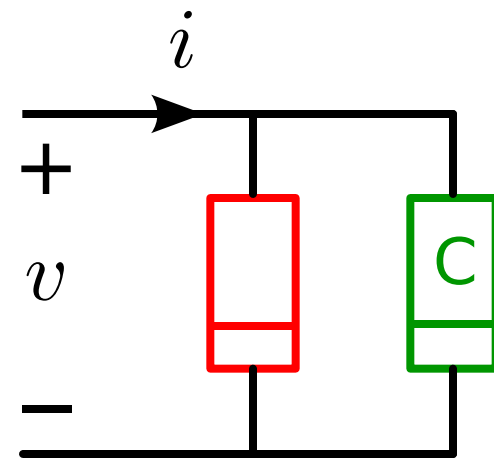Anti-parallel connection of equal elements




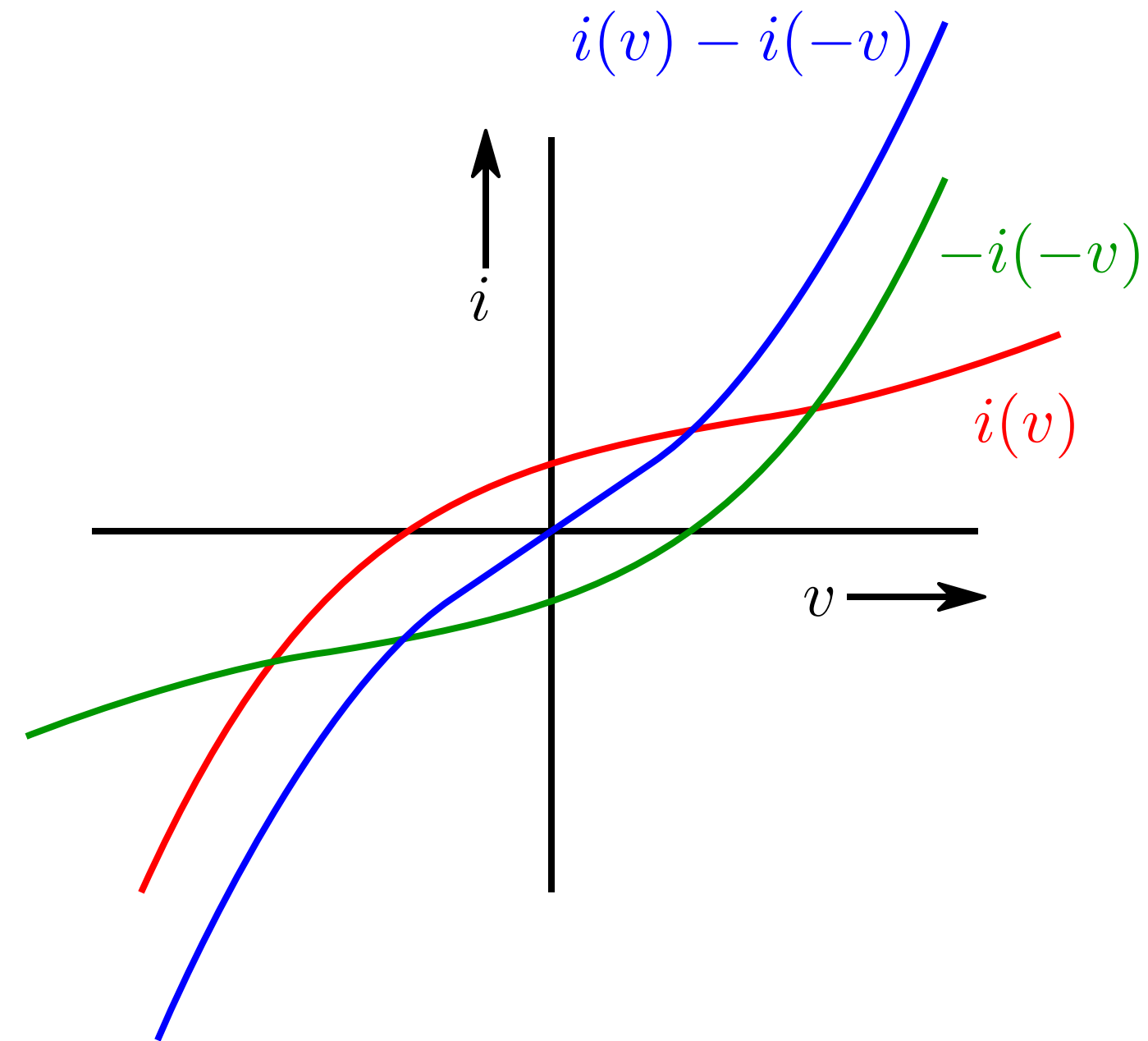Parallel connection of complementary elements





Anti-parallel and complementary-parallel connections


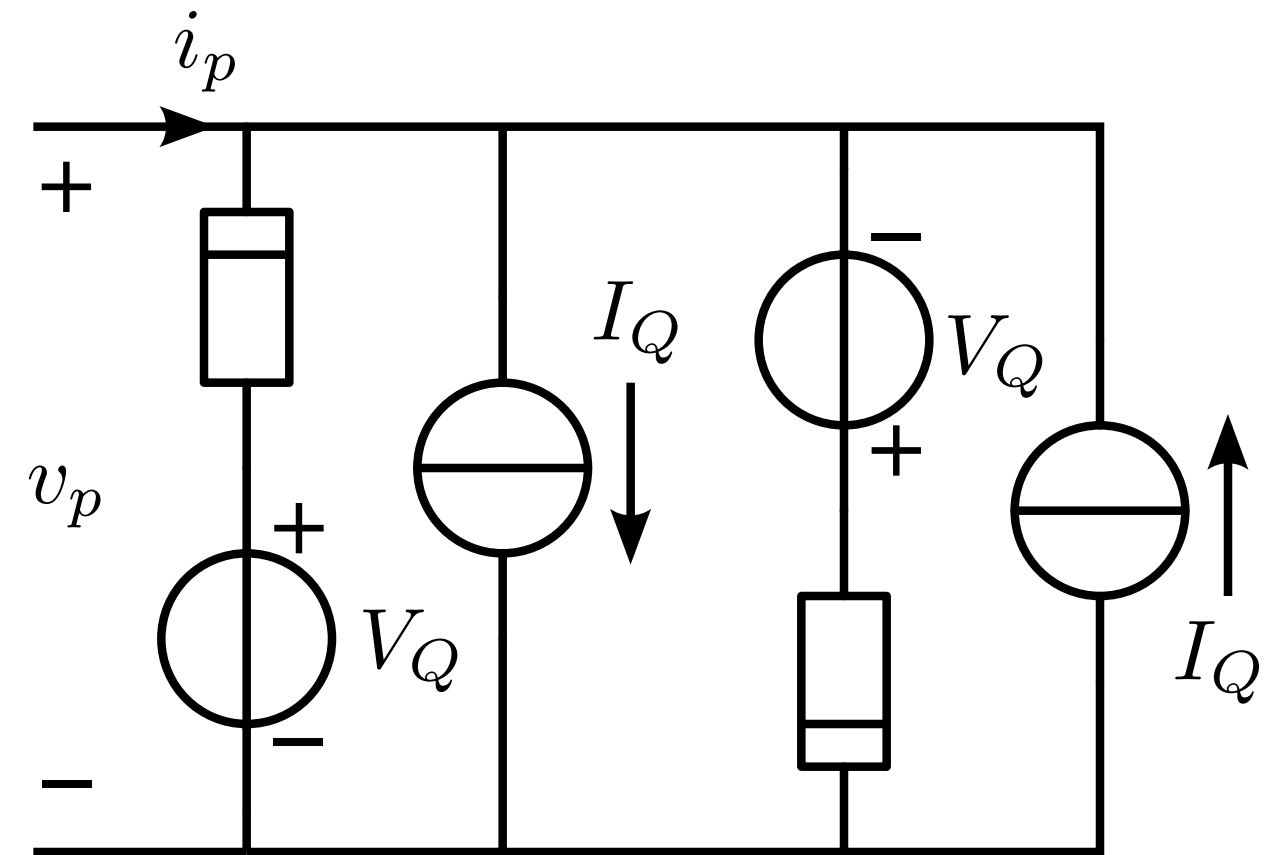
Anti-parallel and complementary-parallel connections



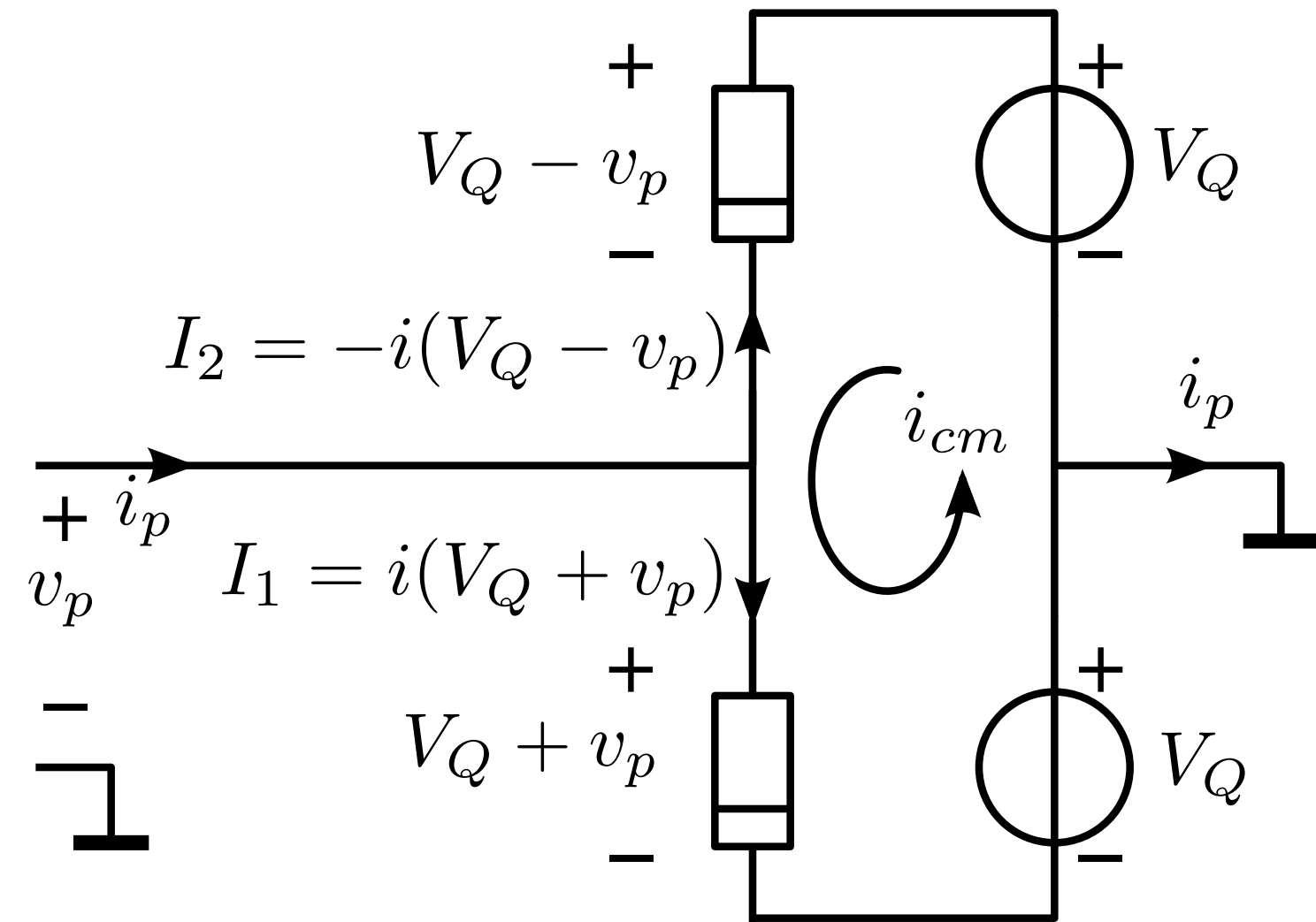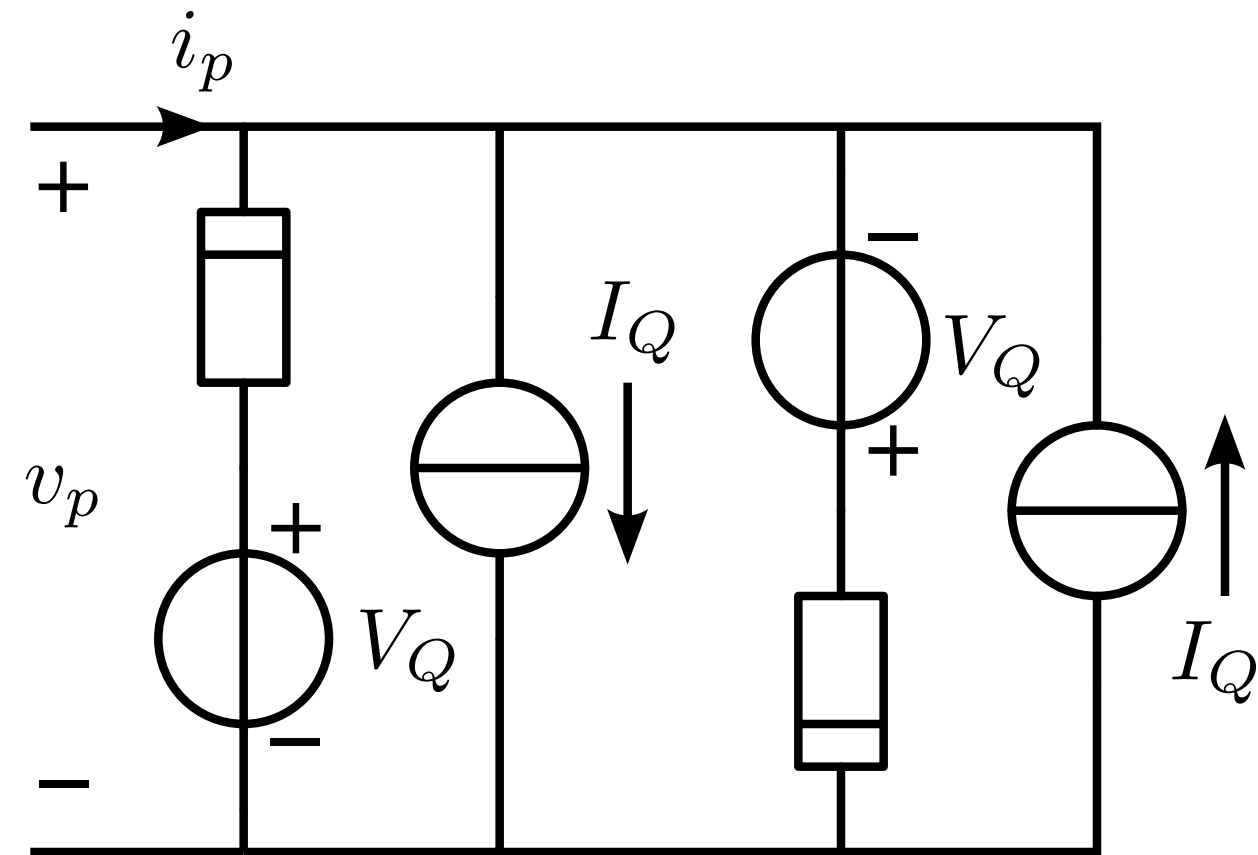Anti-parallel and complementary-parallel connections





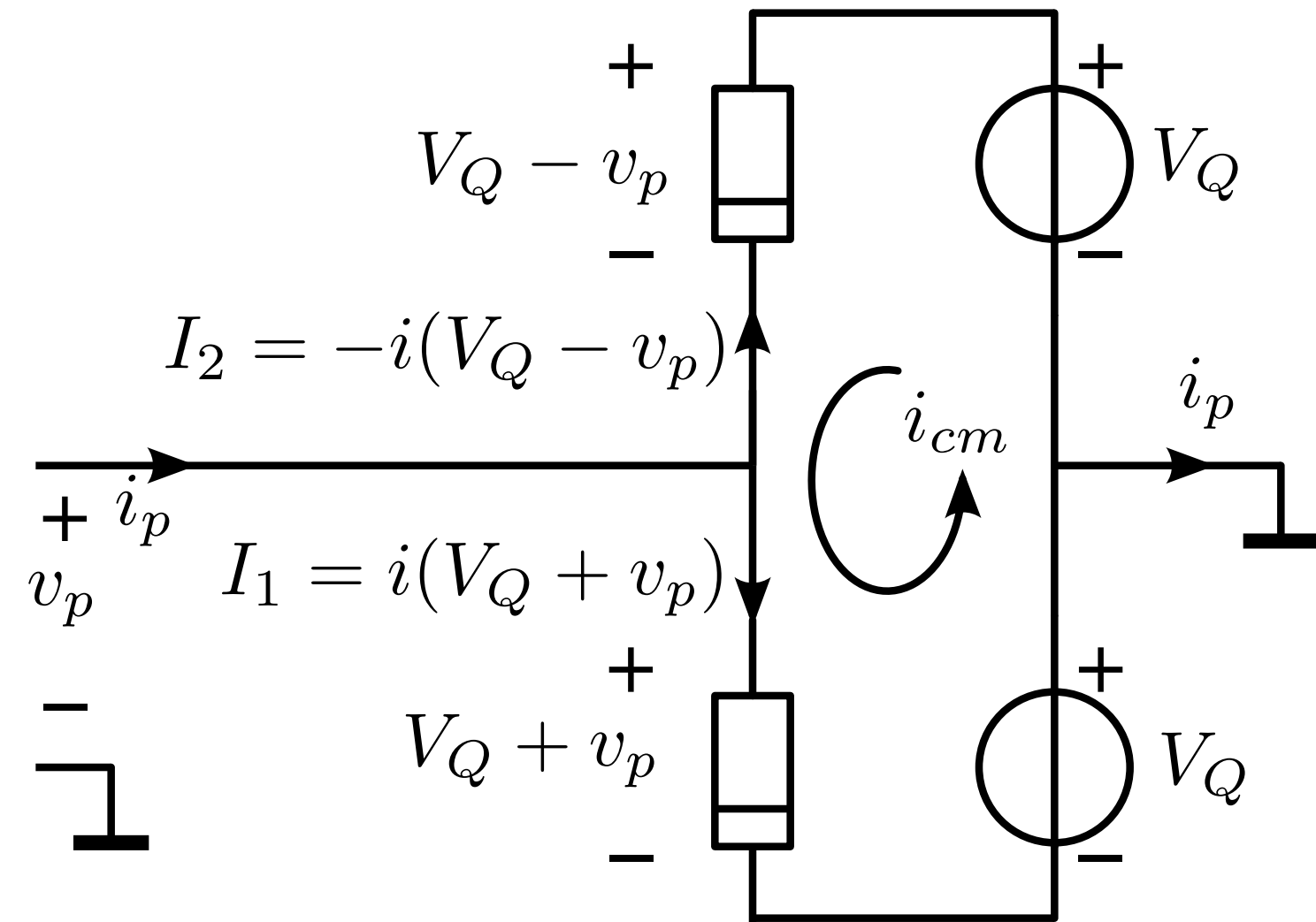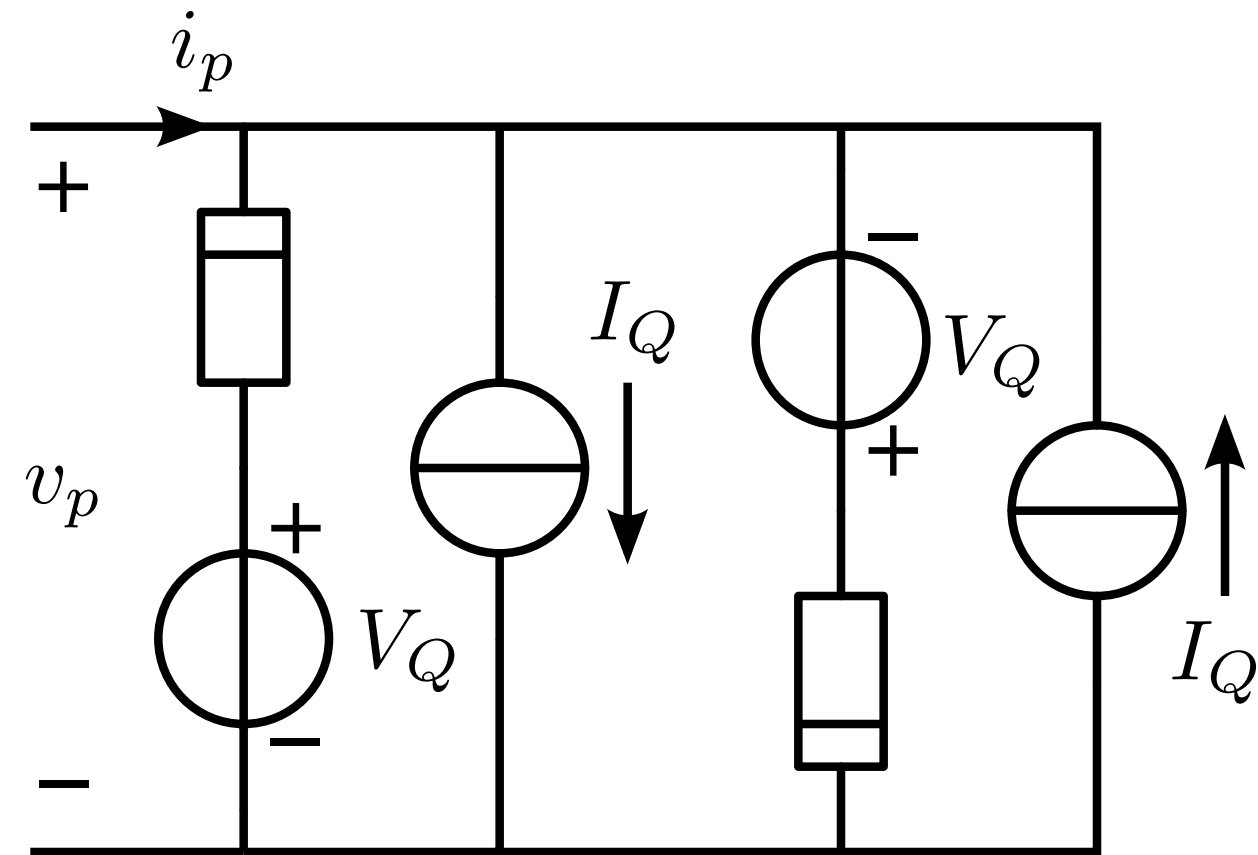Anti-parallel and complementary-parallel connections



Elements can be biased with common-mode voltage sources

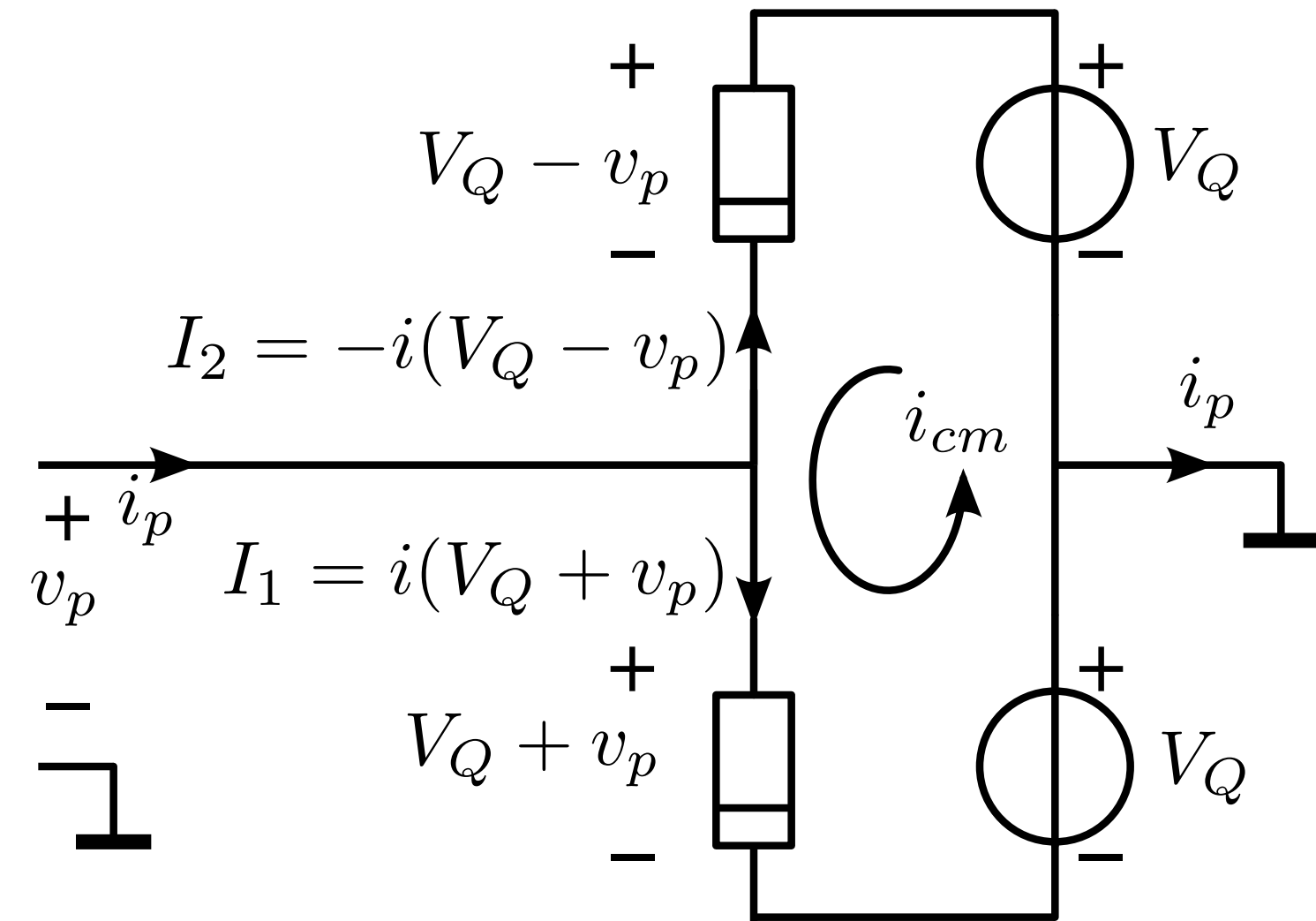
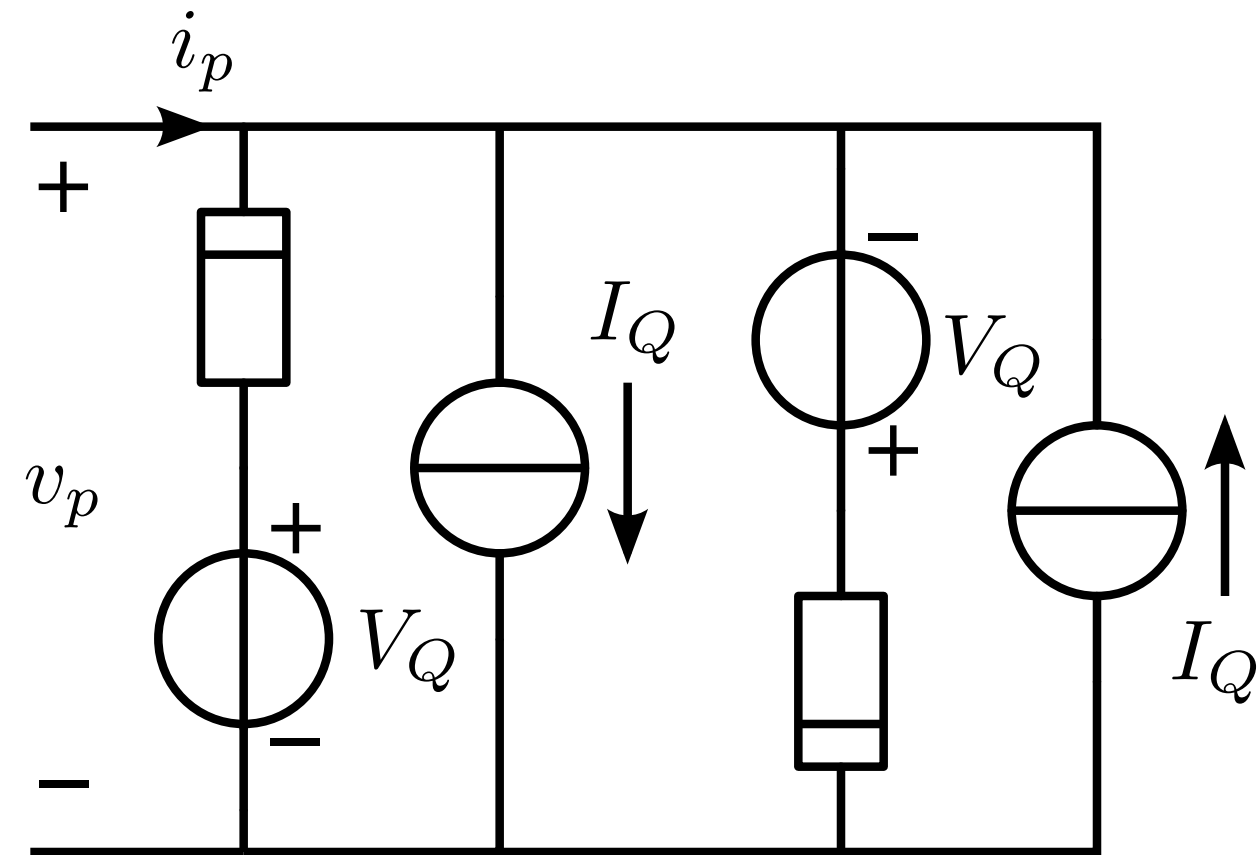
Anti-parallel and complementary-parallel connections



Elements can be biased with common-mode voltage sources

Bias current appears as common-mode current in the circuit

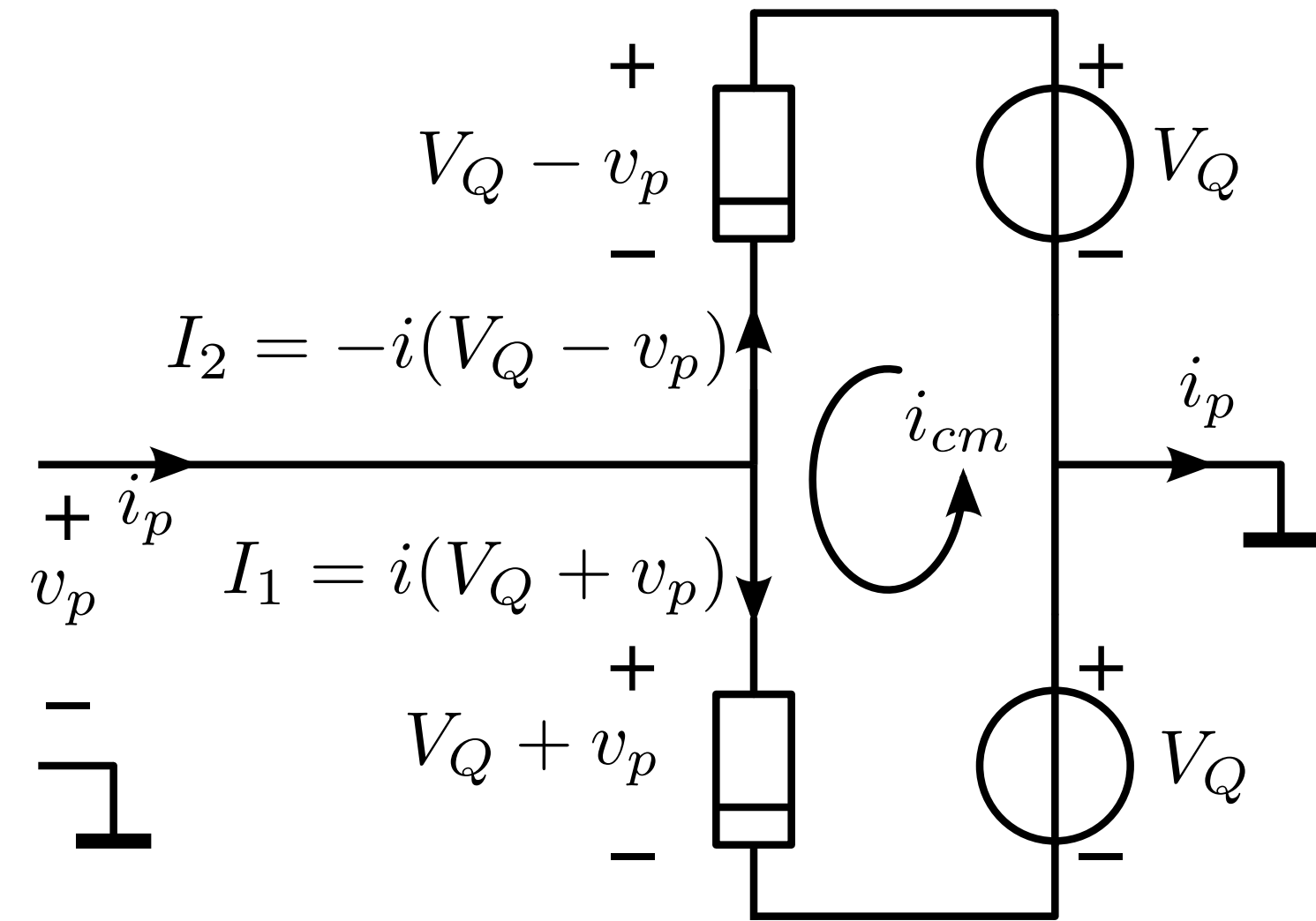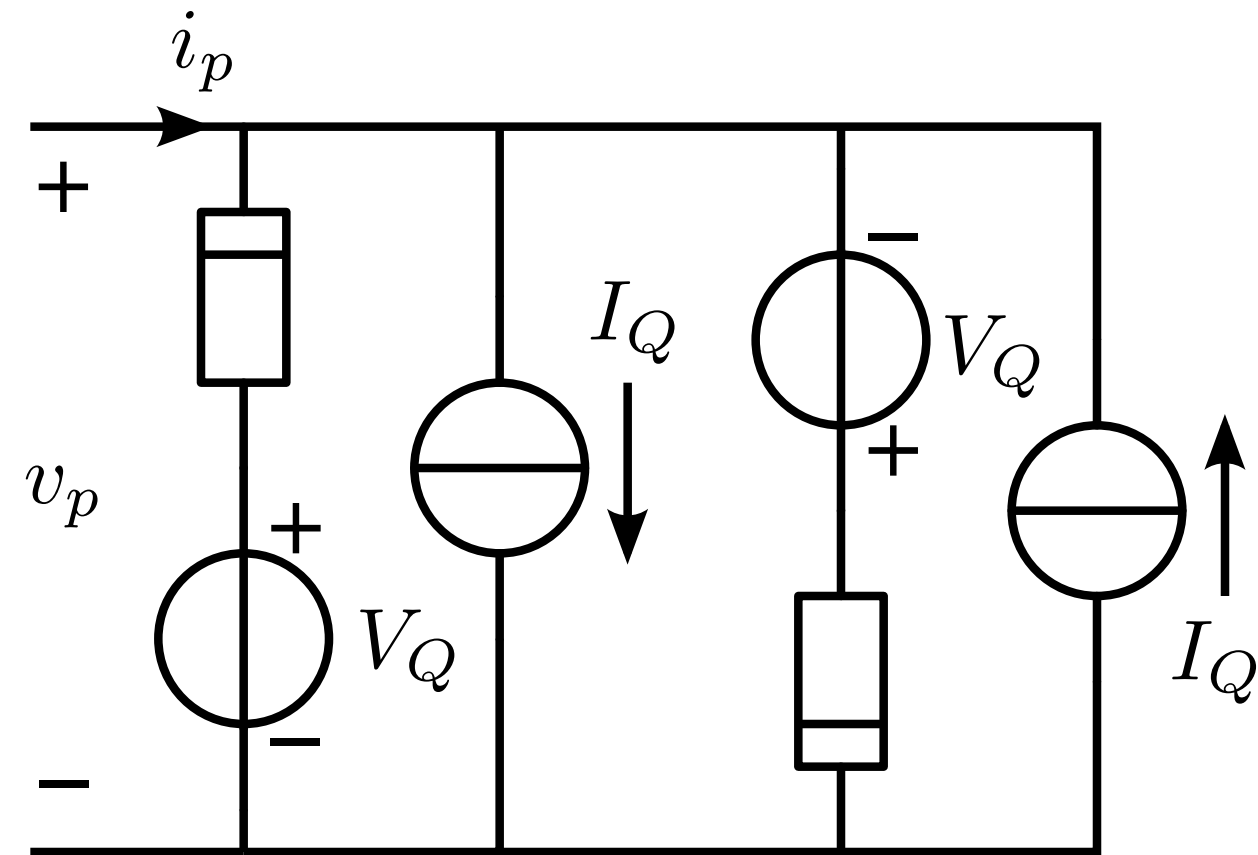Anti-parallel and complementary-parallel connections



Elements can be biased with common-mode voltage sources


Bias current appears as common-mode current in the circuit

Anti-parallel and complementary parallel connections

Small-signal model



Anti-parallel and complementary parallel connections

Small-signal model

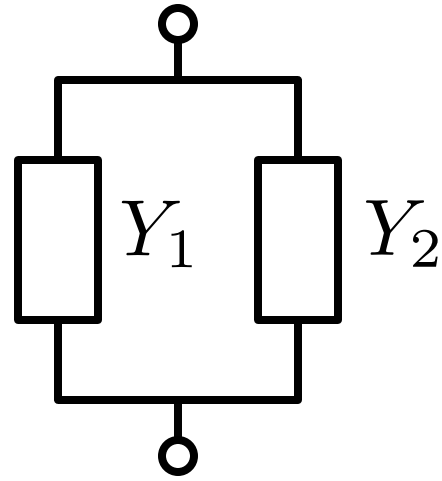



Anti-parallel and complementary parallel connections

Small-signal model

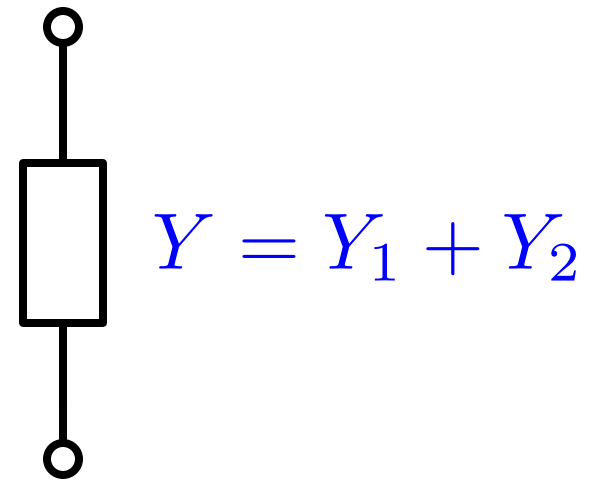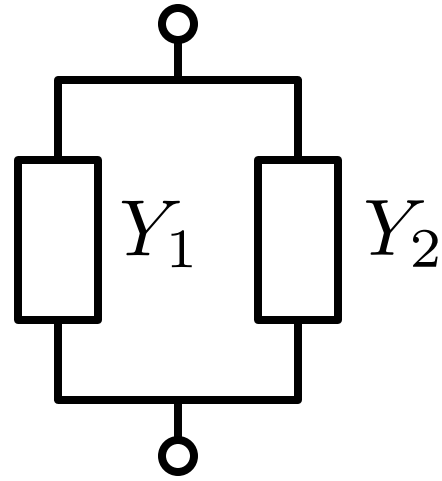

Anti-parallel and complementary parallel connections



Small-signal model

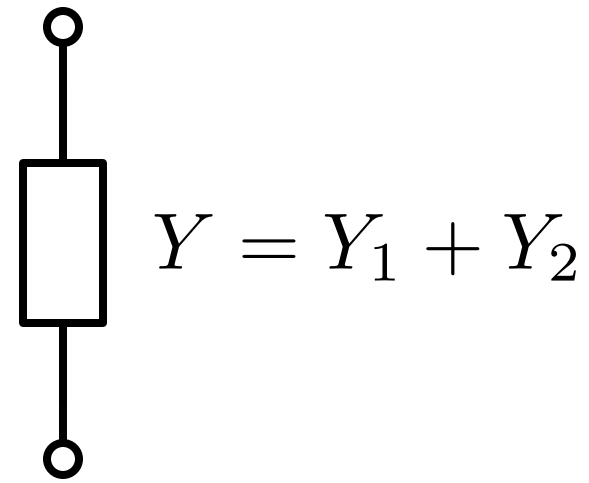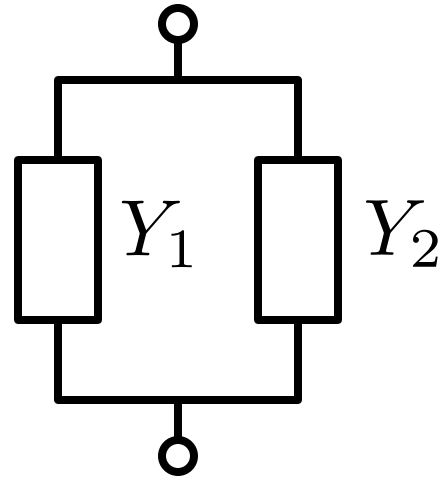

Small-signal admittance is
sum of small-signal
admittances of the
constituting elements

Anti-parallel and complementary parallel connections

Small-signal model

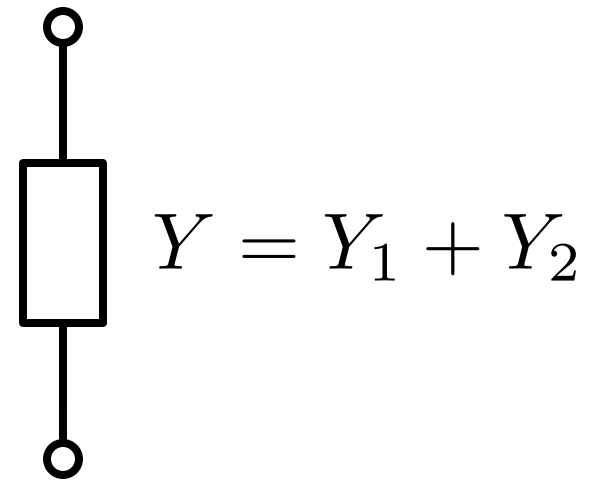
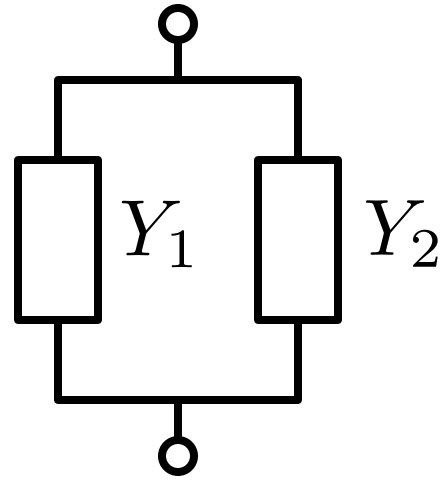


Small-signal admittance is sum of small-signal admittances of the constituting elements

$$Y = 2Y_1 = 2Y_2$$

Anti-parallel and complementary parallel connections

Small-signal model

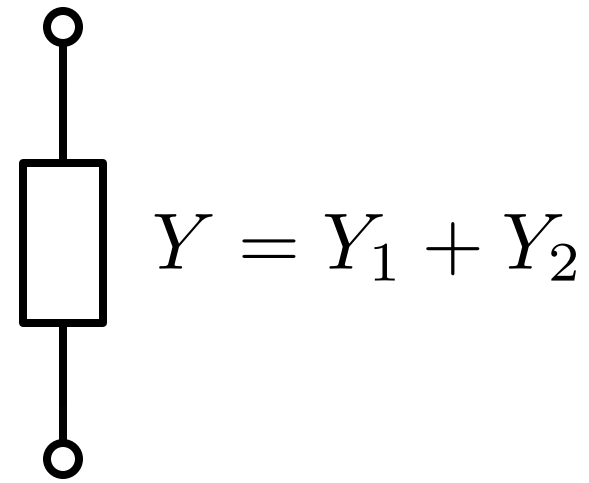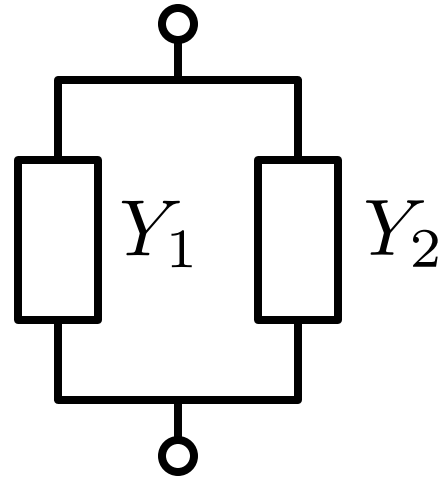



Small-signal admittance is sum of small-signal admittances of the constituting elements

$$Y = 2Y_1 = 2Y_2$$

Twice the admittance in the quiescent operating point

Anti-parallel and complementary parallel connections

Small-signal model

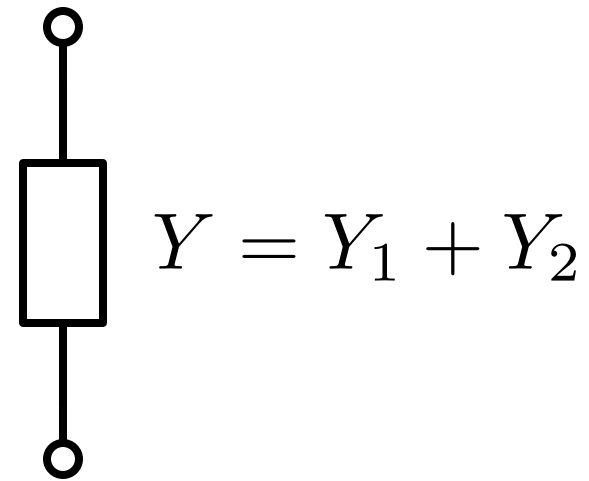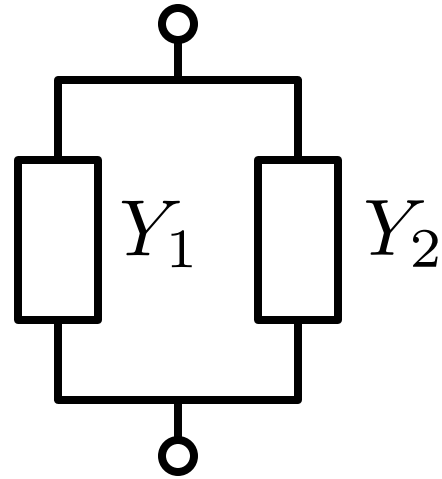

Small-signal admittance is sum of small-signal admittances of the constituting elements



$$Y = 2Y_1 = 2Y_2$$

Twice the admittance in the quiescent operating point

Current noise spectral density is the sum of the current noise spectral densities of the constituting elements

Anti-parallel and complementary parallel connections

Small-signal model

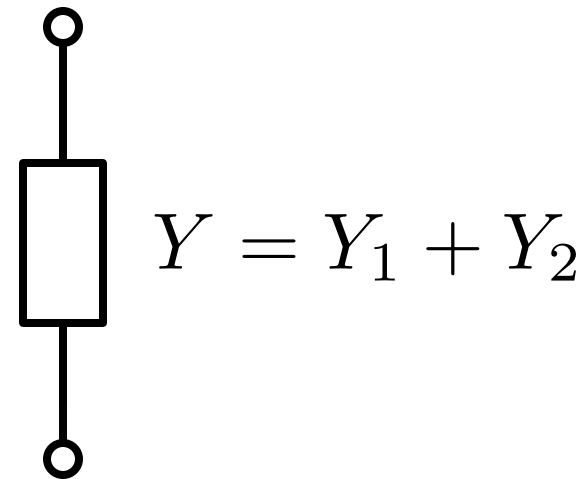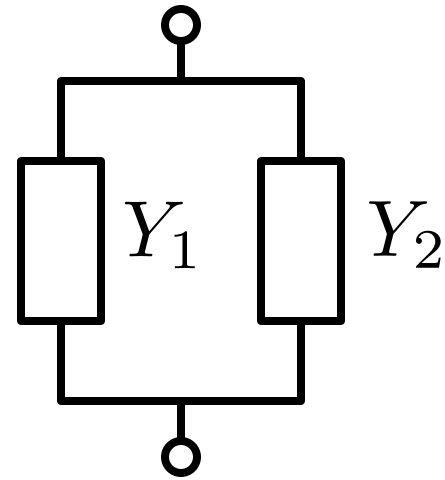


Small-signal admittance is sum of small-signal admittances of the constituting elements

$$Y = 2Y_1 = 2Y_2$$

Twice the admittance in the quiescent operating point

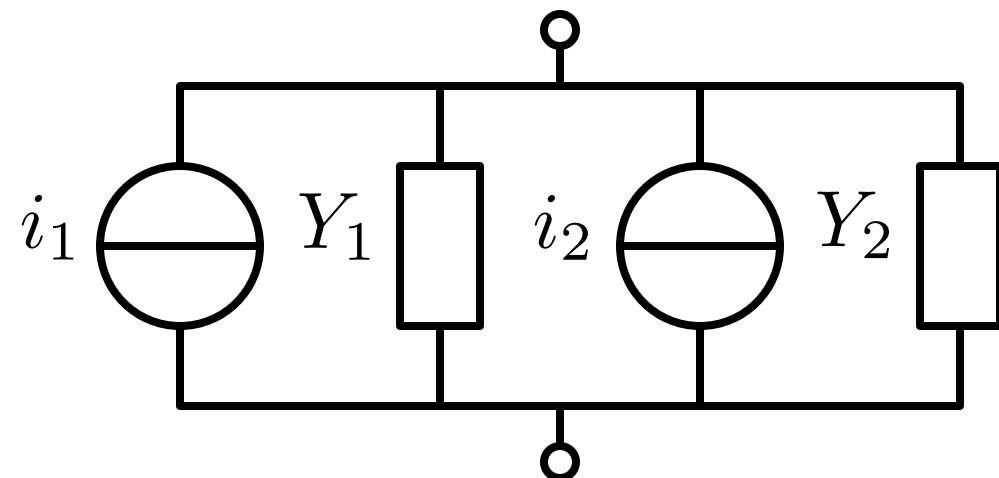Current noise spectral density is the sum of the current noise spectral densities of the constituting elements





$$S_{i_1} = 4kT\text{Re}(Y_1)$$

$$S_{i_2} = 4kT\text{Re}(Y_2)$$

Anti-parallel and complementary parallel connections

Small-signal model

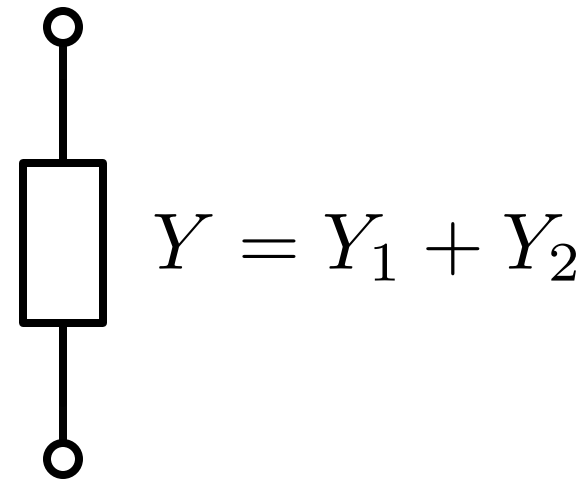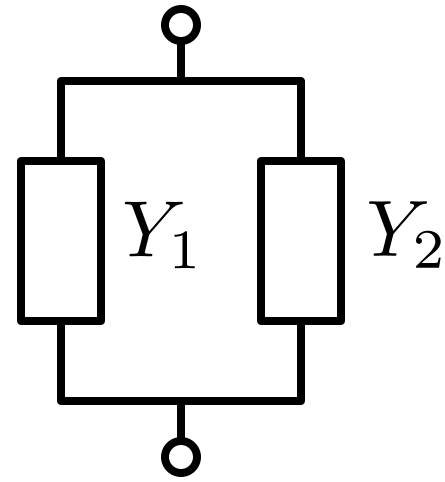


Small-signal admittance is sum of small-signal admittances of the constituting elements

$$Y = 2Y_1 = 2Y_2$$


Twice the admittance in the quiescent operating point

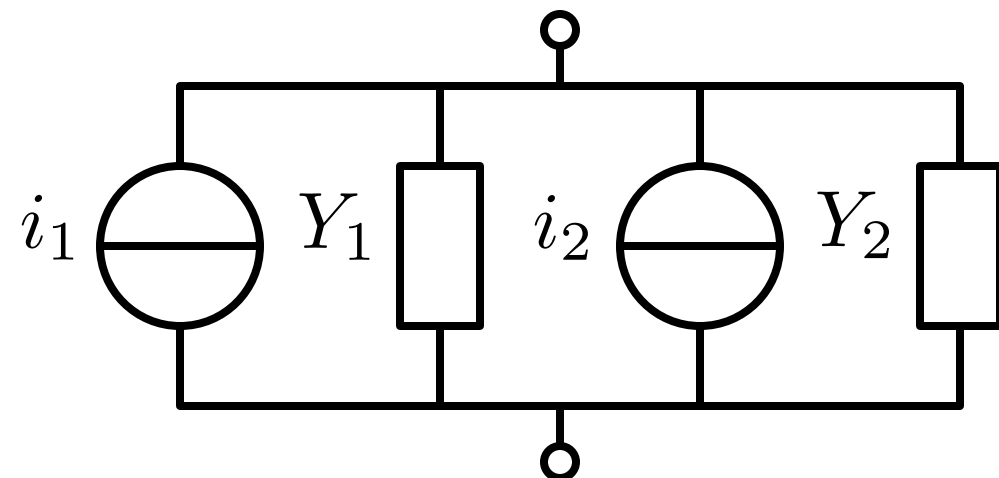Current noise spectral density is the sum of the current noise spectral densities of the constituting elements



$$S_{i_1} = 4kT\text{Re}(Y_1)$$



$$S_{i_2} = 4kT\text{Re}(Y_2)$$

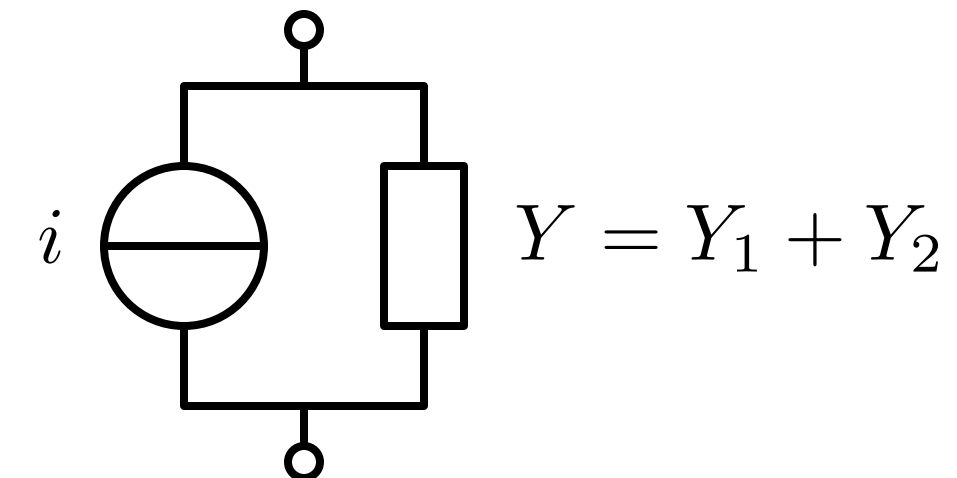

$$S_i = 4kT\text{Re}(Y_1 + Y_2)$$

Anti-parallel and complementary parallel connections

Small-signal model

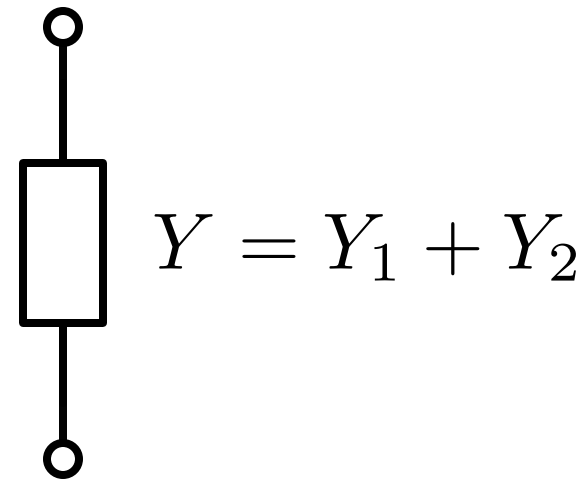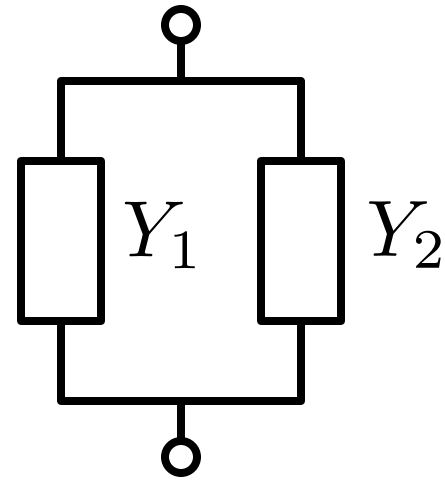


Small-signal admittance is sum of small-signal admittances of the constituting elements

$$Y = 2Y_1 = 2Y_2$$


Twice the admittance in the quiescent operating point

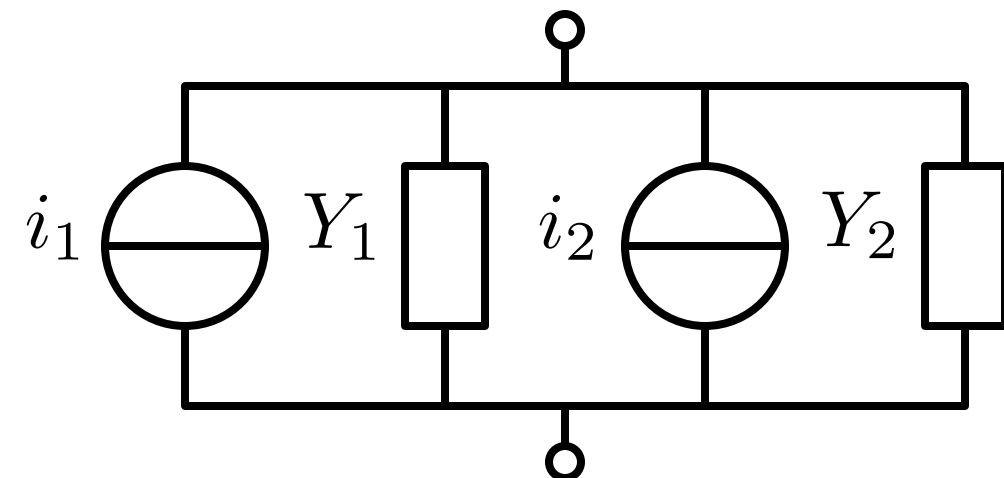Current noise spectral density is the sum of the current noise spectral densities of the constituting elements



$$S_{i_1} = 4kT\text{Re}(Y_1)$$

$$S_{i_2} = 4kT\text{Re}(Y_2)$$

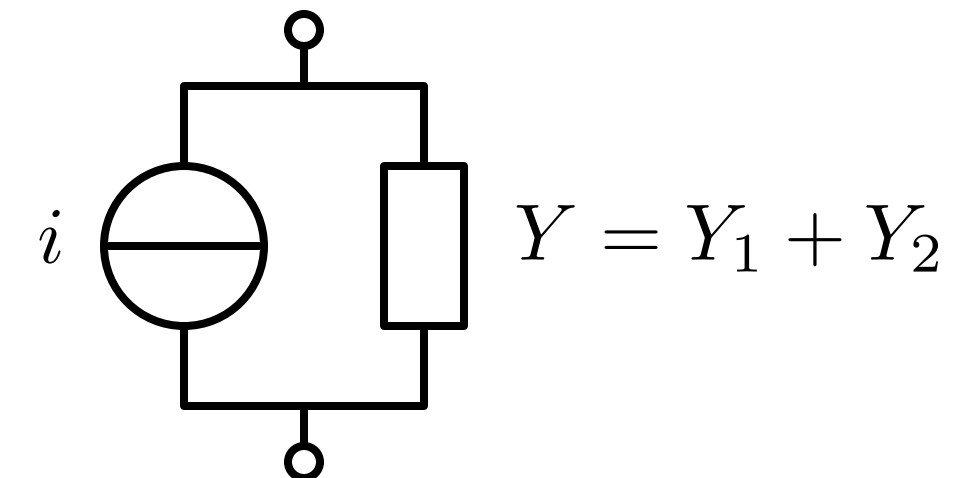

$$S_i = 4kT\text{Re}(Y_1 + Y_2)$$