


# **Structured Electronic Design**

EE4109  
Biasing

*Anton J.M. Montagne*


# Introduction to biasing

# Introduction to biasing

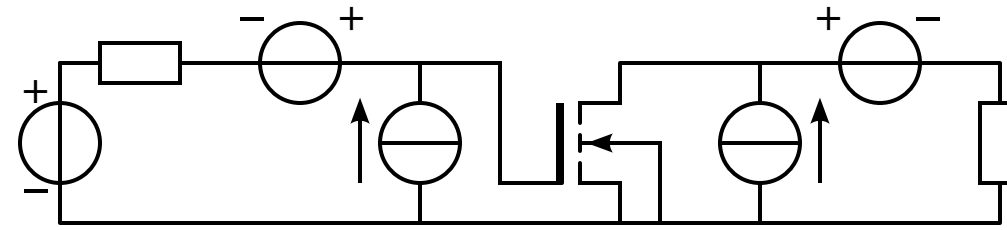


# Introduction to biasing

Values assigned  
during design

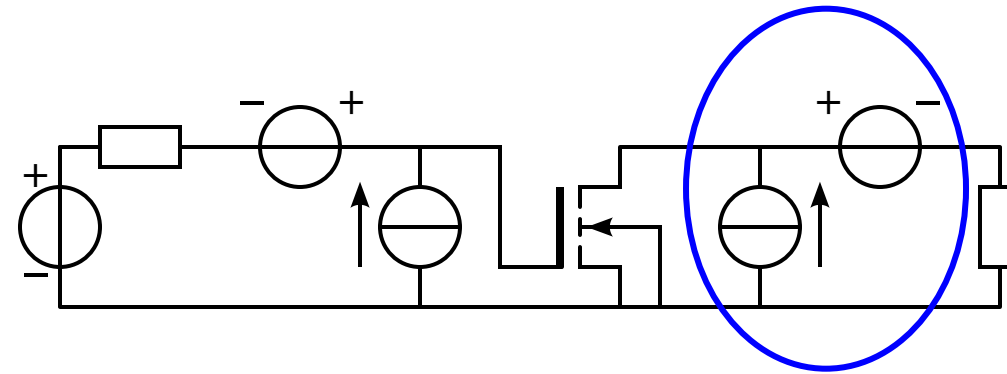

# Introduction to biasing


Values assigned during design

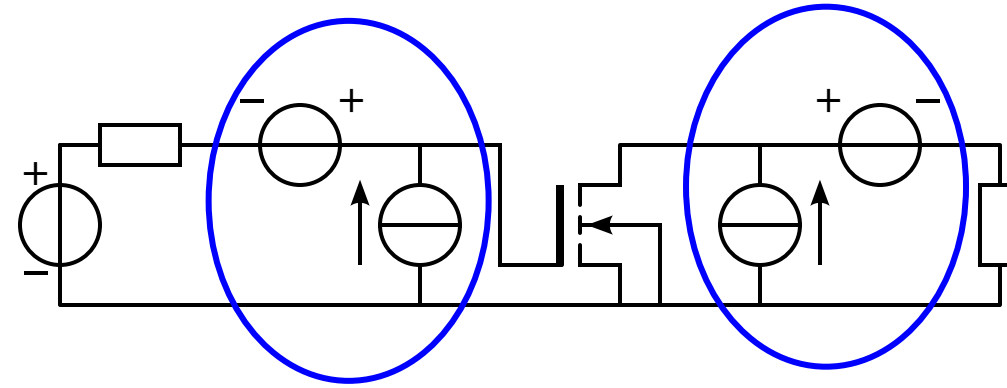

Values depend on

# Introduction to biasing

Values assigned  
during design

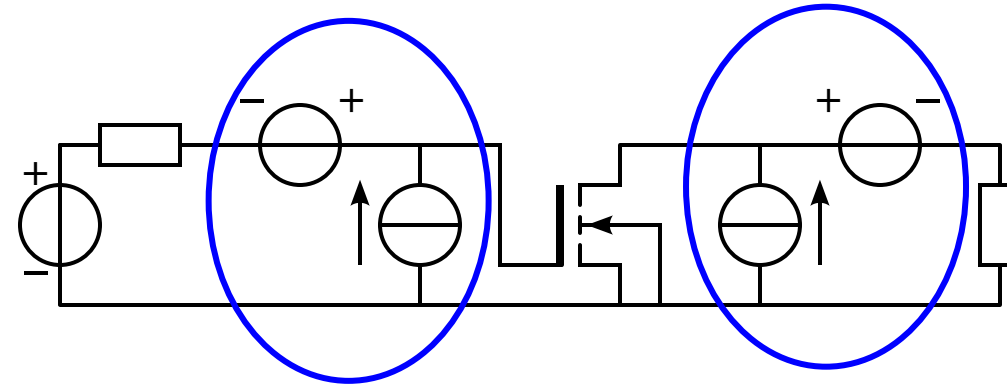


Values depend on

Bias sources at output port

# Introduction to biasing

Values assigned  
during design

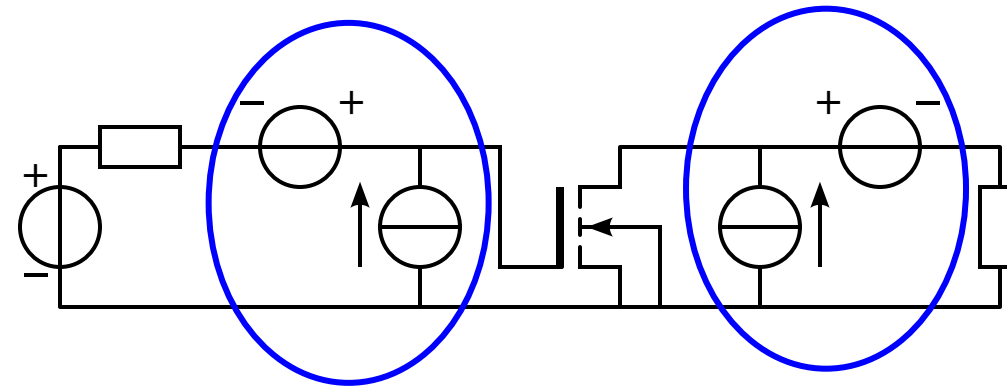


Values depend on

Bias sources at output port

Device characteristics

# Introduction to biasing

Values assigned  
during design

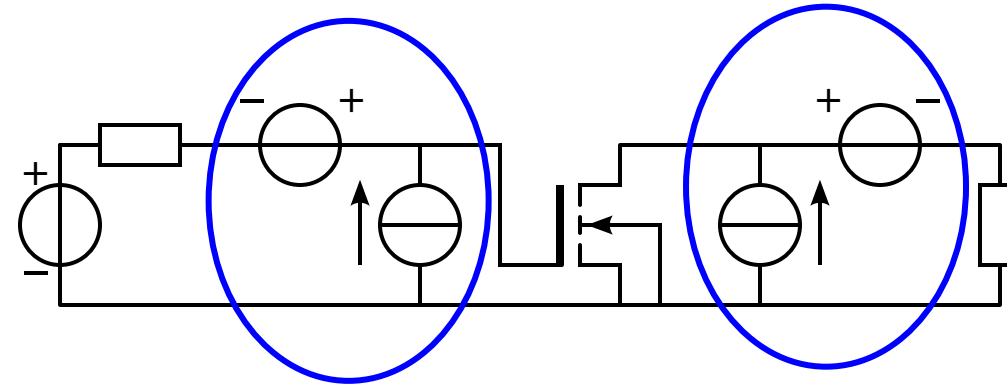

Values depend on

Bias sources at output port


Device characteristics

Temperature



# Introduction to biasing

Values assigned  
during design

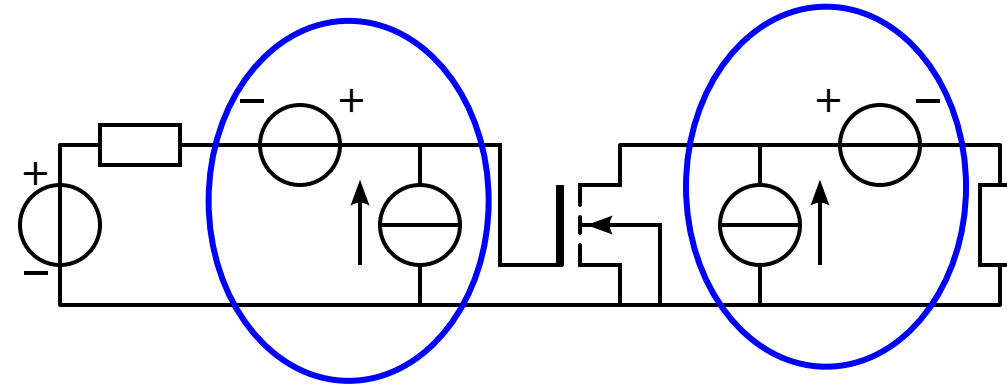


Values depend on

- Bias sources at output port
- Device characteristics
- Temperature

**Biassing**

# Introduction to biasing

Values assigned  
during design

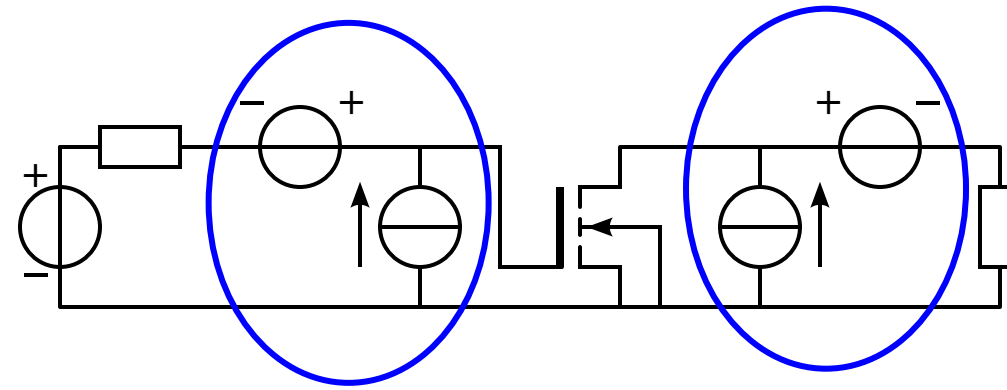

Values depend on


- Bias sources at output port
- Device characteristics
- Temperature

## Biasing

Set the operating voltages and currents of the devices

# Introduction to biasing

Values assigned  
during design

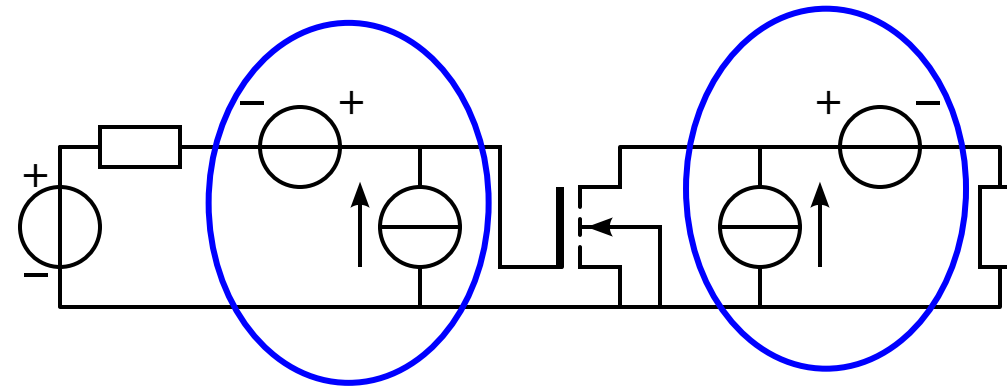

Values depend on

- Bias sources at output port
- Device characteristics
- Temperature


## Biasing

Set the operating voltages and currents of the devices

Derive required voltages and currents from the power supply voltage

# Introduction to biasing

Values assigned  
during design

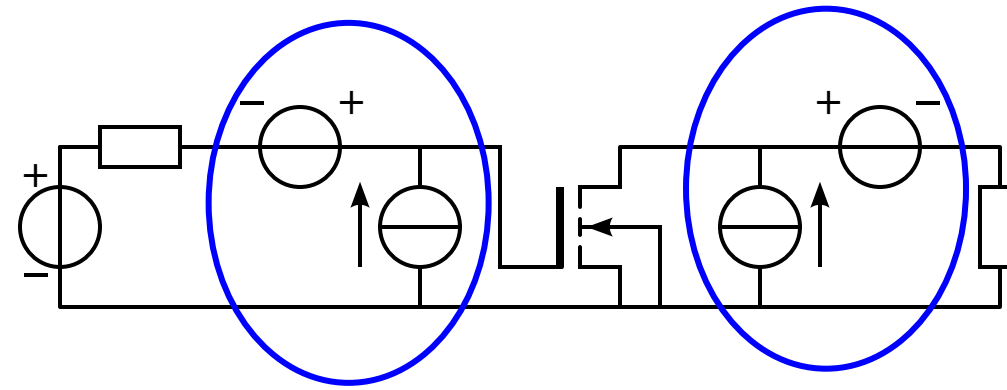

Values depend on

- Bias sources at output port
- Device characteristics
- Temperature

## Biasing

Set the operating voltages and currents of the devices

Derive required voltages and currents from the power supply voltage

# Introduction to biasing

# Introduction to biasing

Biasing is known to be difficult

# Introduction to biasing

Biasing is known to be difficult

Experienced designers concurrently design biasing and signal path

# Introduction to biasing

Biasing is known to be difficult

Experienced designers concurrently design biasing and signal path

Can be understood if all methods and techniques are presented in a structured way



# Introduction to biasing

Biasing is known to be difficult

Experienced designers concurrently design biasing and signal path

Can be understood if all methods and techniques are presented in a structured way

So that's what we will do!

# Introduction to biasing

Biasing is known to be difficult

Experienced designers concurrently design biasing and signal path

Can be understood if all methods and techniques are presented in a structured way

So that's what we will do!



# Design of biasing concept

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements



# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

Define CM bias voltage(s) and/or current(s)

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

Define CM bias voltage(s) and/or current(s)

[Brute-force CM biasing](#)

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

Define CM bias voltage(s) and/or current(s)

Brute-force CM biasing

[Model-based CM biasing](#)

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

Define CM bias voltage(s) and/or current(s)

Brute-force CM biasing

Model-based CM biasing

Negative feedback CM biasing

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

- Define CM bias voltage(s) and/or current(s)

  - Brute-force CM biasing

  - Model-based CM biasing

  - Negative feedback CM biasing

If differential-mode bias voltages and current are not well-defined:

- Define DM bias voltage(s) and/or current(s)

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

- Define CM bias voltage(s) and/or current(s)

  - Brute-force CM biasing

  - Model-based CM biasing

  - Negative feedback CM biasing

If differential-mode bias voltages and current are not well-defined:

- Define DM bias voltage(s) and/or current(s)

  - Brute-force DM biasing

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

- Define CM bias voltage(s) and/or current(s)

  - Brute-force CM biasing

  - Model-based CM biasing

  - Negative feedback CM biasing

If differential-mode bias voltages and current are not well-defined:

- Define DM bias voltage(s) and/or current(s)

  - Brute-force DM biasing

  - Model-based DM biasing



# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

Define CM bias voltage(s) and/or current(s)

Brute-force CM biasing

Model-based CM biasing

Negative feedback CM biasing

If differential-mode bias voltages and current are not well-defined:

Define DM bias voltage(s) and/or current(s)

Brute-force DM biasing

Model-based DM biasing

Negative feedback DM biasing

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

Define CM bias voltage(s) and/or current(s)

Brute-force CM biasing

Model-based CM biasing

Negative feedback CM biasing

If differential-mode bias voltages and current are not well-defined:

Define DM bias voltage(s) and/or current(s)

Brute-force DM biasing

Model-based DM biasing

Negative feedback DM biasing

AC signal coupling and DC (low-pass) bias feedback over the largest possible number of stages

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

- Define CM bias voltage(s) and/or current(s)

  - Brute-force CM biasing

  - Model-based CM biasing

  - Negative feedback CM biasing

If differential-mode bias voltages and current are not well-defined:

- Define DM bias voltage(s) and/or current(s)

  - Brute-force DM biasing

  - Model-based DM biasing

  - Negative feedback DM biasing

    - AC signal coupling and DC (low-pass) bias feedback over the largest possible number of stages

    - [Auto-zero biasing](#)

# Design of biasing concept

Connect the (conceptually biased) circuit to the power supply

Redirect the current sources over the power supply

Minimize the number of floating bias voltage sources

Replace ideal sources with passive biasing elements and complete the biasing concept

Set-up specifications for biasing elements

If common-mode bias voltages and current are not well-defined:

- Define CM bias voltage(s) and/or current(s)

  - Brute-force CM biasing

  - Model-based CM biasing

  - Negative feedback CM biasing

If differential-mode bias voltages and current are not well-defined:

- Define DM bias voltage(s) and/or current(s)

  - Brute-force DM biasing

  - Model-based DM biasing

  - Negative feedback DM biasing

    - AC signal coupling and DC (low-pass) bias feedback over the largest possible number of stages

    - Auto-zero biasing


Connect the biased circuit to the power supply

# Connect the biased circuit to the power supply

Initial CS-stage biasing

# Connect the biased circuit to the power supply

## Initial CS-stage biasing

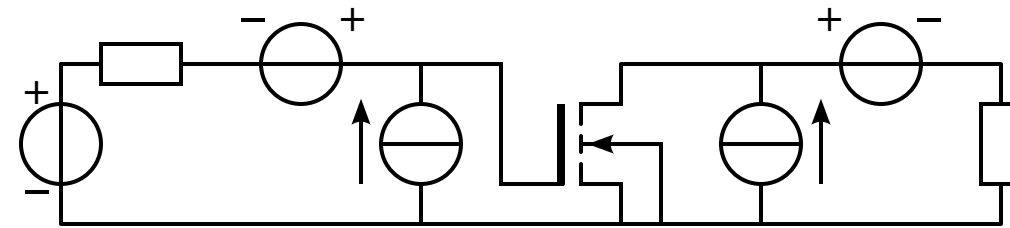


# Connect the biased circuit to the power supply

Connected to supply




# Connect the biased circuit to the power supply

Connected to supply

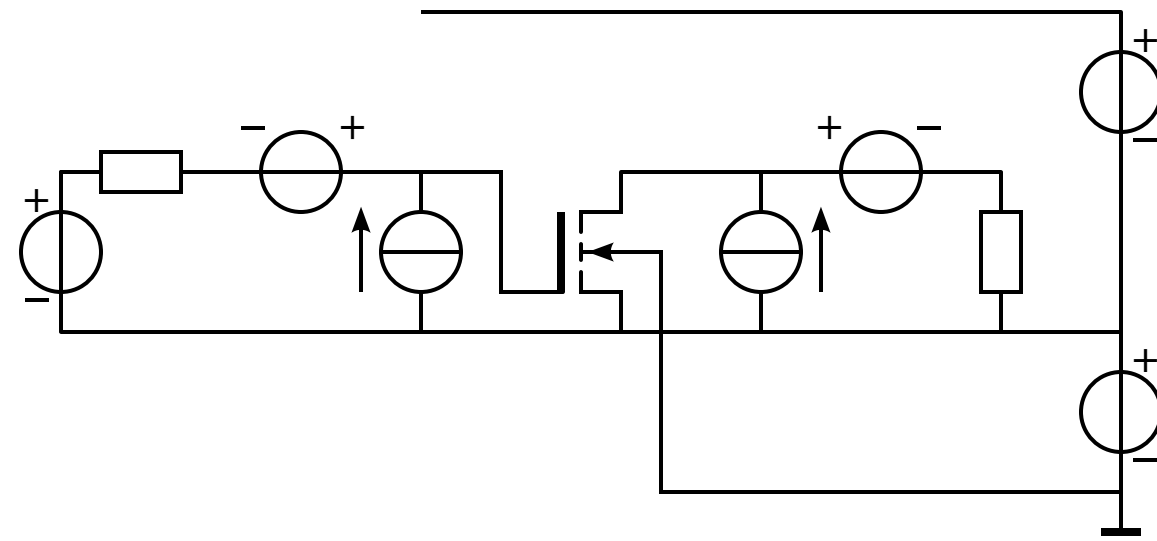

# Connect the biased circuit to the power supply


Connected to supply

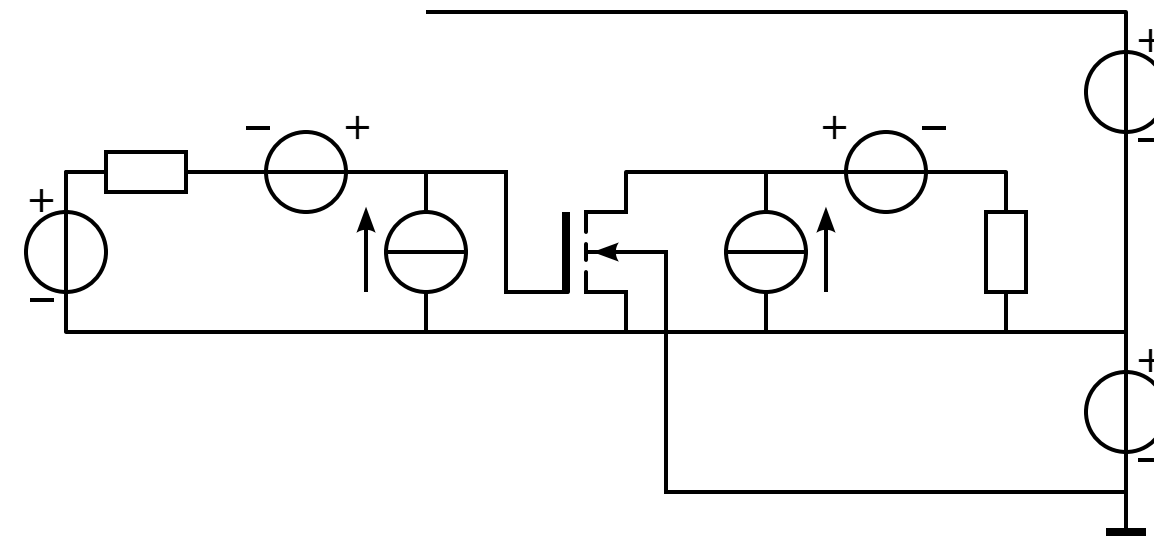

For all signal levels:

# Connect the biased circuit to the power supply

Connected to supply

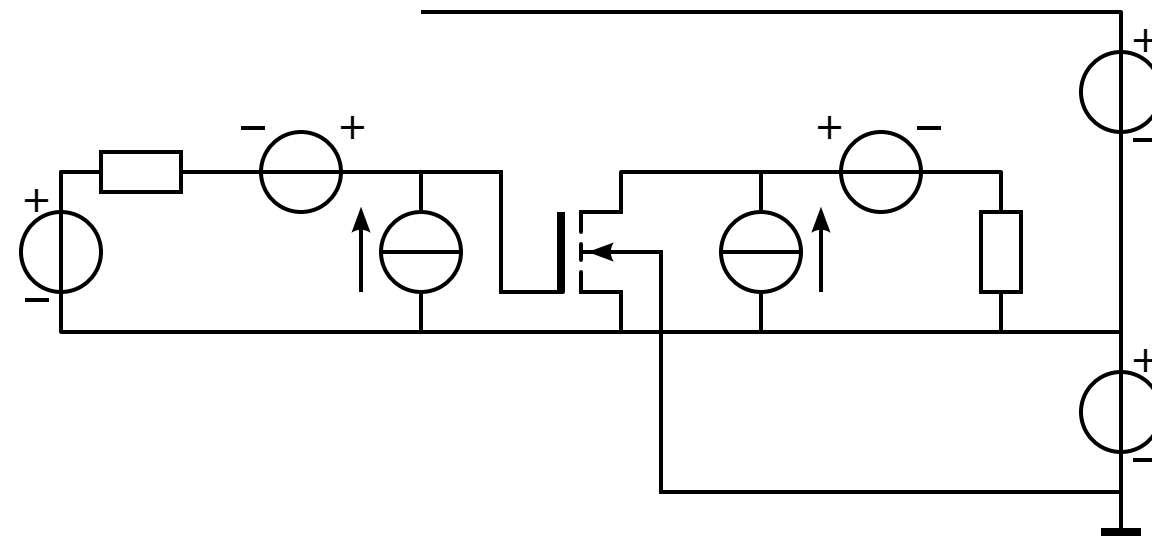


For all signal levels:

Nodal voltages should be within valid range

# Connect the biased circuit to the power supply

Connected to supply

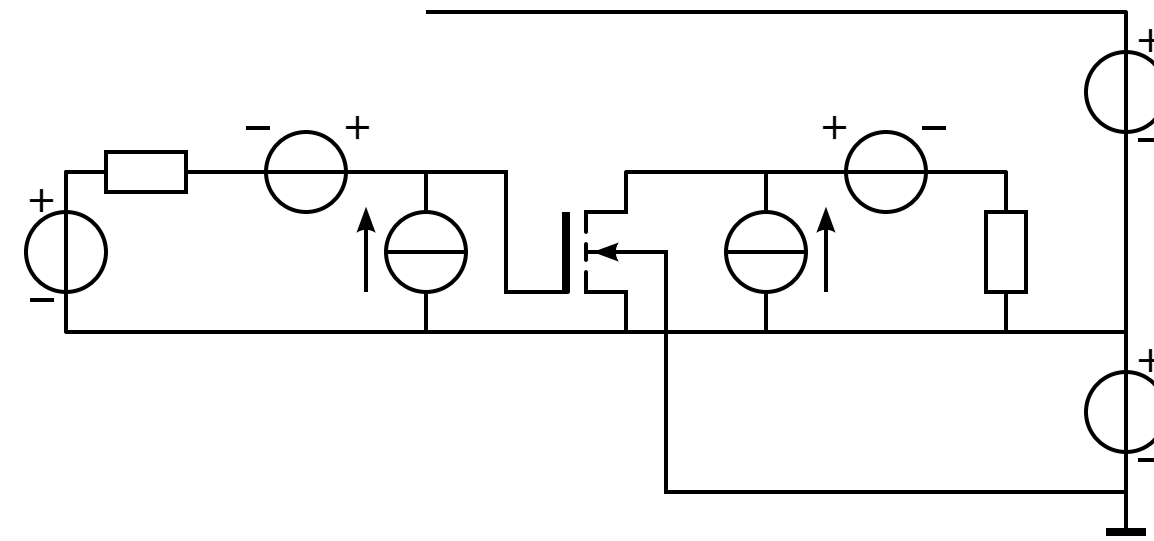


For all signal levels:


Nodal voltages should be within valid range

# Redirect bias current sources

# Redirect bias current sources

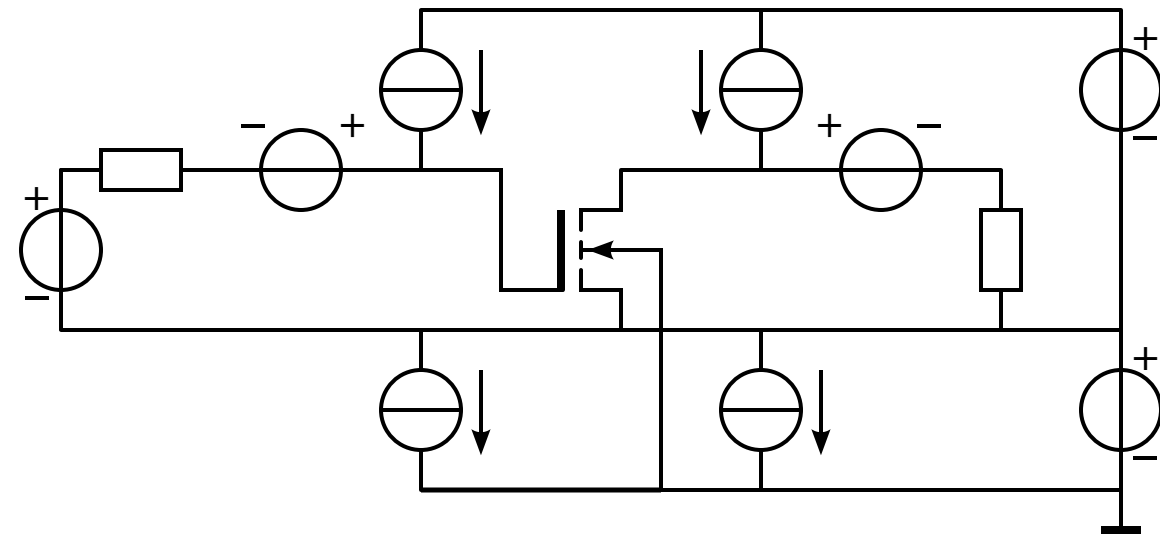


# Redirect bias current sources

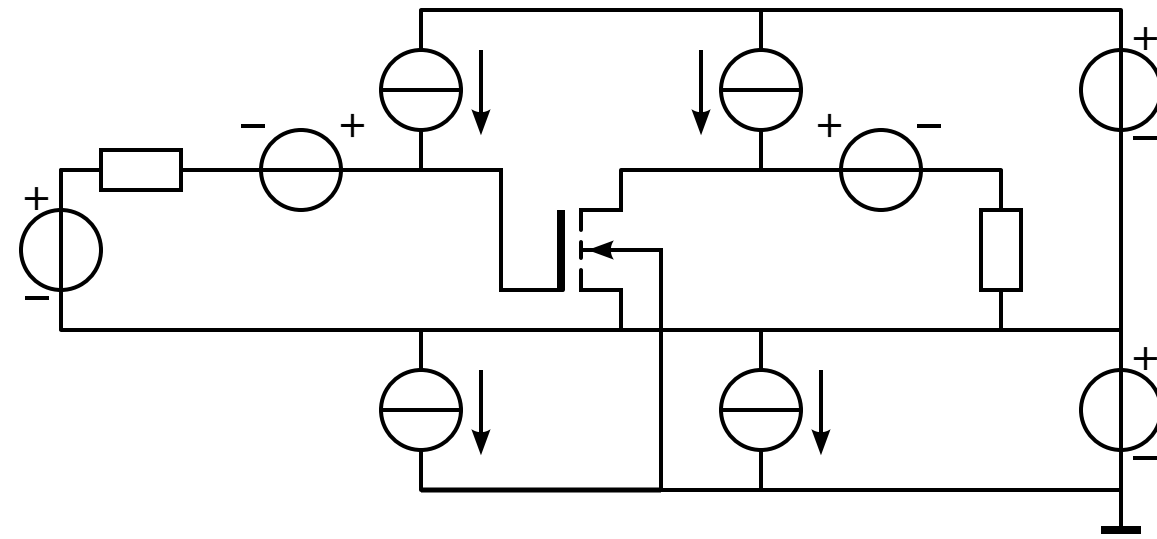

Sources can be implemented with passive devices

# Redirect bias current sources

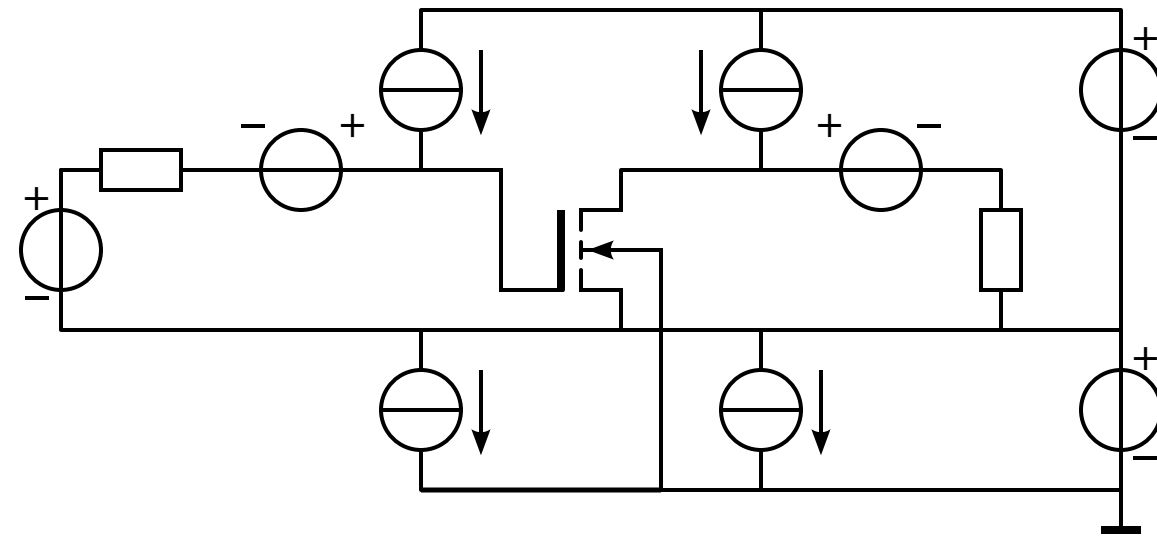


Sources can be implemented with passive devices




# Minimize the number of floating voltage sources

Consider a two-stage amplifier

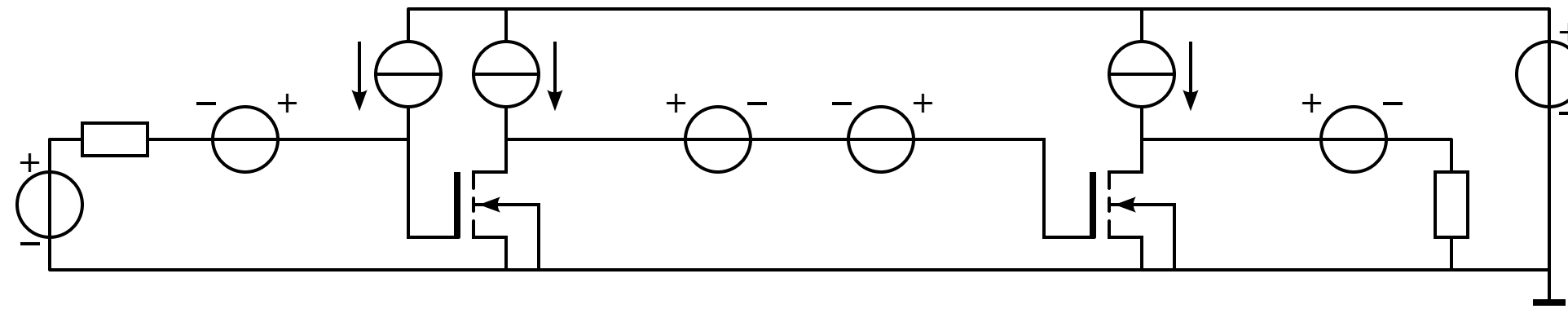


# Minimize the number of floating voltage sources

Change the voltage level of a stage

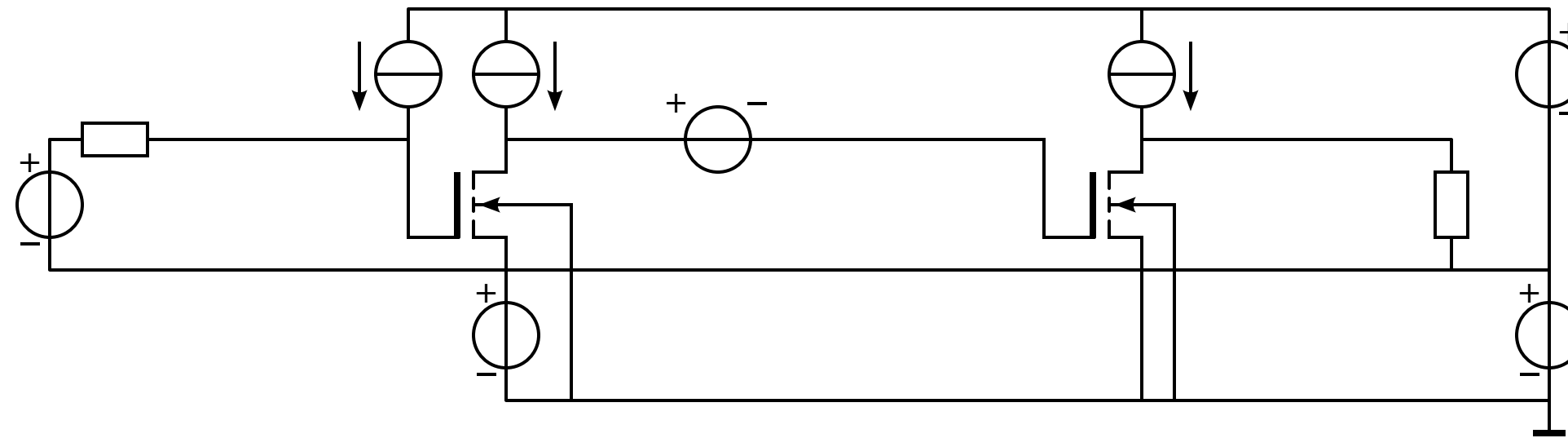

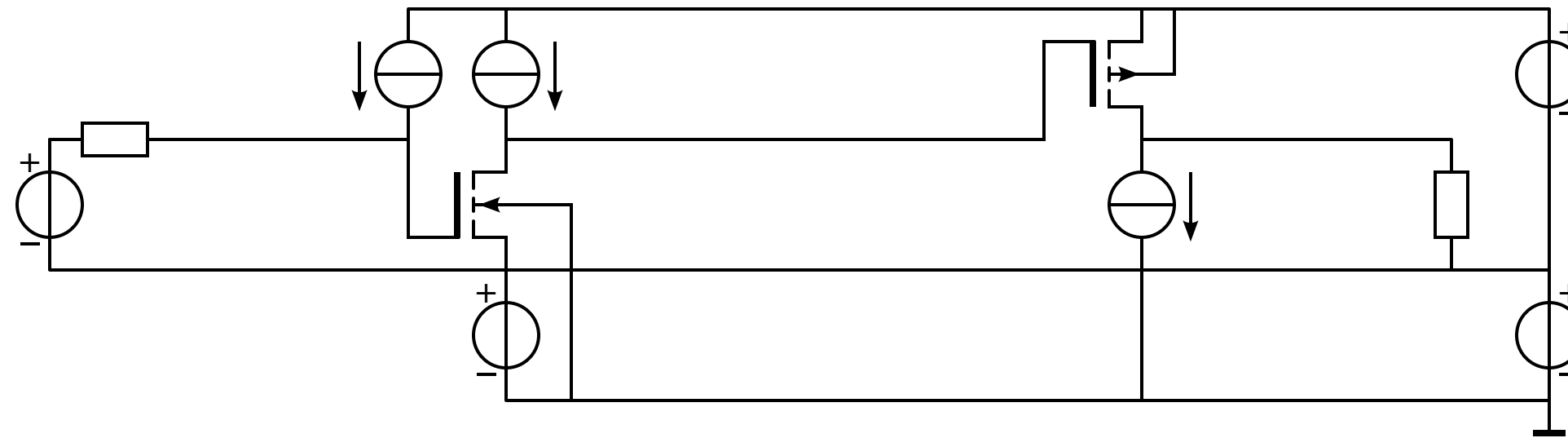
# Minimize the number of floating voltage sources

Replace a device with its complementary version



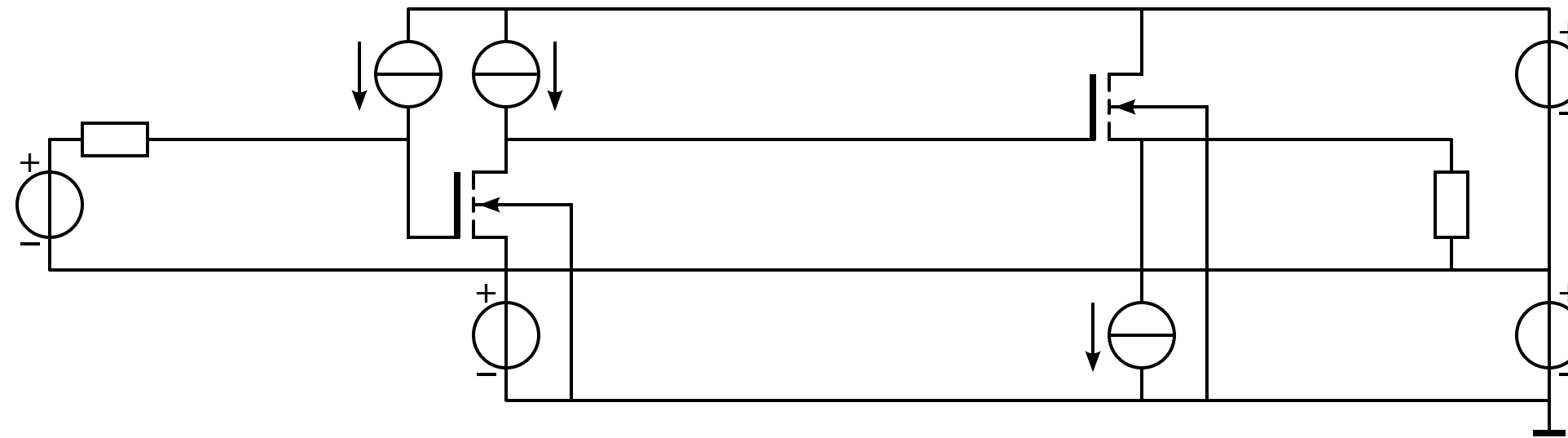
# Minimize the number of floating voltage sources

Replace a stage with a local feedback stage



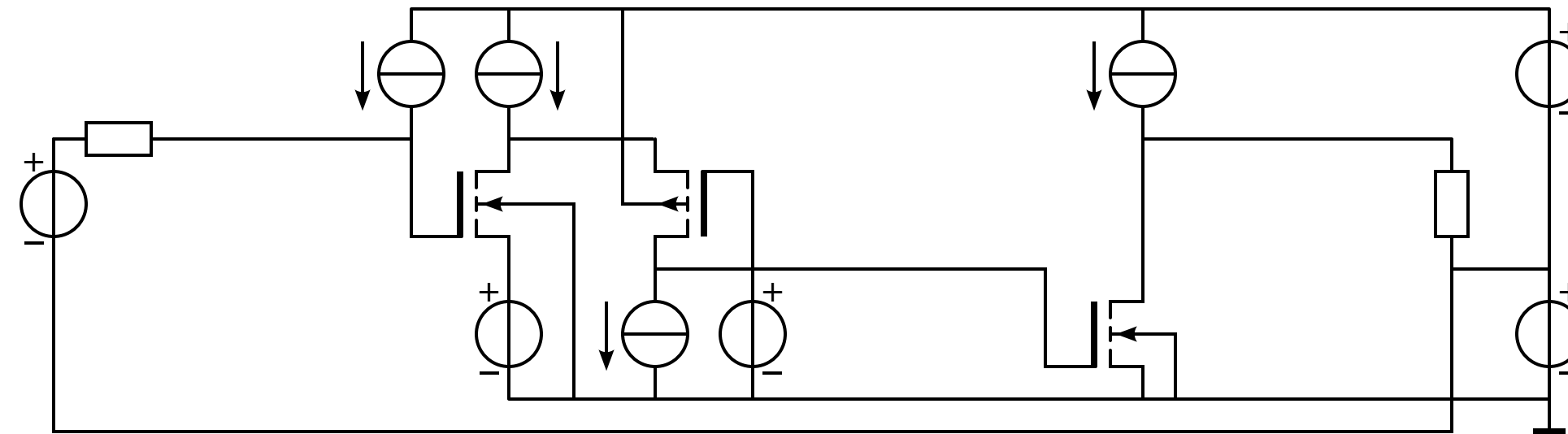
# Minimize the number of floating voltage sources

Add a local feedback stage and use a complementary type


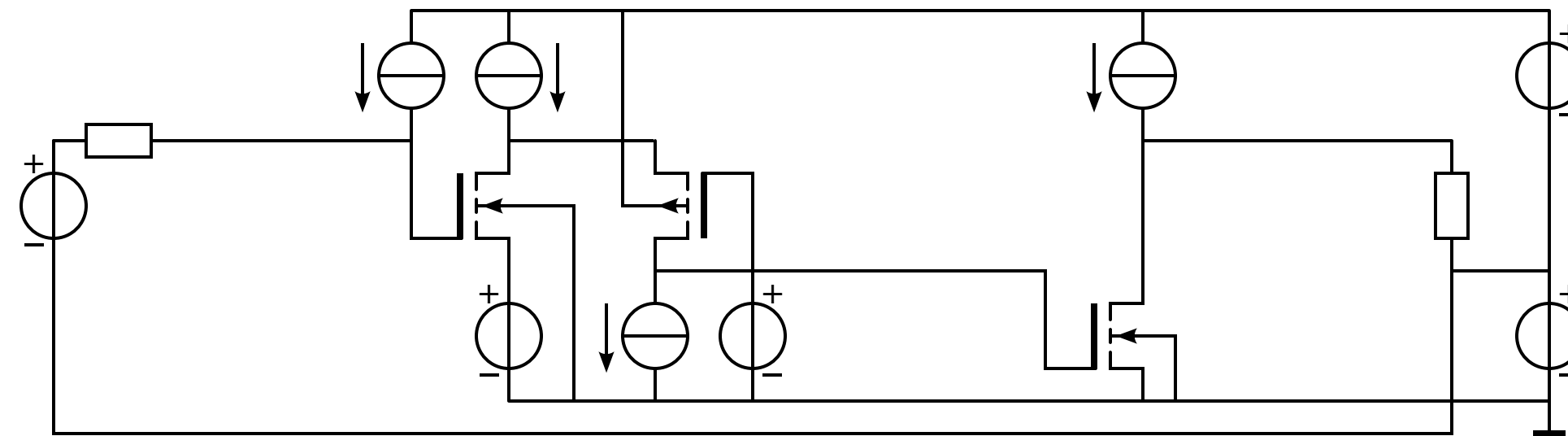
# Minimize the number of floating voltage sources


Add a local feedback stage and use a complementary type



"Folded cascode"
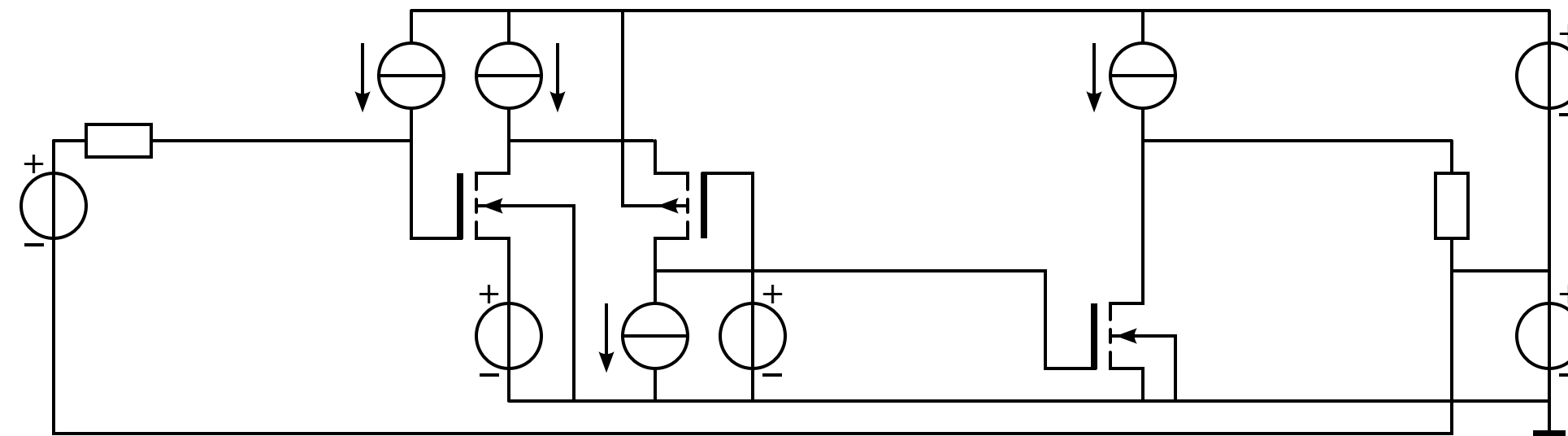
# Minimize the number of floating voltage sources

Add a local feedback stage and use a complementary type



"Folded cascode"

# Complete biasing concept with passive biasing elements




# Complete biasing concept with passive biasing elements

## Nonlinear resistive elements


# Complete biasing concept with passive biasing elements

## Nonlinear resistive elements

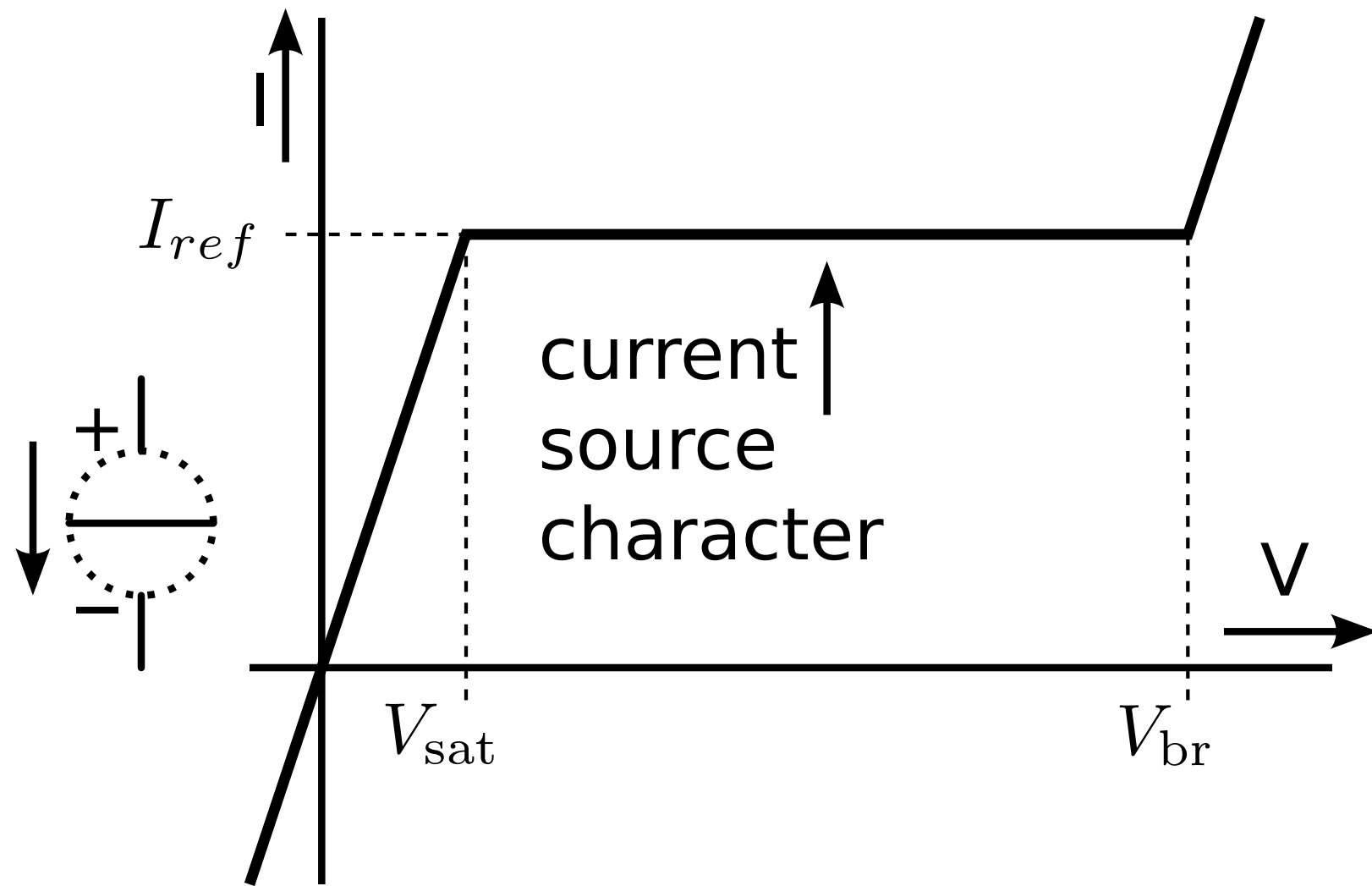

# Complete biasing concept with passive biasing elements


## Nonlinear resistive elements

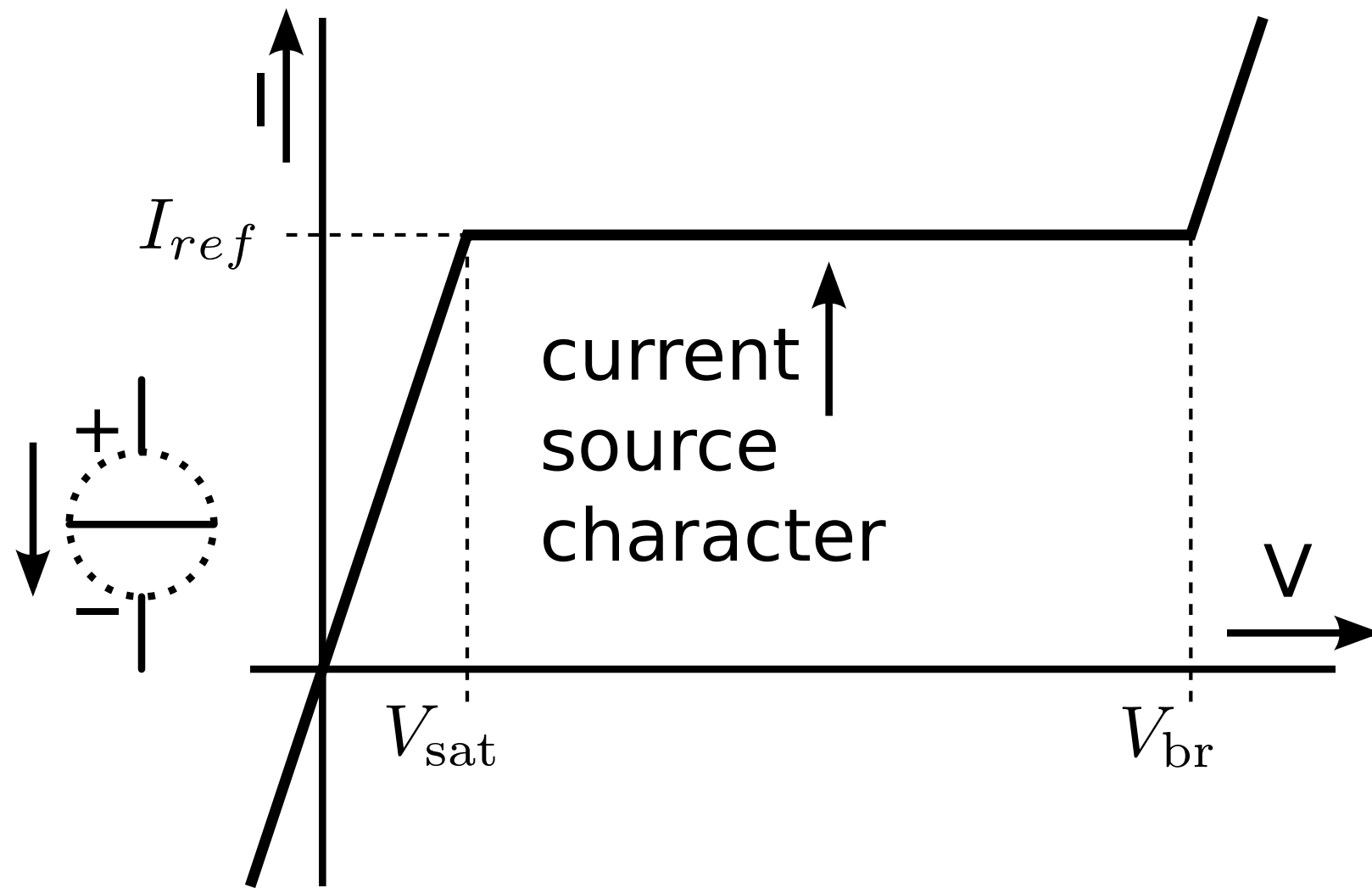

Current source behavior requires voltage drop:

# Complete biasing concept with passive biasing elements

## Nonlinear resistive elements

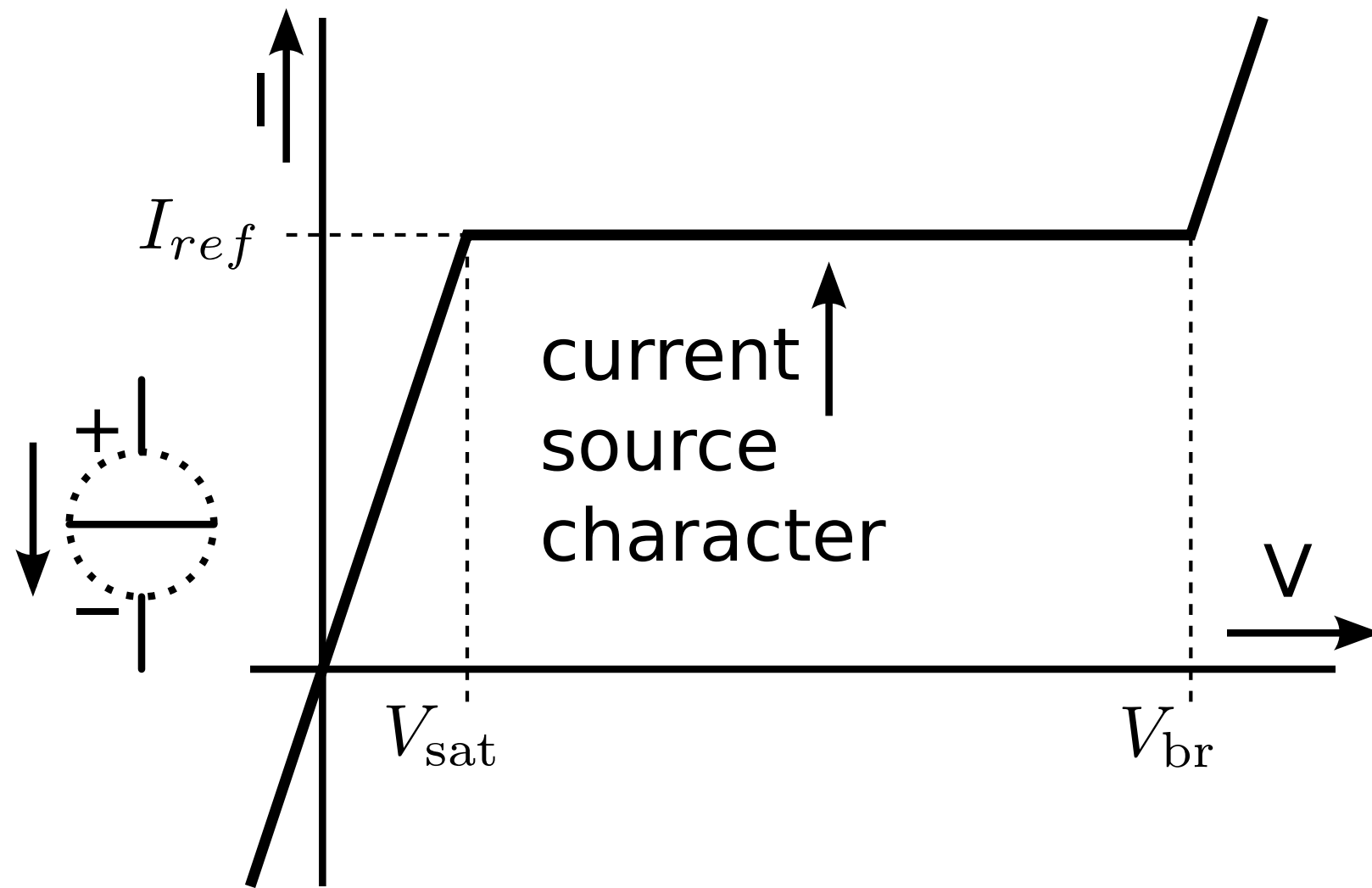


Current source behavior requires voltage drop:

Voltage between saturation and breakdown

# Complete biasing concept with passive biasing elements

## Nonlinear resistive elements


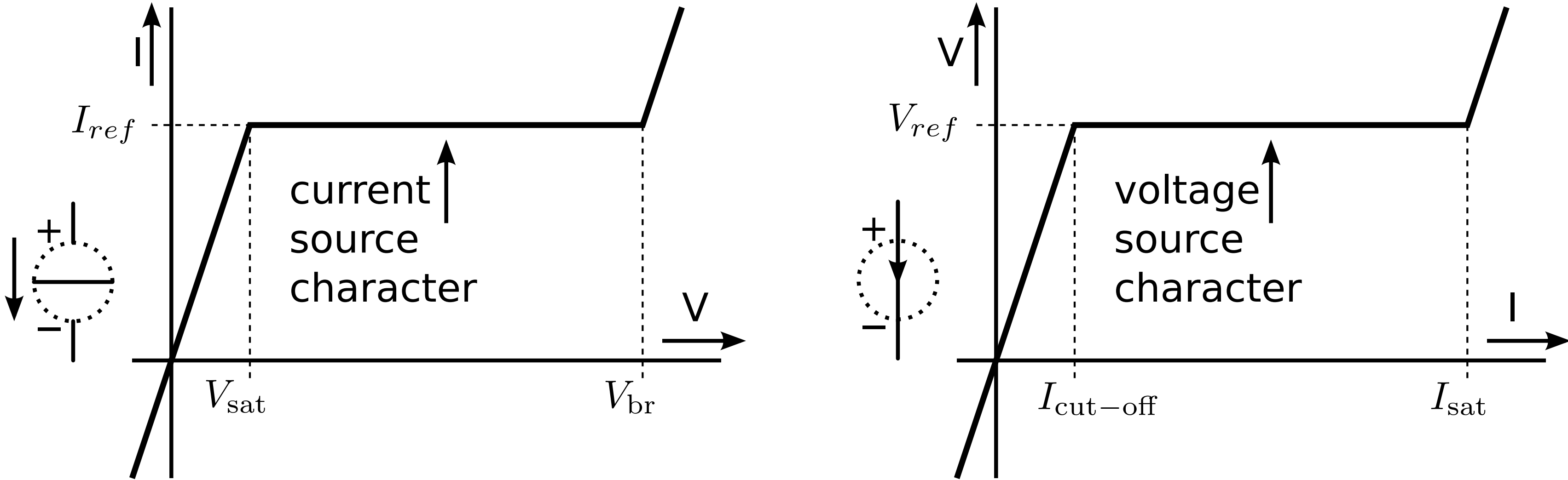


Current source behavior requires voltage drop:

Voltage between saturation and breakdown

# Complete biasing concept with passive biasing elements

## Nonlinear resistive elements

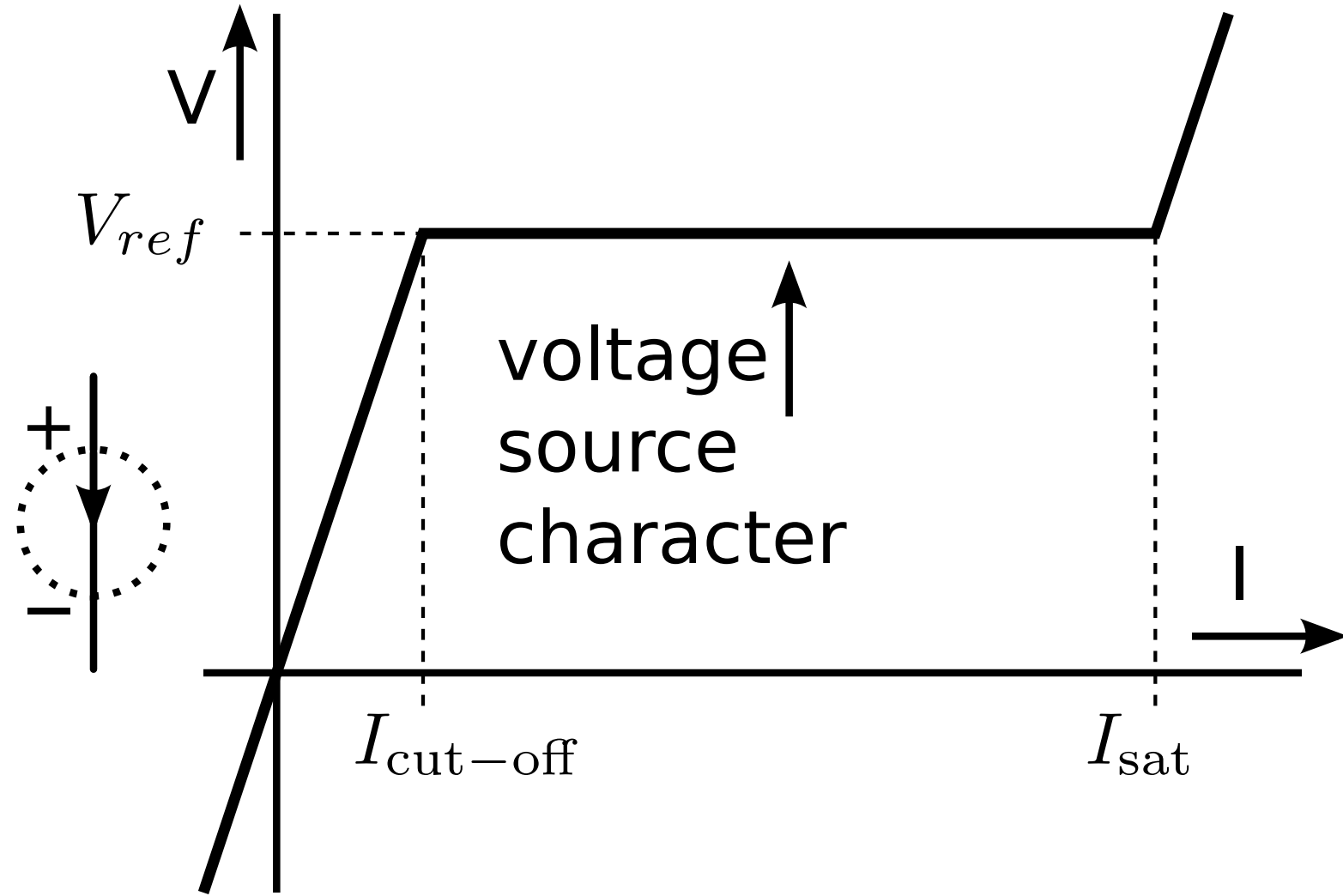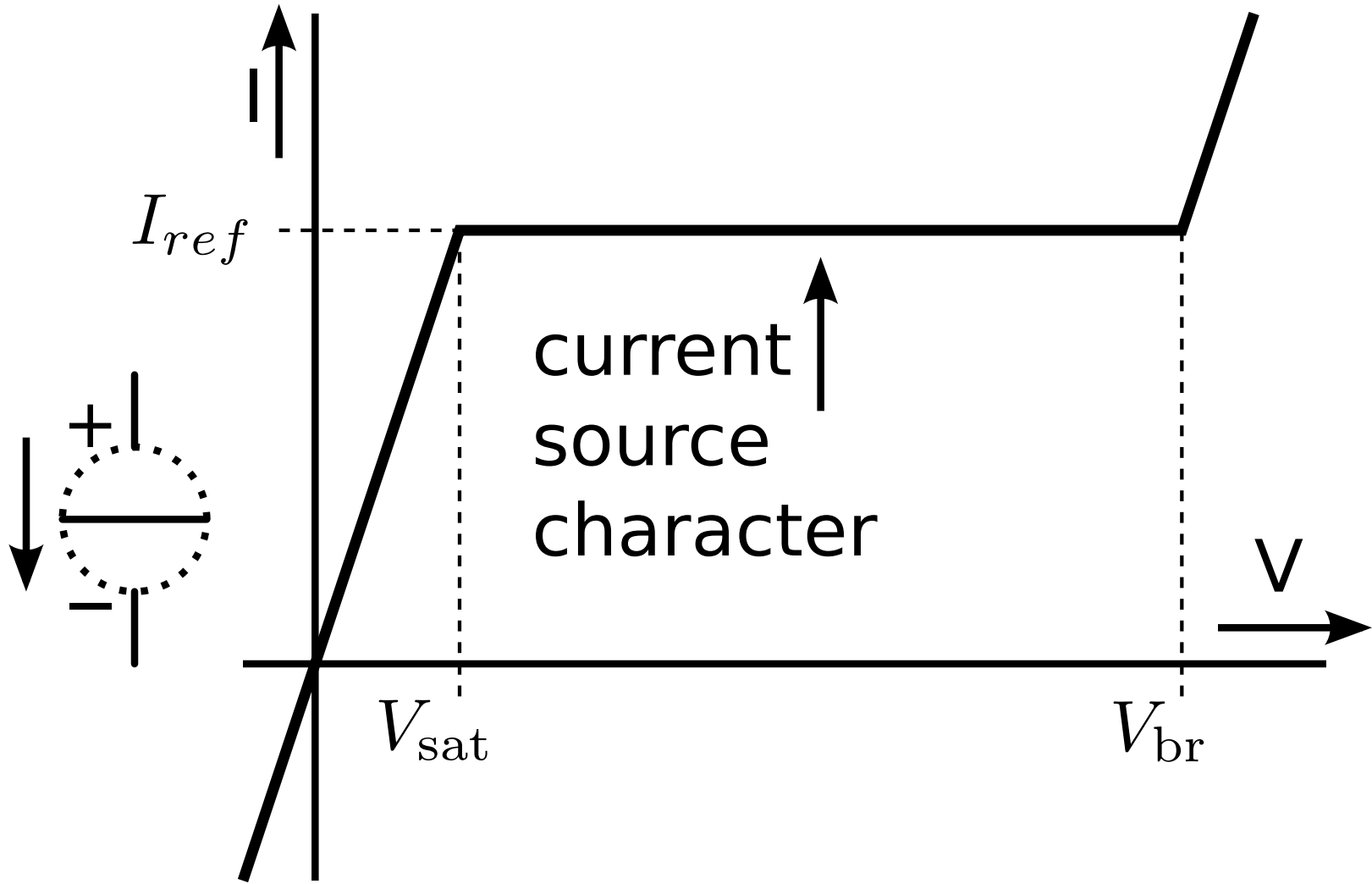



Current source behavior requires voltage drop:

Voltage between saturation and breakdown

Voltage source behavior requires current flow:

# Complete biasing concept with passive biasing elements

## Nonlinear resistive elements

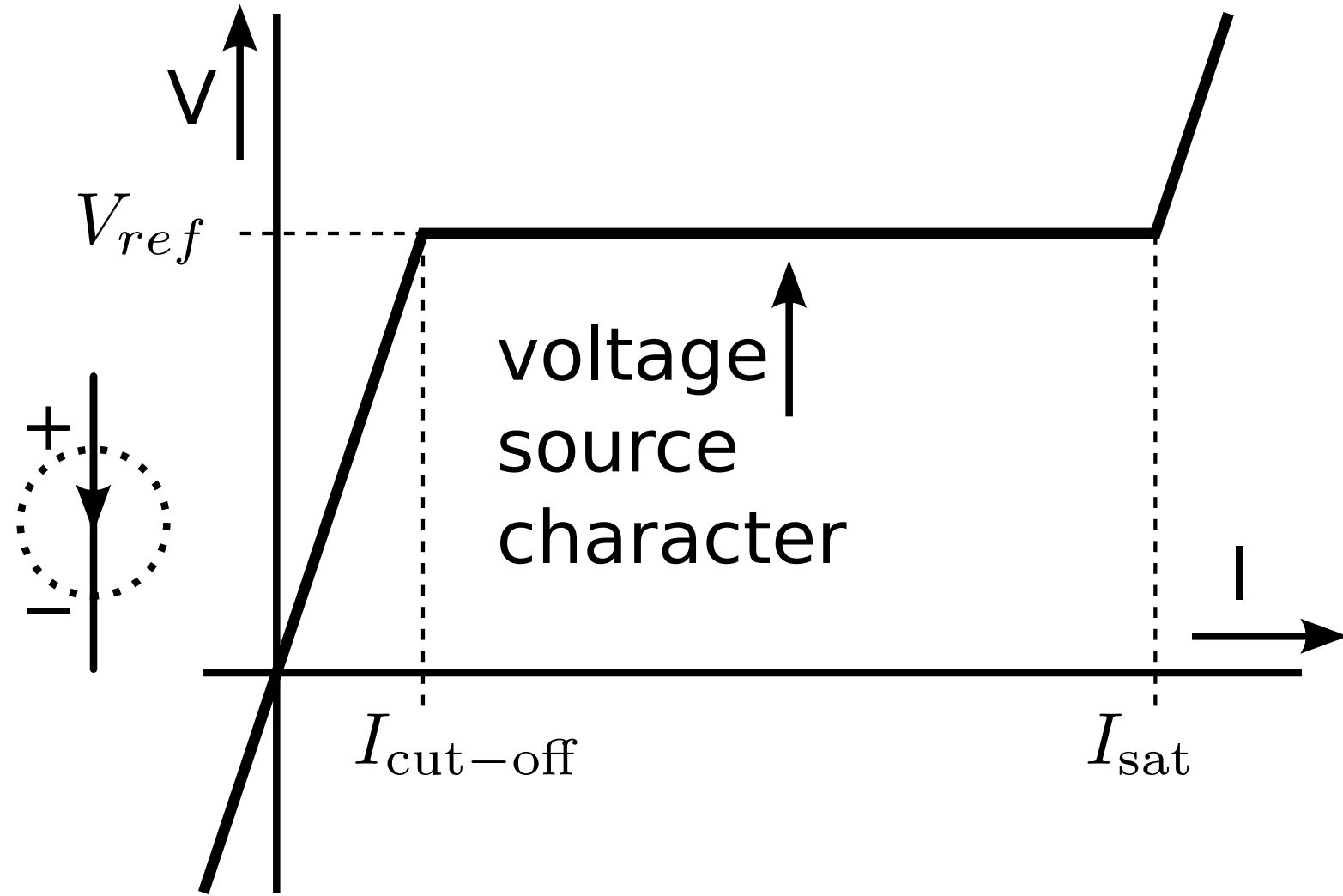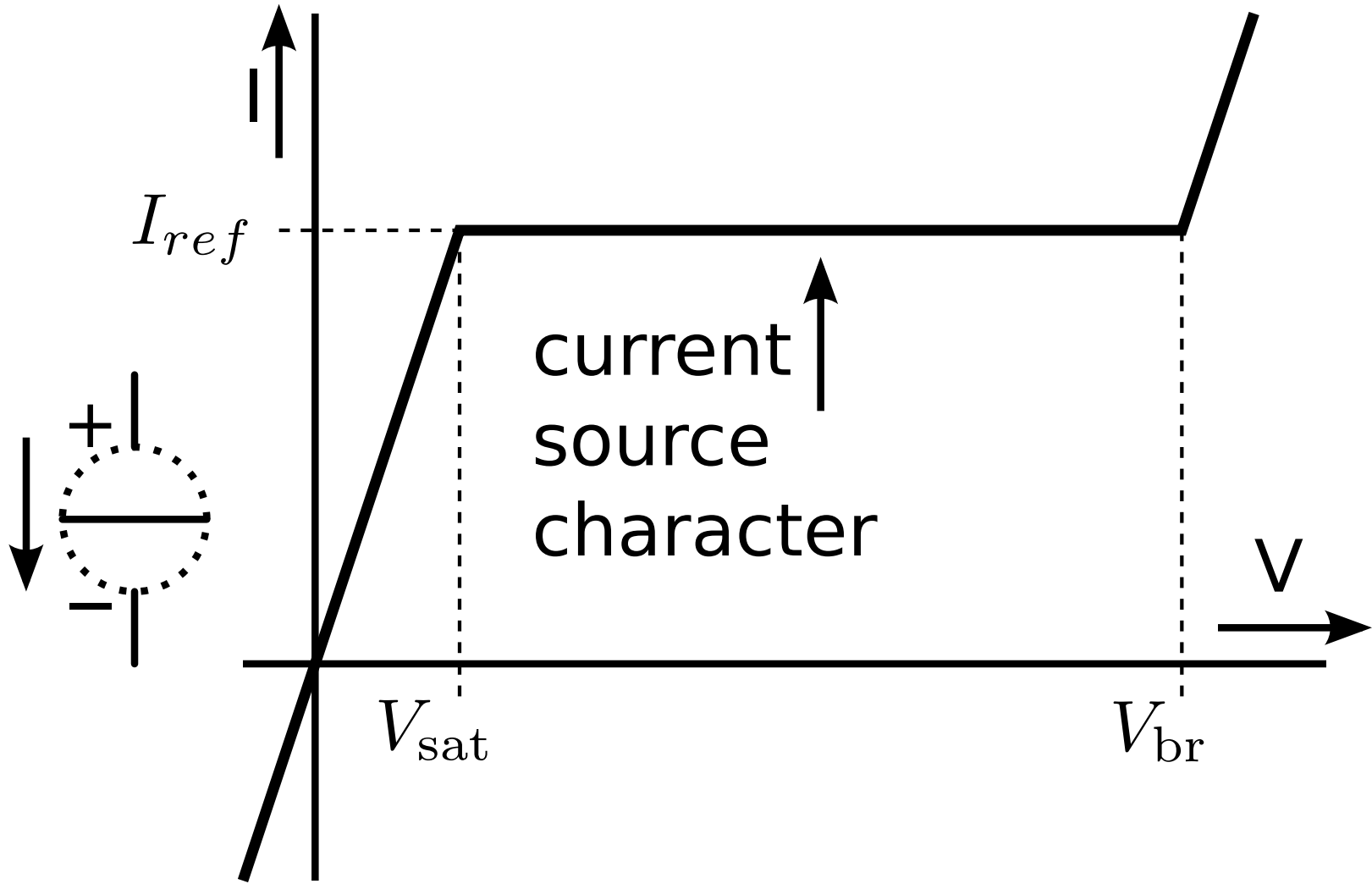

Current source behavior requires voltage drop:



Voltage between saturation and breakdown

Voltage source behavior requires current flow:

Current between cut-off and saturation

# Complete biasing concept with passive biasing elements

## Nonlinear resistive elements

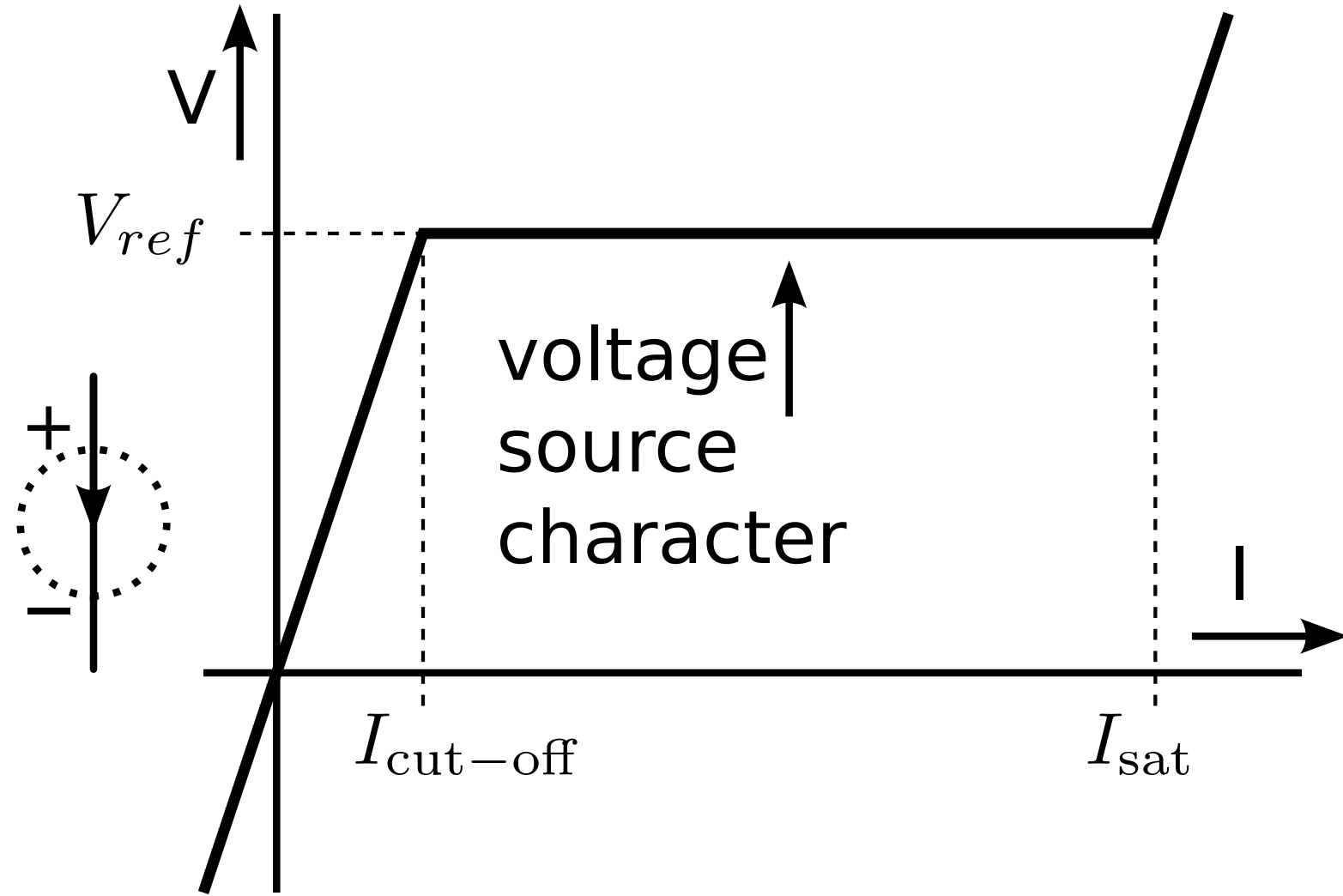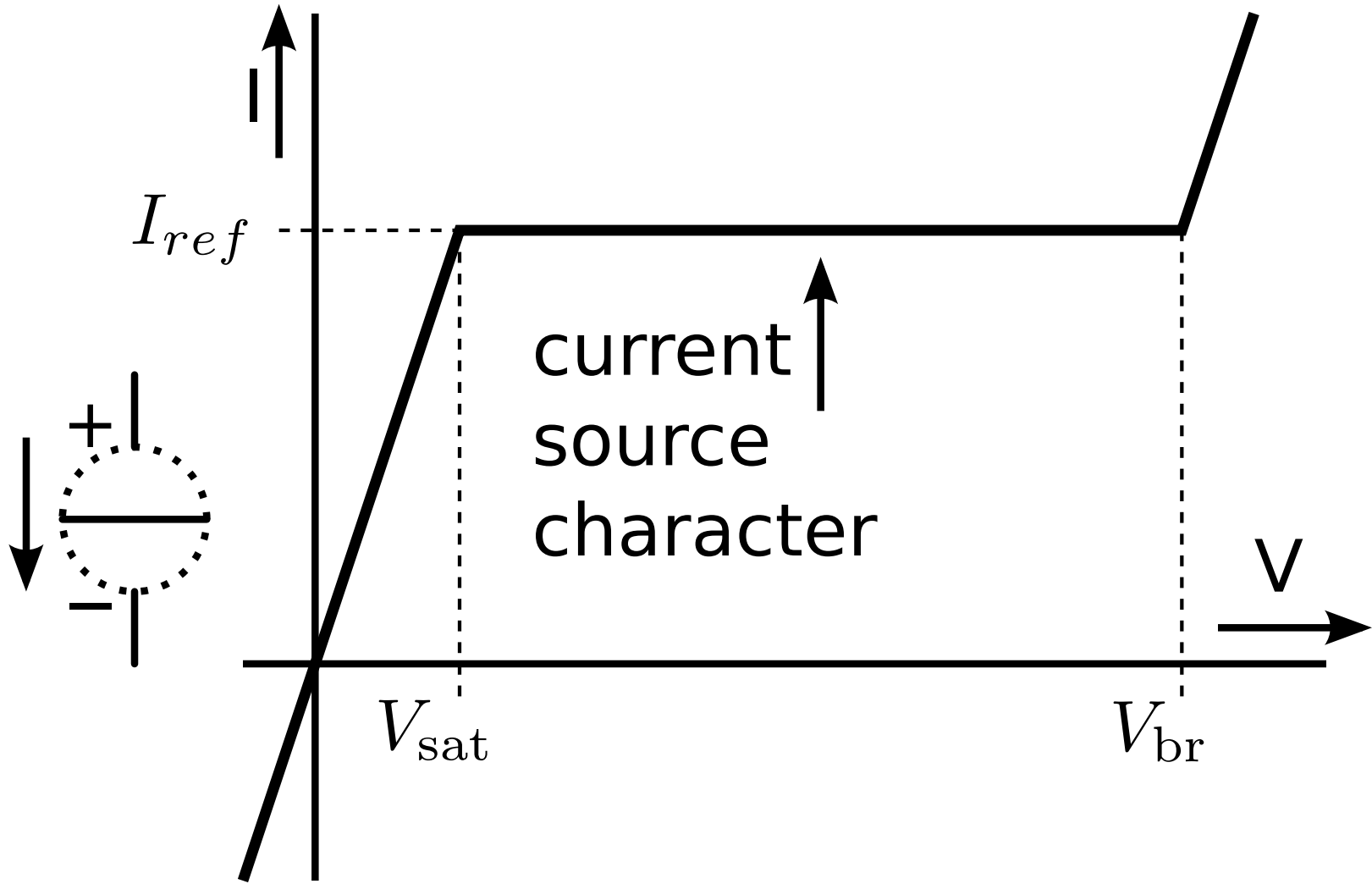

Current source behavior requires voltage drop:

Voltage between saturation and breakdown


Voltage source behavior requires current flow:

Current between cut-off and saturation



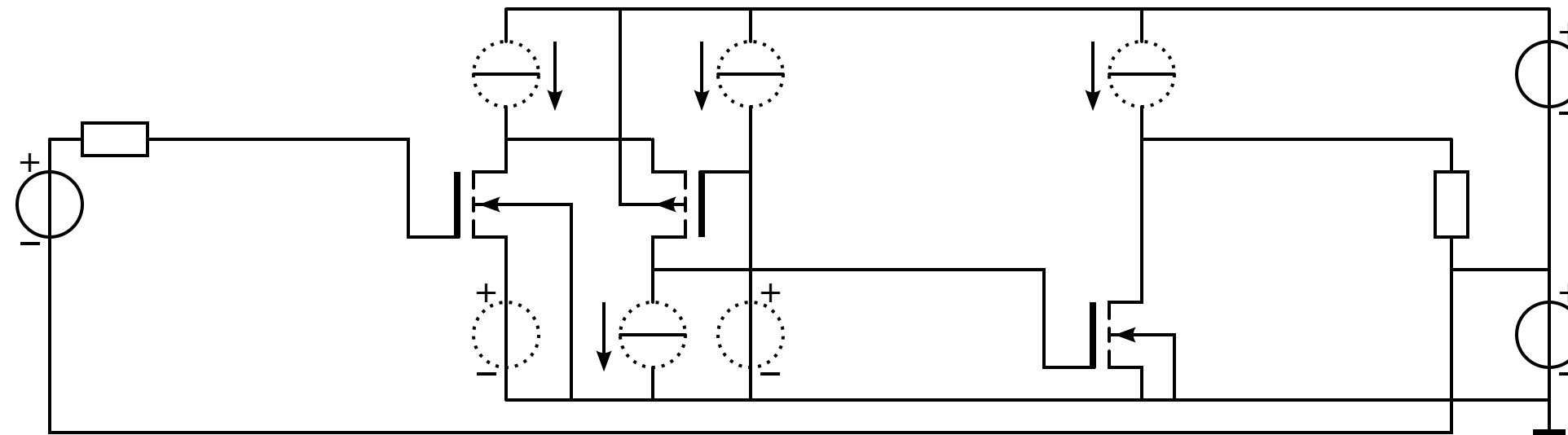
# Complete biasing with passive biasing elements

Added current source element for biasing the voltage source element of the cascode


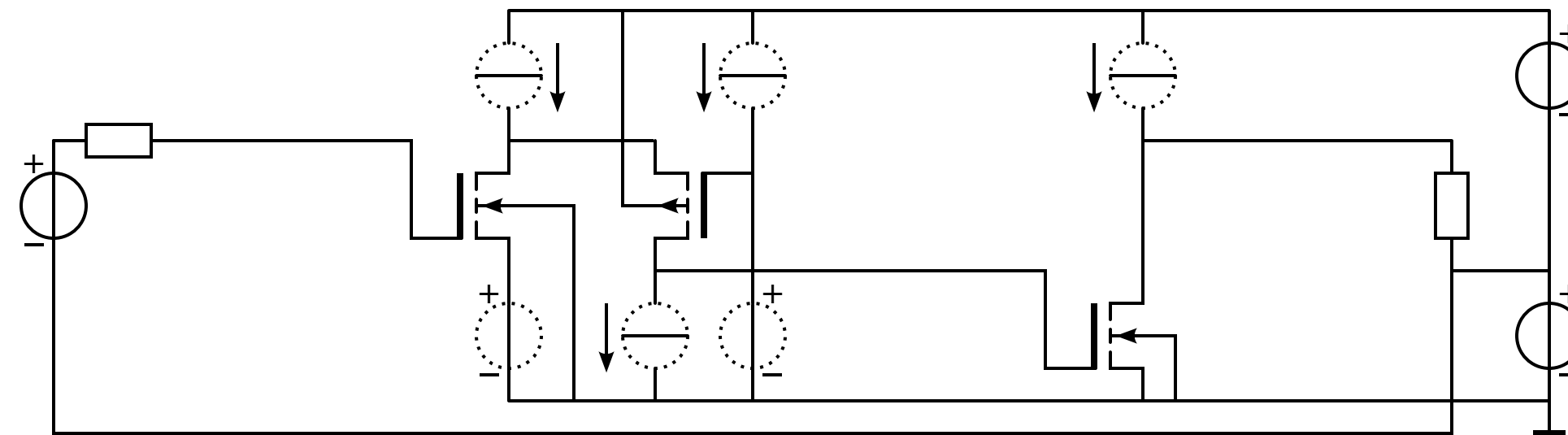
# Complete biasing with passive biasing elements

Added current source element for biasing the voltage source element of the cascode



# Specify biasing elements

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

PSRR



# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

PSRR

CMRR (in case of a floating port)

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

PSRR

CMRR (in case of a floating port)

Gain inaccuracy

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

PSRR

CMRR (in case of a floating port)

Gain inaccuracy

Weak nonlinearity (distortion)

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

PSRR

CMRR (in case of a floating port)

Gain inaccuracy

Weak nonlinearity (distortion)

Temperature dependency

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

- Noise
- Drive capability
- Power consumption
- PSRR
- CMRR (in case of a floating port)
- Gain inaccuracy
- Weak nonlinearity (distortion)
- Temperature dependency

## Bias voltage sources:

- Voltage
- Total error
- Saturation current
- Cut-off current
- Small-signal impedance
- Noise spectral density

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

PSRR

CMRR (in case of a floating port)

Gain inaccuracy

Weak nonlinearity (distortion)

Temperature dependency

Bias voltage sources:

Voltage

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

PSRR

CMRR (in case of a floating port)

Gain inaccuracy

Weak nonlinearity (distortion)

Temperature dependency

Bias voltage sources:

Voltage

Total error

Bias current sources:

Current

Total error

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

PSRR

CMRR (in case of a floating port)

Gain inaccuracy

Weak nonlinearity (distortion)

Temperature dependency

Bias voltage sources:

Voltage

Total error

Saturation current



# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

PSRR

CMRR (in case of a floating port)

Gain inaccuracy

Weak nonlinearity (distortion)

Temperature dependency

Bias voltage sources:

Voltage

Total error

Saturation current

Cut-off current

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

PSRR

CMRR (in case of a floating port)

Gain inaccuracy

Weak nonlinearity (distortion)

Temperature dependency

Bias voltage sources:

Voltage

Total error

Saturation current

Cut-off current

Small-signal impedance

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

Noise

Drive capability

Power consumption

PSRR

CMRR (in case of a floating port)

Gain inaccuracy

Weak nonlinearity (distortion)

Temperature dependency

Bias voltage sources:

Voltage

Total error

Saturation current

Cut-off current

Small-signal impedance

Noise spectral density

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

- Noise
- Drive capability
- Power consumption
- PSRR
- CMRR (in case of a floating port)
- Gain inaccuracy
- Weak nonlinearity (distortion)
- Temperature dependency

Bias voltage sources:

- Voltage
- Total error
- Saturation current
- Cut-off current
- Small-signal impedance
- Noise spectral density

Bias current sources:

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

- Noise
- Drive capability
- Power consumption
- PSRR
- CMRR (in case of a floating port)
- Gain inaccuracy
- Weak nonlinearity (distortion)
- Temperature dependency

Bias voltage sources:

- Voltage
- Total error
- Saturation current
- Cut-off current
- Small-signal impedance
- Noise spectral density

Bias current sources:

Current

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

- Noise
- Drive capability
- Power consumption
- PSRR
- CMRR (in case of a floating port)
- Gain inaccuracy
- Weak nonlinearity (distortion)
- Temperature dependency

Bias voltage sources:

- Voltage
- Total error
- Saturation current
- Cut-off current
- Small-signal impedance
- Noise spectral density

Bias current sources:

- Current
- Total error

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

- Noise
- Drive capability
- Power consumption
- PSRR
- CMRR (in case of a floating port)
- Gain inaccuracy
- Weak nonlinearity (distortion)
- Temperature dependency

Bias voltage sources:

- Voltage
- Total error
- Saturation current
- Cut-off current
- Small-signal impedance
- Noise spectral density

Bias current sources:

- Current
- Total error
- Saturation voltage

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

- Noise
- Drive capability
- Power consumption
- PSRR
- CMRR (in case of a floating port)
- Gain inaccuracy
- Weak nonlinearity (distortion)
- Temperature dependency

Bias voltage sources:

- Voltage
- Total error
- Saturation current
- Cut-off current
- Small-signal impedance
- Noise spectral density

Bias current sources:

- Current
- Total error
- Saturation voltage
- Breakdown voltage



# Specify biasing elements

Relate amplifier specifications to those of biasing elements

- Noise
- Drive capability
- Power consumption
- PSRR
- CMRR (in case of a floating port)
- Gain inaccuracy
- Weak nonlinearity (distortion)
- Temperature dependency

Bias voltage sources:

- Voltage
- Total error
- Saturation current
- Cut-off current
- Small-signal impedance
- Noise spectral density

Bias current sources:

- Current
- Total error
- Saturation voltage
- Breakdown voltage
- Small-signal impedance

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

- Noise
- Drive capability
- Power consumption
- PSRR
- CMRR (in case of a floating port)
- Gain inaccuracy
- Weak nonlinearity (distortion)
- Temperature dependency

Bias voltage sources:

- Voltage
- Total error
- Saturation current
- Cut-off current
- Small-signal impedance
- Noise spectral density

Bias current sources:

- Current
- Total error
- Saturation voltage
- Breakdown voltage
- Small-signal impedance
- Noise spectral density

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

- Noise
- Drive capability
- Power consumption
- PSRR
- CMRR (in case of a floating port)
- Gain inaccuracy
- Weak nonlinearity (distortion)
- Temperature dependency

Bias voltage sources:

- Voltage
- Total error
- Saturation current
- Cut-off current
- Small-signal impedance
- Noise spectral density

Bias current sources:

- Current
- Total error
- Saturation voltage
- Breakdown voltage
- Small-signal impedance
- Noise spectral density

Check performance after implementation of bias sources

Design improvements if necessary

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

- Noise
- Drive capability
- Power consumption
- PSRR
- CMRR (in case of a floating port)
- Gain inaccuracy
- Weak nonlinearity (distortion)
- Temperature dependency

Bias voltage sources:

- Voltage
- Total error
- Saturation current
- Cut-off current
- Small-signal impedance
- Noise spectral density

Bias current sources:

- Current
- Total error
- Saturation voltage
- Breakdown voltage
- Small-signal impedance
- Noise spectral density

Check performance after implementation of bias sources

Design improvements if necessary

# Specify biasing elements

Relate amplifier specifications to those of biasing elements

- Noise
- Drive capability
- Power consumption
- PSRR
- CMRR (in case of a floating port)
- Gain inaccuracy
- Weak nonlinearity (distortion)
- Temperature dependency

Bias voltage sources:

- Voltage
- Total error
- Saturation current
- Cut-off current
- Small-signal impedance
- Noise spectral density

Bias current sources:

- Current
- Total error
- Saturation voltage
- Breakdown voltage
- Small-signal impedance
- Noise spectral density

Check performance after implementation of bias sources

Design improvements if necessary


# Define differential-mode quantities

# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:
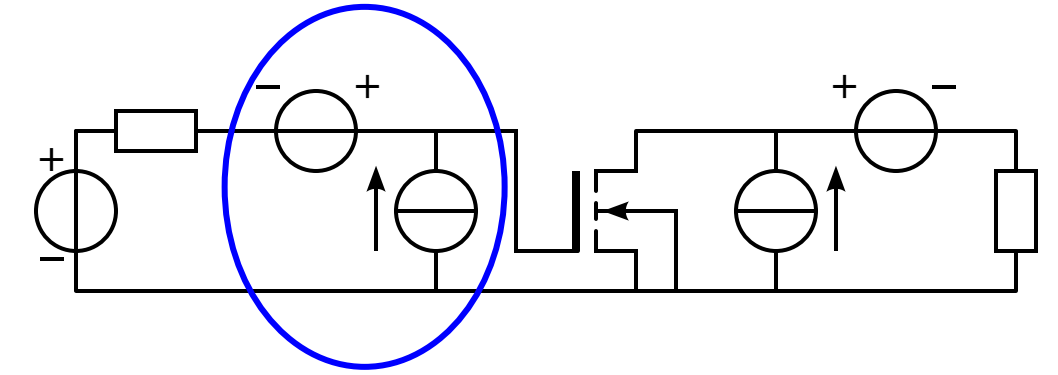
# Define differential-mode quantities


With  $n$  transistors we need to control  $2n$  bias quantities:




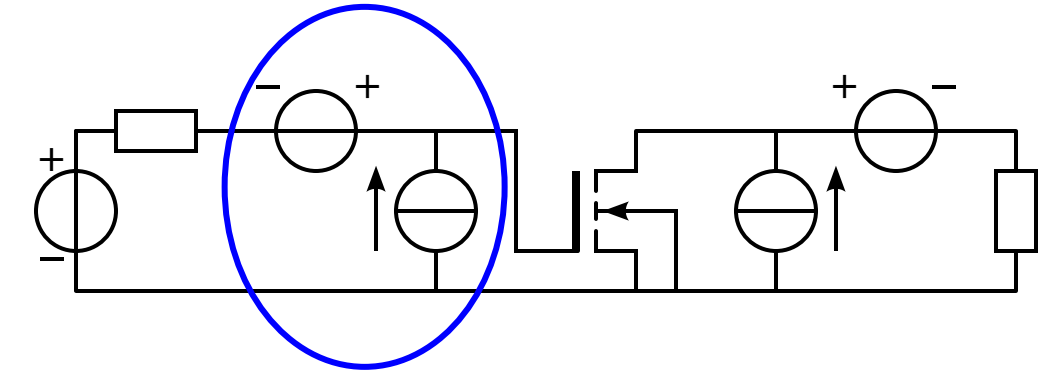
# Define differential-mode quantities


With  $n$  transistors we need to control  $2n$  bias quantities:




Where have they gone?
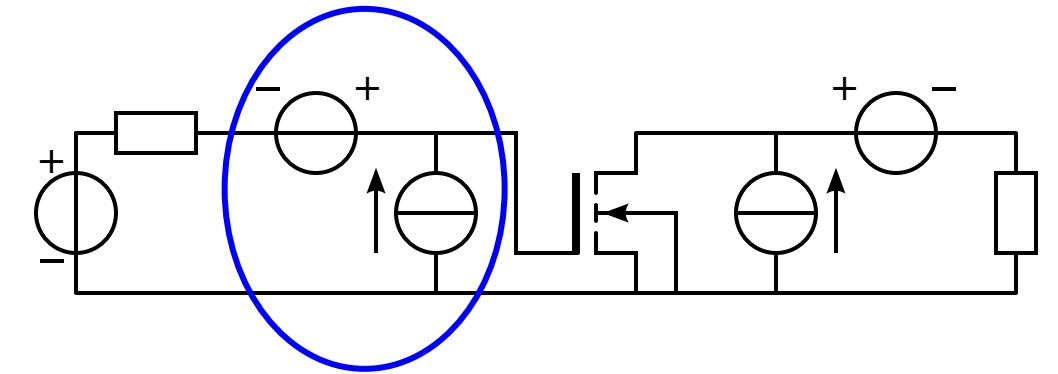
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:




Where have they gone?

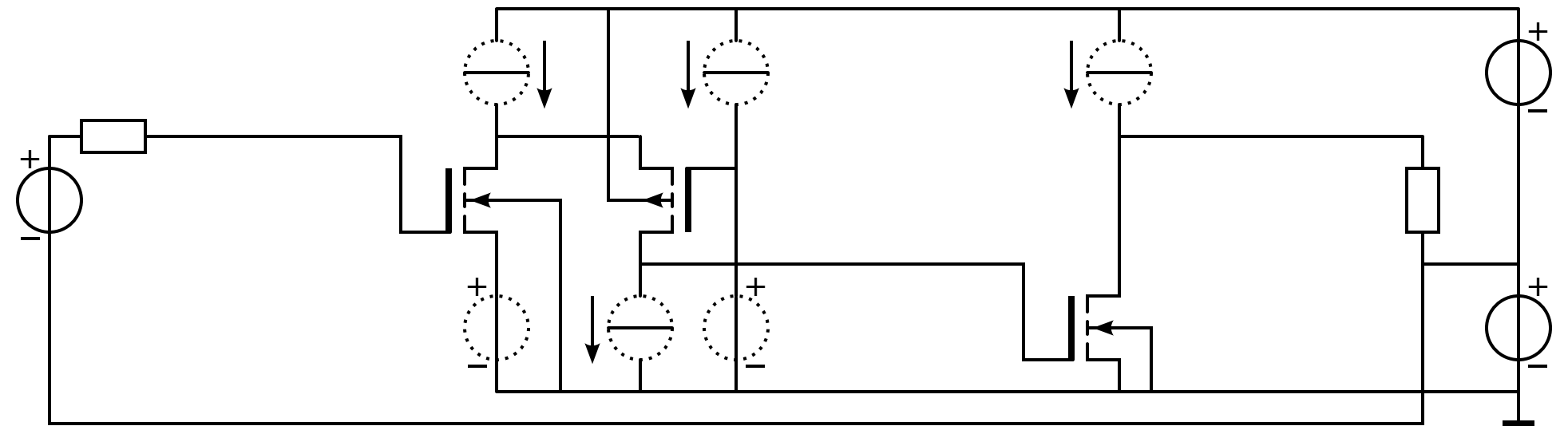

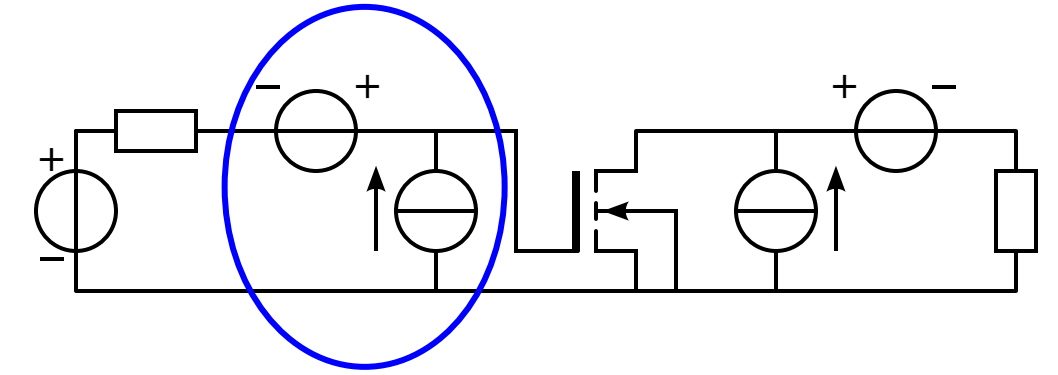
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:




Where have they gone?

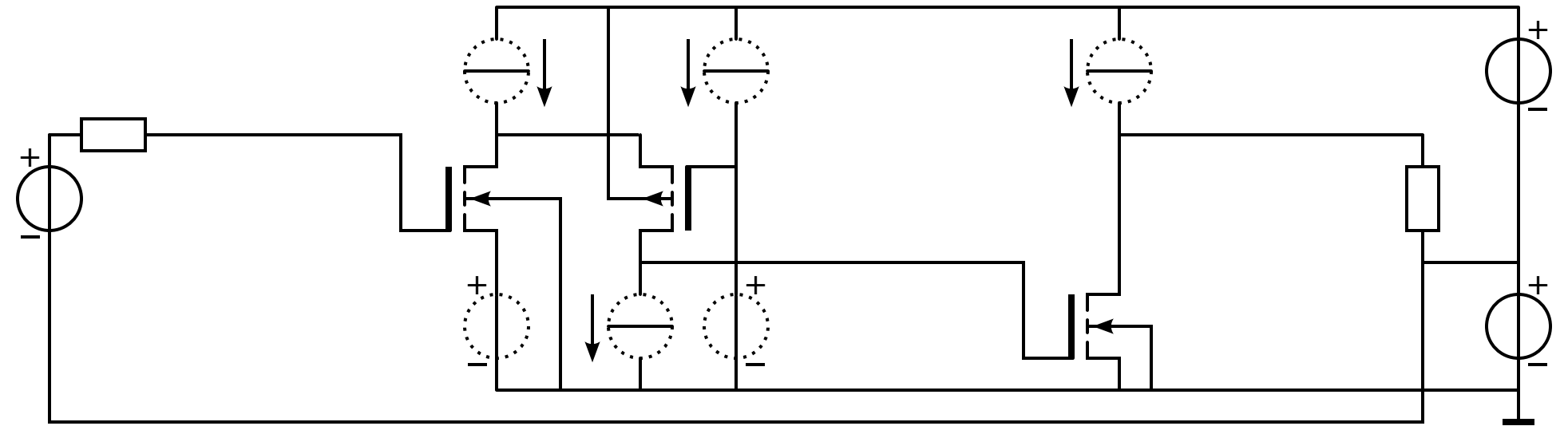


If all stages are DC coupled, biasing errors propagate
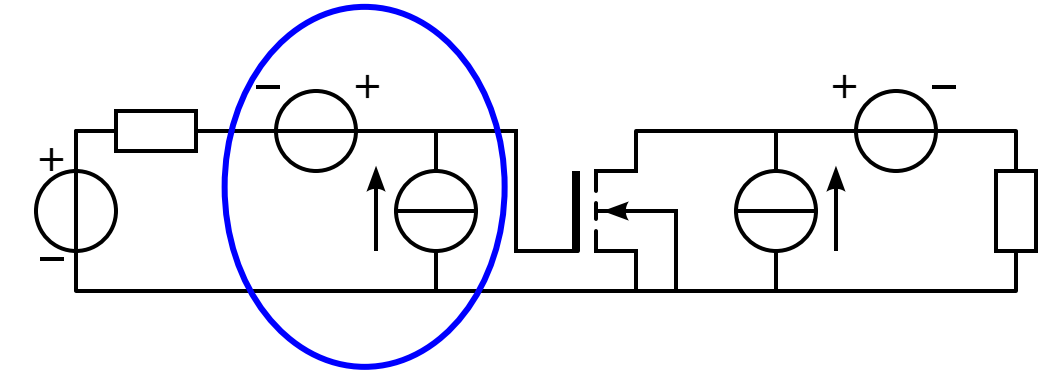
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:



Where have they gone?

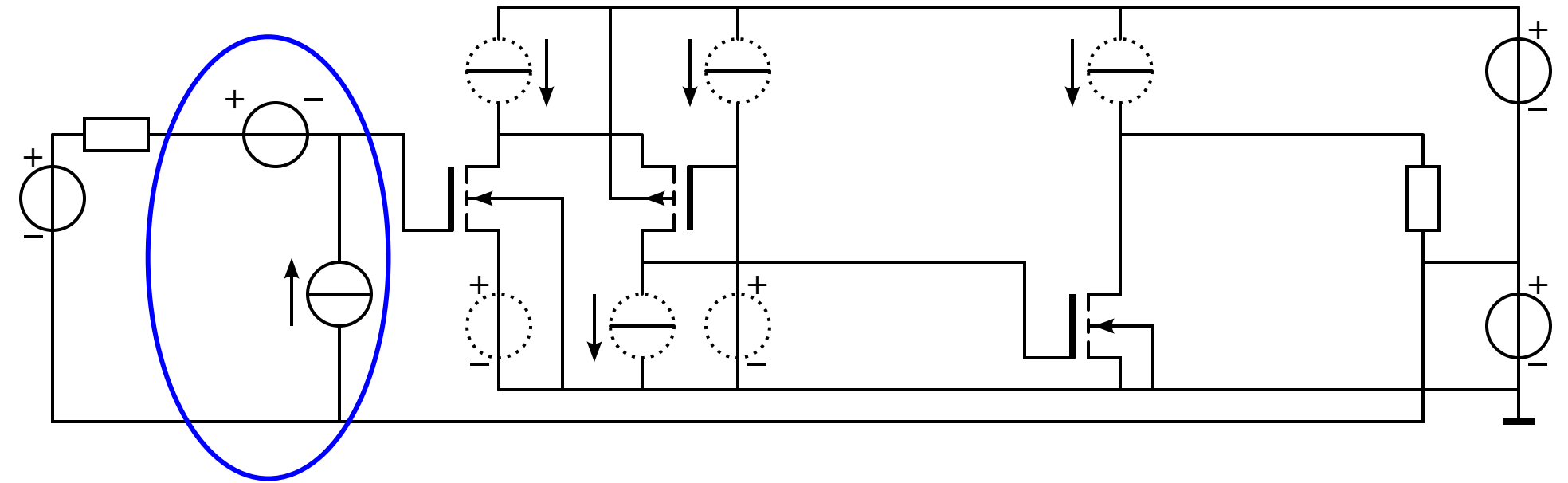


If all stages are DC coupled, biasing errors propagate


If non of the stages is clipping, biasing errors add up to equivalent-input voltage and current bias sources
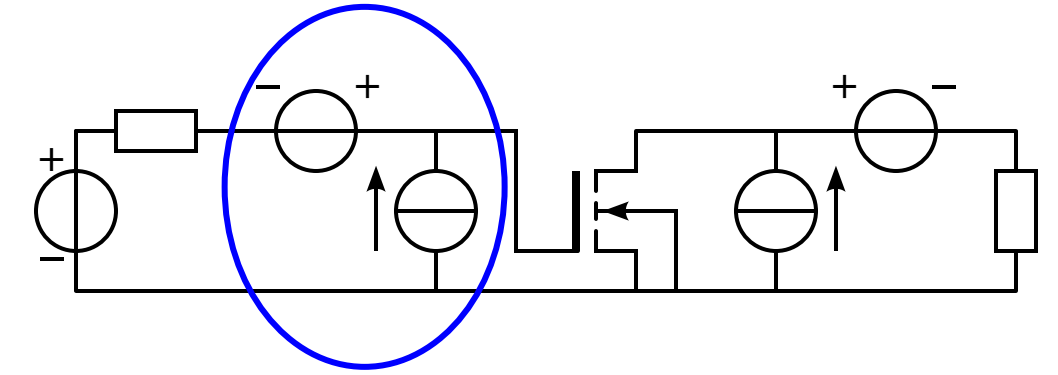
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:



Where have they gone?

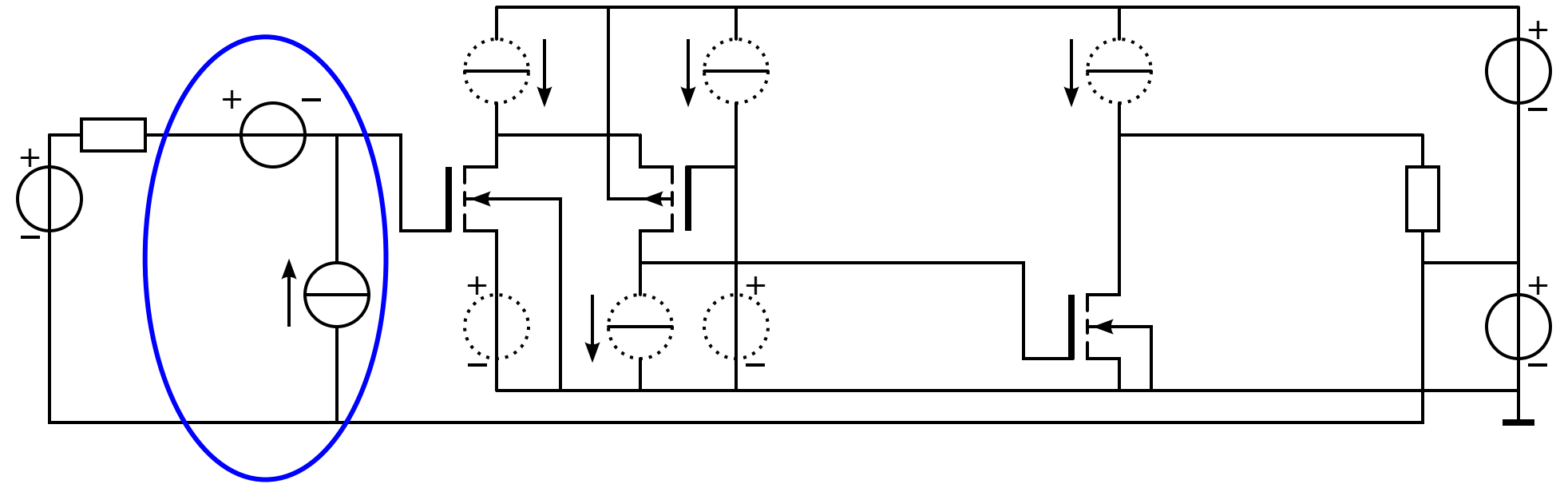


If all stages are DC coupled, biasing errors propagate

If non of the stages is clipping, biasing errors add up to equivalent-input voltage and current bias sources


If the biasing error at the output is too large, over-all error-reduction can be applied:
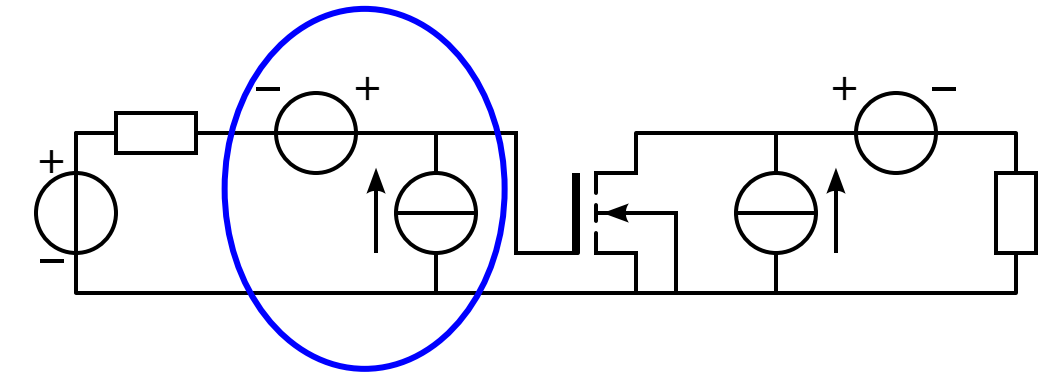
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:



Where have they gone?

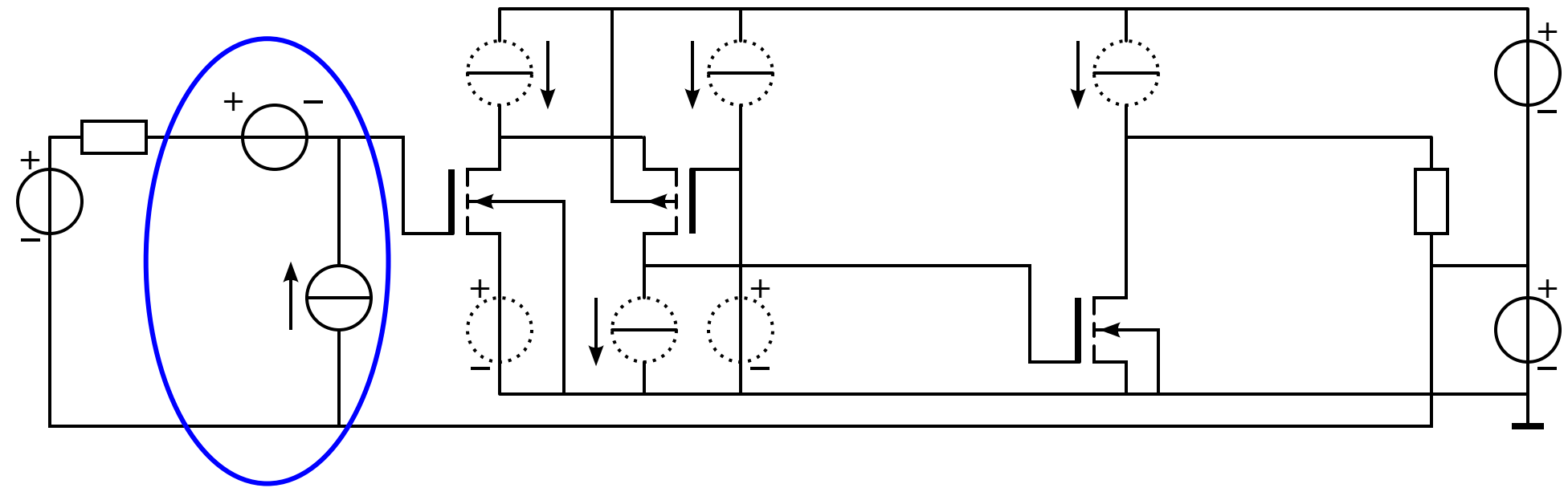

If all stages are DC coupled, biasing errors propagate


If non of the stages is clipping, biasing errors add up to equivalent-input voltage and current bias sources

If the biasing error at the output is too large, over-all error-reduction can be applied:


[Over-all model-based biasing](#)
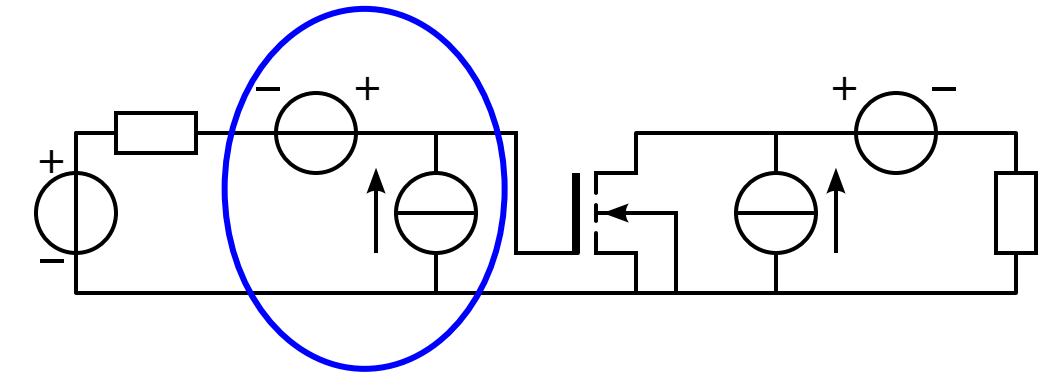
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:



Where have they gone?

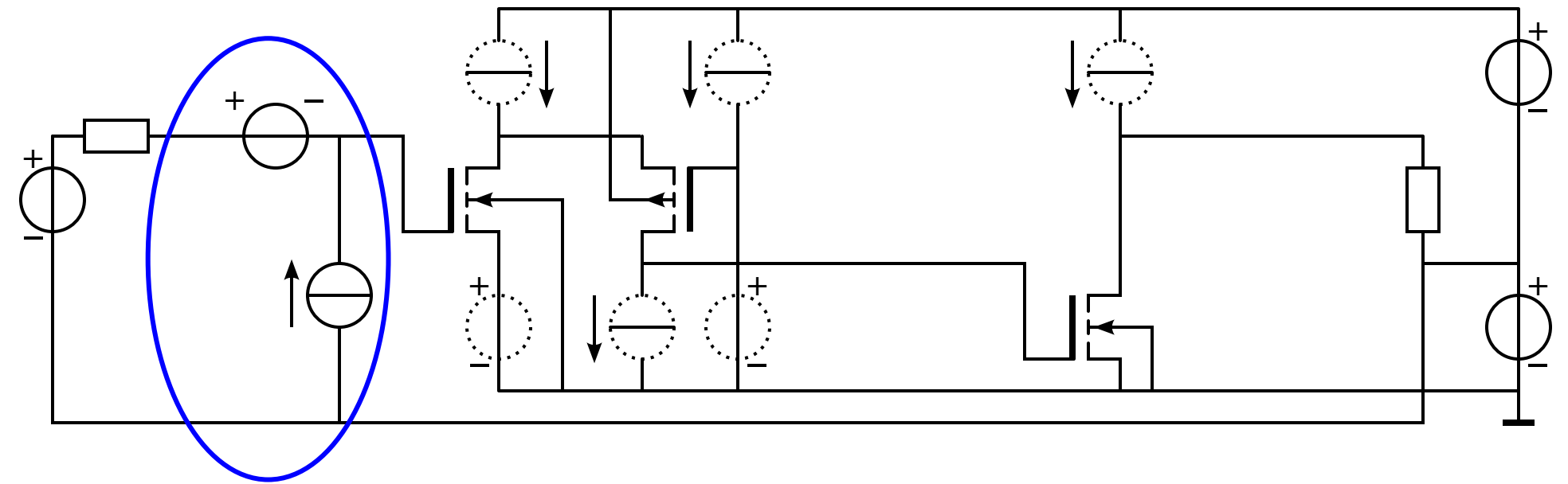

If all stages are DC coupled, biasing errors propagate

If non of the stages is clipping, biasing errors add up to equivalent-input voltage and current bias sources


If the biasing error at the output is too large, over-all error-reduction can be applied:

Over-all model-based biasing


Over-all negative-feedback biasing
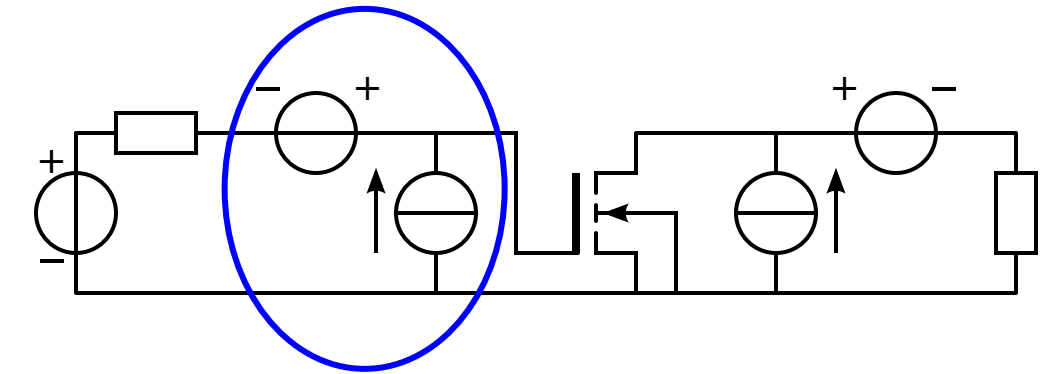
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:



Where have they gone?

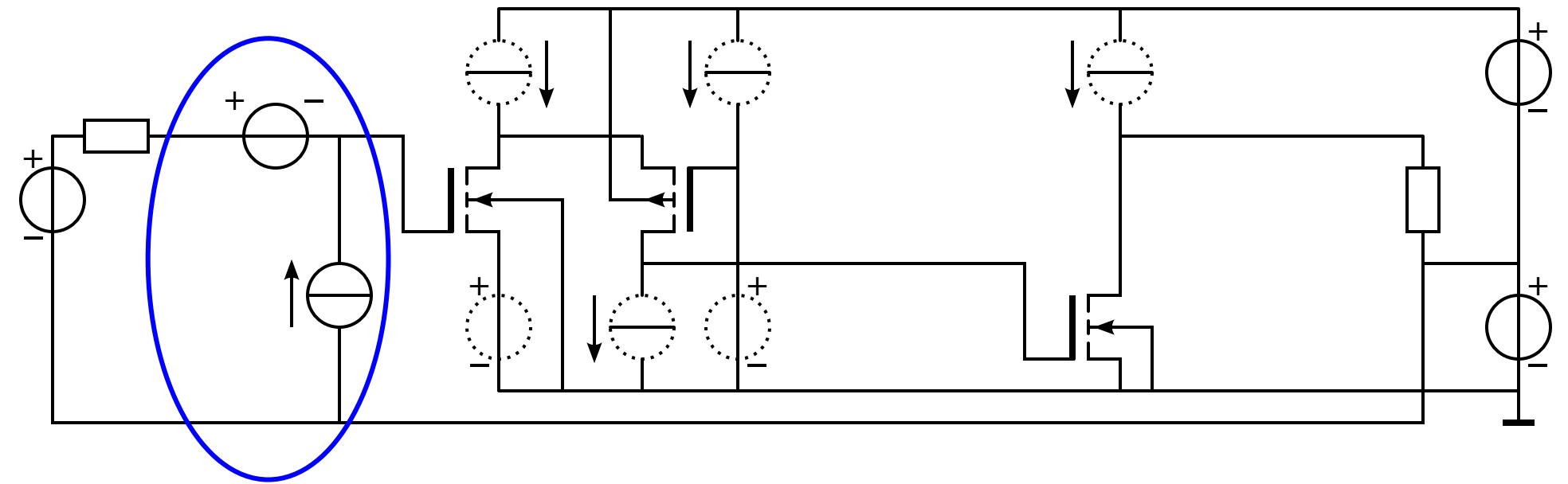

If all stages are DC coupled, biasing errors propagate

If non of the stages is clipping, biasing errors add up to equivalent-input voltage and current bias sources

If the biasing error at the output is too large, over-all error-reduction can be applied:

- Over-all model-based biasing


- Over-all negative-feedback biasing

- Over-all auto-zeroing



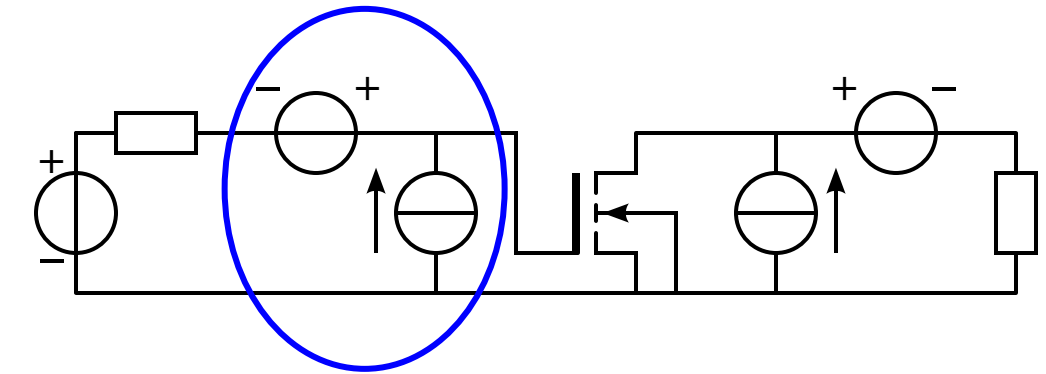
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:



Where have they gone?

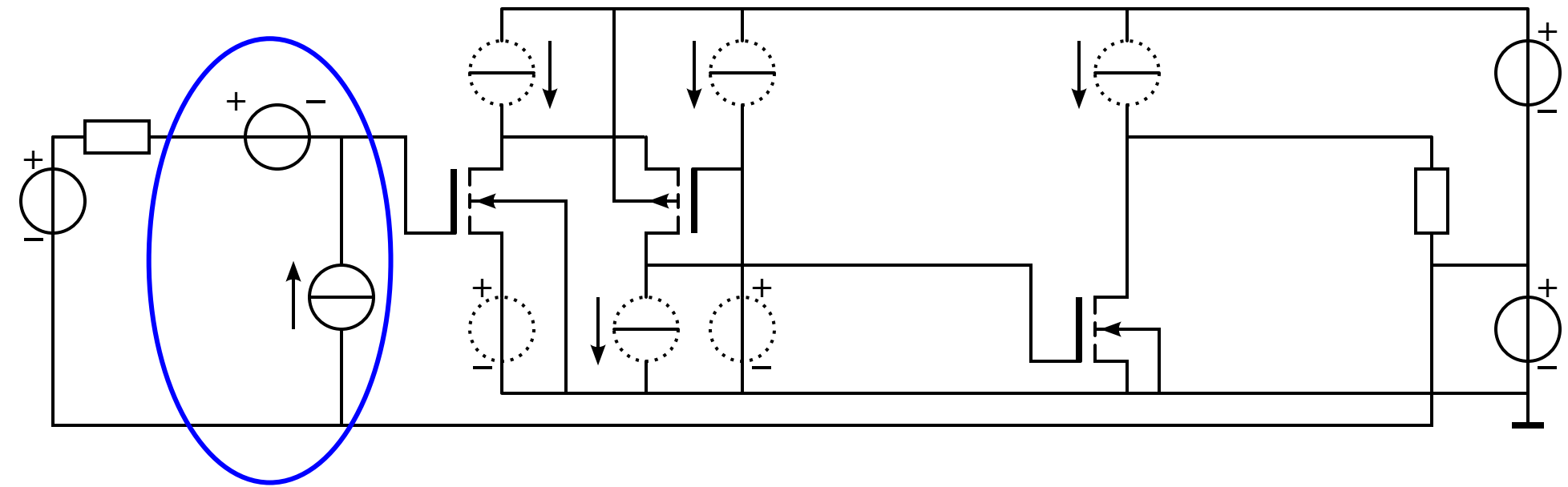

If all stages are DC coupled, biasing errors propagate

If non of the stages is clipping, biasing errors add up to equivalent-input voltage and current bias sources

If the biasing error at the output is too large, over-all error-reduction can be applied:

- Over-all model-based biasing


- Over-all negative-feedback biasing

- Over-all auto-zeroing


If one of the stages is clipping, it can be observed at the output, and the accuracy of local biasing has to be improved
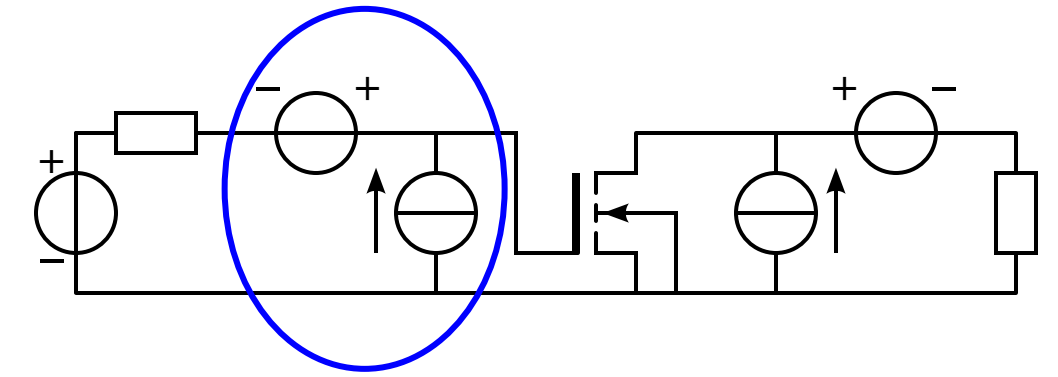
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:



Where have they gone?

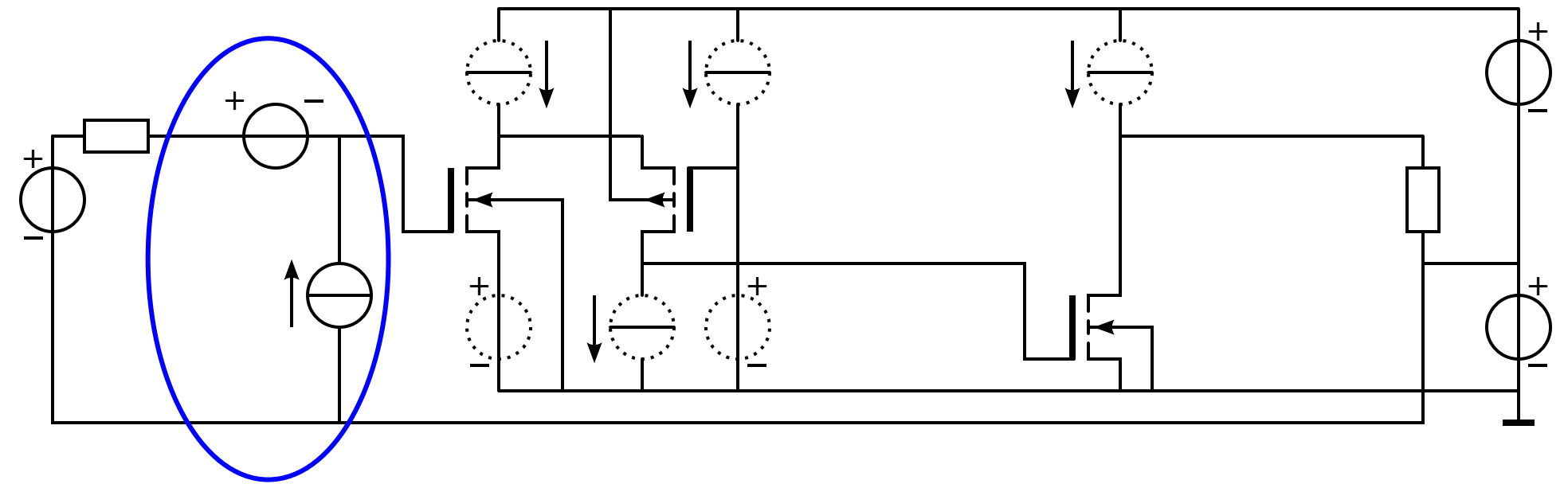

If all stages are DC coupled, biasing errors propagate

If non of the stages is clipping, biasing errors add up to equivalent-input voltage and current bias sources

If the biasing error at the output is too large, over-all error-reduction can be applied:

- Over-all model-based biasing

- Over-all negative-feedback biasing


- Over-all auto-zeroing

If one of the stages is clipping, it can be observed at the output, and the accuracy of local biasing has to be improved


- [Local model-based biasing](#)
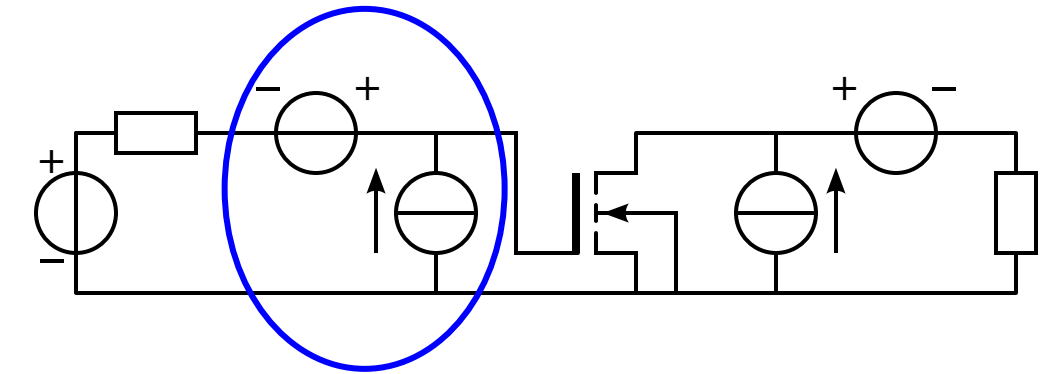
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:



Where have they gone?

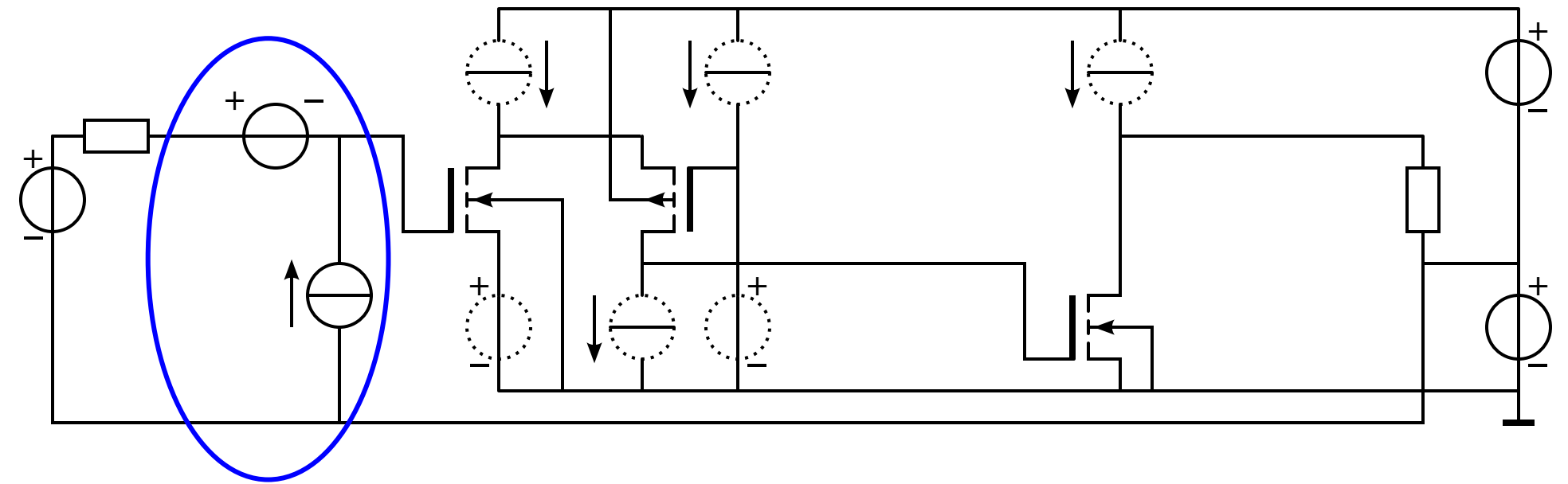

If all stages are DC coupled, biasing errors propagate

If non of the stages is clipping, biasing errors add up to equivalent-input voltage and current bias sources

If the biasing error at the output is too large, over-all error-reduction can be applied:

- Over-all model-based biasing

- Over-all negative-feedback biasing

- Over-all auto-zeroing


If one of the stages is clipping, it can be observed at the output, and the accuracy of local biasing has to be improved

- Local model-based biasing


- Local negative-feedback biasing
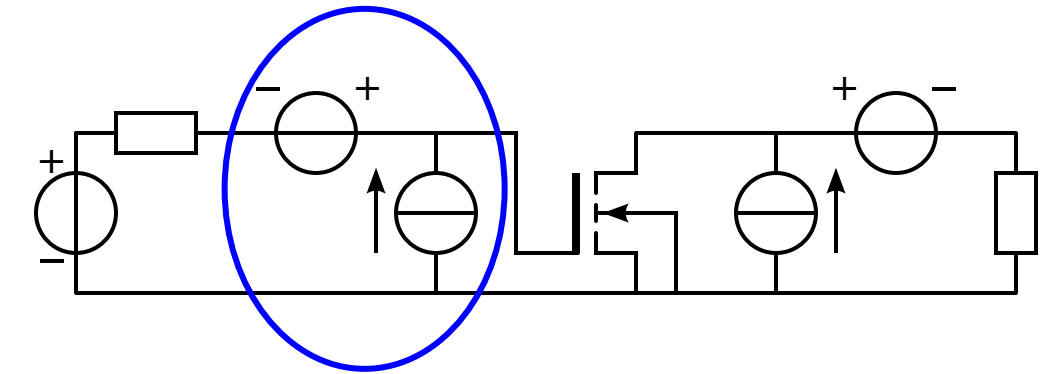
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:



Where have they gone?

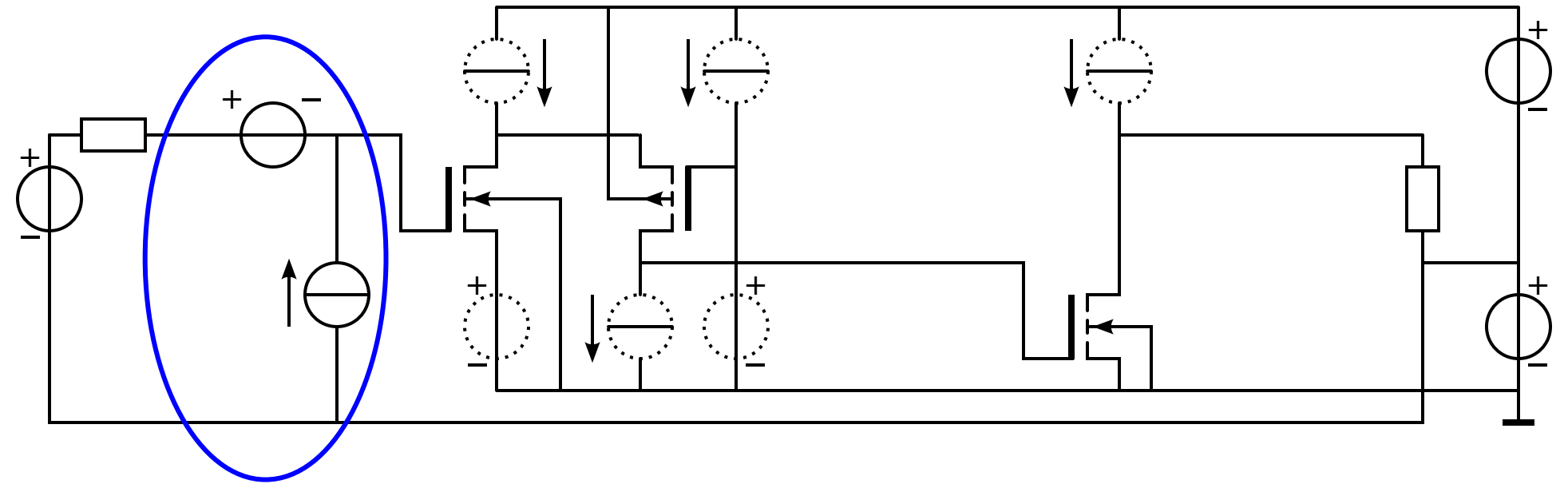

If all stages are DC coupled, biasing errors propagate

If non of the stages is clipping, biasing errors add up to equivalent-input voltage and current bias sources

If the biasing error at the output is too large, over-all error-reduction can be applied:

- Over-all model-based biasing

- Over-all negative-feedback biasing

- Over-all auto-zeroing

If one of the stages is clipping, it can be observed at the output, and the accuracy of local biasing has to be improved


- Local model-based biasing

- Local negative-feedback biasing


- Local auto-zeroing
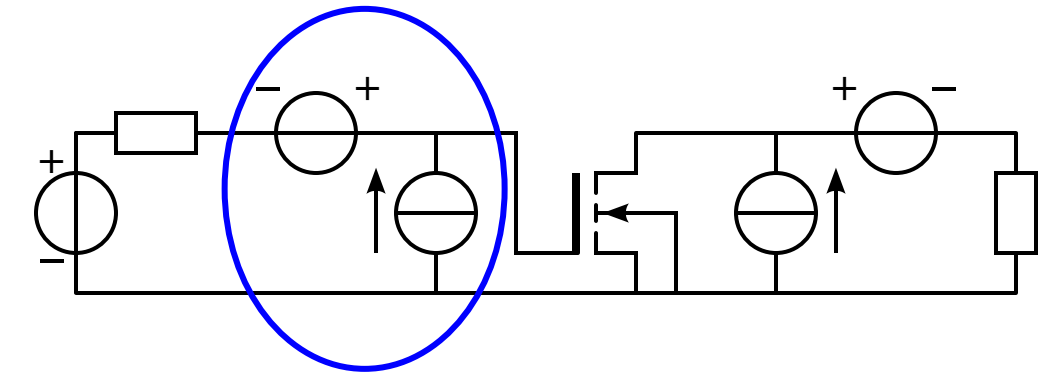
# Define differential-mode quantities

With  $n$  transistors we need to control  $2n$  bias quantities:



Where have they gone?

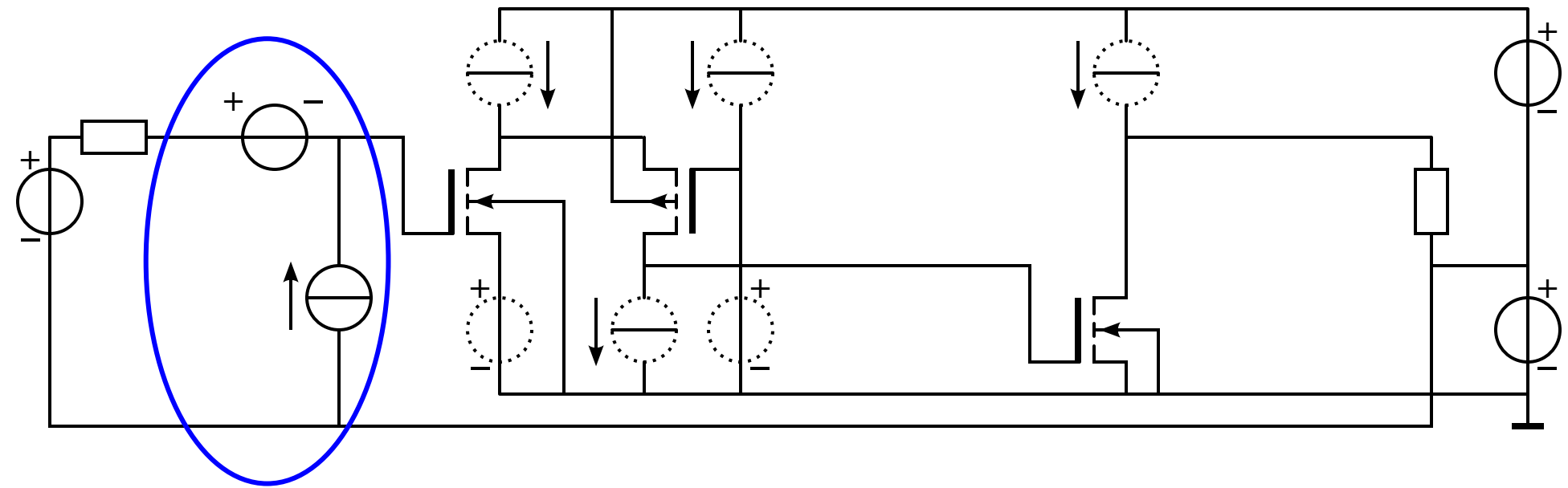

If all stages are DC coupled, biasing errors propagate

If non of the stages is clipping, biasing errors add up to equivalent-input voltage and current bias sources

If the biasing error at the output is too large, over-all error-reduction can be applied:

- Over-all model-based biasing

- Over-all negative-feedback biasing

- Over-all auto-zeroing

If one of the stages is clipping, it can be observed at the output, and the accuracy of local biasing has to be improved

- Local model-based biasing

- Local negative-feedback biasing

- Local auto-zeroing

# Define common-mode quantities

# Define common-mode quantities

Common-mode biasing errors only propagate if:

# Define common-mode quantities

Common-mode biasing errors only propagate if:

Stages are DC coupled



# Define common-mode quantities

Common-mode biasing errors only propagate if:

Stages are DC coupled

Stages have common-mode transfer or common-mode to differential-mode conversion

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

- Common-mode voltage or current can be defined in one stage:

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

Common-mode voltage or current can be defined in one stage:

[Local brute-force common-mode biasing](#)

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

Common-mode voltage or current can be defined in one stage:

- Local brute-force common-mode biasing

- [Local model-based common-mode biasing](#)

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

Common-mode voltage or current can be defined in one stage:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

- [Local common-mode feedback biasing](#)

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

Common-mode voltage or current can be defined in one stage:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

- Local common-mode feedback biasing

Over-all common-mode feedback can be applied as error-reduction technique

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

Common-mode voltage or current can be defined in one stage:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

- Local common-mode feedback biasing

Over-all common-mode feedback can be applied as error-reduction technique

Low-pass filtering is not required if common-mode to differential-mode conversion is negligible



# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

Common-mode voltage or current can be defined in one stage:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

- Local common-mode feedback biasing

Over-all common-mode feedback can be applied as error-reduction technique

Low-pass filtering is not required if common-mode to differential-mode conversion is negligible

Else:

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

Common-mode voltage or current can be defined in one stage:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

- Local common-mode feedback biasing

Over-all common-mode feedback can be applied as error-reduction technique

Low-pass filtering is not required if common-mode to differential-mode conversion is negligible

Else:

Common-mode voltage or current needs to be defined locally:

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

Common-mode voltage or current can be defined in one stage:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

- Local common-mode feedback biasing

Over-all common-mode feedback can be applied as error-reduction technique

Low-pass filtering is not required if common-mode to differential-mode conversion is negligible

Else:

Common-mode voltage or current needs to be defined locally:

- Local brute-force common-mode biasing

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

Common-mode voltage or current can be defined in one stage:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

- Local common-mode feedback biasing

Over-all common-mode feedback can be applied as error-reduction technique

Low-pass filtering is not required if common-mode to differential-mode conversion is negligible

Else:

Common-mode voltage or current needs to be defined locally:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

Common-mode voltage or current can be defined in one stage:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

- Local common-mode feedback biasing

Over-all common-mode feedback can be applied as error-reduction technique

Low-pass filtering is not required if common-mode to differential-mode conversion is negligible

Else:

Common-mode voltage or current needs to be defined locally:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

- Local common-mode feedback biasing

# Define common-mode quantities

Common-mode biasing errors only propagate if:

- Stages are DC coupled

- Stages have common-mode transfer or common-mode to differential-mode conversion

If over-all (source-to-load) common-mode transfer exists:

Common-mode voltage or current can be defined in one stage:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

- Local common-mode feedback biasing

Over-all common-mode feedback can be applied as error-reduction technique

Low-pass filtering is not required if common-mode to differential-mode conversion is negligible

Else:

Common-mode voltage or current needs to be defined locally:

- Local brute-force common-mode biasing

- Local model-based common-mode biasing

- Local common-mode feedback biasing