Structured Electronic Design

CS stage: Noise optimization with a resistive source

Anton J.M. Montagne





 v_n : total source-referred noise



 v_n : total source-referred noise $S_{v_n} = 4kTR_s + \left|B + DR_s\right|^2 S_{id}$



 v_n : total source-referred noise $S_{v_n} = 4kTR_s + \left|B + DR_s\right|^2 S_{id}$ $S_{v_n} = 4kTR_s + \left|\frac{1}{g_m} + \frac{jf}{f_T}R_s\right|^2 S_{id}$



 v_n : total source-referred noise $S_{v_n} = 4kTR_s + |B + DR_s|^2 S_{id}$ $S_{v_n} = 4kTR_s + \left|\frac{1}{g_m} + \frac{jf}{f_T}R_s\right|^2 S_{id}$ $S_{v_n} = 4kTR_s + \left(\frac{1}{g_m^2} + \frac{f^2}{f_T^2}R_s^2\right)S_{id}$



 v_n : total source-referred noise $S_{v_{n}} = 4kTR_{s} + |B + DR_{s}|^{2} S_{id}$ $S_{v_n} = 4kTR_s + \left|\frac{1}{g_m} + \frac{jf}{f_T}R_s\right|^2 S_{id}$ $S_{v_n} = 4kTR_s + \left(\frac{1}{g_m^2} + \frac{f^2}{f_T^2}R_s^2\right)S_{id}$ $S_{v_n} = 4kT \left(R_s + \frac{n\Gamma}{g_m} + \frac{f^2}{f_T^2} R_s^2 g_m n\Gamma \right)$













$$\overline{v_n^2} = \int_{f_{min}}^{f_{max}} 4kT \left(R_s + \frac{n\Gamma}{g_{m_0}} \frac{W_0}{W} + \frac{f^2}{f_T^2} R_s^2 n\Gamma g_{m_0} \frac{W}{W_0} \right) dr$$

df

$$\overline{v_n^2} = \int_{f_{min}}^{f_{max}} 4kT \left(R_s + \frac{n\Gamma}{g_{m_0}} \frac{W_0}{W} + \frac{f^2}{f_T^2} R_s^2 n\Gamma g_{m_0} \frac{W}{W_0} \right)$$

 g_{m_0} small-signal transconductance at width W_0

df

$$\overline{v_n^2} = \int_{f_{min}}^{f_{max}} 4kT \left(R_s + \frac{n\Gamma}{g_{m_0}} \frac{W_0}{W} + \frac{f^2}{f_T^2} R_s^2 n\Gamma g_{m_0} \frac{W}{W_0} \right)$$

 g_{m_0} small-signal transconductance at width W_0

$$F = \frac{\overline{v_n^2}}{4kTR_s(f_{max} - f_{min})}$$

df

$$\overline{v_n^2} = \int_{f_{min}}^{f_{max}} 4kT \left(R_s + \frac{n\Gamma}{g_{m_0}} \frac{W_0}{W} + \frac{f^2}{f_T^2} R_s^2 n\Gamma g_{m_0} \frac{W}{W_0} \right).$$

 g_{m_0} small-signal transconductance at width W_0

$$F = \frac{\overline{v_n^2}}{4kTR_s(f_{max} - f_{min})}$$

Lowest value at maximum inversion coefficient and optimum device width

df

$$\overline{v_n^2} = \int_{f_{min}}^{f_{max}} 4kT \left(R_s + \frac{n\Gamma}{g_{m_0}} \frac{W_0}{W} + \frac{f^2}{f_T^2} R_s^2 n\Gamma g_{m_0} \frac{W}{W_0} \right).$$

 g_{m_0} small-signal transconductance at width W_0

$$F = \frac{\overline{v_n^2}}{4kTR_s(f_{max} - f_{min})}$$

Lowest value at maximum inversion coefficient and optimum device width

df

Book example 5.10

Book example 5.10

SLiCAP determination of optimum width and noise figure for 6000hm at critical inversion

Book example 5.10

SLiCAP determination of optimum width and noise figure for 6000hm at critical inversion Book example 5.11

Book example 5.10

SLiCAP determination of optimum width and noise figure for 6000hm at critical inversion

Book example 5.11

Spice determination of optimum width and noise figure for 6000hm at critical inversion

Book example 5.10

SLiCAP determination of optimum width and noise figure for 6000hm at critical inversion

Book example 5.11

Spice determination of optimum width and noise figure for 6000hm at critical inversion

Spice circuit:

Book example 5.10

SLiCAP determination of optimum width and noise figure for 6000hm at critical inversion

Book example 5.11

Spice determination of optimum width and noise figure for 6000hm at critical inversion

Spice circuit:



Book example 5.10

SLiCAP determination of optimum width and noise figure for 6000hm at critical inversion

Book example 5.11

Spice determination of optimum width and noise figure for 6000hm at critical inversion

Spice circuit: Results depend on library models!



Book example 5.10

SLiCAP determination of optimum width and noise figure for 6000hm at critical inversion

Book example 5.11

Spice determination of optimum width and noise figure for 6000hm at critical inversion

Spice circuit: Results depend on library models!

