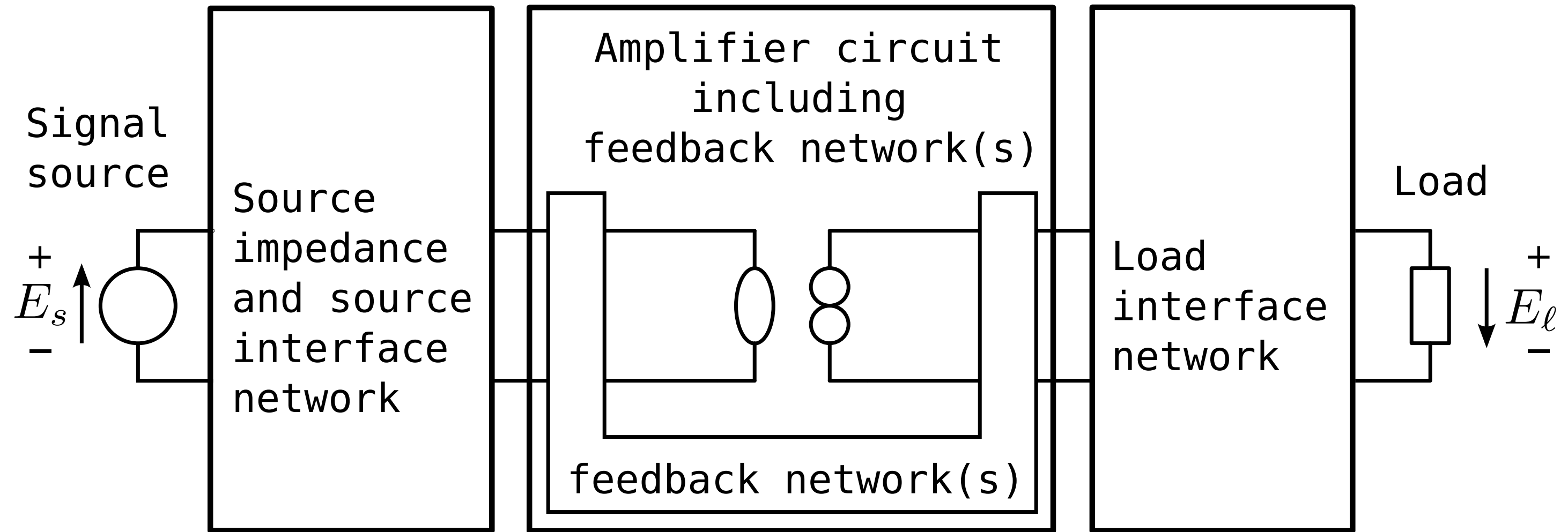


# **Structured Electronic Design**

## Noise Design of Input Stage MOS in Feedback Amplifiers

*Anton J.M. Montagne*

# Structure Feedback Amplifier




Known at the start of the controller's noise design

Source impedance  
Load impedance  
Feedback network(s)

Source interface network  
Load interface network  
Output noise weighting function

# Noise Transfer Functions

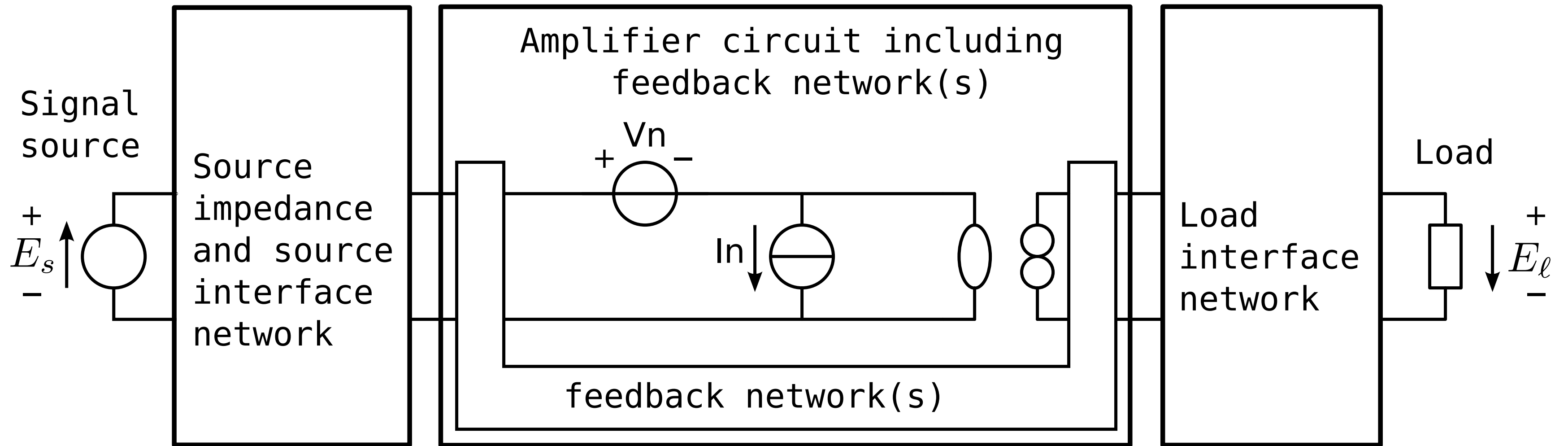

$H_v(f)$ : Transfer function from  $V_n$  to the output noise  $e_{\ell_n}$

$H_i(f)$ : Transfer function from  $I_n$  to the output noise  $e_{\ell_n}$


$\frac{H_i(f)}{H_v(f)} = Z_n(f)$ : Driving-point impedance at nullor input.

$W(f)$ : Noise weighting function

$$e_{\ell_n}^2 = \int_{f_{\min}}^{f_{\max}} S_{v_n} |H_v(f)W(f)|^2 df + \int_{f_{\min}}^{f_{\max}} S_{i_n} |H_i(f)W(f)|^2 df + \int_{f_{\min}}^{f_{\max}} S_0 |W(f)|^2 df$$

Contribution of  $V_n$  to the weighted output noise
Contribution of  $I_n$  to the weighted output noise
Contribution of the source, the feedback and the interface network(s) to the weighted output noise

# MOS Noise Model

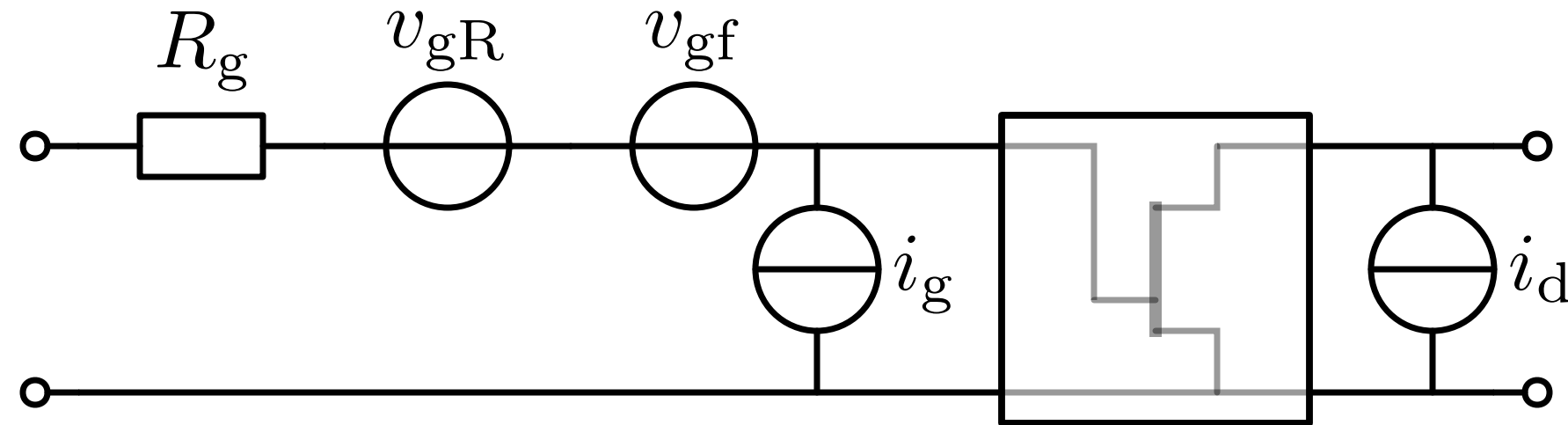

$R_g$ : gate (series) resistance


$v_{gR}$ : noise voltage gate (series) resistance:  $S_{v_{gR}} = 4kTR_g \text{ V}^2/\text{Hz}$

$v_{gf}$ : input-referred flicker noise voltage:  $S_{v_{gf}} = \frac{K_F}{C_{OX}^2 W L f^{AF}} \text{ V}^2/\text{Hz}$

$i_g$ : gate leakage current noise:  $S_{i_g} = 2qI_G \text{ A}^2/\text{Hz}$

$i_d$ : channel current noise:  $S_{i_d} = 4kTn\Gamma g_m \text{ A}^2/\text{Hz}$

# MOS Noise Transformations-1

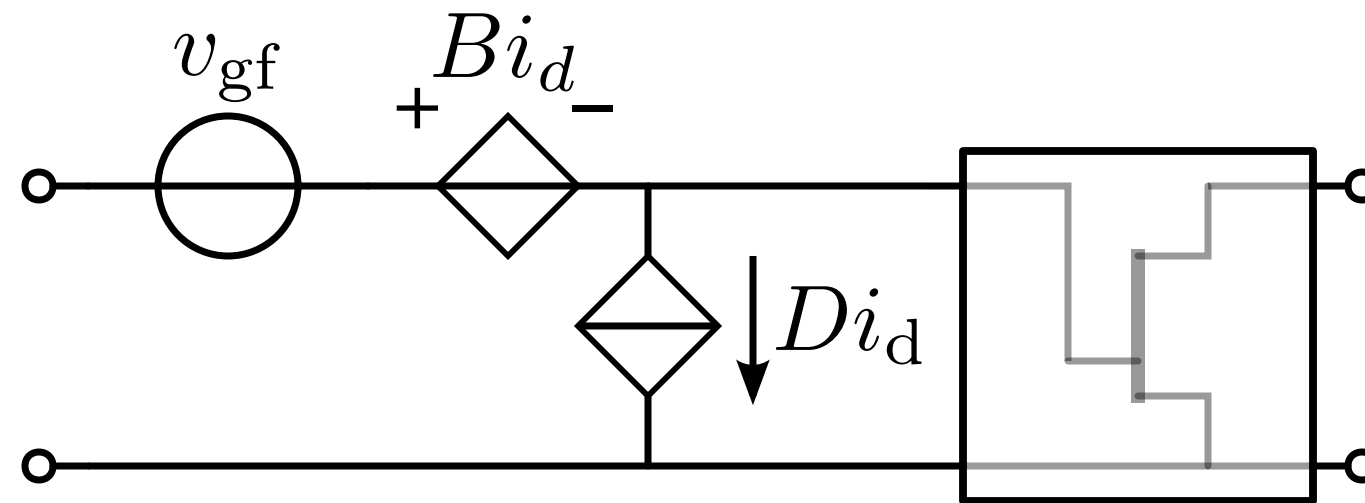


$$B = \frac{1}{j2\pi f c_{dg} - g_m} \approx \frac{1}{g_m}$$

$$D = \frac{j2\pi f c_{iss}}{j2\pi f c_{dg} - g_m} \approx \frac{j2\pi f c_{iss}}{g_m}$$

Negative signs accounted for in the source directions

# MOS Noise Transformations-2

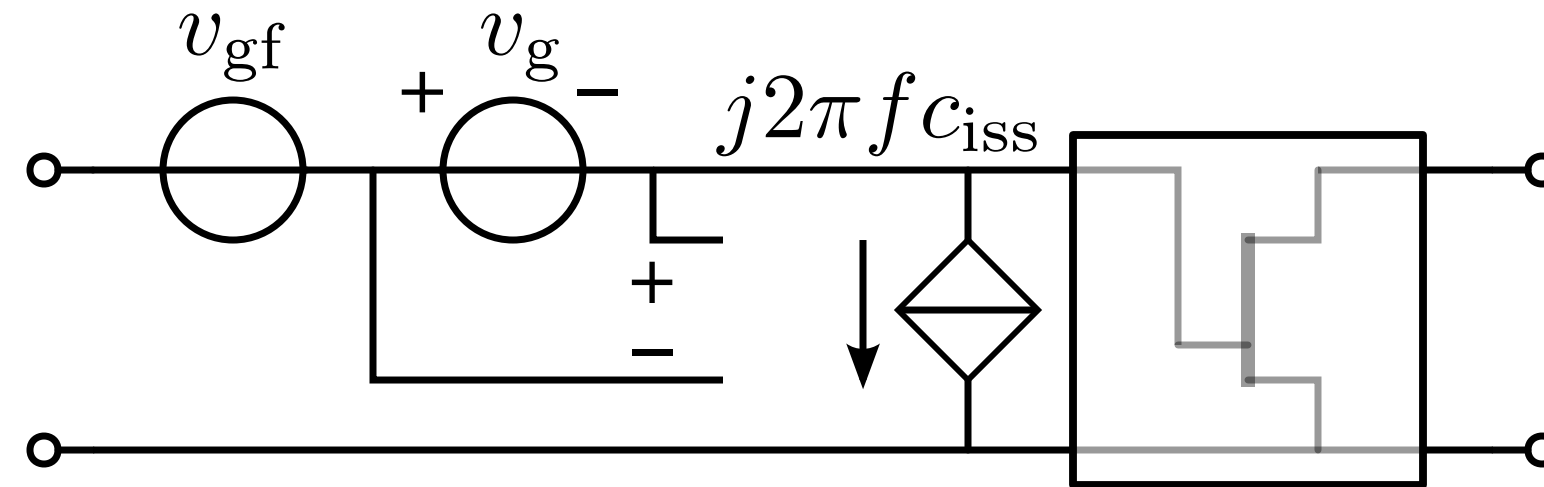

$$S_{v_g} = \frac{4kTn\Gamma}{g_m}$$

Ignore the overlap capacitances:  
the input capacitance is proportional with the oxide capacitance:

$$c_{iss} = \chi W L C_{OX} \quad S_{v_{gf}} = \frac{K_F}{C_{OX}^2 W L f^{AF}} \approx \frac{\chi K_F}{C_{OX} c_{iss} f^{AF}} \text{ V}^2/\text{Hz}$$


$\chi$ ,  $\Gamma$  and  $K_F$  depend on the inversion level

$\chi = 0.26 \dots 0.6$  with  $IC = 0 \dots \infty$  and  $n = 1.35$

$\Gamma = \frac{1}{2} \dots \frac{2}{3}$  with  $IC = 0 \dots \infty$

$S_{v_g}$  and  $S_{v_{gf}}$  are now expressed in the MOS design parameters  $g_m$  and  $c_{iss}$

# Feedback amplifier MOS Noise

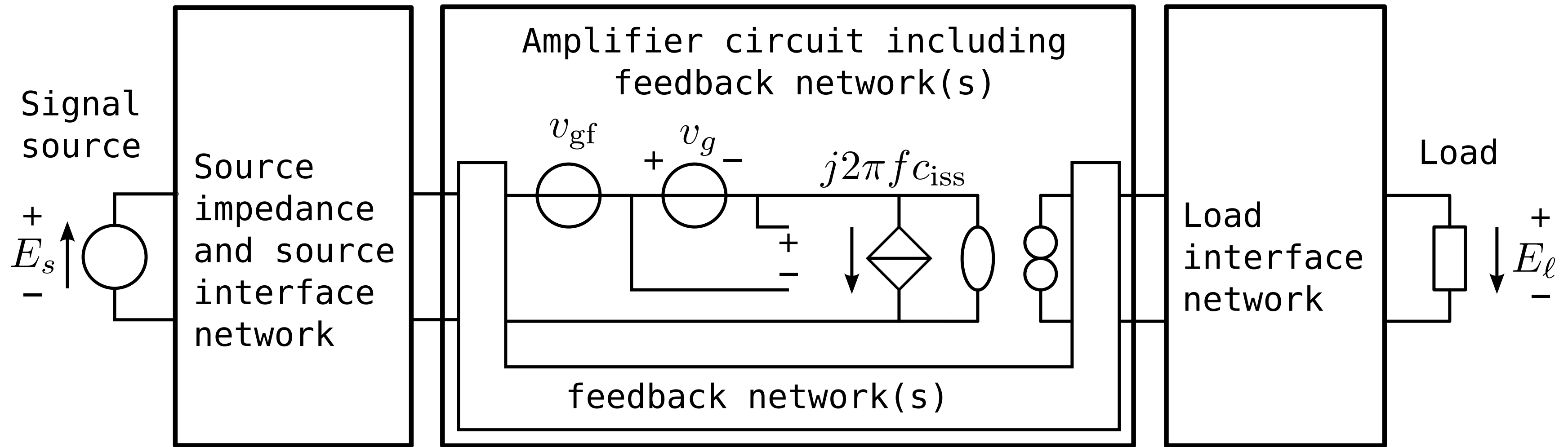

$$S_{v_g} = \frac{4kTn\Gamma}{g_m} \quad \text{V}^2/\text{Hz}$$

$$S_{v_{gf}} = \frac{\chi K_F}{C_{OX} c_{iss} f^{AF}} \quad \text{V}^2/\text{Hz}$$

Next step: determine MOS parameters  $g_m$  and  $c_{iss}$  at a given inversion level

# Feedback amplifier MOS noise design equation

Unweighted output noise spectrum

$$S_{el} = \frac{\chi K_F}{C_{OX}} \frac{1}{c_{iss} f^{AF}} |H_v|^2 + \frac{4kTn\Gamma}{g_m} |H_v + H_i 2\pi j f c_{iss}|^2 + S_0$$

$$\begin{aligned} S_{el} = & \frac{1}{c_{iss}} \frac{\chi K_F |H_v|^2}{C_{OX} f^{AF}} \\ & + \frac{1}{g_m} 4kTn\Gamma |H_v|^2 \\ & + \frac{c_{iss}}{g_m} 16kTn\Gamma \pi f (\Im(H_v) \Re(H_i) - \Re(H_v) \Im(H_i)) \\ & + \frac{c_{iss}^2}{g_m} 16kTn\Gamma \pi^2 f^2 |H_i|^2 \\ & + S_0 \end{aligned}$$

$$e_\ell^2 = \int_0^\infty |W_f|^2 S_{no} df$$

$$e_\ell^2 = \alpha \frac{1}{c_{iss}} + \beta \frac{1}{g_m} + \gamma \frac{c_{iss}}{g_m} + \delta \frac{c_{iss}^2}{g_m} + \epsilon$$

# Feedback amplifier MOS noise design equation

$$e_{\ell}^2 = \alpha \frac{1}{c_{iss}} + \beta \frac{1}{g_m} + \gamma \frac{c_{iss}}{g_m} + \delta \frac{c_{iss}^2}{g_m} + \epsilon$$

$$\alpha = \frac{\chi K_F}{C_{OX}} \int_0^{\infty} \frac{|W_f H_v|^2}{f^{AF}} df$$

$$\beta = 4kTn\Gamma \int_0^{\infty} |W_f H_v|^2 df$$

$$\gamma = 16kTn\Gamma\pi \int_0^{\infty} f |W_f|^2 [\Im(H_v)\Re(H_i) - \Re(H_v)\Im(H_i)] df = -16kTn\Gamma\pi \int_0^{\infty} f |W_f|^2 \Im(Z_n) |H_v|^2 df$$

$$\delta = 16kTn\Gamma\pi^2 \int_0^{\infty} f^2 |W_f H_i|^2 df$$

$$\Im(Z_n) = \frac{\Im(H_i)\Re(H_v) - \Re(H_i)\Im(H_v)}{|H_v|^2}$$

$$\epsilon = \int_0^{\infty} |W_f|^2 S_0 df$$

Coefficients  $\alpha \cdots \epsilon$  have numeric values at the start of the MOS noise design.

# Feedback amplifier MOS noise design equation

Total squared weighted output noise:

$$e_{\ell}^2 = \alpha \frac{1}{c_{iss}} + \beta \frac{1}{g_m} + \gamma \frac{c_{iss}}{g_m} + \delta \frac{c_{iss}^2}{g_m} + \epsilon$$

MOS contribution to squared weighted output noise:

$$e_{\ell M}^2 = \alpha \frac{1}{c_{iss}} + \beta \frac{1}{g_m} + \gamma \frac{c_{iss}}{g_m} + \delta \frac{c_{iss}^2}{g_m}$$


Remember coefficients depend on inversion level!

Relation between transconductance and input capacitance to meet requirement:

$$g_m \geq \frac{c_{iss}}{e_{\ell M}^2 c_{iss} - \alpha} (\beta + \gamma c_{iss} + \delta c_{iss}^2)$$

This noise design equation has one minimum transconductance for:  $c_{iss} > \frac{\alpha}{e_{\ell M}^2}$

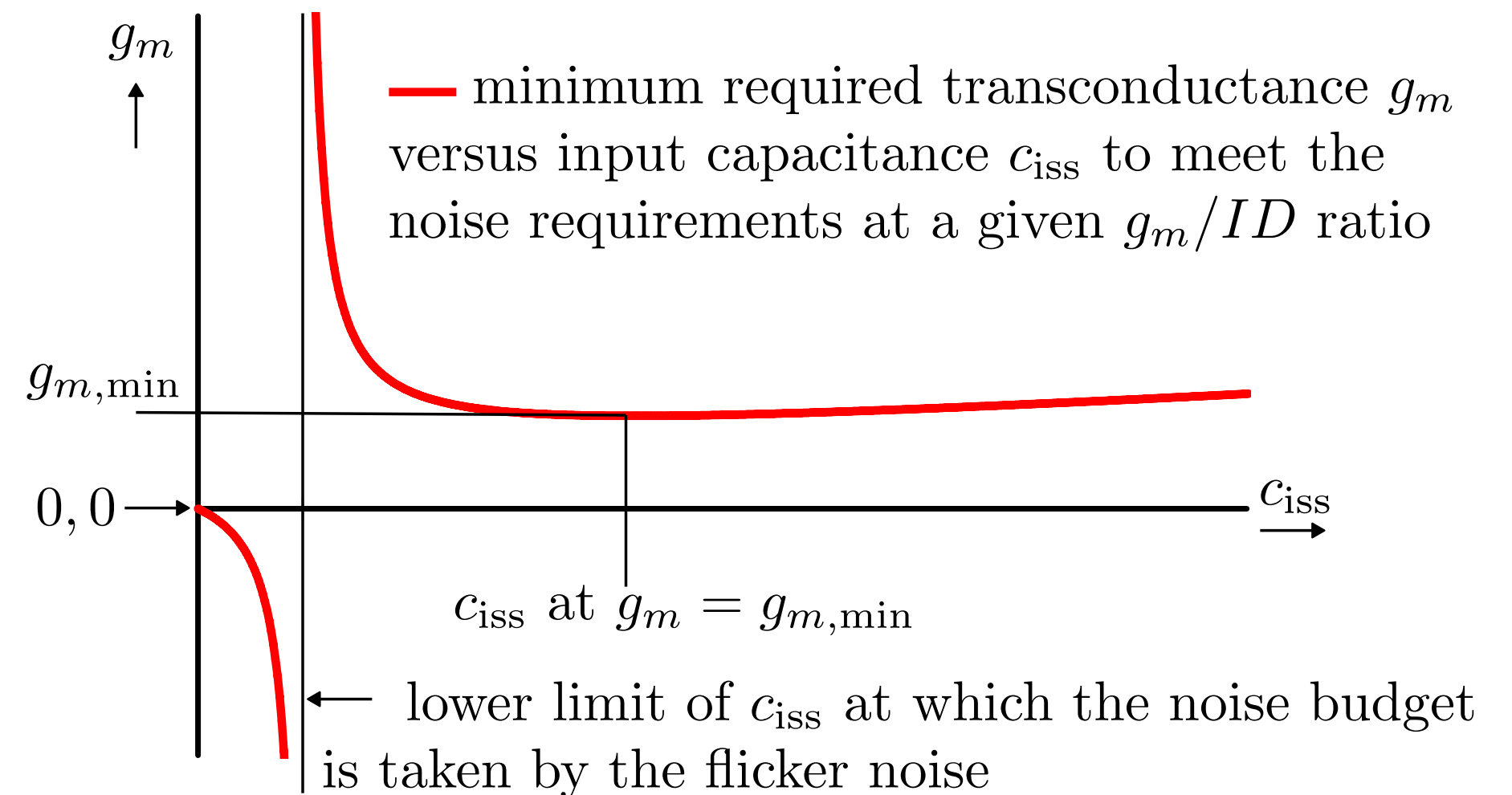Minimum can be below technological minimum set by the minimum channel width and length.



# Feasibility of the noise design

Total squared weighted output noise:

$$e_{\ell}^2 = \alpha \frac{1}{c_{iss}} + \beta \frac{1}{g_m} + \gamma \frac{c_{iss}}{g_m} + \delta \frac{c_{iss}^2}{g_m} + \epsilon$$

MOS contribution to squared weighted output noise:

$$e_{\ell M}^2 = \alpha \frac{1}{c_{iss}} + \beta \frac{1}{g_m} + \gamma \frac{c_{iss}}{g_m} + \delta \frac{c_{iss}^2}{g_m}$$

NOT

FEASIBLE:

If  $\epsilon$  exceeds the requirement for the total squared weighted output noise.

If  $f_T = \frac{g_m}{2\pi c_{iss}}$  is too low.

$$e_{\ell}^2 = \frac{\alpha}{c_{iss}} + \frac{\beta}{2\pi f_T c_{iss}} + \frac{\gamma}{2\pi f_T} + \frac{\delta c_{iss}}{2\pi f_T} + \epsilon \quad c_{issOpt} = \sqrt{\frac{2\pi f_T \alpha + \beta}{\delta}}.$$

Lowest noise:

$$e_{\ell}^2 = \frac{\alpha}{c_{issOpt}} + \frac{\beta}{2\pi f_{Tmax} c_{issOpt}} + \frac{\gamma}{2\pi f_{Tmax}} + \frac{\delta c_{issOpt}}{2\pi f_{Tmax}} + \epsilon$$

Area and current limitations may put extra constraints to the feasibility.

# From transconductance and capacitance to current and geometry

$$c_{\text{iss}} = \chi C_{\text{OX}} W L + W (C_{\text{GSO}} + C_{\text{GDO}}) + 2 L C_{\text{GBO}}$$

$$\chi = \frac{2-x}{3} + \frac{(1+x)(n-1)}{3n}$$

$$x = \frac{\sqrt{IC} + 0.25 + 1.5}{(\sqrt{IC} + 0.25 + 0.5)^2}$$

$$I_{\text{DS}} = IC \frac{W}{L} I_0 \quad I_0 \triangleq 2n\mu_0 C_{\text{OX}} V_T^2$$

$$\frac{g_m}{I_{\text{DS}}} = \frac{1}{nV_T \sqrt{IC \left(1 + \frac{IC}{IC_{\text{crit}}}\right) + 0.5 \sqrt{IC \left(1 + \frac{IC}{IC_{\text{crit}}}\right) + 1}}}$$

Ignore lateral field velocity saturation:

$$IC_{\text{crit}} = (4nV_T\theta)^{-2}$$

$$c_{\text{iss}} = aWL + bW + cL$$

$$g_m = d \frac{W}{L}$$

$$a = \chi C_{\text{OX}}$$

$$b = C_{\text{GSO}} + C_{\text{GDO}}$$

$$c = 2C_{\text{GBO}}$$

$$d = \frac{2\mu_0 C_{\text{OX}} IC}{\sqrt{IC \left(1 + \frac{IC}{IC_{\text{crit}}}\right) + 0.5 \sqrt{IC \left(1 + \frac{IC}{IC_{\text{crit}}}\right) + 1}}}$$


$$W = \frac{cd + bg_m}{2ad} \left( \sqrt{1 + \frac{4adg_m c_{\text{iss}}}{(cd + bg_m)^2}} - 1 \right) \approx \sqrt{\frac{g_m c_{\text{iss}}}{ad}}$$

$$L = \frac{cd + bg_m}{2ag_m} \left( \sqrt{1 + \frac{4adg_m c_{\text{iss}}}{(cd + bg_m)^2}} - 1 \right) \approx \sqrt{\frac{d c_{\text{iss}}}{ag_m}}$$

$$I_{\text{DS}} = \frac{1}{g_m / I_{\text{DS}}} g_m$$

# Example
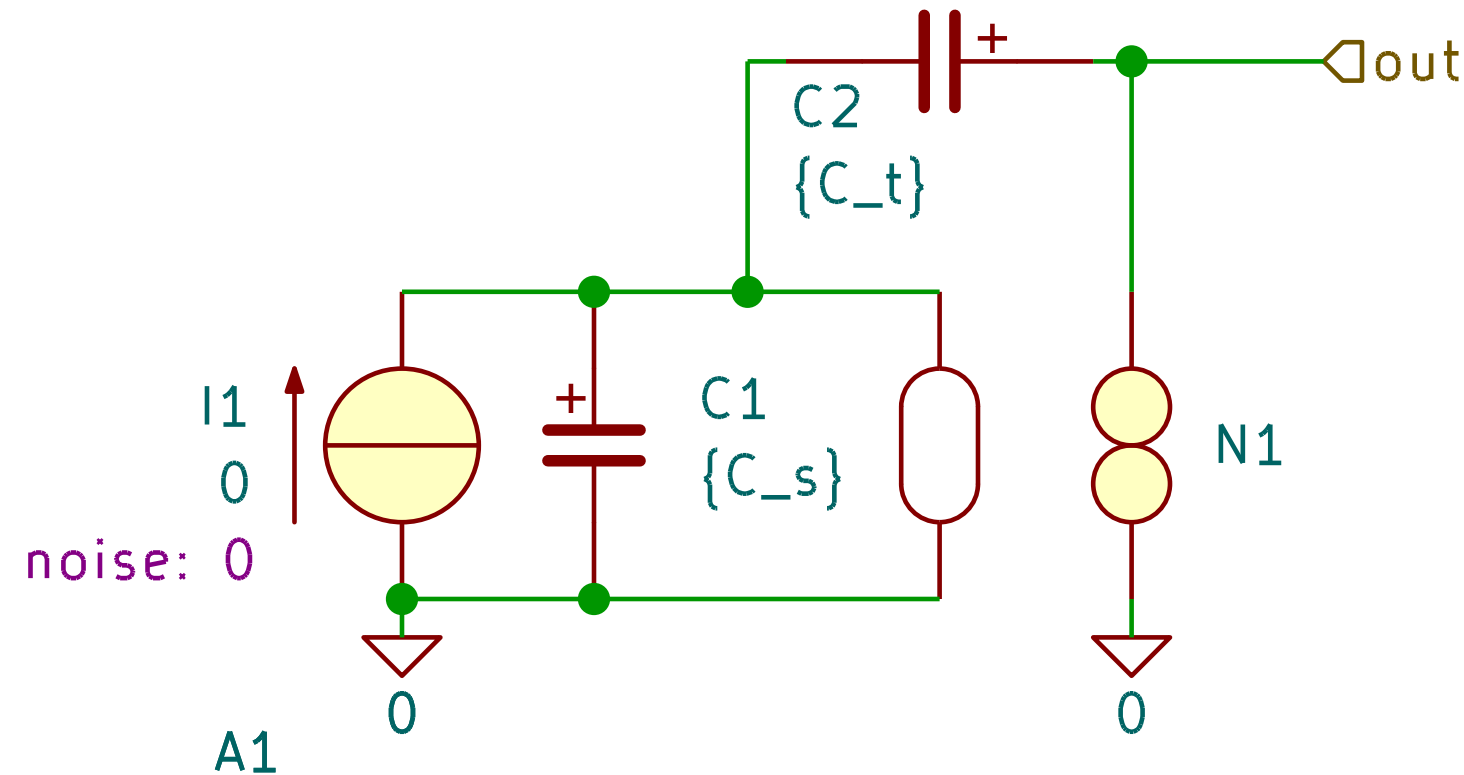
## Transimpedance integrator with capacitive source



If we ignore flicker noise:

$$C_{issOpt} = \sqrt{\frac{\beta}{\delta}} = C_s + C_t = 1.2 \text{ pF}$$

$$v_{n_{out}}^2 = \frac{16kTn\Gamma}{g_m} \left( \frac{C_s + C_t}{C_t} \right)^2 (f_{max} - f_{min})$$

Coefficients of the symbolic noise equation (determined with SLiCAP):

term coefficient

$$\frac{1}{C_{iss}} \quad \alpha = \int_{f_{min}}^{f_{max}} \frac{K_F \chi f^{-A_F} (C_s + C_t)^2}{C_{OX} C_t^2} df$$

$$\frac{1}{g_m} \quad \beta = \int_{f_{min}}^{f_{max}} \frac{4\Gamma T k n (C_s + C_t)^2}{C_t^2} df$$


$$\frac{C_{iss}}{g_m} \quad \gamma = \int_{f_{min}}^{f_{max}} \frac{8\Gamma T k n (C_s + C_t)}{C_t^2} df$$

$$\frac{C_{iss}^2}{g_m} \quad \delta = \int_{f_{min}}^{f_{max}} \frac{4\Gamma T k n}{C_t^2} df$$

$$1 \quad \epsilon = 0$$



# SLiCAP design automation

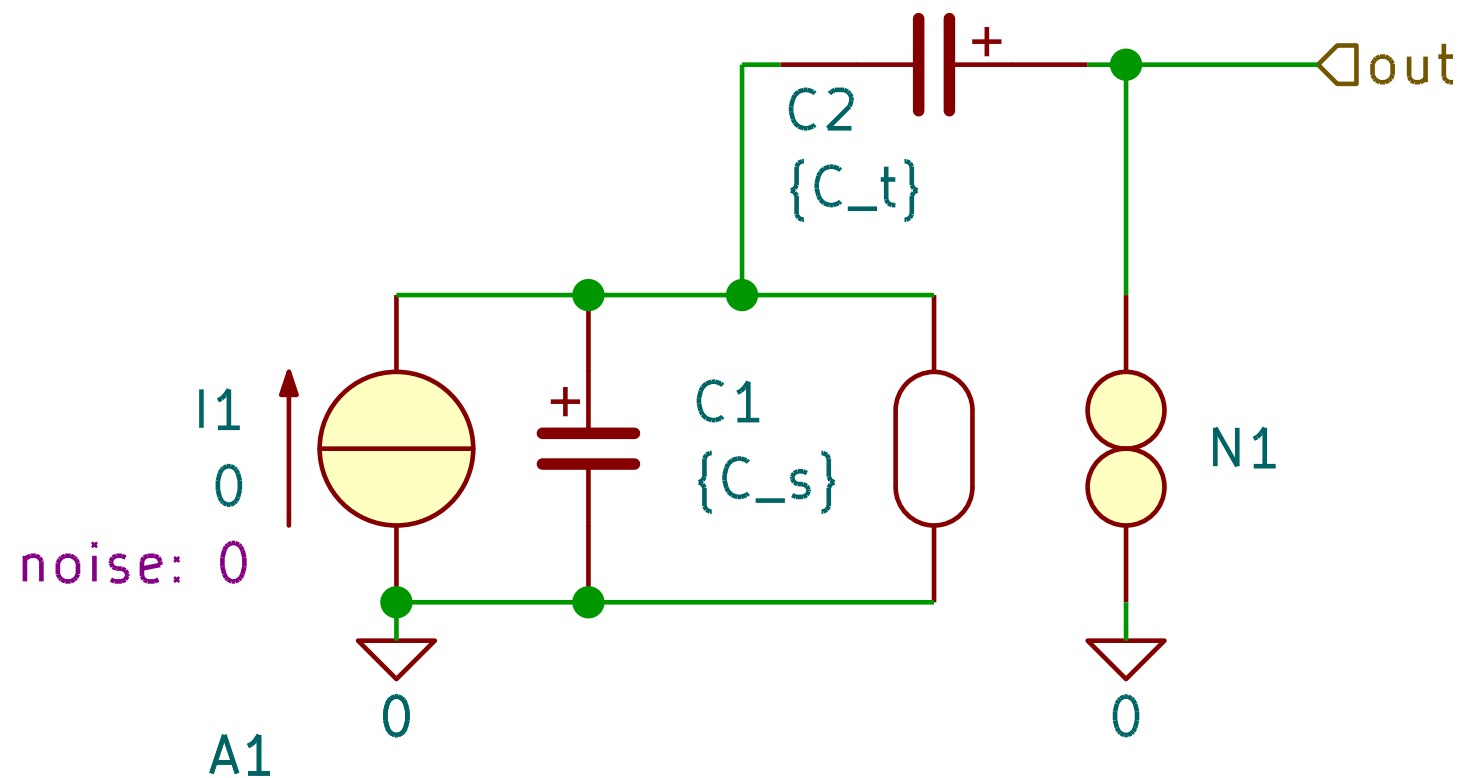

.detector V\_out

A2

.param C\_s=1p C\_t=0.2p IG=0

1. Select CMOS process and fit EKV parameters to BSIM
2. Create KiCAD amplifier circuit with nullor as controller
3. Define noise requirements (frequency range and budgets)
4. Define technology requirements  
(channel type, minimum and maximum geometry)
5. Define circuit requirements  
(inversion coefficient or gm/ID ratio, and current budget)
6. Run the design automation script
7. Select one valid option for design

SLiCAP replaces the nullor with an N-channel or a P-channel noisy nullor and evaluates  $W$ ,  $L$ , and  $I_{DS}$  for six scenarios for the selected inversion coefficient or gm/ID ratio:

1. Minimum noise at maximum inversion level
2. Minimum current to meet the noise specification
3. Minimum cut-off frequency to meet the noise specification
4. Minimum product of  $g_m$  and  $c_{iss}$  to meet the noise specification
5. Minimum area at a given current budget to meet the noise specification
6. Maximum area at a given current budget to meet the noise specification