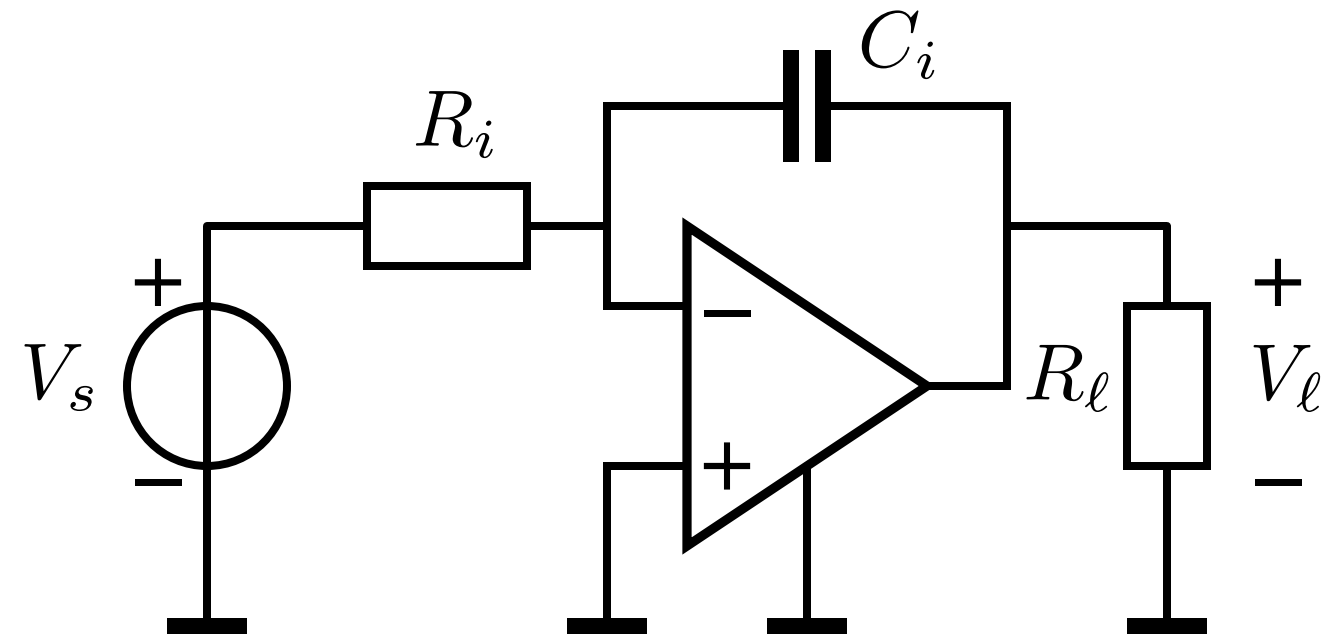


Structured Electronic Design

Example:
Bandwidth of a
Negative Feedback Integrator

Anton J.M. Montagne

Example integrator bandwidth




OpAmp modeled as VCVS:

$$A_v = \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$$

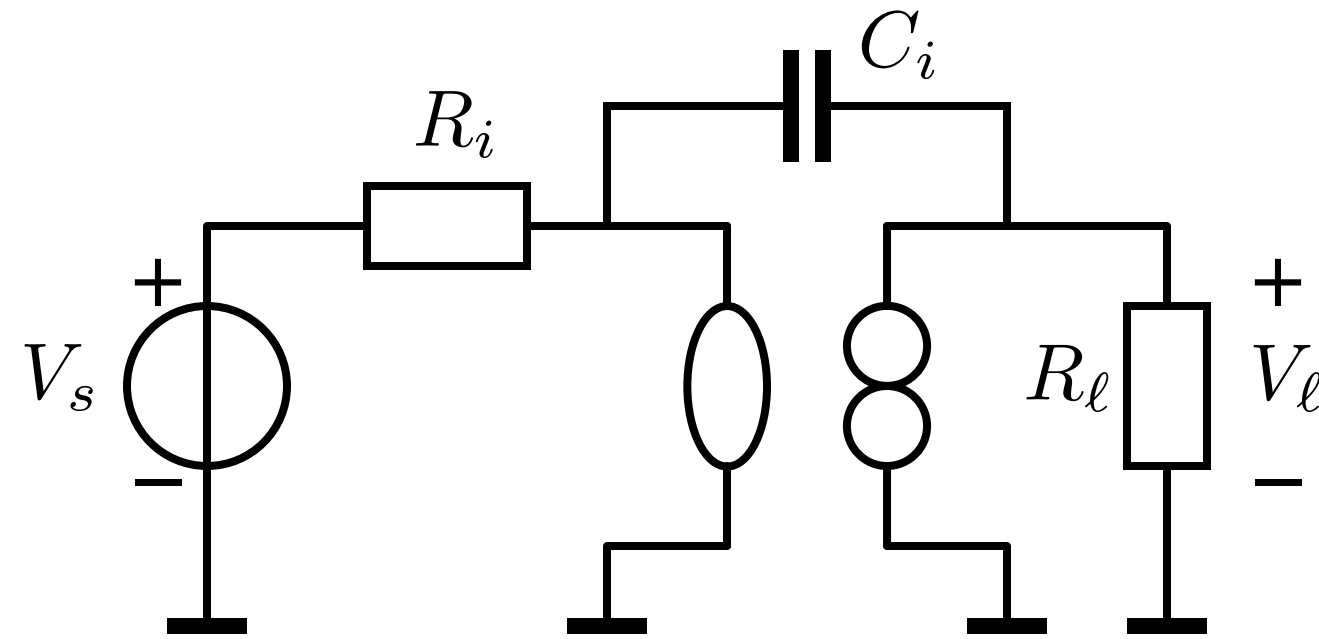Example integrator bandwidth


Ideal gain: replace controller with a nullor:



$$\frac{V_\ell}{V_s} = -\frac{1}{sR_iC_i}$$

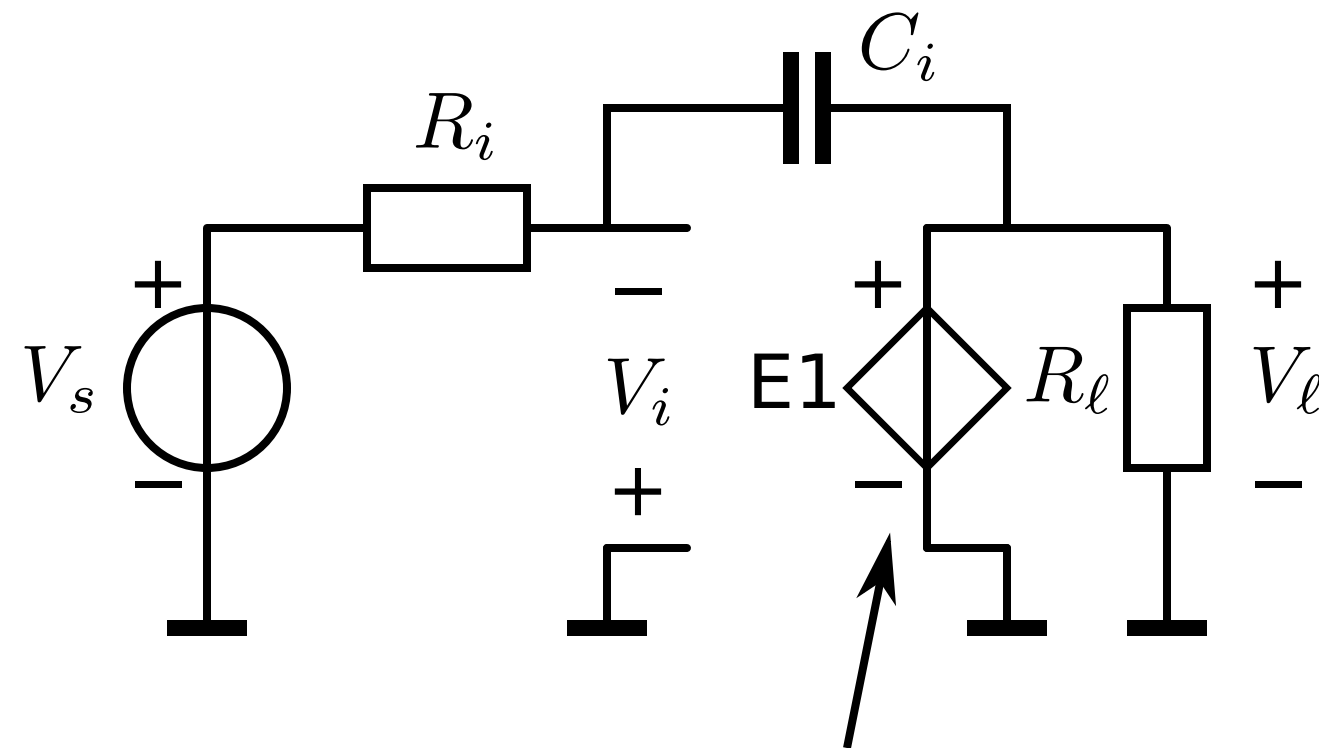Example integrator bandwidth


Select loop gain reference such that the asymptotic gain equals the ideal gain



$$V_i \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$$

Example integrator bandwidth


Evaluate the loop gain:

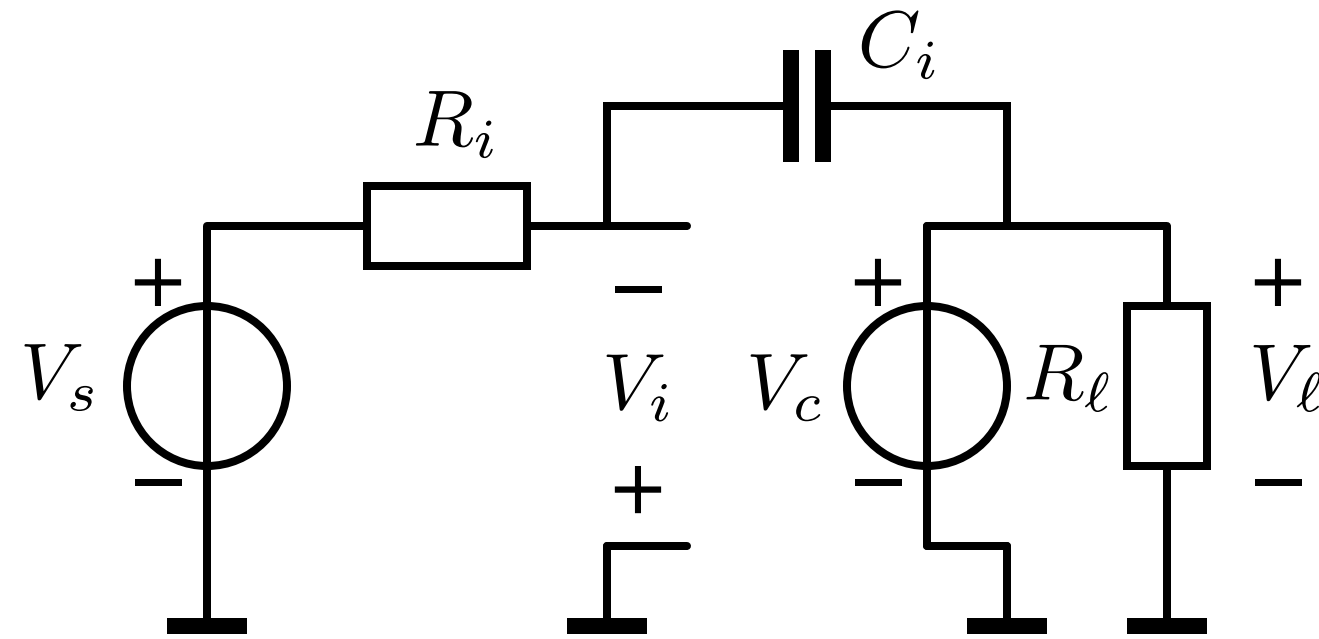

$$A_{\text{ref}} = \frac{A_0}{1 + s \frac{A_0}{2\pi \text{GB}}}$$

$$\lambda\beta\kappa = \left. \frac{V_i}{V_c} \right|_{V_s=0} = -\frac{sR_iC_i}{1 + sR_iC_i} \quad L = -\frac{sR_iC_i}{1 + sR_iC_i} \frac{A_0}{1 + s \frac{A_0}{2\pi \text{GB}}}$$


Example integrator bandwidth

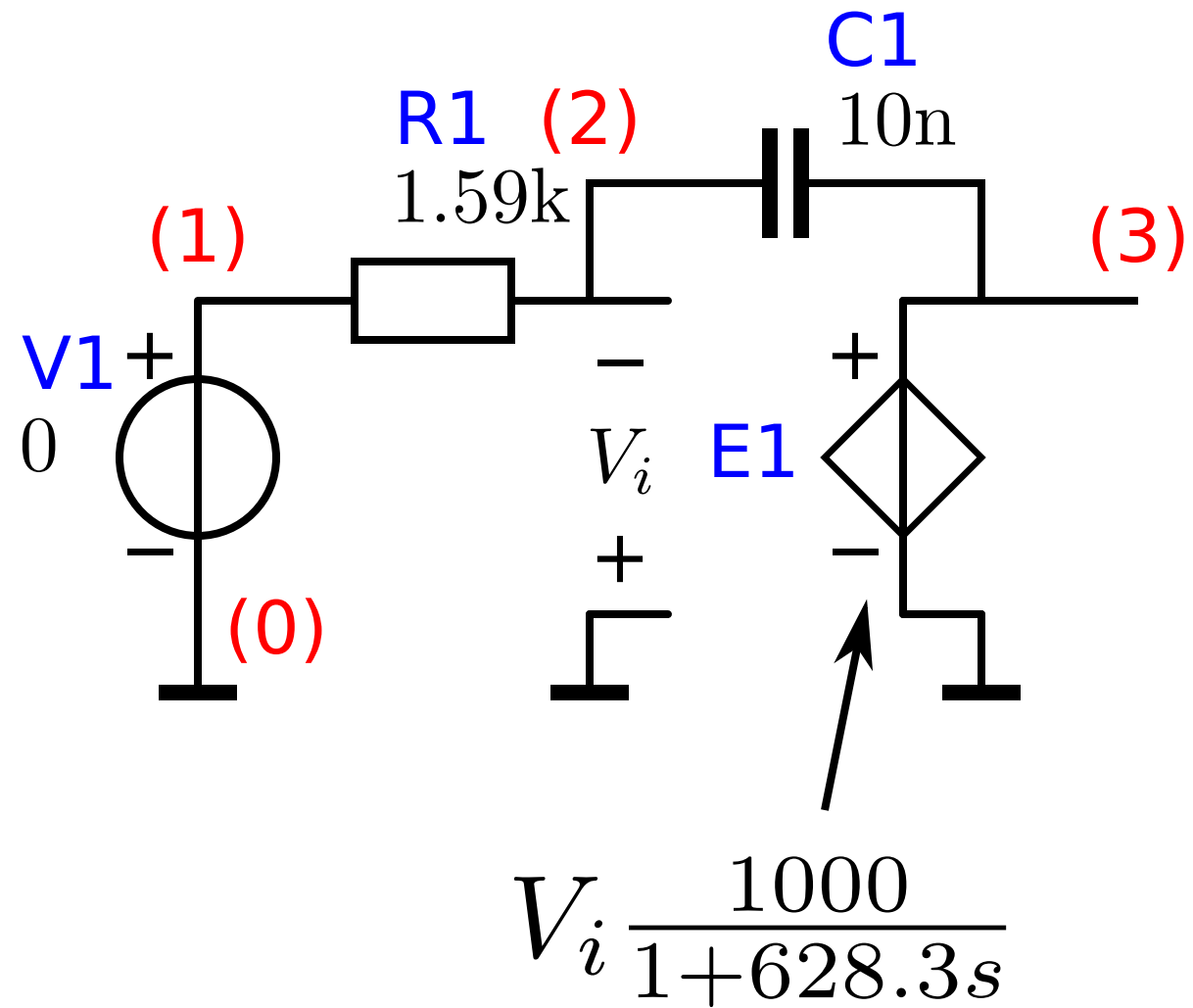

Integrator

```

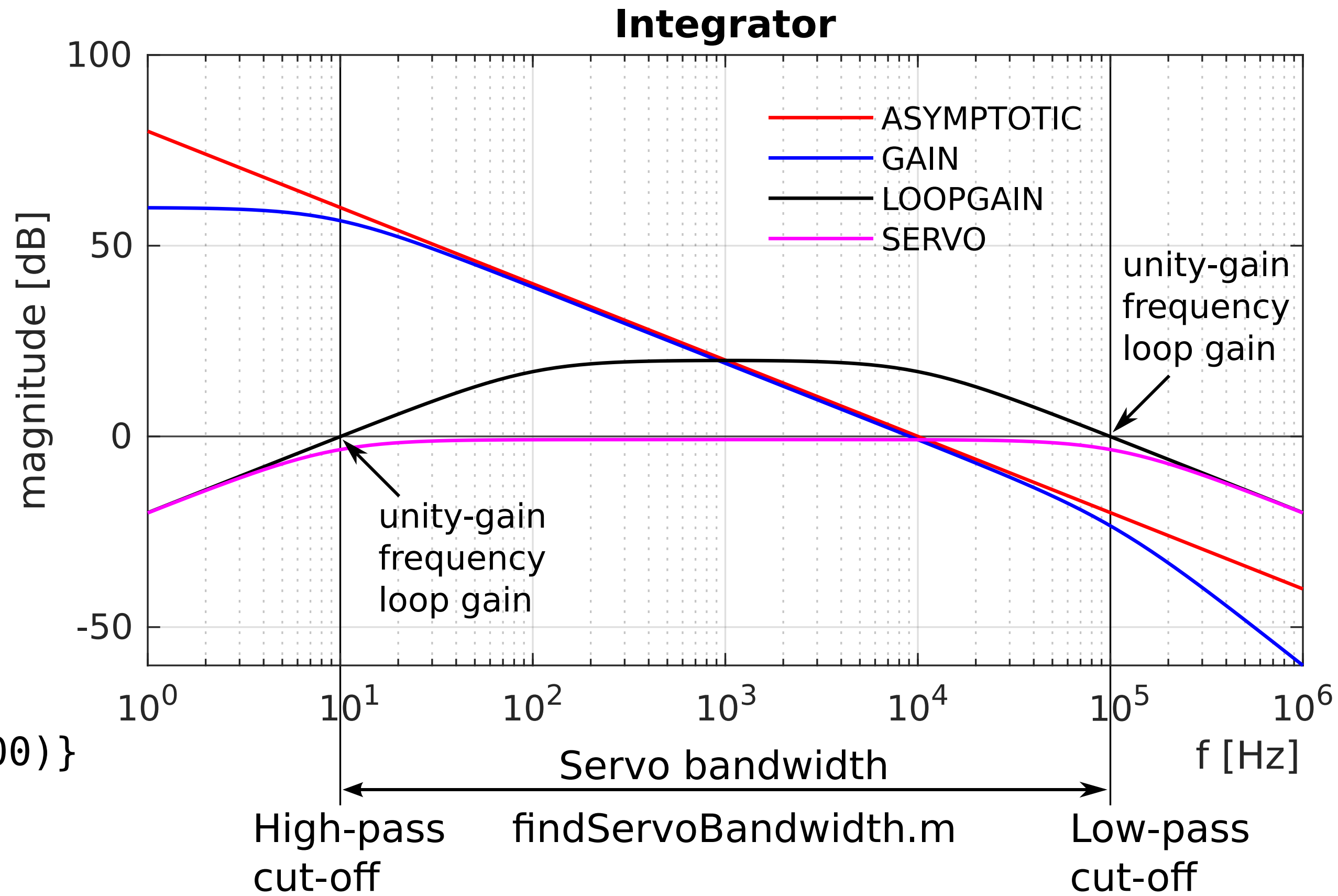V1 1 0 0
R1 1 2 1.59k
C1 2 3 10n
E1 3 0 0 2 {1k/(1+s/2/pi/100)}
.end
    
```



Design questions



In which way, and to what extent does the controller contribute to the bandwidth of the servo function?



The product of the DC loop gain and the dominant poles of the loop gain, determines the bandwidth of the servo function



The contribution of the controller to this product should be large enough