
Structured Electronic Design

Asymptotic-gain feedback model

Anton J.M. Montagne


Superposition model

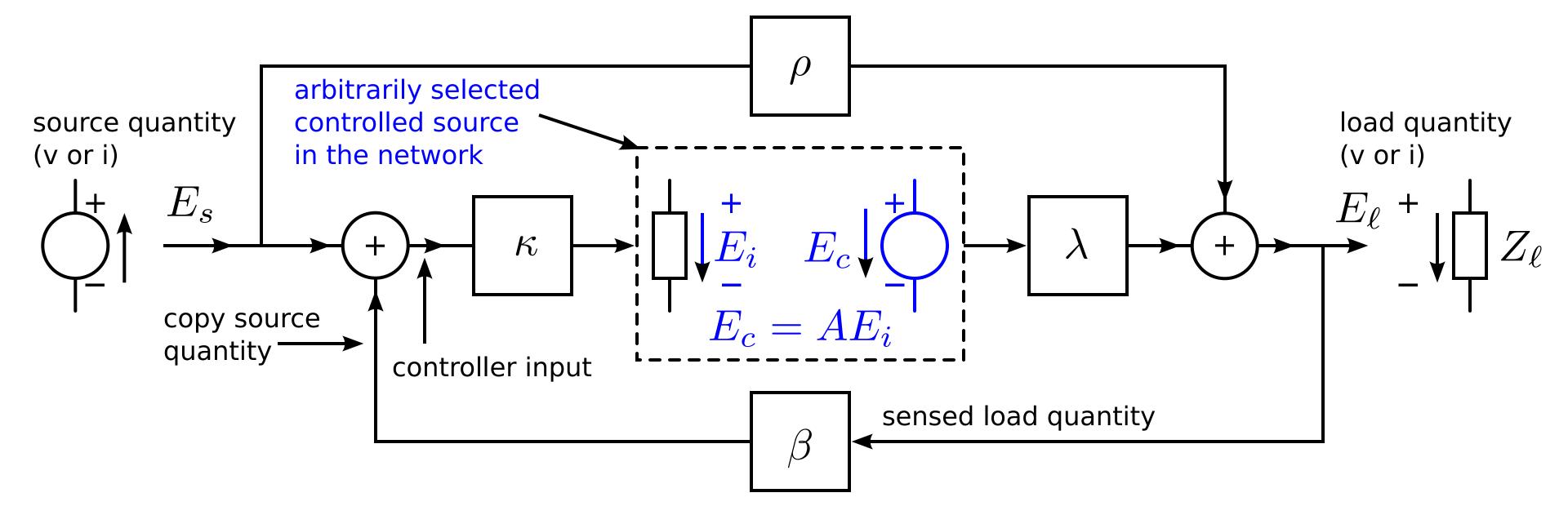

The loop is 'opened' by replacing this controlled source with an independent source, while denoting:

$$E_c = AE_i$$

Superposition model

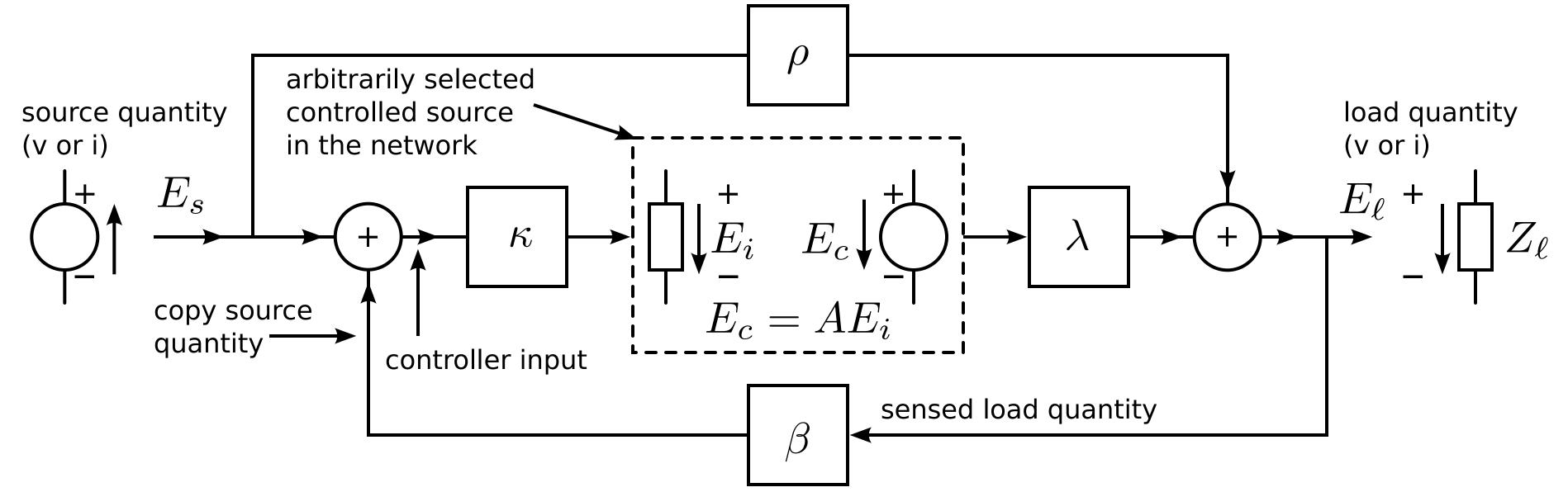


We now have the following equations:

$$\begin{pmatrix} E_{\ell} \\ E_{i} \end{pmatrix} = \begin{pmatrix} \rho & \lambda \\ \kappa (1 + \rho\beta) & \lambda\beta\kappa \end{pmatrix} \begin{pmatrix} E_{s} \\ E_{c} \end{pmatrix}$$


loop gain reference $E_c = AE_i$

Superposition model: loop gain

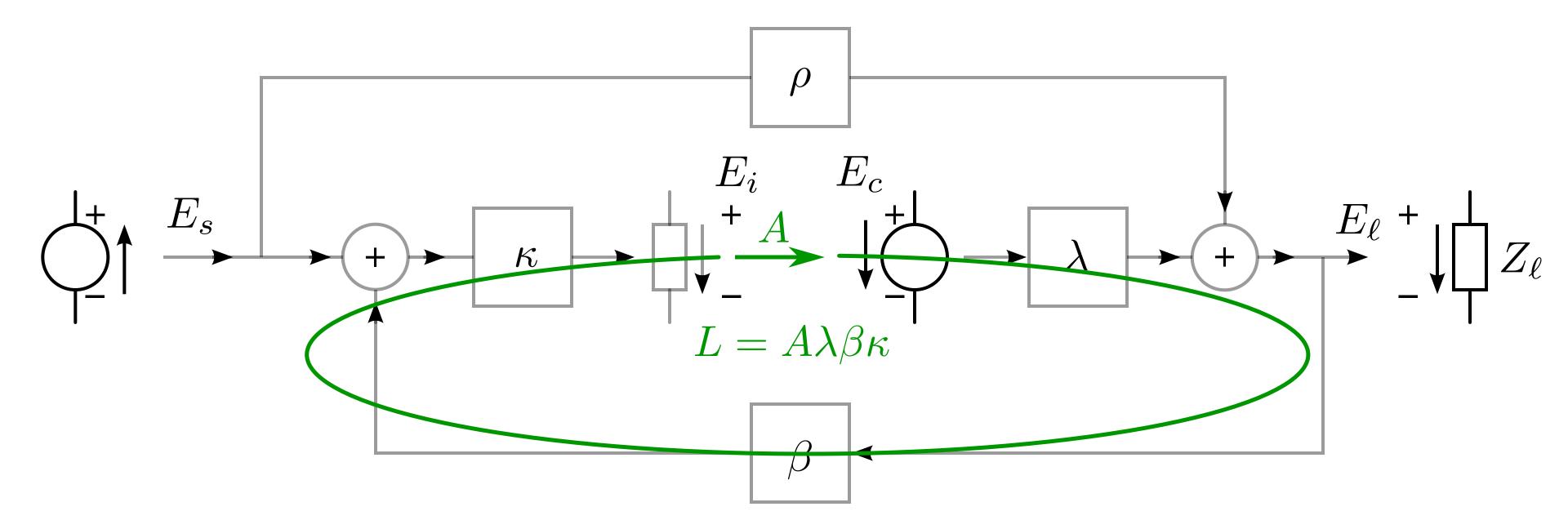


L = Loop gain = gain enclosed in the loop $= A\lambda\beta\kappa$

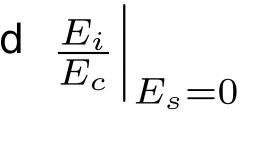Calculate from product of: \boldsymbol{A} and Negative feedback: L < 0




Superposition model

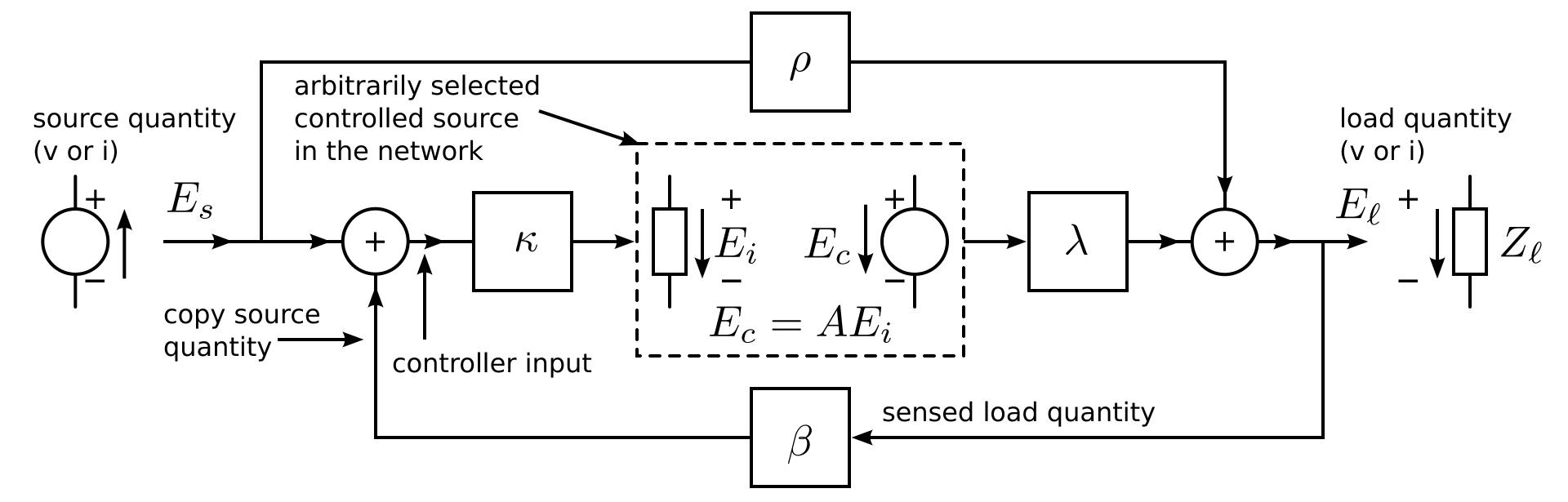

Source-to-load transfer: $A_f = \frac{E_\ell}{E_s} = \rho \frac{1+L}{1-L} - \rho \frac{E_\ell}{1-L}$

$$\frac{1}{\beta} \frac{-L}{1-L}$$

Asymptotic-gain model

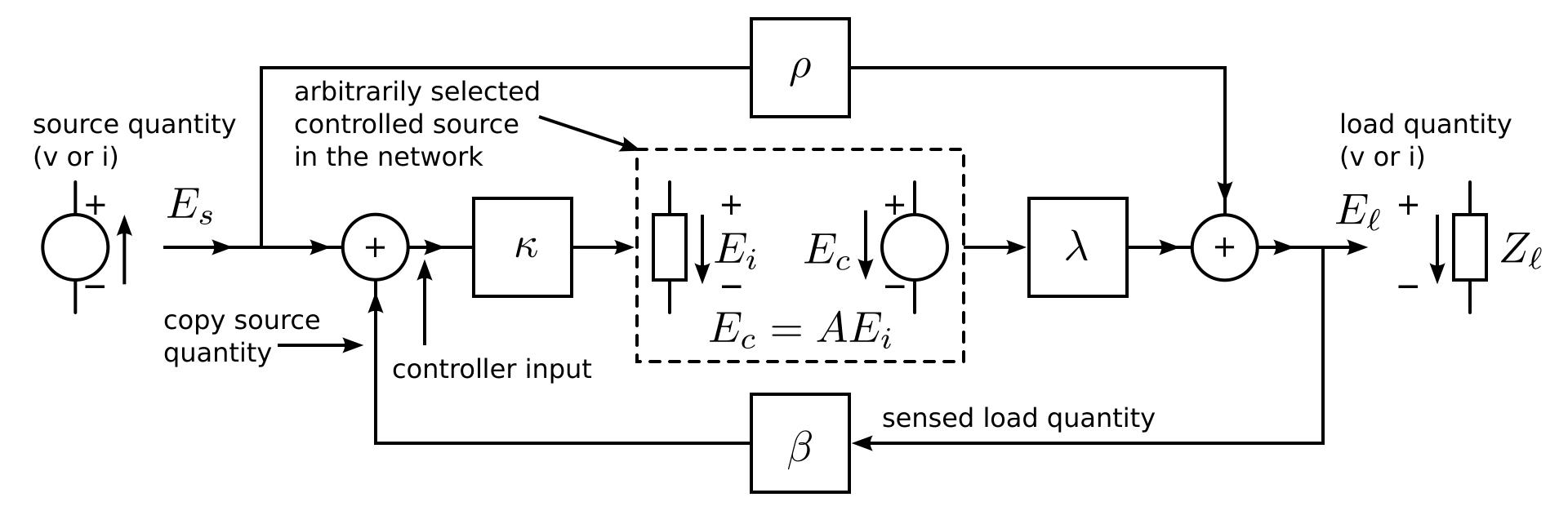

Asymptotic-gain:

$$A_{f\infty} \triangleq \lim_{A \to \infty} A_f$$
$$A_{f\infty} = -\rho - \frac{1}{\beta}$$

Source-to-load transfer:


$$A_f = A_{f\infty} \frac{-L}{1-L} + \frac{\rho}{1-L}$$

Asymptotic-gain model

$$A_{f} = A_{f\infty} \frac{-L}{1-L} + \frac{\rho}{1-L} \qquad A_{f\infty} = \text{Asymptot}$$
$$L = \text{Loop gain}$$
$$\rho = \text{Direct trans}$$

If
$$\frac{\rho}{A_{f\infty}(1-L)} \ll 1$$
 then: $A_f = A_{f\infty} \frac{-L}{1-L}$

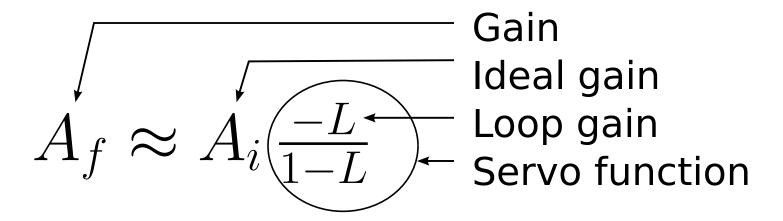Two-step design if ideal gain (designed in first step) equals asymptotic gain



This requires proper selection of the loop gain reference

tic-gain insfer

Looks like Black's model, but no premisses

Equal to Black's model if:

$$\rho = 0$$
$$\kappa = 1$$
$$\lambda = 1$$
$$\beta = \frac{1}{k}$$