Structured Electronic Design

Feedback model of Black

Anton J.M. Montagne

1927: Black: first negative feedback amplifier

1927: Black: first negative feedback amplifier 1932: Black: Wave translation system

1927: Black: first negative feedback amplifier 1932: Black: Wave translation system **1932: Nyquist: Regeneration theory**

1927: Black: first negative feedback amplifier 1932: Black: Wave translation system 1932: Nyquist: Regeneration theory 1945: Bode: Network analysis and Feedback Amplifier Design

1927: Black: first negative feedback amplifier 1932: Black: Wave translation system 1932: Nyquist: Regeneration theory 1945: Bode: Network analysis and Feedback Amplifier Design





Equations:

$$\varepsilon = E_i - kE_o,$$
$$\varepsilon = \frac{1}{H}E_o.$$



Equations:

$$\varepsilon = E_i - kE_o,$$
$$\varepsilon = \frac{1}{H}E_o.$$



Equations:

$$\varepsilon = E_i - kE_o,$$
$$\varepsilon = \frac{1}{H}E_o.$$

Input-output transfer:

loop gain: Hk



Equations:

$$\varepsilon = E_i - kE_o,$$
$$\varepsilon = \frac{1}{H}E_o.$$

- loop gain: Hk
- Ideal gain: $Hk
 ightarrow \infty$



Equations:

$$\varepsilon = E_i - kE_o,$$
$$\varepsilon = \frac{1}{H}E_o.$$

$$\frac{H}{1 + Hk}$$

- loop gain: Hk
- Ideal gain: $Hk \to \infty$ $\lim_{Hk \to \infty} \left(\frac{E_o}{E_i}\right) = \frac{1}{k}$



$$\varepsilon = E_i - kE_o,$$
$$\varepsilon = \frac{1}{H}E_o.$$

$$\frac{H}{1 + Hk}$$

- loop gain: Hk
- Ideal gain: $Hk
 ightarrow \infty$ $\lim_{Hk\to\infty} \left(\frac{E_o}{E_i}\right) = \frac{1}{k}$
- Input-output transfer, rewritten:



Input-output transfer, rewritten:

 $\varepsilon = E_i - kE_o,$ $\varepsilon = \frac{1}{H}E_o.$

 $\frac{E_o}{E_i} =$

Input-output transfer:

$$\frac{H}{1 + Hk}$$

loop gain: Hk

Ideal gain: $Hk \to \infty$ $\lim_{Hk \to \infty} \left(\frac{E_o}{E_i}\right) = \frac{1}{k}$

$$\frac{1}{k} \left(\frac{Hk}{1 + Hk} \right)$$



Input-output transfer, rewritten:

 $\varepsilon = E_i - kE_o,$ $\varepsilon = \frac{1}{H}E_o.$

 $\frac{E_o}{E_i} =$

Input-output transfer:

$$\frac{H}{1 + Hk}$$

loop gain: Hk

Ideal gain: $Hk \to \infty$ $\lim_{Hk \to \infty} \left(\frac{E_o}{E_i}\right) = \frac{1}{k}$

$$\frac{1}{k} \left(\frac{Hk}{1 + Hk} \right)$$





Ideal subtraction requires infinite CMRR, subtraction result does not depend on:



Ideal subtraction requires infinite CMRR, subtraction result does not depend on:



- Ideal subtraction requires infinite CMRR, subtraction result does not depend on:

 - Input impedance controller



- Ideal subtraction requires infinite CMRR, subtraction result does not depend on:

 - Input impedance controller
 - Output impedance feedback network



- Ideal subtraction requires infinite CMRR, subtraction result does not depend on:

 - Input impedance controller
 - Output impedance feedback network
- No direct transfer from input to output.



- Ideal subtraction requires infinite CMRR, subtraction result does not depend on:

 - Input impedance controller
 - Output impedance feedback network
- No direct transfer from input to output.
- No reverse transfer in the controller and in the feedback network.



- Ideal subtraction requires infinite CMRR, subtraction result does not depend on:

 - Input impedance controller
 - Output impedance feedback network
- No direct transfer from input to output.
- No reverse transfer in the controller and in the feedback network.
- The controller gain does not depend on:



- Ideal subtraction requires infinite CMRR, subtraction result does not depend on:

 - Input impedance controller
 - Output impedance feedback network
- No direct transfer from input to output.
- No reverse transfer in the controller and in the feedback network.
- The controller gain does not depend on:
 - Input impedance feedback network



Source impedance

Load impedance

- Ideal subtraction requires infinite CMRR, subtraction result does not depend on:

 - Input impedance controller
 - Output impedance feedback network
- No direct transfer from input to output.
- No reverse transfer in the controller and in the feedback network.
- The controller gain does not depend on:
 - Input impedance feedback network



Source impedance

Load impedance

- Ideal subtraction requires infinite CMRR, subtraction result does not depend on:

 - Input impedance controller
 - Output impedance feedback network
- No direct transfer from input to output.
- No reverse transfer in the controller and in the feedback network.
- The controller gain does not depend on:
 - Input impedance feedback network





Loop gain not simply the product of the controller gain (H) and the gain of the feedback network (k)



Loop gain not simply the product of the controller gain (H) and the gain of the feedback network (k)

Suited for system-level analysis (no interaction between blocks)



feedback network (k)

on circuit level

- Loop gain not simply the product of the controller gain (H) and the gain of the
- Suited for system-level analysis (no interaction between blocks)
- Not suited for obtaining design information



feedback network (k)

on circuit level

- Loop gain not simply the product of the controller gain (H) and the gain of the
- Suited for system-level analysis (no interaction between blocks)
- Not suited for obtaining design information
 - See example 10.1 and 10.2



feedback network (k)

on circuit level

- Loop gain not simply the product of the controller gain (H) and the gain of the
- Suited for system-level analysis (no interaction between blocks)
- Not suited for obtaining design information
 - See example 10.1 and 10.2