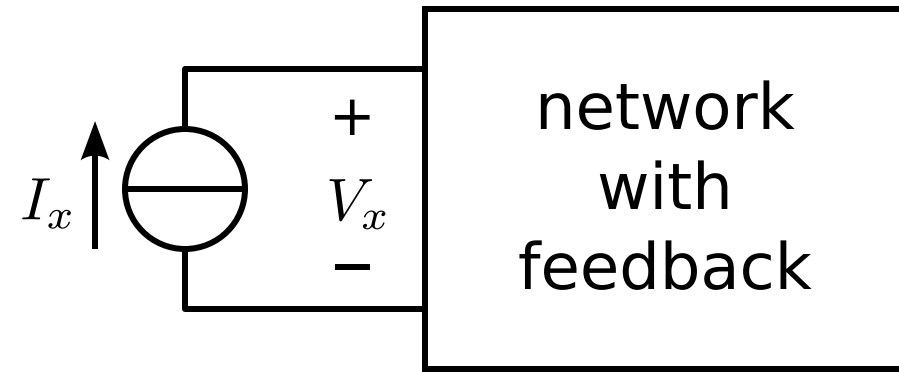


Structured Electronic Design

Port impedance of single-loop feedback amplifiers

Anton J.M. Montagne

Port impedance and the asymptotic-gain model



Impedance port x $Z_{xf} = \frac{V_x}{I_x}$

$$Z_{xf} = \rho \frac{1-L_{sc}}{1-L_o}$$

ρ Port impedance with gain of loop gain reference set to zero

L_{sc} Loop gain with port x shorted

L_o Loop gain with port x open

Single-loop feedback amplifiers

Parallel feedback at a port: $L_{sc} = 0$

Asymptotic-value of port impedance equals zero

Series feedback at a port: $L_o = 0$

Asymptotic-value of port impedance equals infinity