

# **Structured Electronic Design**

## Implementation of Phantom Zeros

*Anton J.M. Montagne*

# Circuit implementation of phantom zeros

# Circuit implementation of phantom zeros

1. Poles in the ideal gain can only be found in circuitry outside the controller

# Circuit implementation of phantom zeros

1. Poles in the ideal gain can only be found in circuitry outside the controller
  - a. A pole in the transfer from the source to the input of the amplifier

# Circuit implementation of phantom zeros

1. Poles in the ideal gain can only be found in circuitry outside the controller
  - a. A pole in the transfer from the source to the input of the amplifier
  - b. A pole in the transfer from the output of the amplifier to the load

# Circuit implementation of phantom zeros

1. Poles in the ideal gain can only be found in circuitry outside the controller
  - a. A pole in the transfer from the source to the input of the amplifier
  - b. A pole in the transfer from the output of the amplifier to the load
  - c. A zero in the transfer of the feedback network

# Circuit implementation of phantom zeros

1. Poles in the ideal gain can only be found in circuitry outside the controller
  - a. A pole in the transfer from the source to the input of the amplifier
  - b. A pole in the transfer from the output of the amplifier to the load
  - c. A zero in the transfer of the feedback network
  
2. The pole in the ideal gain is an 'effective' zero in the loop gain if

# Circuit implementation of phantom zeros

1. Poles in the ideal gain can only be found in circuitry outside the controller
  - a. A pole in the transfer from the source to the input of the amplifier
  - b. A pole in the transfer from the output of the amplifier to the load
  - c. A zero in the transfer of the feedback network
  
2. The pole in the ideal gain is an 'effective' zero in the loop gain if
  - a. It does not add a new dominant pole in the loop gain



# Circuit implementation of phantom zeros

1. Poles in the ideal gain can only be found in circuitry outside the controller
  - a. A pole in the transfer from the source to the input of the amplifier
  - b. A pole in the transfer from the output of the amplifier to the load
  - c. A zero in the transfer of the feedback network
  
2. The pole in the ideal gain is an 'effective' zero in the loop gain if
  - a. It does not add a new dominant pole in the loop gain
  - b. It does not significantly change the position of a dominant pole of the loop gain

# Circuit implementation of phantom zeros

1. Poles in the ideal gain can only be found in circuitry outside the controller
  - a. A pole in the transfer from the source to the input of the amplifier
  - b. A pole in the transfer from the output of the amplifier to the load
  - c. A zero in the transfer of the feedback network
  
2. The pole in the ideal gain is an 'effective' zero in the loop gain if
  - a. It does not add a new dominant pole in the loop gain
  - b. It does not significantly change the position of a dominant pole of the loop gain

This is the case if, for frequencies above that of the zero,  
the zero significantly reduces an existing attenuation in the loop gain

# Circuit implementation of phantom zeros

1. Poles in the ideal gain can only be found in circuitry outside the controller
  - a. A pole in the transfer from the source to the input of the amplifier
  - b. A pole in the transfer from the output of the amplifier to the load
  - c. A zero in the transfer of the feedback network
  
2. The pole in the ideal gain is an 'effective' zero in the loop gain if
  - a. It does not add a new dominant pole in the loop gain
  - b. It does not significantly change the position of a dominant pole of the loop gain

This is the case if, for frequencies above that of the zero,  
the zero significantly reduces an existing attenuation in the loop gain

# Circuit implementation of phantom zeros

# Circuit implementation of phantom zeros

Pole in the asymptotic gain:

# Circuit implementation of phantom zeros

Pole in the asymptotic gain:

a. Low-pass transfer from source and input

# Circuit implementation of phantom zeros

Pole in the asymptotic gain:

- a. Low-pass transfer from source and input
- b. Low-pass transfer from output and load

# Circuit implementation of phantom zeros

Pole in the asymptotic gain:


a. Low-pass transfer from source and input

b. Low-pass transfer from output and load

c. Zero in feedback network


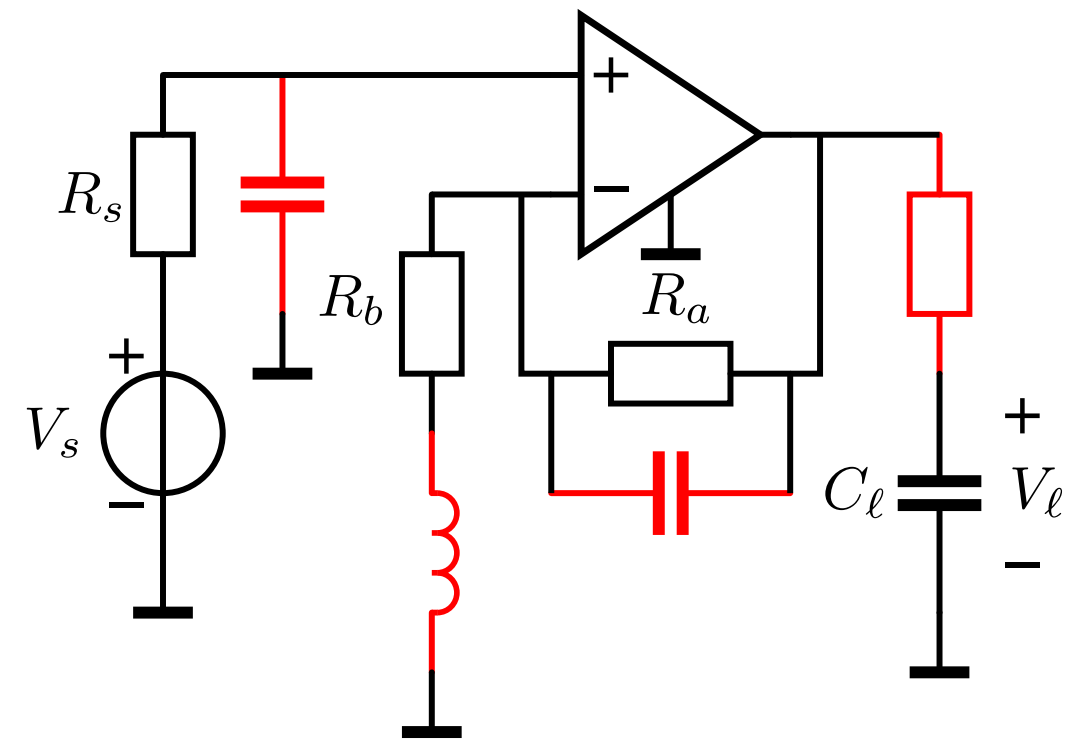
# Circuit implementation of phantom zeros




Possible phantom zero implementations in a voltage amplifier with resistive source capacitive load and resistive feedback

Pole in the asymptotic gain:

- Low-pass transfer from source and input
- Low-pass transfer from output and load
- Zero in feedback network
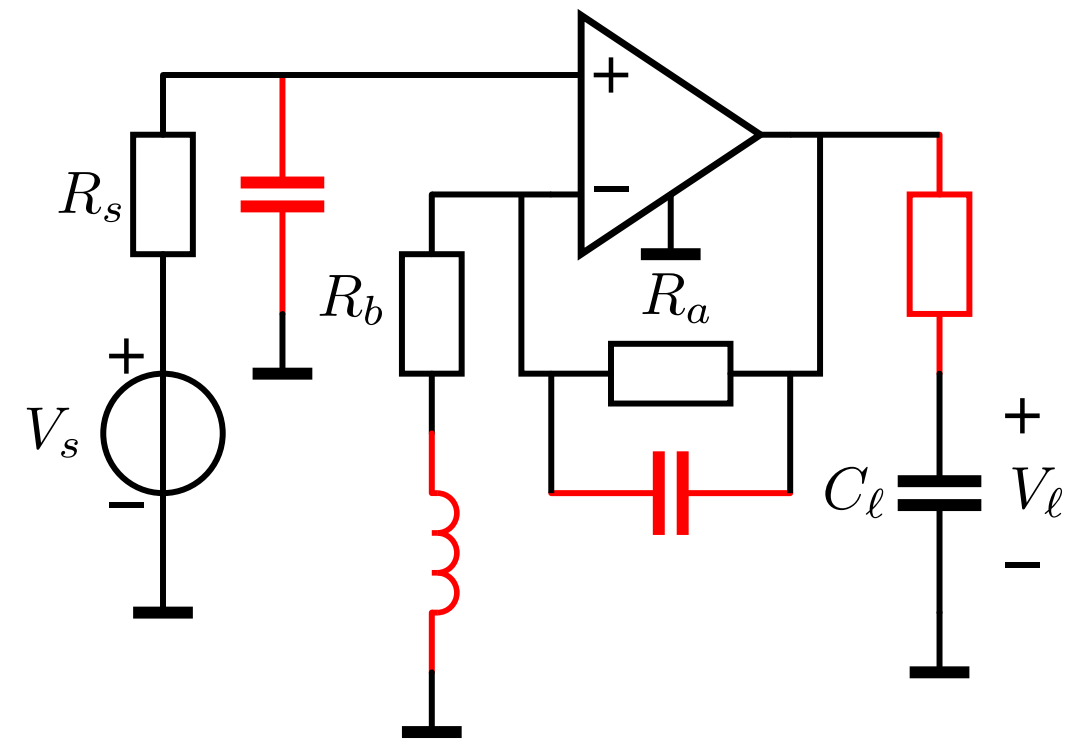
# Circuit implementation of phantom zeros




Possible phantom zero implementations in a voltage amplifier with resistive source capacitive load and resistive feedback

Pole in the asymptotic gain:

- a. Low-pass transfer from source and input
- b. Low-pass transfer from output and load
- c. Zero in feedback network

Zero in the loop gain:
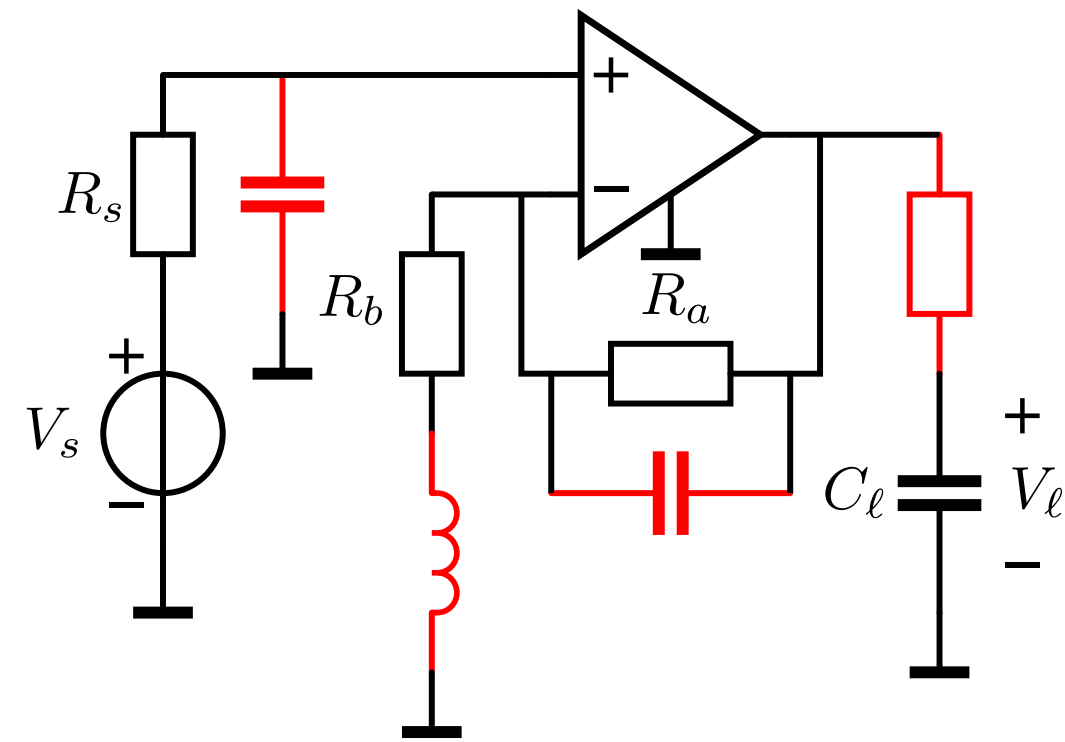
# Circuit implementation of phantom zeros



Possible phantom zero implementations in a voltage amplifier with resistive source capacitive load and resistive feedback


Pole in the asymptotic gain:

- Low-pass transfer from source and input
- Low-pass transfer from output and load
- Zero in feedback network

Zero in the loop gain:

- The compensation element establishes an open circuit in series with the signal path (of the loop gain) at the frequency of the zero
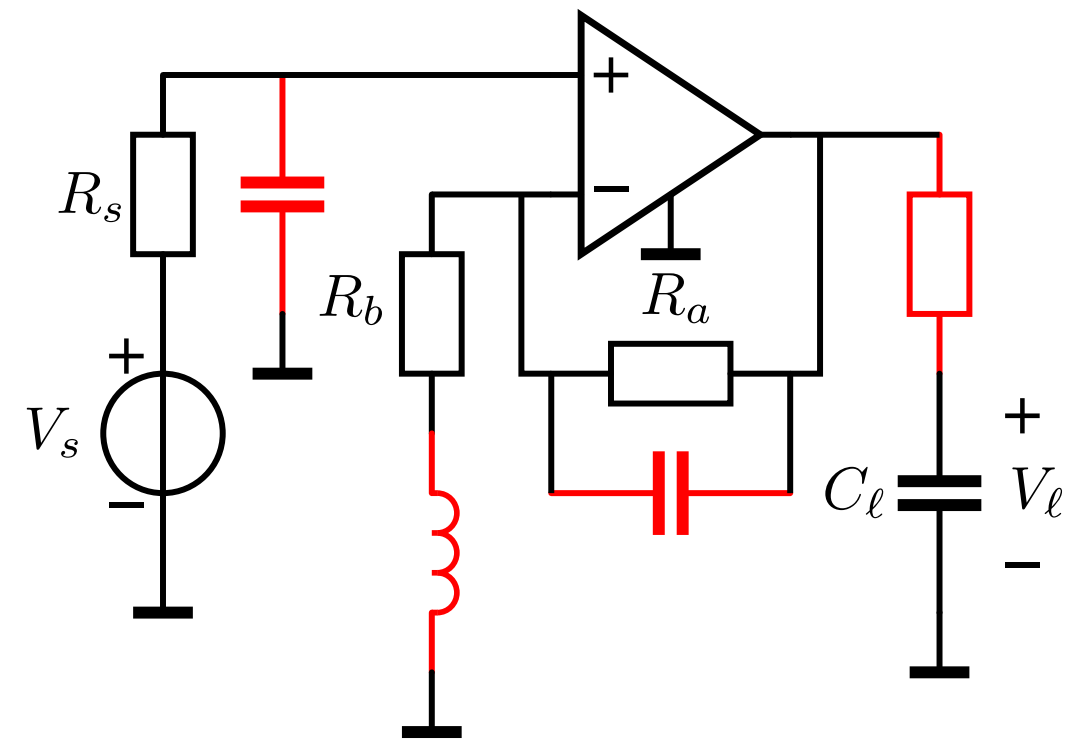
# Circuit implementation of phantom zeros



Possible phantom zero implementations in a voltage amplifier with resistive source capacitive load and resistive feedback


Pole in the asymptotic gain:

- Low-pass transfer from source and input
- Low-pass transfer from output and load
- Zero in feedback network

Zero in the loop gain:

- The compensation element establishes an open circuit in series with the signal path (of the loop gain) at the frequency of the zero
- The compensation element establishes a short circuit in parallel with the signal path (of the loop gain) at the frequency of the zero
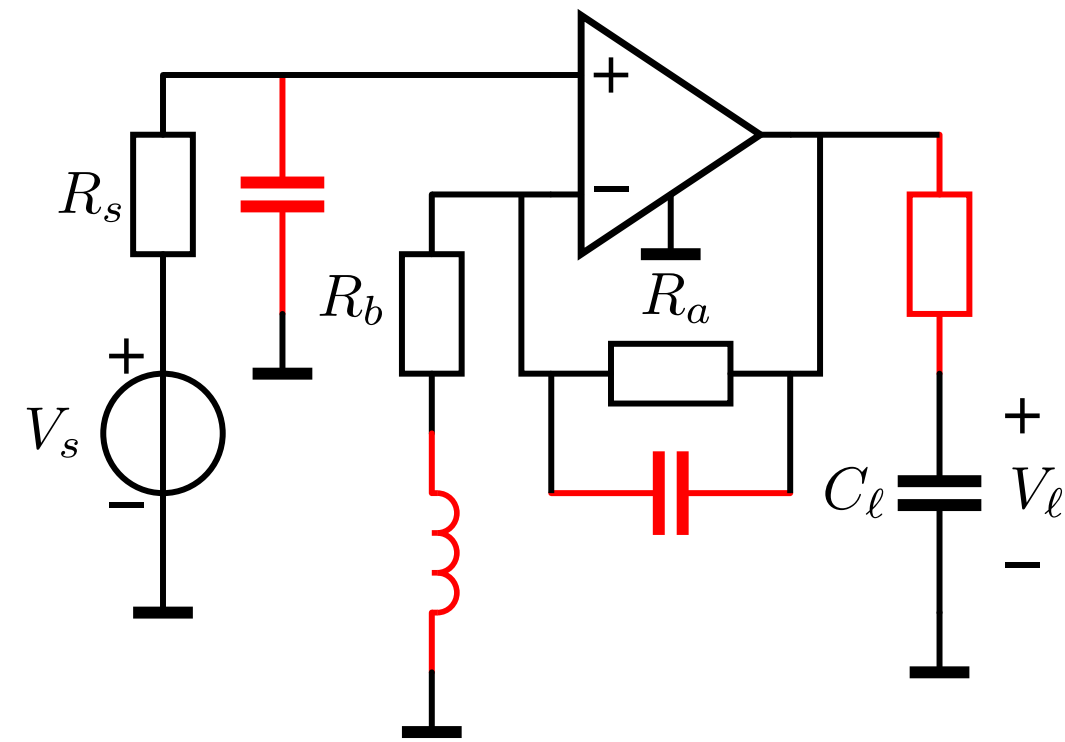
# Circuit implementation of phantom zeros



Possible phantom zero implementations in a voltage amplifier with resistive source capacitive load and resistive feedback


Pole in the asymptotic gain:

- Low-pass transfer from source and input
- Low-pass transfer from output and load
- Zero in feedback network

Zero in the loop gain:

- The compensation element establishes an open circuit in series with the signal path (of the loop gain) at the frequency of the zero
- The compensation element establishes a short circuit in parallel with the signal path (of the loop gain) at the frequency of the zero
- This zero is effective
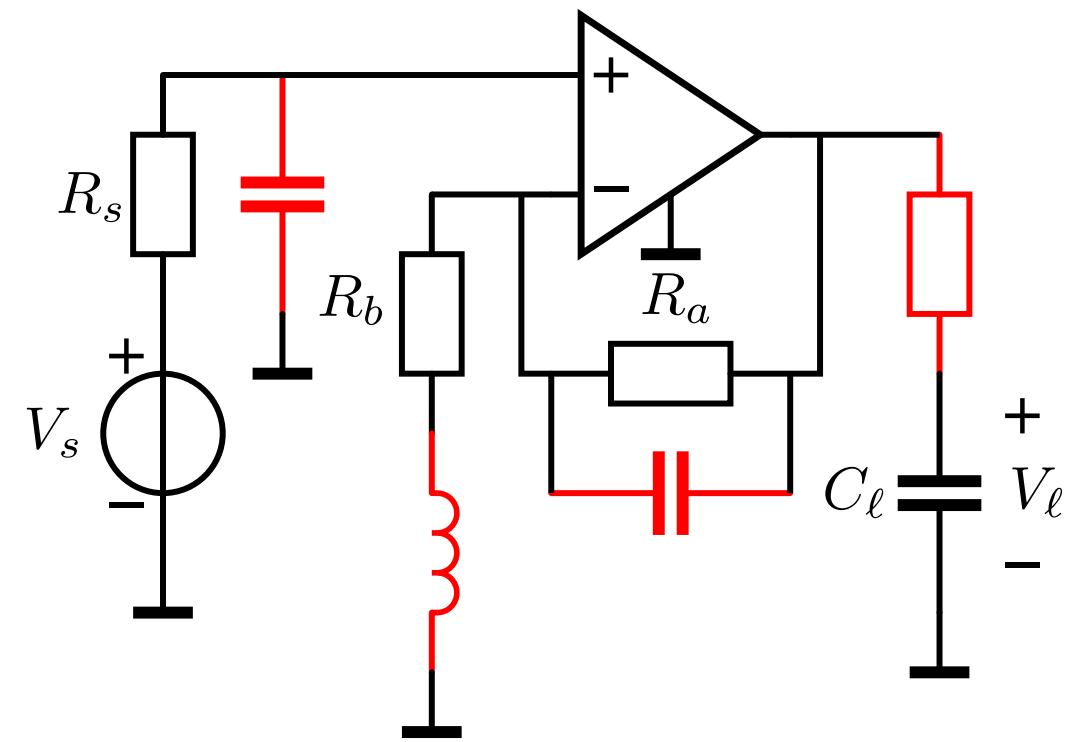
# Circuit implementation of phantom zeros



Possible phantom zero implementations in a voltage amplifier with resistive source capacitive load and resistive feedback

Pole in the asymptotic gain:


- Low-pass transfer from source and input
- Low-pass transfer from output and load
- Zero in feedback network

Zero in the loop gain:

- The compensation element establishes an open circuit in series with the signal path (of the loop gain) at the frequency of the zero
- The compensation element establishes a short circuit in parallel with the signal path (of the loop gain) at the frequency of the zero
- This zero is effective



# Effectiveness of phantom zeros

# Effectiveness of phantom zeros


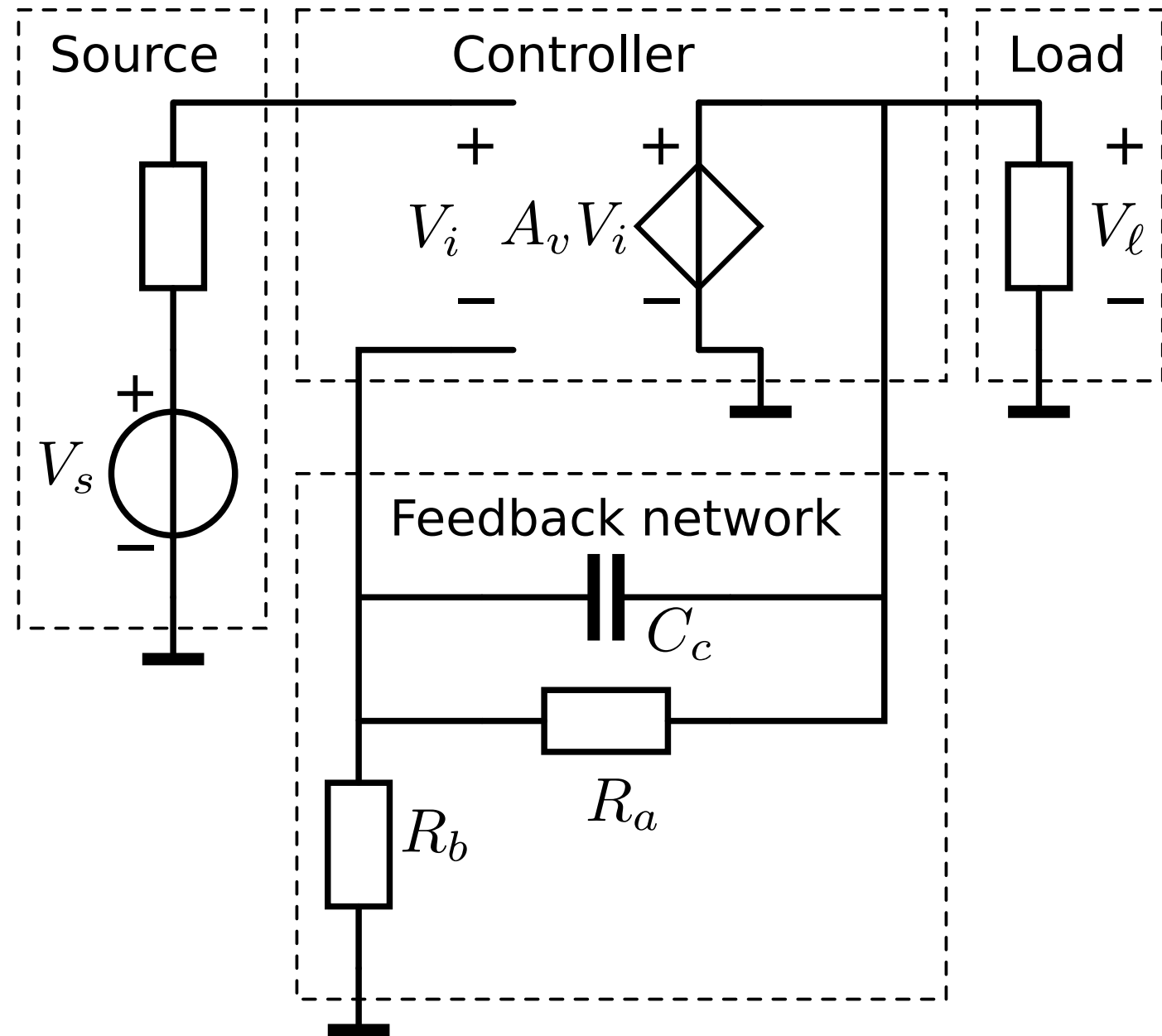




# Effectiveness of phantom zeros

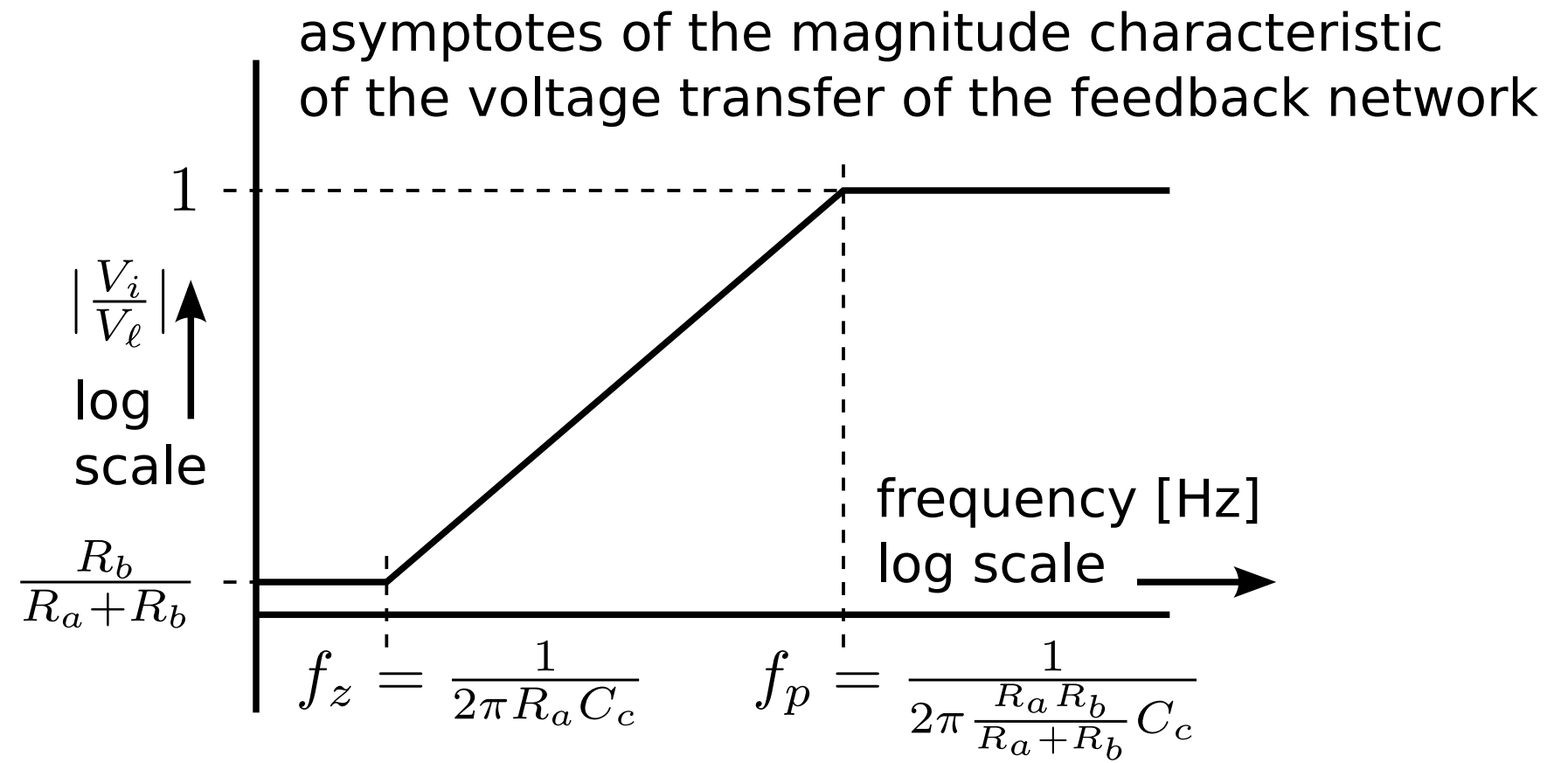
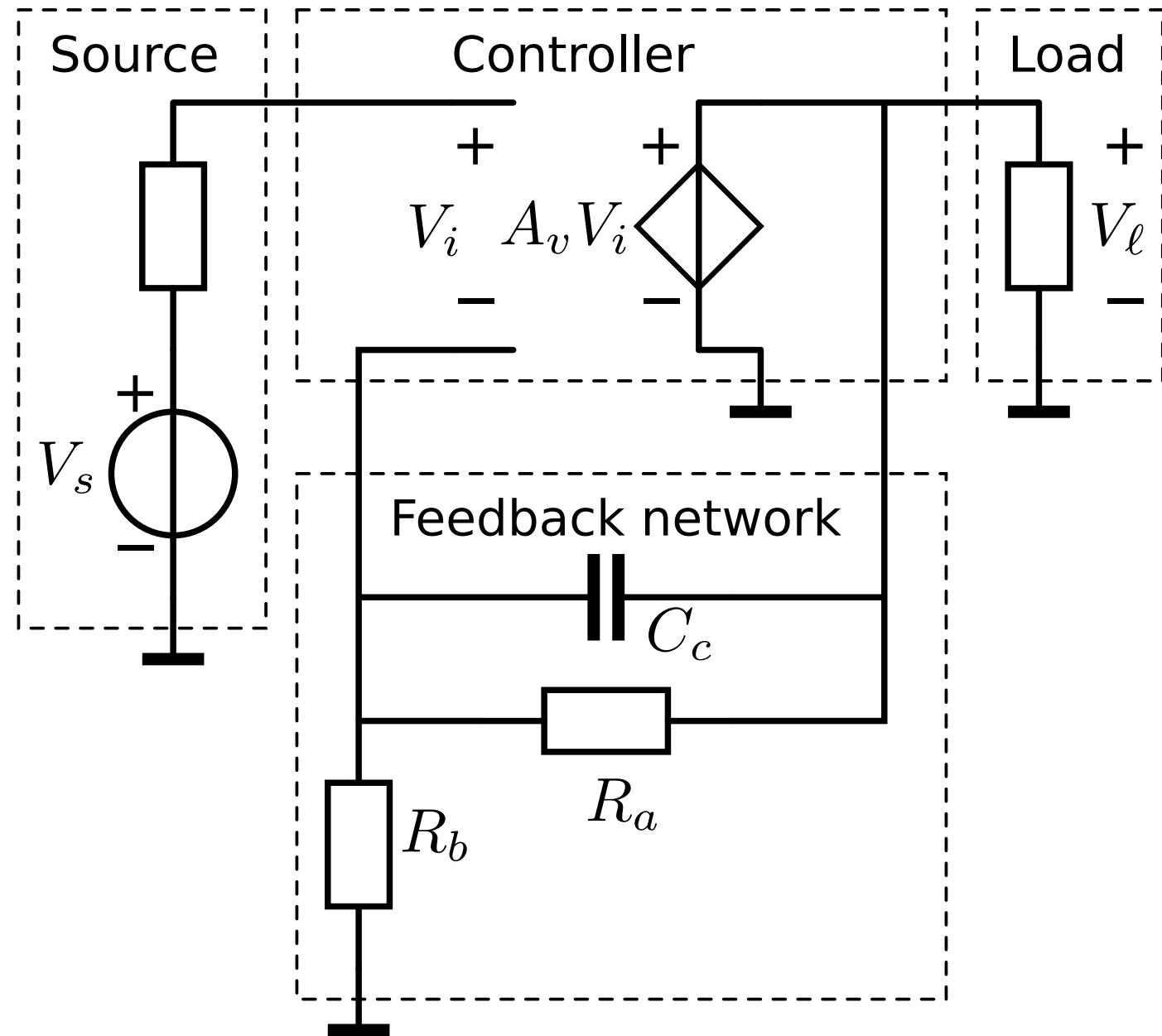


# Effectiveness of phantom zeros

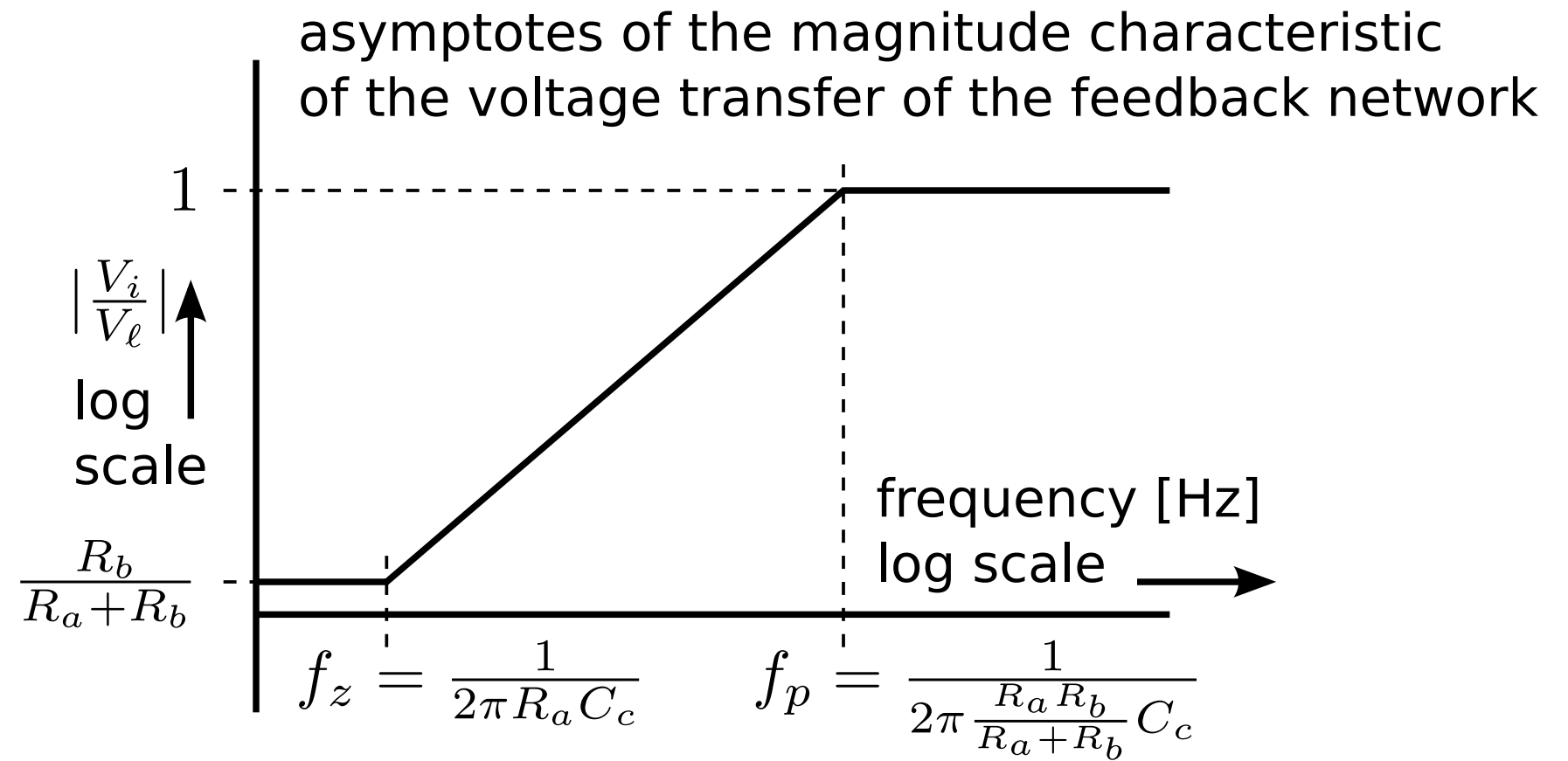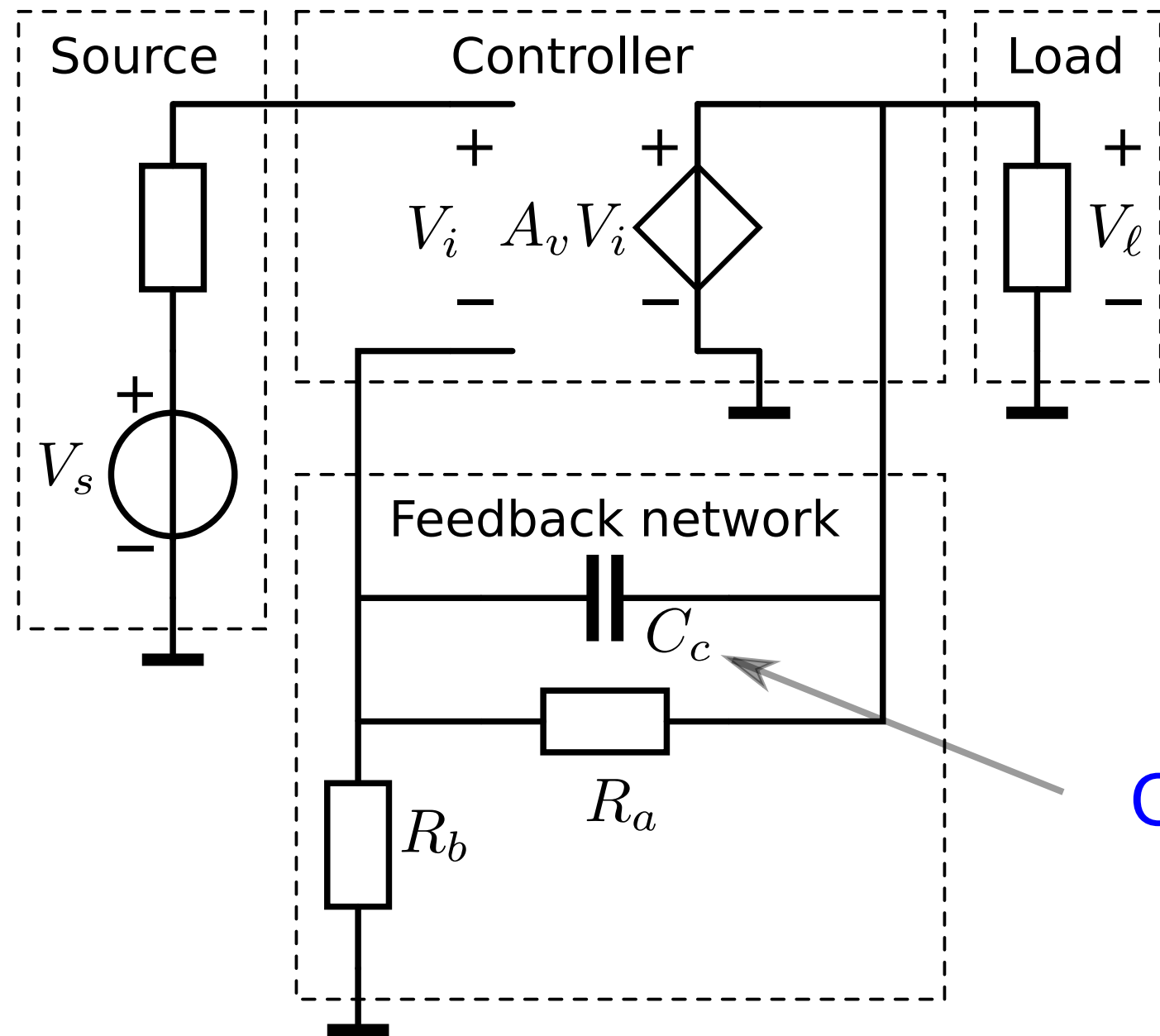



Compensation capacitance causes:

# Effectiveness of phantom zeros

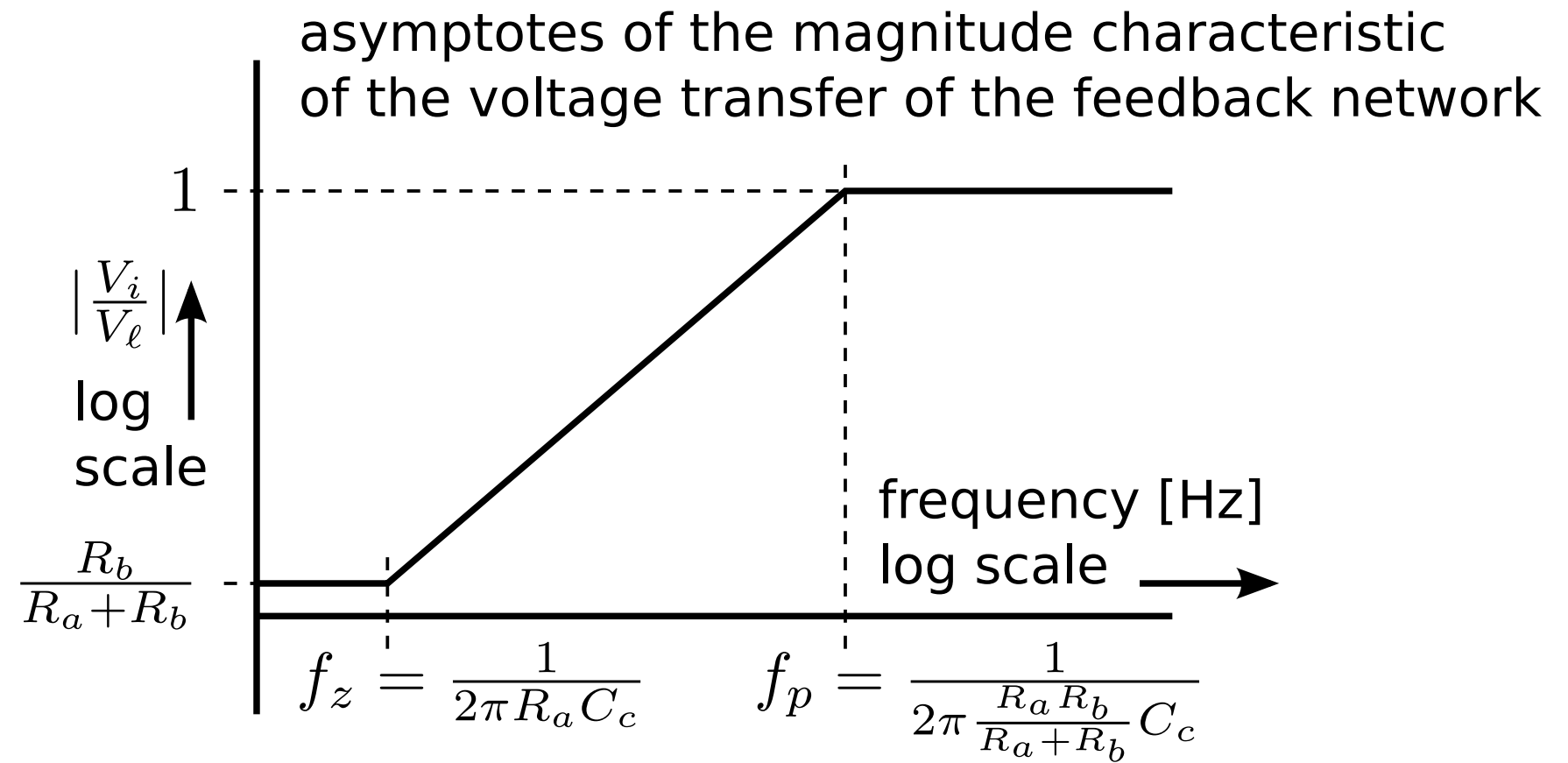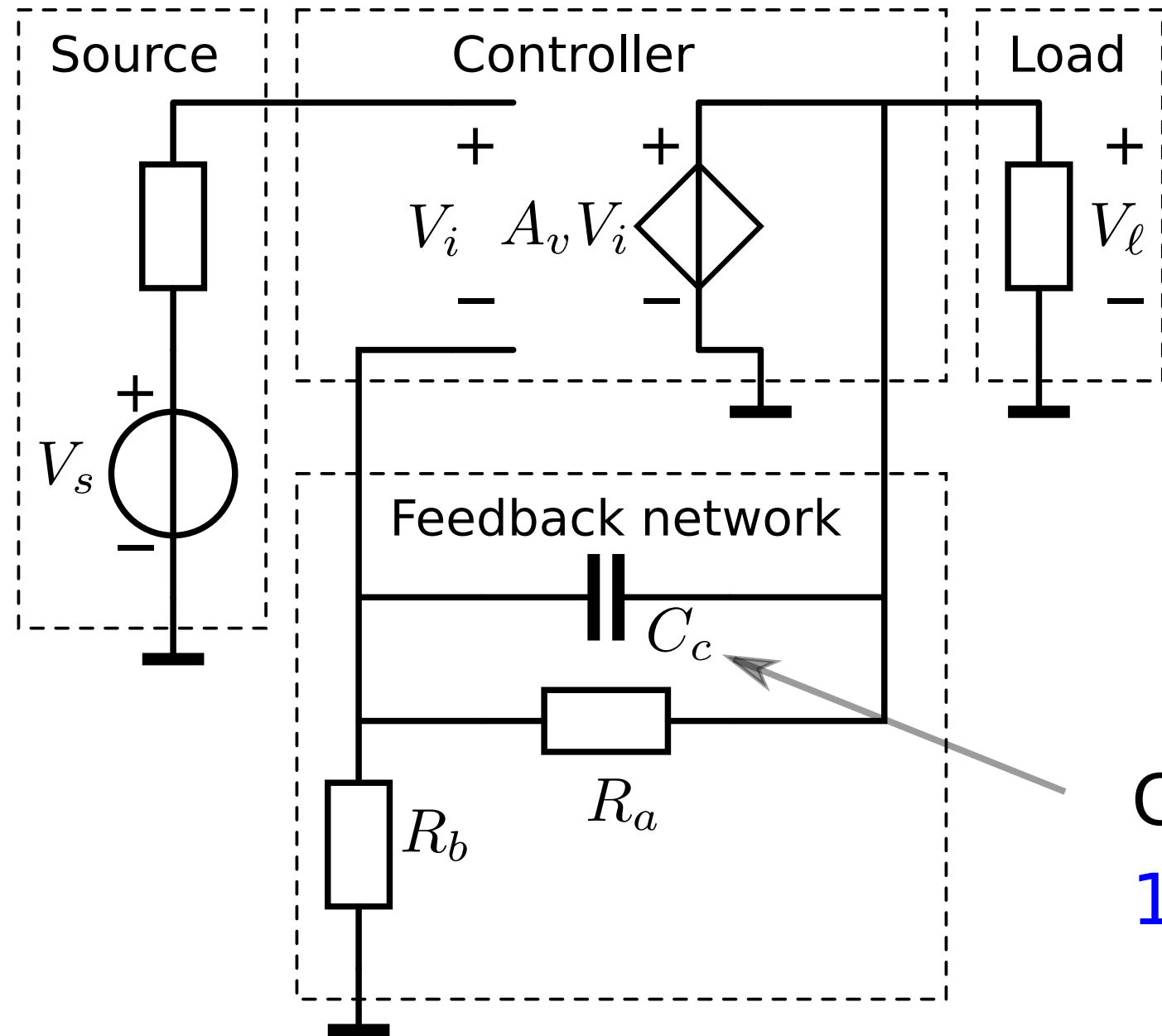



Compensation capacitance causes:  
**1. A pole in the asymptotic gain**

# Effectiveness of phantom zeros

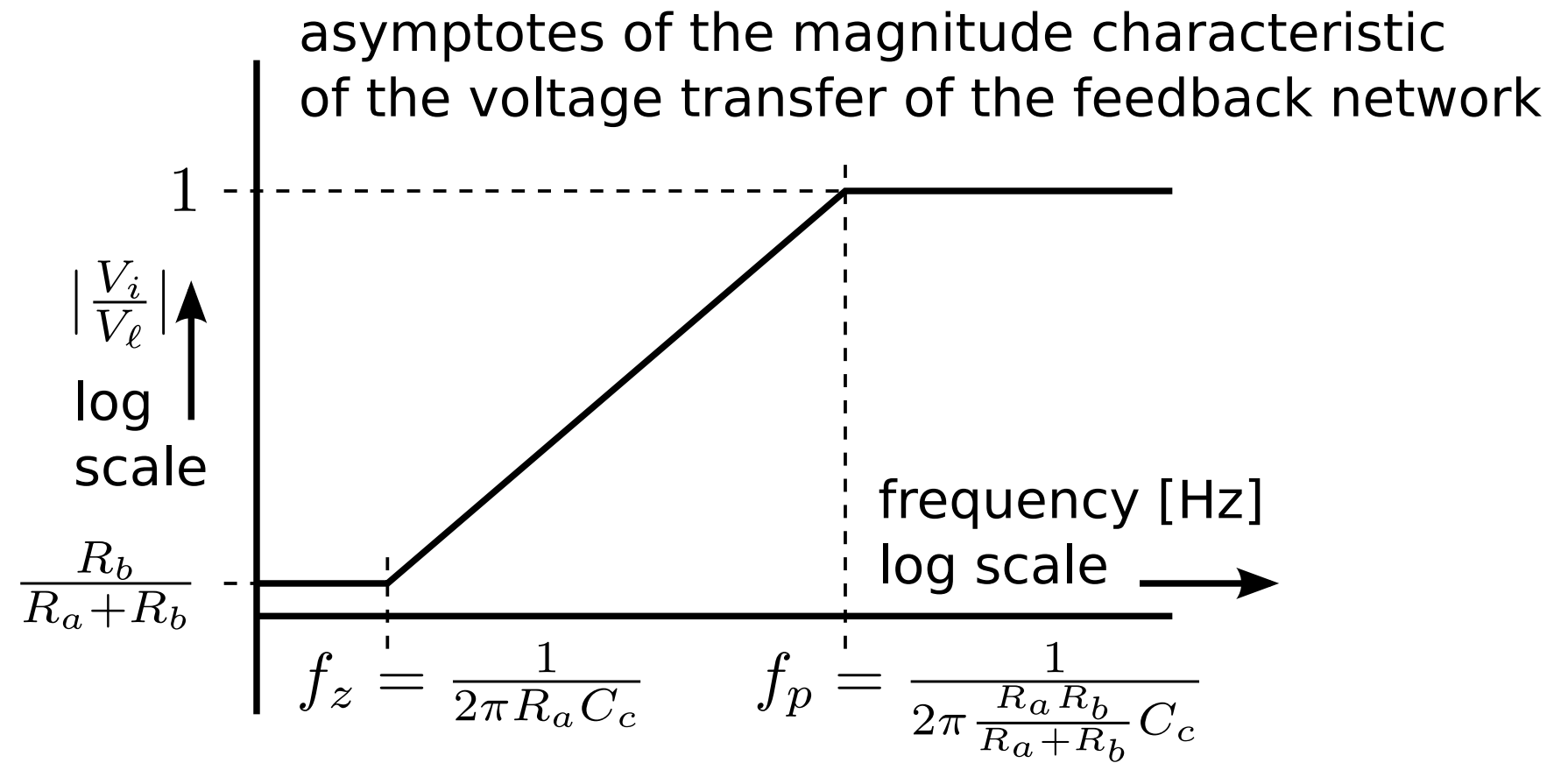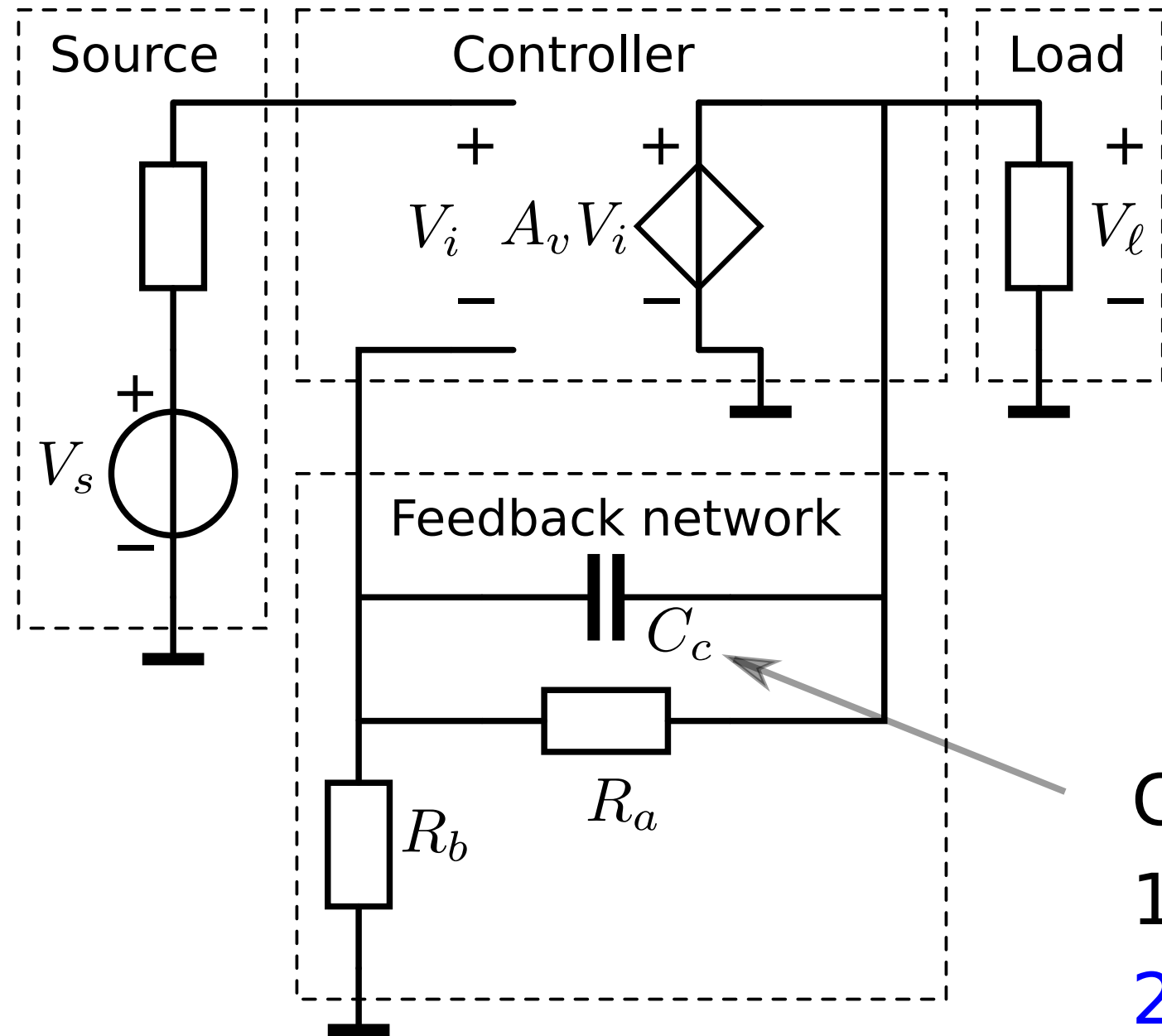

- Compensation capacitance causes:
1. A pole in the asymptotic gain
  2. A zero in the loop gain

# Effectiveness of phantom zeros

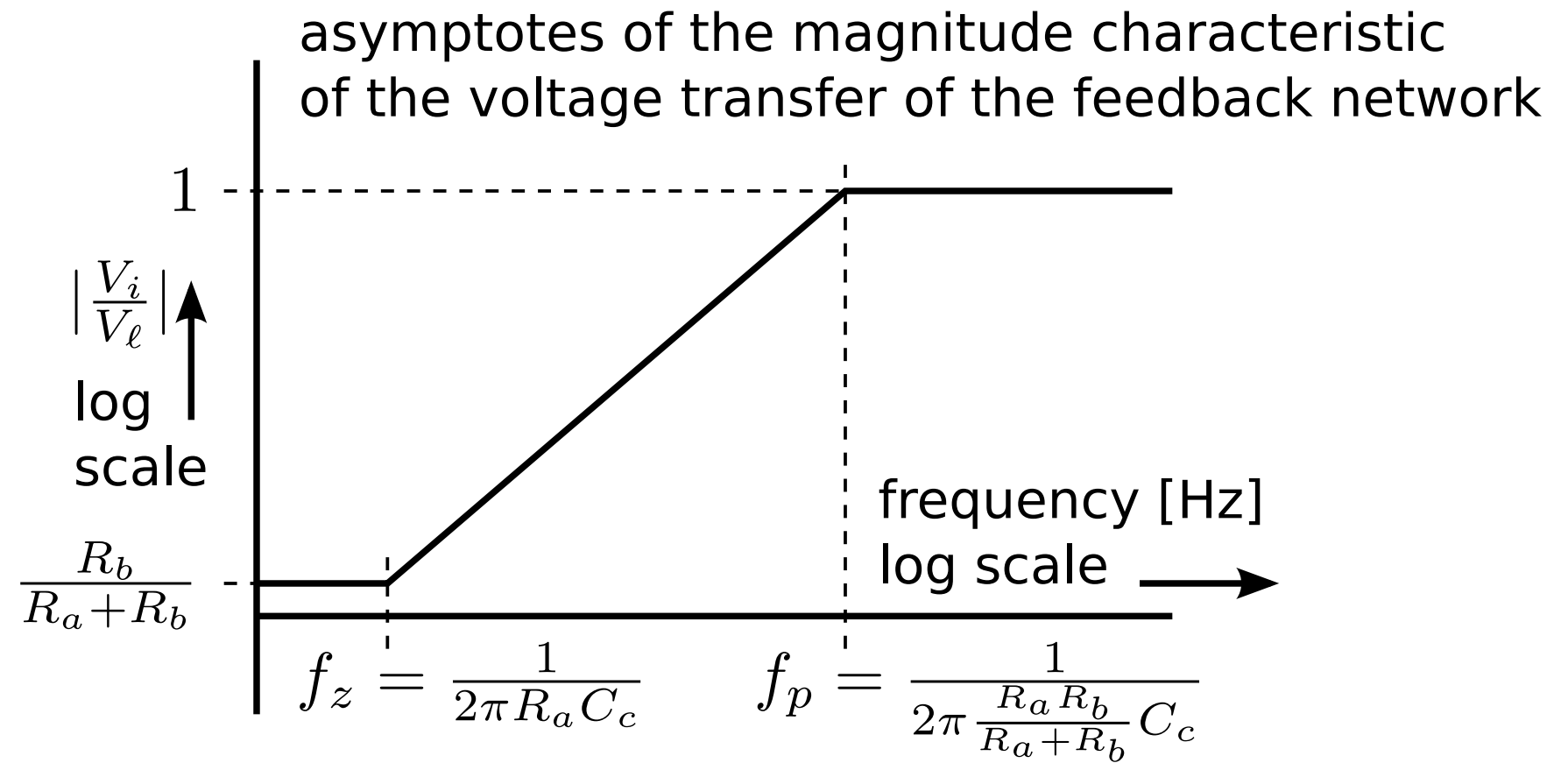
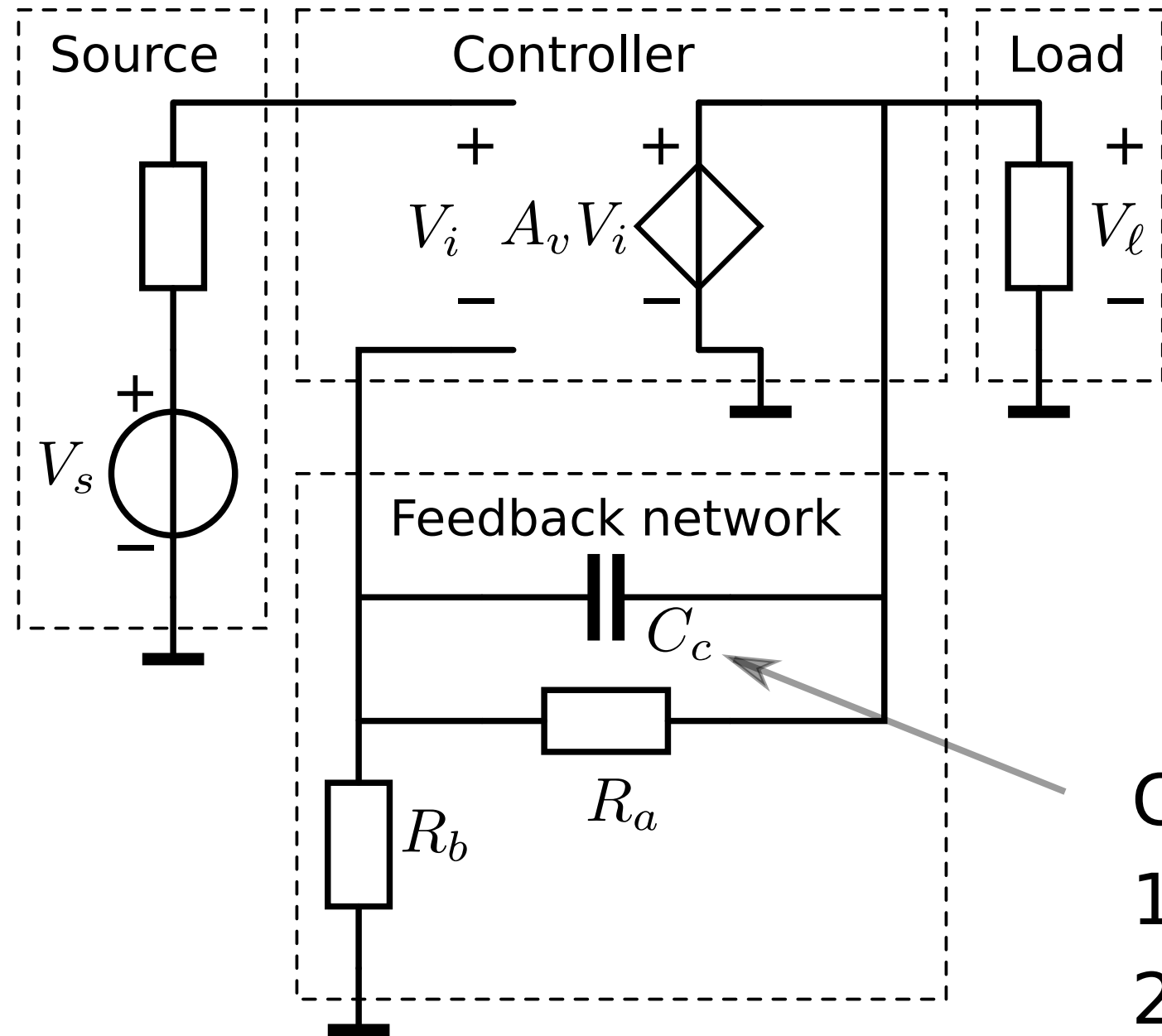


Compensation capacitance causes:

1. A pole in the asymptotic gain
2. A zero in the loop gain

$$\left. \begin{array}{l} 1. \text{ A pole in the asymptotic gain} \\ 2. \text{ A zero in the loop gain} \end{array} \right\} s = -\frac{1}{2\pi R_a C_c}$$

# Effectiveness of phantom zeros

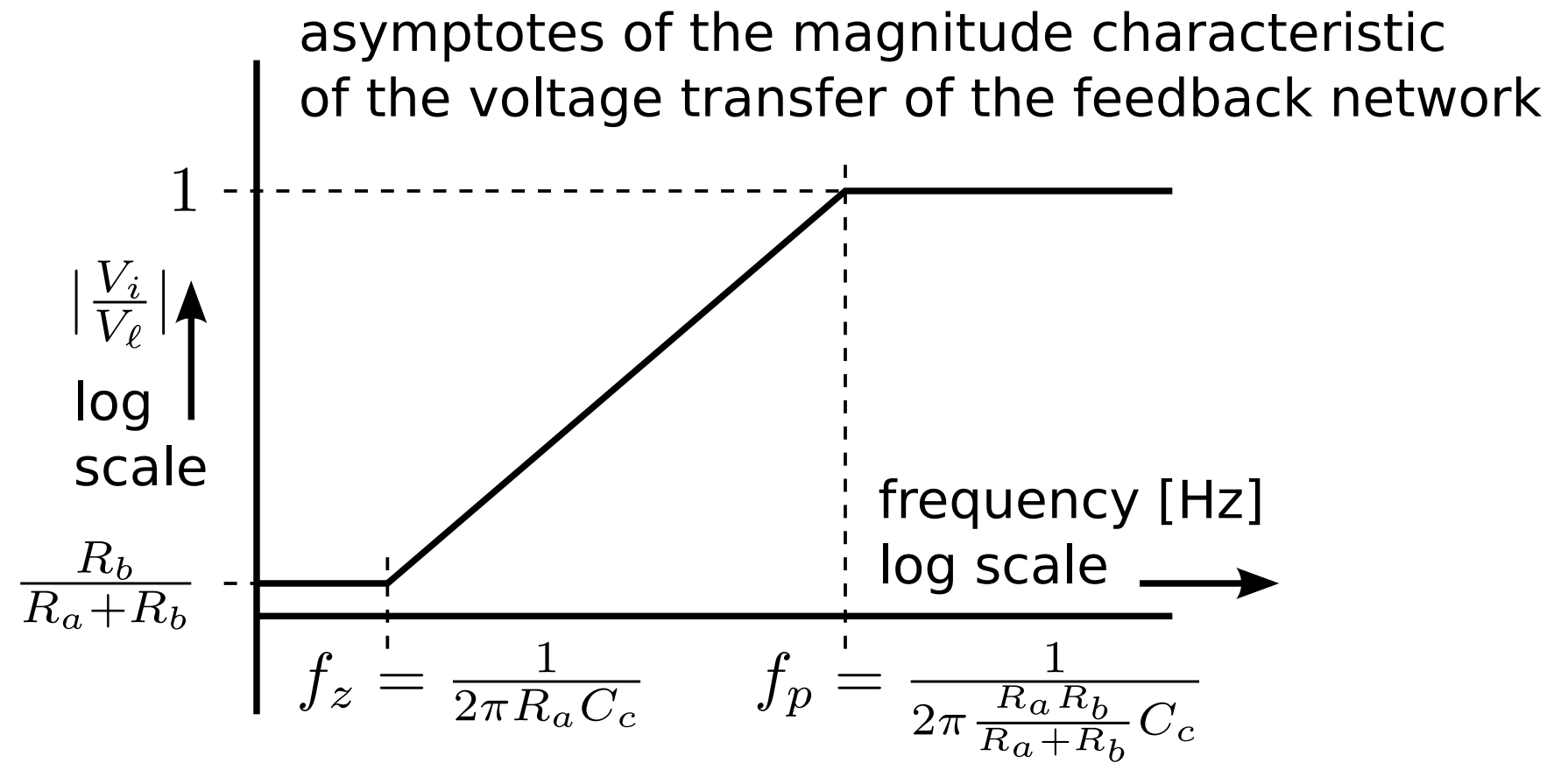
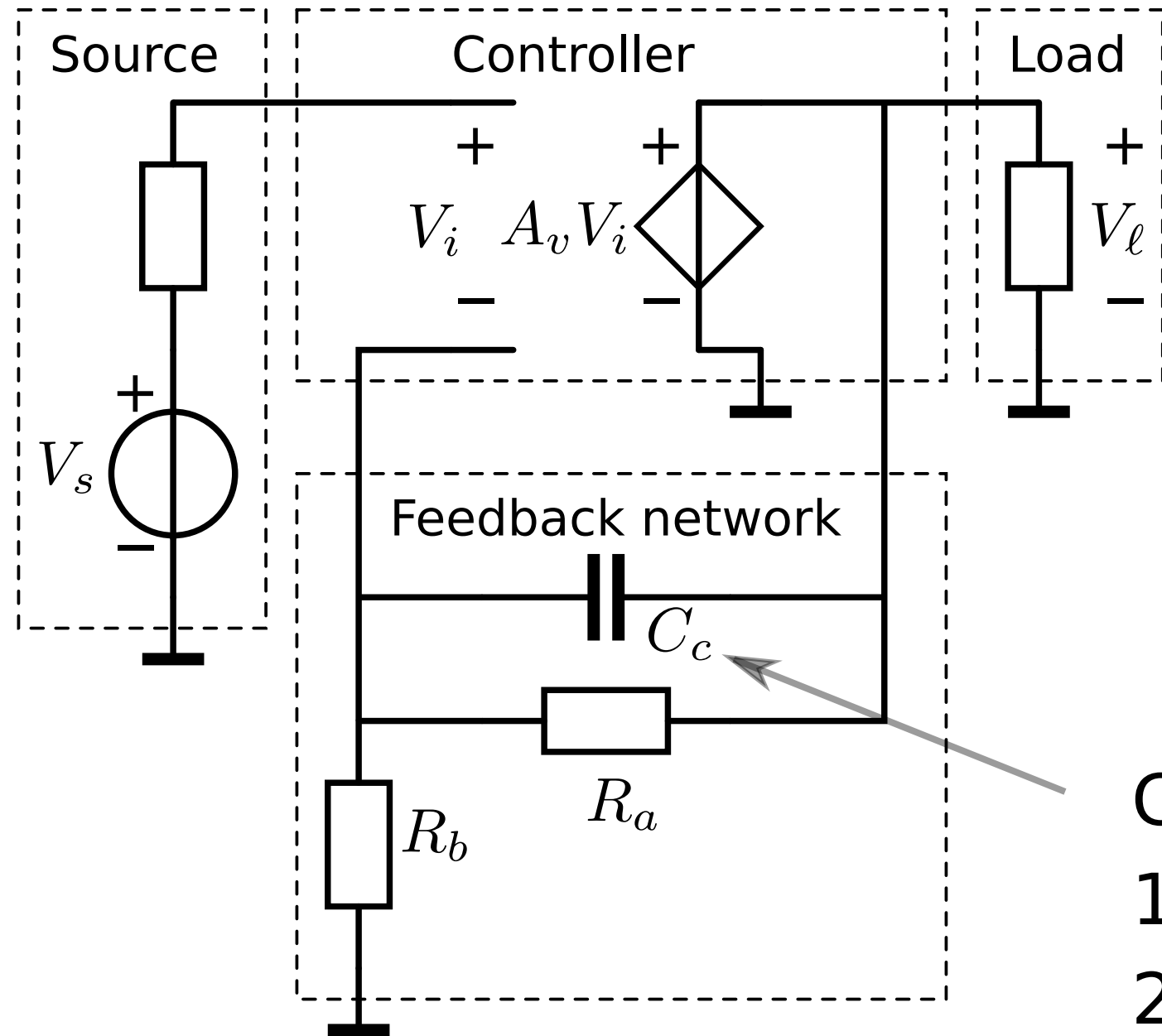


Compensation capacitance causes:

1. A pole in the asymptotic gain
2. A zero in the loop gain
3. A zero in the asymptotic gain

$$\left. \begin{array}{l} 1. \text{ A pole in the asymptotic gain} \\ 2. \text{ A zero in the loop gain} \end{array} \right\} s = -\frac{1}{2\pi R_a C_c}$$

# Effectiveness of phantom zeros

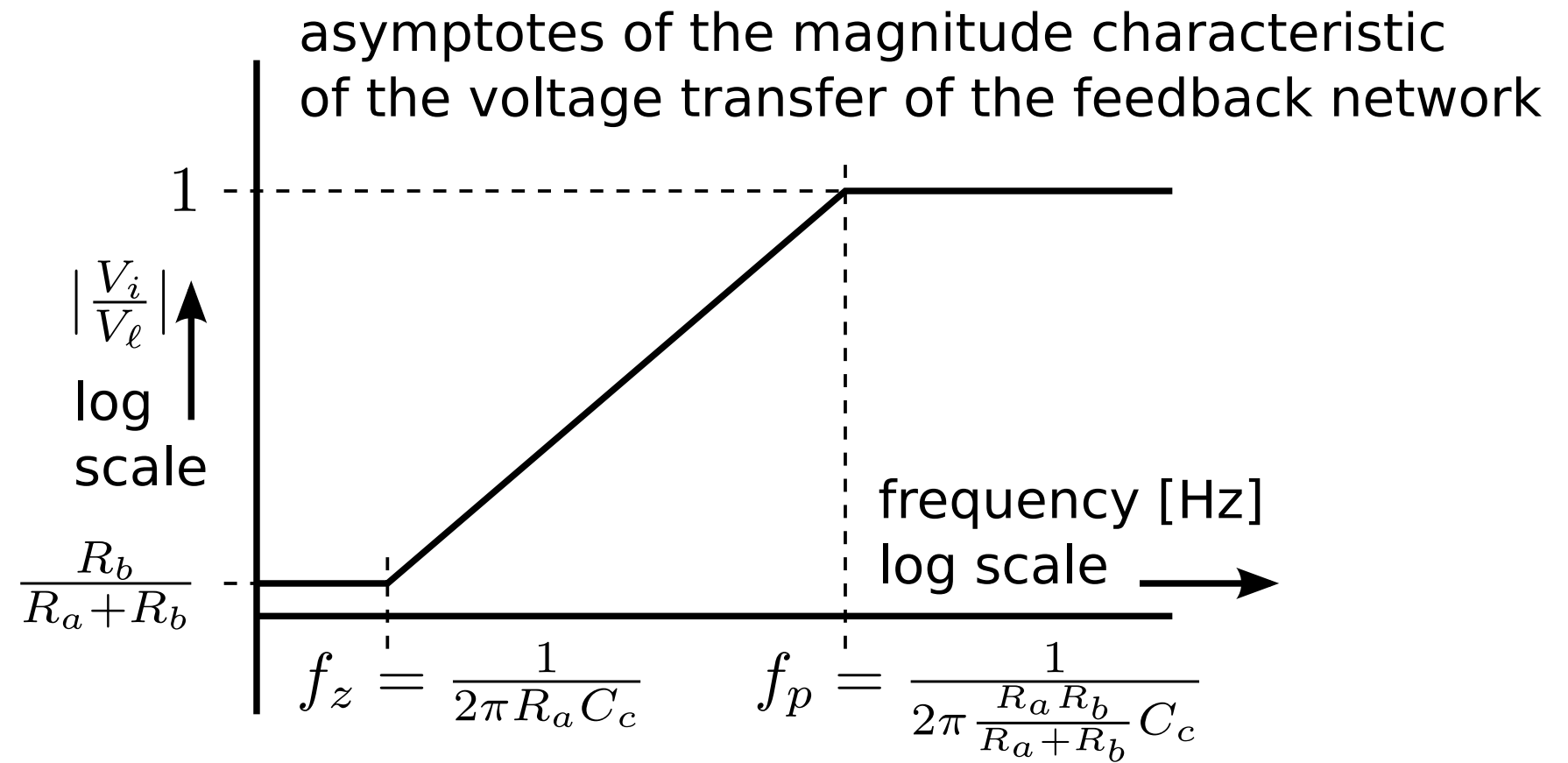
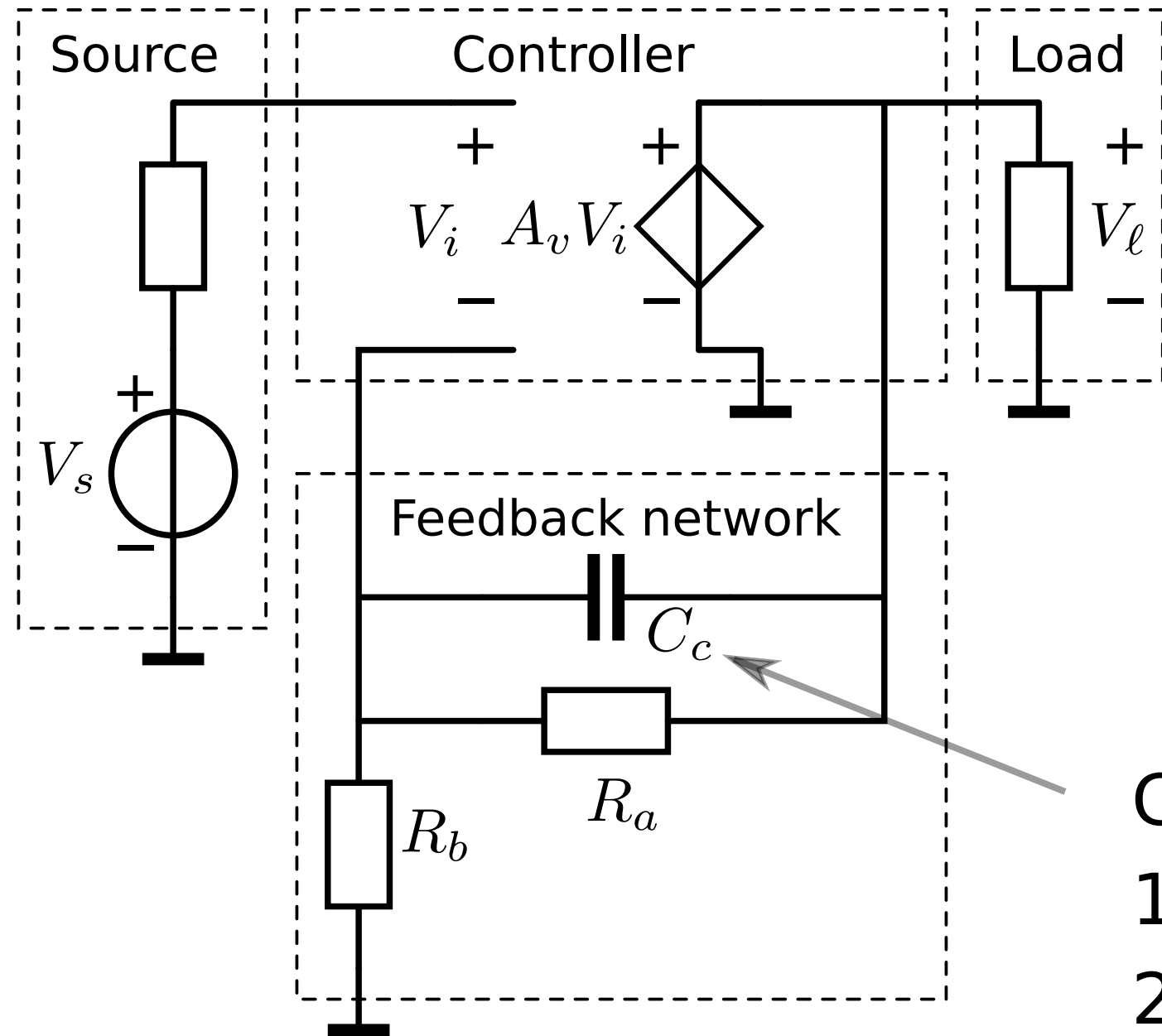


Compensation capacitance causes:

1. A pole in the asymptotic gain
2. A zero in the loop gain
3. A zero in the asymptotic gain
4. A pole in the loop gain

$$\left. \begin{array}{l} 1. \text{ A pole in the asymptotic gain} \\ 2. \text{ A zero in the loop gain} \\ 3. \text{ A zero in the asymptotic gain} \\ 4. \text{ A pole in the loop gain} \end{array} \right\} s = -\frac{1}{2\pi R_a C_c}$$

# Effectiveness of phantom zeros

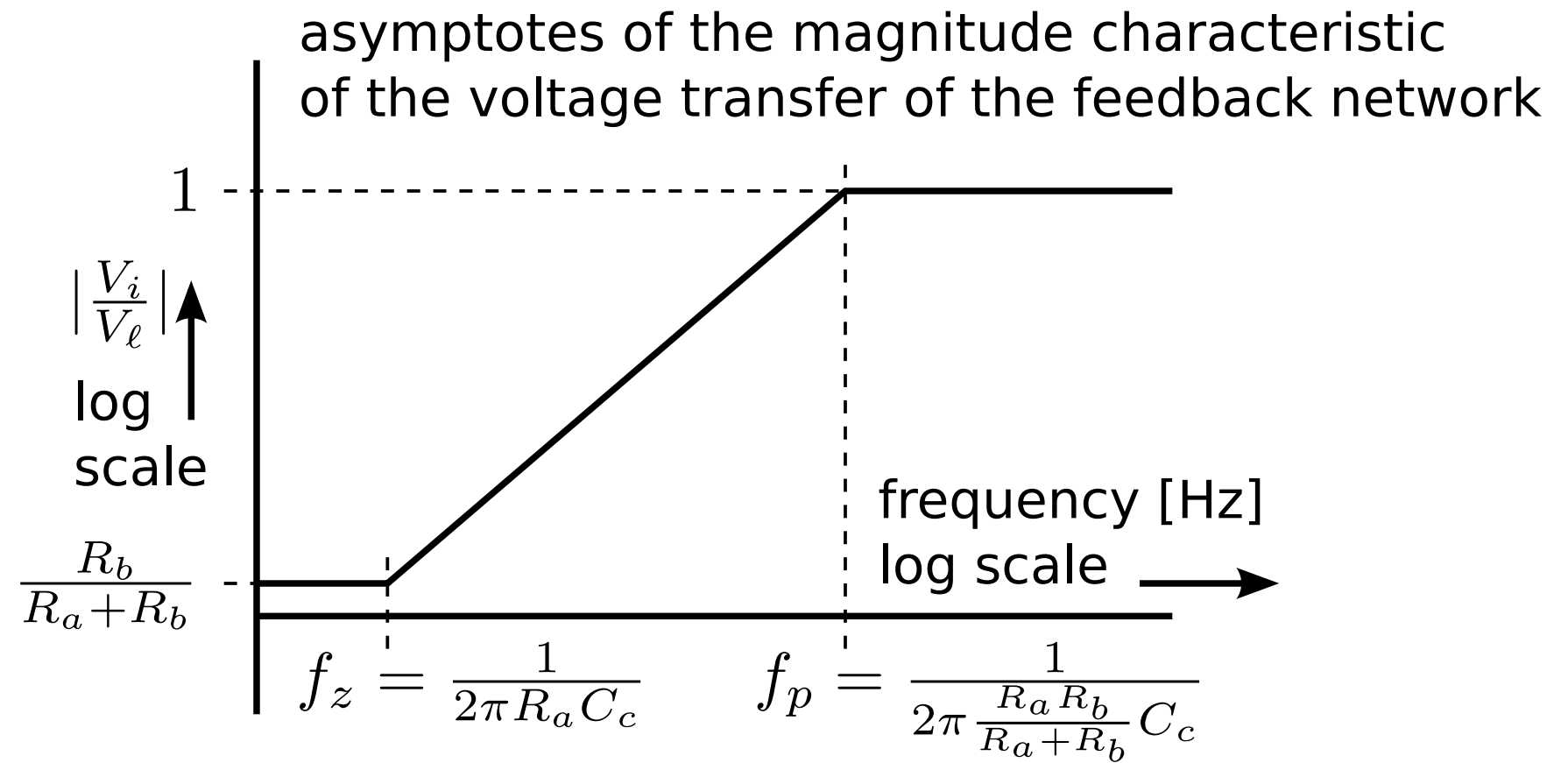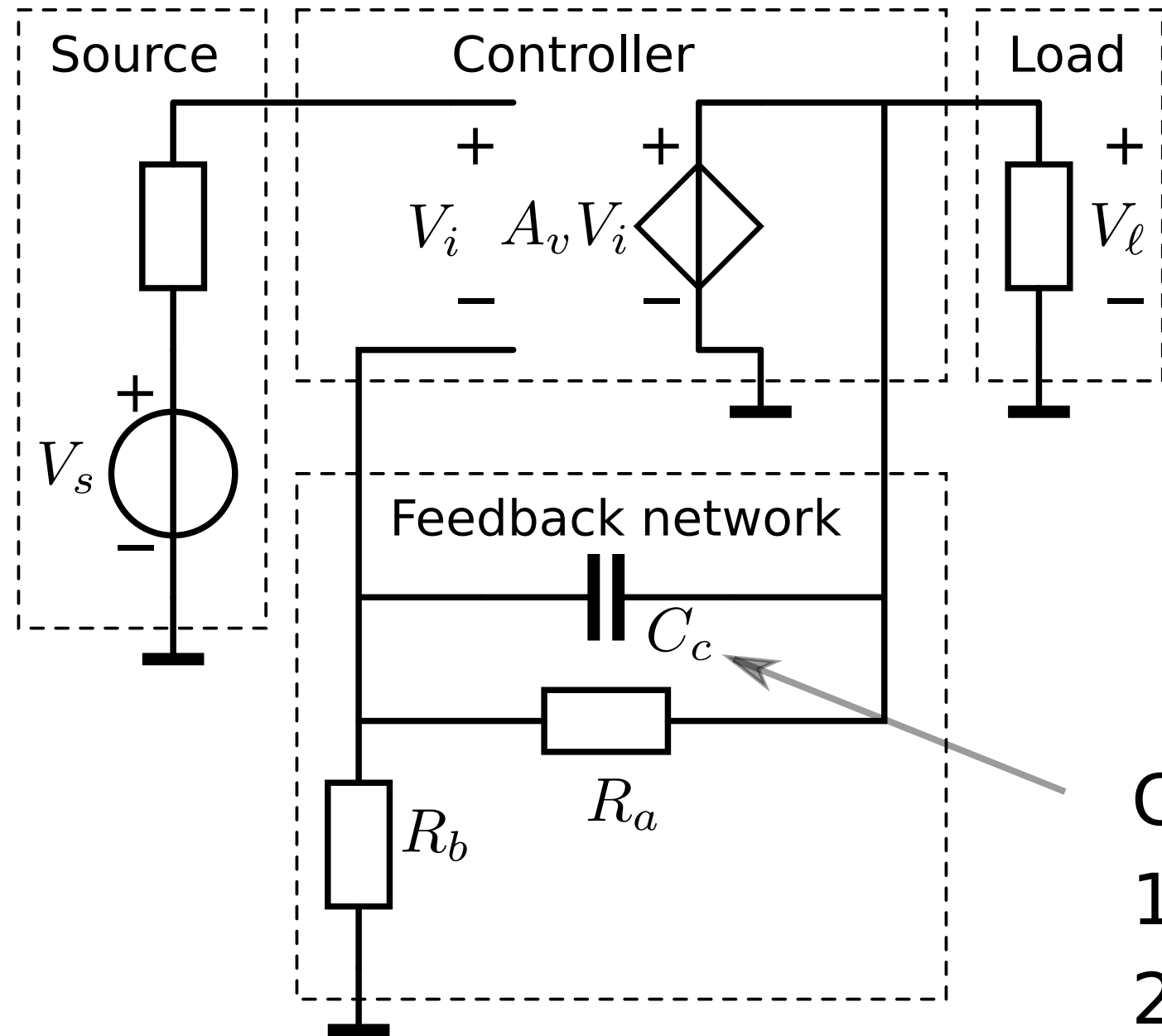

Compensation capacitance causes:



1. A pole in the asymptotic gain
2. A zero in the loop gain
3. A zero in the asymptotic gain
4. A pole in the loop gain

$$\left. \begin{array}{l} 1. \text{ A pole in the asymptotic gain} \\ 2. \text{ A zero in the loop gain} \end{array} \right\} s = -\frac{1}{2\pi R_a C_c}$$

$$\left. \begin{array}{l} 3. \text{ A zero in the asymptotic gain} \\ 4. \text{ A pole in the loop gain} \end{array} \right\} s = -\frac{1}{2\pi \frac{R_a R_b}{R_a + R_b} C_c}$$



# Effectiveness of phantom zeros

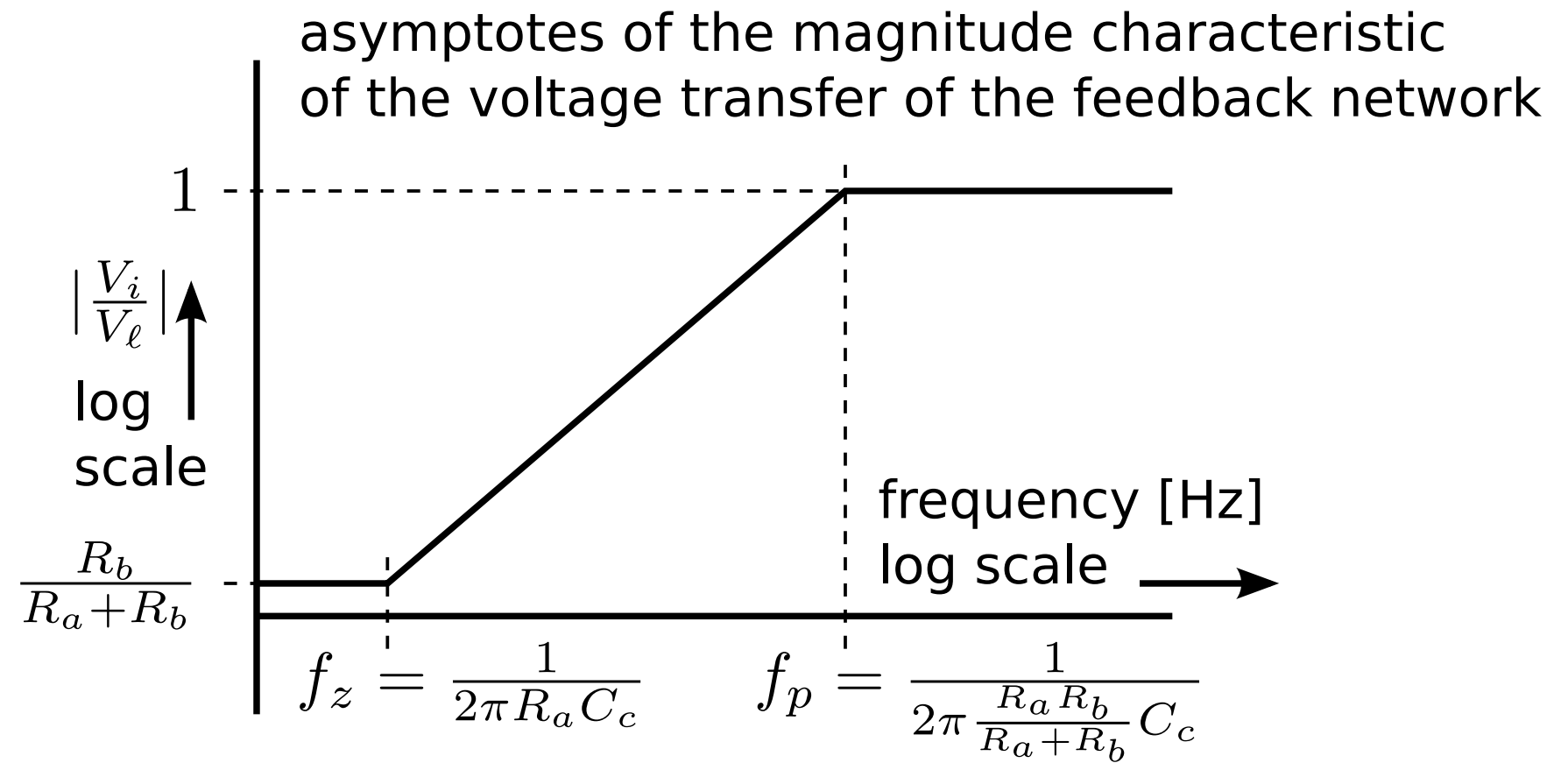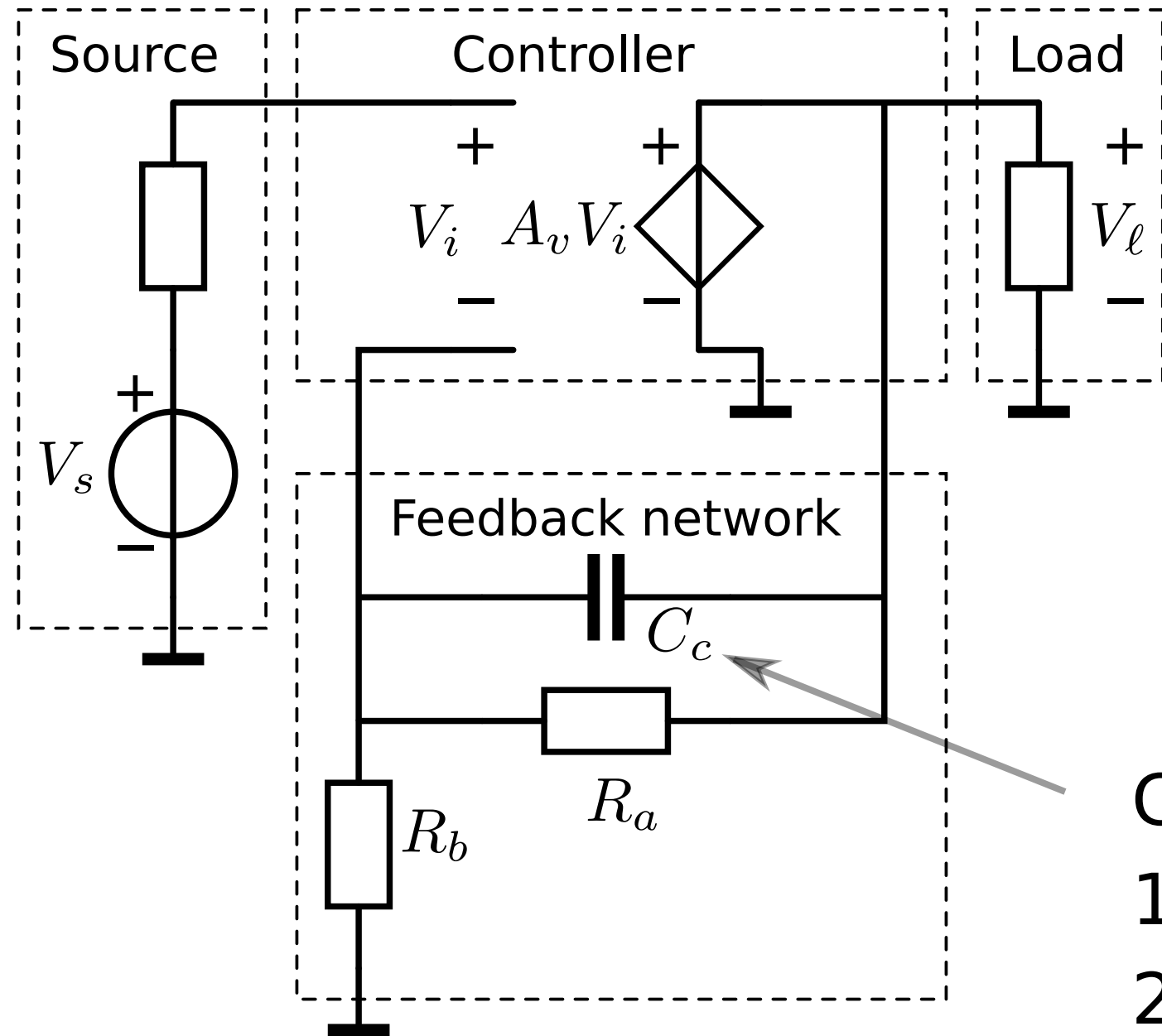

Compensation capacitance causes:



1. A pole in the asymptotic gain
2. A zero in the loop gain
3. A zero in the asymptotic gain
4. A pole in the loop gain

$$\left. \begin{array}{l} 1. \text{ A pole in the asymptotic gain} \\ 2. \text{ A zero in the loop gain} \end{array} \right\} s = -\frac{1}{2\pi R_a C_c}$$

$$\left. \begin{array}{l} 3. \text{ A zero in the asymptotic gain} \\ 4. \text{ A pole in the loop gain} \end{array} \right\} s = -\frac{1}{2\pi \frac{R_a R_b}{R_a + R_b} C_c}$$

Effective phantom zero (in this case, not a rule!) if:

# Effectiveness of phantom zeros

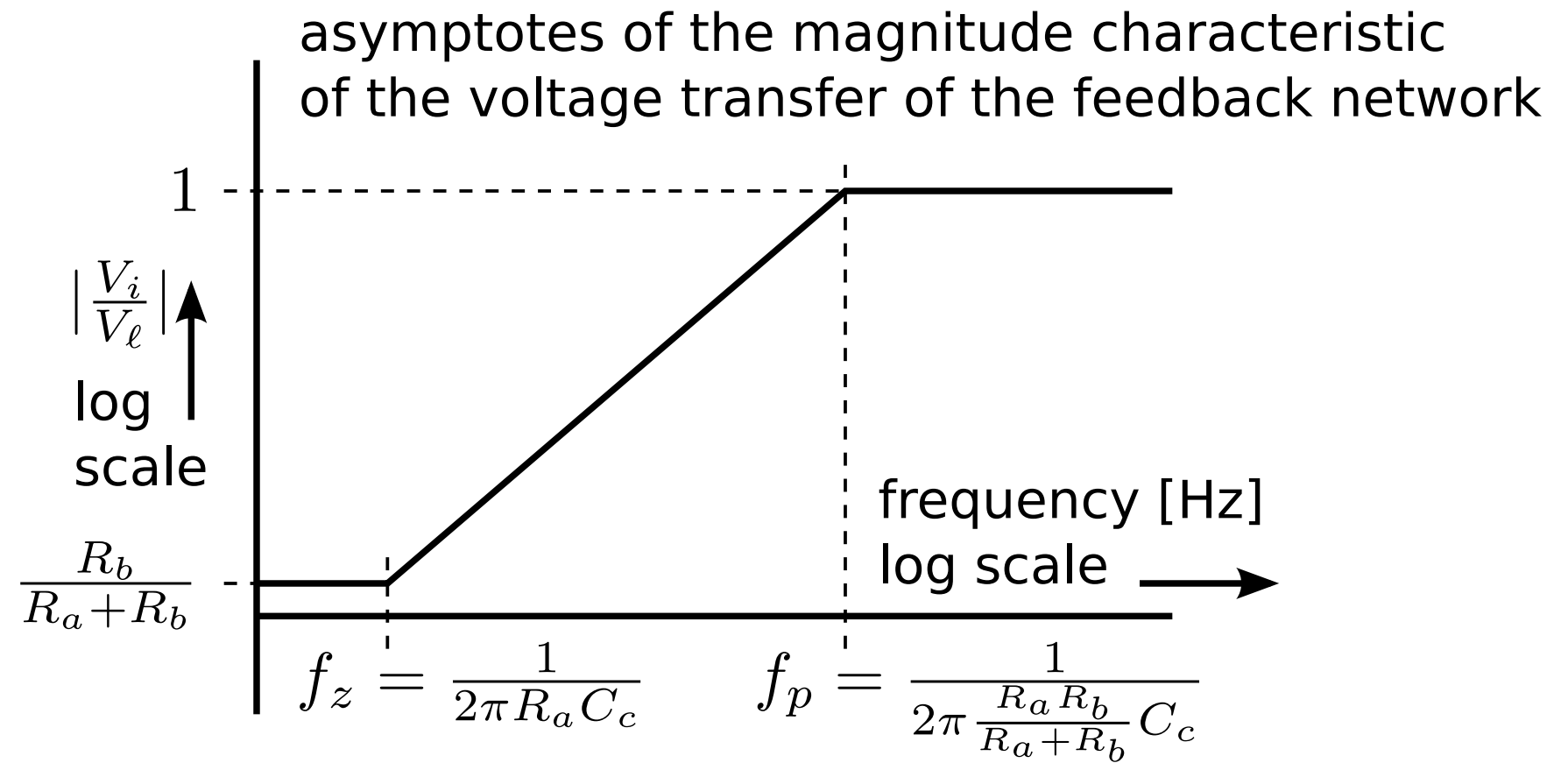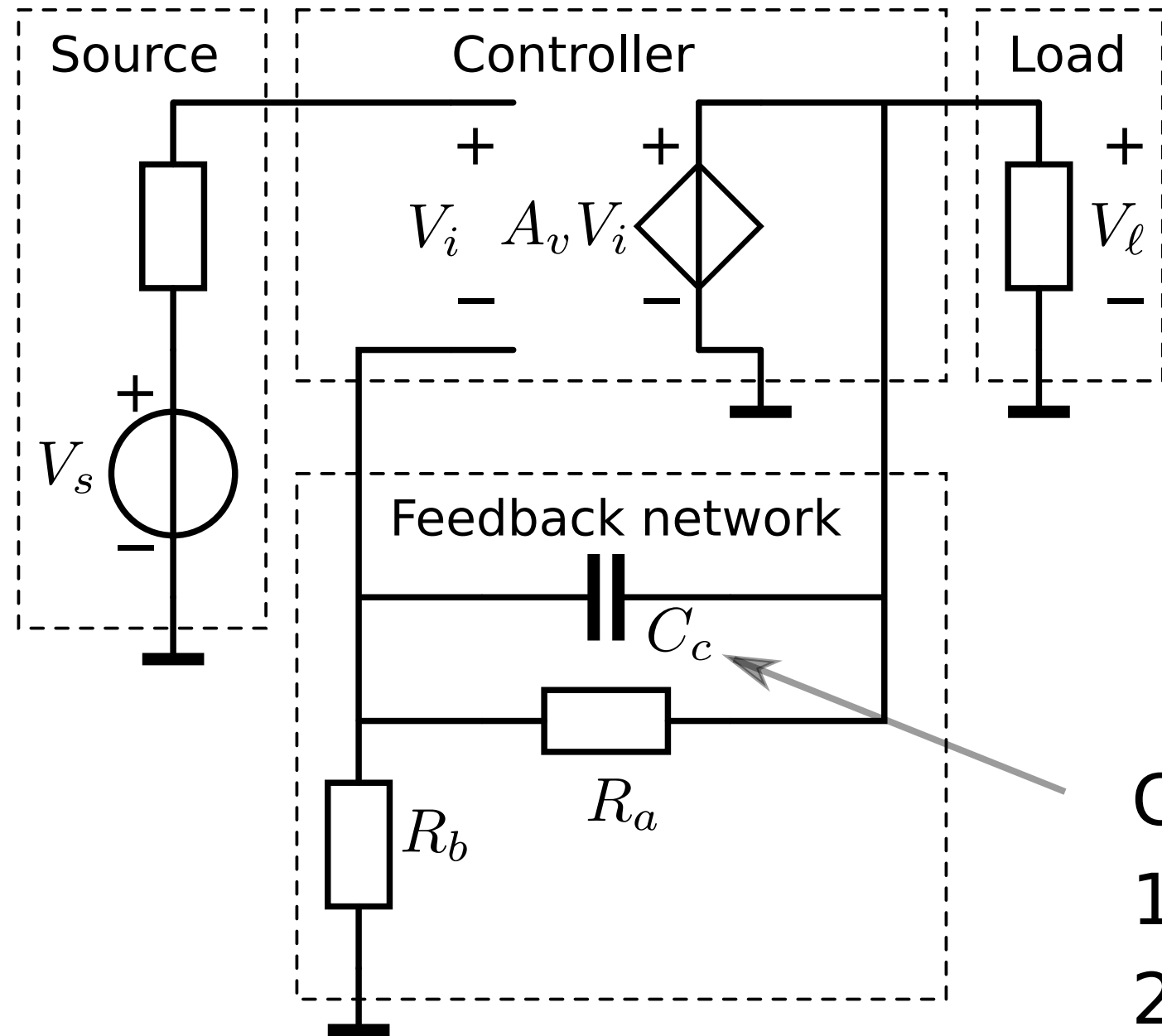

Compensation capacitance causes:



1. A pole in the asymptotic gain
2. A zero in the loop gain
3. A zero in the asymptotic gain
4. A pole in the loop gain

$$\left. \begin{array}{l} 1. \text{ A pole in the asymptotic gain} \\ 2. \text{ A zero in the loop gain} \end{array} \right\} s = -\frac{1}{2\pi R_a C_c}$$

$$\left. \begin{array}{l} 3. \text{ A zero in the asymptotic gain} \\ 4. \text{ A pole in the loop gain} \end{array} \right\} s = -\frac{1}{2\pi \frac{R_a R_b}{R_a + R_b} C_c}$$

Effective phantom zero (in this case, not a rule!) if:  $R_a \gg R_b$

# Effectiveness of phantom zeros

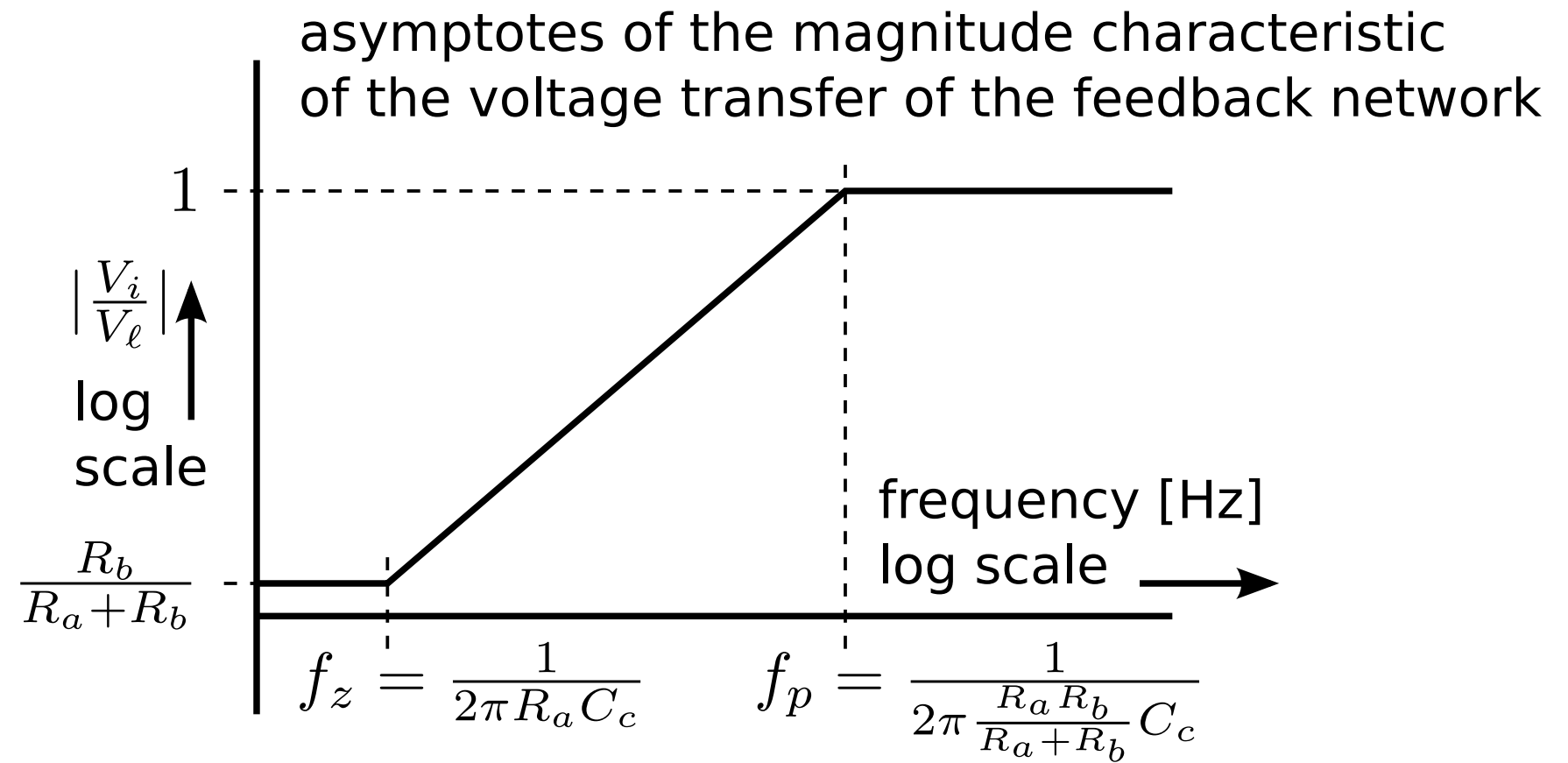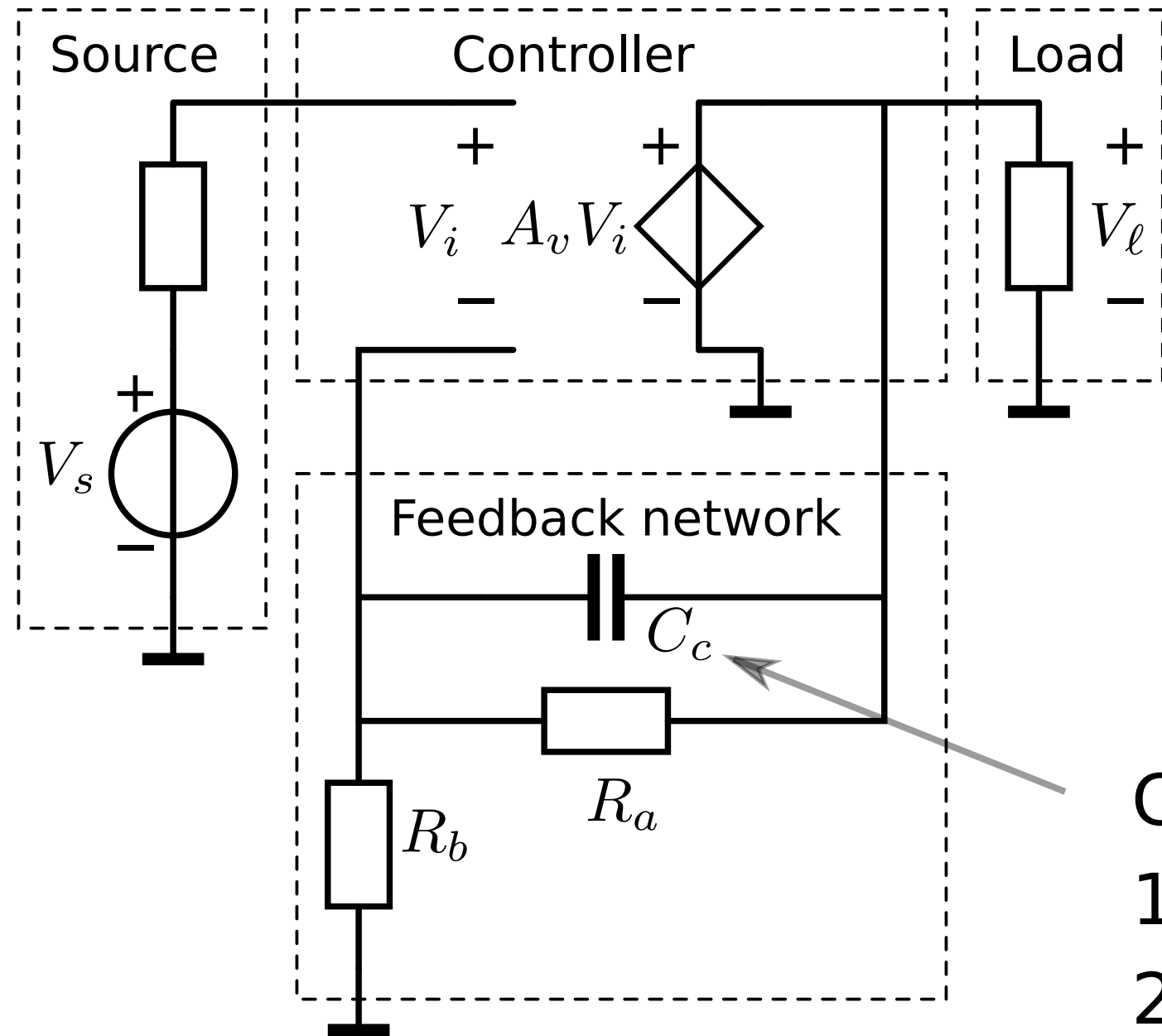

Compensation capacitance causes:

1. A pole in the asymptotic gain
2. A zero in the loop gain
3. A zero in the asymptotic gain
4. A pole in the loop gain

$$\left. \begin{array}{l} 1. \text{ A pole in the asymptotic gain} \\ 2. \text{ A zero in the loop gain} \end{array} \right\} s = -\frac{1}{2\pi R_a C_c}$$

$$\left. \begin{array}{l} 3. \text{ A zero in the asymptotic gain} \\ 4. \text{ A pole in the loop gain} \end{array} \right\} s = -\frac{1}{2\pi \frac{R_a R_b}{R_a + R_b} C_c}$$

Effective phantom zero (in this case, not a rule!) if:  $R_a \gg R_b$