

Structured Electronic Design

Contribution of Stages to LP product

Loop gain-poles product

Loop gain-poles product

? How much can a stage contribute to the product of the loop gain and the dominant poles

Loop gain-poles product

? How much can a stage contribute to the product of the loop gain and the dominant poles

Negative feedback increases the bandwidth:

Loop gain-poles product

? How much can a stage contribute to the product of the loop gain and the dominant poles

Negative feedback increases the bandwidth:

Negative feedback may move a pole outside the group of dominant poles

Loop gain-poles product

? How much can a stage contribute to the product of the loop gain and the dominant poles

Negative feedback increases the bandwidth:

Negative feedback may move a pole outside the group of dominant poles

If this is the case, the contribution of a stage to the LP product is reduced

Loop gain-poles product

? How much can a stage contribute to the product of the loop gain and the dominant poles

Negative feedback increases the bandwidth:

Negative feedback may move a pole outside the group of dominant poles

If this is the case, the contribution of a stage to the LP product is reduced

Resistive broadbanding increases the bandwidth:

Loop gain-poles product

? How much can a stage contribute to the product of the loop gain and the dominant poles

Negative feedback increases the bandwidth:

Negative feedback may move a pole outside the group of dominant poles

If this is the case, the contribution of a stage to the LP product is reduced

Resistive broadbanding increases the bandwidth:

Resistive broadbanding may move a pole outside the group of dominant poles

Loop gain-poles product

? How much can a stage contribute to the product of the loop gain and the dominant poles

Negative feedback increases the bandwidth:

Negative feedback may move a pole outside the group of dominant poles

If this is the case, the contribution of a stage to the LP product is reduced

Resistive broadbanding increases the bandwidth:

Resistive broadbanding may move a pole outside the group of dominant poles

If so the contribution of a stage to the LP product is reduced

Loop gain-poles product

? How much can a stage contribute to the product of the loop gain and the dominant poles

Negative feedback increases the bandwidth:

Negative feedback may move a pole outside the group of dominant poles

If this is the case, the contribution of a stage to the LP product is reduced

Resistive broadbanding increases the bandwidth:

Resistive broadbanding may move a pole outside the group of dominant poles

If so the contribution of a stage to the LP product is reduced

Current-driven shorted CS stage (or balanced) has the largest contribution to LP product

Loop gain-poles product

? How much can a stage contribute to the product of the loop gain and the dominant poles

Negative feedback increases the bandwidth:

Negative feedback may move a pole outside the group of dominant poles

If this is the case, the contribution of a stage to the LP product is reduced

Resistive broadbanding increases the bandwidth:

Resistive broadbanding may move a pole outside the group of dominant poles

If so the contribution of a stage to the LP product is reduced

Current-driven shorted CS stage (or balanced) has the largest contribution to LP product

Maximum contribution = f_T

Loop gain-poles product

? How much can a stage contribute to the product of the loop gain and the dominant poles

Negative feedback increases the bandwidth:

Negative feedback may move a pole outside the group of dominant poles

If this is the case, the contribution of a stage to the LP product is reduced

Resistive broadbanding increases the bandwidth:

Resistive broadbanding may move a pole outside the group of dominant poles

If so the contribution of a stage to the LP product is reduced

Current-driven shorted CS stage (or balanced) has the largest contribution to LP product

Maximum contribution = f_T

Number of stages

Number of stages

Rough estimate:

Number of stages

Rough estimate:

LP_1 = single-stage LP product

Number of stages

Rough estimate:

LP_1 = single-stage LP product

f_H = minimum value of low-pass cut-off frequency of servo function

Number of stages

Rough estimate:

LP_1 = single-stage LP product

f_H = minimum value of low-pass cut-off frequency of servo function

m = number of dominant poles of single-stage solution

Number of stages

Rough estimate:

LP_1 = single-stage LP product

f_H = minimum value of low-pass cut-off frequency of servo function

m = number of dominant poles of single-stage solution

n = minimum number of stages that need to be added to achieve f_H

Number of stages

Rough estimate:

LP_1 = single-stage LP product

f_H = minimum value of low-pass cut-off frequency of servo function

m = number of dominant poles of single-stage solution

n = minimum number of stages that need to be added to achieve f_H

Design equation:

Number of stages

Rough estimate:

LP_1 = single-stage LP product

f_H = minimum value of low-pass cut-off frequency of servo function

m = number of dominant poles of single-stage solution

n = minimum number of stages that need to be added to achieve f_H

Design equation:

$$f_H = \sqrt[n+m]{f^n LP_1}$$

Number of stages

Rough estimate:

LP_1 = single-stage LP product

f_H = minimum value of low-pass cut-off frequency of servo function

m = number of dominant poles of single-stage solution

n = minimum number of stages that need to be added to achieve f_H

Design equation:

$$f_H = \sqrt[n+m]{f_T^n LP_1}$$

Solution:

Number of stages

Rough estimate:

LP_1 = single-stage LP product

f_H = minimum value of low-pass cut-off frequency of servo function

m = number of dominant poles of single-stage solution

n = minimum number of stages that need to be added to achieve f_H

Design equation:

$$f_H = \sqrt[n+m]{f_T^n LP_1}$$

Solution:

$$n = \frac{m \log f_H - \log LP_1}{\log \frac{f_T}{f_H}}$$

Number of stages

Rough estimate:

LP_1 = single-stage LP product

f_H = minimum value of low-pass cut-off frequency of servo function

m = number of dominant poles of single-stage solution

n = minimum number of stages that need to be added to achieve f_H

Design equation:

$$f_H = \sqrt[n+m]{f_T^n LP_1}$$

Solution:

$$n = \frac{m \log f_H - \log LP_1}{\log \frac{f_T}{f_H}}$$

Structured Electronic Design

Contribution of Stages to LP product