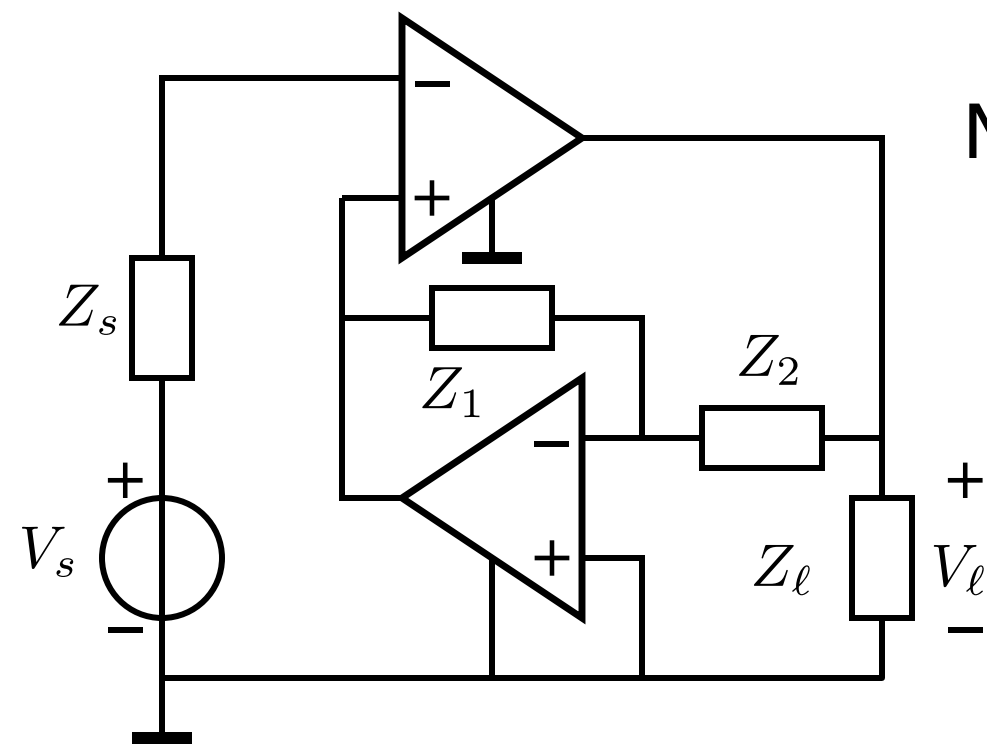


Structured Electronic Design

Multiple-nullor Circuit Synthesis



Anton J.M. Montagne

Multiple nullor synthesis technique



Inverting voltage amplifier


Nullors

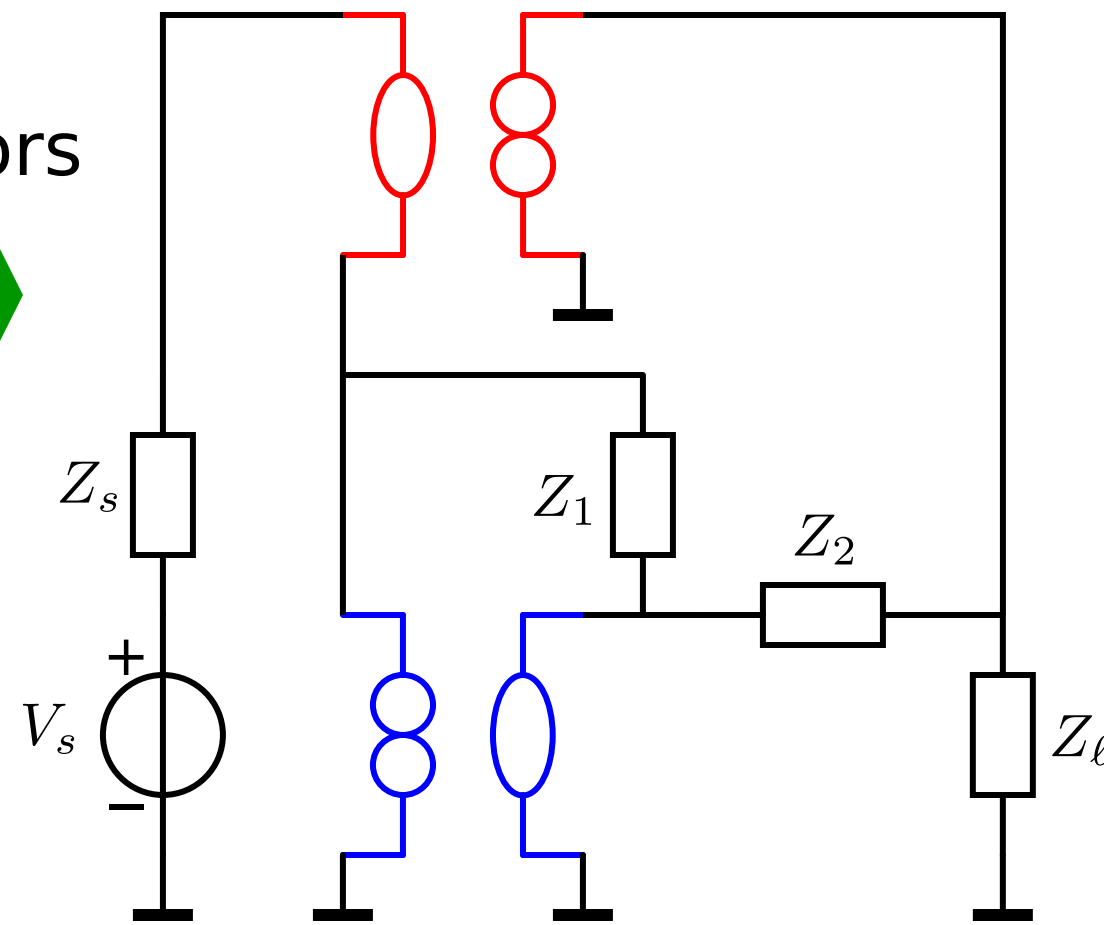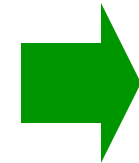

Pair differently



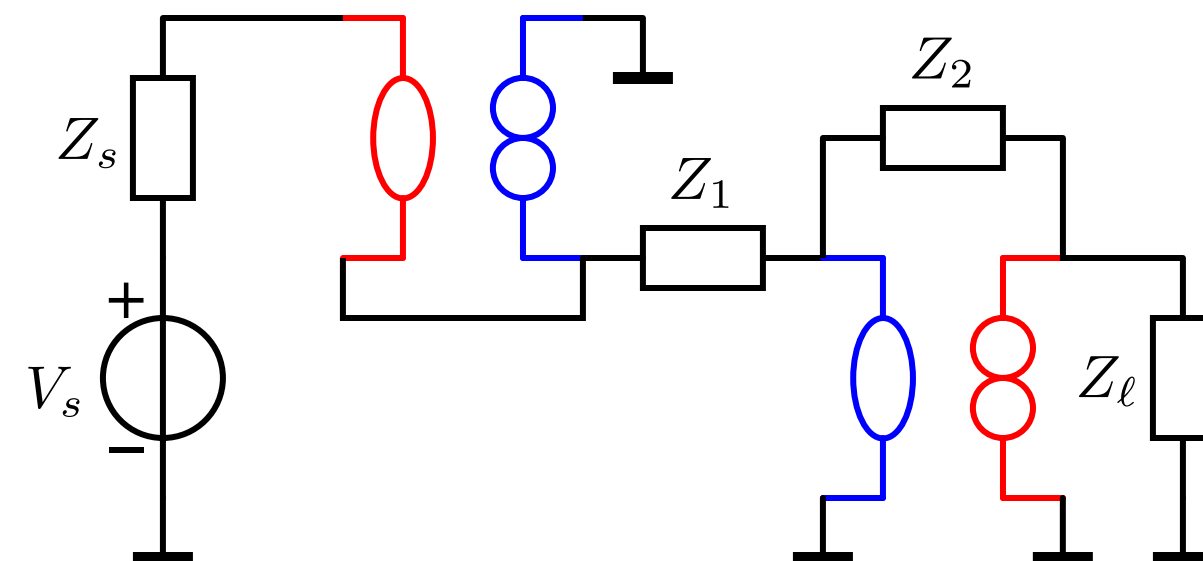Nulator and norator are independent network elements



Another inverting voltage amplifier

