

Structured Electronic Design

EE3C11

Topics from Network Theory
Modified Nodal Analysis

Anton J.M. Montagne

Modified Nodal Analysis

Modified Nodal Analysis

Voltage-controlled notation

Modified Nodal Analysis

Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the(ir) branch current(s) can be expressed in terms of branch voltage(s)

Modified Nodal Analysis

Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the(ir) branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Modified Nodal Analysis

Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the(ir) branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Current cannot be written as a function of the voltage

Modified Nodal Analysis

Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the(ir) branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Current cannot be written as a function of the voltage

Voltage can be written as a function of the current:

Modified Nodal Analysis


Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the(ir) branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Current cannot be written as a function of the voltage

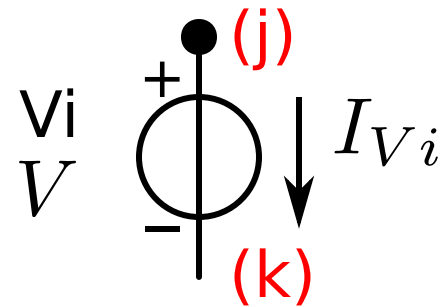Voltage can be written as a function of the current:



$$V_j - V_k = V, \forall I_{V_i}$$

Branch voltage equation
in current-controlled notation.

Modified Nodal Analysis

Voltage-controlled notation


Nodal Analysis only suited for networks with elements of which the(ir) branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Procedure

Current cannot be written as a function of the voltage

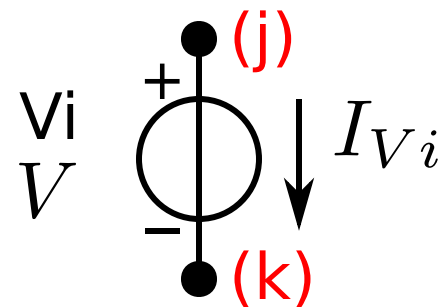Voltage can be written as a function of the current:



$$V_j - V_k = V, \forall I_{V_i}$$

Branch voltage equation
in current-controlled notation.

Modified Nodal Analysis


Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the (ir) branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Current cannot be written as a function of the voltage

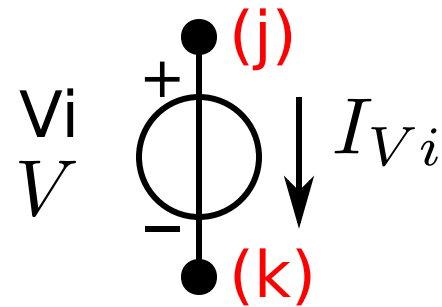Voltage can be written as a function of the current:



$$V_j - V_k = V, \forall I_{V_i}$$

Branch voltage equation
in current-controlled notation.

Procedure

Add the branch relation in current-controlled notation to the set of matrix equations:

Modified Nodal Analysis


Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the(ir)
branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Current cannot be written as a function of the voltage

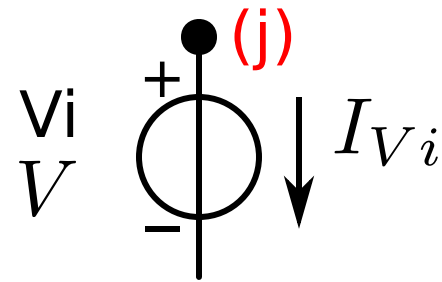Voltage can be written as a function of the current:



$$V_j - V_k = V, \forall I_{V_i}$$

Branch voltage equation
in current-controlled notation.

Procedure

Add the branch relation in current-controlled
notation to the set of matrix equations:

Unknown current is added to vector with
nodal voltages. It flows from node j to node k

Modified Nodal Analysis


Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the(ir)
branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Current cannot be written as a function of the voltage

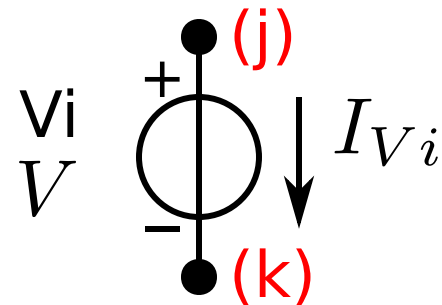Voltage can be written as a function of the current:



$$V_j - V_k = V, \forall I_{V_i}$$

Branch voltage equation
in current-controlled notation.

Procedure

Add the branch relation in current-controlled
notation to the set of matrix equations:

Unknown current is added to vector with
nodal voltages. It flows from node j to node k

Known voltage is added to vector with
nodal currents

Modified Nodal Analysis


Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the(ir)
branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Current cannot be written as a function of the voltage

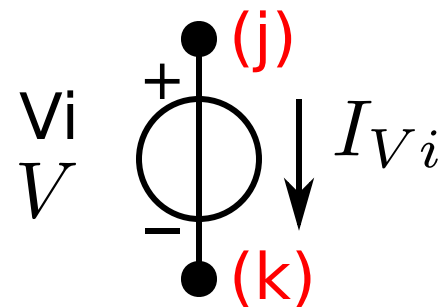Voltage can be written as a function of the current:



$$V_j - V_k = V, \forall I_{Vi}$$


Branch voltage equation
in current-controlled notation.

Procedure

Add the branch relation in current-controlled
notation to the set of matrix equations:

Unknown current is added to vector with
nodal voltages. It flows from node j to node k

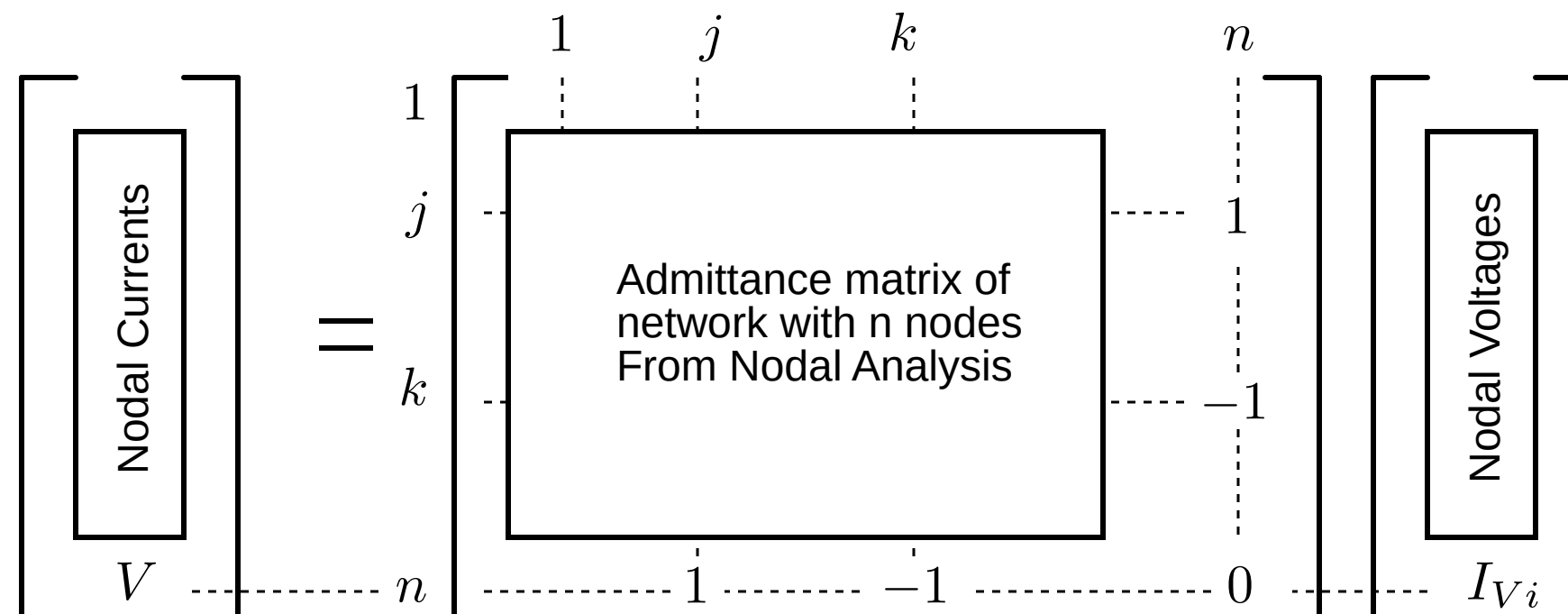Known voltage is added to vector with
nodal currents



Modified Nodal Analysis


Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the(ir)
branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Current cannot be written as a function of the voltage

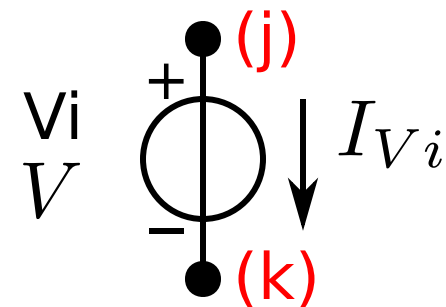Voltage can be written as a function of the current:



$$V_j - V_k = V, \forall I_{V_i}$$

Branch voltage equation
in current-controlled notation.


Procedure

Add the branch relation in current-controlled
notation to the set of matrix equations:

Unknown current is added to vector with
nodal voltages. It flows from node j to node k

Known voltage is added to vector with
nodal currents

Branch voltage
equation →

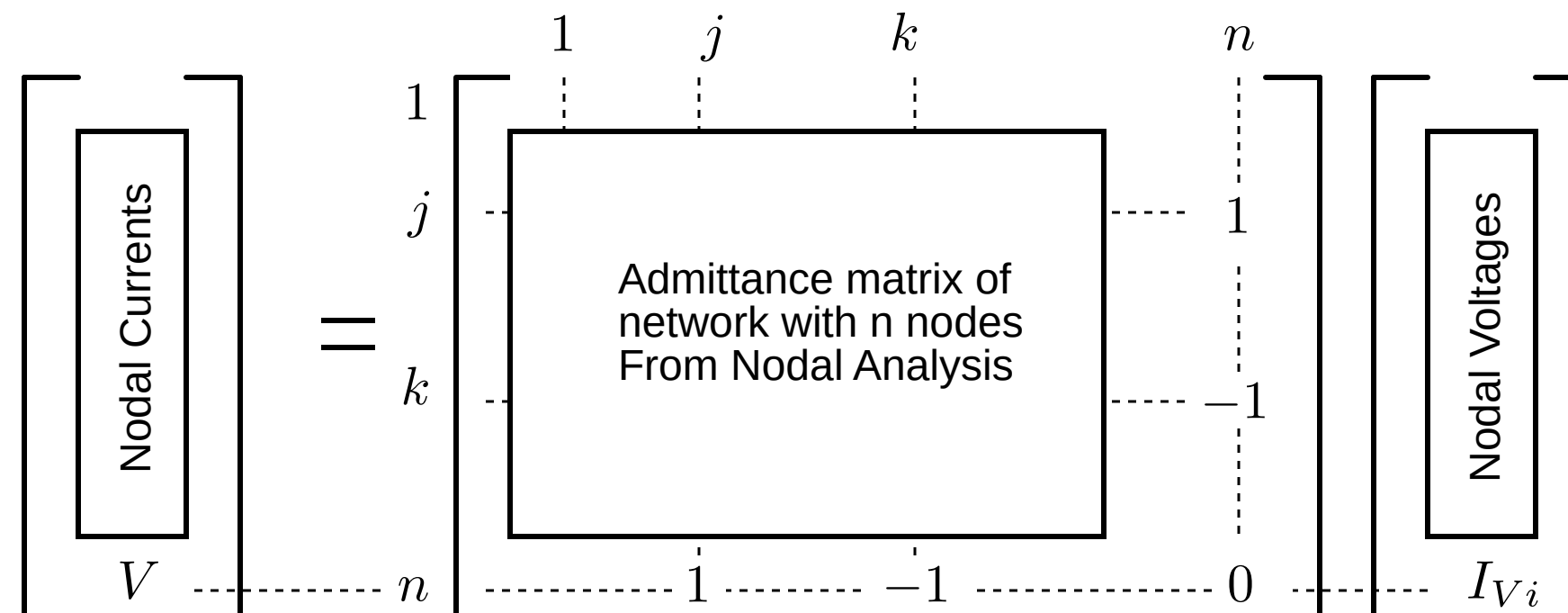

Modified Nodal Analysis


Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the(ir)
branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Current cannot be written as a function of the voltage

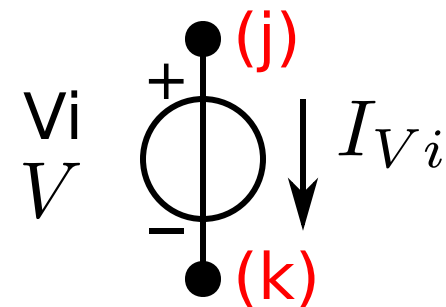Voltage can be written as a function of the current:



$$V_j - V_k = V, \forall I_{V_i}$$


Branch voltage equation
in current-controlled notation.

Procedure

Add the branch relation in current-controlled
notation to the set of matrix equations:

Unknown current is added to vector with
nodal voltages. It flows from node j to node k

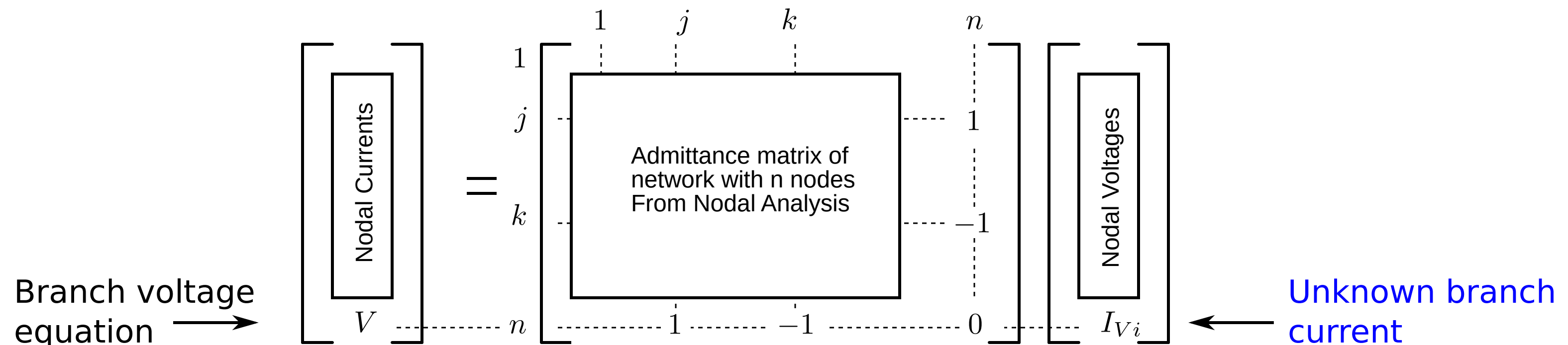Known voltage is added to vector with
nodal currents



Modified Nodal Analysis


Voltage-controlled notation

Nodal Analysis only suited for networks with elements of which the(ir)
branch current(s) can be expressed in terms of branch voltage(s)

Voltage source (example)

Current cannot be written as a function of the voltage

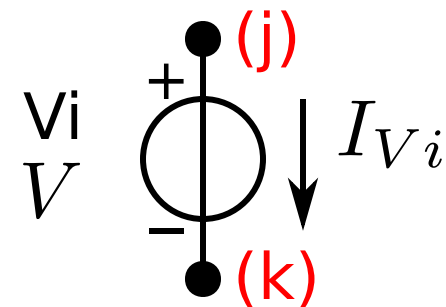Voltage can be written as a function of the current:



$$V_j - V_k = V, \forall I_{V_i}$$


Branch voltage equation
in current-controlled notation.

Procedure

Add the branch relation in current-controlled
notation to the set of matrix equations:

Unknown current is added to vector with
nodal voltages. It flows from node j to node k

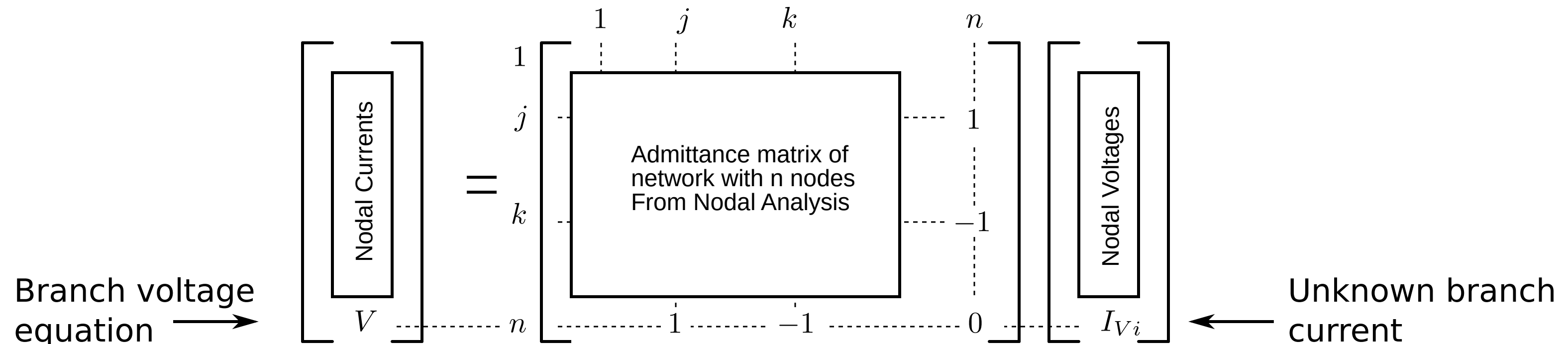Known voltage is added to vector with
nodal currents



Transfer function

Transfer function

Transfer from independent variable k to dependent variable j

Transfer function

Transfer from independent variable k to dependent variable j

$$\frac{\mathbf{V}_j}{\mathbf{I}_k} = \mathbf{M}_{j,k}^{-1} = \frac{(-1)^{j+k} \det(\mathcal{M}_{k,j})}{\det(\mathbf{M})}$$

Transfer function

Transfer from independent variable k to dependent variable j

$$\frac{\mathbf{V}_j}{\mathbf{I}_k} = \mathbf{M}_{j,k}^{-1} = \frac{(-1)^{j+k} \det(\mathcal{M}_{k,j})}{\det(\mathbf{M})}$$

Minor matrix: $\mathcal{M}_{k,j}$ equals \mathbf{M} after leaving out row k and column j .

Transfer function

Transfer from independent variable k to dependent variable j

$$\frac{\mathbf{V}_j}{\mathbf{I}_k} = \mathbf{M}_{j,k}^{-1} = \frac{(-1)^{j+k} \det(\mathcal{M}_{k,j})}{\det(\mathbf{M})}$$

Minor matrix: $\mathcal{M}_{k,j}$ equals \mathbf{M} after leaving out row k and column j .

Poles: $\det(\mathbf{M}) = 0$

Transfer function

Transfer from independent variable k to dependent variable j

$$\frac{\mathbf{V}_j}{\mathbf{I}_k} = \mathbf{M}_{j,k}^{-1} = \frac{(-1)^{j+k} \det(\mathcal{M}_{k,j})}{\det(\mathbf{M})}$$

Minor matrix: $\mathcal{M}_{k,j}$ equals \mathbf{M} after leaving out row k and column j .

Poles: $\det(\mathbf{M}) = 0$

Zeros: $\det(\mathcal{M}_{k,j}) = 0$

Transfer function

Transfer from independent variable k to dependent variable j

$$\frac{\mathbf{V}_j}{\mathbf{I}_k} = \mathbf{M}_{j,k}^{-1} = \frac{(-1)^{j+k} \det(\mathcal{M}_{k,j})}{\det(\mathbf{M})}$$

Minor matrix: $\mathcal{M}_{k,j}$ equals \mathbf{M} after leaving out row k and column j .

Poles: $\det(\mathbf{M}) = 0$

Zeros: $\det(\mathcal{M}_{k,j}) = 0$