

Structured Electronic Design

EE3C11

Topics from Network Theory
Nodal Analysis


Anton J.M. Montagne

Nodal Analysis

An electrical network consists of interconnected network elements

Node: interconnection point

Branch: element between two nodes

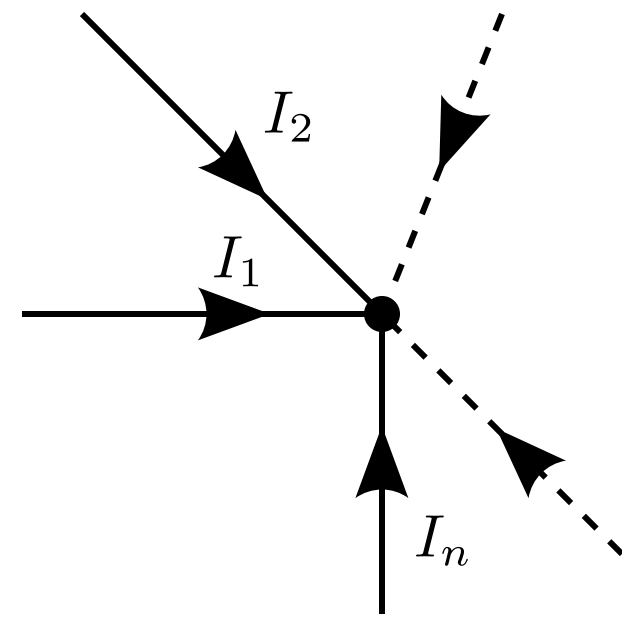

Kirchhoff's current law

The sum of the branch currents that flow into (or from) a node, equals zero:

$$\sum_{i=1}^{i=n} I_i = 0$$

Network with n nodes

1 node selected as reference node
n-1 nodal voltages w.r.t. voltage of ref. node
n-1 independent nodal equations

Only voltage-controlled elements:
Branch current can be written as
a function of the branch voltage

$$\mathbf{I} = \mathbf{Y} \cdot \mathbf{V}$$

Diagram illustrating the nodal analysis equation $\mathbf{I} = \mathbf{Y} \cdot \mathbf{V}$:


- \mathbf{I} : Vector with sum of independent currents flowing into a node
- \mathbf{Y} : Admittance matrix
- \mathbf{V} : Vector with nodal voltages


Admittance Matrix

General form of nodal equation:

Sum of independent currents flowing into node k


Diagonal element: sum of admittances connected to node k

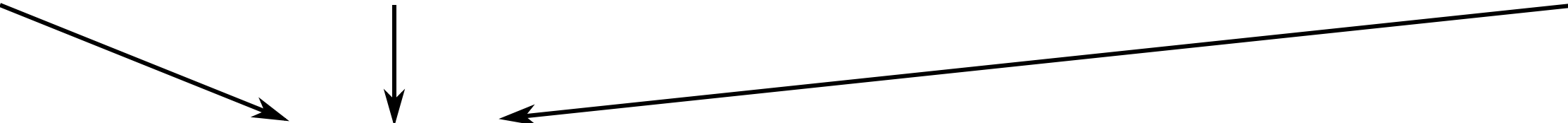
$$\sum i_k = - \sum \mathbf{Y}_{k,1} v_1 - \sum \mathbf{Y}_{k,2} v_2 \dots + \sum \mathbf{Y}_{k,k} v_k \dots - \sum \mathbf{Y}_{k,n-1} v_{n-1}$$



Off-diagonal element: $\sum \mathbf{Y}_{k,j} =$ Sum of admittances connected between node k and node j

Nodal Analysis

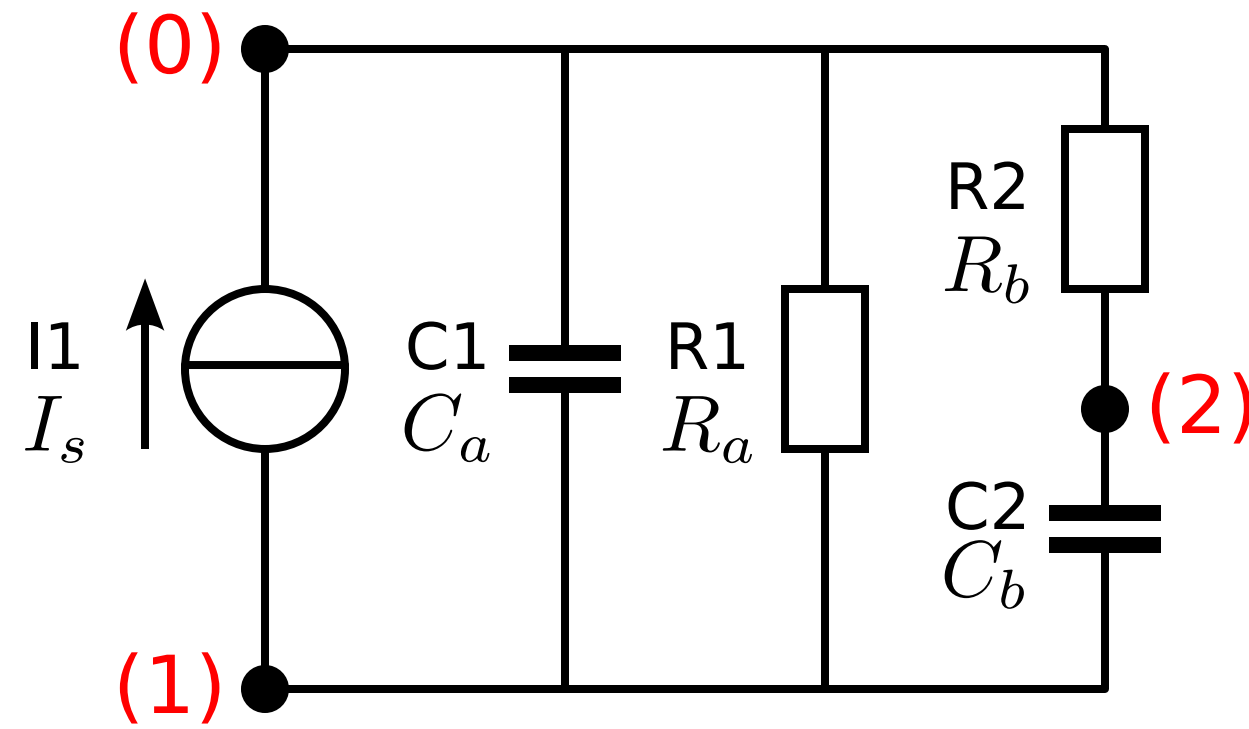

Node (0) is reference node

Two independent nodal equations:

$$(1) \quad 0 = I_s + V_1 s C_a + V_1 \frac{1}{R_a} + (V_1 - V_2) s C_b$$

$$(2) \quad 0 = V_2 \frac{1}{R_b} + (V_2 - V_1) s C_b$$

In matrix form:

$$\begin{pmatrix} -I_s \\ 0 \end{pmatrix} = \begin{pmatrix} s(C_a + C_b) + \frac{1}{R_a} & -sC_b \\ -sC_b & sC_b + \frac{1}{R_b} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$