

# **Structured Electronic Design**

Design of application-specific  
negative feedback amplifiers  
in CMOS technology  
(recap)


*Anton J.M. Montagne*

# **Structured Electronic Design**

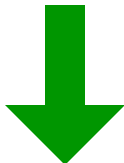
## Step 1 Setting up the specification

*Anton J.M. Montagne*


Design of independent performance aspects



*Setting up specifications*

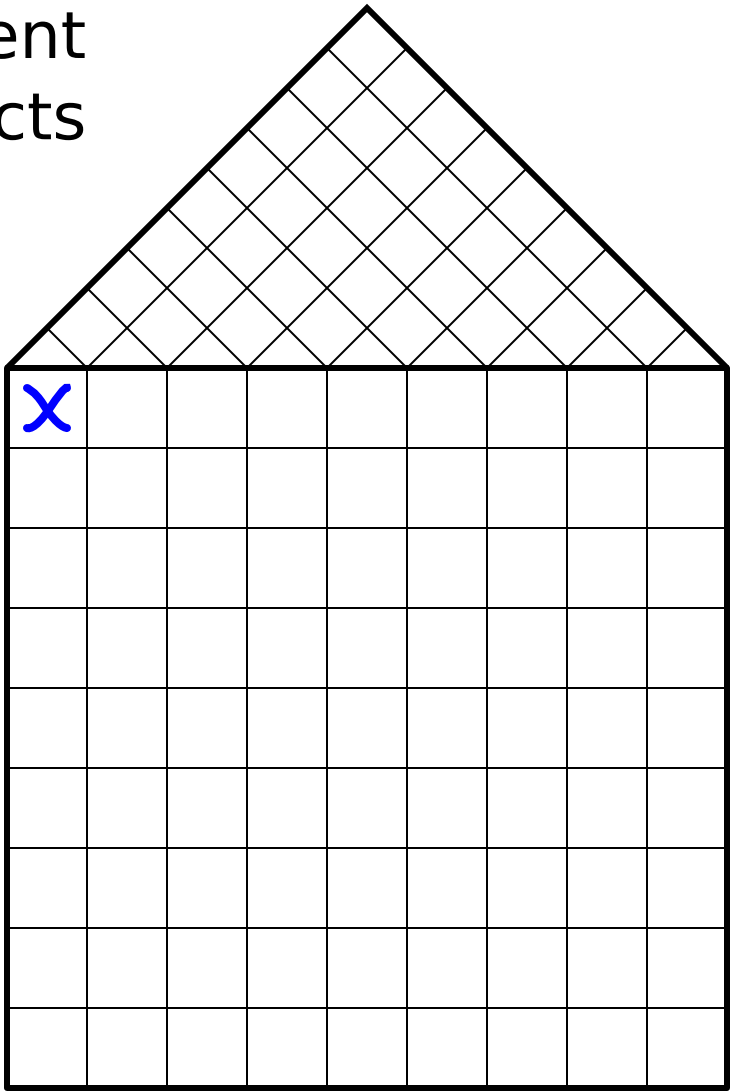


interaction between design aspects

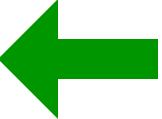


SLiCAP

*Function, performance, costs and environment*


design aspects

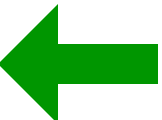

**Design of the active antenna:**

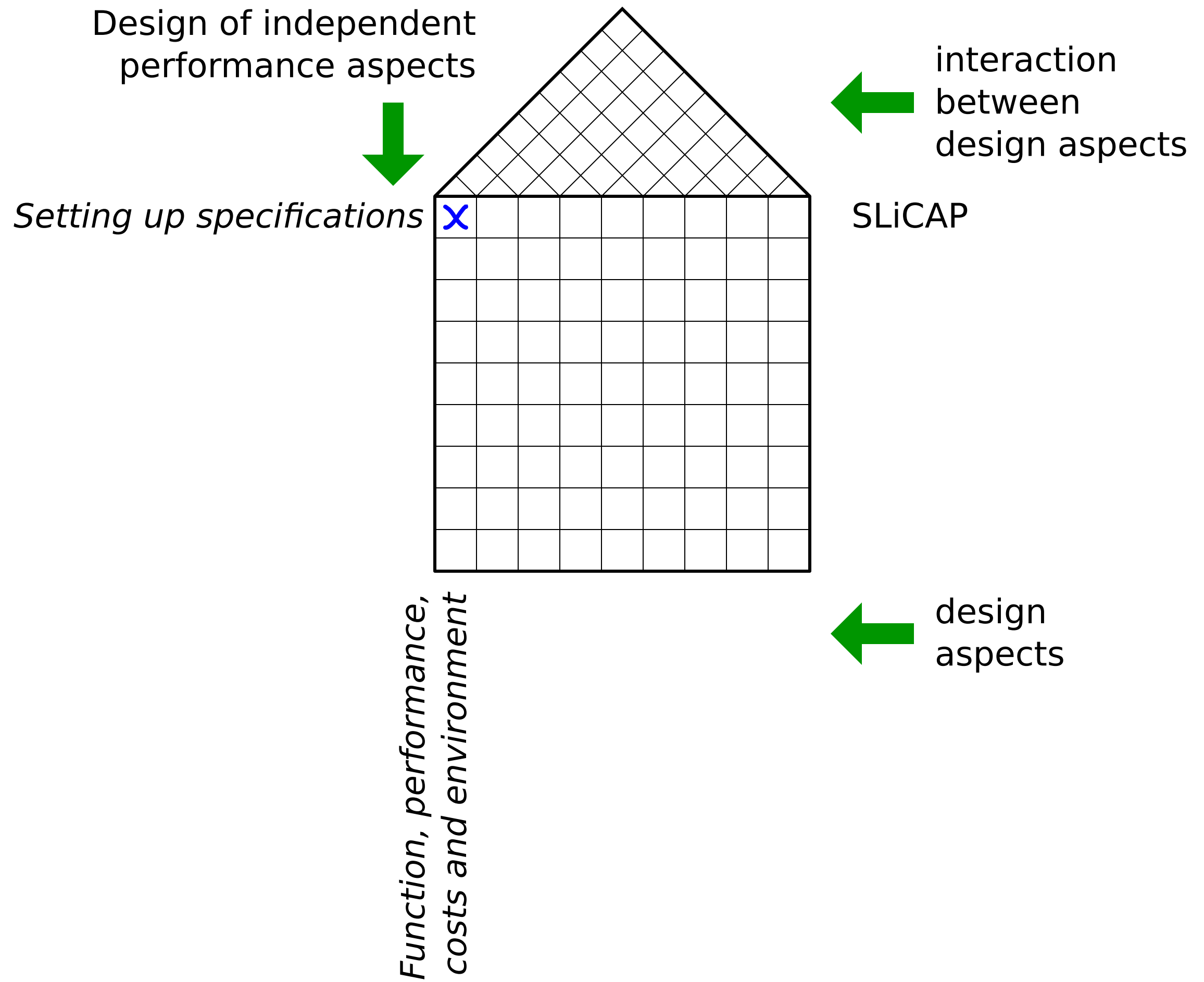

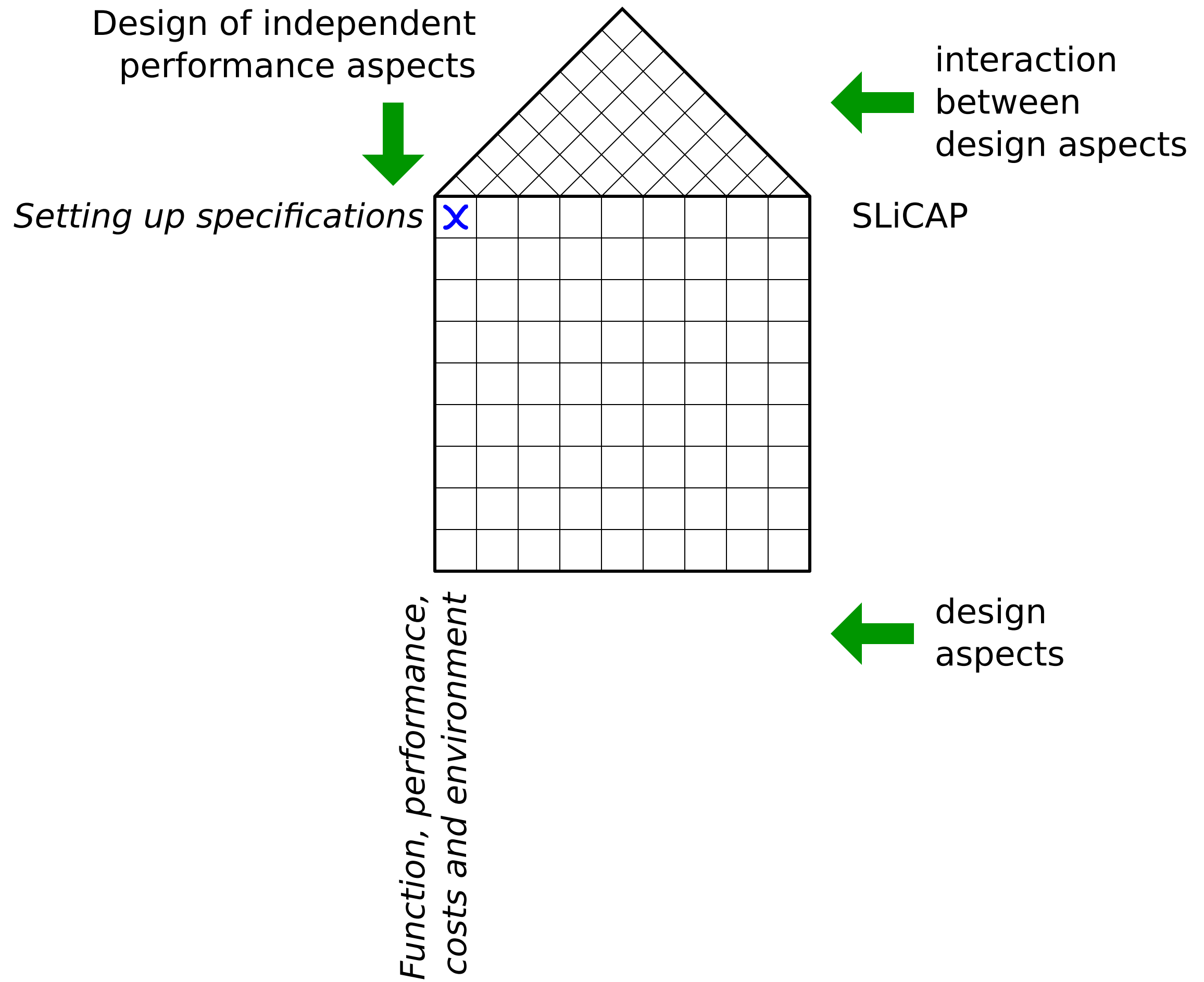
**Design of the active antenna:**  
From the application description derive:



**Design of the active antenna:**

From the application description derive:

Functional requirements

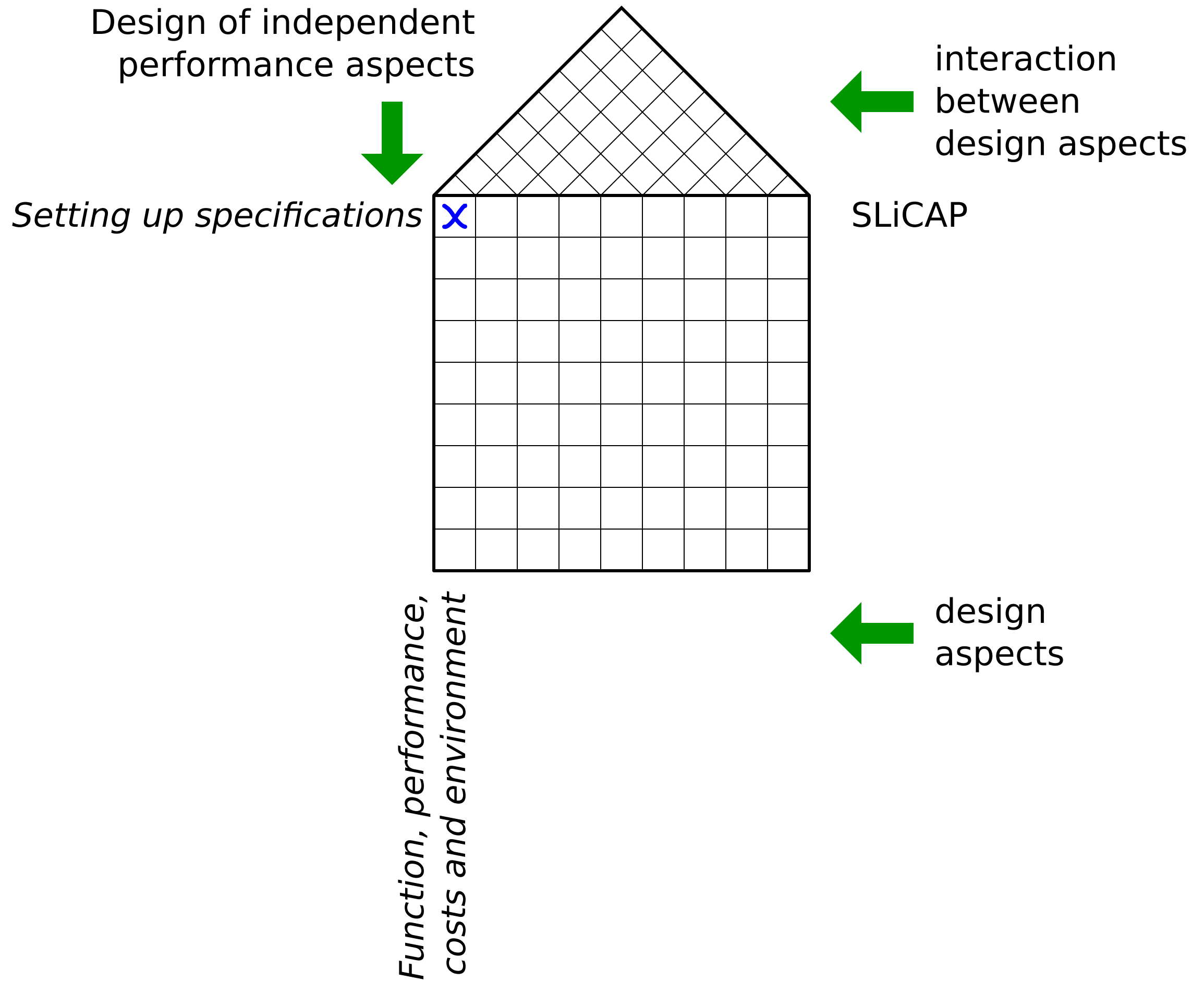

## Design of the active antenna:


From the application description derive:

Functional requirements


Port impedances

*Setting up specifications*

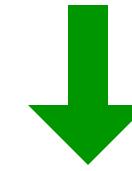
Design of independent performance aspects



interaction between design aspects

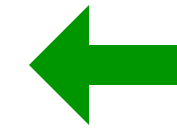


SLiCAP

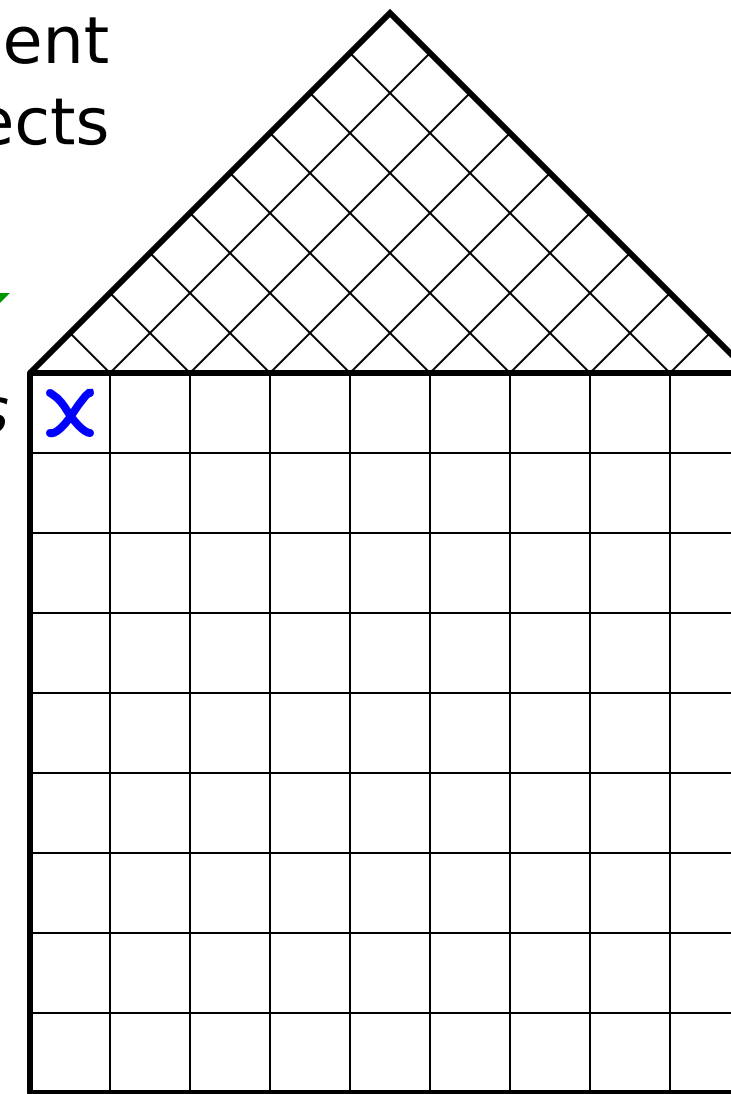

*Function, performance, costs and environment*

design aspects

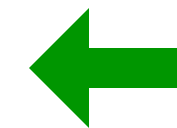

## Design of the active antenna:

From the application description derive:


Functional requirements

Port impedances


Source-to-load transfer

*Setting up specifications*

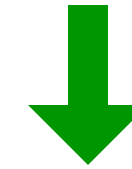
Design of independent performance aspects



interaction between design aspects

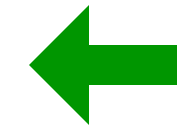


SLiCAP

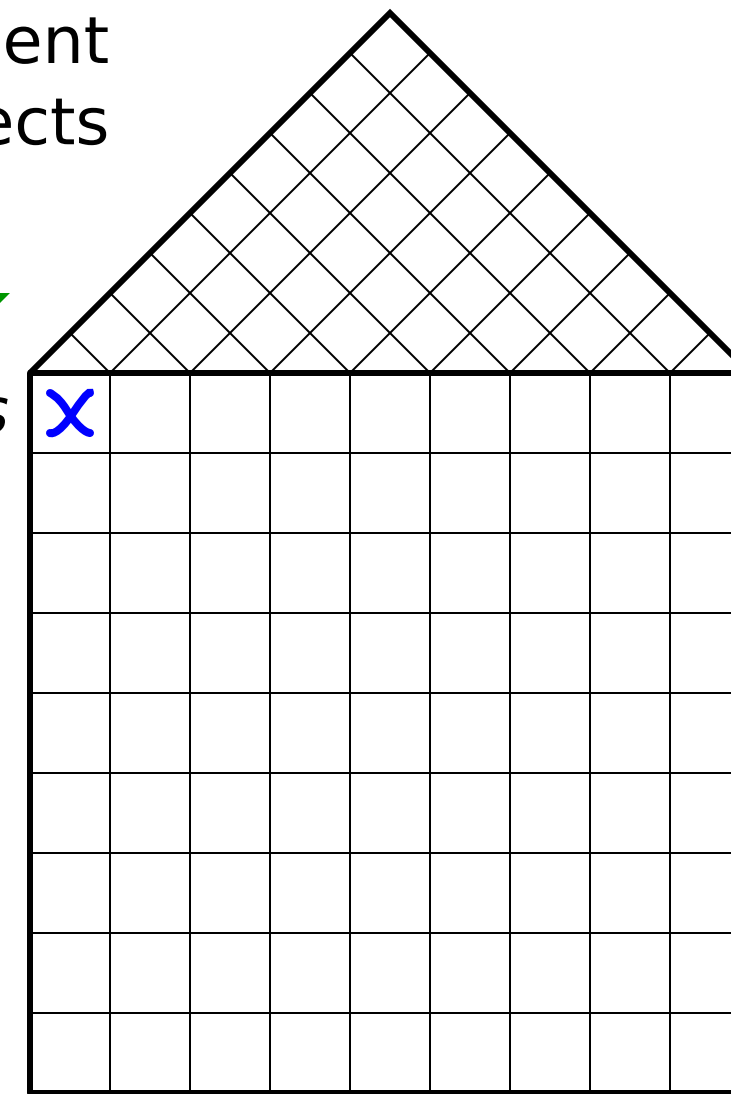

*Function, performance, costs and environment*

design aspects

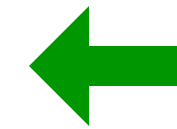




**Design of the active antenna:**

From the application description derive:



- Functional requirements
  - Port impedances
  - Source-to-load transfer

Performance requirements  
(information processing capacity and quality):

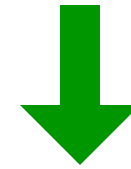Design of independent performance aspects




*Setting up specifications*

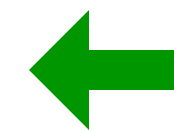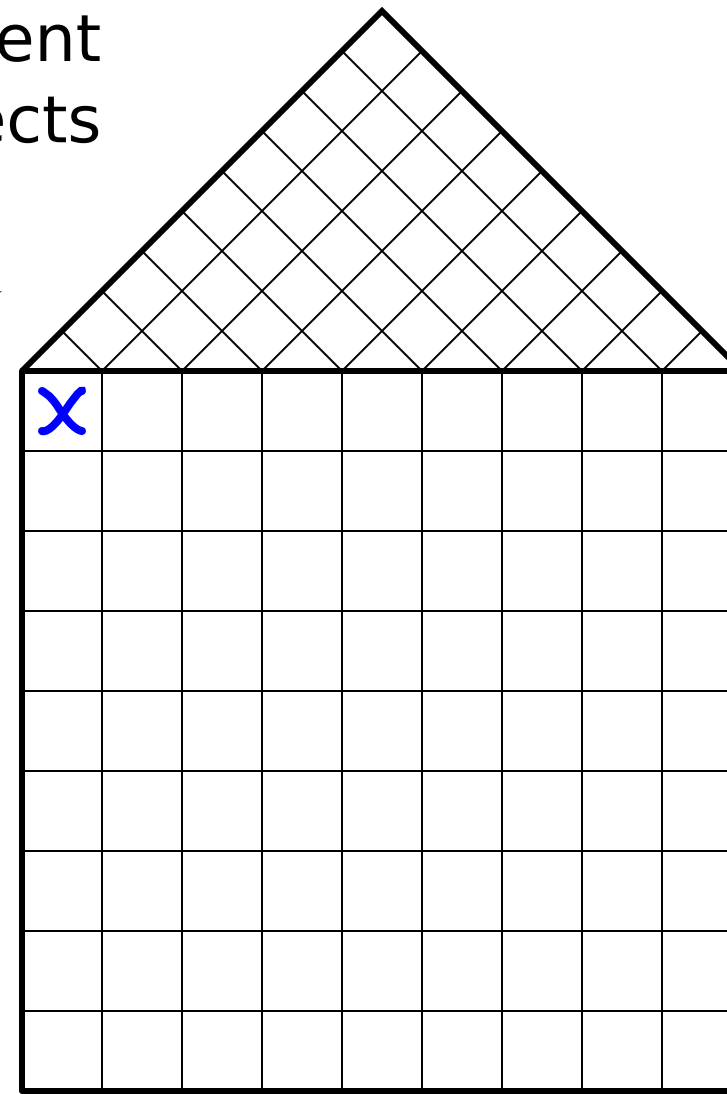

interaction between design aspects

SLiCAP

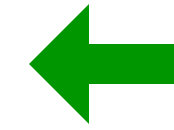

design aspects

*Function, performance, costs and environment*

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances


Source-to-load transfer

Performance requirements


(information processing capacity and quality):

Noise addition (temperature offset drift)

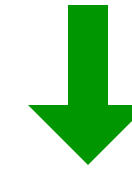Design of independent  
performance aspects



*Setting up specifications*

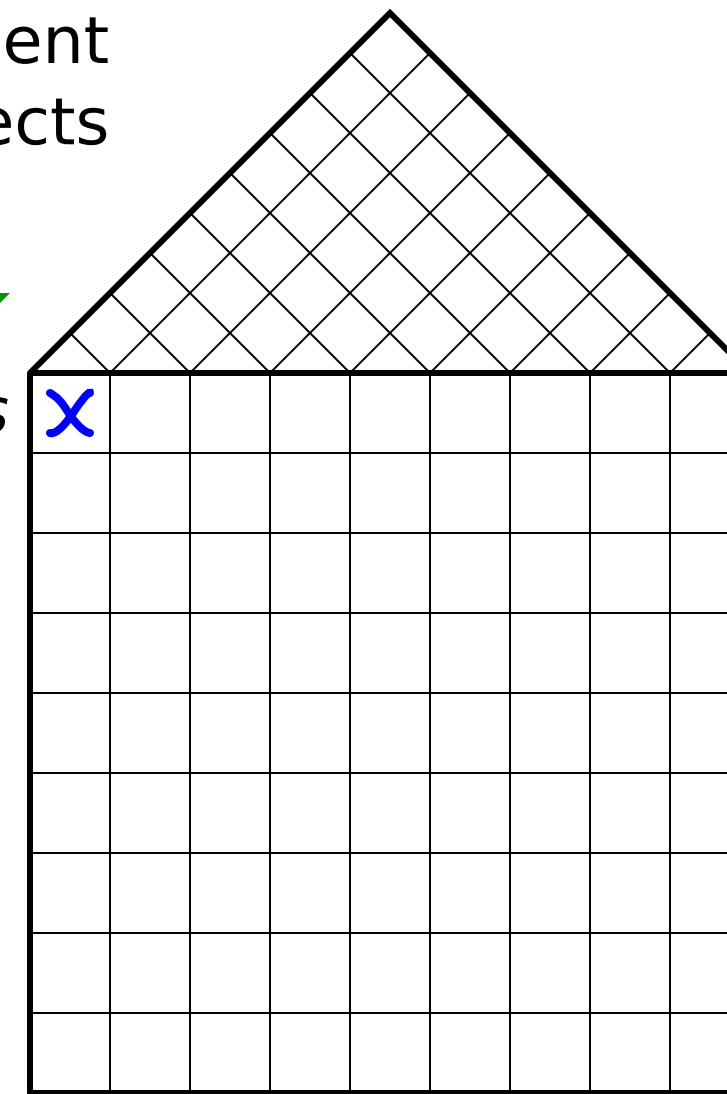

interaction  
between  
design aspects

SLiCAP

design  
aspects

*Function, performance,  
costs and environment*

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer


Performance requirements

(information processing capacity and quality):


Noise addition (temperature offset drift)

Static and dynamic signal handling capability

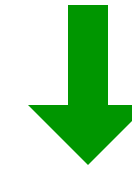Design of independent  
performance aspects



*Setting up specifications*

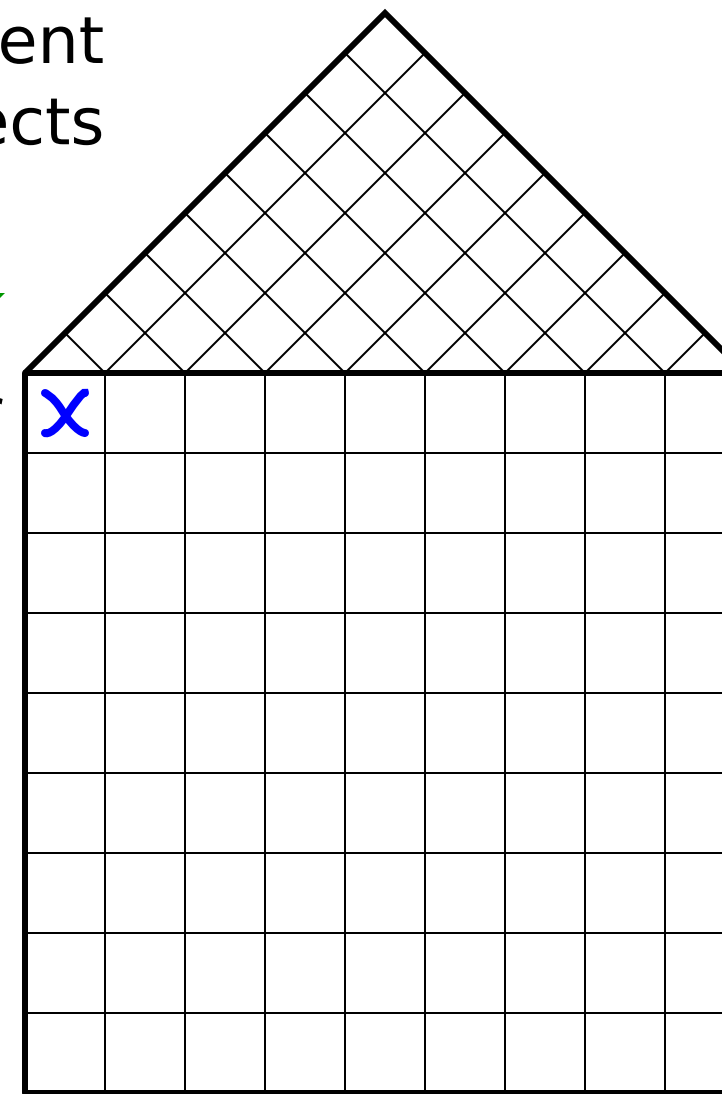

← interaction  
between  
design aspects

SLiCAP

*Function, performance,  
costs and environment*

← design  
aspects

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer

Performance requirements


(information processing capacity and quality):

Noise addition (temperature offset drift)



Static and dynamic signal handling capability

Inaccuracy (temperature gain drift)

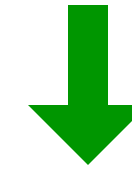Design of independent  
performance aspects




*Setting up specifications*

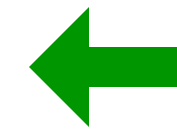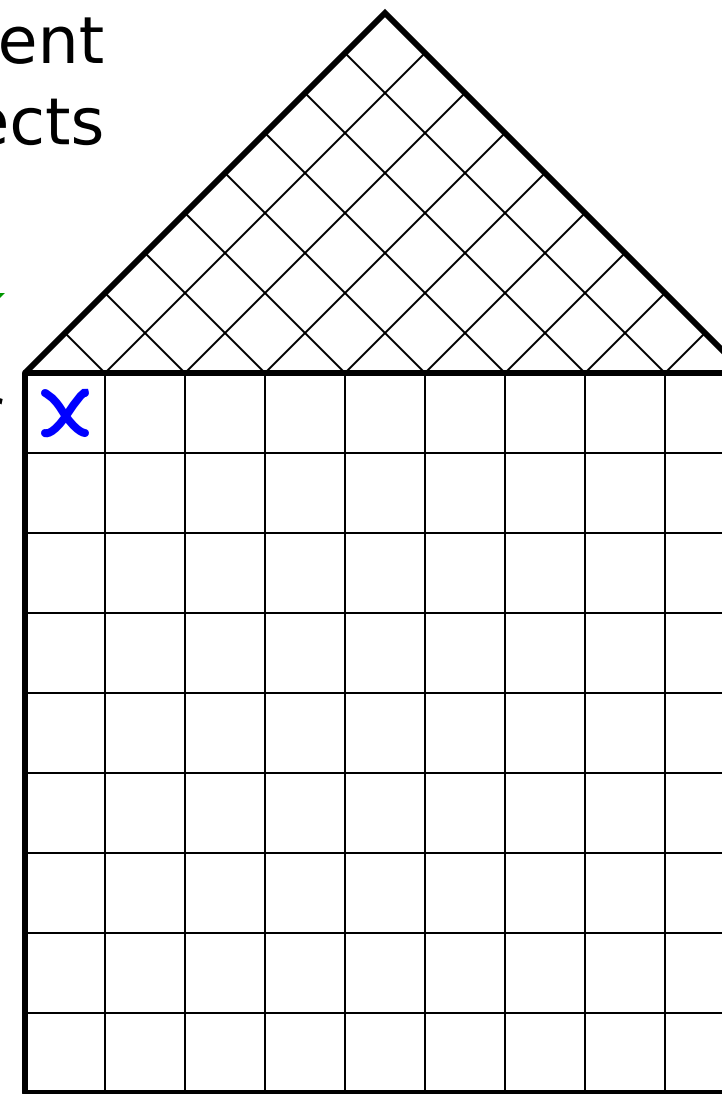

interaction  
between  
design aspects

SLiCAP

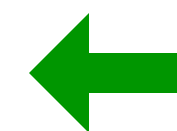*Function, performance,  
costs and environment*



design  
aspects

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer

Performance requirements

(information processing capacity and quality):


Noise addition (temperature offset drift)

Static and dynamic signal handling capability


Inaccuracy (temperature gain drift)

Frequency or time domain response

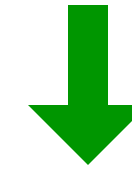Design of independent  
performance aspects



*Setting up specifications*

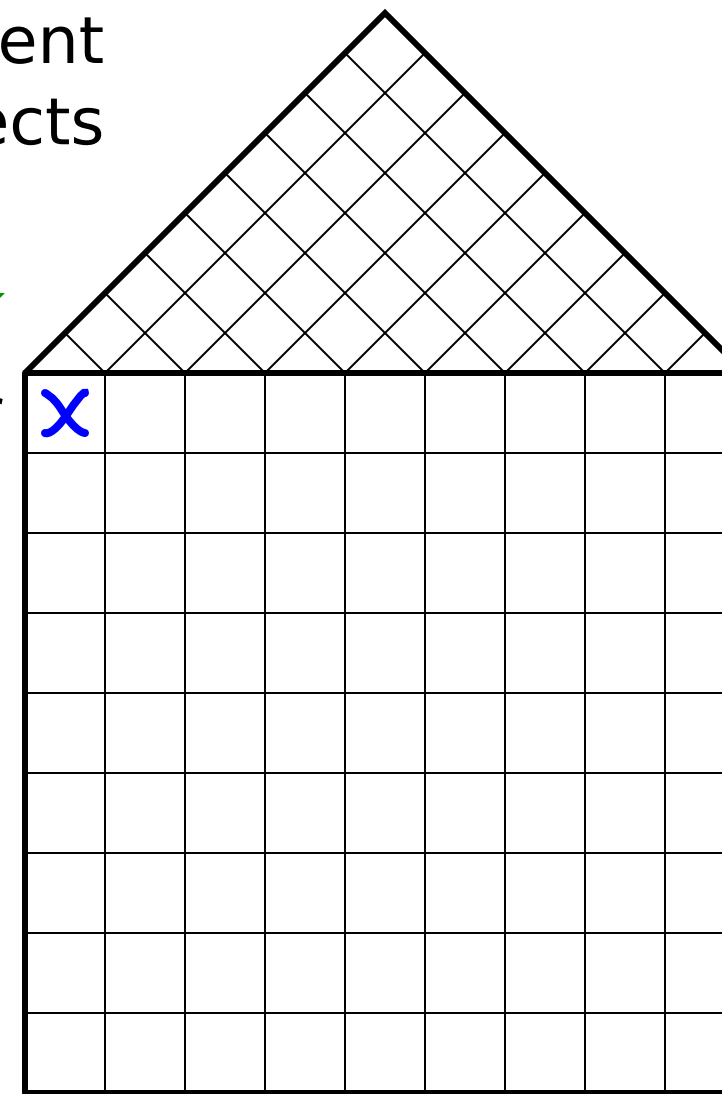

interaction  
between  
design aspects

SLiCAP

*Function, performance,  
costs and environment*

design  
aspects

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer

Performance requirements

(information processing capacity and quality):

Noise addition (temperature offset drift)


Static and dynamic signal handling capability

Inaccuracy (temperature gain drift)


Frequency or time domain response

Weak nonlinearity

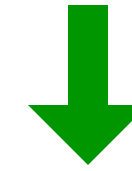Design of independent  
performance aspects



*Setting up specifications*

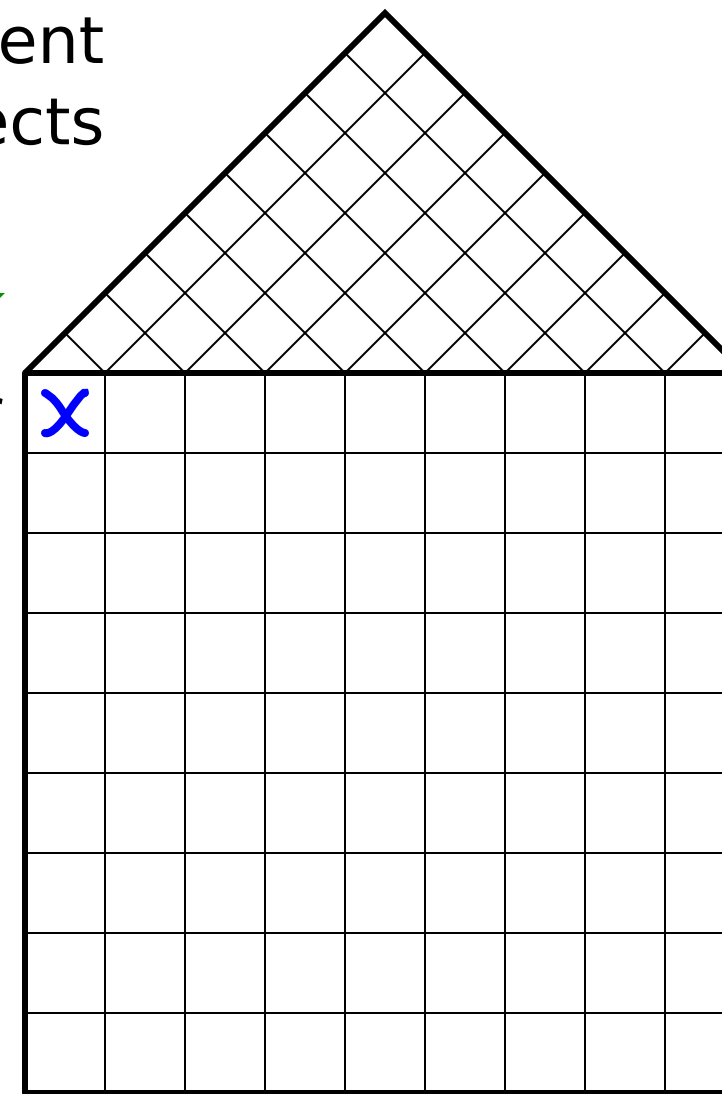

← interaction  
between  
design aspects

SLiCAP

*Function, performance,  
costs and environment*

← design  
aspects

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer

Performance requirements

(information processing capacity and quality):

Noise addition (temperature offset drift)

Static and dynamic signal handling capability

Inaccuracy (temperature gain drift)


Frequency or time domain response

Weak nonlinearity


Cost factors:

*Setting up specifications*

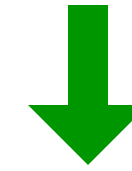
Design of independent  
performance aspects



interaction  
between  
design aspects

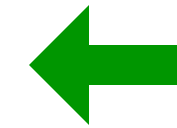


SLiCAP

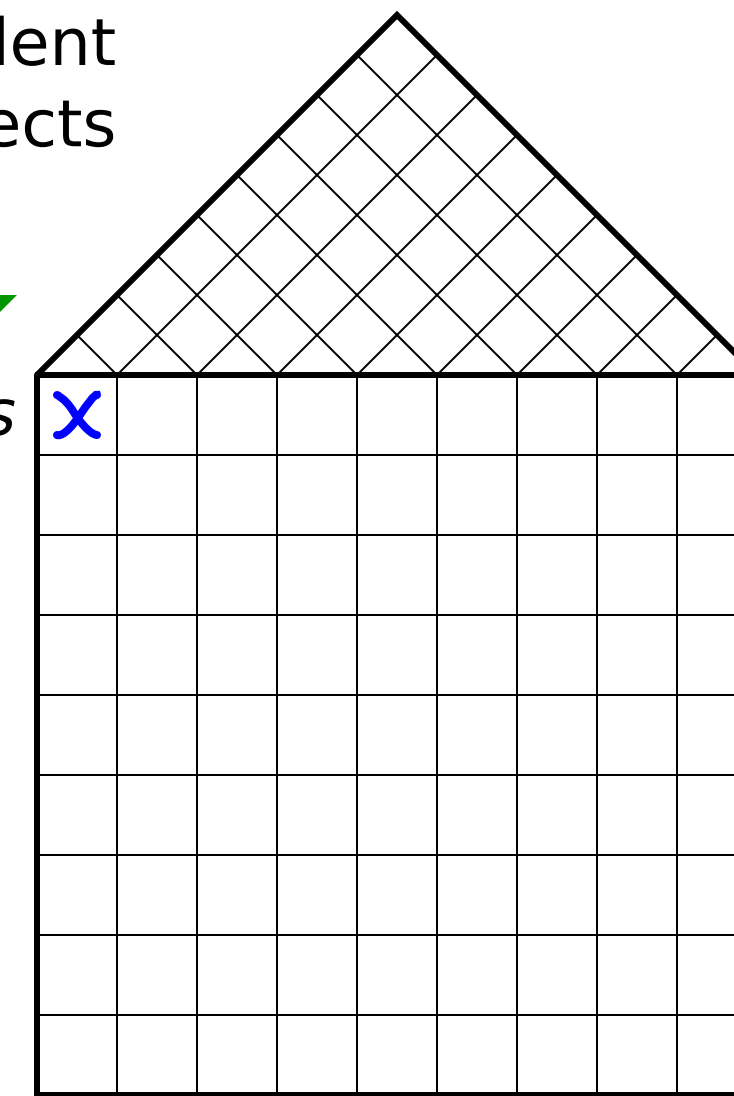

*Function, performance,  
costs and environment*

design  
aspects

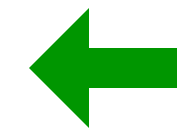

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer

Performance requirements

(information processing capacity and quality):

Noise addition (temperature offset drift)

Static and dynamic signal handling capability

Inaccuracy (temperature gain drift)


Frequency or time domain response

Weak nonlinearity


Cost factors:

Supply voltage

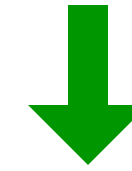Design of independent  
performance aspects



*Setting up specifications*

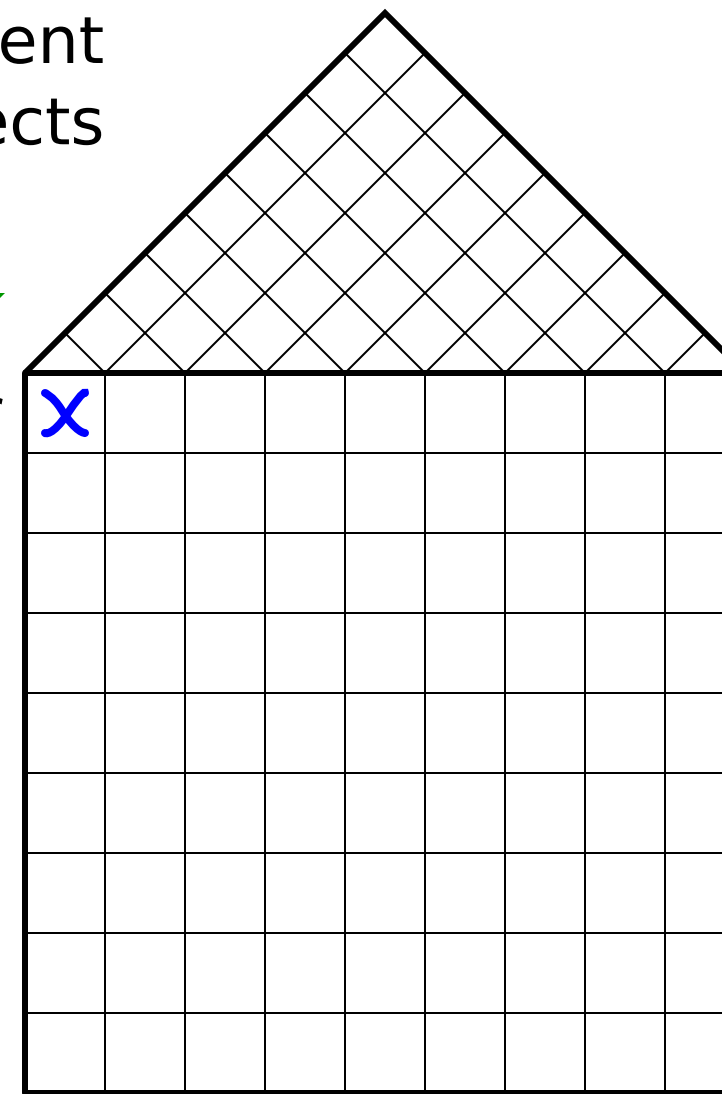

← interaction  
between  
design aspects

SLiCAP

*Function, performance,  
costs and environment*

← design  
aspects



## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer

Performance requirements

(information processing capacity and quality):

Noise addition (temperature offset drift)

Static and dynamic signal handling capability

Inaccuracy (temperature gain drift)

Frequency or time domain response


Weak nonlinearity

Cost factors:


Supply voltage

Current consumption

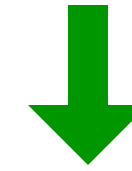Design of independent  
performance aspects



*Setting up specifications*

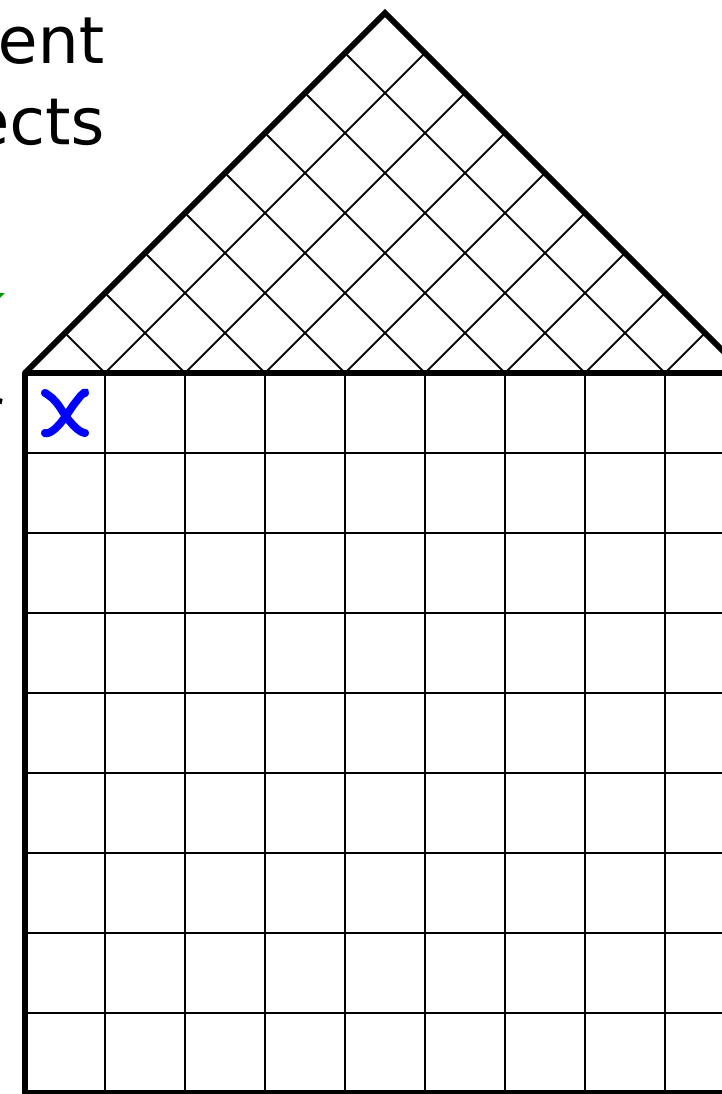

interaction  
between  
design aspects

SLiCAP

*Function, performance,  
costs and environment*

design  
aspects

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer

Performance requirements

(information processing capacity and quality):

Noise addition (temperature offset drift)

Static and dynamic signal handling capability

Inaccuracy (temperature gain drift)

Frequency or time domain response

Weak nonlinearity


Cost factors:

Supply voltage


Current consumption

Dimensions

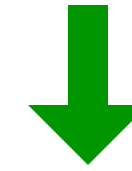Design of independent  
performance aspects



*Setting up specifications*

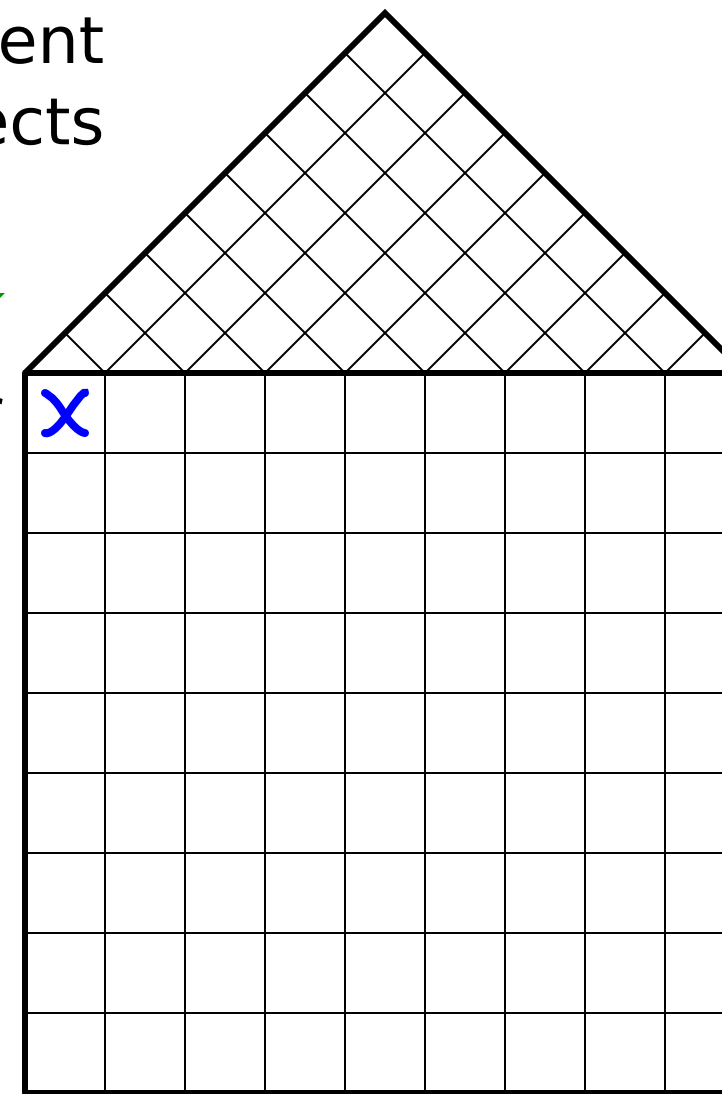

← interaction  
between  
design aspects

SLiCAP

*Function, performance,  
costs and environment*

← design  
aspects

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer

Performance requirements

(information processing capacity and quality):

Noise addition (temperature offset drift)

Static and dynamic signal handling capability

Inaccuracy (temperature gain drift)

Frequency or time domain response

Weak nonlinearity

Cost factors:


Supply voltage

Current consumption


Dimensions

Operating conditions:

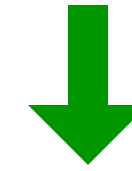Design of independent performance aspects



*Setting up specifications*

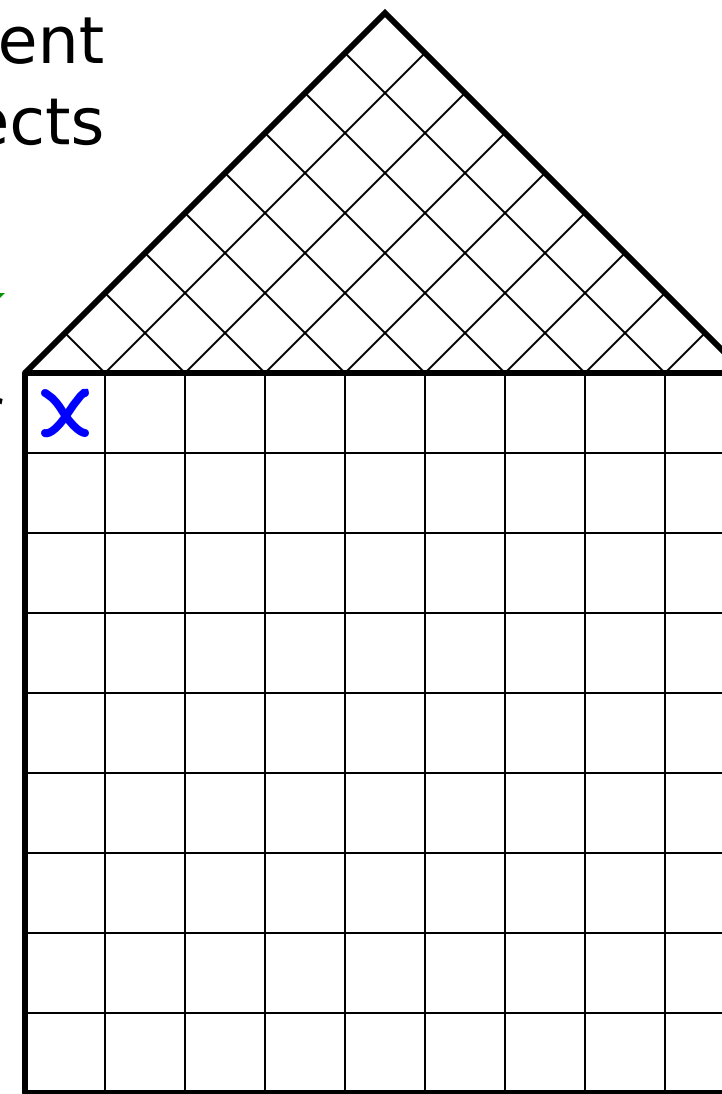

interaction between design aspects

SLiCAP

*Function, performance, costs and environment*

design aspects

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer

Performance requirements

(information processing capacity and quality):

Noise addition (temperature offset drift)

Static and dynamic signal handling capability

Inaccuracy (temperature gain drift)

Frequency or time domain response

Weak nonlinearity

Cost factors:

Supply voltage


Current consumption

Dimensions


Operating conditions:

Temperature range

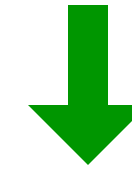Design of independent  
performance aspects



*Setting up specifications*

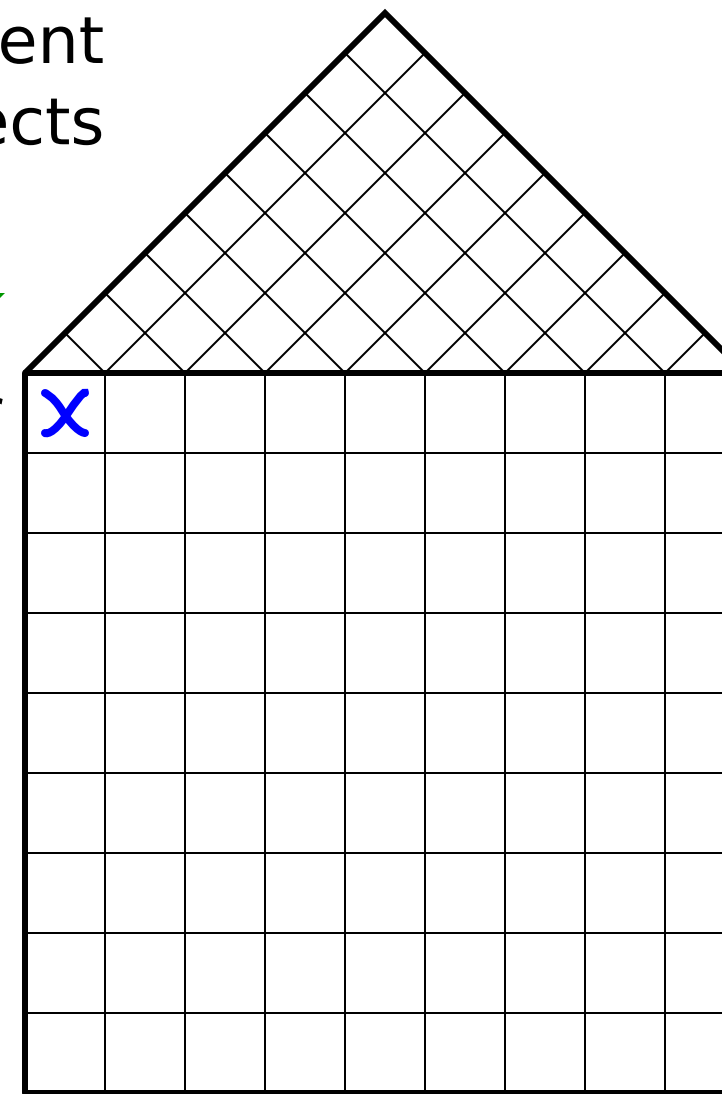

interaction  
between  
design aspects

SLiCAP

*Function, performance,  
costs and environment*

design  
aspects

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer

Performance requirements

(information processing capacity and quality):

Noise addition (temperature offset drift)

Static and dynamic signal handling capability

Inaccuracy (temperature gain drift)

Frequency or time domain response

Weak nonlinearity

Cost factors:

Supply voltage

Current consumption


Dimensions

Operating conditions:


Temperature range

EMI, ESD

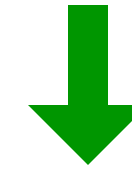Design of independent  
performance aspects



*Setting up specifications*

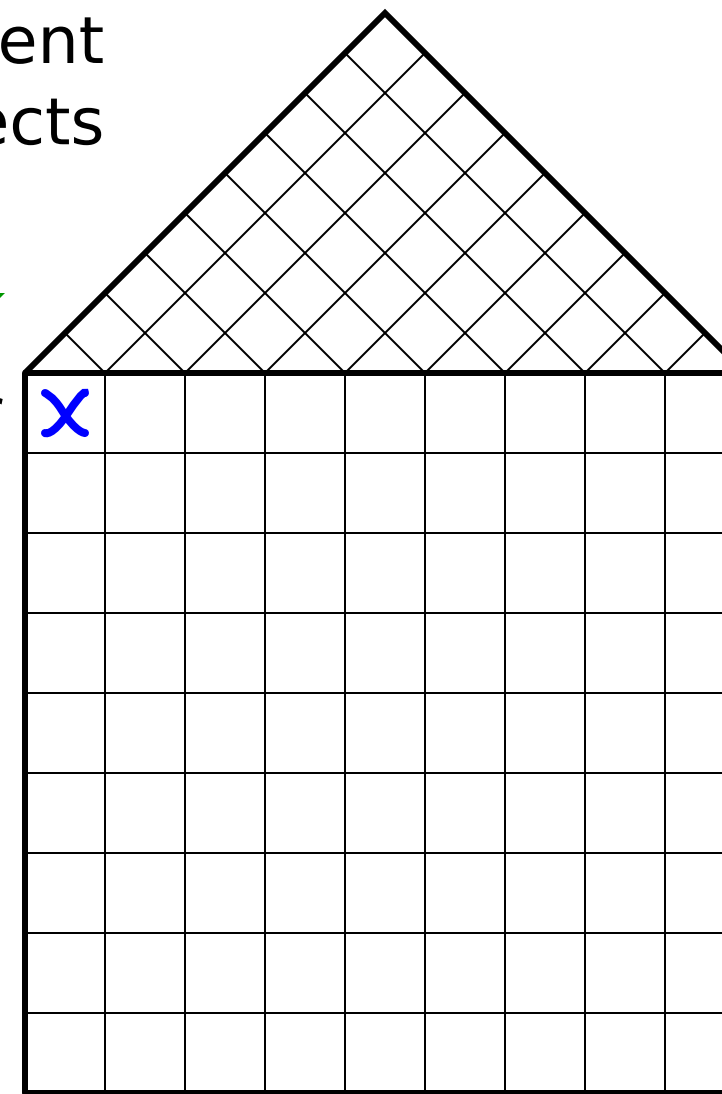

← interaction  
between  
design aspects

SLiCAP

*Function, performance,  
costs and environment*

← design  
aspects

## Design of the active antenna:

From the application description derive:

Functional requirements

Port impedances

Source-to-load transfer

Performance requirements

(information processing capacity and quality):

Noise addition (temperature offset drift)

Static and dynamic signal handling capability

Inaccuracy (temperature gain drift)

Frequency or time domain response

Weak nonlinearity

Cost factors:

Supply voltage

Current consumption


Dimensions

Operating conditions:



Temperature range

EMI, ESD

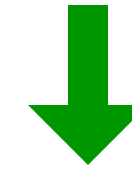Design of independent  
performance aspects




*Setting up specifications*

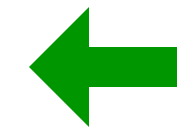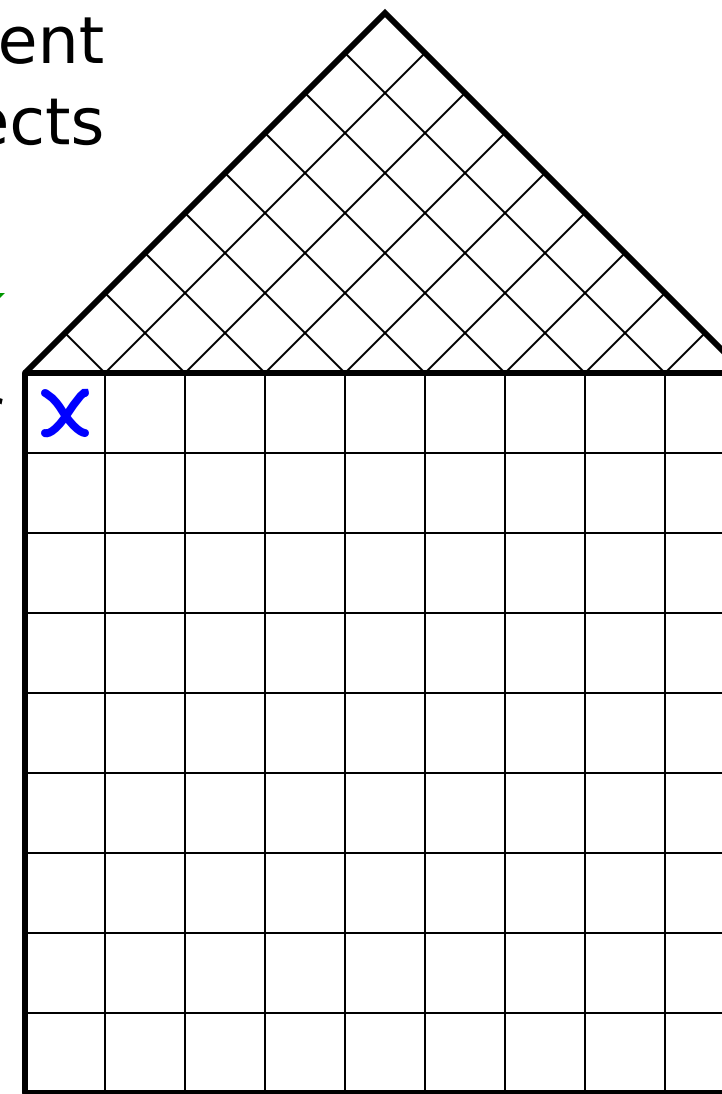


interaction  
between  
design aspects


SLiCAP

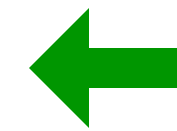*Function, performance,  
costs and environment*




design  
aspects

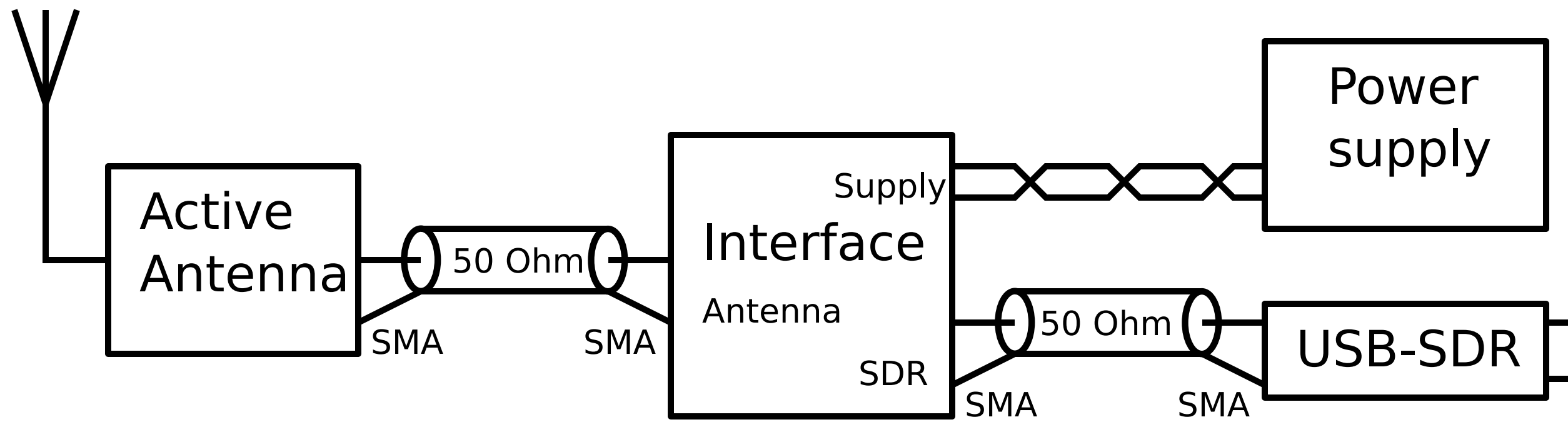

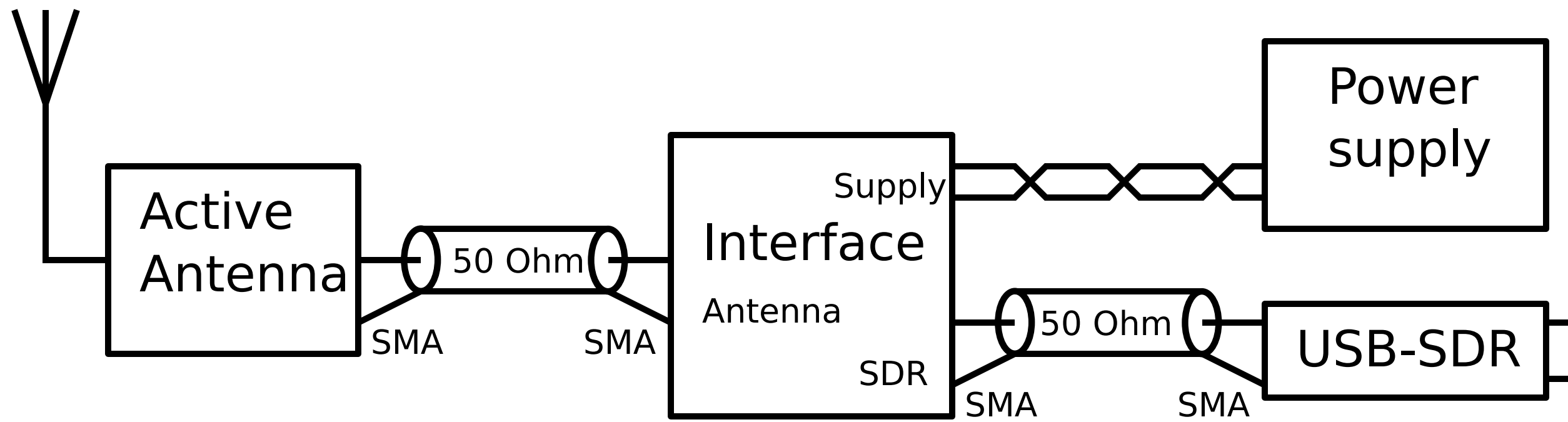


## Performance



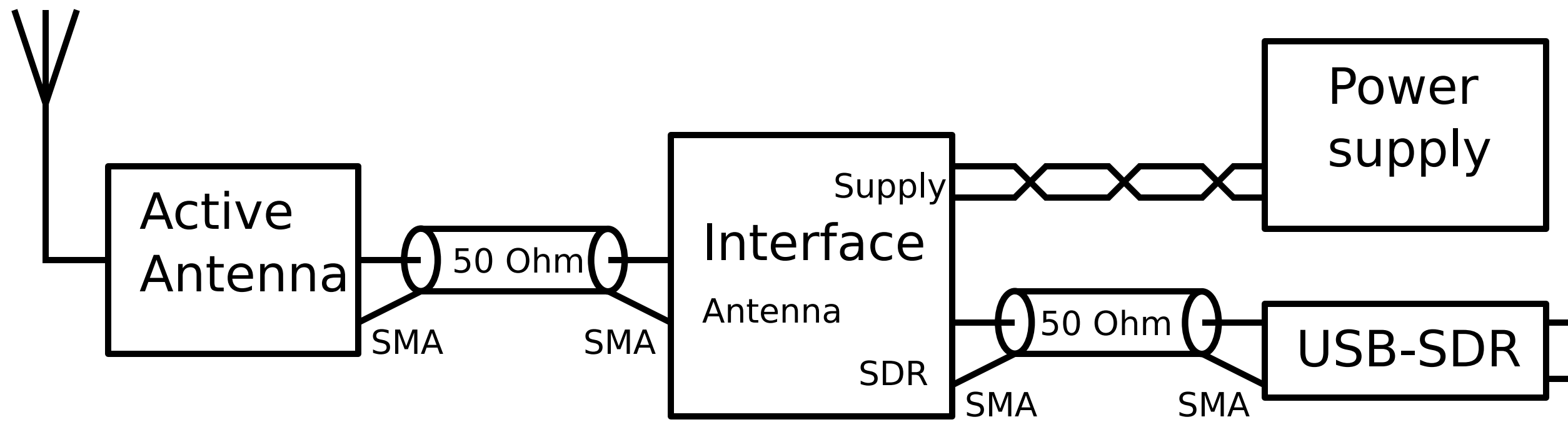

## Performance


Maximum RMS input signal

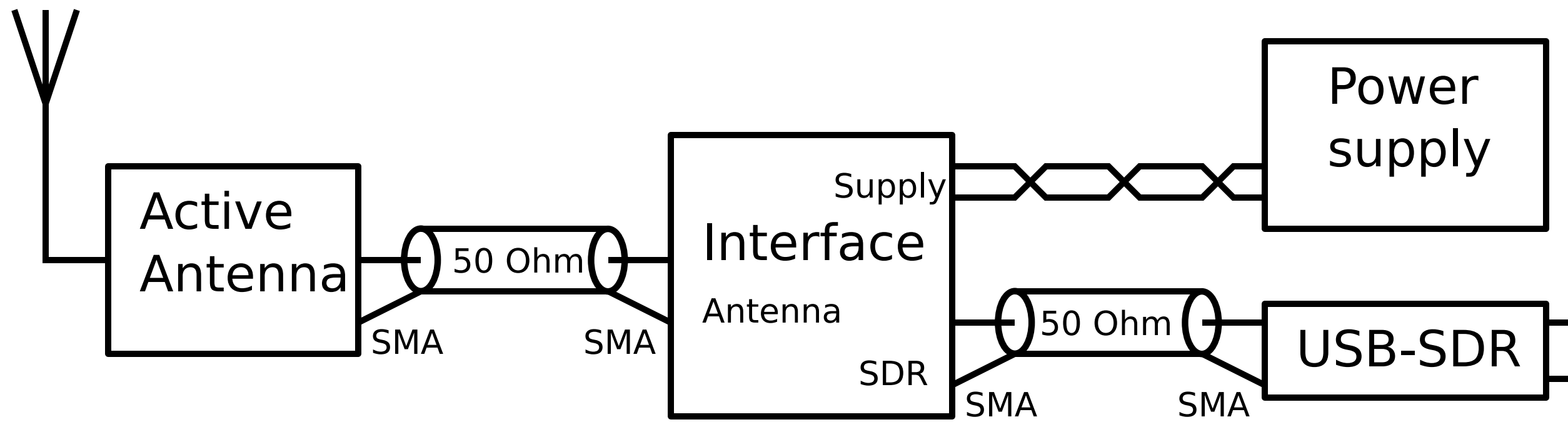

## Performance

Maximum RMS input signal

Maximum RMS output voltage across 50 Ohm

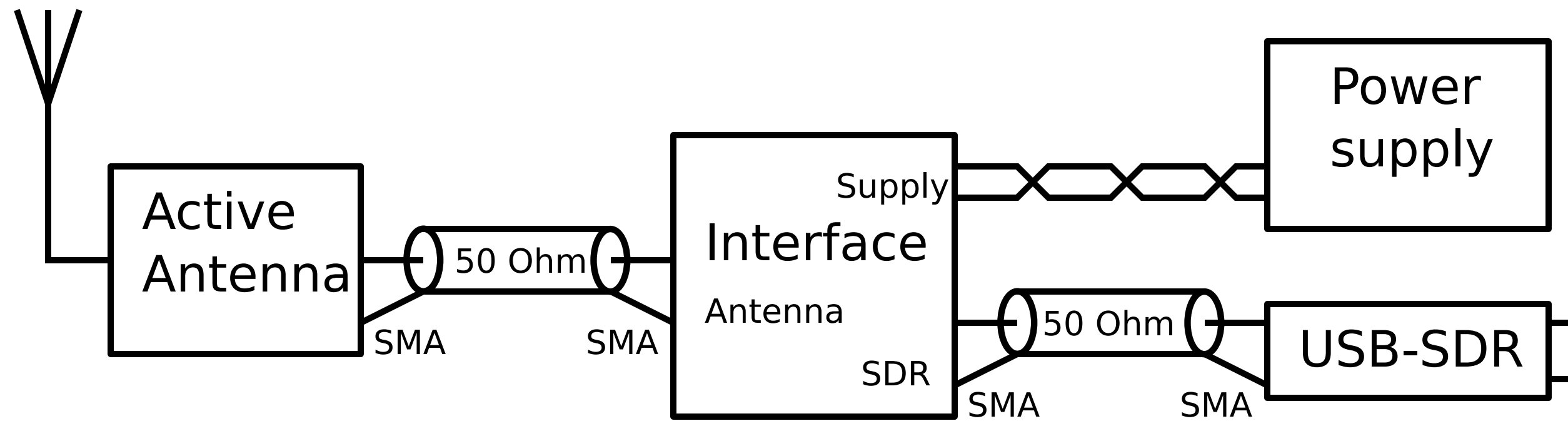


## Performance

Maximum RMS input signal

Maximum RMS output voltage across 50 Ohm

Antenna referred noise

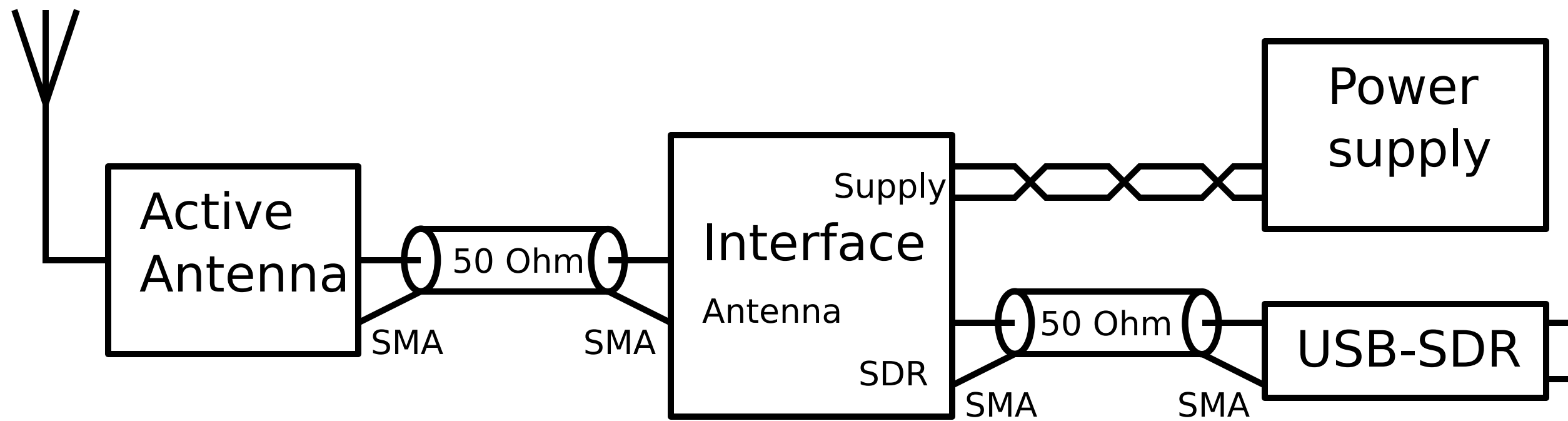


## Performance

Maximum RMS input signal

Maximum RMS output voltage across 50 Ohm

Antenna referred noise

Output impedance

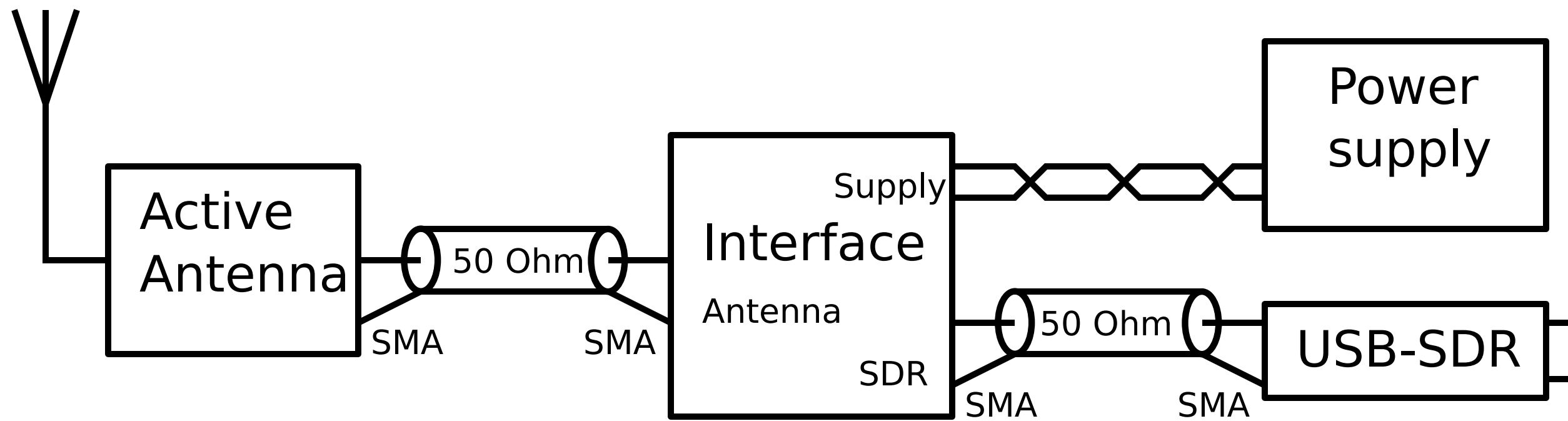

## Performance


Maximum RMS input signal

Maximum RMS output voltage across 50 Ohm

Antenna referred noise

Output impedance

Frequency range of interest

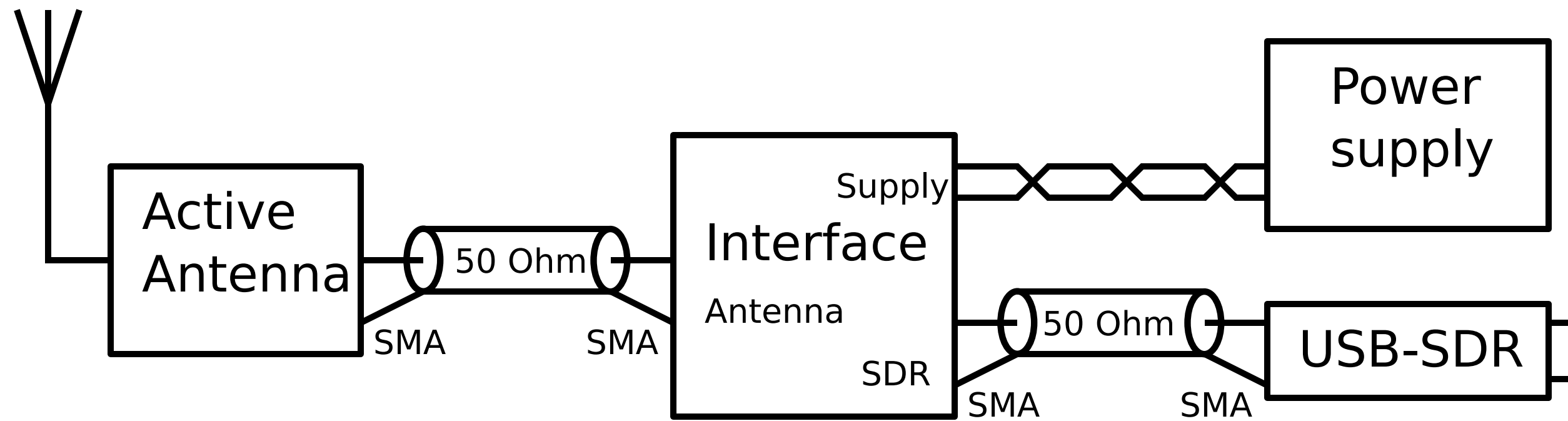

## Performance

Maximum RMS input signal


Maximum RMS output voltage across 50 Ohm

Antenna referred noise

Output impedance

Frequency range of interest

Response type

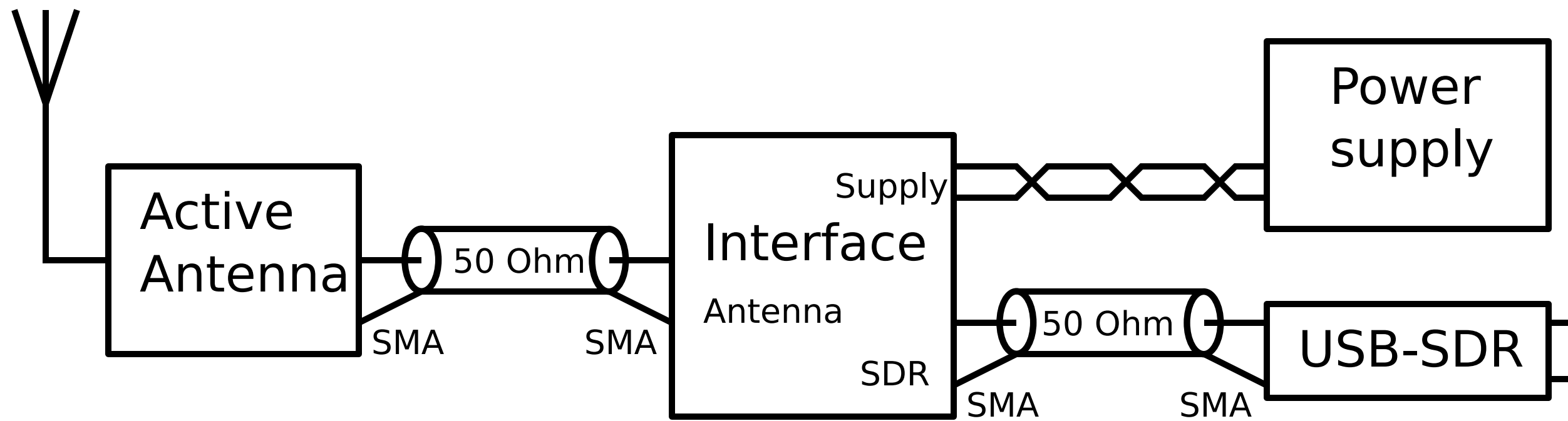

## Performance

Maximum RMS input signal

Maximum RMS output voltage across 50 Ohm


Antenna referred noise

Output impedance

Frequency range of interest

Response type

IMD

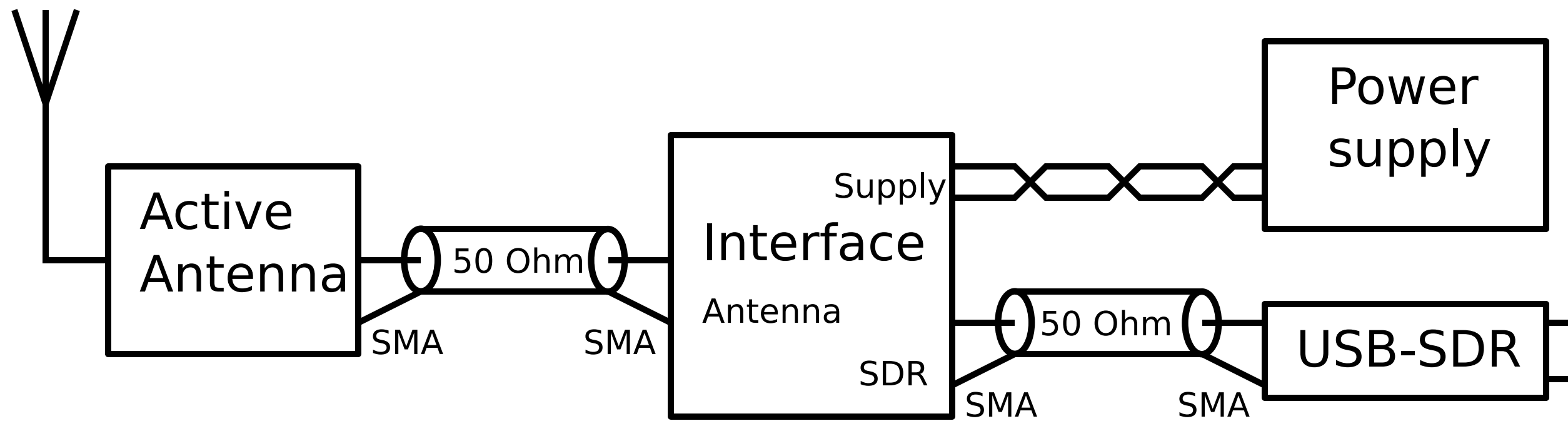

## Performance

Maximum RMS input signal

Maximum RMS output voltage across 50 Ohm

Antenna referred noise

Output impedance


Frequency range of interest

Response type

IMD

## Costs



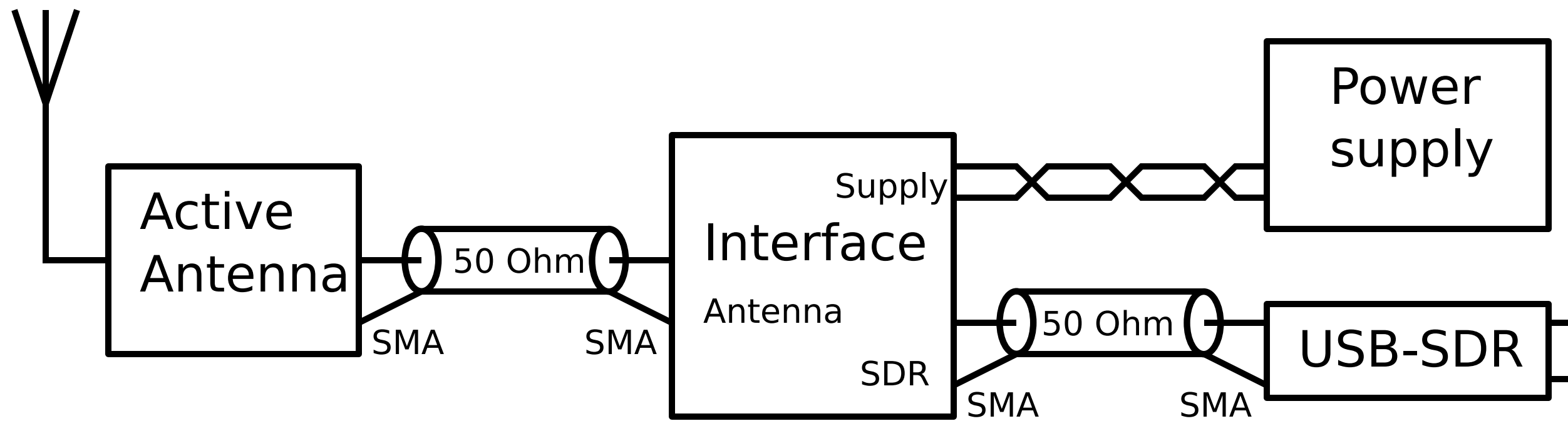


## Performance

- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD

## Costs

- Antenne length

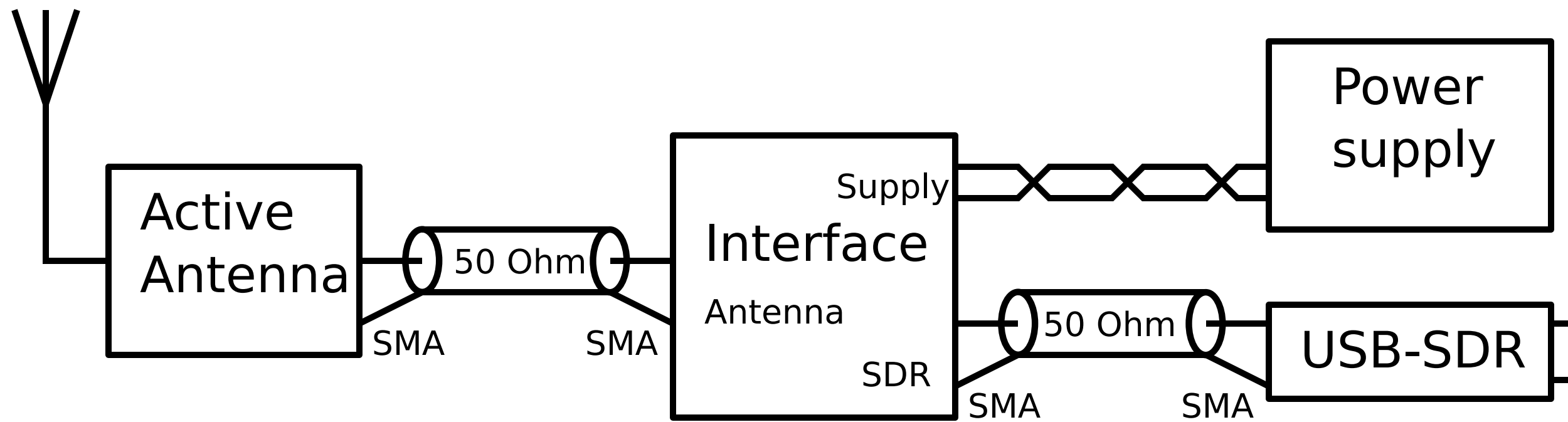


## Performance

- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD

## Costs

- Antenne length
- Supply voltage

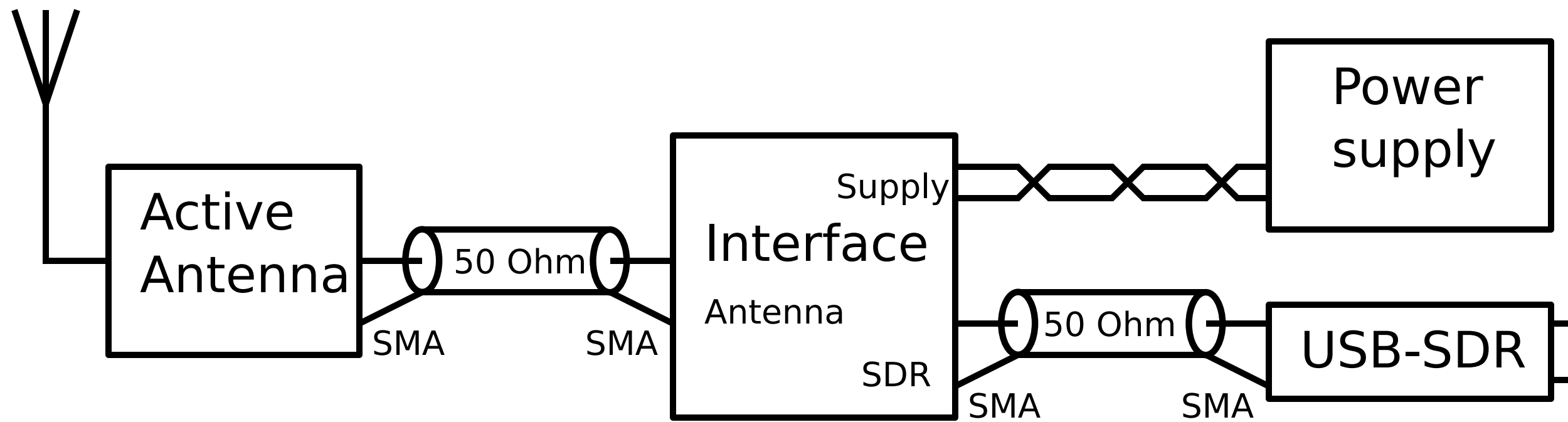


## Performance

- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD
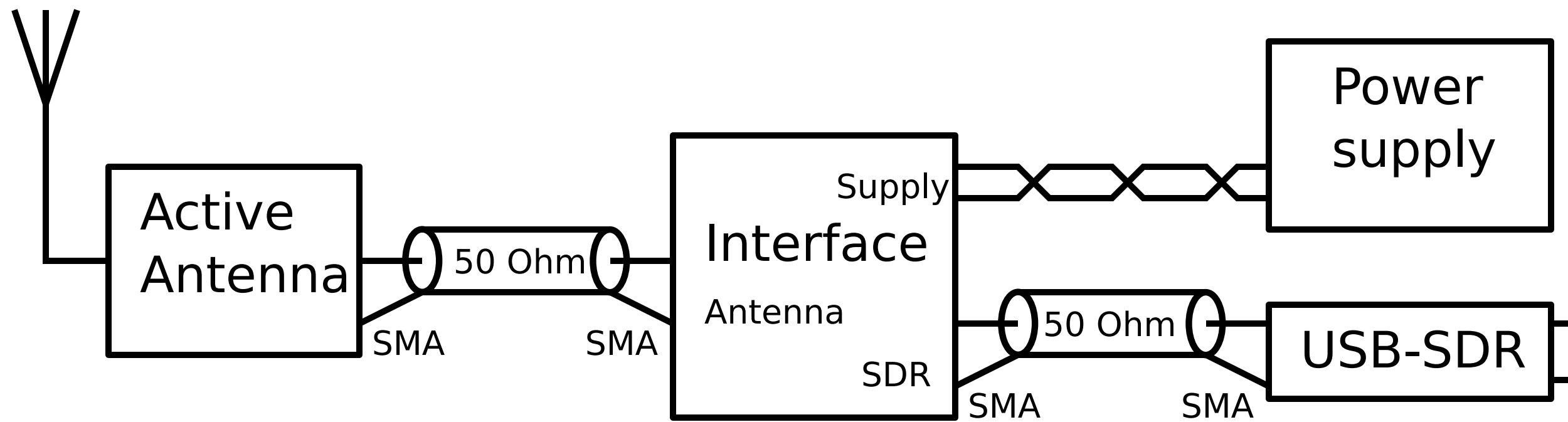
## Costs

- Antenne length
- Supply voltage
- Power consumption




## Performance

- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD

## Costs

- Antenne length
- Supply voltage
- Power consumption

## Dimensions

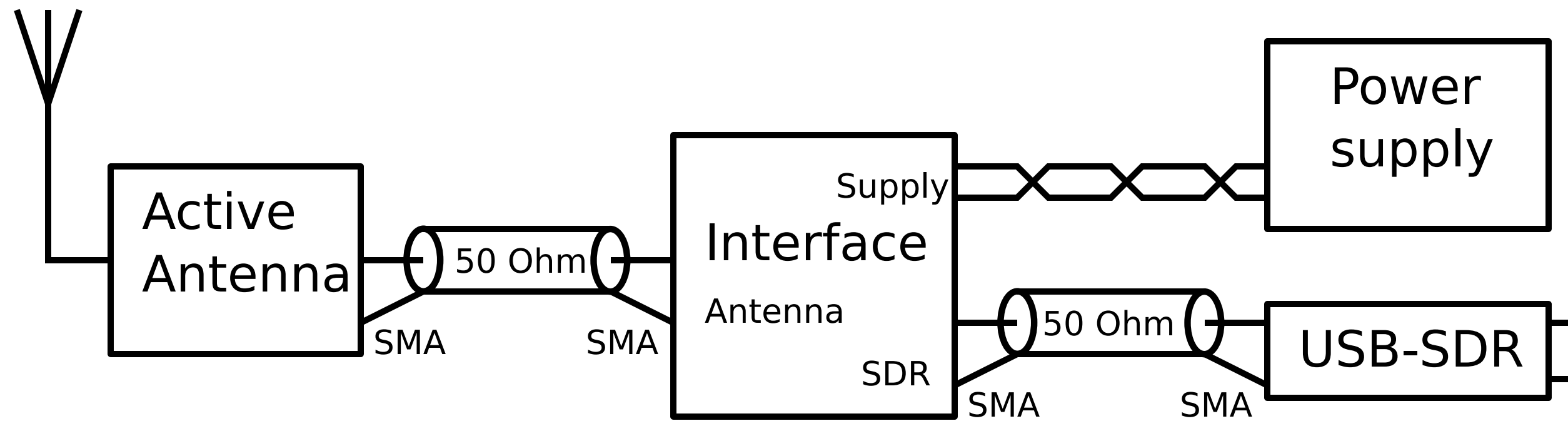


## Performance

- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD

## Costs

- Antenne length
- Supply voltage
- Power consumption
- Dimensions

## Technology

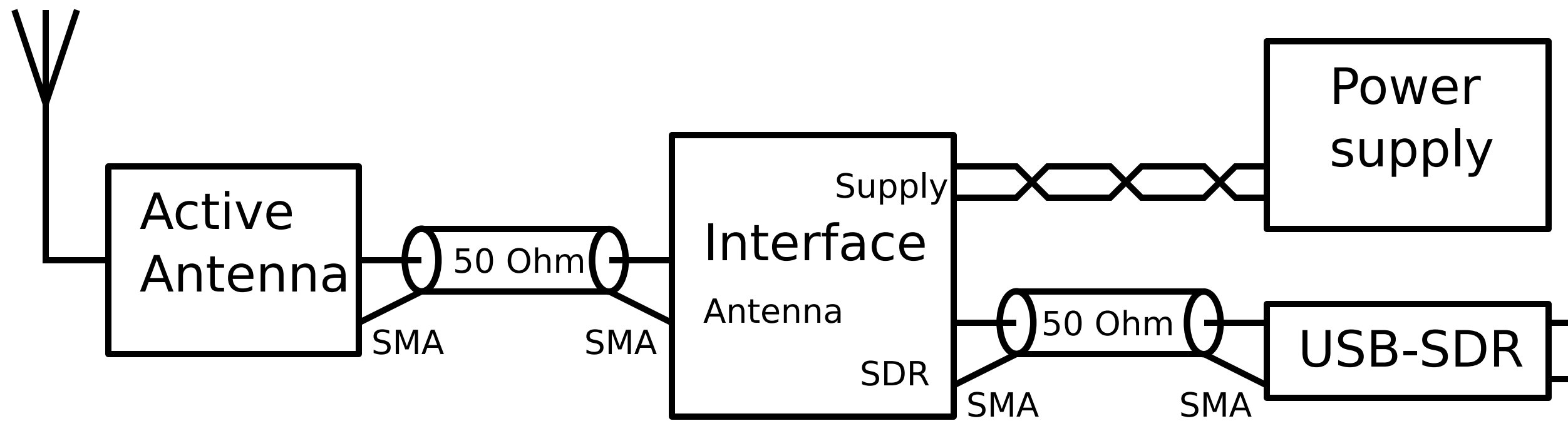


## Performance

- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD
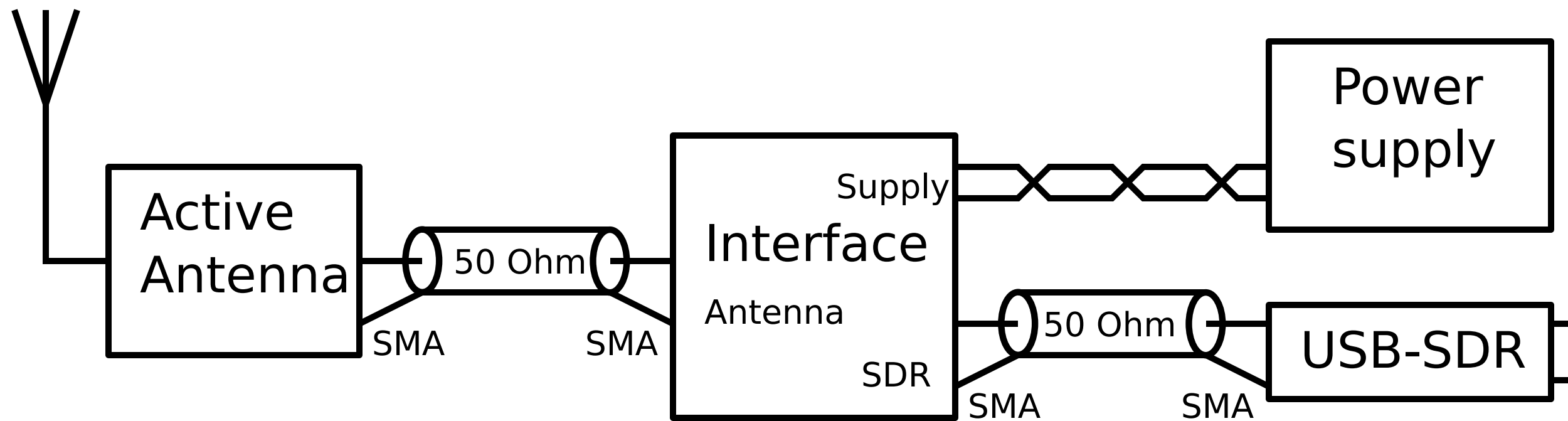
## Costs

- Antenne length
- Supply voltage
- Power consumption
- Dimensions
- Technology
- External components




## Performance

- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD
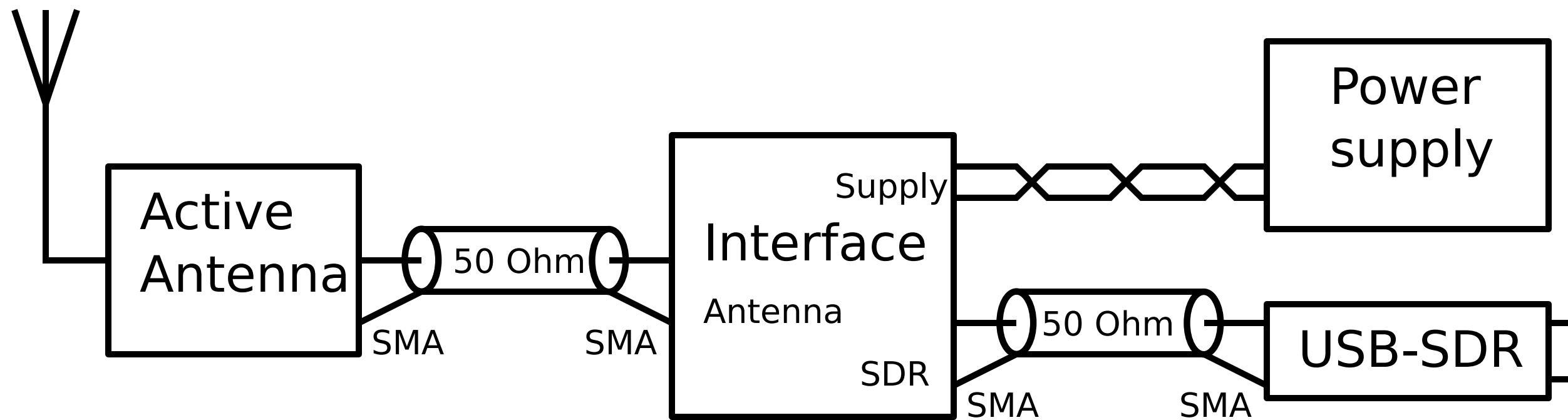
## Costs

- Antenne length
- Supply voltage
- Power consumption
- Dimensions
- Technology
- External components
- Package



## Performance


- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD

## Costs

- Antenne length
- Supply voltage
- Power consumption
- Dimensions
- Technology
- External components
- Package

## Operating conditions



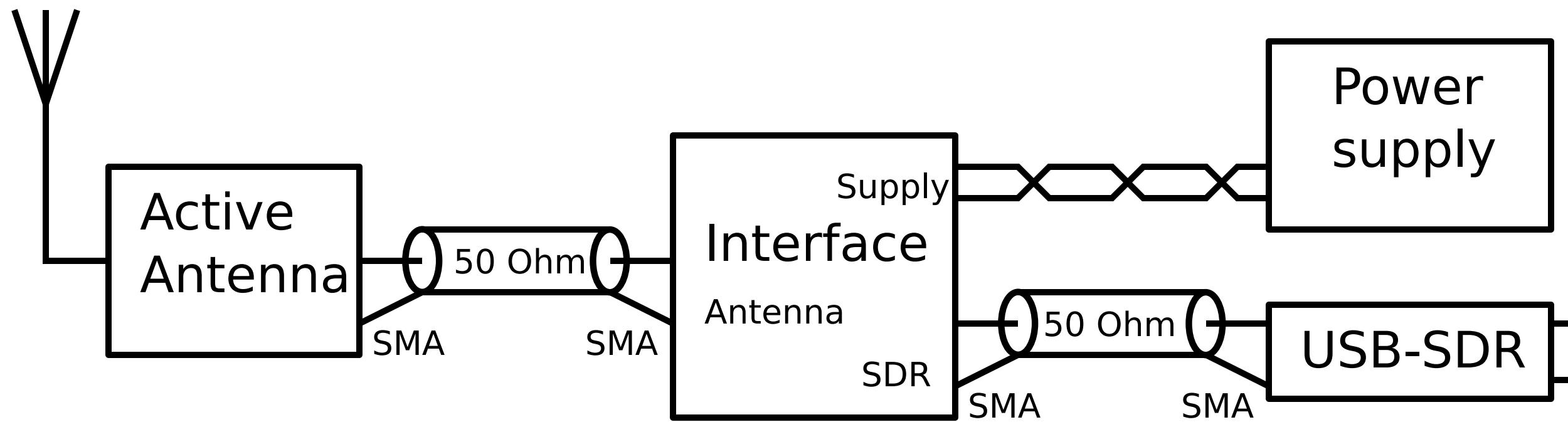

### Performance


- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD

### Costs

- Antenne length
- Supply voltage
- Power consumption
- Dimensions
- Technology
- External components
- Package

### Operating conditions

- Temperature range

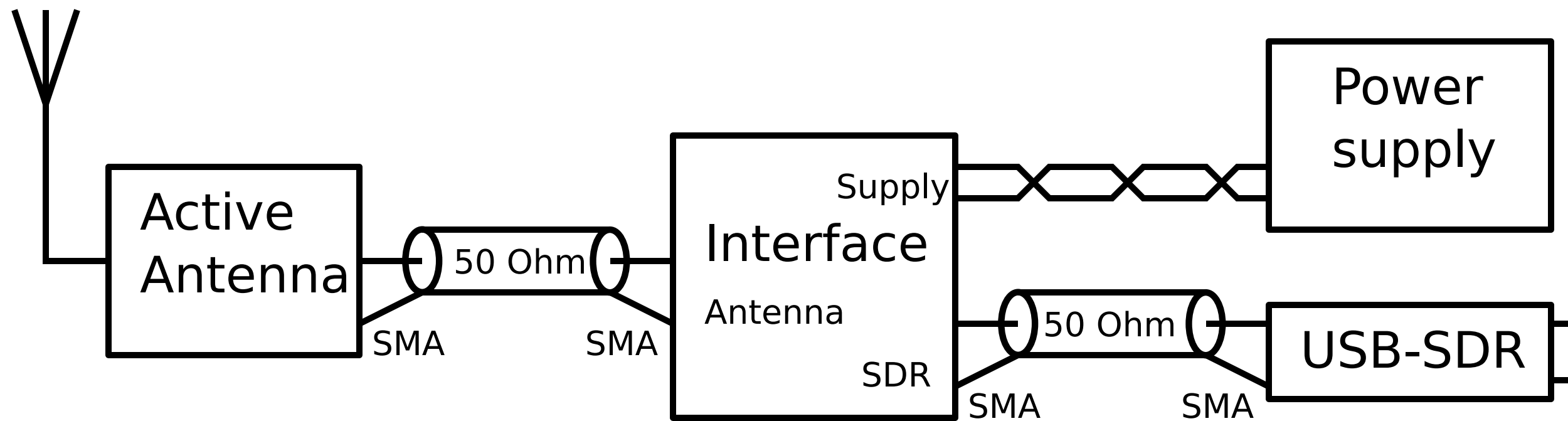

## Performance


- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD

## Costs

- Antenne length
- Supply voltage
- Power consumption
- Dimensions
- Technology
- External components
- Package

## Operating conditions

- Temperature range
- EMI

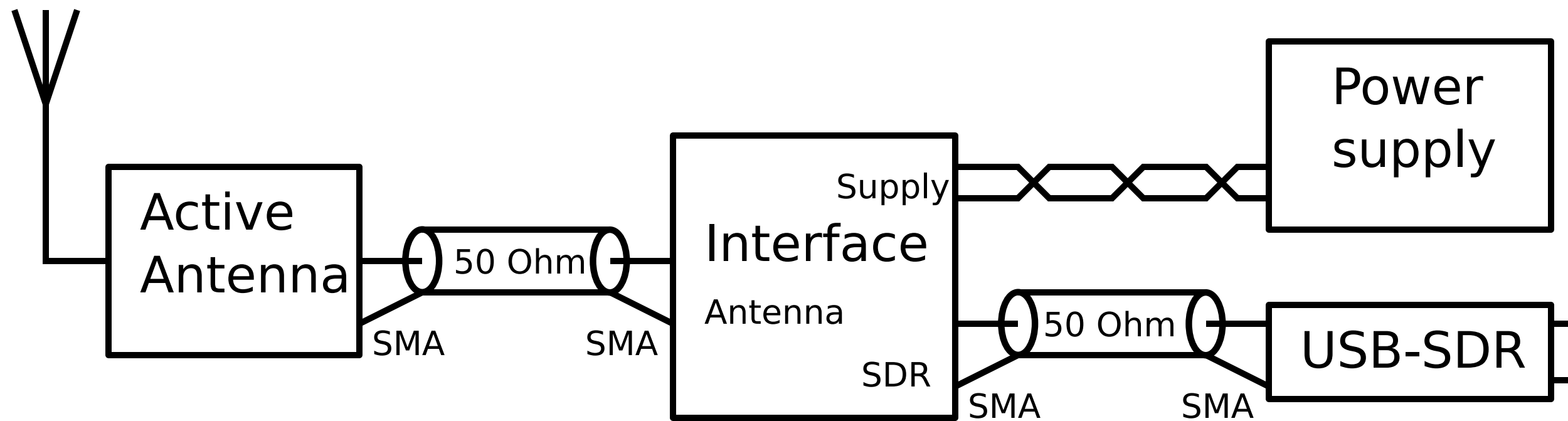

## Performance


- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD

## Costs

- Antenne length
- Supply voltage
- Power consumption
- Dimensions
- Technology
- External components
- Package

## Operating conditions

- Temperature range
- EMI
- ESD

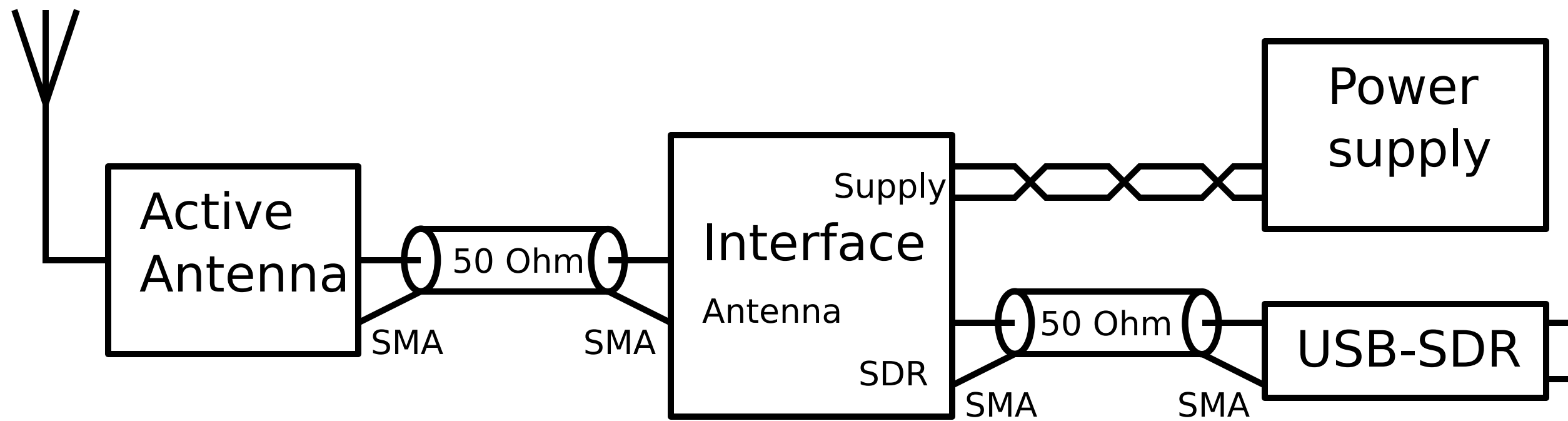

## Performance

- Maximum RMS input signal
- Maximum RMS output voltage across 50 Ohm
- Antenna referred noise
- Output impedance
- Frequency range of interest
- Response type
- IMD

## Costs

- Antenne length
- Supply voltage
- Power consumption
- Dimensions
- Technology
- External components
- Package

## Operating conditions

- Temperature range
- EMI
- ESD


# **Structured Electronic Design**

Step 2



Design of the amplifier type

*Anton J.M. Montagne*

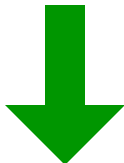Design of independent performance aspects




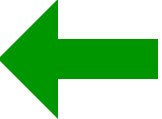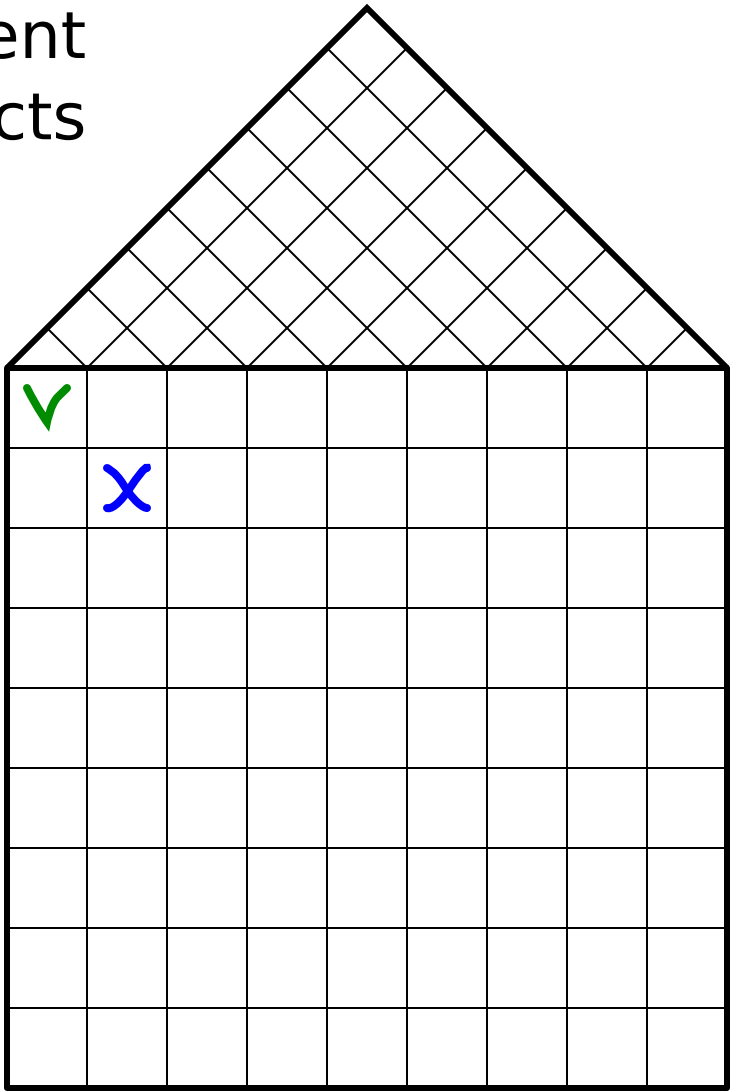Setting up specifications  
Design of amplifier type: A, B, C, D



interaction between design aspects

SLiCAP  
SLiCAP

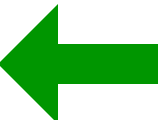

design aspects


Function, performance,  
costs and environment  
Feedback configuration

**Negative feedback amplifiers generally outperform non-feedback amplifiers**

Design of independent performance aspects

interaction between design aspects

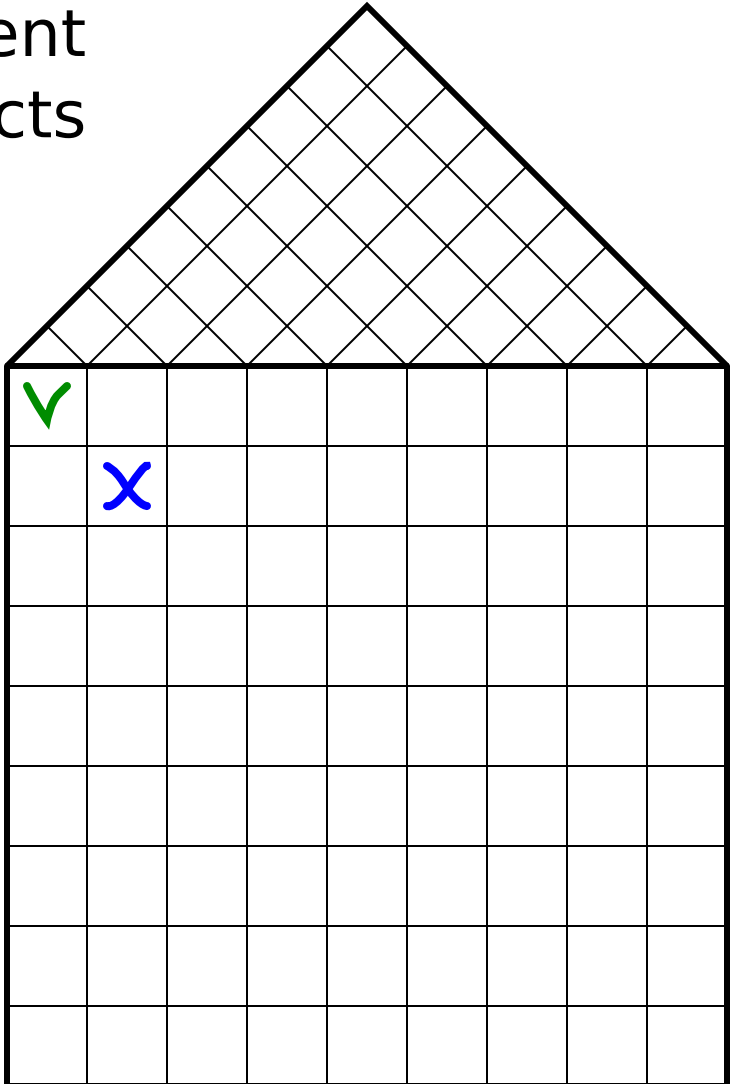Setting up specifications  
Design of amplifier type: A, B, C, D



SLiCAP  
SLiCAP

Function, performance,  
costs and environment  
Feedback configuration


design aspects

**Negative feedback amplifiers generally outperform non-feedback amplifiers**

Design of independent performance aspects

interaction between design aspects

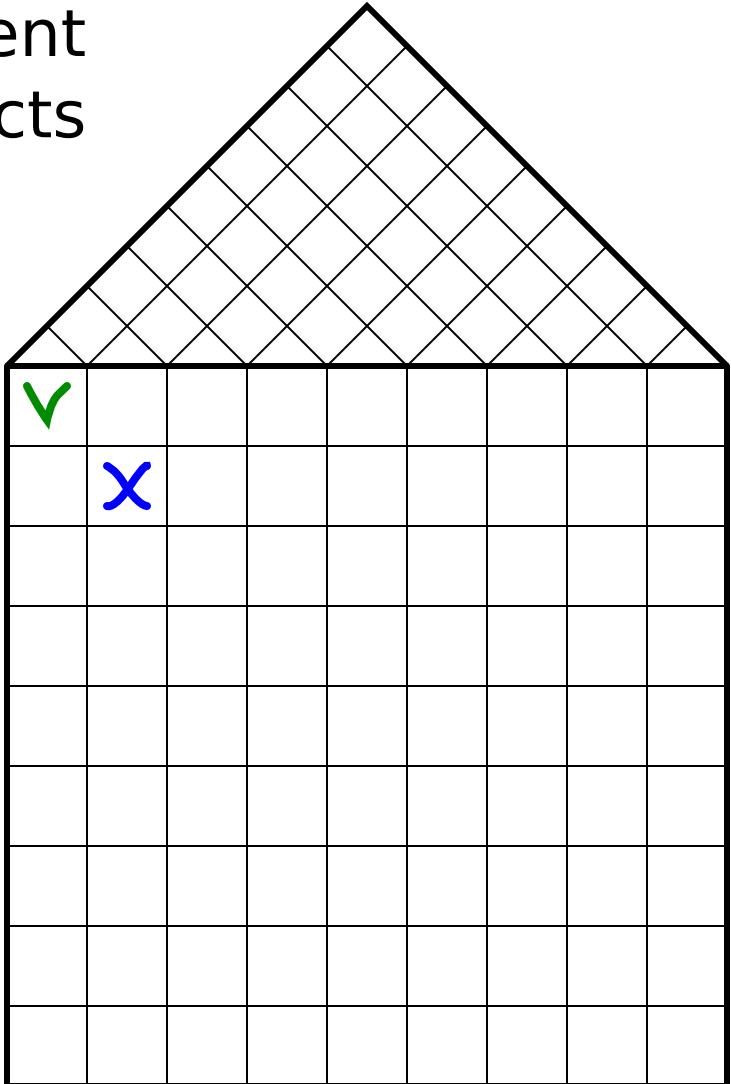Setting up specifications  
 Design of amplifier type: A, B, C, D



SLiCAP  
 SLiCAP

Negative feedback can be applied if:

Function, performance,  
 costs and environment  
 Feedback configuration

design aspects




**Negative feedback amplifiers generally outperform non-feedback amplifiers**

Design of independent performance aspects

interaction between design aspects

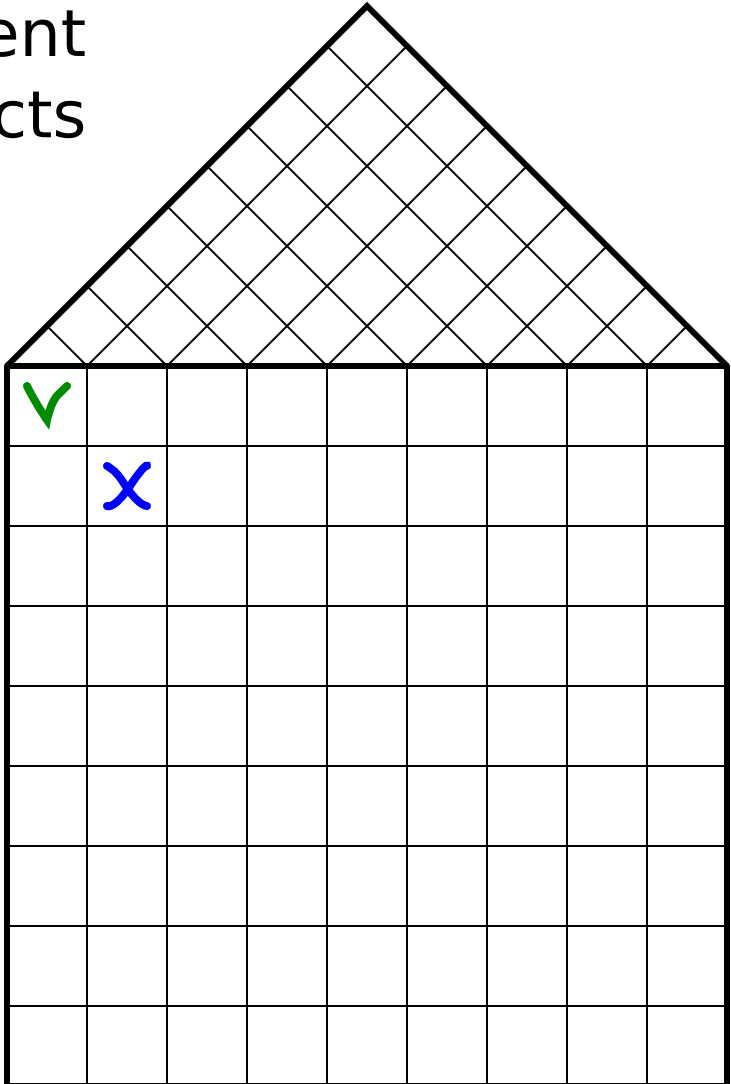Setting up specifications  
 Design of amplifier type: A, B, C, D



SLiCAP  
 SLiCAP

Negative feedback can be applied if:

Circuit dimensions are much smaller than the wavelength of the highest frequency of interest

Function, performance, costs and environment  
 Feedback configuration


design aspects

**Negative feedback amplifiers generally outperform non-feedback amplifiers**

Design of independent performance aspects

interaction between design aspects

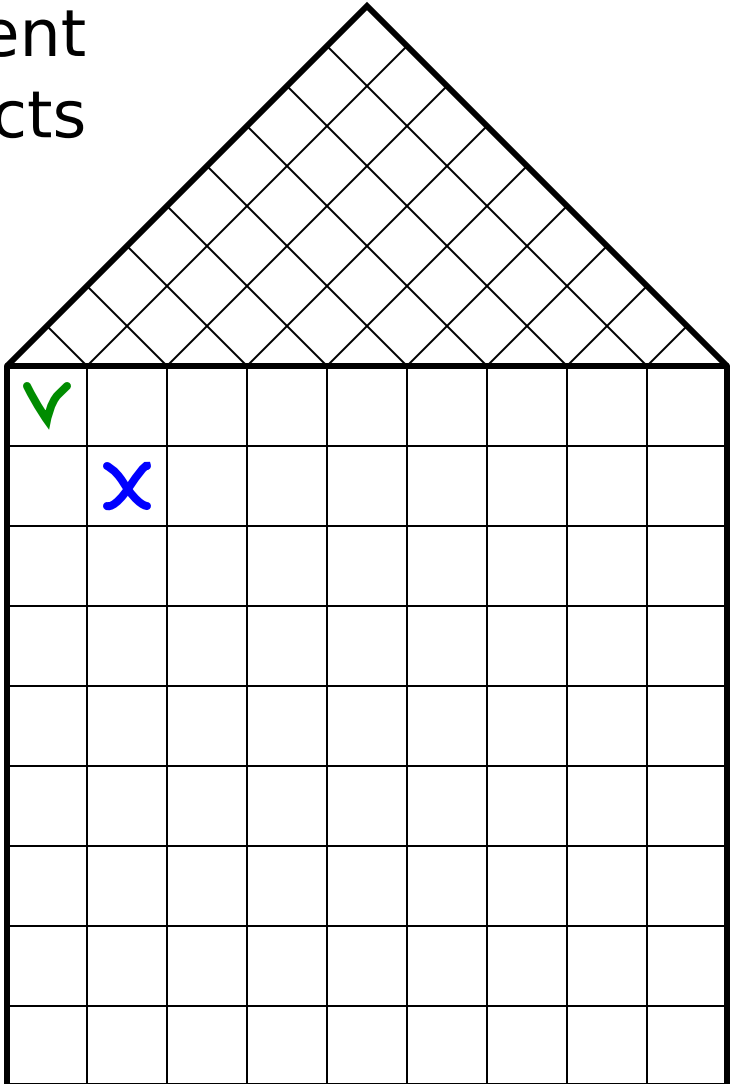Setting up specifications  
Design of amplifier type: A, B, C, D



Negative feedback can be applied if:

Circuit dimensions are much smaller than the wavelength of the highest frequency of interest

Process cut-off frequency is much larger than the highest frequency of interest

Function, performance, costs and environment  
Feedback configuration


design aspects

**Negative feedback amplifiers generally outperform non-feedback amplifiers**

Design of independent performance aspects

interaction between design aspects

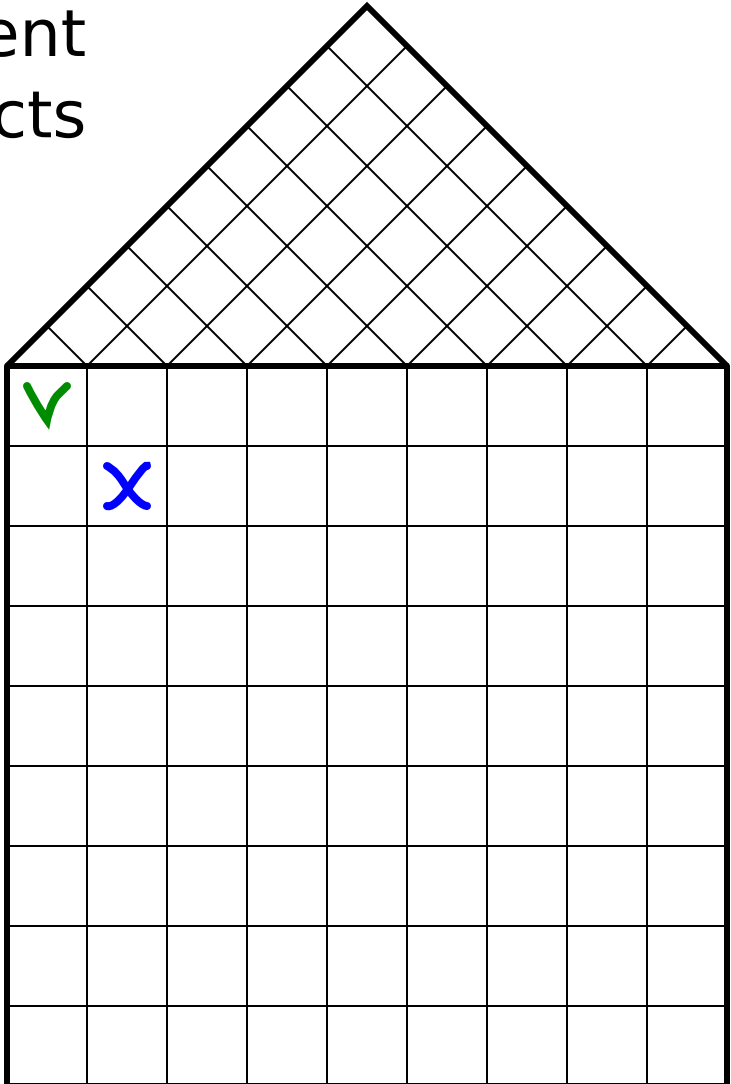Setting up specifications  
Design of amplifier type: A, B, C, D



SLiCAP  
SLiCAP

Negative feedback can be applied if:

Circuit dimensions are much smaller than the wavelength of the highest frequency of interest

Process cut-off frequency is much larger than the highest frequency of interest

**Design of the active antenna:**

Function, performance, costs and environment  
Feedback configuration


design aspects

# Negative feedback amplifiers generally outperform non-feedback amplifiers

Design of independent performance aspects

interaction between design aspects

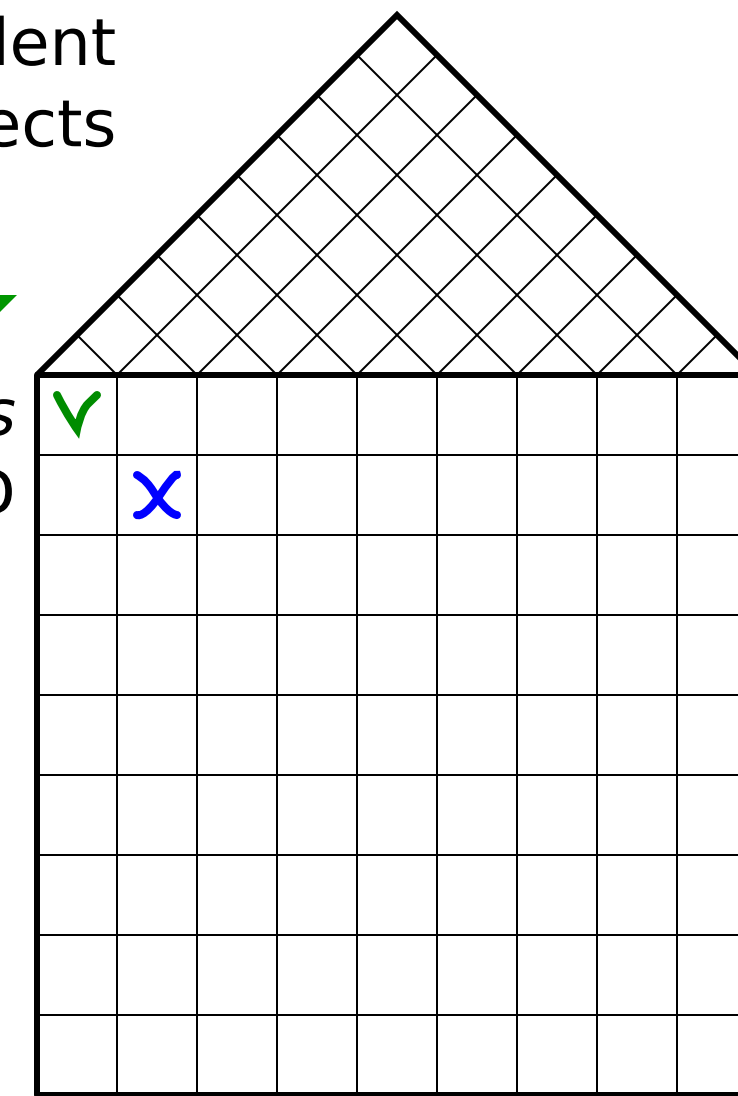Setting up specifications  
Design of amplifier type: A, B, C, D



SLiCAP  
SLiCAP

Negative feedback can be applied if:

Circuit dimensions are much smaller than the wavelength of the highest frequency of interest

Process cut-off frequency is much larger than the highest frequency of interest

## Design of the active antenna:

Determine valid combinations of T1 parameters A, B, C, D

Function, performance, costs and environment  
Feedback configuration


design aspects

**Negative feedback amplifiers generally outperform non-feedback amplifiers**

Design of independent performance aspects

interaction between design aspects

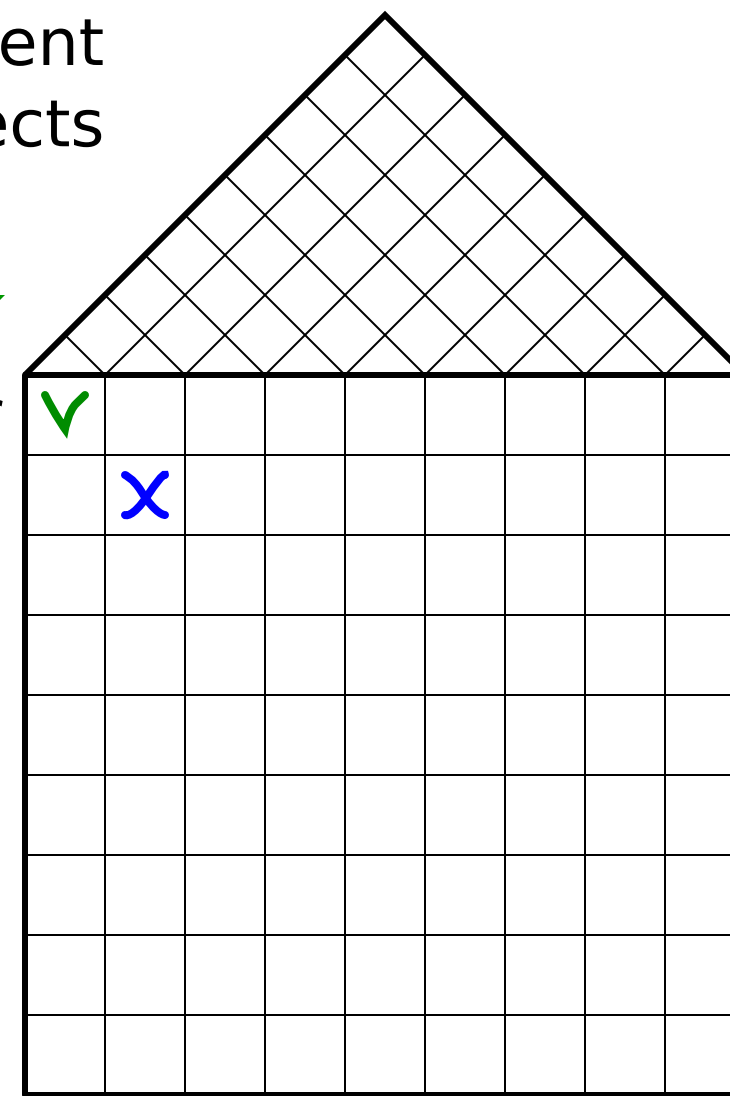Setting up specifications  
Design of amplifier type: A, B, C, D



SLiCAP  
SLiCAP

Negative feedback can be applied if:

Circuit dimensions are much smaller than the wavelength of the highest frequency of interest

Process cut-off frequency is much larger than the highest frequency of interest

**Design of the active antenna:**

Determine valid combinations of T1 parameters A, B, C, D

Design feedback configurations for these combinations

Function, performance, costs and environment  
Feedback configuration


design aspects

# Negative feedback amplifiers generally outperform non-feedback amplifiers

Design of independent performance aspects

interaction between design aspects

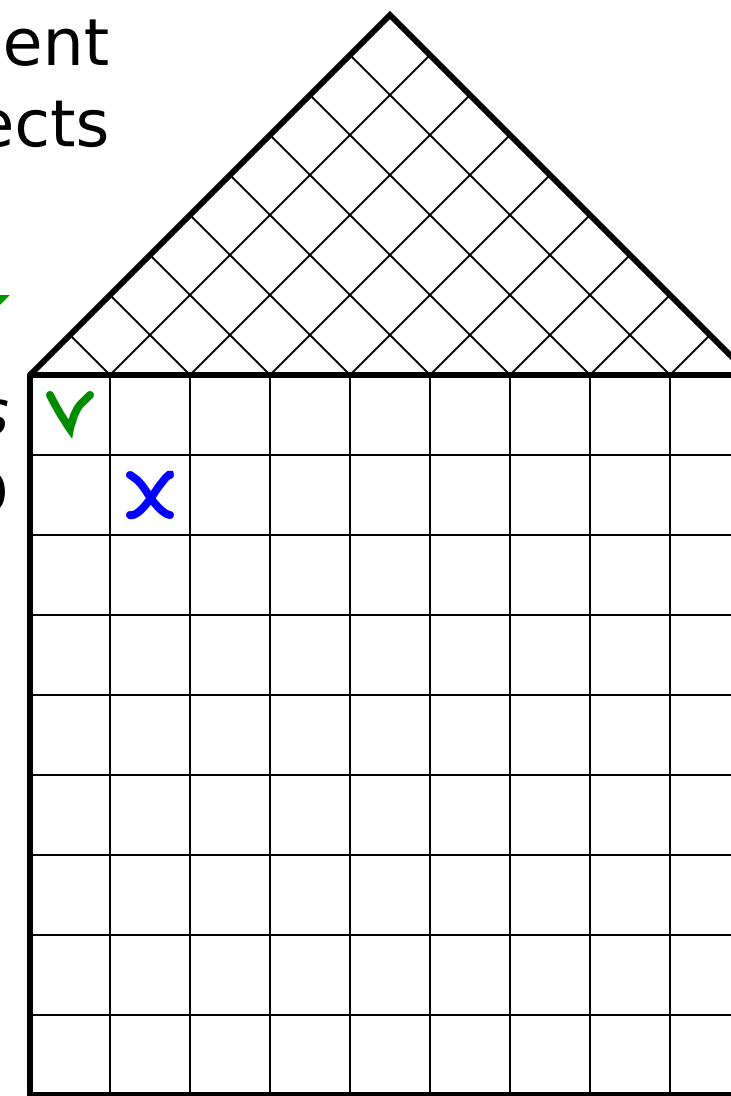Setting up specifications  
Design of amplifier type: A, B, C, D



SLiCAP  
SLiCAP

Negative feedback can be applied if:

Circuit dimensions are much smaller than the wavelength of the highest frequency of interest

Process cut-off frequency is much larger than the highest frequency of interest

## Design of the active antenna:

Determine valid combinations of T1 parameters A, B, C, D

Design feedback configurations for these combinations

Discuss their feasibility (comparison table or decision matrix)

Function, performance, costs and environment  
Feedback configuration


design aspects

# Negative feedback amplifiers generally outperform non-feedback amplifiers

Design of independent performance aspects

interaction between design aspects

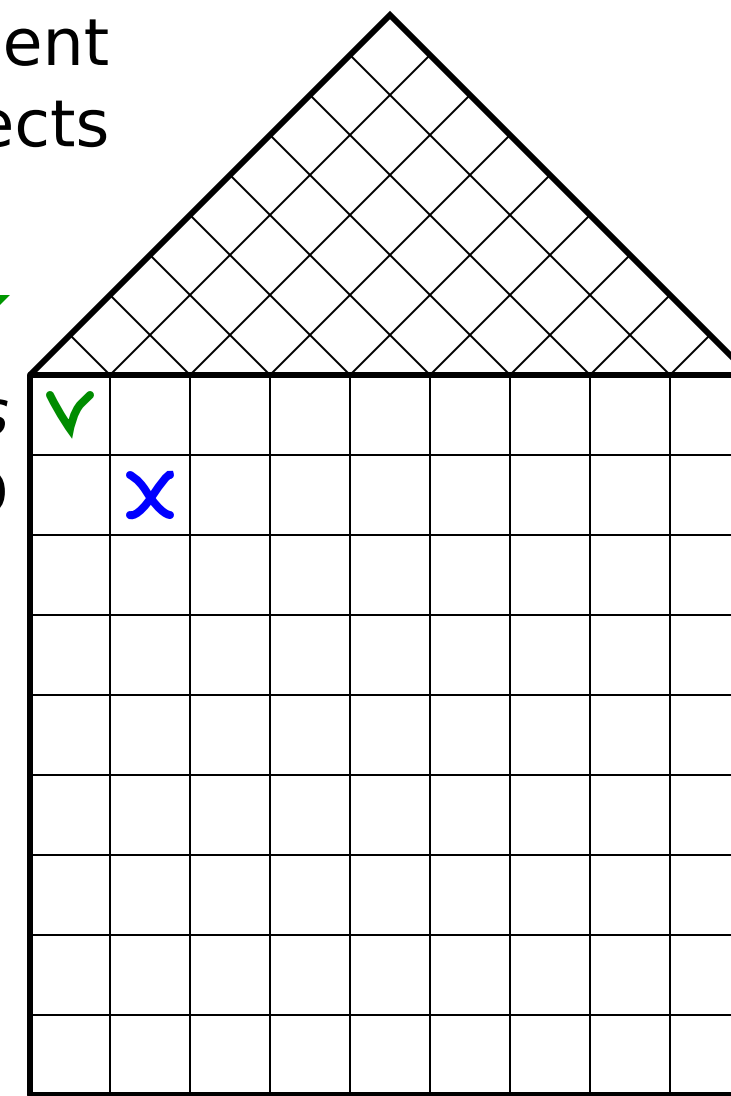Setting up specifications  
Design of amplifier type: A, B, C, D



Negative feedback can be applied if:

Circuit dimensions are much smaller than the wavelength of the highest frequency of interest

Process cut-off frequency is much larger than the highest frequency of interest

## Design of the active antenna:

- Determine valid combinations of T1 parameters A, B, C, D
- Design feedback configurations for these combinations
- Discuss their feasibility (comparison table or decision matrix)

Design studies level fo detailing depends on experience

Function, performance, costs and environment Feedback configuration


design aspects

# Negative feedback amplifiers generally outperform non-feedback amplifiers

Design of independent performance aspects

interaction between design aspects

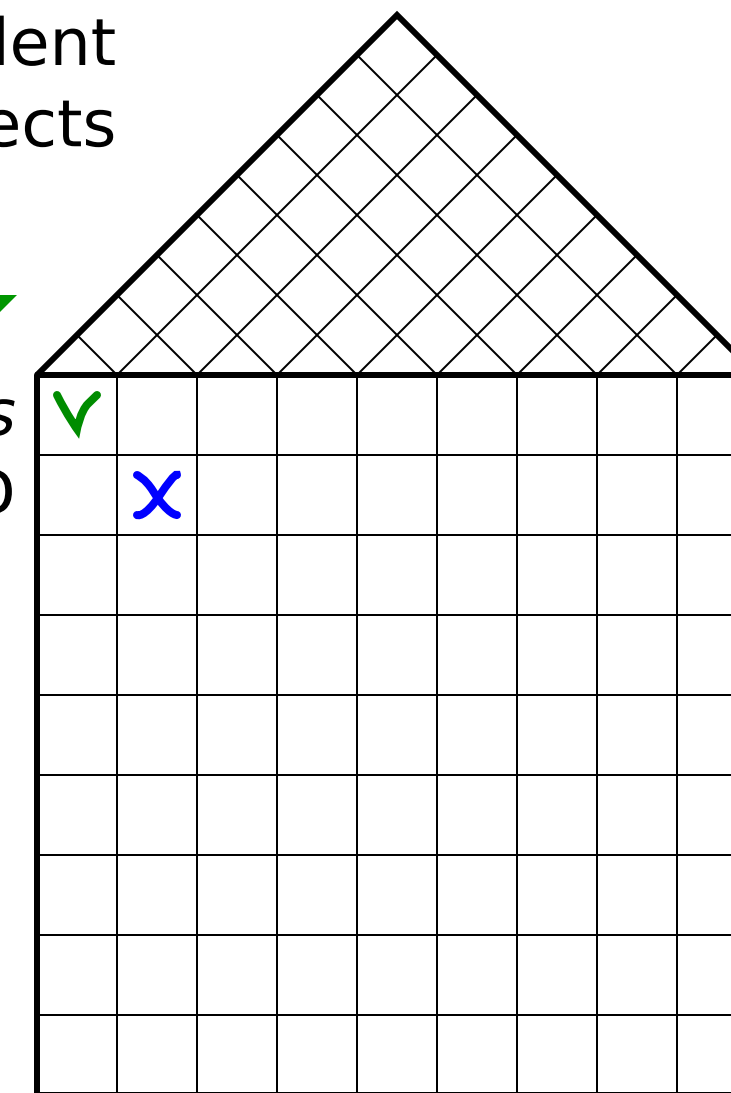Setting up specifications  
Design of amplifier type: A, B, C, D



Negative feedback can be applied if:

Circuit dimensions are much smaller than the wavelength of the highest frequency of interest

Process cut-off frequency is much larger than the highest frequency of interest

## Design of the active antenna:

- Determine valid combinations of T1 parameters A, B, C, D
- Design feedback configurations for these combinations
- Discuss their feasibility (comparison table or decision matrix)
- Select the most promising solution

Design studies level fo detailing depends on experience

Function, performance, costs and environment Feedback configuration

design aspects




# Negative feedback amplifiers generally outperform non-feedback amplifiers

Design of independent performance aspects

interaction between design aspects

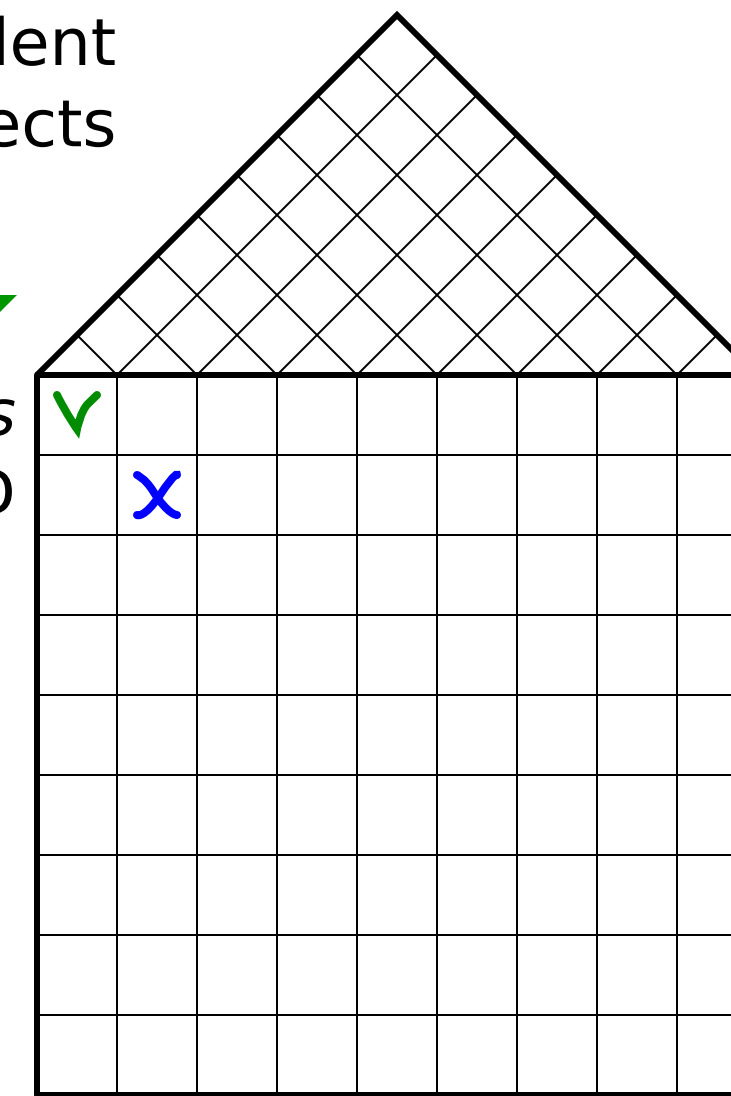Setting up specifications  
Design of amplifier type: A, B, C, D



Negative feedback can be applied if:

Circuit dimensions are much smaller than the wavelength of the highest frequency of interest

Process cut-off frequency is much larger than the highest frequency of interest

## Design of the active antenna:

- Determine valid combinations of T1 parameters A, B, C, D
- Design feedback configurations for these combinations
- Discuss their feasibility (comparison table or decision matrix)
- Select the most promising solution

design aspects

Result is a functional design or concept design which is assumed feasible

Design studies level fo detailing depends on experience


Function, performance, costs and environment Feedback configuration

## Negative feedback amplifiers generally outperform non-feedback amplifiers

Design of independent performance aspects

interaction between design aspects

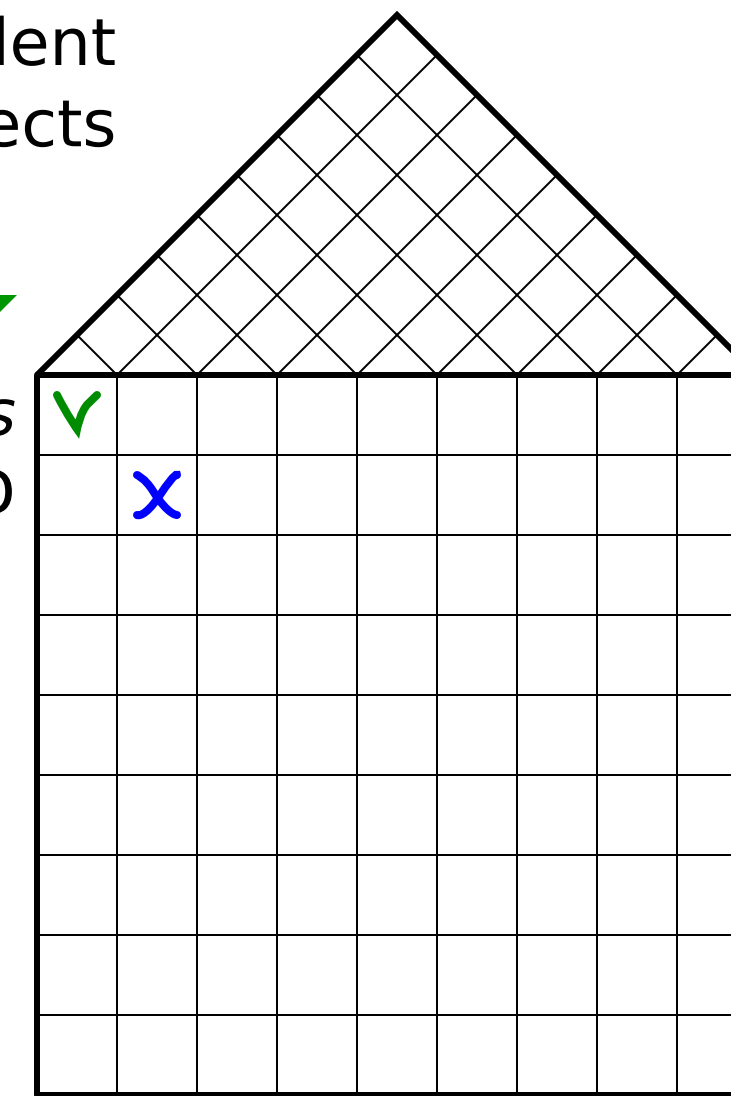Setting up specifications  
Design of amplifier type: A, B, C, D



SLiCAP  
SLiCAP

Negative feedback can be applied if:

Circuit dimensions are much smaller than the wavelength of the highest frequency of interest

Process cut-off frequency is much larger than the highest frequency of interest

## Design of the active antenna:

- Determine valid combinations of T1 parameters A, B, C, D
- Design feedback configurations for these combinations
- Discuss their feasibility (comparison table or decision matrix)
- Select the most promising solution

design aspects

Result is a functional design or concept design which is assumed feasible


Design studies level fo detailing depends on experience

Function, performance, costs and environment  
Feedback configuration


# Active antenna configurations

# Active antenna configurations


A, B

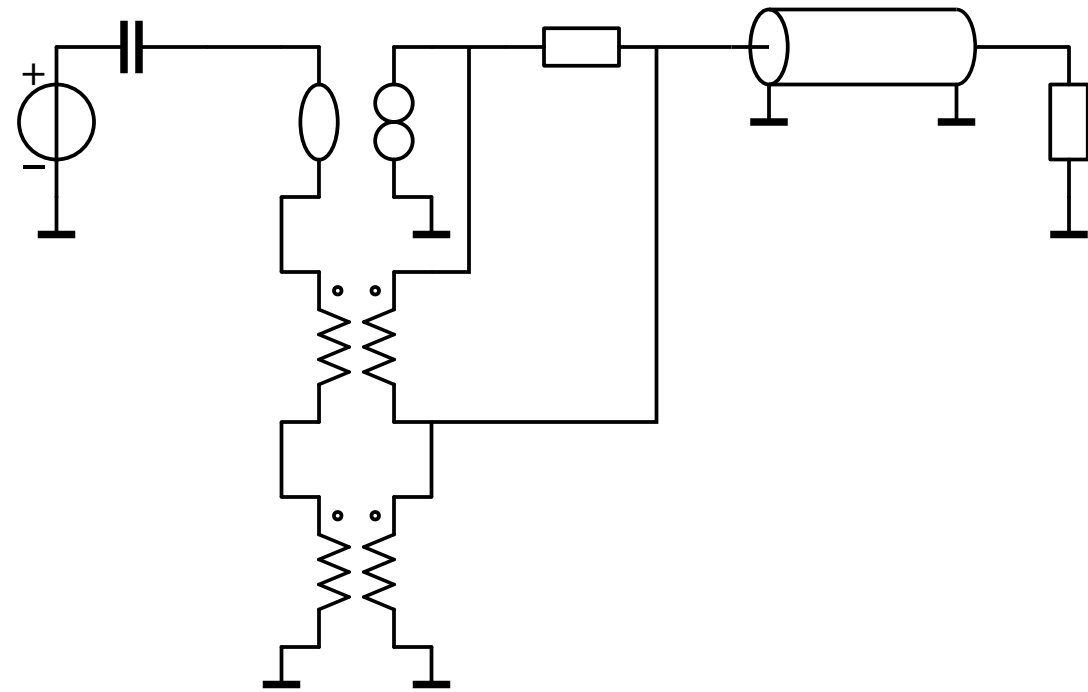


# Active antenna configurations

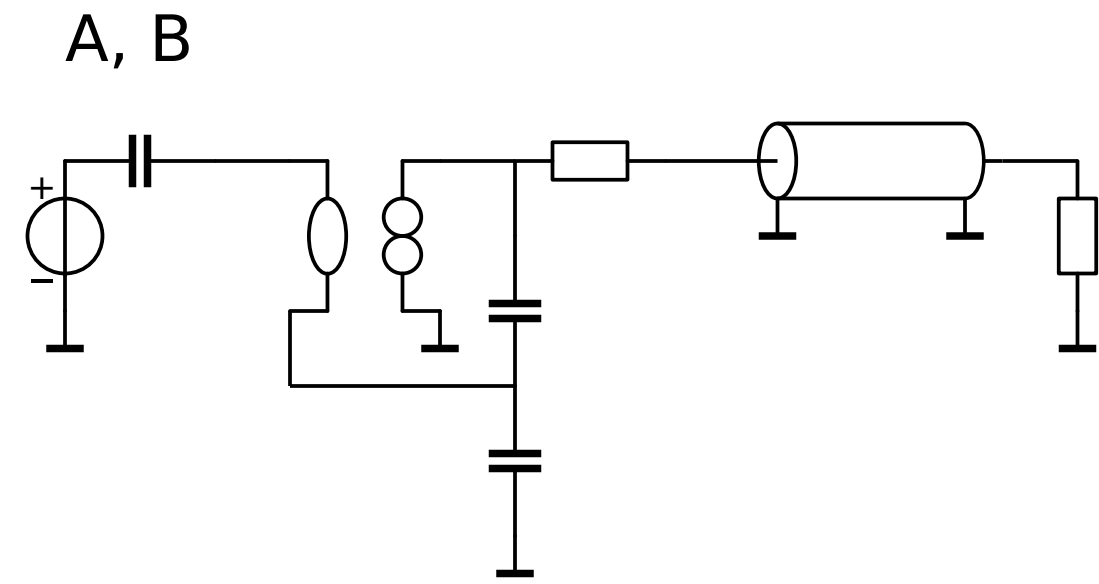


# Active antenna configurations

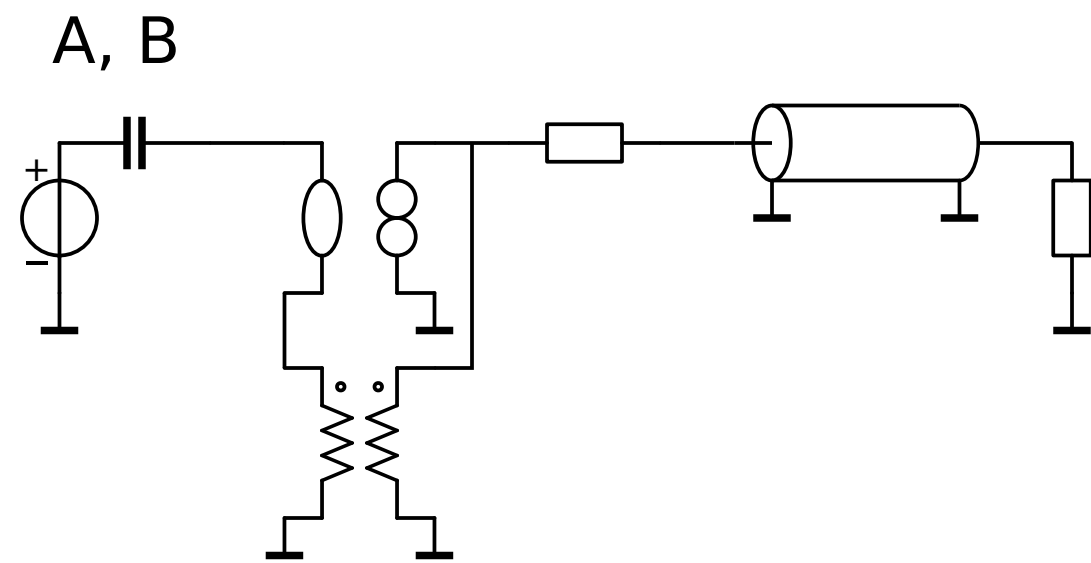

# Active antenna configurations

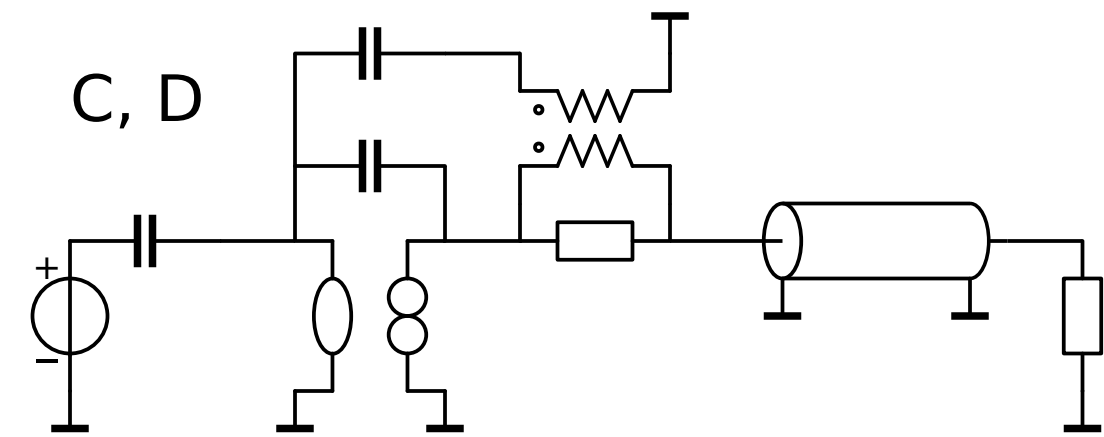


# Active antenna configurations

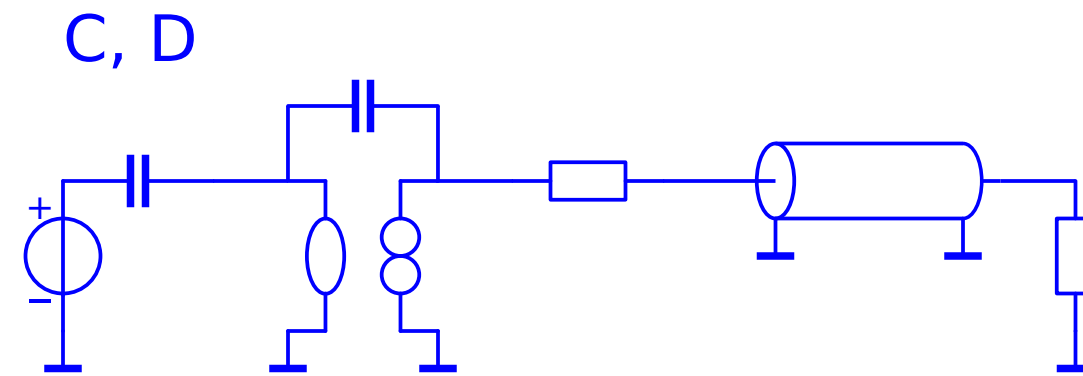




# Active antenna configurations


A, B

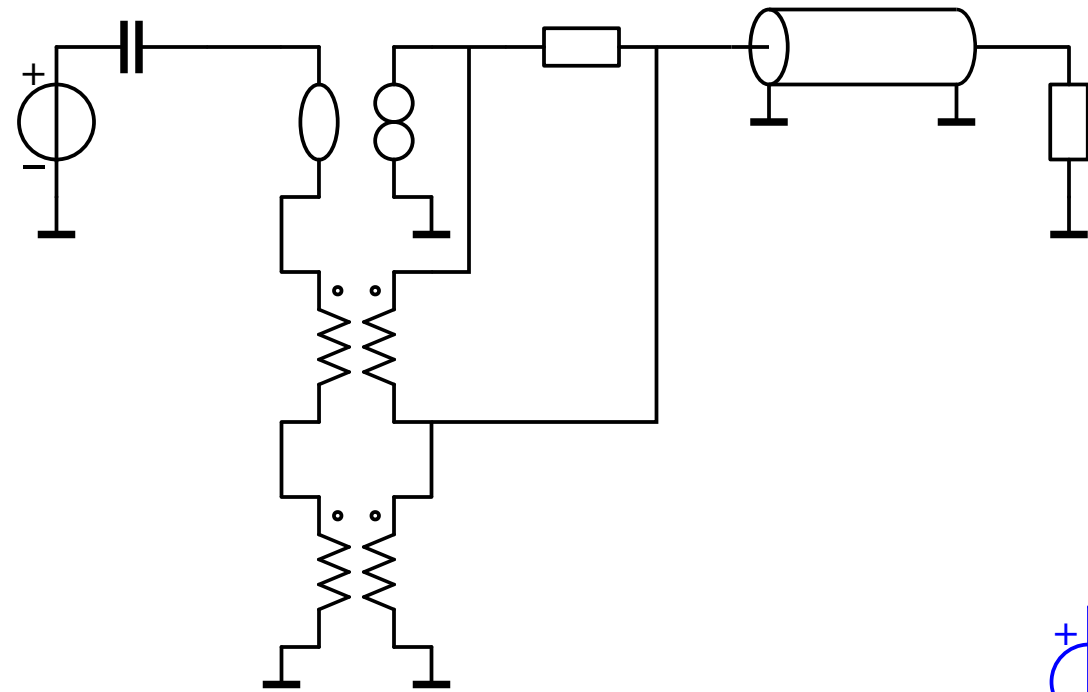


A, B

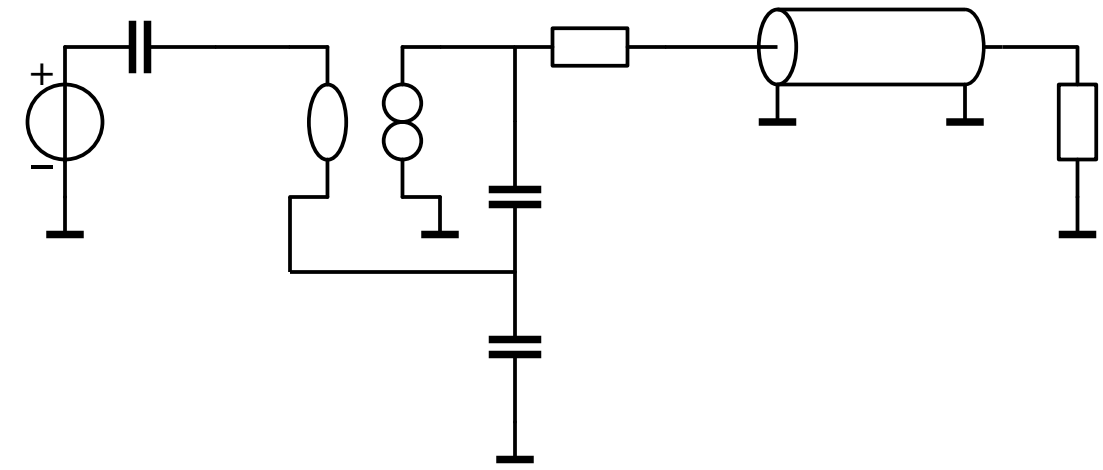


C, D

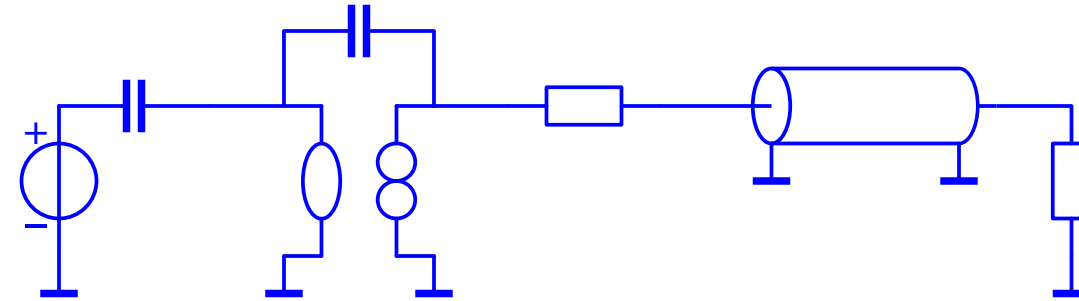

A, B

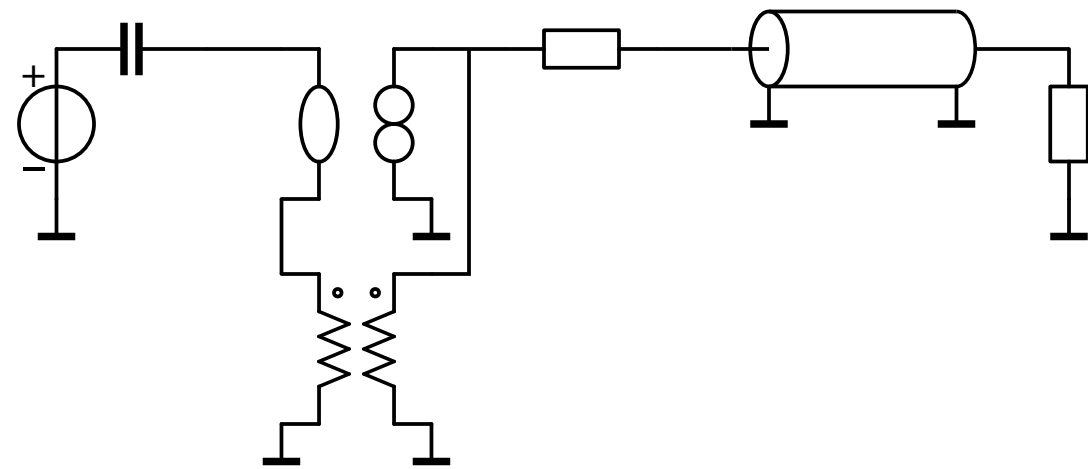

C, D

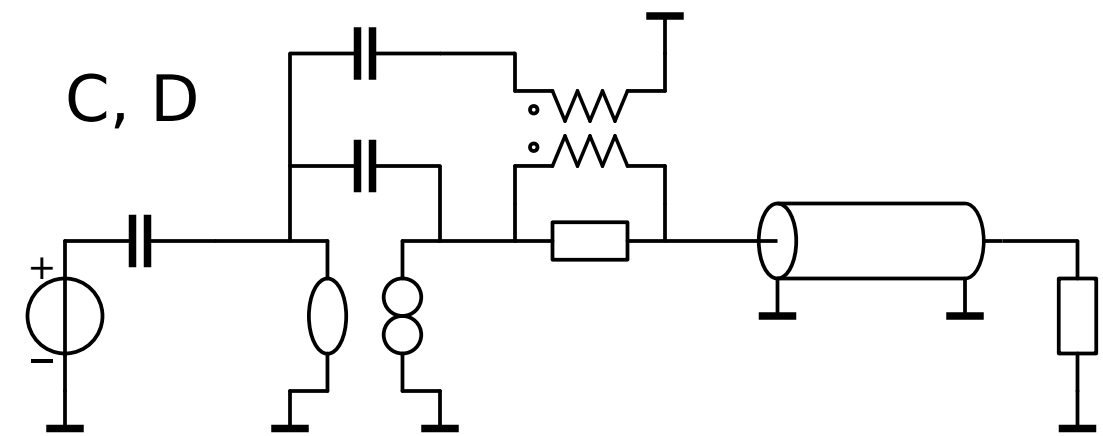


# **Structured Electronic Design**

## Step 3

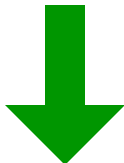
### Feasibility of the noise requirements

*Anton J.M. Montagne*


Design of independent performance aspects



interaction between design aspects

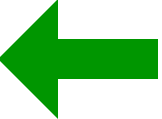

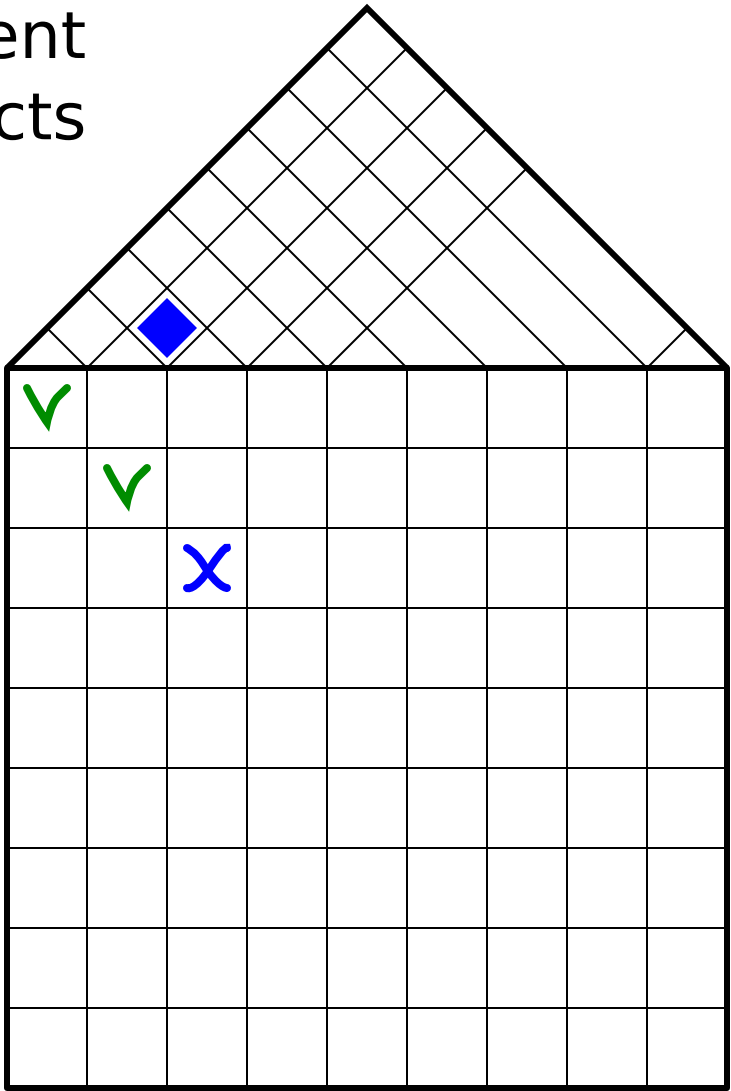
Setting up specifications  
Design of amplifier type: A, B, C, D  
Feasibility of noise (temperature drift) specifications




SLiCAP  
SLiCAP  
SLiCAP

Function, performance,  
costs and environment  
Feedback configuration  
Controller input stage


design aspects

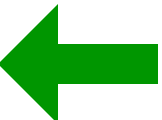

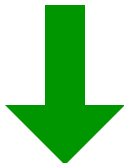Design of independent performance aspects



interaction between design aspects

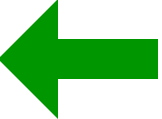


Setting up specifications

Design of amplifier type: A, B, C, D

Feasibility of noise (temperature drift) specifications


SLiCAP  
SLiCAP  
SLiCAP

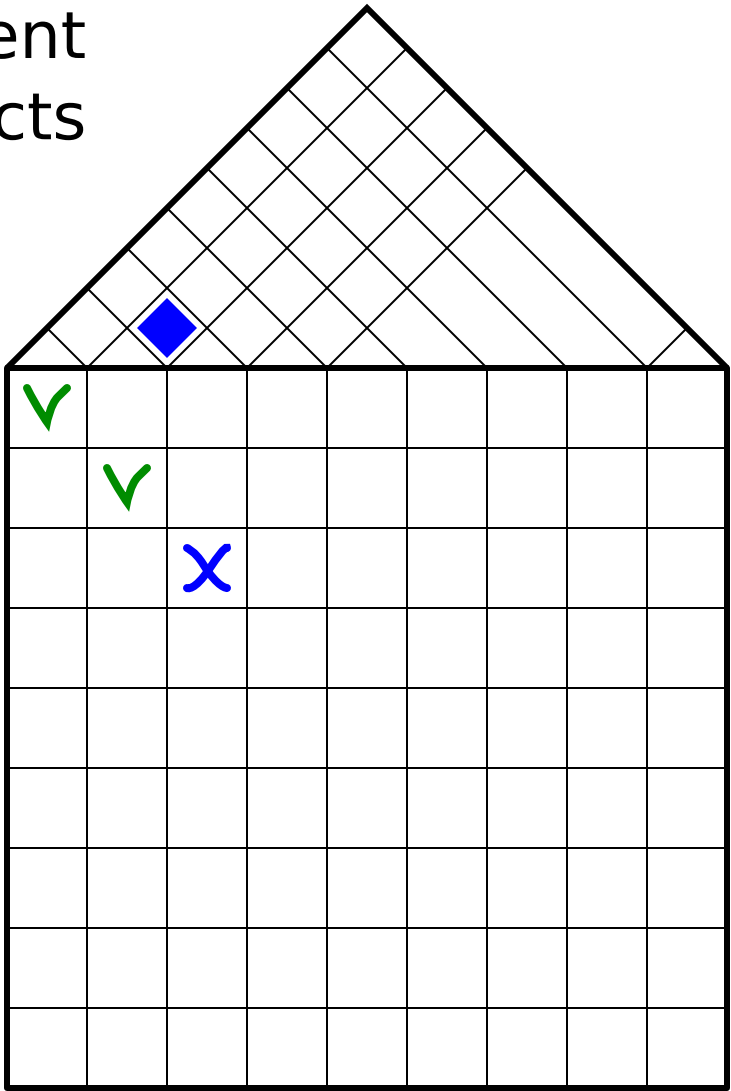


**Design of the feedback network and the input stage of the controller**

Function, performance, costs and environment  
Feedback configuration  
Controller input stage


design aspects

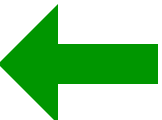

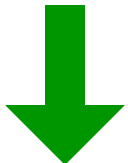Design of independent performance aspects



interaction between design aspects

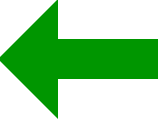


Setting up specifications

Design of amplifier type: A, B, C, D

Feasibility of noise (temperature drift) specifications

SLiCAP  
SLiCAP  
SLiCAP

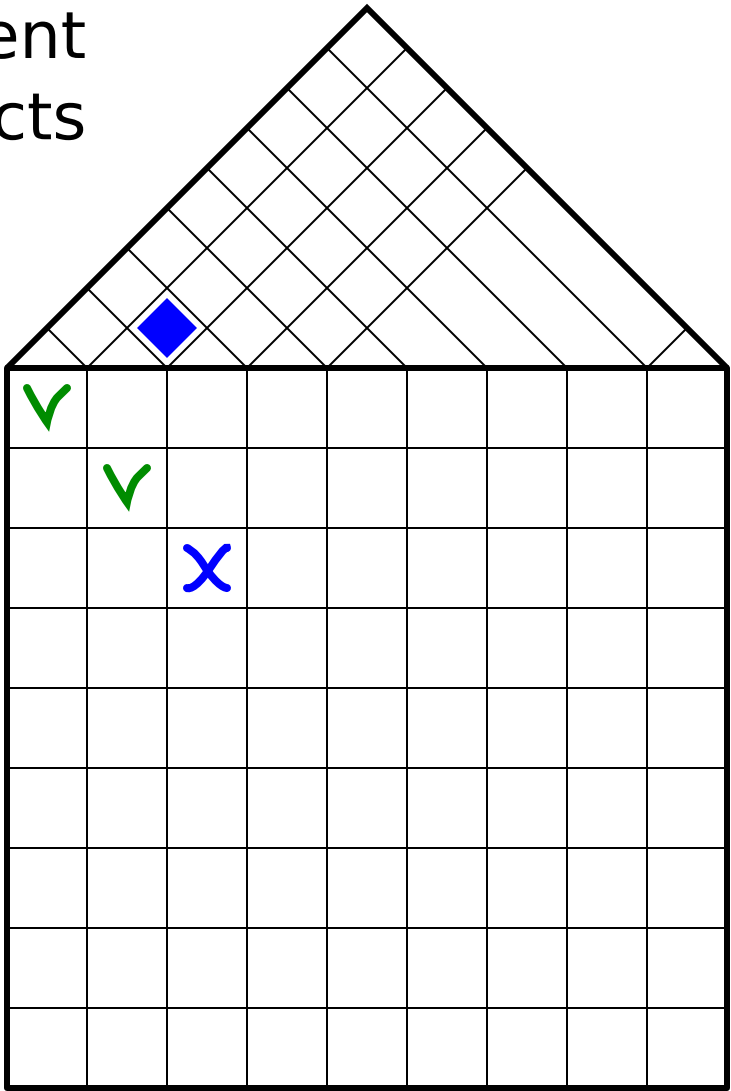


### Design of the feedback network and the input stage of the controller


If the frequency range of temperature variations overlaps with that of the signal, equivalent input offset and bias variations have to be considered as input noise sources.

Function, performance, costs and environment  
Feedback configuration  
Controller input stage


design aspects

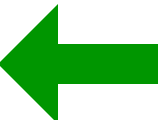

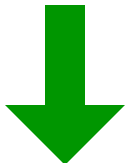Design of independent performance aspects




interaction between design aspects

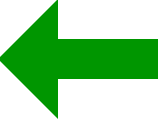

Setting up specifications

Design of amplifier type: A, B, C, D

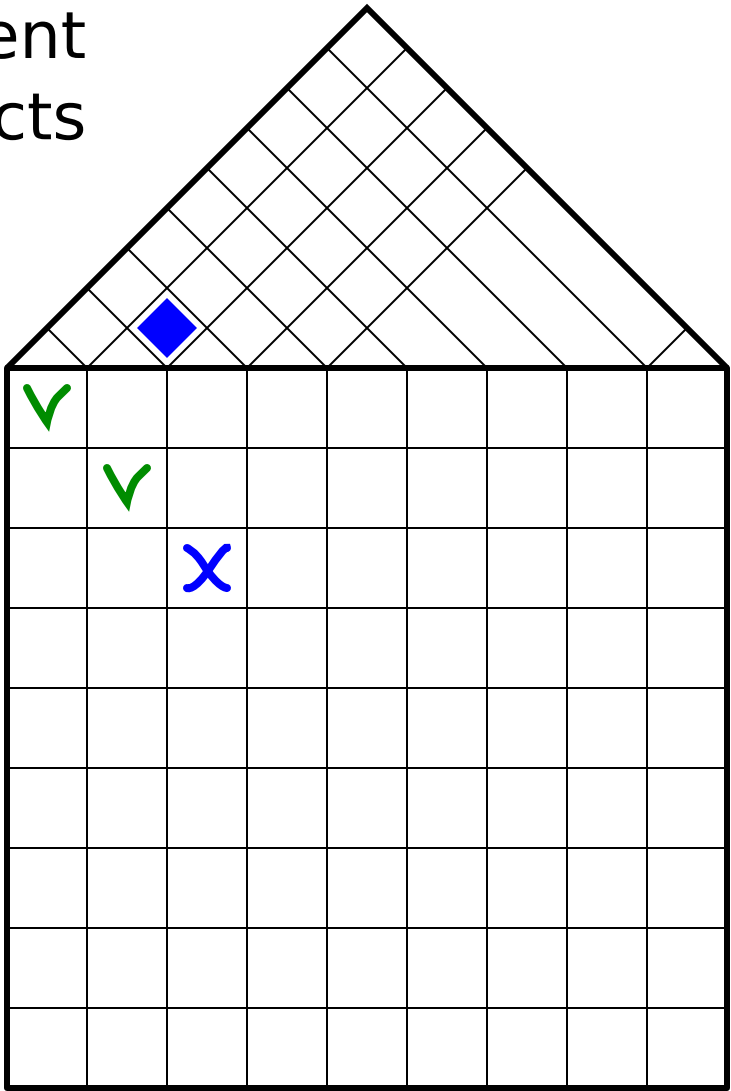Feasibility of noise (temperature drift) specifications



SLiCAP  
SLiCAP  
SLiCAP


### Design of the feedback network and the input stage of the controller

If the frequency range of temperature variations overlaps with that of the signal, equivalent input offset and bias variations have to be considered as input noise sources.


Otherwise, the influence of temperature variations can be dealt with at a later stage of the design.

Function, performance, costs and environment  
Feedback configuration  
Controller input stage


design aspects

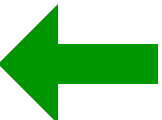

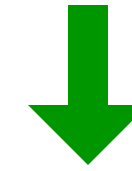Design of independent performance aspects



interaction between design aspects

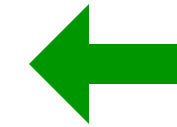


Setting up specifications

Design of amplifier type: A, B, C, D

Feasibility of noise (temperature drift) specifications

SLiCAP  
SLiCAP  
SLiCAP

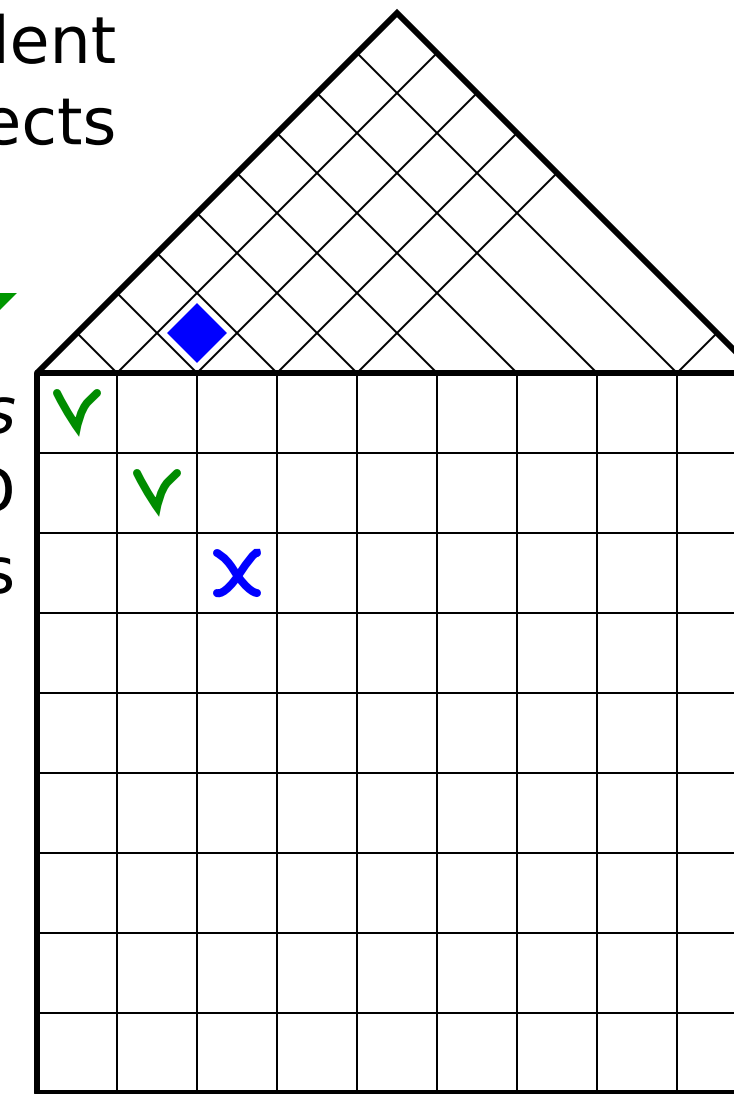


## Design of the feedback network and the input stage of the controller

If the frequency range of temperature variations overlaps with that of the signal, equivalent input offset and bias variations have to be considered as input noise sources.

Otherwise, the influence of temperature variations can be dealt with at a later stage of the design.

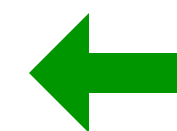
## Design of the active antenna:

Function, performance,  
costs and environment  
Feedback configuration  
Controller input stage




design aspects

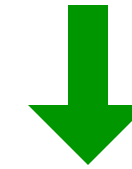Design of independent performance aspects



interaction between design aspects

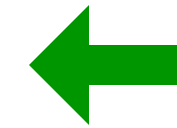


Setting up specifications

Design of amplifier type: A, B, C, D

Feasibility of noise (temperature drift) specifications

SLiCAP  
SLiCAP  
SLiCAP

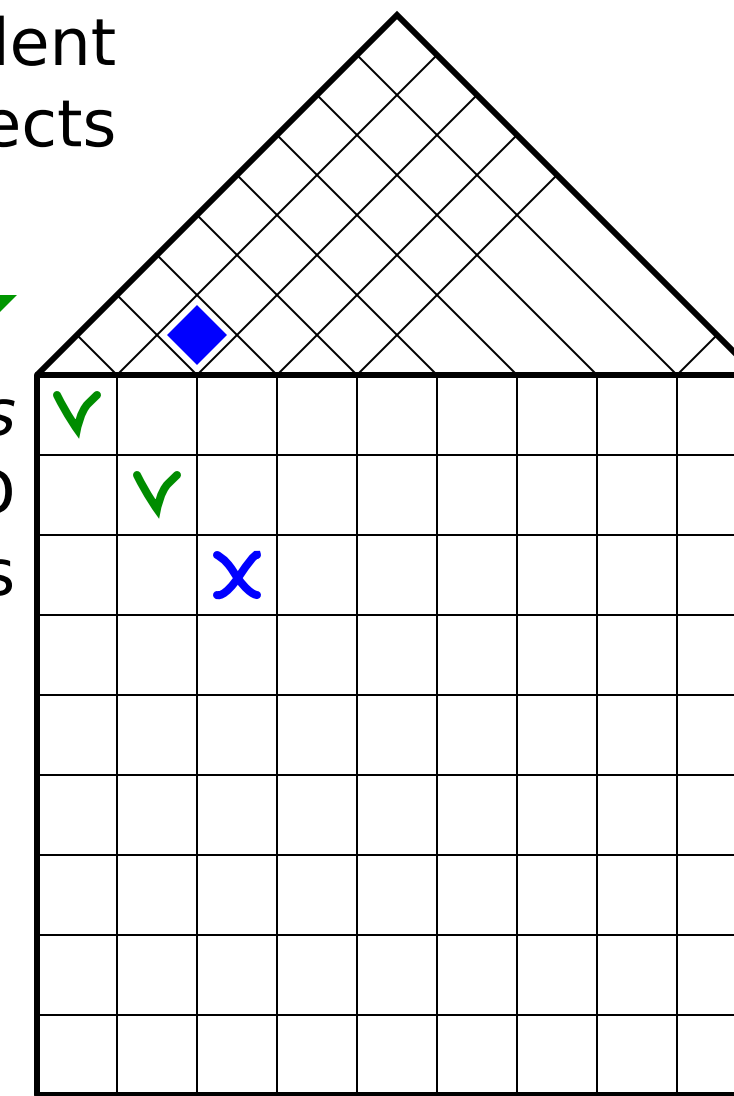

## Design of the feedback network and the input stage of the controller


If the frequency range of temperature variations overlaps with that of the signal, equivalent input offset and bias variations have to be considered as input noise sources.

Otherwise, the influence of temperature variations can be dealt with at a later stage of the design.
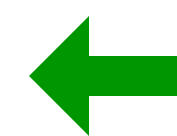
## Design of the active antenna:

Design a CS stage with sufficiently low noise performance


Function, performance, costs and environment  
Feedback configuration  
Controller input stage




design aspects



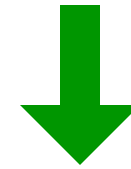Design of independent performance aspects



interaction between design aspects

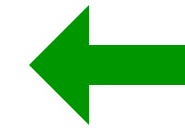


Setting up specifications

Design of amplifier type: A, B, C, D

Feasibility of noise (temperature drift) specifications

SLiCAP  
SLiCAP  
SLiCAP

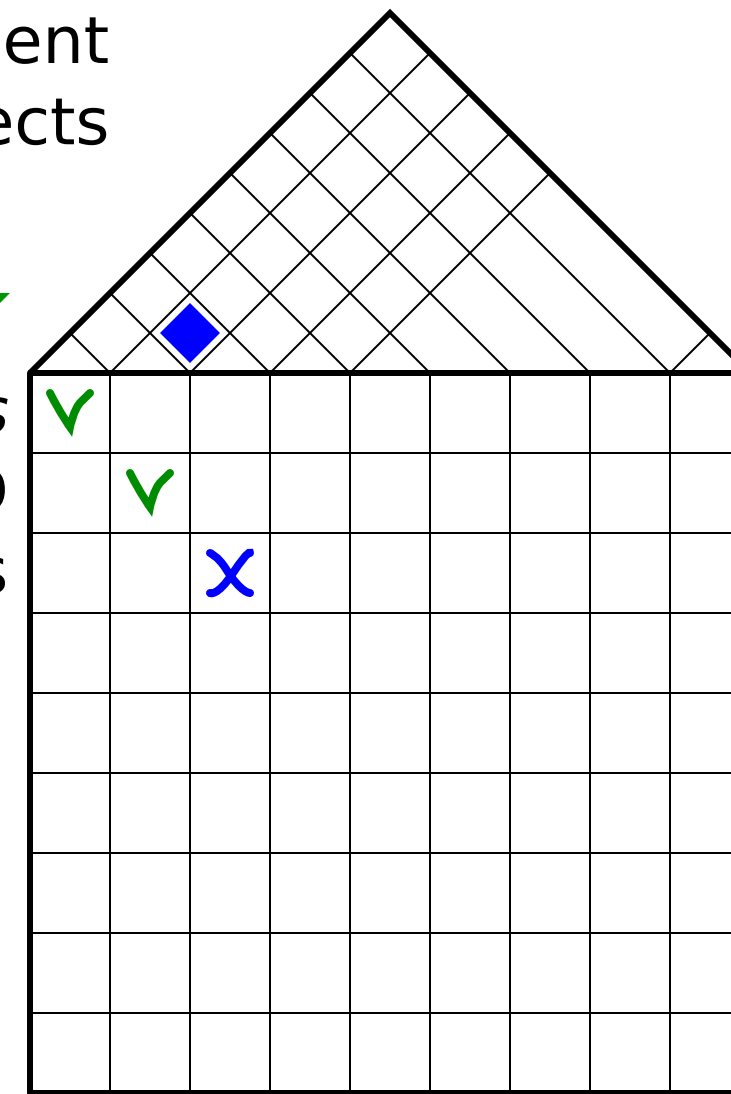

## Design of the feedback network and the input stage of the controller

If the frequency range of temperature variations overlaps with that of the signal, equivalent input offset and bias variations have to be considered as input noise sources.


Otherwise, the influence of temperature variations can be dealt with at a later stage of the design.

## Design of the active antenna:

Design a CS stage with sufficiently low noise performance


Determine valid ranges for:  $I_{DS}$ ,  $W$ ,  $L$ ,  $M$

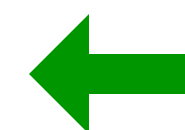Function, performance, costs and environment  
Feedback configuration  
Controller input stage




design aspects

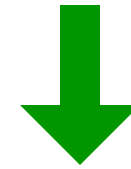Design of independent performance aspects



interaction between design aspects

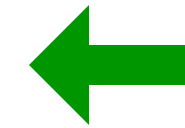


Setting up specifications

Design of amplifier type: A, B, C, D

Feasibility of noise (temperature drift) specifications

SLiCAP  
SLiCAP  
SLiCAP

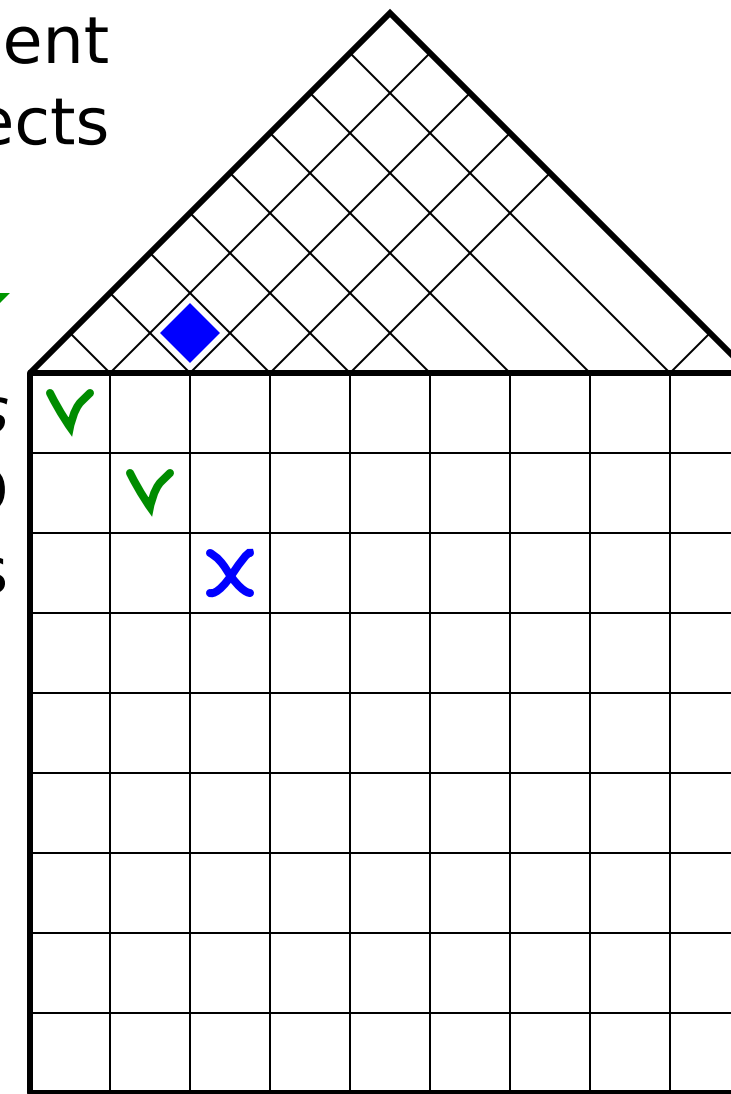

## Design of the feedback network and the input stage of the controller

If the frequency range of temperature variations overlaps with that of the signal, equivalent input offset and bias variations have to be considered as input noise sources.


Otherwise, the influence of temperature variations can be dealt with at a later stage of the design.

## Design of the active antenna:

Design a CS stage with sufficiently low noise performance

Determine valid ranges for:  $I_{DS}$ ,  $W$ ,  $L$ ,  $M$

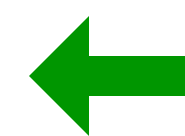
Function, performance, costs and environment  
Feedback configuration  
Controller input stage




design aspects

# CS input stage design

# CS input stage design

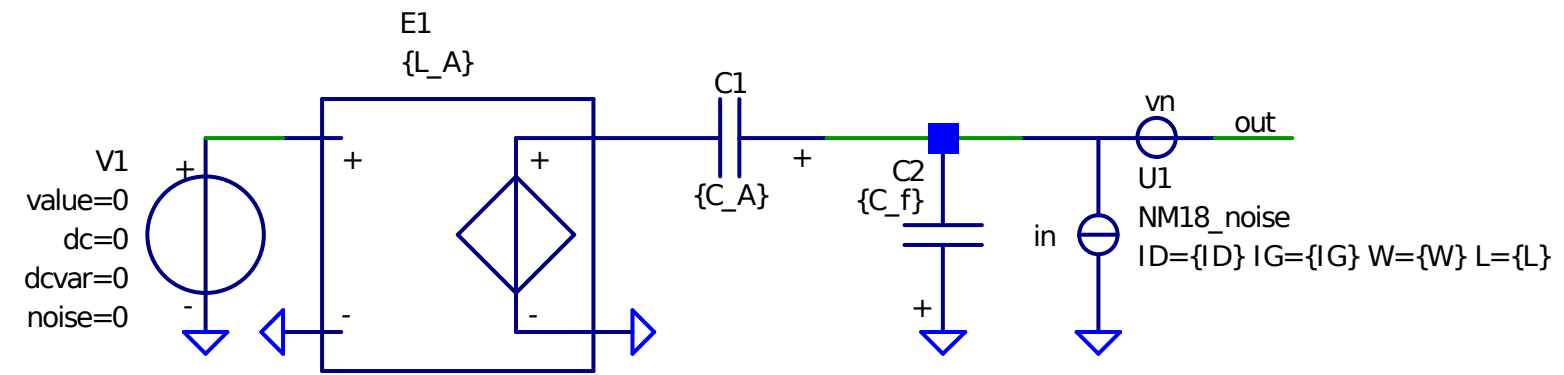


# CS input stage design

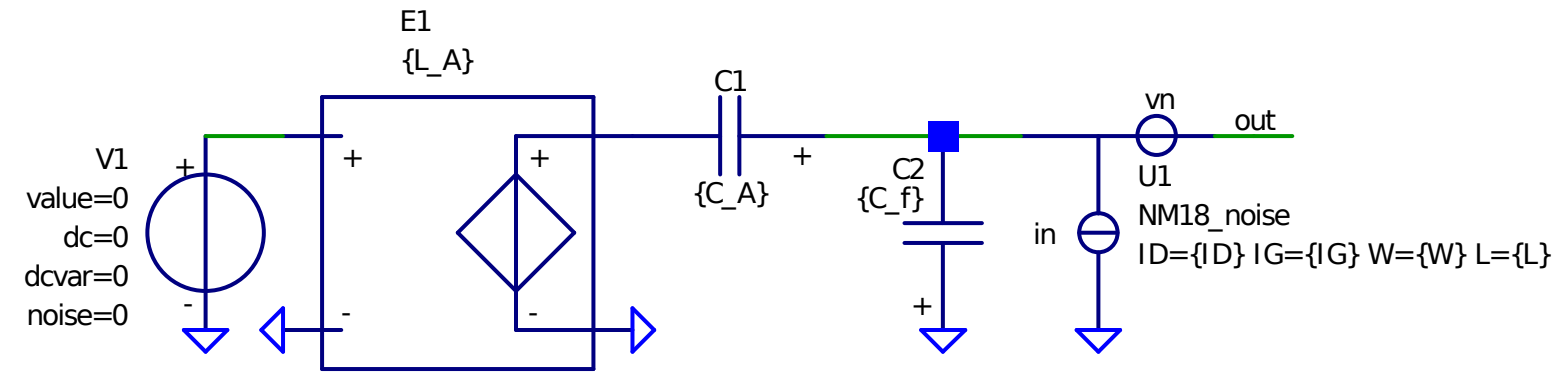

Source-referred noise at the output of E1:

# CS input stage design

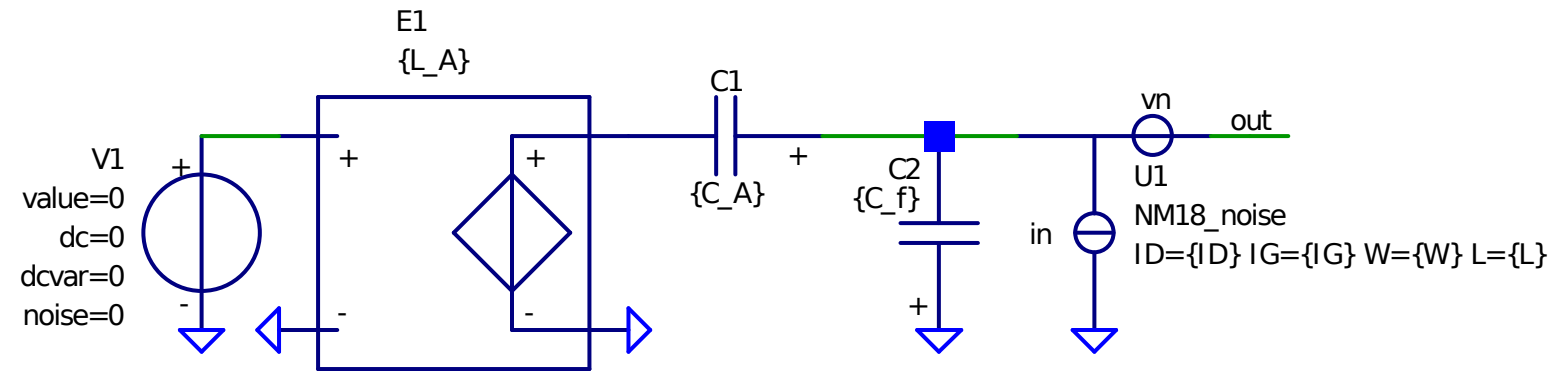


Source-referred noise at the output of E1:

$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2 \left(1 + \frac{f_l}{f}\right)$$

$$f_l = \alpha f_T = \alpha \frac{g_m}{2\pi c_{iss}} \quad \alpha: \text{process parameter}$$

# CS input stage design

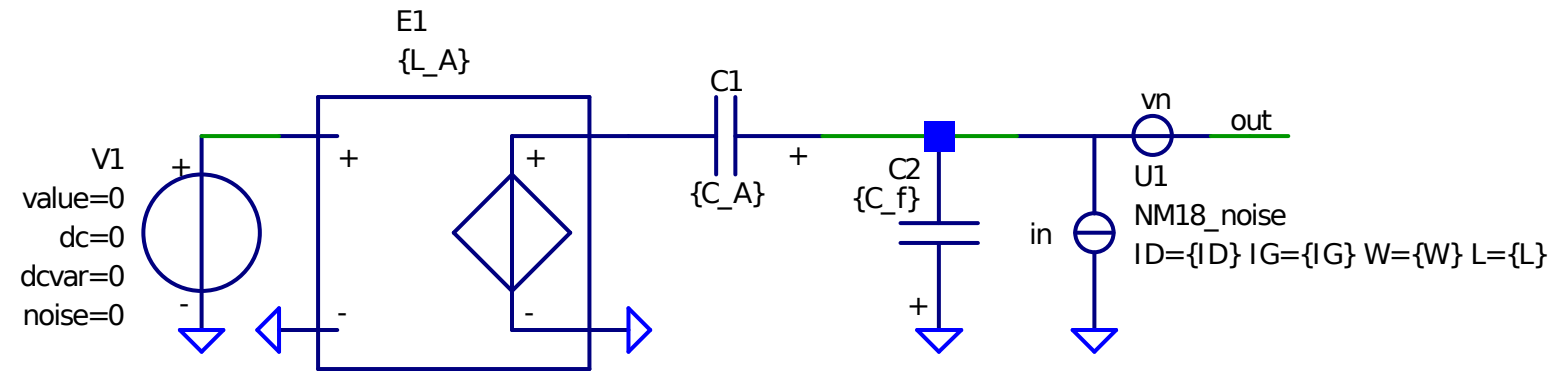


Source-referred noise at the output of E1:

$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iSS}}{C_s}\right)^2 \left(1 + \frac{f_l}{f}\right)$$

$$f_l = \alpha f_T = \alpha \frac{g_m}{2\pi c_{iSS}} \quad \alpha: \text{process parameter}$$

1/f noise: 
$$S_{v_{n_f}} = \frac{2kTn\Gamma\alpha}{\pi f c_{iSS}} \left(1 + \frac{c_{iSS}}{C_s}\right)^2$$

# CS input stage design

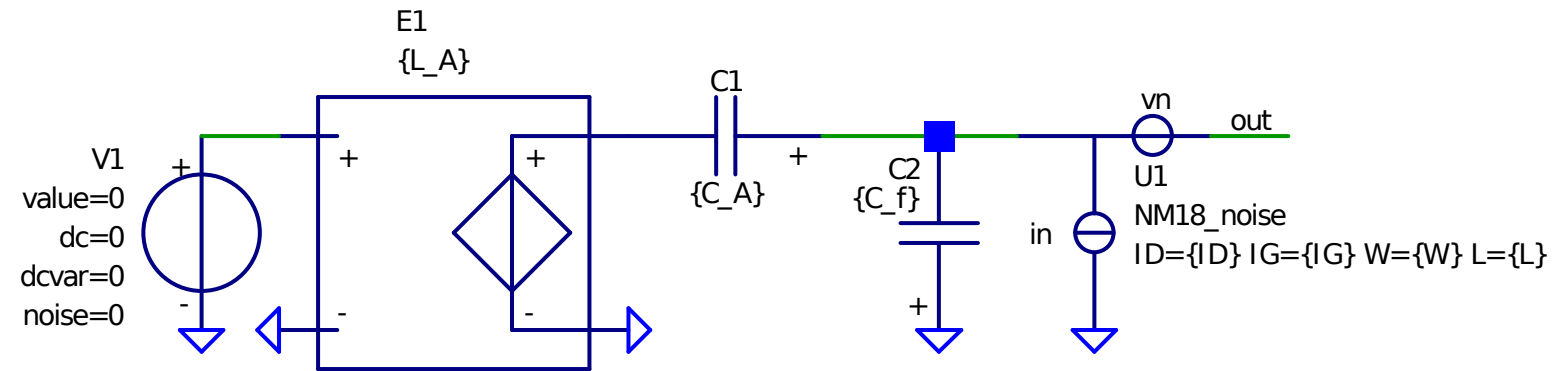

Source-referred noise at the output of E1:

$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iSS}}{C_s}\right)^2 \left(1 + \frac{f_l}{f}\right)$$


$$f_l = \alpha f_T = \alpha \frac{g_m}{2\pi c_{iSS}} \quad \alpha: \text{process parameter}$$

$$\text{1/f noise:} \quad S_{v_{n_f}} = \frac{2kTn\Gamma\alpha}{\pi f c_{iSS}} \left(1 + \frac{c_{iSS}}{C_s}\right)^2$$

$$\text{Lowest 1/f if:} \quad c_{iSS} = C_s$$



# CS input stage design

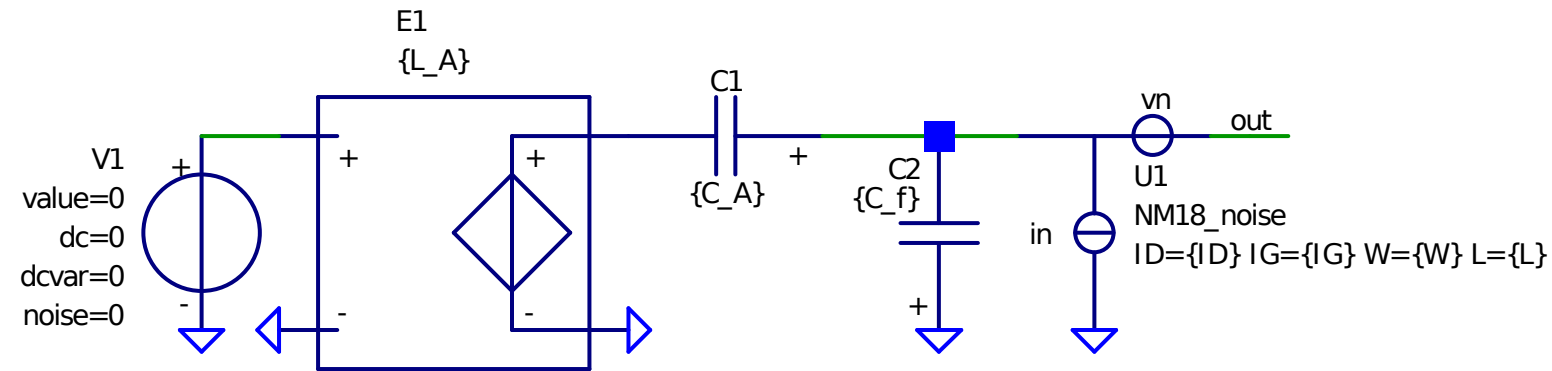

Source-referred noise at the output of E1:

$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2 \left(1 + \frac{f_l}{f}\right)$$


$$f_l = \alpha f_T = \alpha \frac{g_m}{2\pi c_{iss}} \quad \alpha: \text{process parameter}$$

1/f noise: 
$$S_{v_{n_f}} = \frac{2kTn\Gamma\alpha}{\pi f c_{iss}} \left(1 + \frac{c_{iss}}{C_s}\right)^2$$

Lowest 1/f if: 
$$c_{iss} = C_s$$

Four noise: 
$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2$$

# CS input stage design

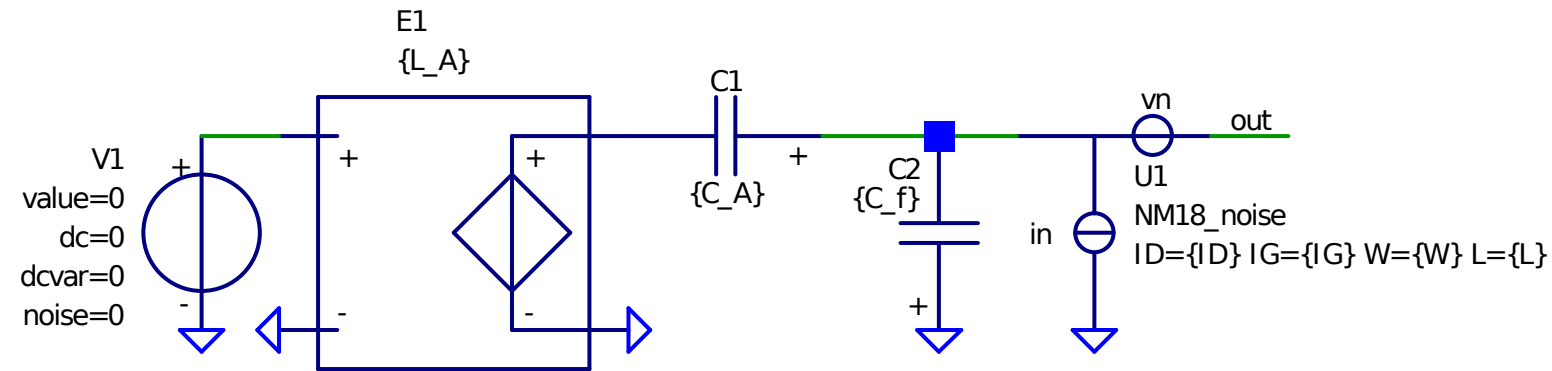

Source-referred noise at the output of E1:


$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2 \left(1 + \frac{f_l}{f}\right)$$

$$f_l = \alpha f_T = \alpha \frac{g_m}{2\pi c_{iss}} \quad \alpha: \text{process parameter}$$

1/f noise: 
$$S_{v_{n_f}} = \frac{2kTn\Gamma\alpha}{\pi f c_{iss}} \left(1 + \frac{c_{iss}}{C_s}\right)^2$$



Lowest 1/f if: 
$$c_{iss} = C_s$$

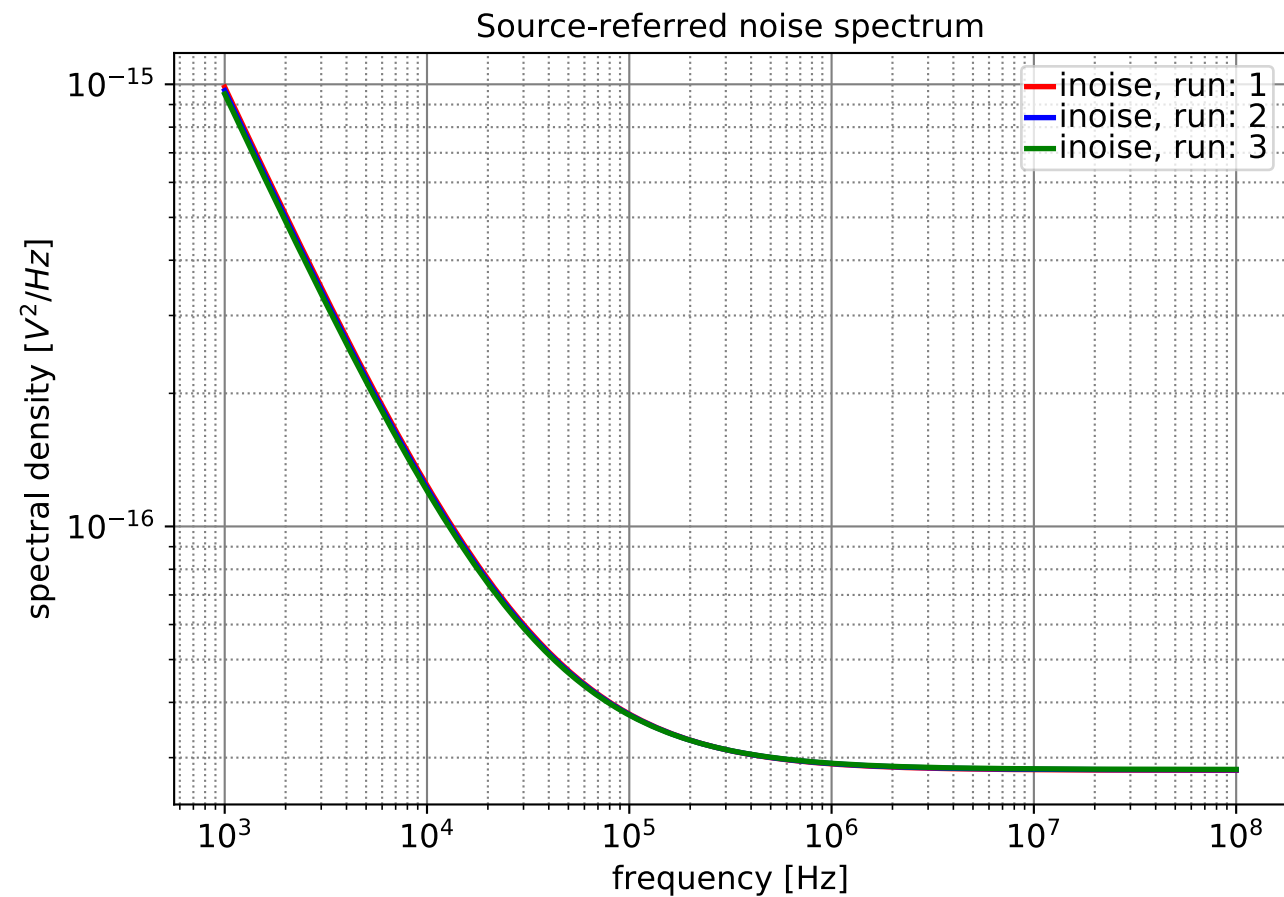Four noise: 
$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2$$



Antenna-referred noise:

# CS input stage design

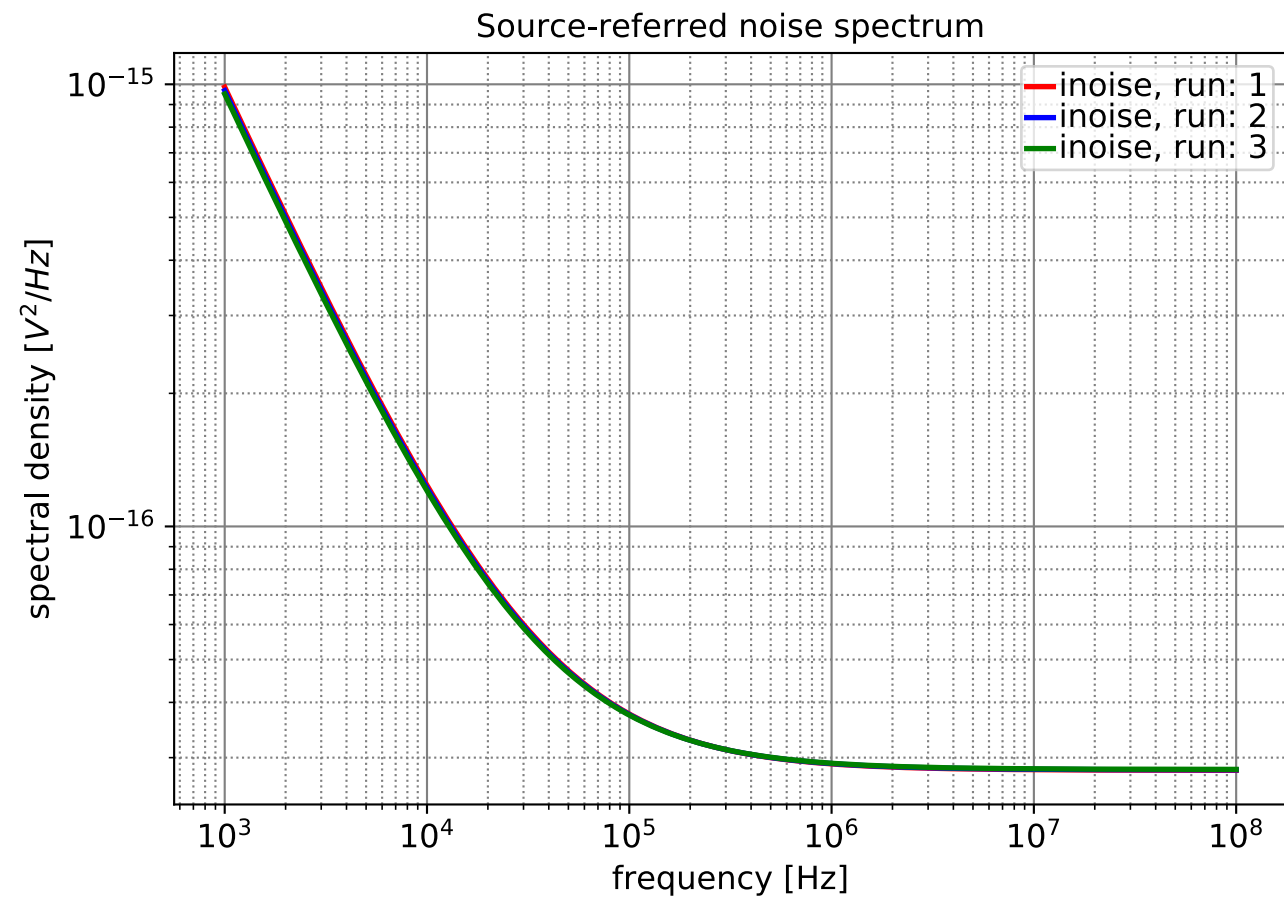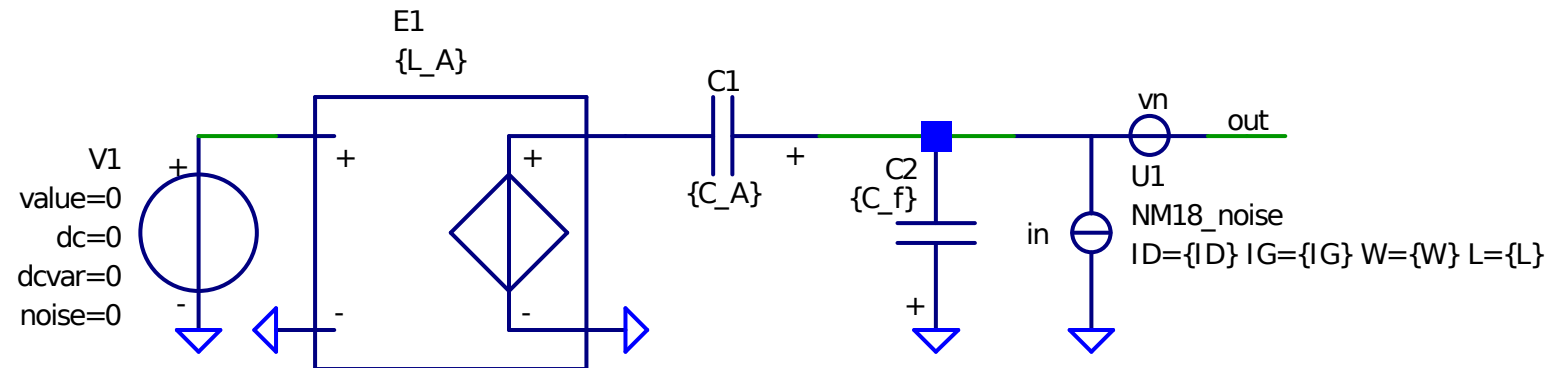

Source-referred noise at the output of E1:

$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2 \left(1 + \frac{f_l}{f}\right)$$

$$f_l = \alpha f_T = \alpha \frac{g_m}{2\pi c_{iss}} \quad \alpha: \text{process parameter}$$

1/f noise:  $S_{v_{n_f}} = \frac{2kTn\Gamma\alpha}{\pi f c_{iss}} \left(1 + \frac{c_{iss}}{C_s}\right)^2$



Lowest 1/f if:  $c_{iss} = C_s$

Four noise:  $S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2$

Antenna-referred noise:

1 :  $W = 1.20e-3, L = 1.25e-6, ID = 1.39e-03, S_f = 2.81e-17, f_{ell} = 3.41e+4, C_{iss} = 1.03e-11, IC=2.27e+0.$

# CS input stage design

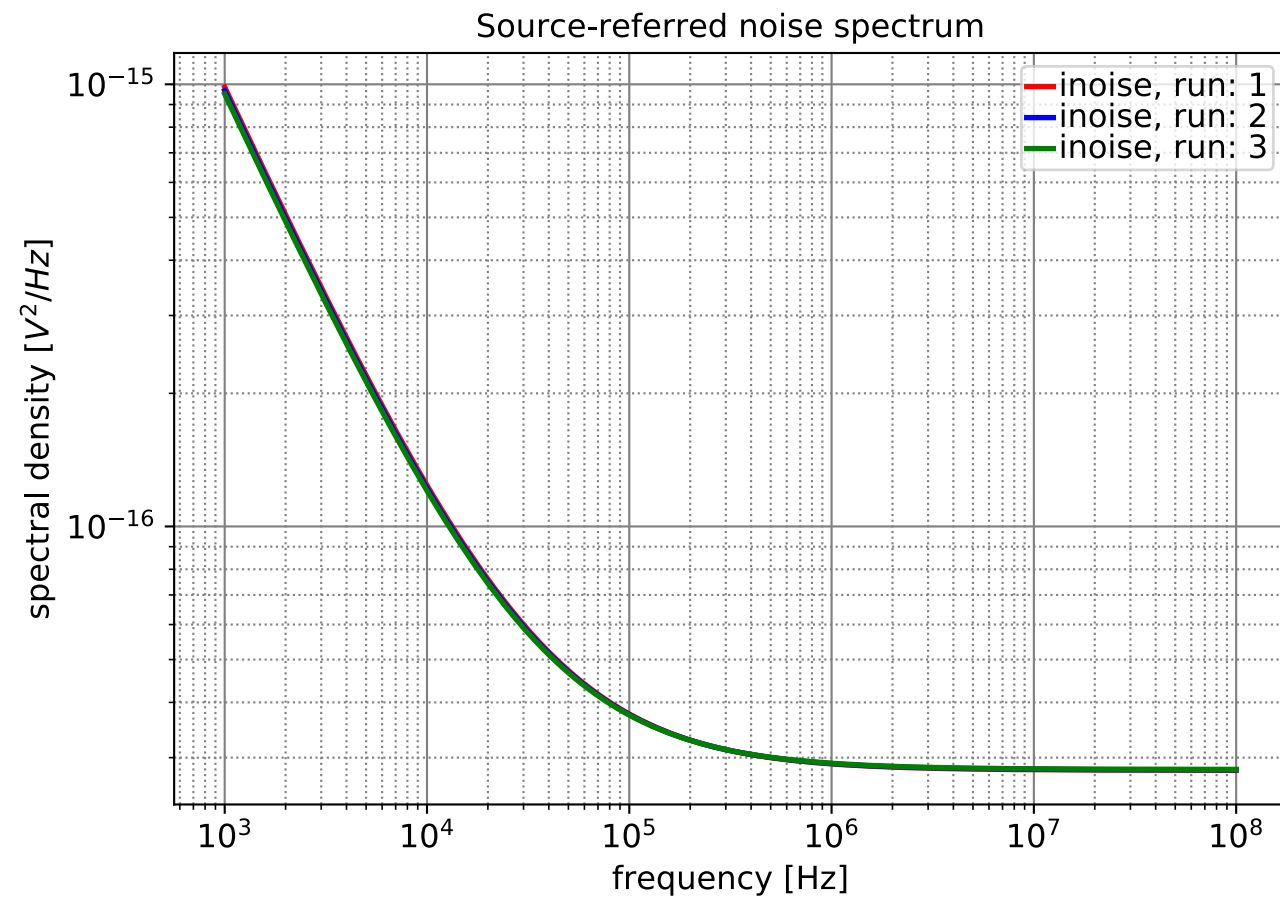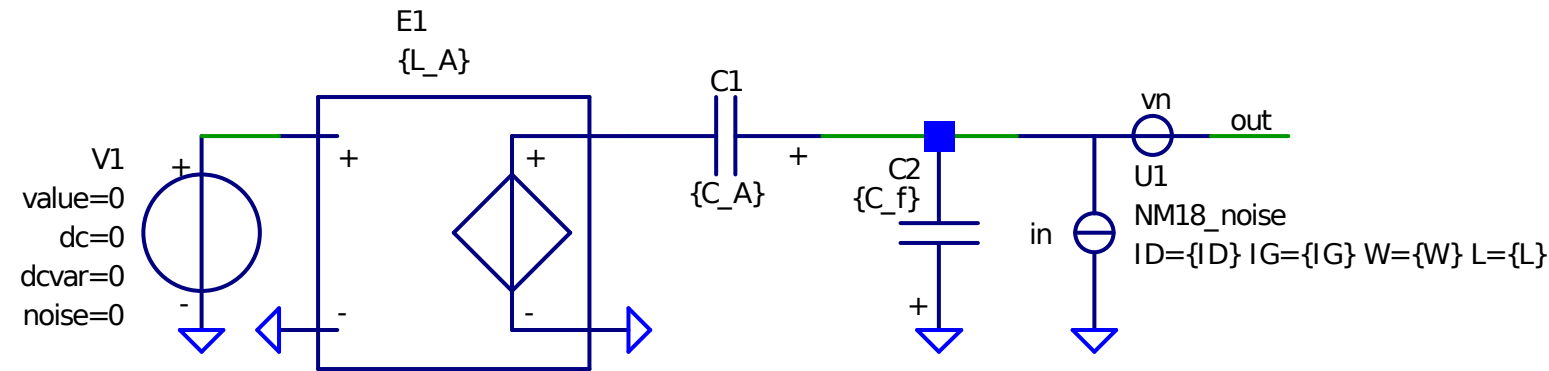

Source-referred noise at the output of E1:

$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2 \left(1 + \frac{f_l}{f}\right)$$

$$f_l = \alpha f_T = \alpha \frac{g_m}{2\pi c_{iss}} \quad \alpha: \text{process parameter}$$

1/f noise: 
$$S_{v_{n_f}} = \frac{2kTn\Gamma\alpha}{\pi f c_{iss}} \left(1 + \frac{c_{iss}}{C_s}\right)^2$$

Lowest 1/f if: 
$$c_{iss} = C_s$$


Four noise: 
$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2$$

Antenna-referred noise:

1 :  $W = 1.20e-3$ ,  $L = 1.25e-6$ ,  $ID = 1.39e-03$ ,  $S_f = 2.81e-17$ ,  $f_{ell} = 3.41e+4$ ,  $C_{iss} = 1.03e-11$ ,  $IC=2.27e+0$ .

2 :  $W = 9.00e-4$ ,  $L = 1.71e-6$ ,  $ID = 2.13e-03$ ,  $S_f = 2.82e-17$ ,  $f_{ell} = 3.34e+4$ ,  $C_{iss} = 1.03e-11$ ,  $IC=6.31e+0$ .

# CS input stage design

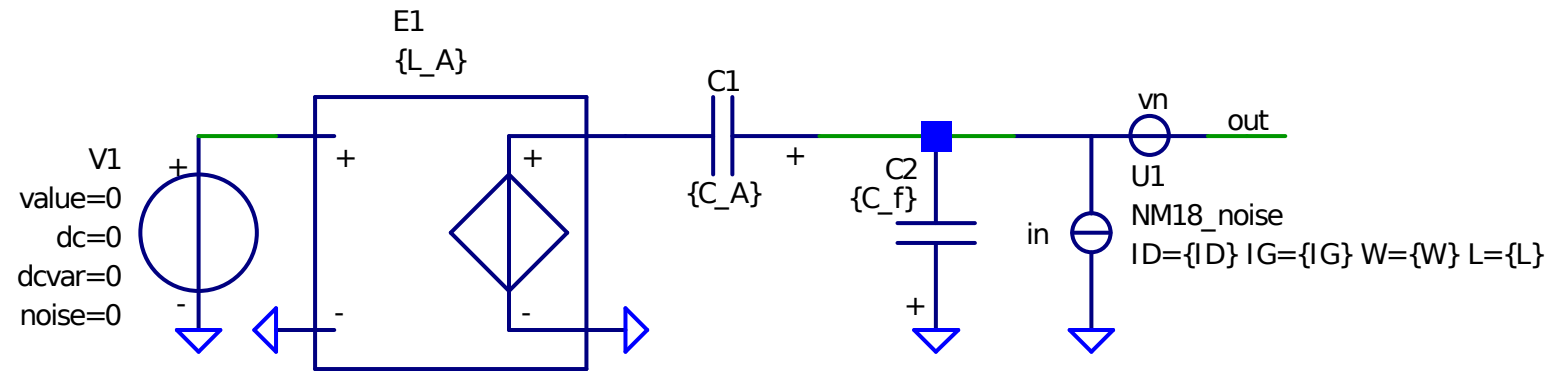

Source-referred noise at the output of E1:


$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2 \left(1 + \frac{f_\ell}{f}\right)$$

$$f_\ell = \alpha f_T = \alpha \frac{g_m}{2\pi c_{iss}} \quad \alpha: \text{process parameter}$$

1/f noise: 
$$S_{v_{n_f}} = \frac{2kTn\Gamma\alpha}{\pi f c_{iss}} \left(1 + \frac{c_{iss}}{C_s}\right)^2$$

Lowest 1/f if: 
$$c_{iss} = C_s$$


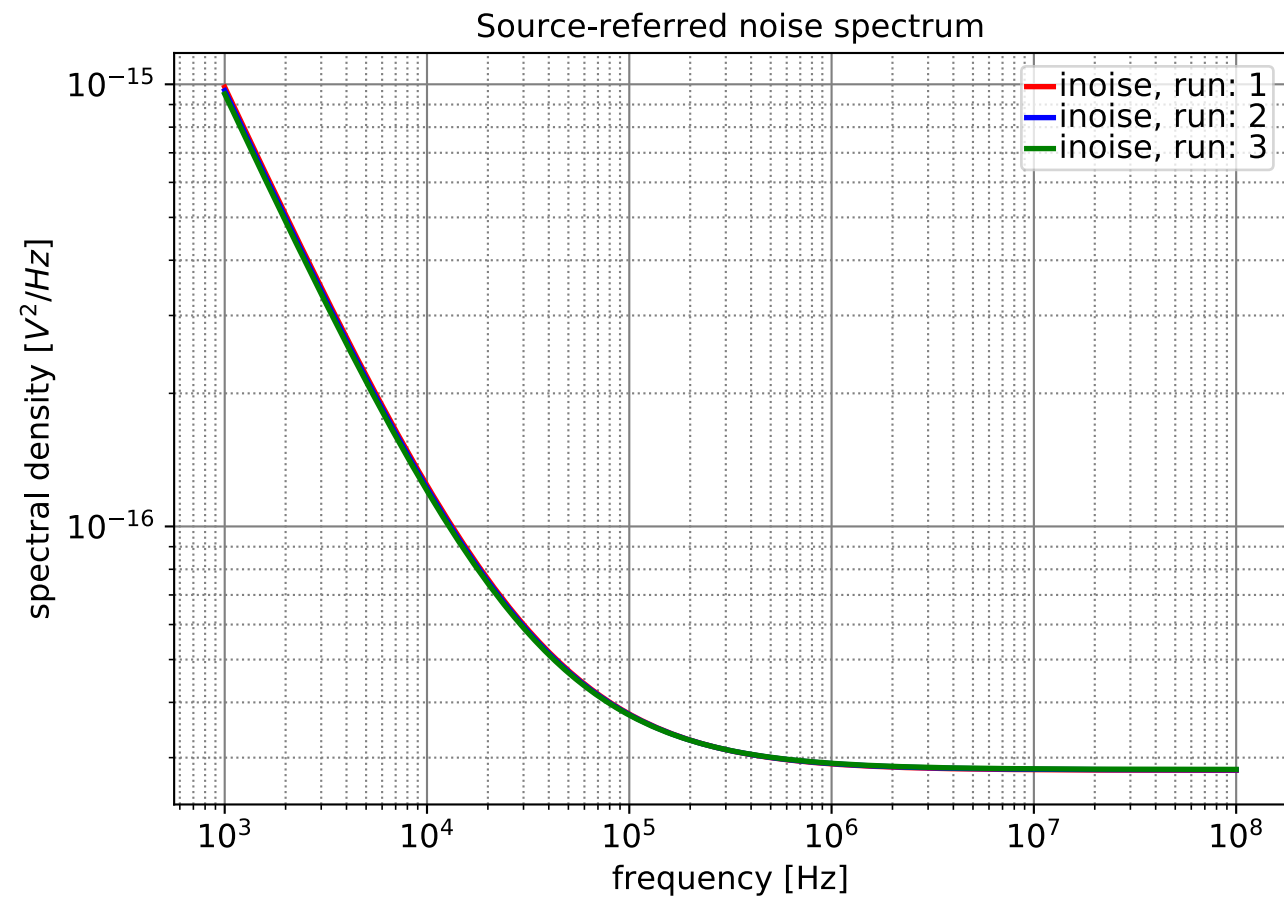
Four noise: 
$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2$$



Antenna-referred noise:

- 1 :  $W = 1.20e-3$ ,  $L = 1.25e-6$ ,  $ID = 1.39e-03$ ,  $S_f = 2.81e-17$ ,  $f_{ell} = 3.41e+4$ ,  $C_{iss} = 1.03e-11$ ,  $IC=2.27e+0$ .
- 2 :  $W = 9.00e-4$ ,  $L = 1.71e-6$ ,  $ID = 2.13e-03$ ,  $S_f = 2.82e-17$ ,  $f_{ell} = 3.34e+4$ ,  $C_{iss} = 1.03e-11$ ,  $IC=6.31e+0$ .
- 3 :  $W = 6.00e-4$ ,  $L = 2.61e-6$ ,  $ID = 4.50e-03$ ,  $S_f = 2.82e-17$ ,  $f_{ell} = 3.27e+4$ ,  $C_{iss} = 1.03e-11$ ,  $IC=3.06e+1$ .

# CS input stage design

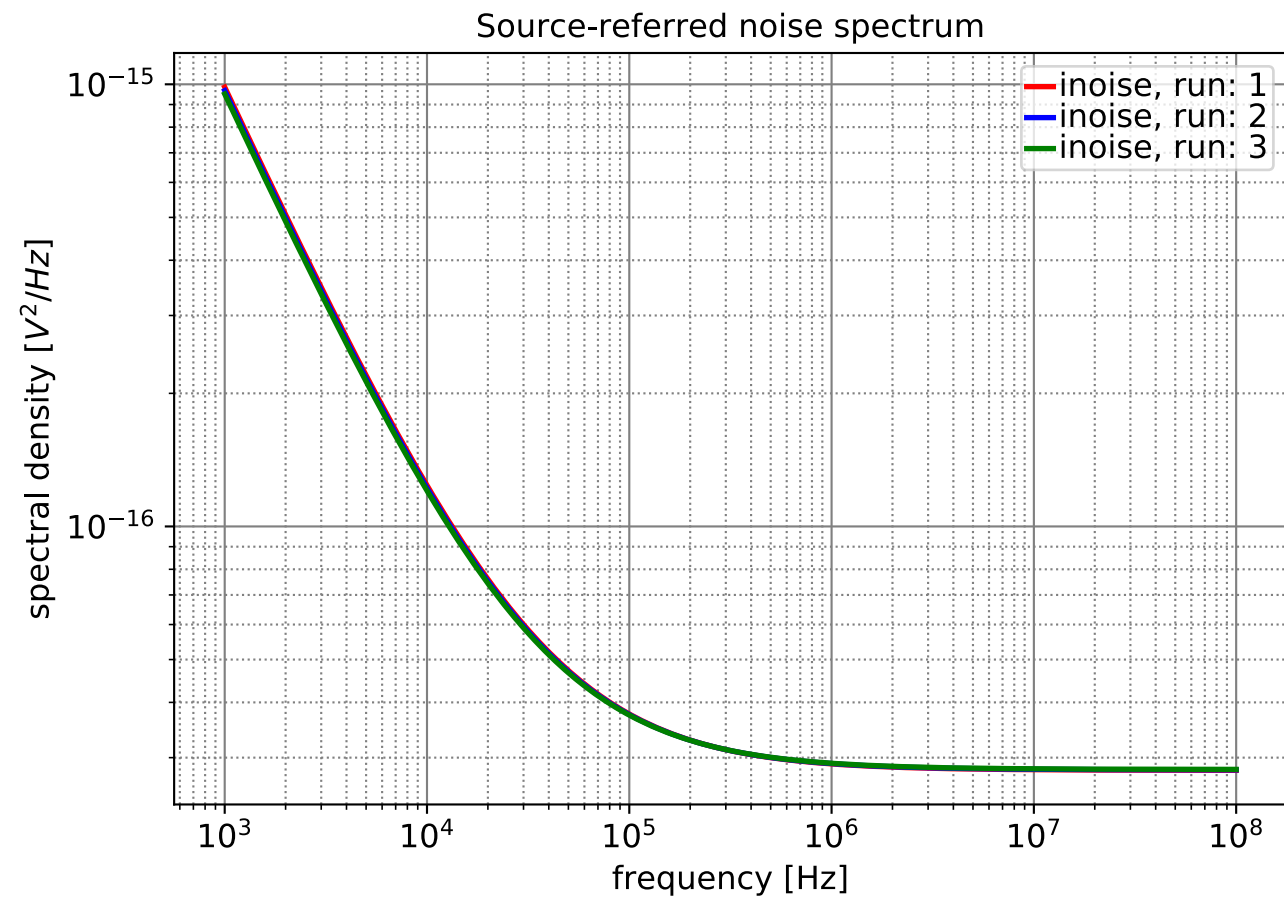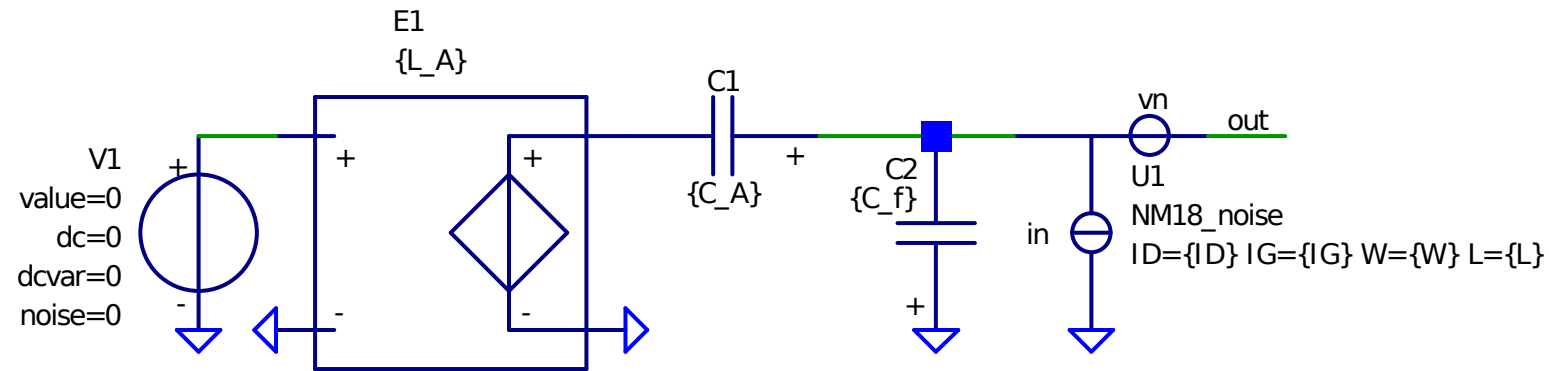

Source-referred noise at the output of E1:

$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2 \left(1 + \frac{f_\ell}{f}\right)$$

$$f_\ell = \alpha f_T = \alpha \frac{g_m}{2\pi c_{iss}} \quad \alpha: \text{process parameter}$$

1/f noise: 
$$S_{v_{n_f}} = \frac{2kTn\Gamma\alpha}{\pi f c_{iss}} \left(1 + \frac{c_{iss}}{C_s}\right)^2$$

Lowest 1/f if: 
$$c_{iss} = C_s$$

Floor noise: 
$$S_{v_n} = \frac{4kTn\Gamma}{g_m} \left(1 + \frac{c_{iss}}{C_s}\right)^2$$

Antenna-referred noise:

- 1 :  $W = 1.20e-3$ ,  $L = 1.25e-6$ ,  $ID = 1.39e-03$ ,  $S_f = 2.81e-17$ ,  $f_{ell} = 3.41e+4$ ,  $C_{iss} = 1.03e-11$ ,  $IC=2.27e+0$ .
- 2 :  $W = 9.00e-4$ ,  $L = 1.71e-6$ ,  $ID = 2.13e-03$ ,  $S_f = 2.82e-17$ ,  $f_{ell} = 3.34e+4$ ,  $C_{iss} = 1.03e-11$ ,  $IC=6.31e+0$ .
- 3 :  $W = 6.00e-4$ ,  $L = 2.61e-6$ ,  $ID = 4.50e-03$ ,  $S_f = 2.82e-17$ ,  $f_{ell} = 3.27e+4$ ,  $C_{iss} = 1.03e-11$ ,  $IC=3.06e+1$ .


# **Structured Electronic Design**

Step 4


Feasibility load drive requirements

*Anton J.M. Montagne*

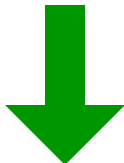
Design of independent performance aspects



interaction between design aspects

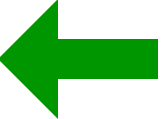

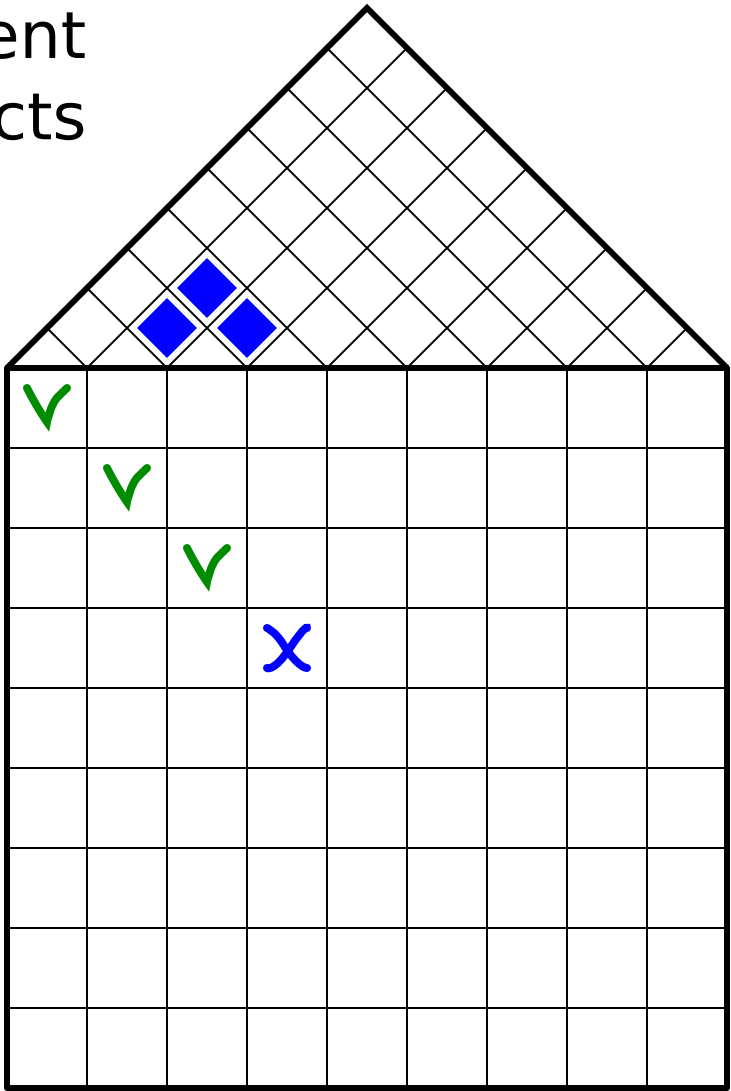
Setting up specifications  
Design of amplifier type: A, B, C, D  
Feasibility of noise (temperature drift) specifications  
Feasibility of static and dynamic drive requirements



SLiCAP  
SLiCAP  
SLiCAP  
LTspice


Function, performance,  
costs and environment  
Feedback configuration  
Controller input stage  
Controller output stage

design aspects

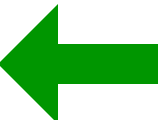




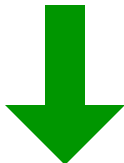Design of independent performance aspects




interaction between design aspects

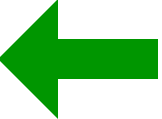

Setting up specifications  
Design of amplifier type: A, B, C, D  
Feasibility of noise (temperature drift) specifications  
Feasibility of static and dynamic drive requirements


SLiCAP  
SLiCAP  
SLiCAP  
LTspice

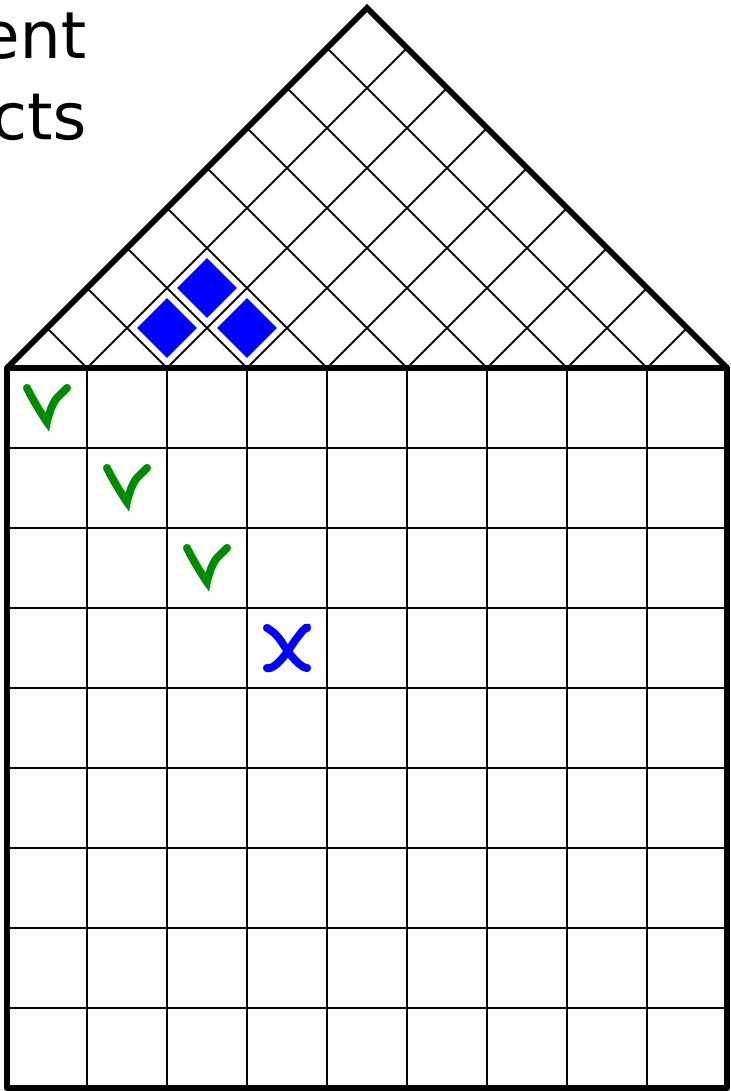


**Design of the feedback network and the output stage of the controller**

Function, performance, costs and environment  
Feedback configuration  
Controller input stage  
Controller output stage

design aspects

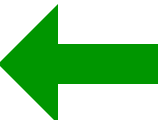


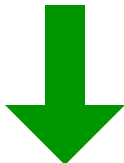Design of independent performance aspects



interaction between design aspects

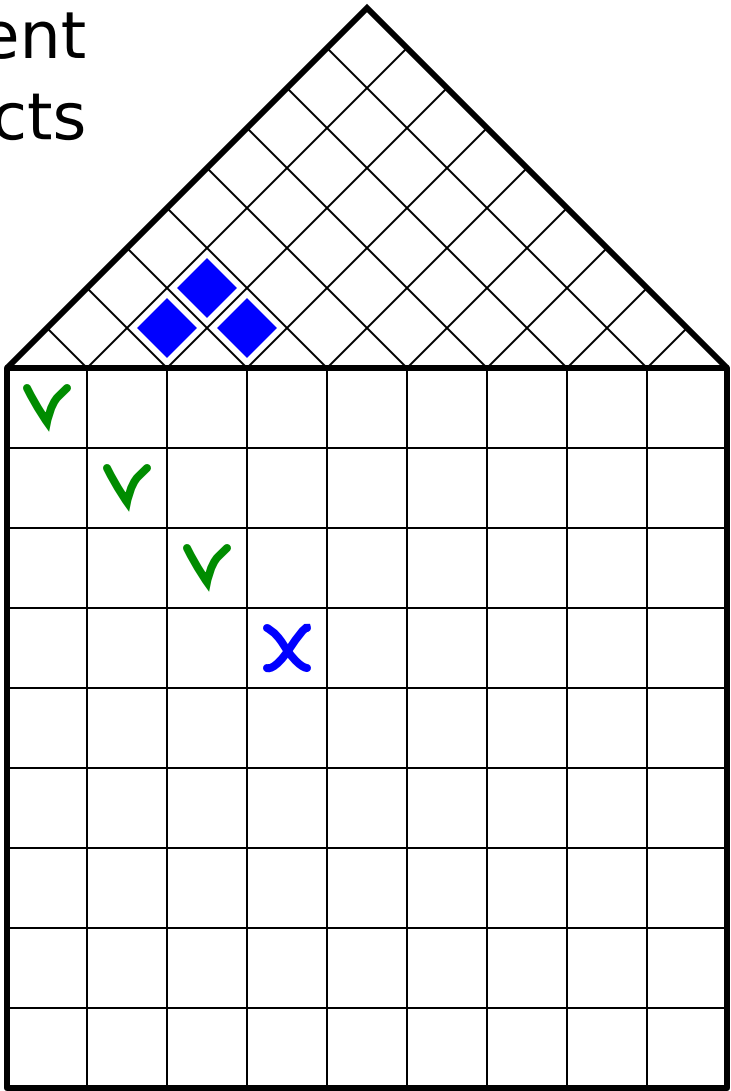Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice


**Design of the feedback network and the output stage of the controller**

**Design of the active antenna:**

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage


design aspects

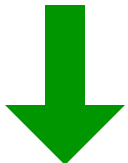Design of independent performance aspects



interaction between design aspects

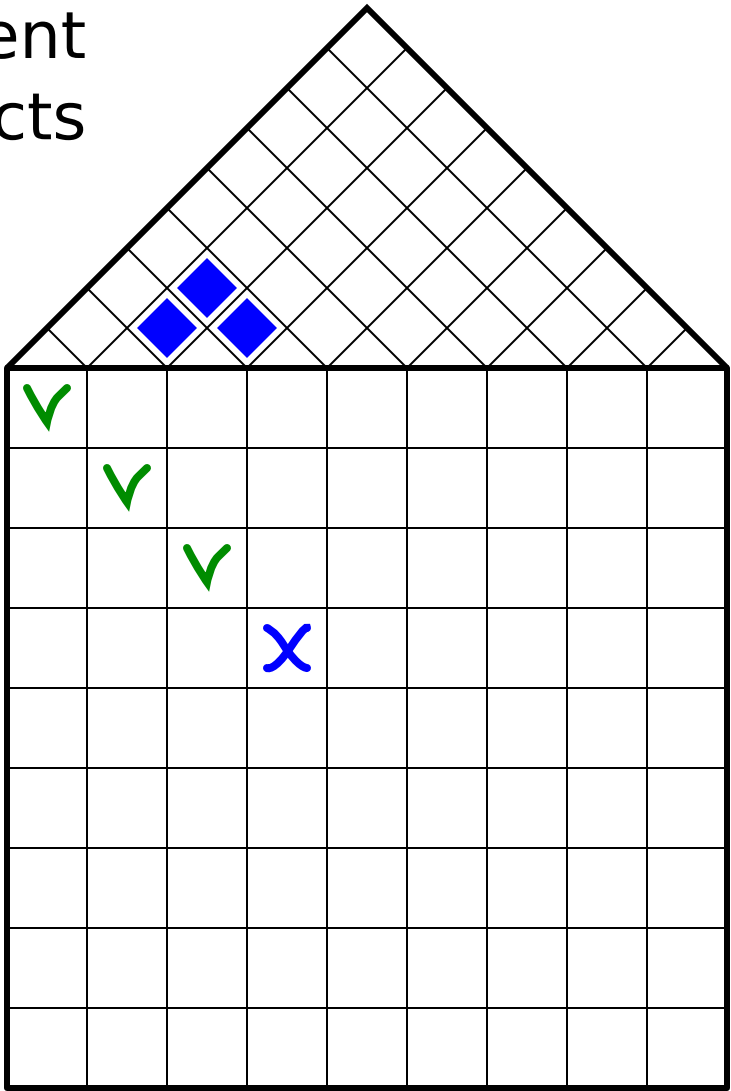*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice

**Design of the feedback network and the output stage of the controller**


**Design of the active antenna:**

Design a CS stage with sufficient static and dynamic drive capability

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage

design aspects

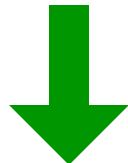
Design of independent performance aspects



interaction between design aspects

Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements

SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice

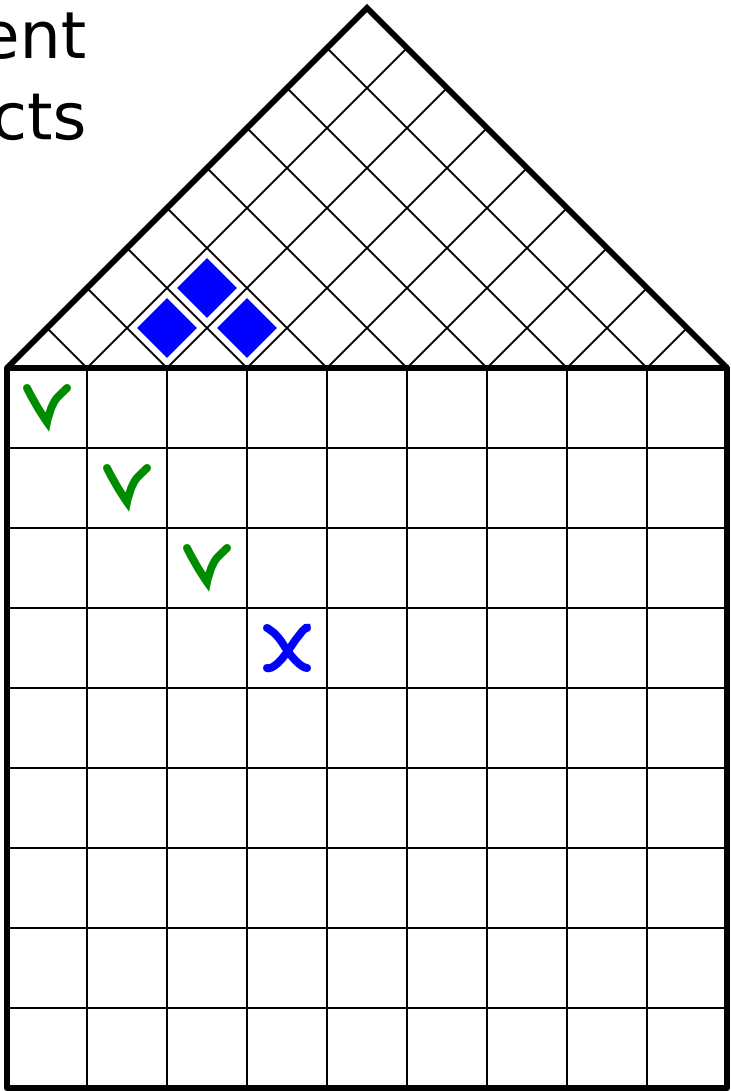

**Design of the feedback network and the output stage of the controller**

**Design of the active antenna:**


Design a CS stage with sufficient static and dynamic drive capability

Determine valid ranges for:  $I_{DS}$ ,  $V_{DS}$ ,  $W$ ,  $L$ ,  $M$


Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage

design aspects

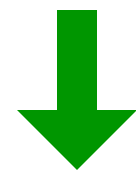Design of independent performance aspects



interaction between design aspects

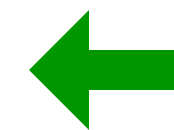


Setting up specifications

Design of amplifier type: A, B, C, D

Feasibility of noise (temperature drift) specifications

Feasibility of static and dynamic drive requirements

SLiCAP  
SLiCAP  
SLiCAP  
LTspice

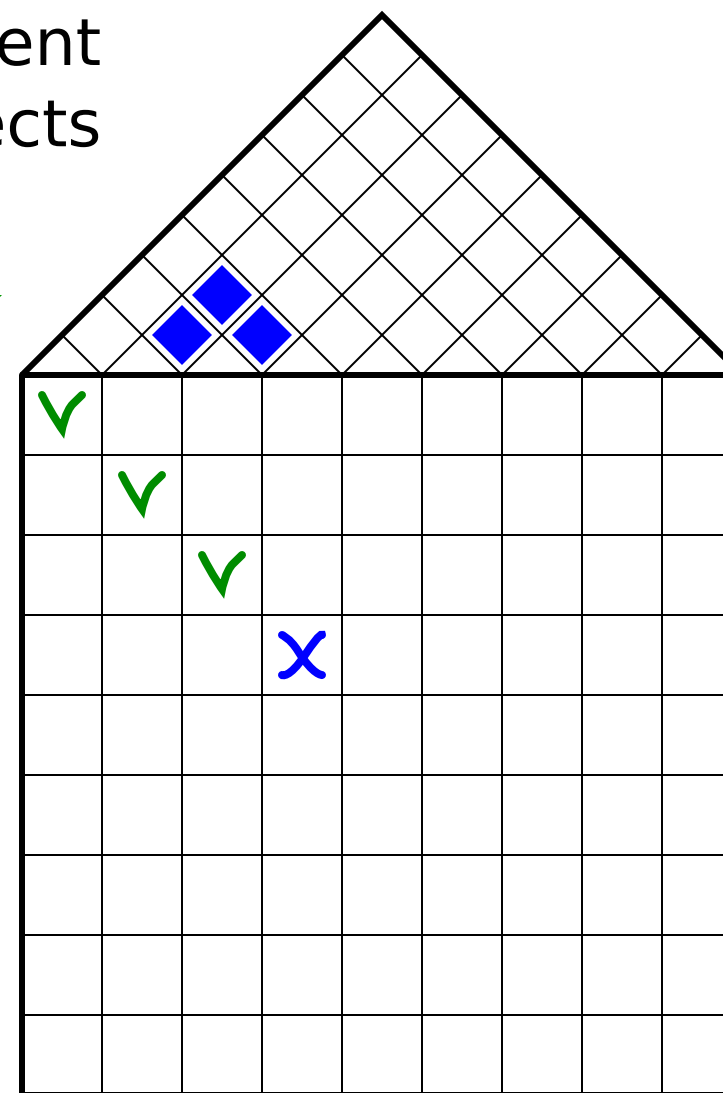

## Design of the feedback network and the output stage of the controller

### Design of the active antenna:


Design a CS stage with sufficient static and dynamic drive capability

Determine valid ranges for:  $I_{DS}$ ,  $V_{DS}$ ,  $W$ ,  $L$ ,  $M$


The performance-to-cost ratio can be improved through application of balancing:

Function, performance, costs and environment  
Feedback configuration  
Controller input stage  
Controller output stage

design aspects

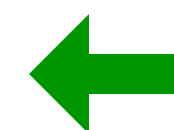

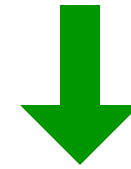
Design of independent performance aspects



interaction between design aspects

Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements

SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice

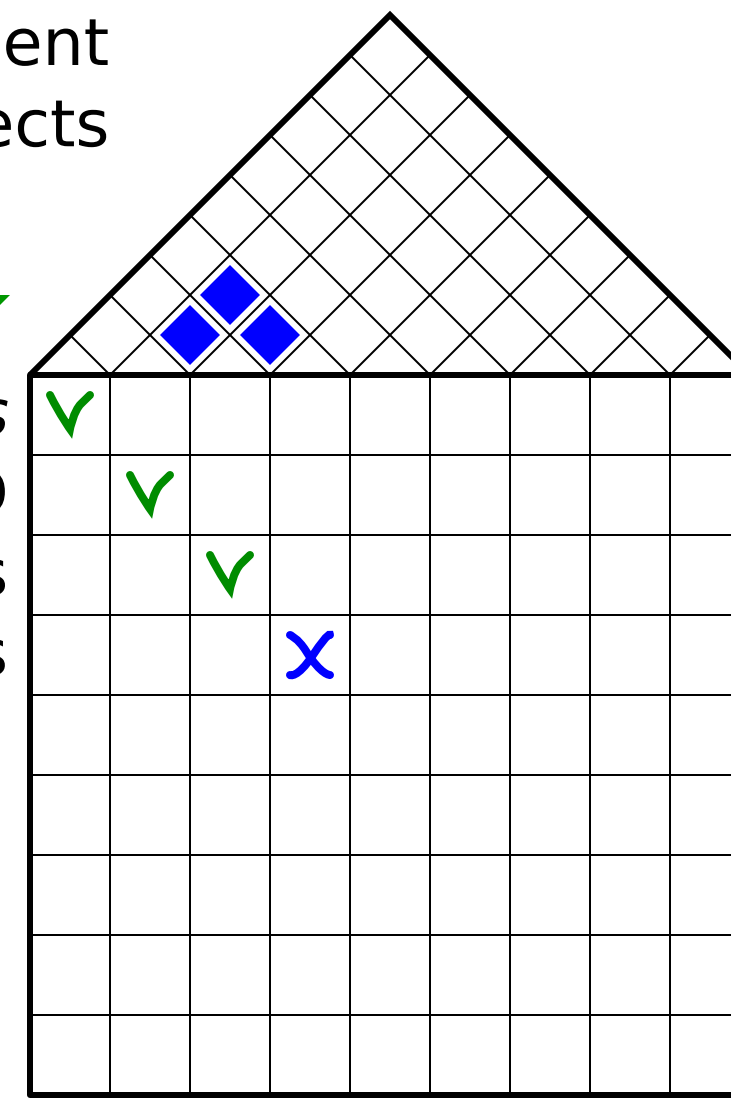

**Design of the feedback network and the output stage of the controller**

**Design of the active antenna:**

Design a CS stage with sufficient static and dynamic drive capability

Determine valid ranges for:  $I_{DS}$ ,  $V_{DS}$ ,  $W$ ,  $L$ ,  $M$


The performance-to-cost ratio can be improved through application of balancing:

Complementary-parallel or push-pull stage.

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage


design aspects

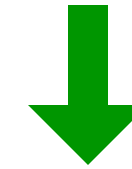Design of independent performance aspects



interaction between design aspects

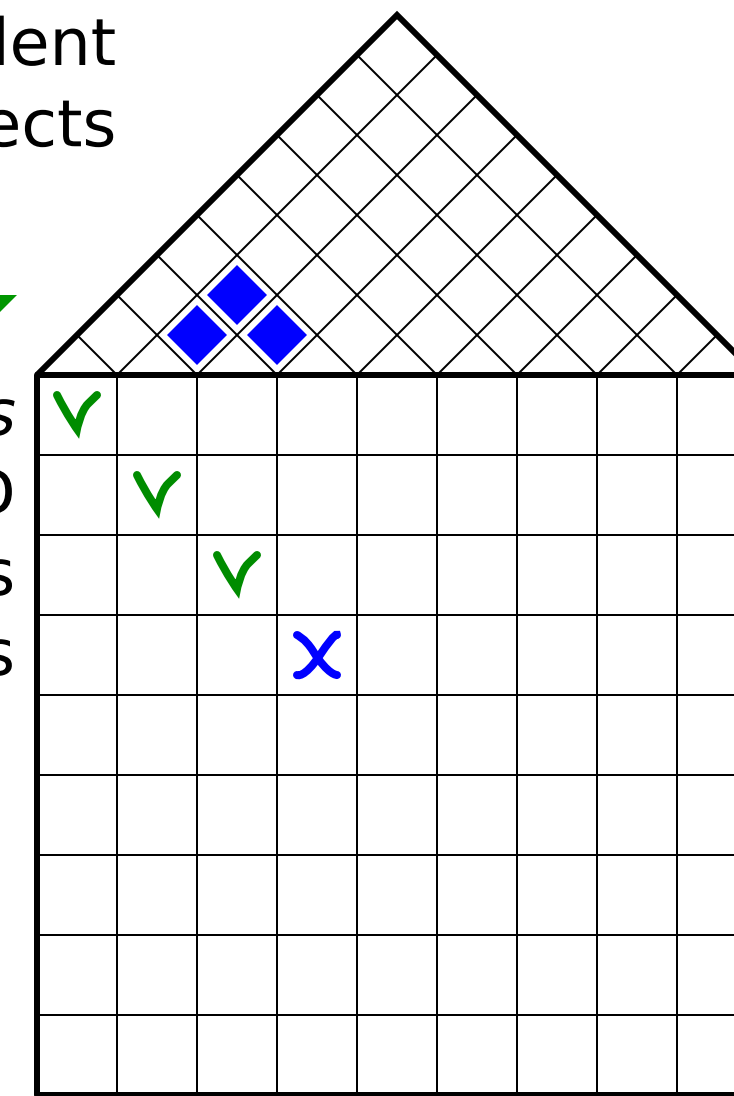Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice

**Design of the feedback network and the output stage of the controller**

**Design of the active antenna:**

Design a CS stage with sufficient static and dynamic drive capability

Determine valid ranges for:  $I_{DS}$ ,  $V_{DS}$ ,  $W$ ,  $L$ ,  $M$

The performance-to-cost ratio can be improved through application of balancing:

Complementary-parallel or push-pull stage.


Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage

design aspects


# CS output stage design



# CS output stage design

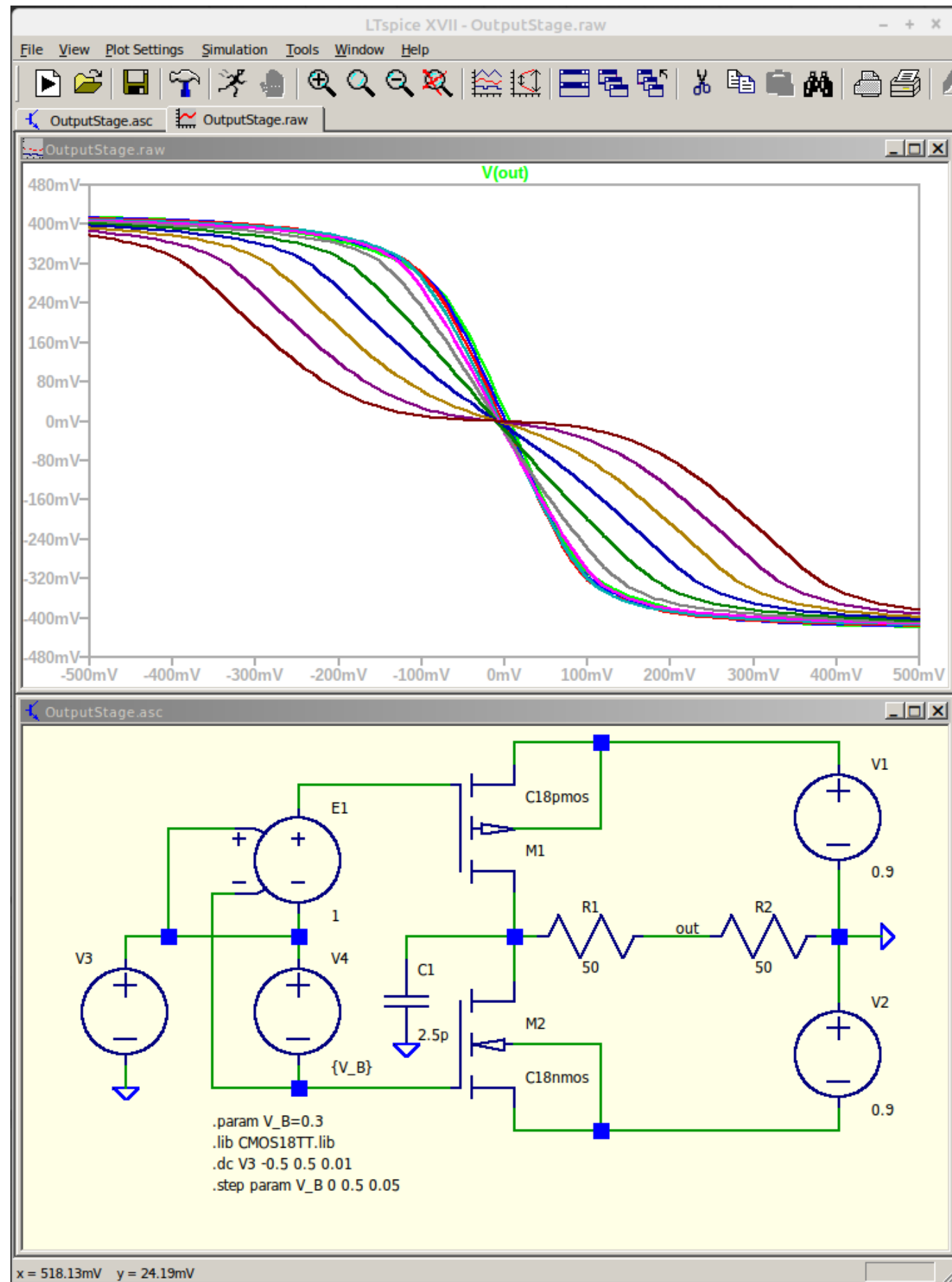


# CS output stage design

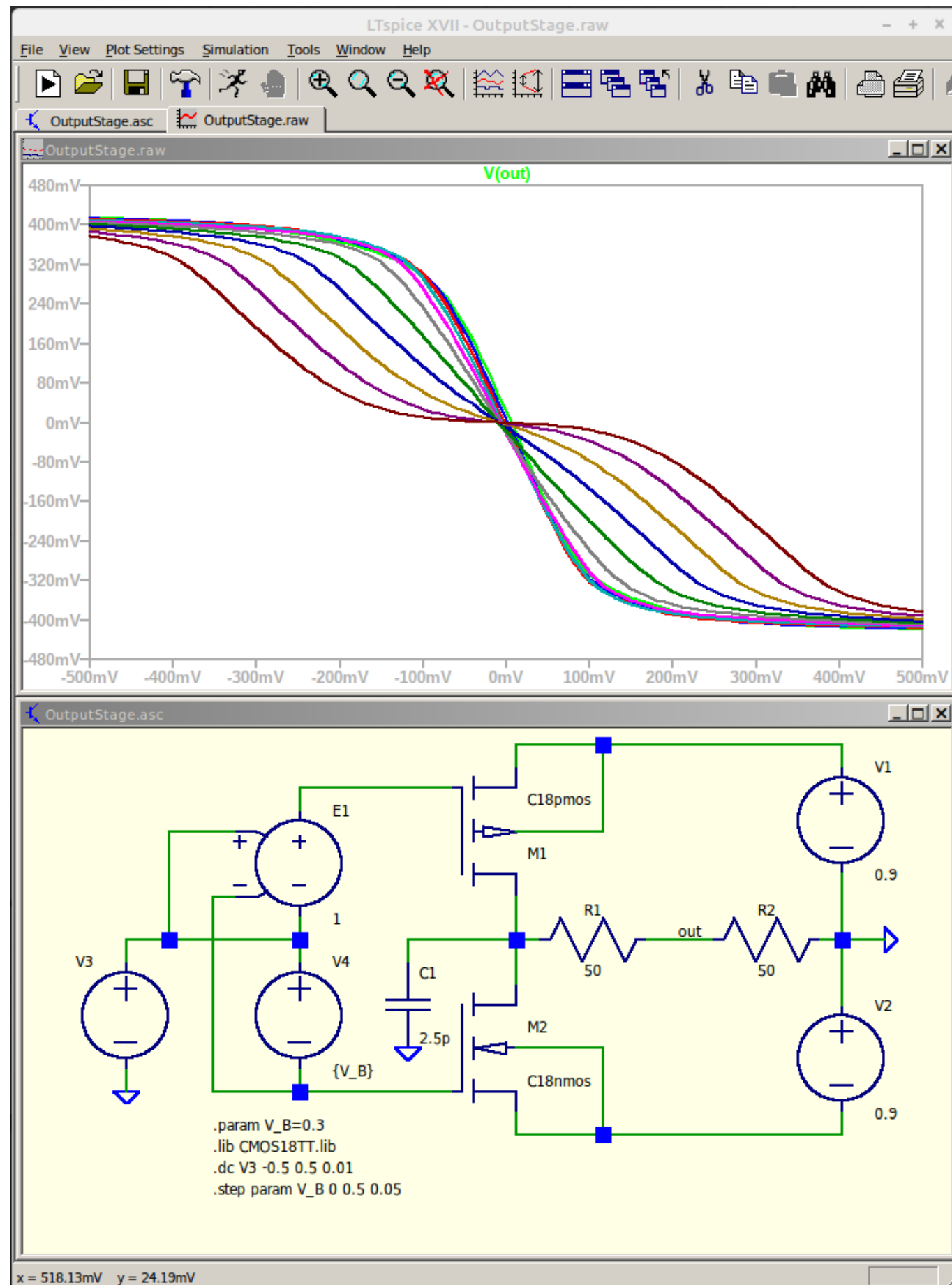

Smallest value for  $L$ : 180nm


# CS output stage design

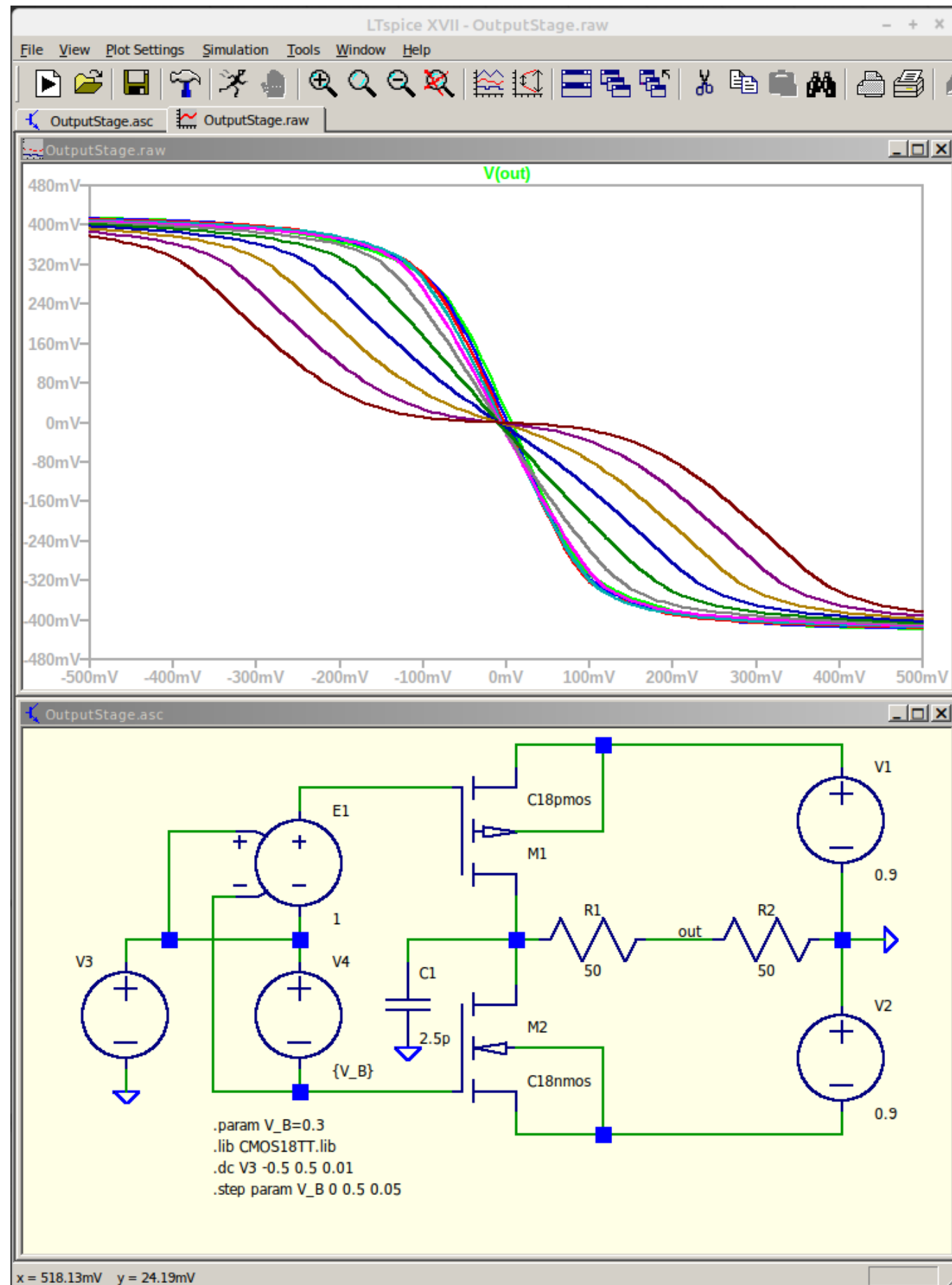

Smallest value for L: 180nm

$$W_{\text{pmos}}/W_{\text{nmos}} = 1/\text{mobility\_ratio}$$

# CS output stage design

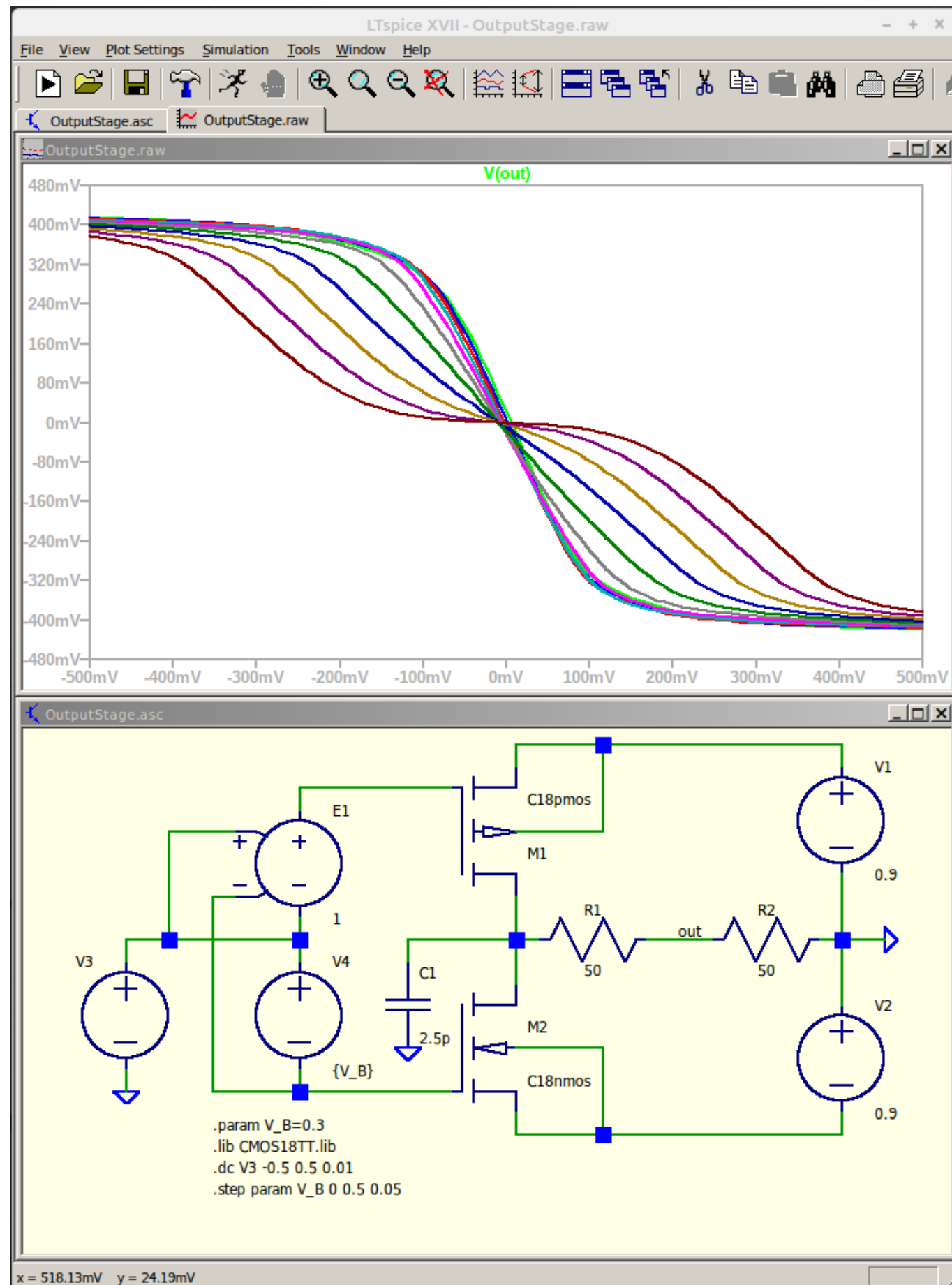


Smallest value for L: 180nm

$W_{pmos}/W_{nmos} = 1/mobility\_ratio$

Determine W and M such that the load can be driven with a sufficiently small drive (V3)

# CS output stage design

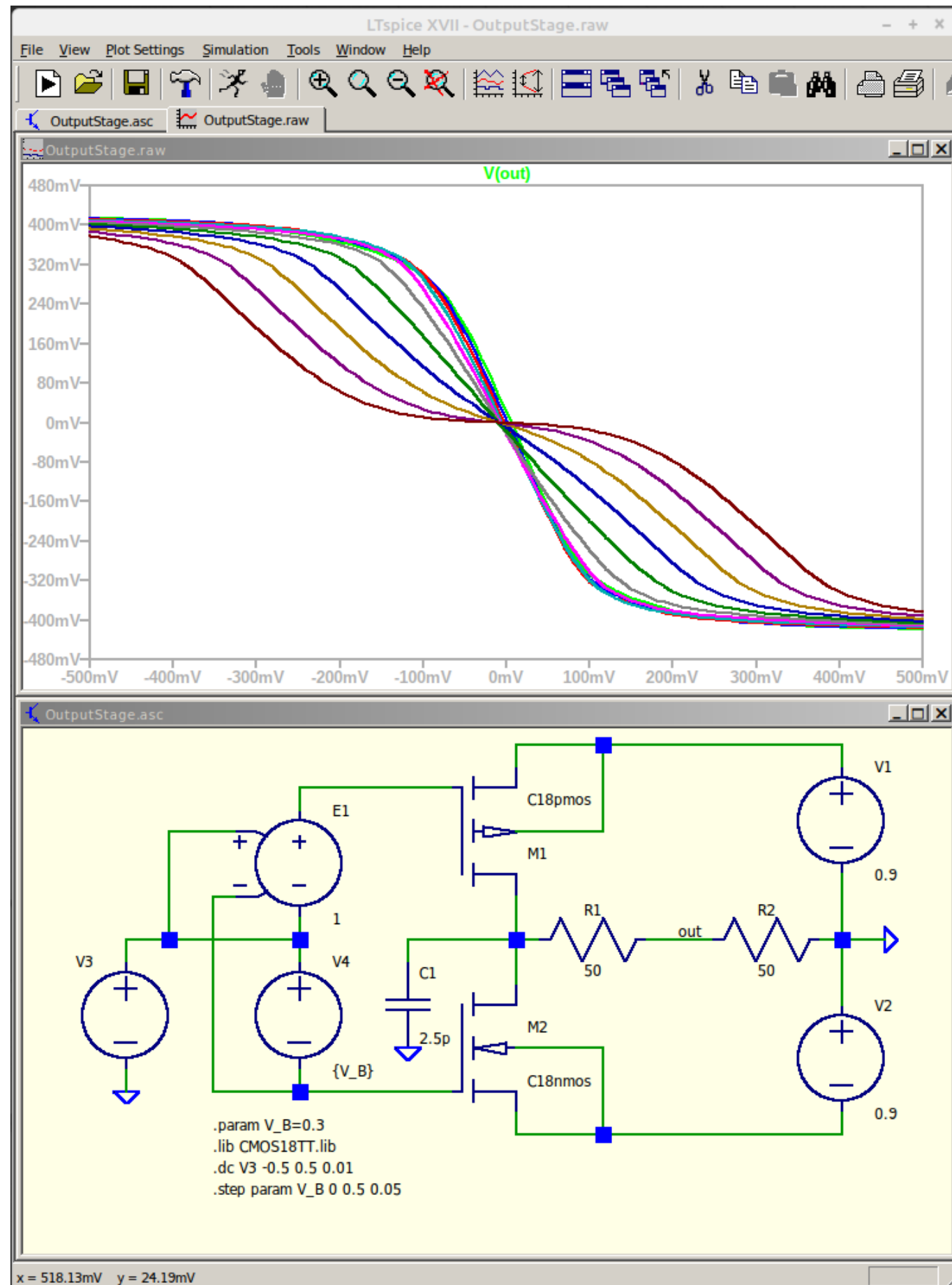


Smallest value for L: 180nm

$W_{pmos}/W_{nmos} = 1/mobility\_ratio$

Determine W and M such that the load can be driven with a sufficiently small drive (V3)

PMOS:  $W=40\mu$ ,  $M=10$

# CS output stage design

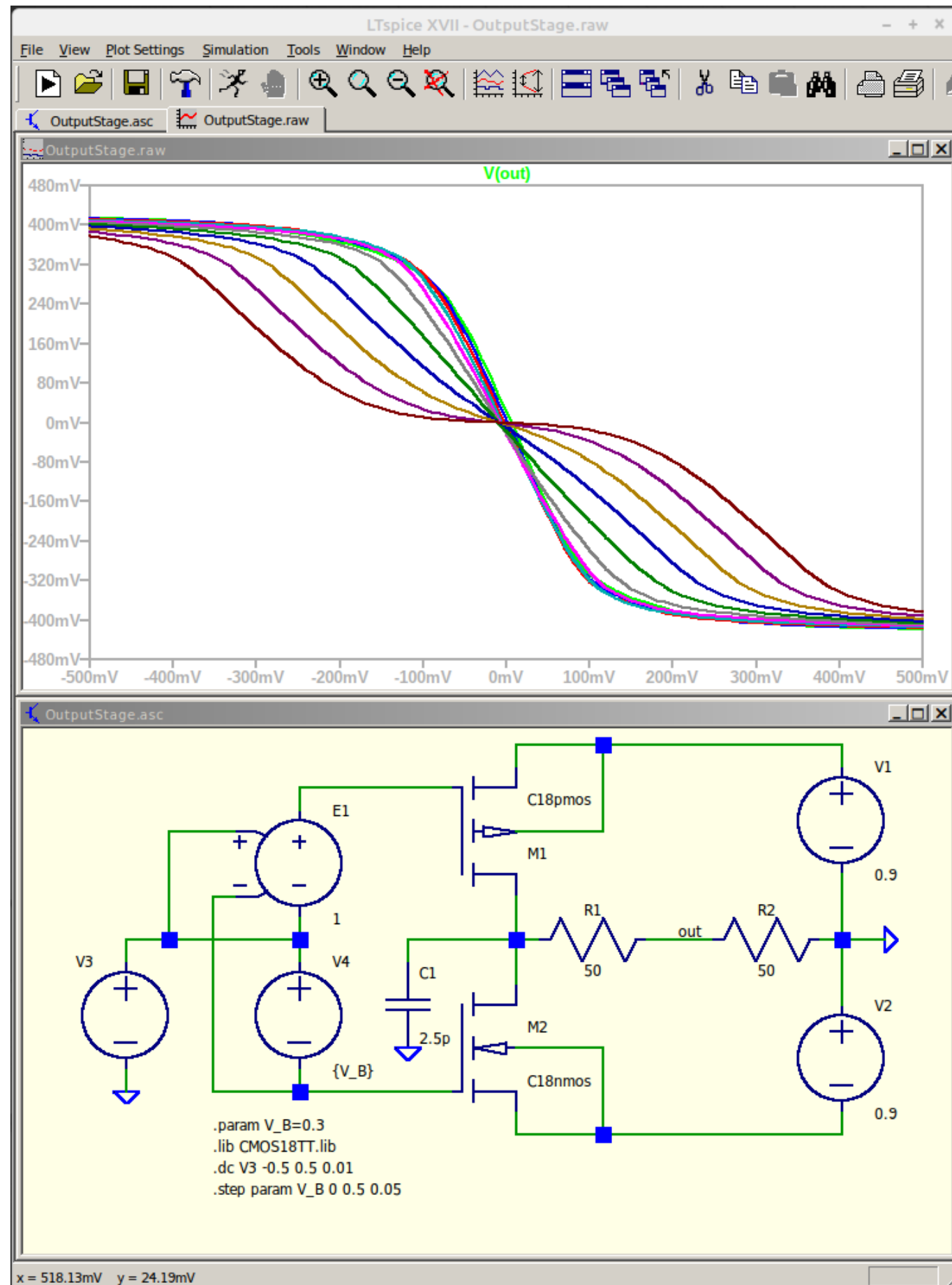

Smallest value for L: 180nm


$W_{pmos}/W_{nmos} = 1/mobility\_ratio$

Determine W and M such that the load can be driven with a sufficiently small drive (V3)

PMOS:  $W=40\mu$ ,  $M=10$

NMOS:  $W=40\mu$ ,  $M=3$

# CS output stage design

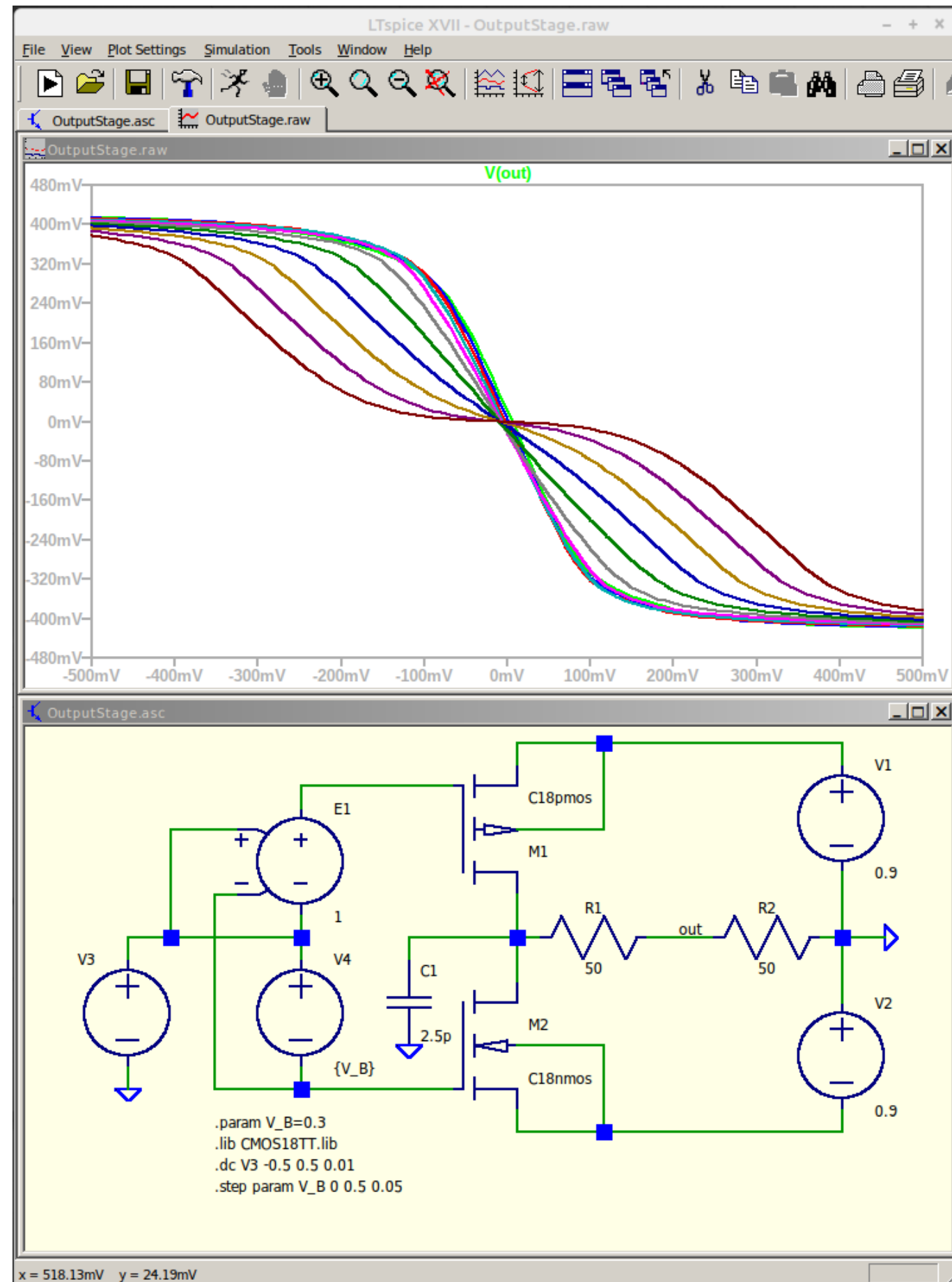

Smallest value for L: 180nm

$W_{\text{pmos}}/W_{\text{nmos}} = 1/\text{mobility\_ratio}$


Determine W and M such that the load can be driven with a sufficiently small drive (V3)

PMOS:  $W=40\mu$ ,  $M=10$

NMOS:  $W=40\mu$ ,  $M=3$

Bias voltage 0.2V

# CS output stage design

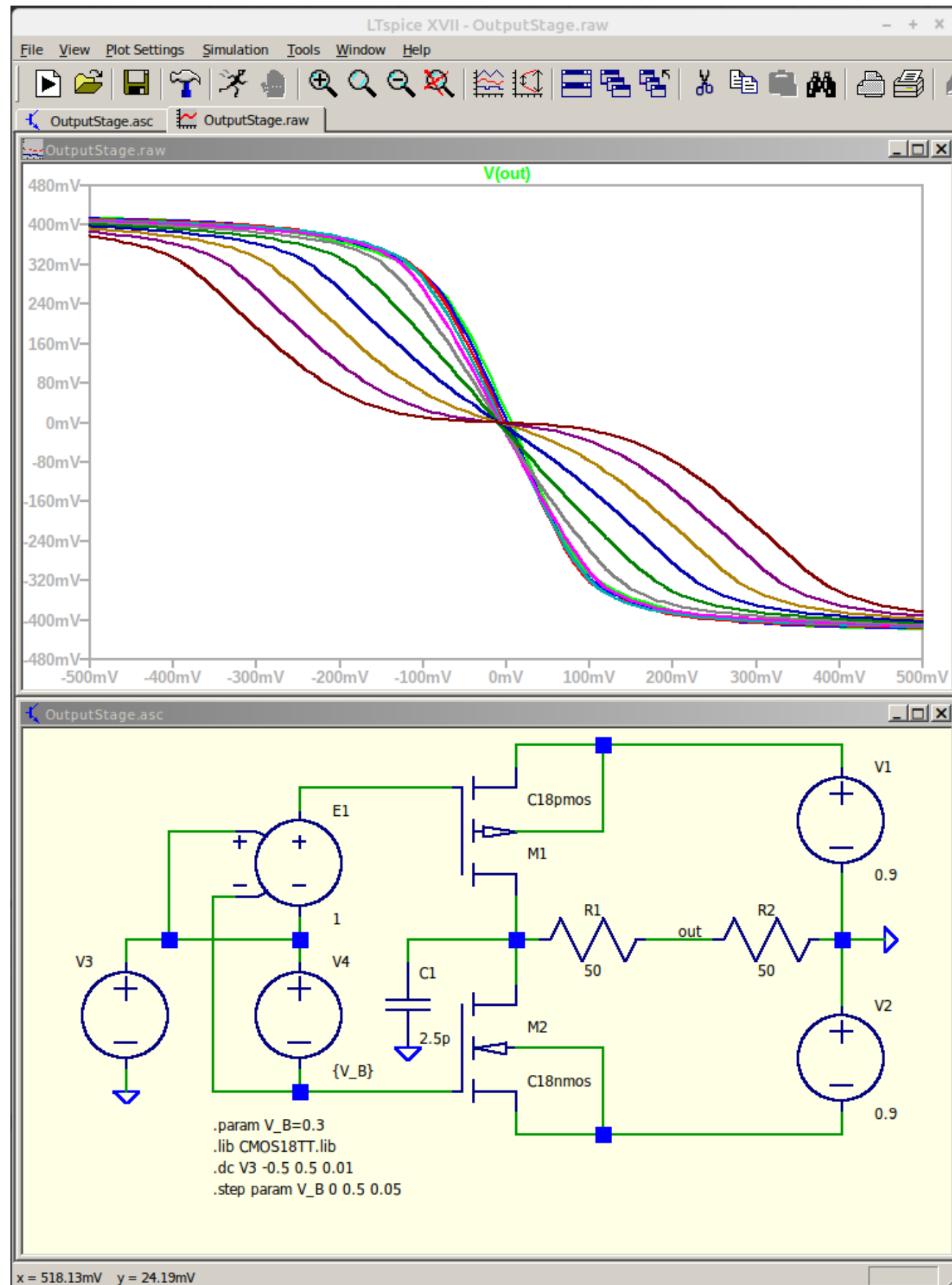

Smallest value for L: 180nm

$W_{\text{pmos}}/W_{\text{nmos}} = 1/\text{mobility\_ratio}$

Determine W and M such that the load can be driven with a sufficiently small drive (V3)

PMOS:  $W=40\mu$ ,  $M=10$


NMOS:  $W=40\mu$ ,  $M=3$

Bias voltage 0.2V

Quiescent current 1mA



# CS output stage design

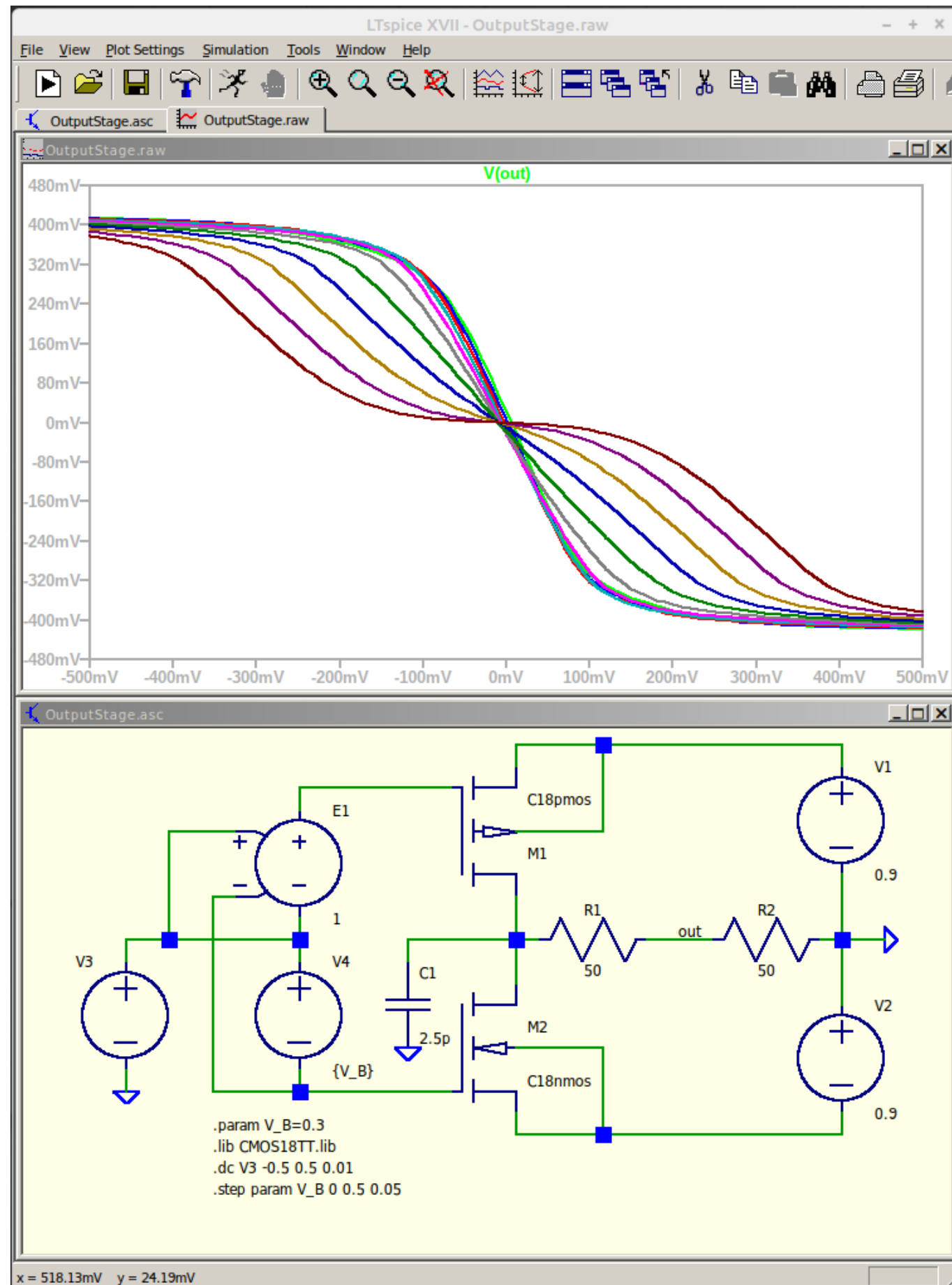

Smallest value for L: 180nm

$W_{\text{pmos}}/W_{\text{nmos}} = 1/\text{mobility\_ratio}$

Determine W and M such that the load can be driven with a sufficiently small drive (V3)

PMOS:  $W=40\mu$ ,  $M=10$


NMOS:  $W=40\mu$ ,  $M=3$

Bias voltage 0.2V

Quiescent current 1mA

Drive requirement +/- 0.2V

# CS output stage design

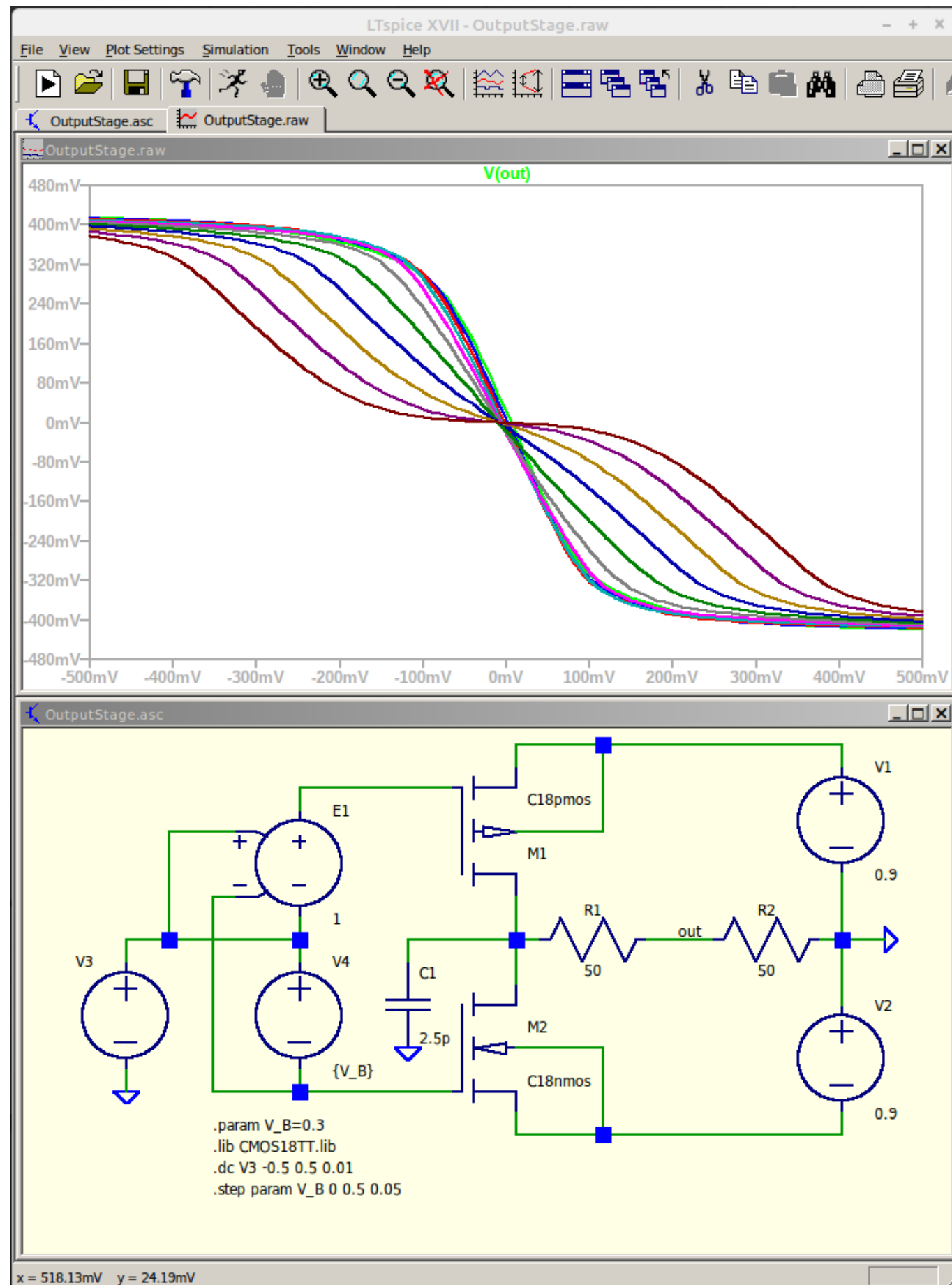

Smallest value for L: 180nm

$W_{\text{pmos}}/W_{\text{nmos}} = 1/\text{mobility\_ratio}$

Determine W and M such that the load can be driven with a sufficiently small drive (V3)

PMOS:  $W=40\mu$ ,  $M=10$

NMOS:  $W=40\mu$ ,  $M=3$

Bias voltage 0.2V

Quiescent current 1mA

Drive requirement +/- 0.2V


# **Structured Electronic Design**

## Step 5

Design of mid-band accuracy and bandwidth


*Anton J.M. Montagne*

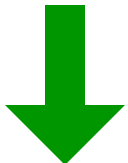Design of independent performance aspects



interaction between design aspects

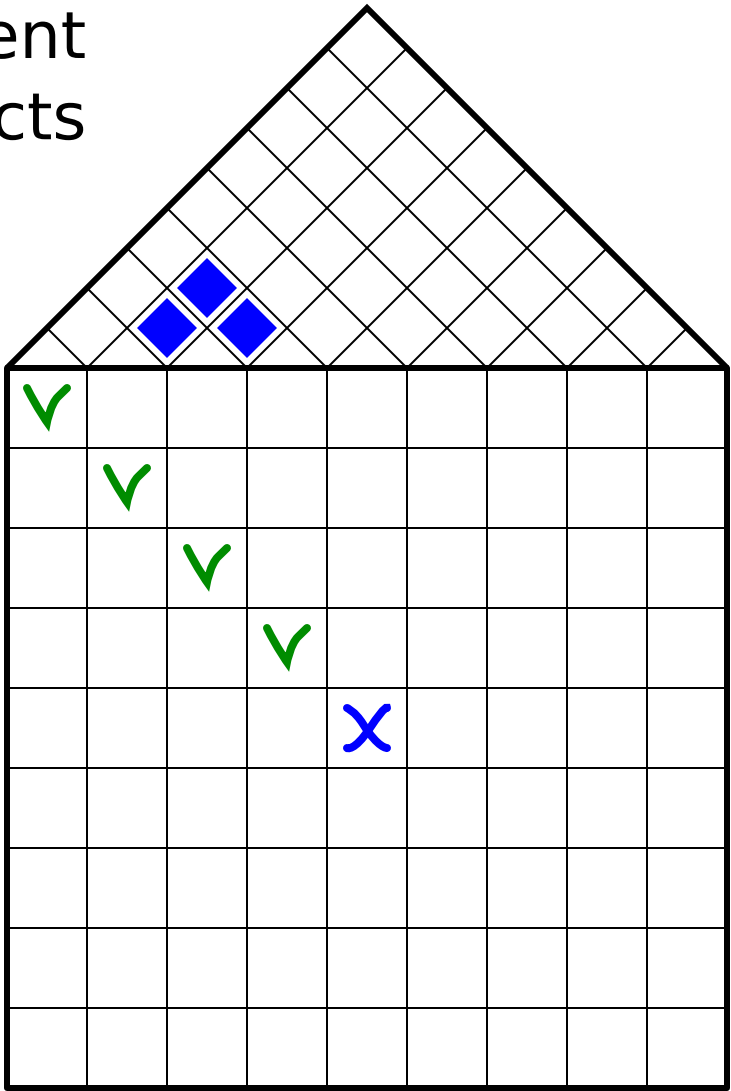Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth




SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP

Function, performance,  
 costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product

design aspects

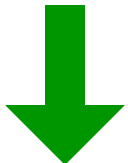
Design of independent performance aspects



interaction between design aspects

*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth

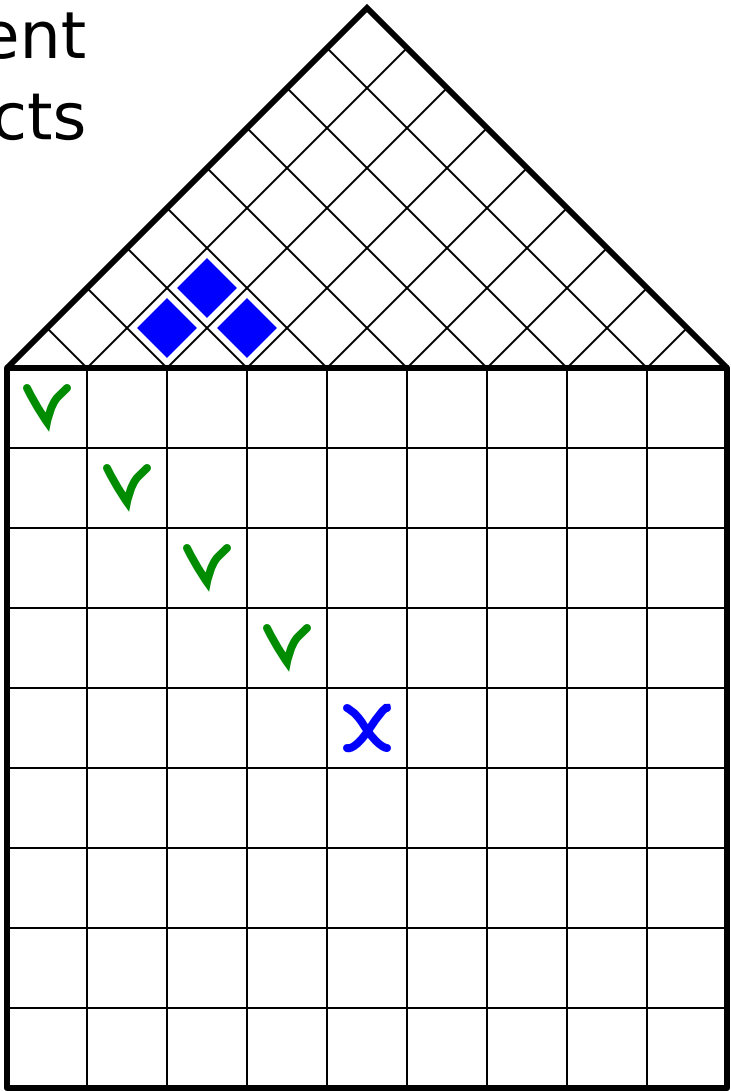SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP




**Design of the number of stages of the controller**

Function, performance,  
 costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product


design aspects

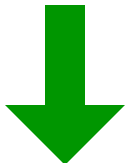Design of independent performance aspects



interaction between design aspects

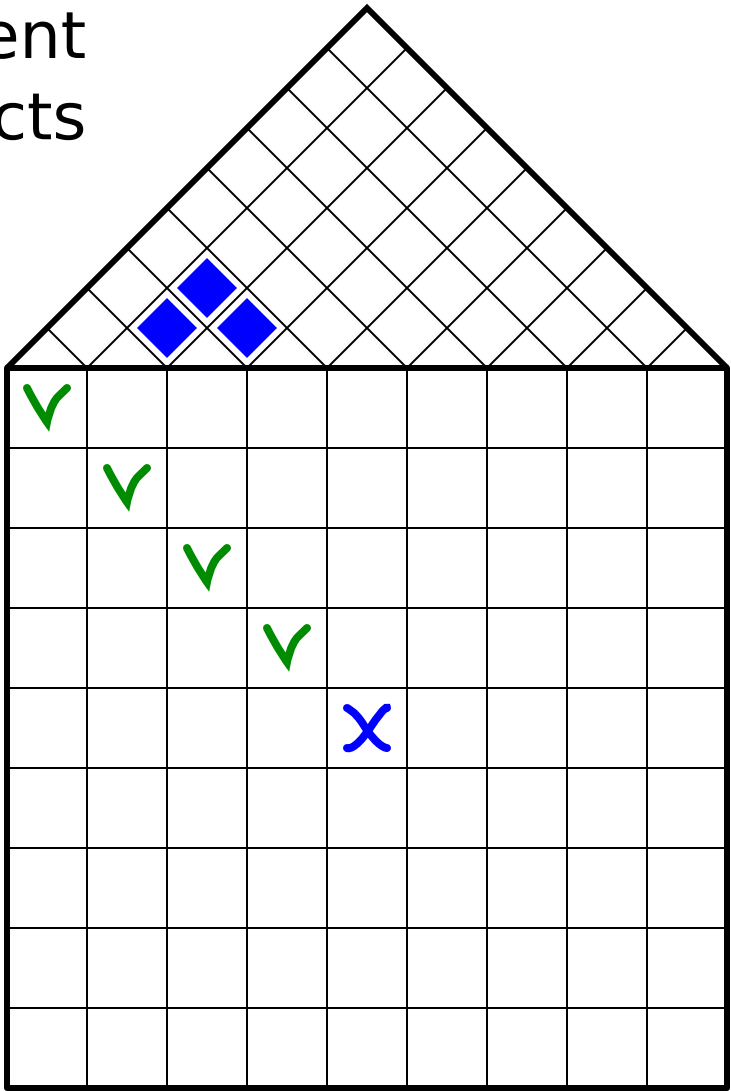*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP


**Design of the number of stages of the controller**

Determine the number of stages required for a sufficiently large mid-band (or DC) loop gain and loop gain-poles product.

*Function, performance, costs and environment*  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product


design aspects

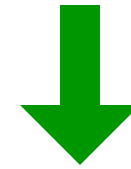Design of independent performance aspects



interaction between design aspects

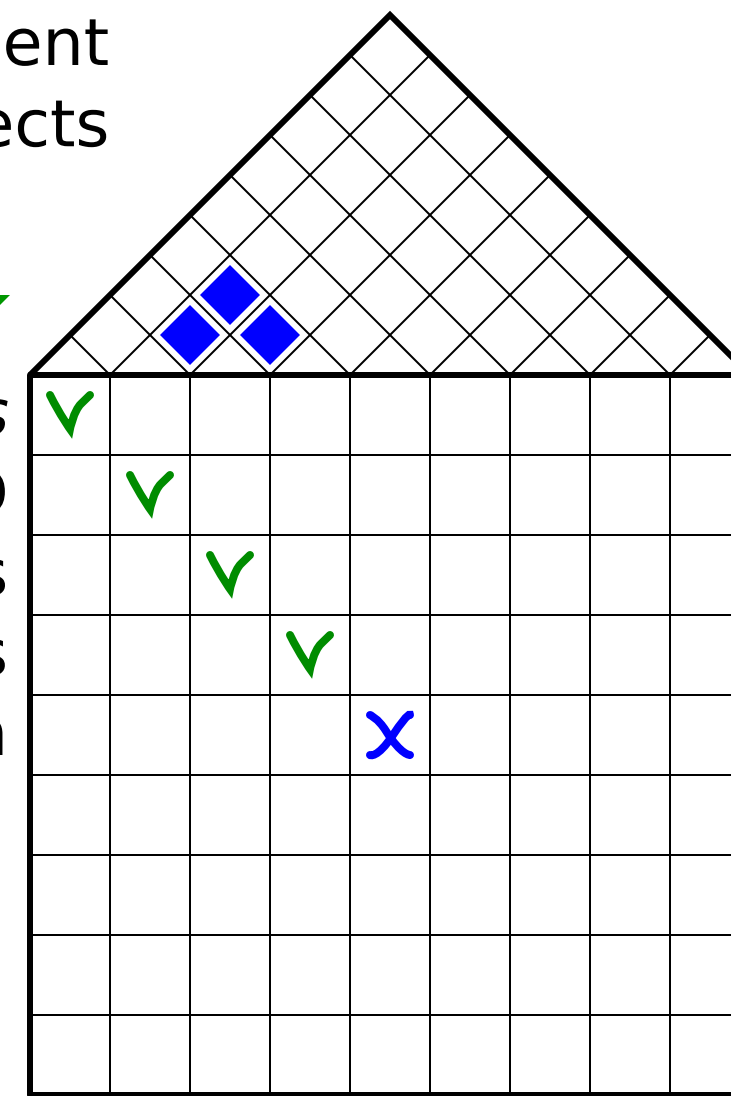*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP

### Design of the number of stages of the controller


Determine the number of stages required for a sufficiently large mid-band (or DC) loop gain and loop gain-poles product.

### Design of the active antenna:

*Function, performance, costs and environment*  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product


design aspects

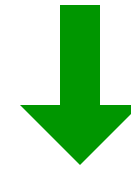Design of independent performance aspects



interaction between design aspects

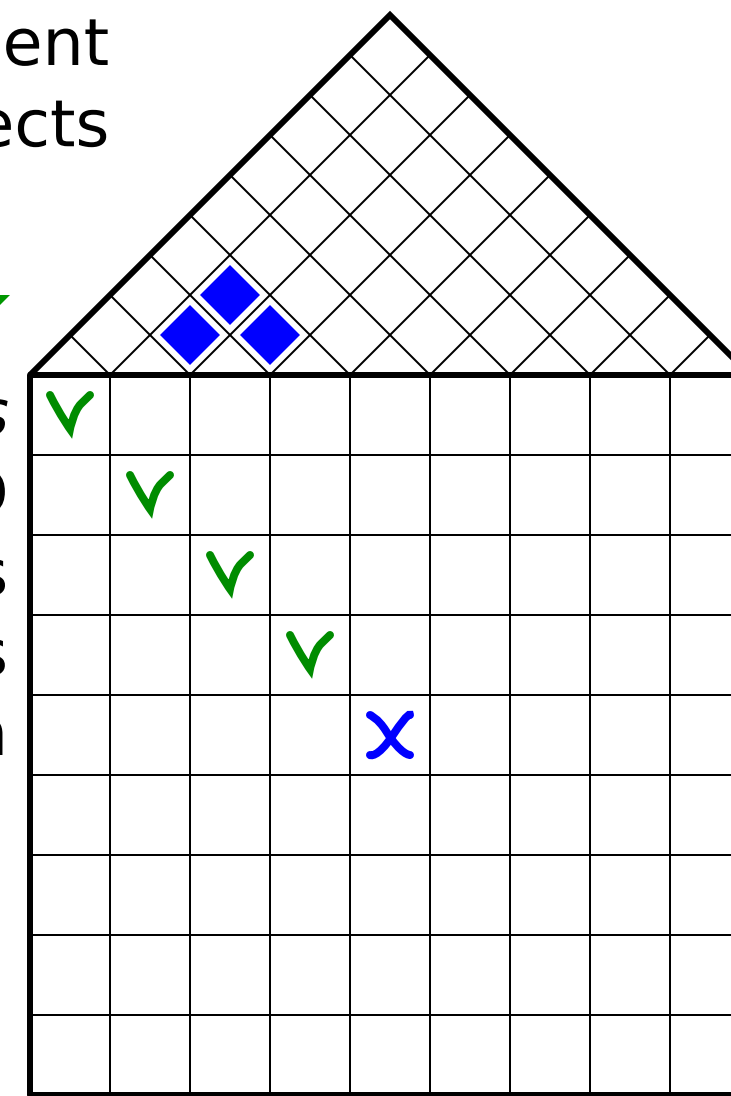*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP

### Design of the number of stages of the controller

Determine the number of stages required for a sufficiently large mid-band (or DC) loop gain and loop gain-poles product.

### Design of the active antenna:


Use the asymptotic gain feedback model to verify the loop gain and the loop gain-poles product of the two-stage solution.

*Function, performance, costs and environment*  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product

design aspects




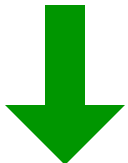Design of independent performance aspects



interaction between design aspects

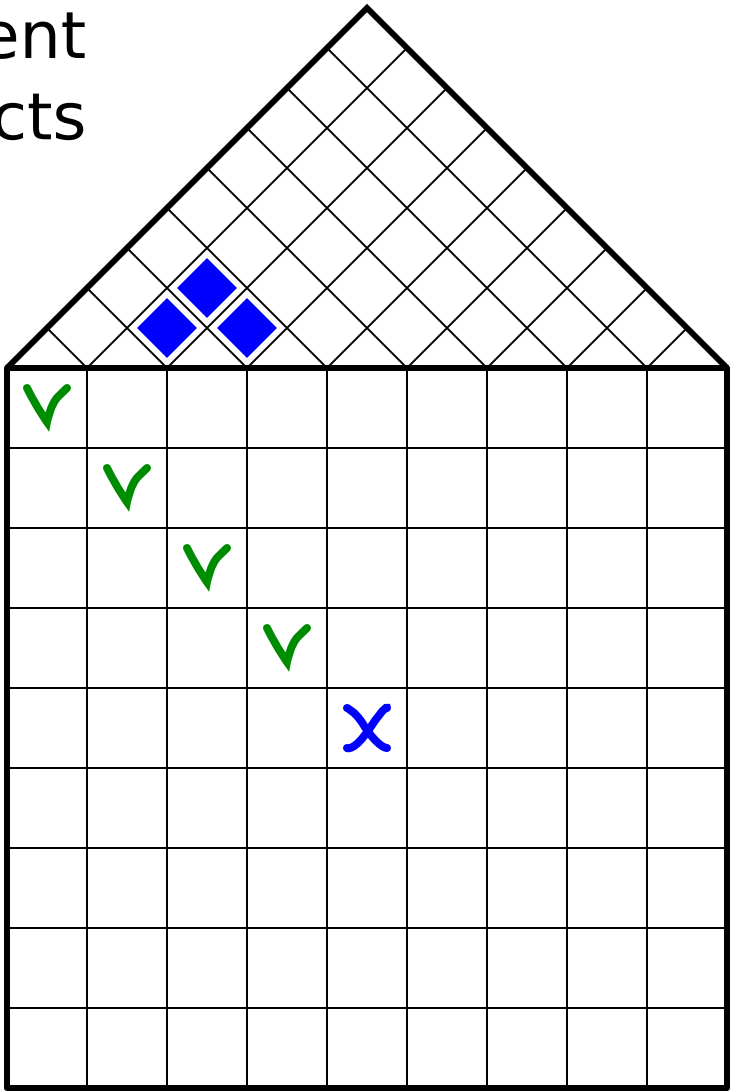*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP

**Design of the number of stages of the controller**

Determine the number of stages required for a sufficiently large mid-band (or DC) loop gain and loop gain-poles product.

**Design of the active antenna:**


Use the asymptotic gain feedback model to verify the loop gain and the loop gain-poles product of the two-stage solution.

*Function, performance, costs and environment*  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product



design aspects

# Bandwidth design


# Bandwidth design

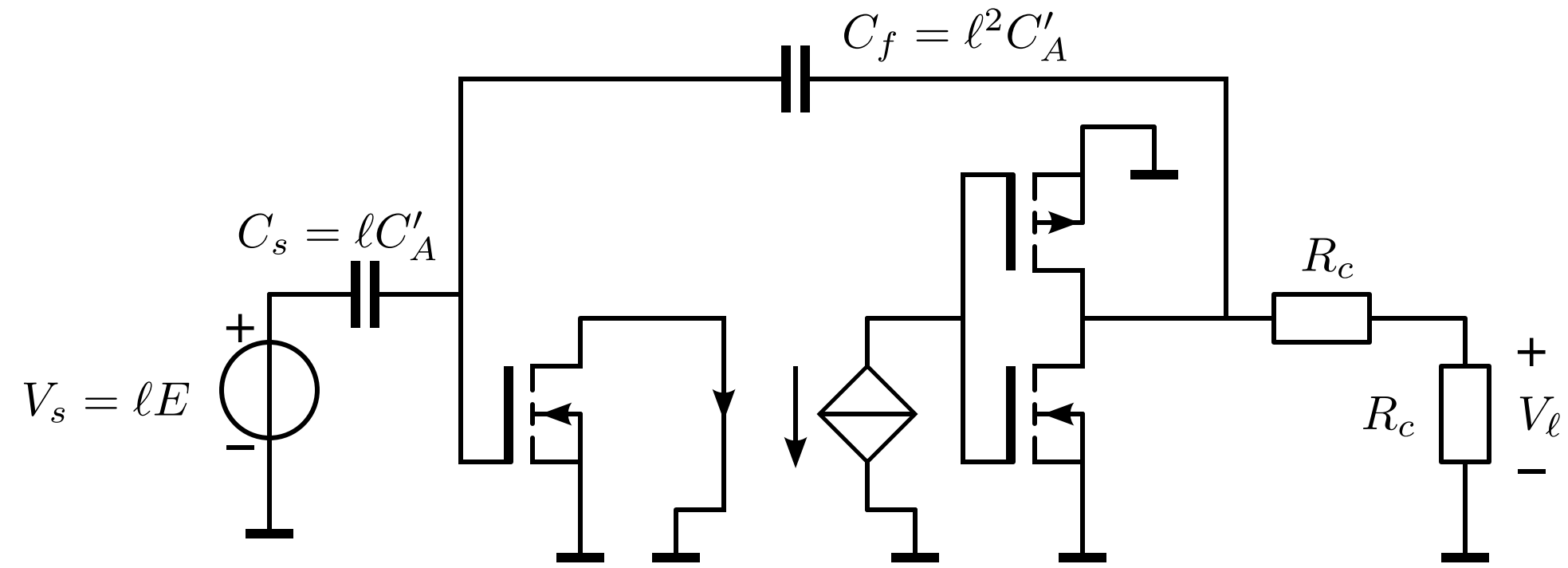


# Bandwidth design

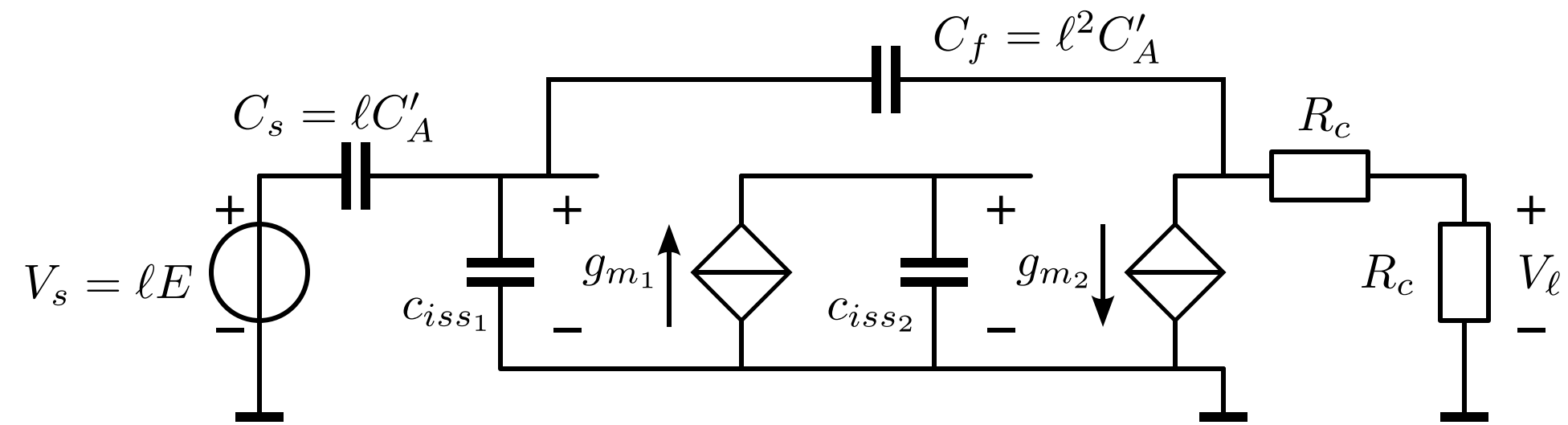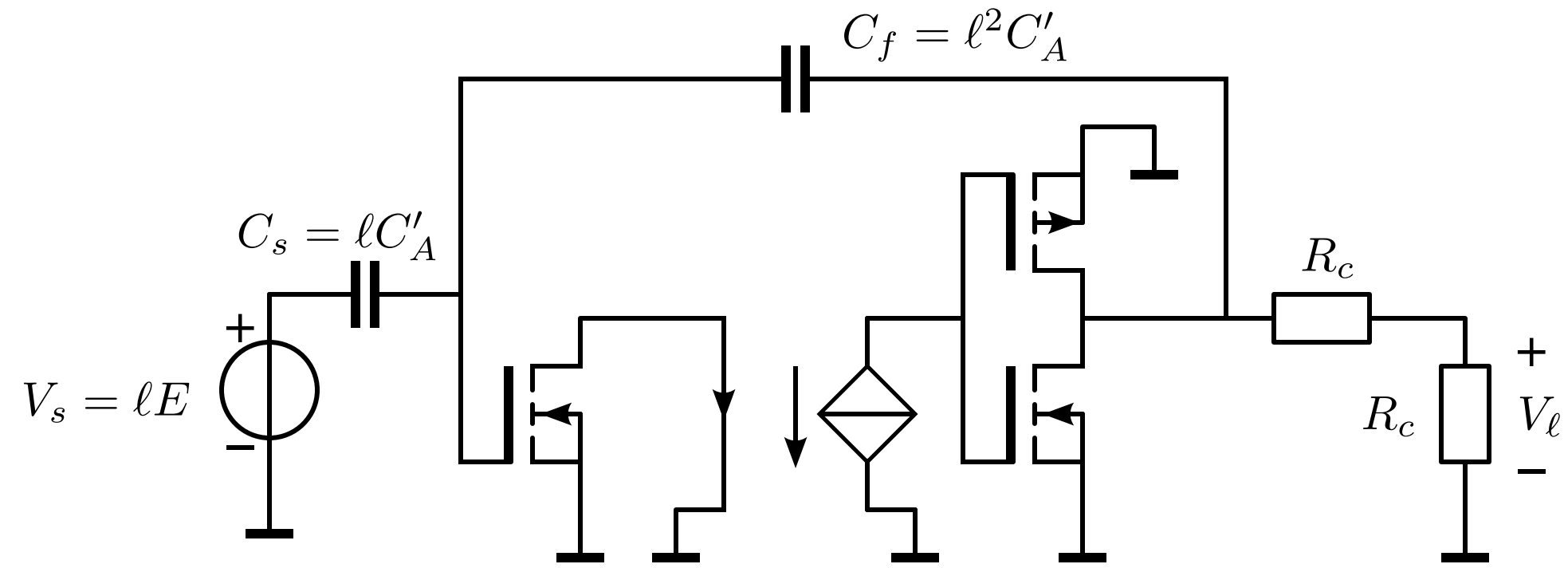


# Bandwidth design

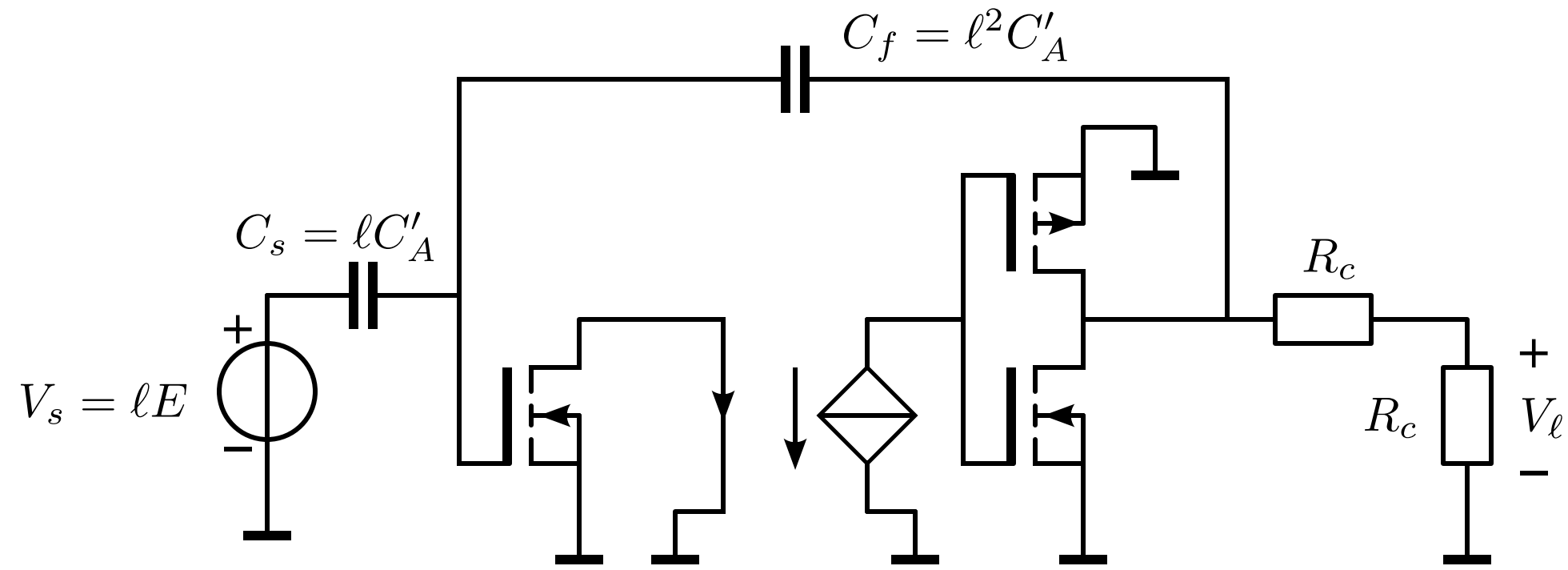

Loop gain, ref:  $g_{m1}$

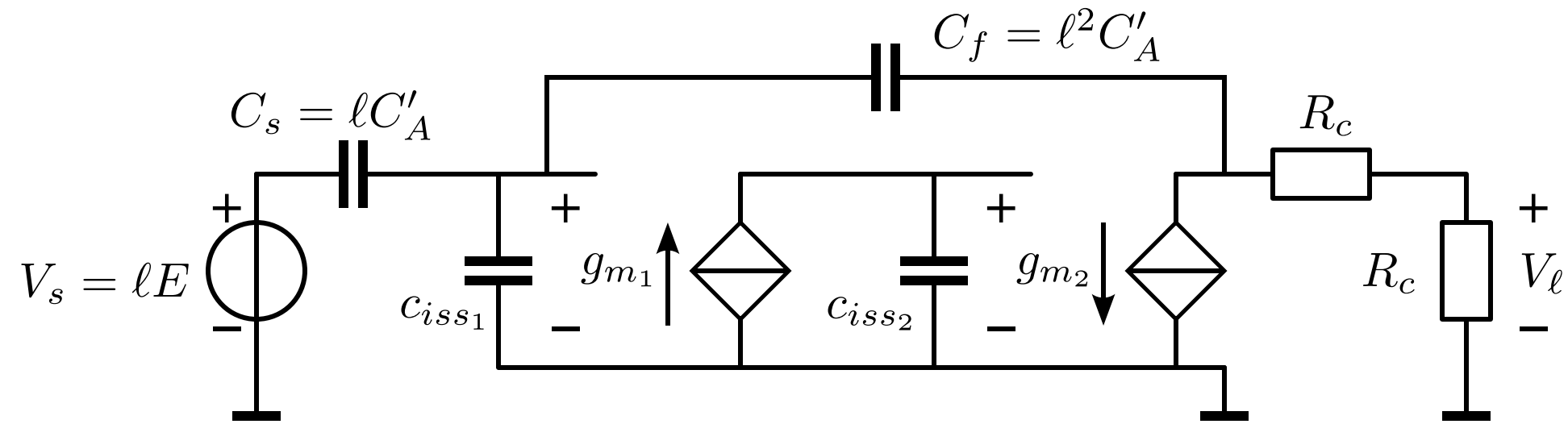


# Bandwidth design

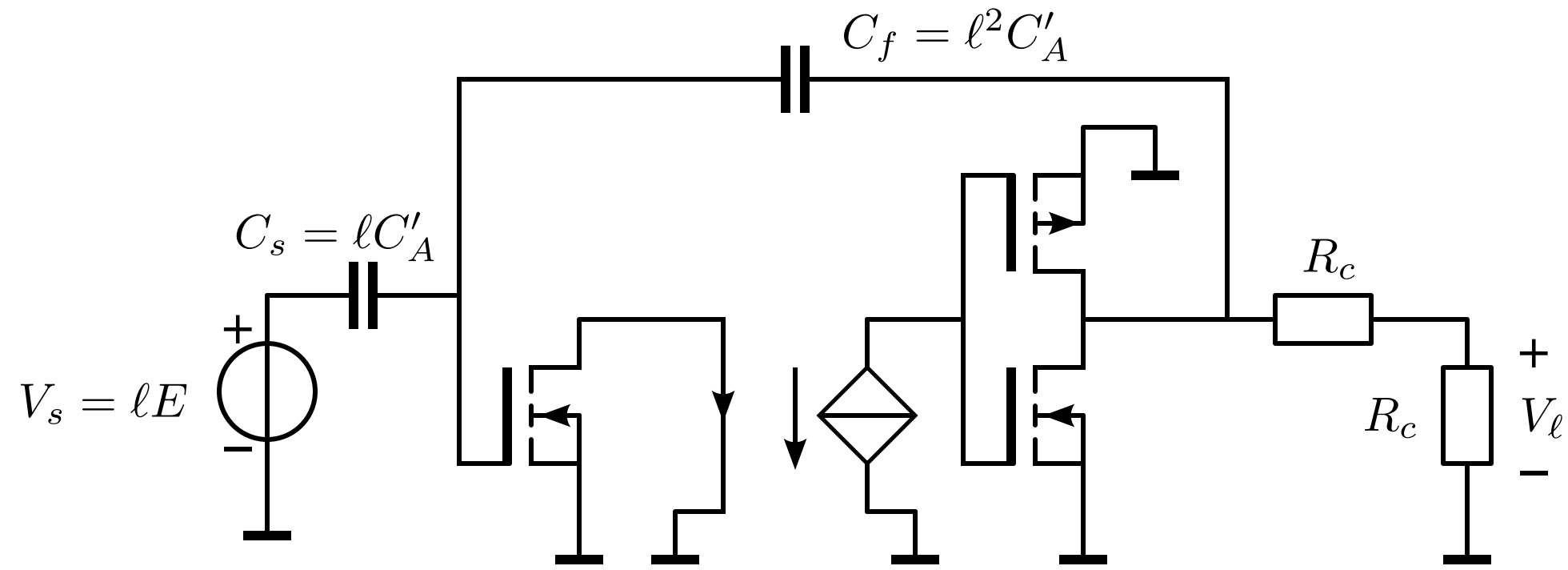


Loop gain, ref:  $g_{m1}$
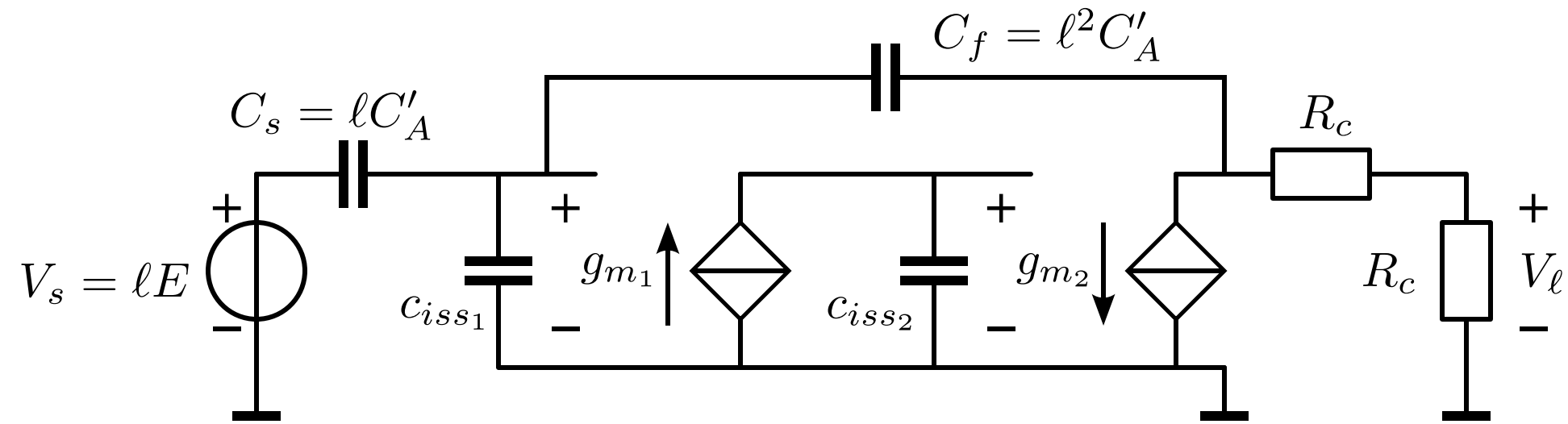
$$L = - \frac{2g_{m1}g_{m2}R_c \frac{C_f}{C_f+C_s+c_{iss1}}}{s c_{iss2} \left( 1 + s 2R_c \frac{C_f(C_s+c_{iss1})}{C_f+C_s+c_{iss1}} \right)}$$




# Bandwidth design

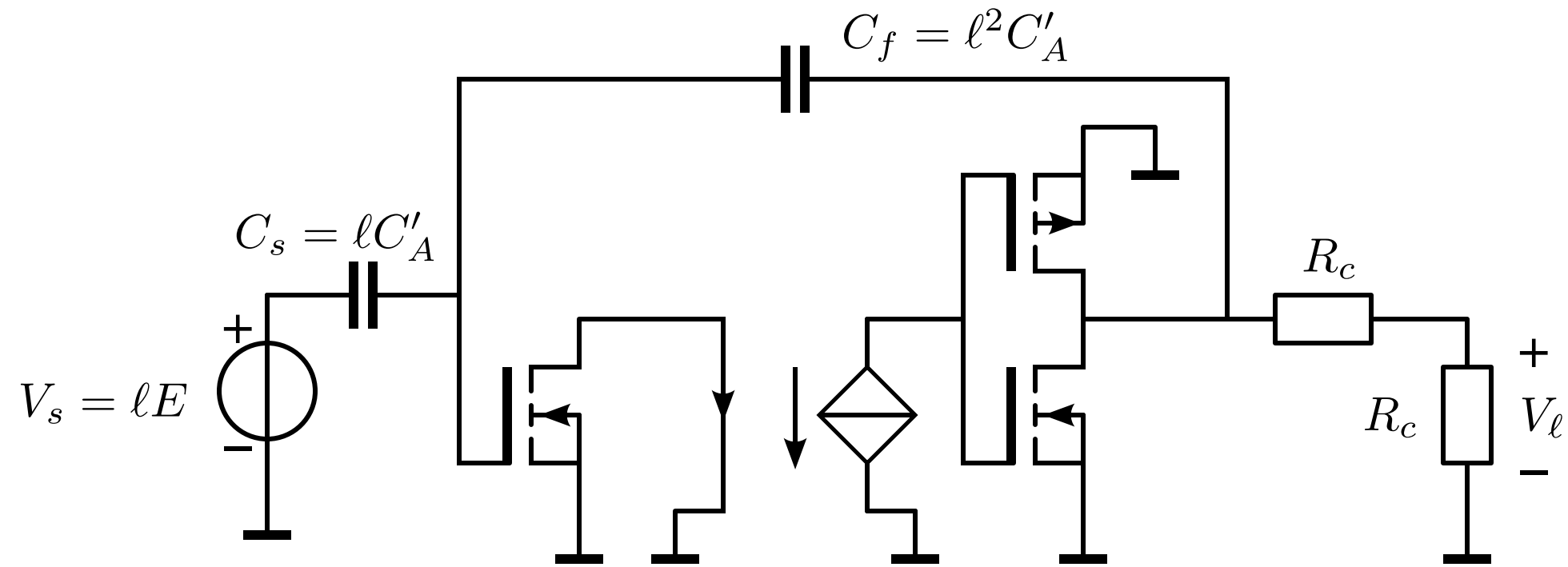


Loop gain, ref:  $g_{m1}$

$$L = - \frac{2g_{m1} g_{m2} R_c \frac{C_f}{C_f + C_s + c_{iss1}}}{s c_{iss2} \left( 1 + s 2R_c \frac{C_f (C_s + c_{iss1})}{C_f + C_s + c_{iss1}} \right)}$$

Second-order loop gain-poles product:

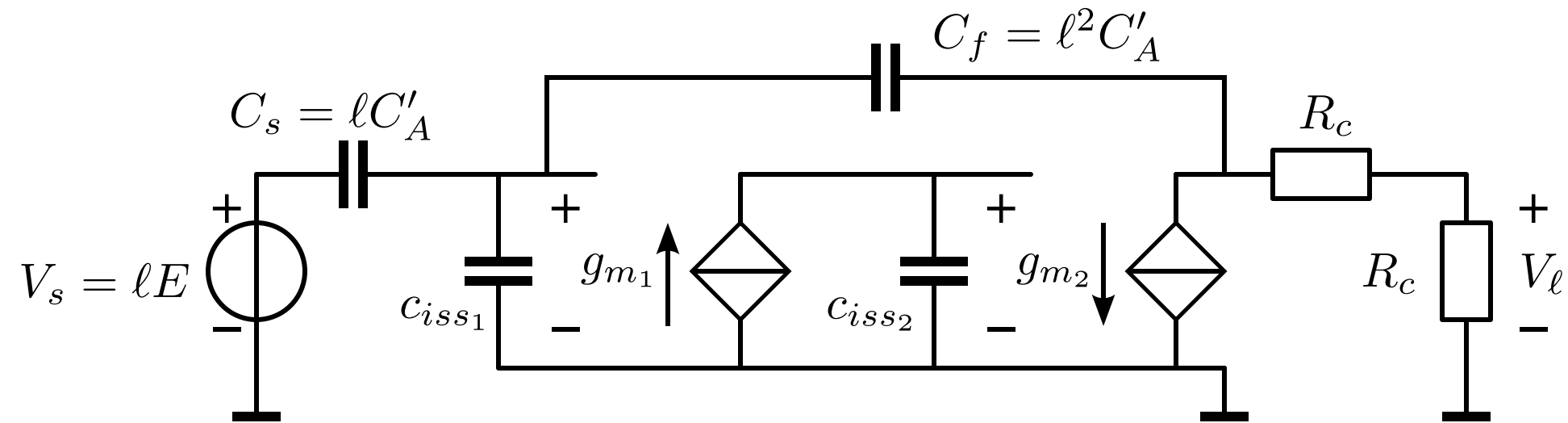

# Bandwidth design

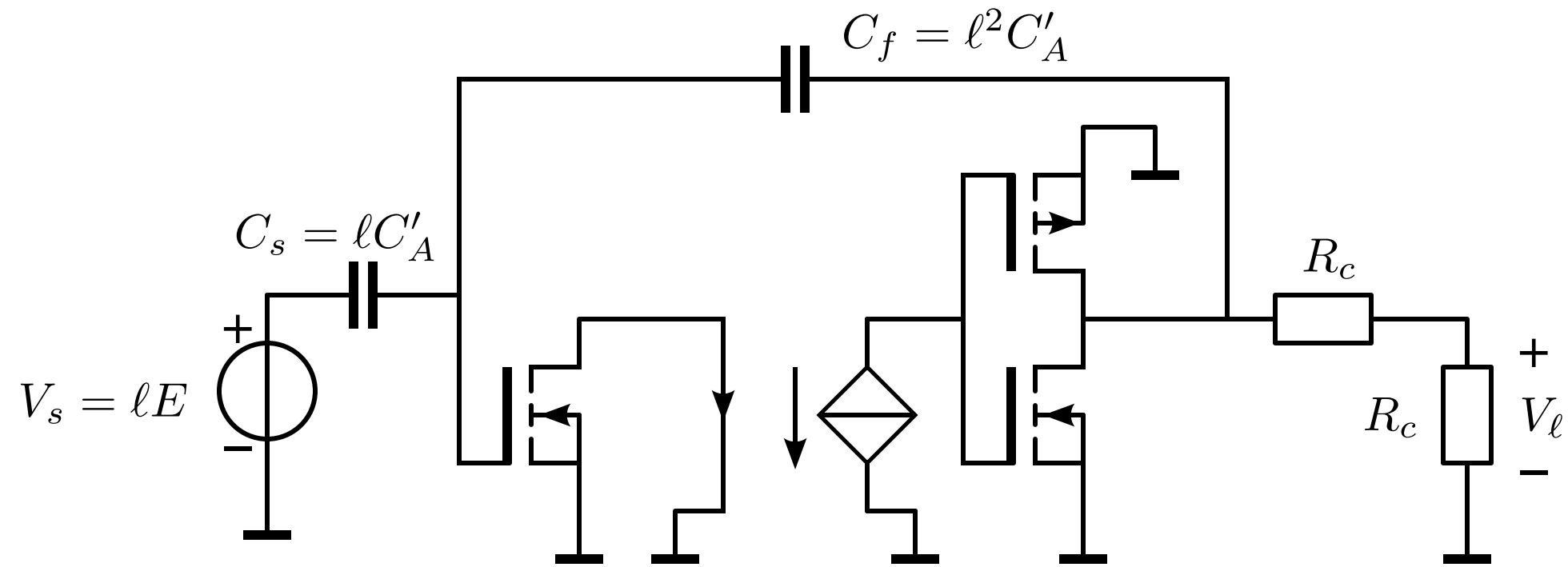


Loop gain, ref:  $g_{m1}$

$$L = - \frac{2g_{m1} g_{m2} R_c \frac{C_f}{C_f + C_s + c_{iss1}}}{s c_{iss2} \left( 1 + s 2R_c \frac{C_f (C_s + c_{iss1})}{C_f + C_s + c_{iss1}} \right)}$$


Second-order loop gain-poles product:
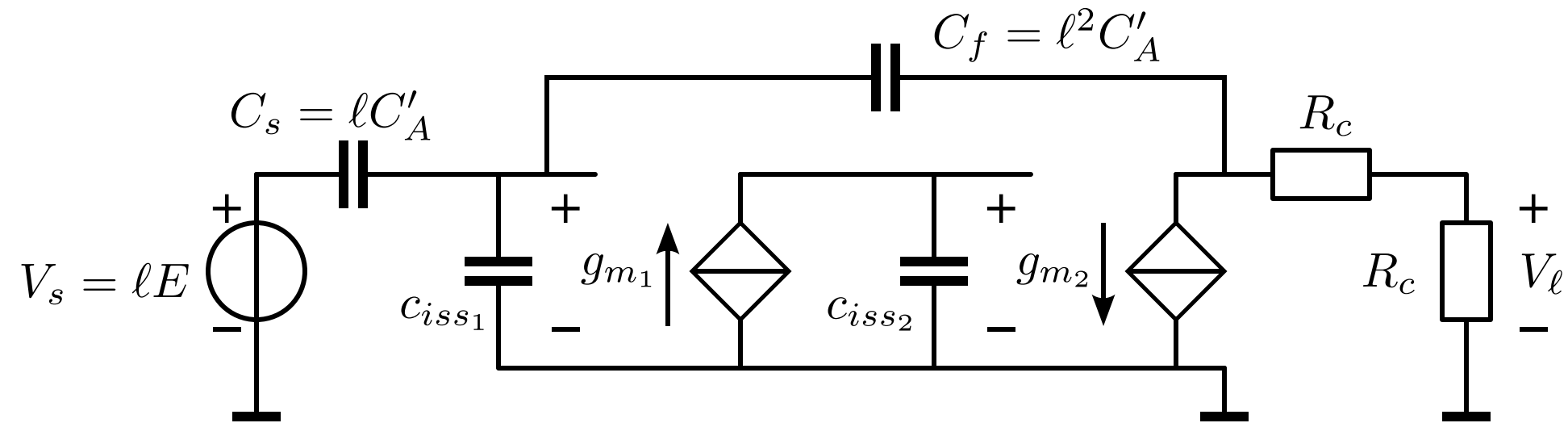
$$LP_2 = \frac{g_{m1} g_{m2}}{c_{iss2} (C_s + c_{iss1})}$$





# Bandwidth design

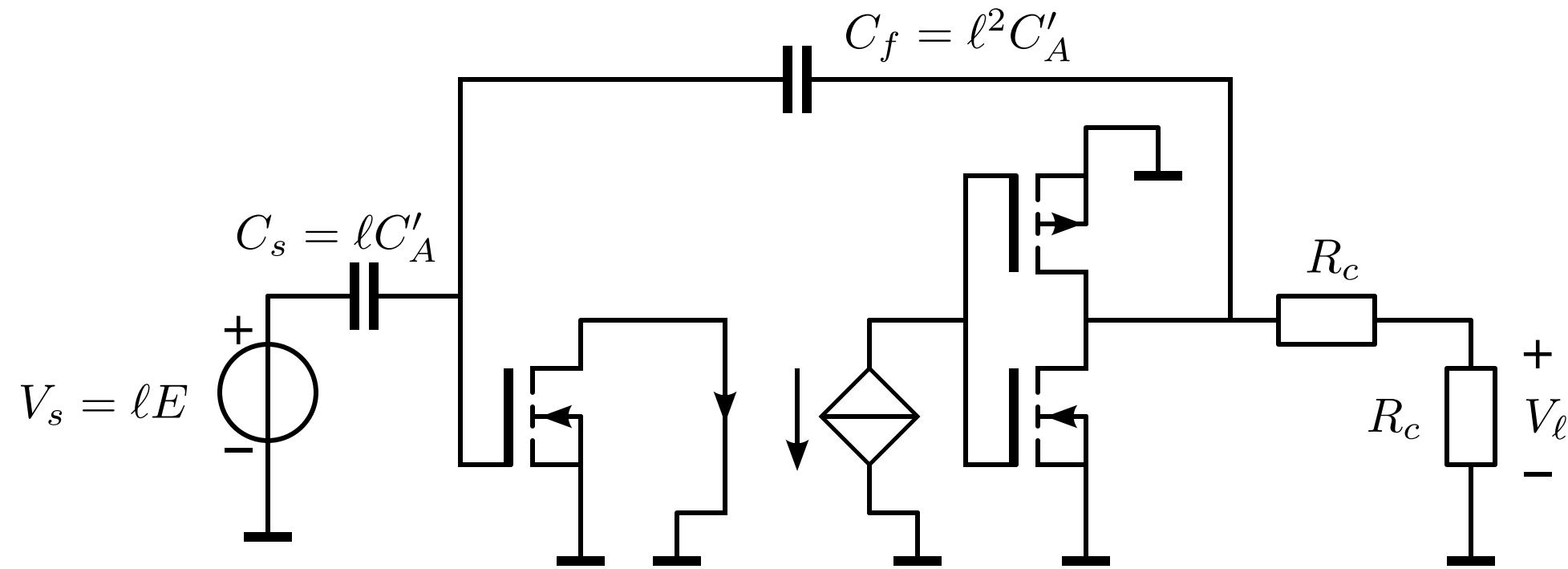


Loop gain, ref:  $g_{m1}$

$$L = - \frac{2g_{m1}g_{m2}R_c \frac{C_f}{C_f+C_s+c_{iss1}}}{s c_{iss2} \left( 1 + s 2R_c \frac{C_f(C_s+c_{iss1})}{C_f+C_s+c_{iss1}} \right)}$$


Second-order loop gain-poles product:

$$LP_2 = \frac{g_{m1}g_{m2}}{c_{iss2}(C_s+c_{iss1})}$$

Circuit element values:

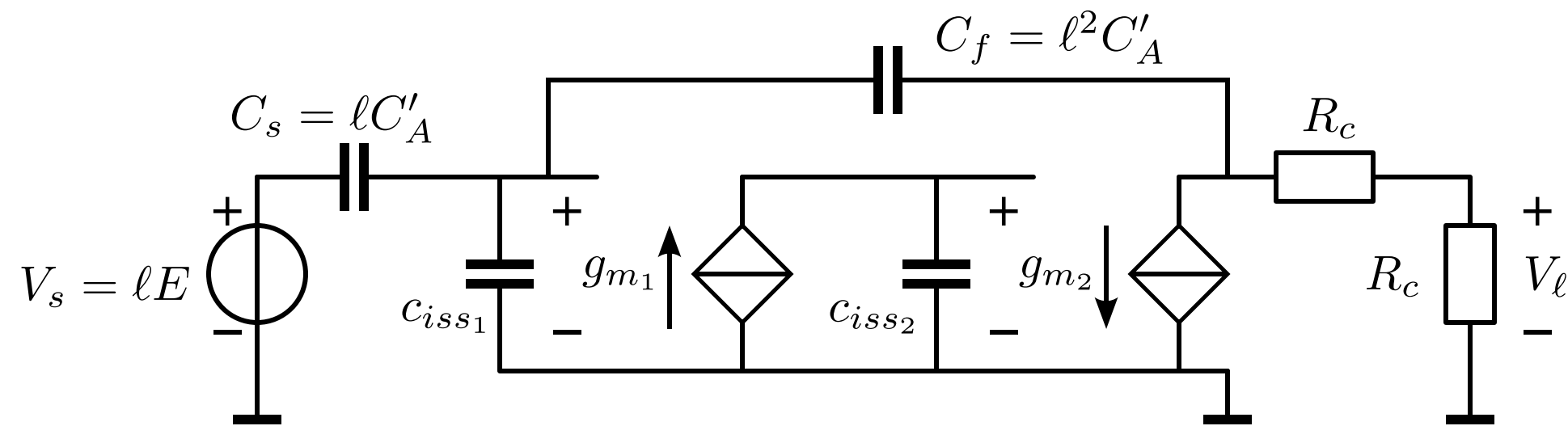

# Bandwidth design

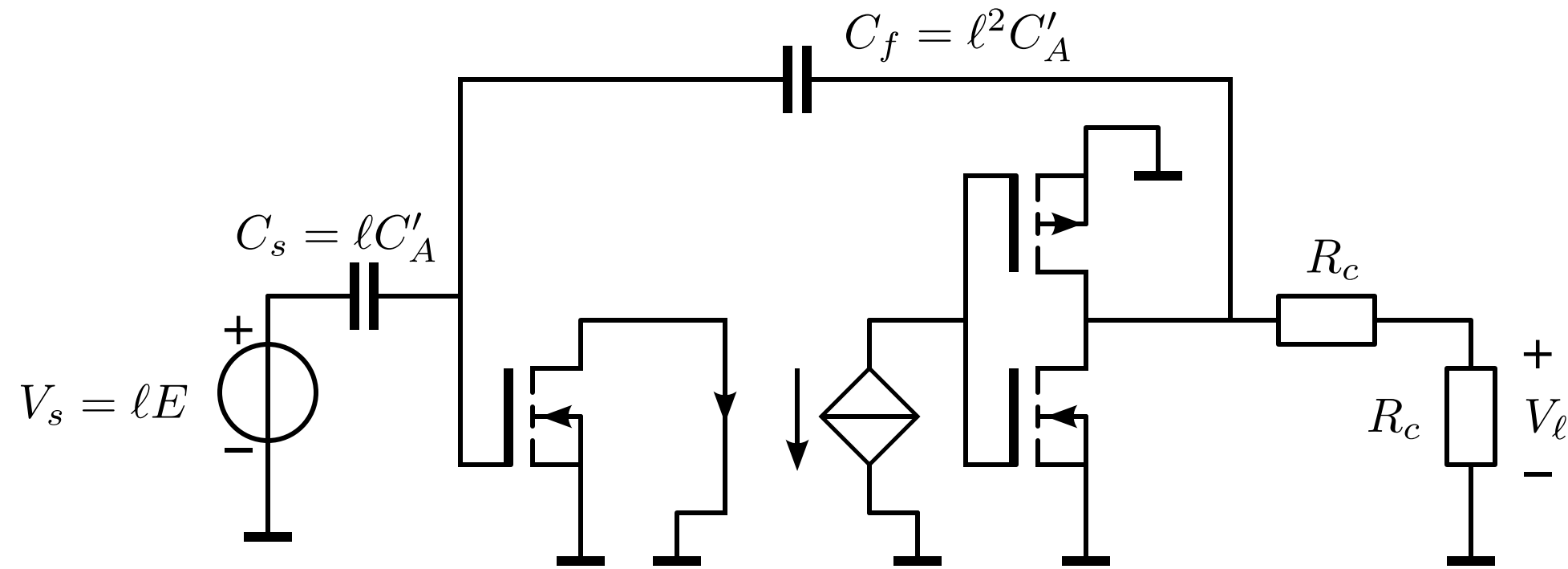

Loop gain, ref:  $g_{m1}$

$$L = - \frac{2g_{m1}g_{m2}R_c \frac{C_f}{C_f+C_s+c_{iss1}}}{s c_{iss2} \left( 1 + s 2R_c \frac{C_f(C_s+c_{iss1})}{C_f+C_s+c_{iss1}} \right)}$$

Second-order loop gain-poles product:

$$LP_2 = \frac{g_{m1}g_{m2}}{c_{iss2}(C_s+c_{iss1})}$$

Circuit element values:


$$g_{m1} = 23\text{m}$$

$$g_{m2} = 28\text{m}$$



$$C_s = 5\text{p}$$

$$c_{iss1} = 1\text{p}$$

$$c_{iss2} = 1.2\text{p}$$

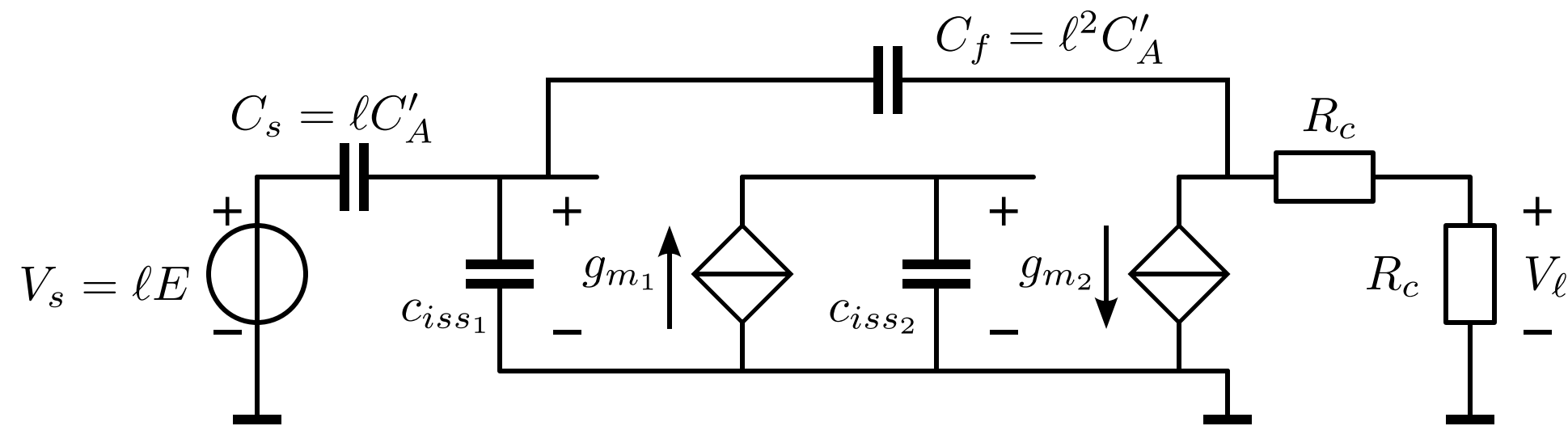

# Bandwidth design

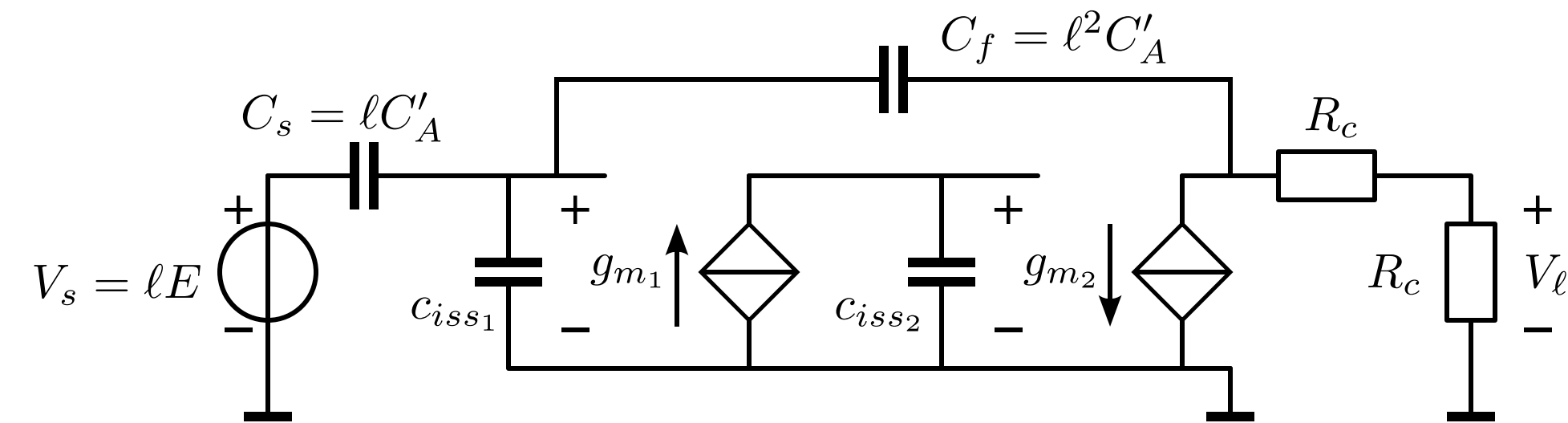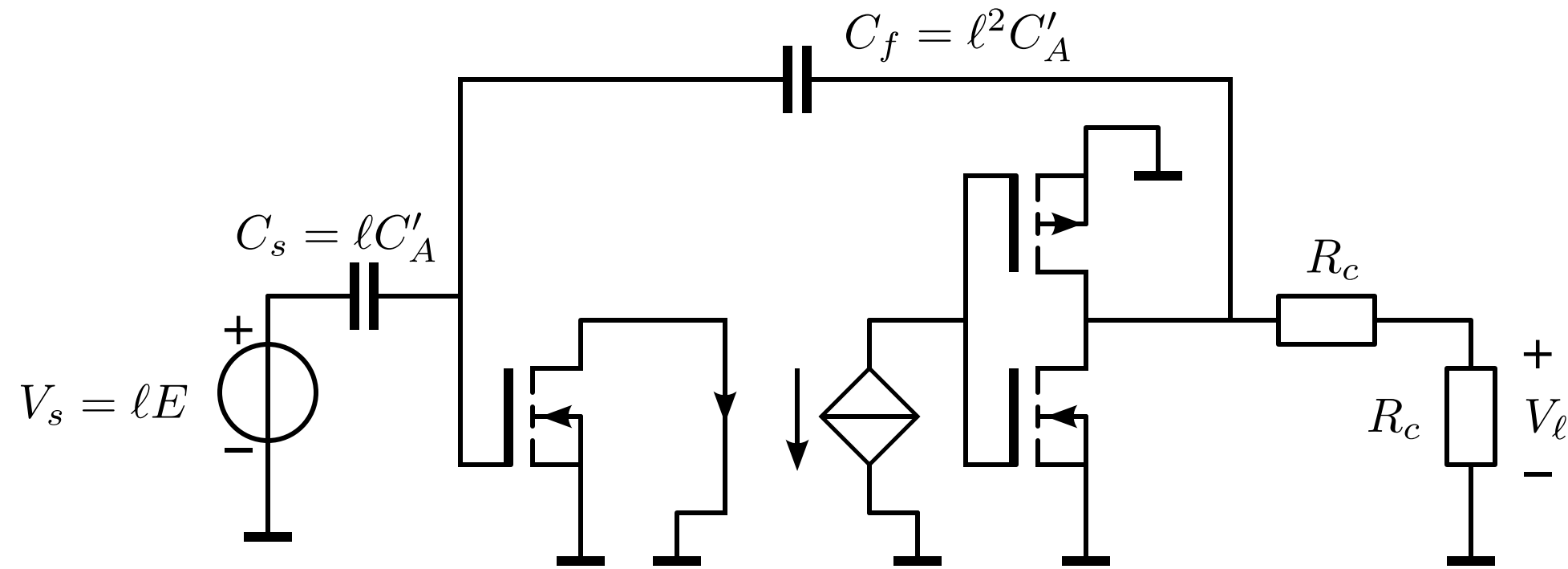

Loop gain, ref:  $g_{m1}$

$$L = - \frac{2g_{m1}g_{m2}R_c \frac{C_f}{C_f+C_s+c_{iss1}}}{s c_{iss2} \left( 1 + s 2R_c \frac{C_f(C_s+c_{iss1})}{C_f+C_s+c_{iss1}} \right)}$$

Second-order loop gain-poles product:

$$LP_2 = \frac{g_{m1}g_{m2}}{c_{iss2}(C_s+c_{iss1})}$$

Circuit element values:

$$g_{m1} = 23\text{m}$$

$$g_{m2} = 28\text{m}$$



$$C_s = 5\text{p}$$

$$c_{iss1} = 1\text{p}$$

$$c_{iss2} = 1.2\text{p}$$

Achievable MFM bandwidth:

# Bandwidth design

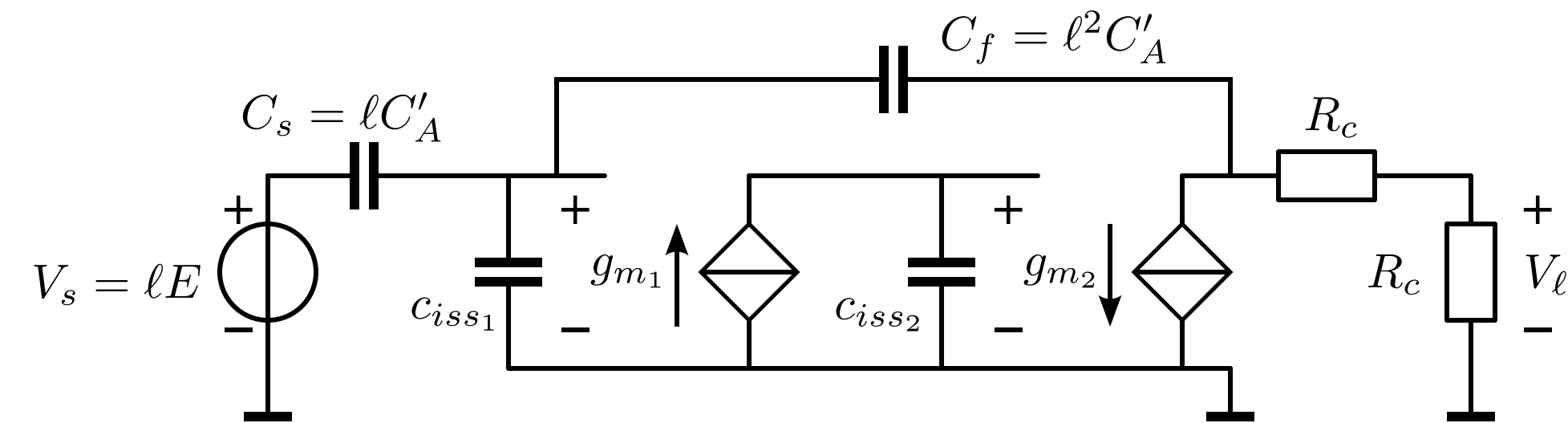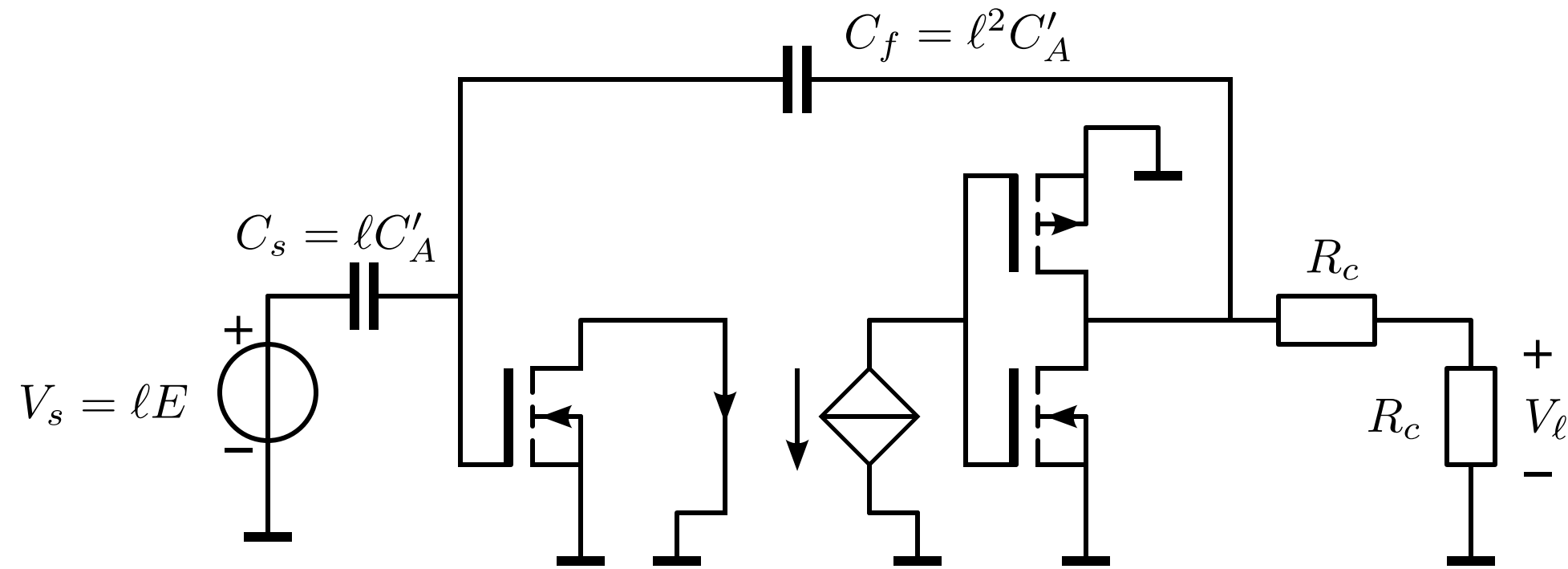

Loop gain, ref:  $g_{m1}$

$$L = - \frac{2g_{m1} g_{m2} R_c \frac{C_f}{C_f + C_s + c_{iss1}}}{s c_{iss2} \left( 1 + s 2R_c \frac{C_f (C_s + c_{iss1})}{C_f + C_s + c_{iss1}} \right)}$$

Second-order loop gain-poles product:

$$LP_2 = \frac{g_{m1} g_{m2}}{c_{iss2} (C_s + c_{iss1})}$$

Circuit element values:

$$g_{m1} = 23\text{m}$$

$$g_{m2} = 28\text{m}$$

$$C_s = 5\text{p}$$


$$c_{iss1} = 1\text{p}$$

$$c_{iss2} = 1.2\text{p}$$

Achievable MFM bandwidth:

$$B_f = \frac{1}{2\pi} \sqrt{LP_2} = 1.5\text{GHz}$$

# Bandwidth design

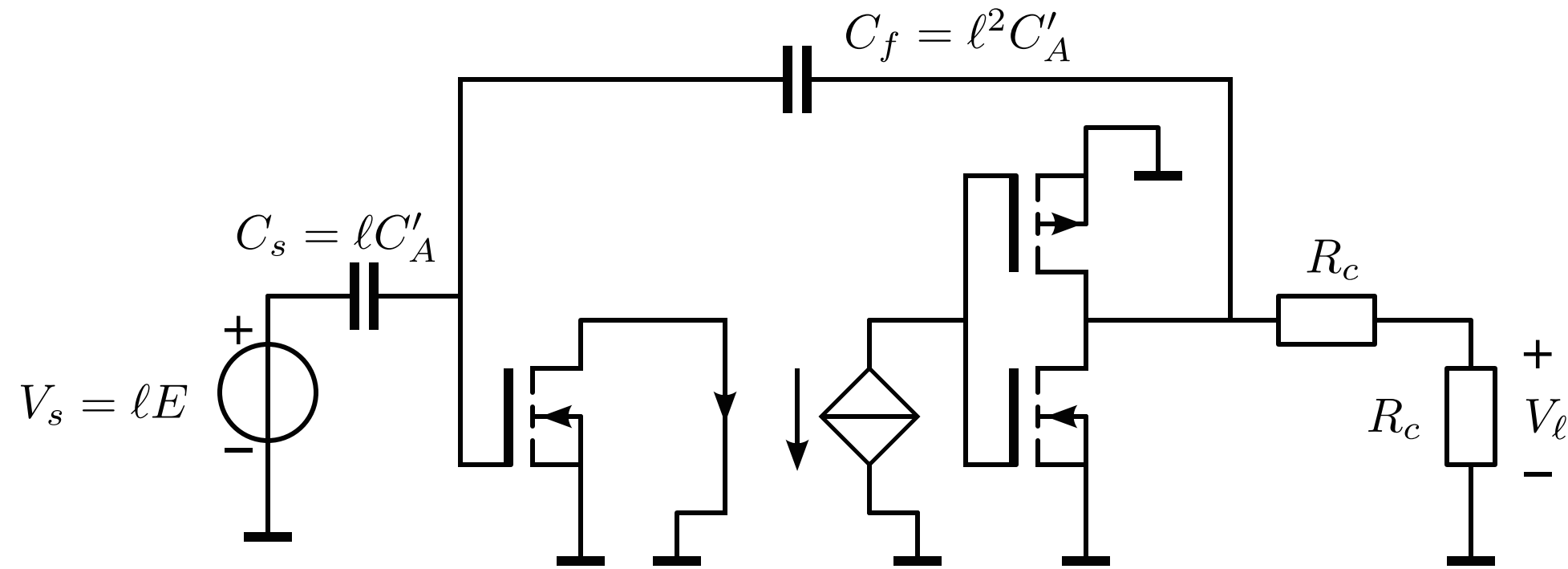

Loop gain, ref:  $g_{m1}$

$$L = - \frac{2g_{m1} g_{m2} R_c \frac{C_f}{C_f + C_s + c_{iss1}}}{s c_{iss2} \left( 1 + s 2R_c \frac{C_f (C_s + c_{iss1})}{C_f + C_s + c_{iss1}} \right)}$$

Second-order loop gain-poles product:

$$LP_2 = \frac{g_{m1} g_{m2}}{c_{iss2} (C_s + c_{iss1})}$$

Circuit element values:

$$g_{m1} = 23\text{m}$$

$$g_{m2} = 28\text{m}$$


$$C_s = 5\text{p}$$

$$c_{iss1} = 1\text{p}$$

$$c_{iss2} = 1.2\text{p}$$

Achievable MFM bandwidth:
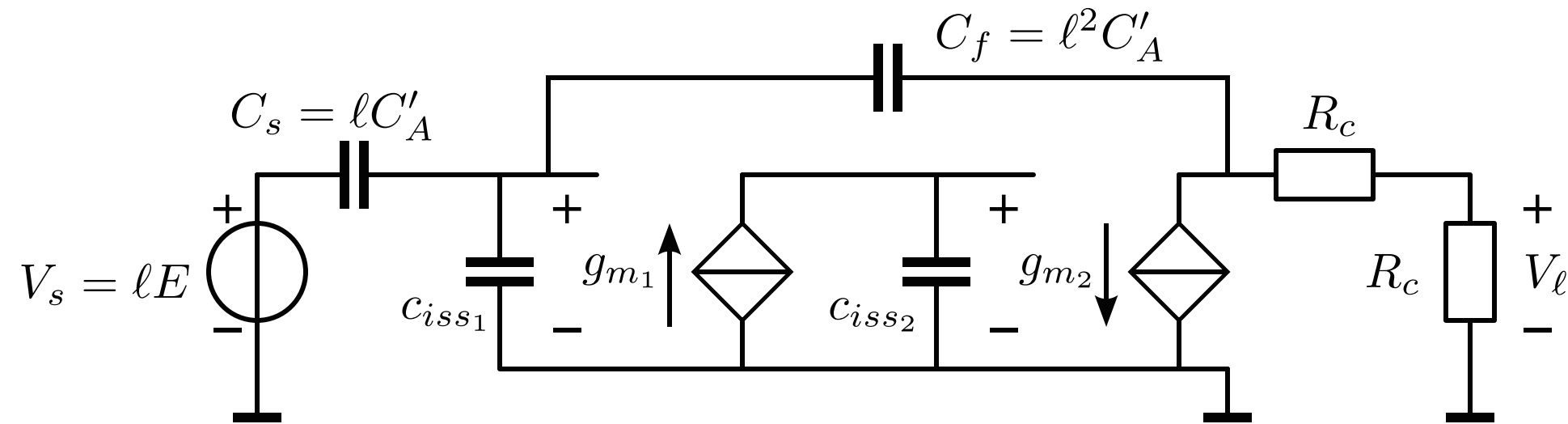
$$B_f = \frac{1}{2\pi} \sqrt{LP_2} = 1.5\text{GHz}$$




# **Structured Electronic Design**

## Step 6

Design of frequency response  
(frequency compensation)


*Anton J.M. Montagne*

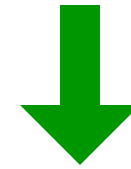Design of independent performance aspects



interaction between design aspects

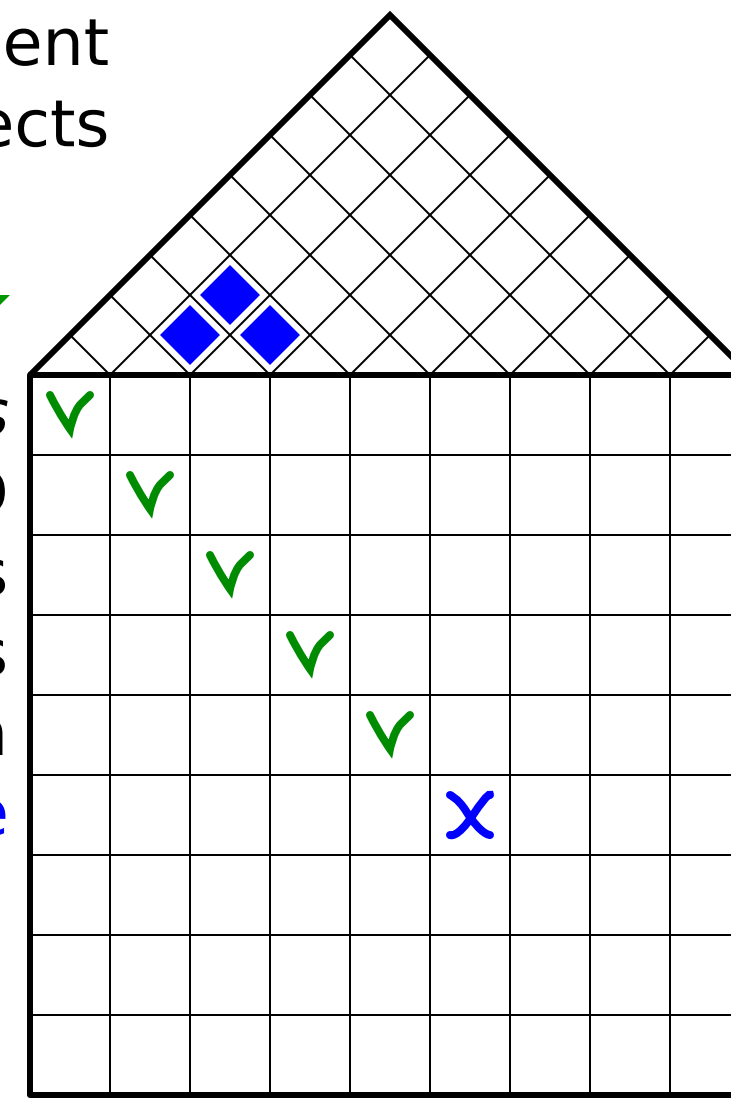Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response




SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP


Function, performance,  
 costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern

design aspects

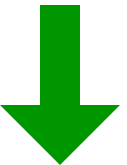Design of independent performance aspects



interaction between design aspects

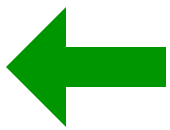

*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response


|   |   |   |   |   |   |  |  |  |  |
|---|---|---|---|---|---|--|--|--|--|
| ✓ |   |   |   |   |   |  |  |  |  |
|   | ✓ |   |   |   |   |  |  |  |  |
|   |   | ✓ |   |   |   |  |  |  |  |
|   |   |   | ✓ |   |   |  |  |  |  |
|   |   |   |   | ✓ |   |  |  |  |  |
|   |   |   |   |   | ✗ |  |  |  |  |
|   |   |   |   |   |   |  |  |  |  |
|   |   |   |   |   |   |  |  |  |  |
|   |   |   |   |   |   |  |  |  |  |

SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP

Frequency compensation


Function, performance,  
 costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern

design aspects

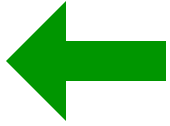




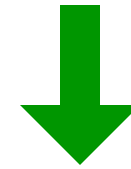Design of independent performance aspects



interaction between design aspects

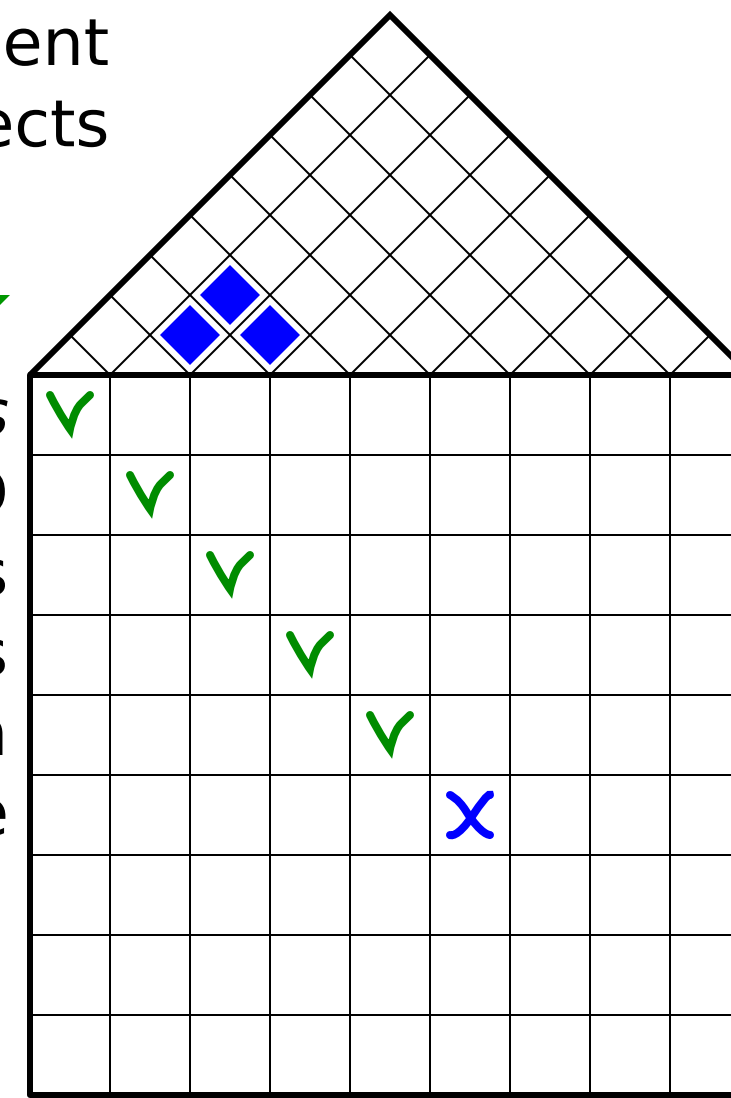Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP


## Frequency compensation

Correct the pole-zero pattern of the uncompensated amplifier without affecting other performance aspects.

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern


design aspects

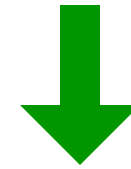Design of independent performance aspects



interaction between design aspects

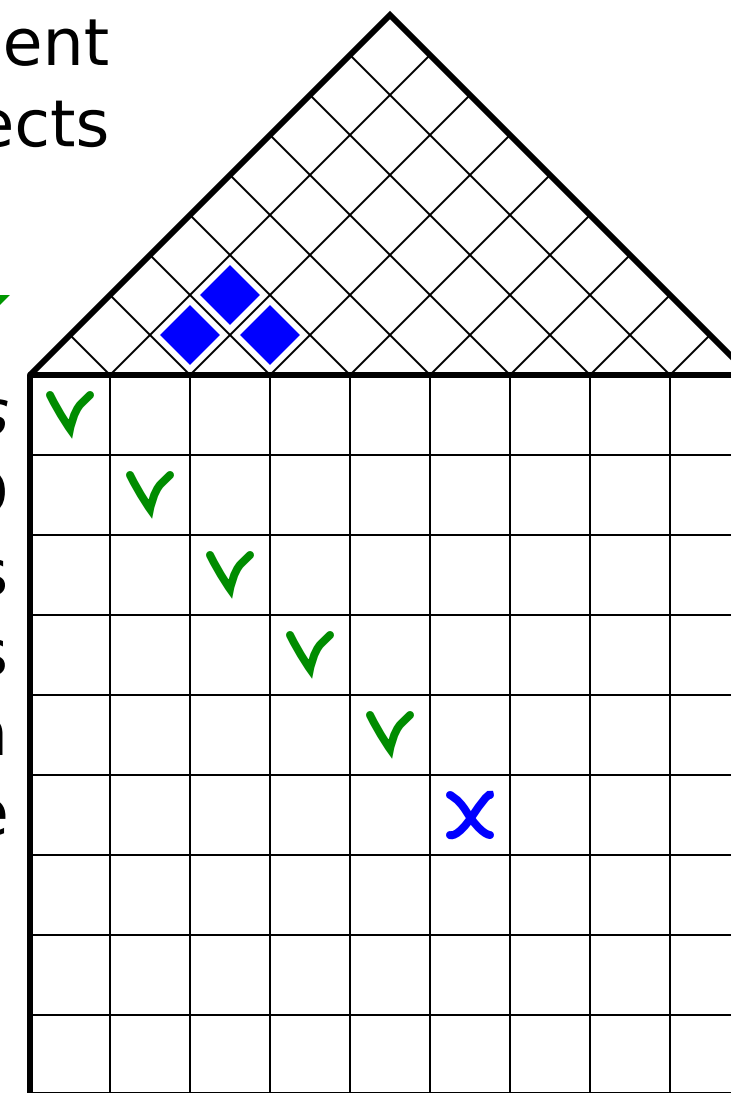*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP

## Frequency compensation


Correct the pole-zero pattern of the uncompensated amplifier without affecting other performance aspects.

The preferred method for low interaction is phantom zero compensation.

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern


design aspects

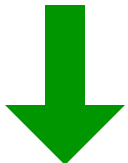Design of independent performance aspects



interaction between design aspects

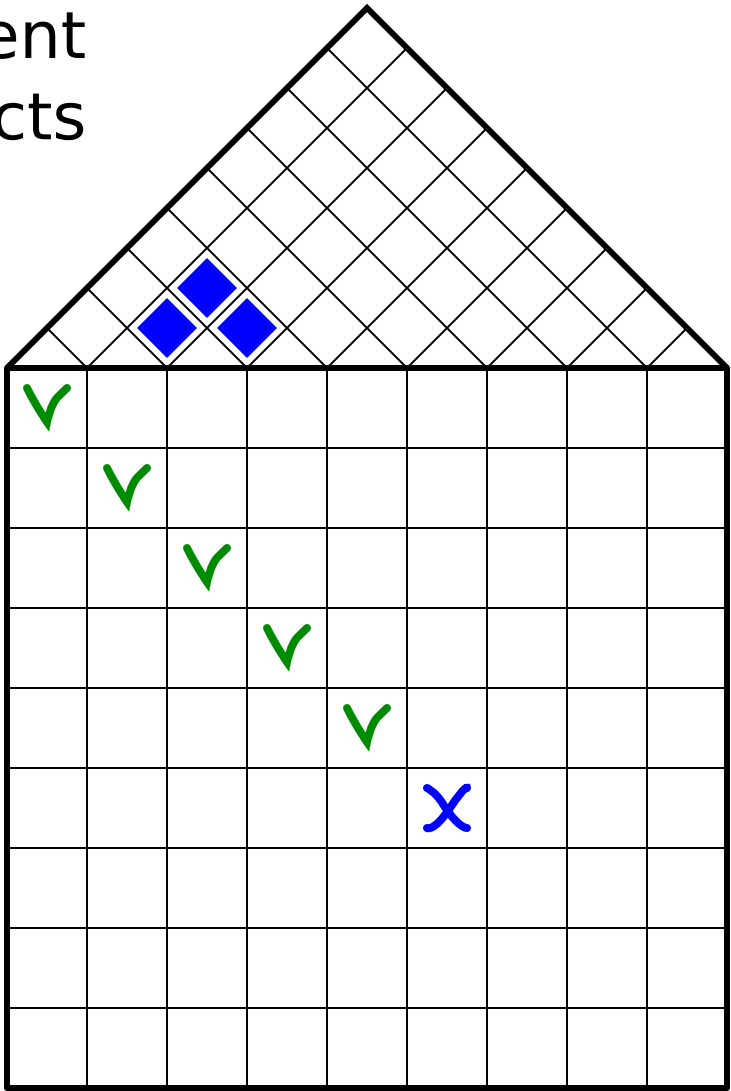*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP

**Frequency compensation**


Correct the pole-zero pattern of the uncompensated amplifier without affecting other performance aspects.  
 The preferred method for low interaction is phantom zero compensation.

**Design of the active antenna:**

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern


design aspects

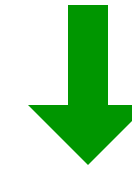Design of independent performance aspects



interaction between design aspects

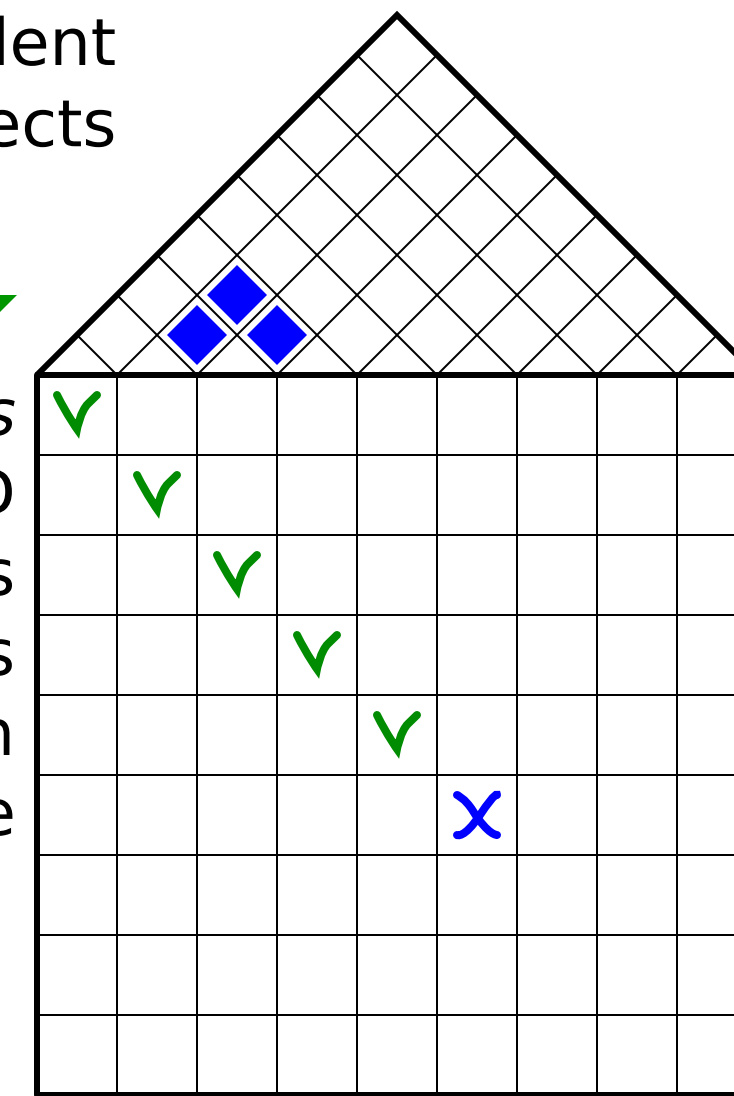*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP

## Frequency compensation

Correct the pole-zero pattern of the uncompensated amplifier without affecting other performance aspects.

The preferred method for low interaction is phantom zero compensation.


## Design of the active antenna:

Correct the frequency characteristic using a phantom zero at the input of the amplifier.

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern


design aspects

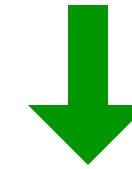Design of independent performance aspects



interaction between design aspects

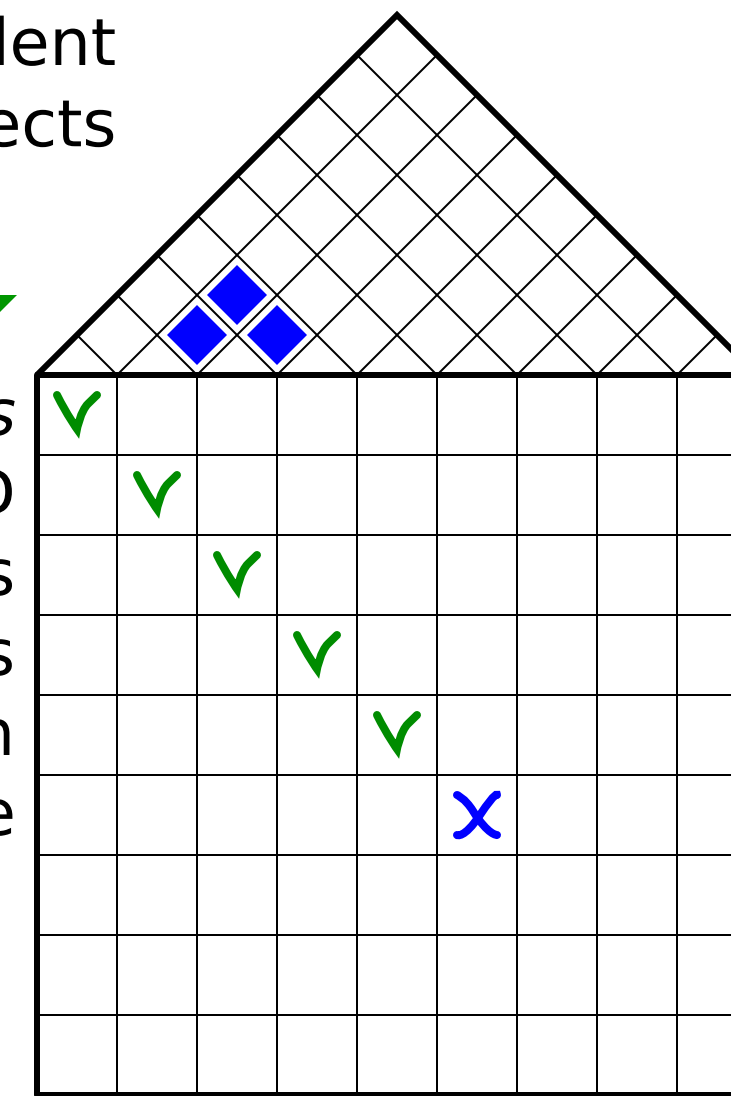Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP

## Frequency compensation

Correct the pole-zero pattern of the uncompensated amplifier without affecting other performance aspects.

The preferred method for low interaction is phantom zero compensation.

## Design of the active antenna:


Correct the frequency characteristic using a phantom zero at the input of the amplifier.

Reduce the influence of out-of-band interference through bandwidth limitation (Master Class)

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern


design aspects

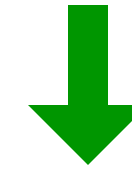Design of independent performance aspects



interaction between design aspects

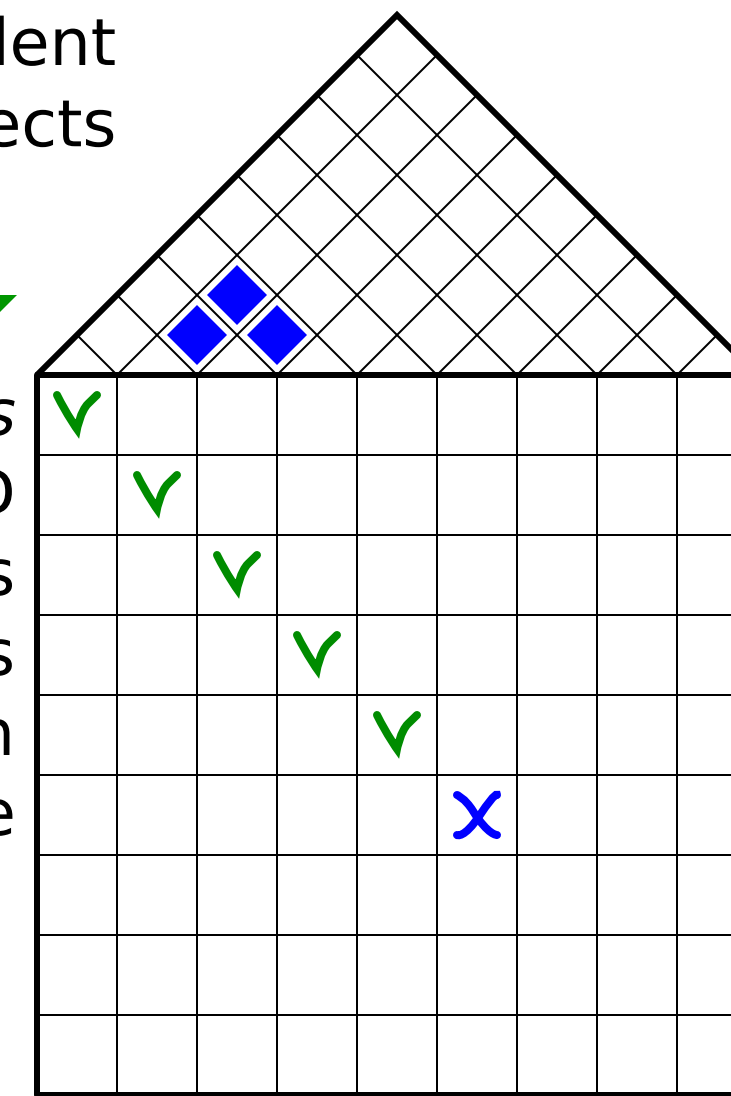*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP

## Frequency compensation

Correct the pole-zero pattern of the uncompensated amplifier without affecting other performance aspects.

The preferred method for low interaction is phantom zero compensation.

## Design of the active antenna:

Correct the frequency characteristic using a phantom zero at the input of the amplifier.


Reduce the influence of out-of-band interference through bandwidth limitation (Master Class)

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern

design aspects

# Phantom-zero compensation


# Phantom-zero compensation

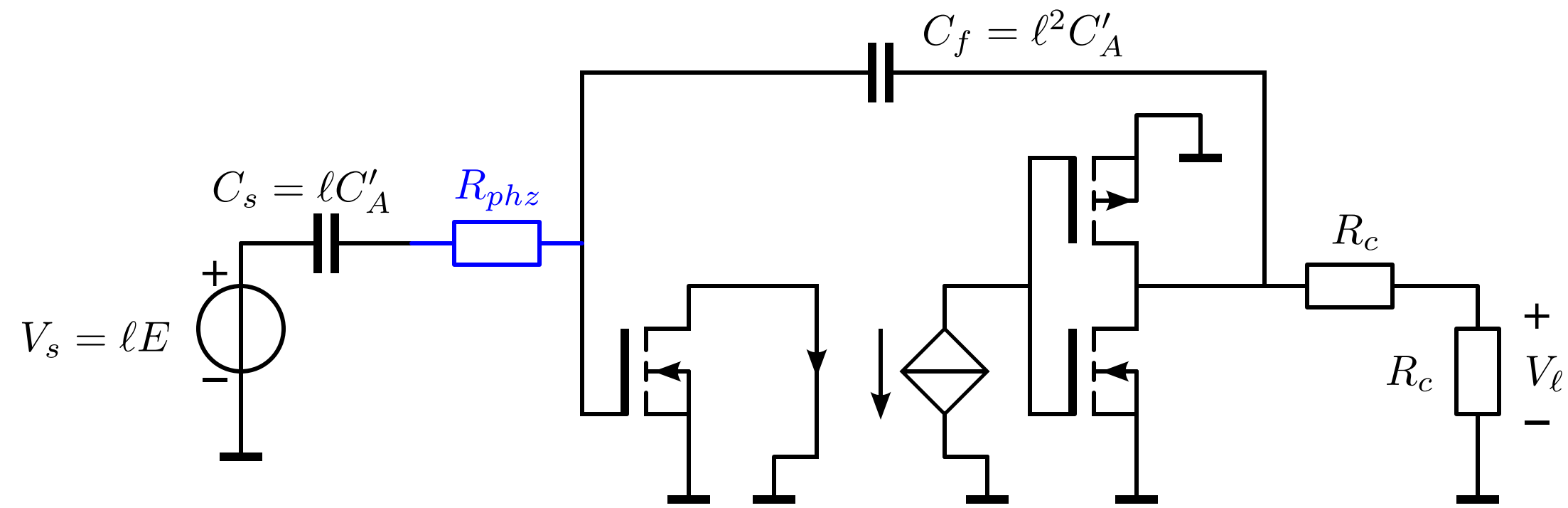



# Phantom-zero compensation

Circuit element values:

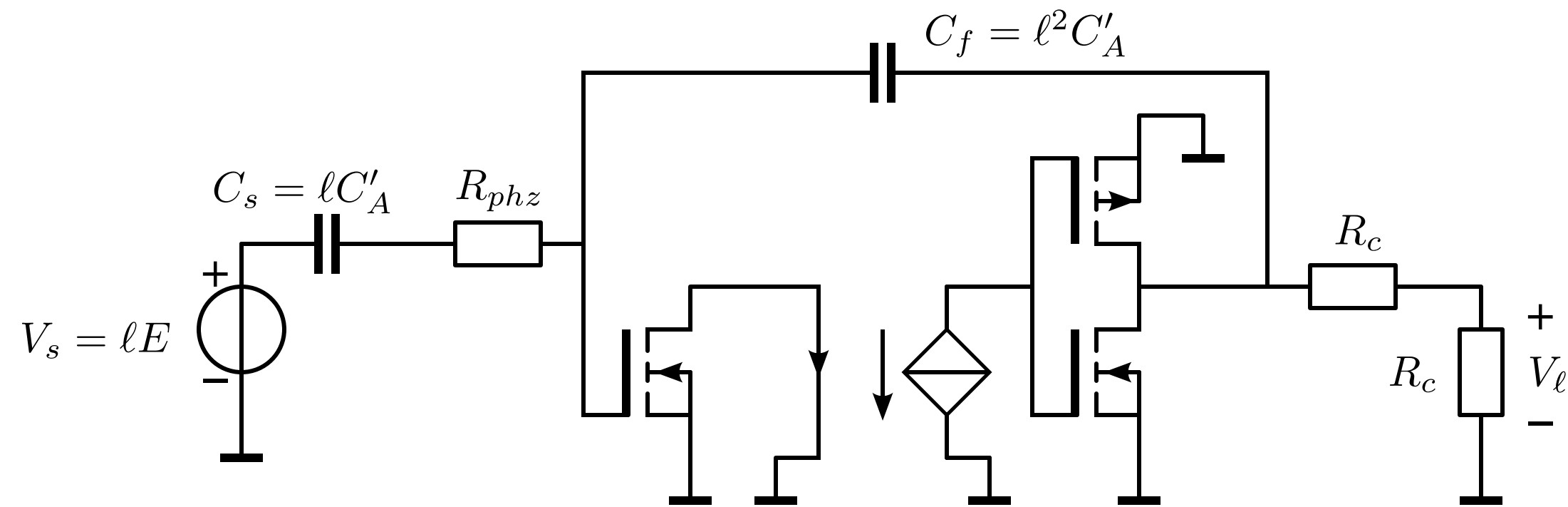

# Phantom-zero compensation

Circuit element values:


$$g_{m1} = 23\text{m}$$

$$g_{m2} = 28\text{m}$$

$$C_s = 5\text{p}$$

$$C_{iss1} = 1\text{p}$$

$$C_{iss2} = 1.2\text{p}$$

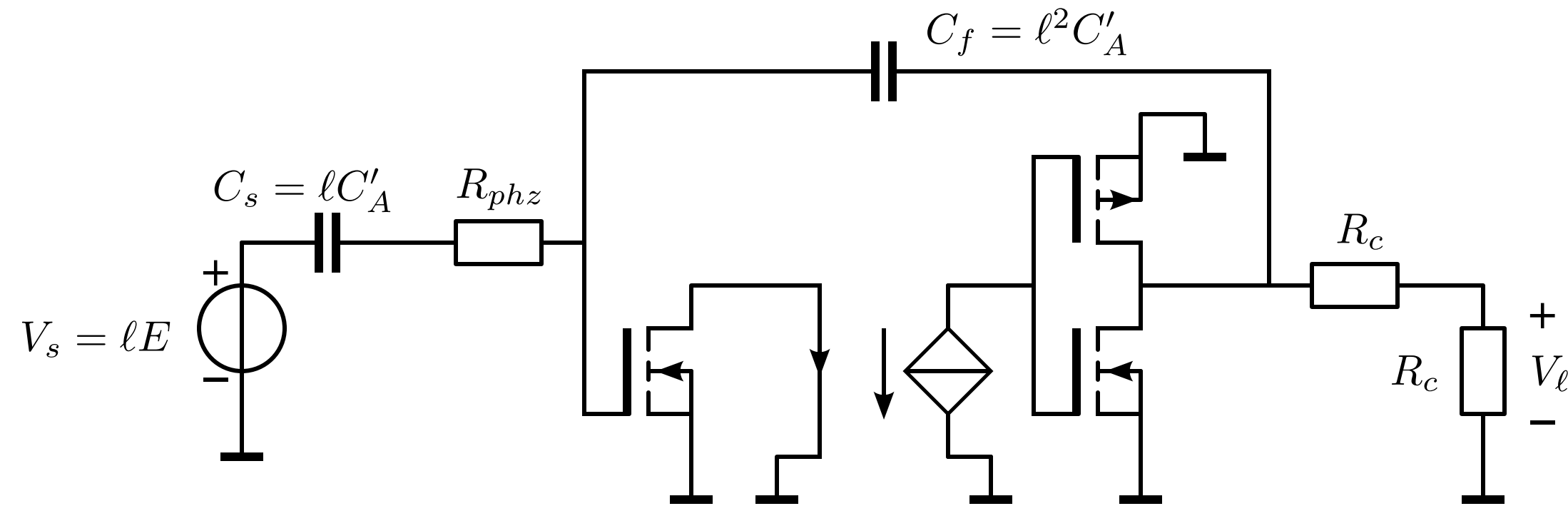

# Phantom-zero compensation

Circuit element values:

$$g_{m_1} = 23\text{m}$$


$$g_{m_2} = 28\text{m}$$

$$C_s = 5\text{p}$$


$$C_{iss1} = 1\text{p}$$

$$C_{iss2} = 1.2\text{p}$$

Achievable MFM bandwidth:

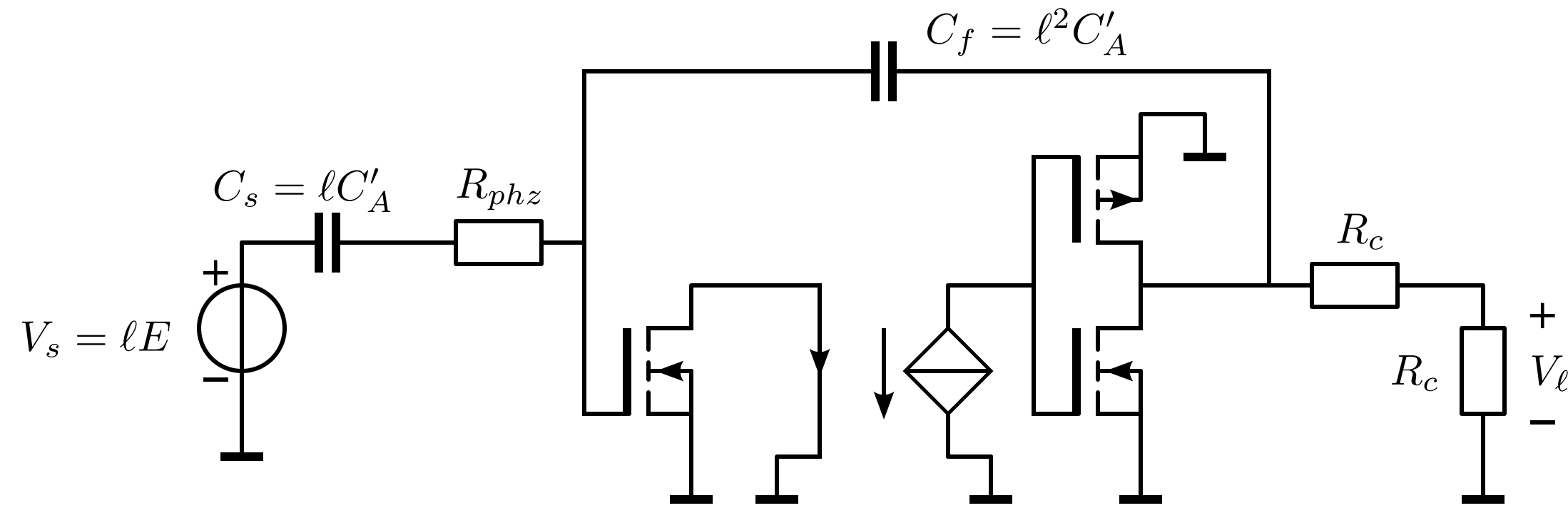

# Phantom-zero compensation

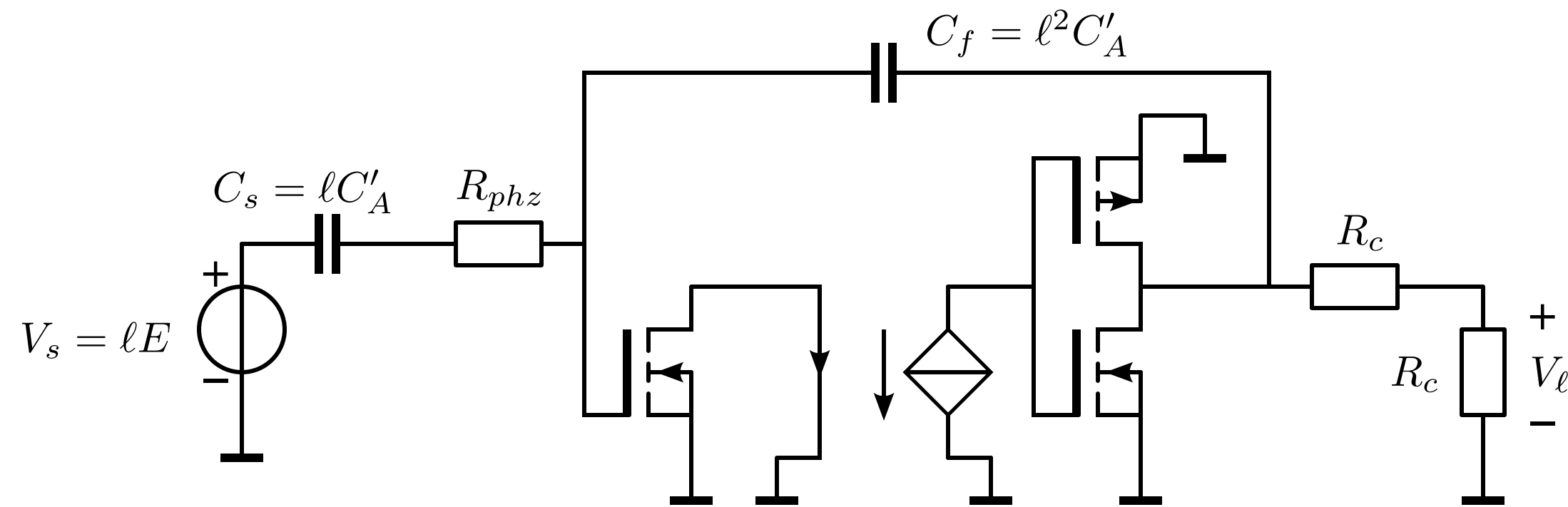

Circuit element values:

$$g_{m_1} = 23\text{m}$$

$$g_{m_2} = 28\text{m}$$

$$C_s = 5\text{p}$$


$$C_{iss1} = 1\text{p}$$

$$C_{iss2} = 1.2\text{p}$$

Achievable MFM bandwidth:

$$B_f = \frac{1}{2\pi} \sqrt{LP_2} = 1.5\text{GHz}$$

# Phantom-zero compensation

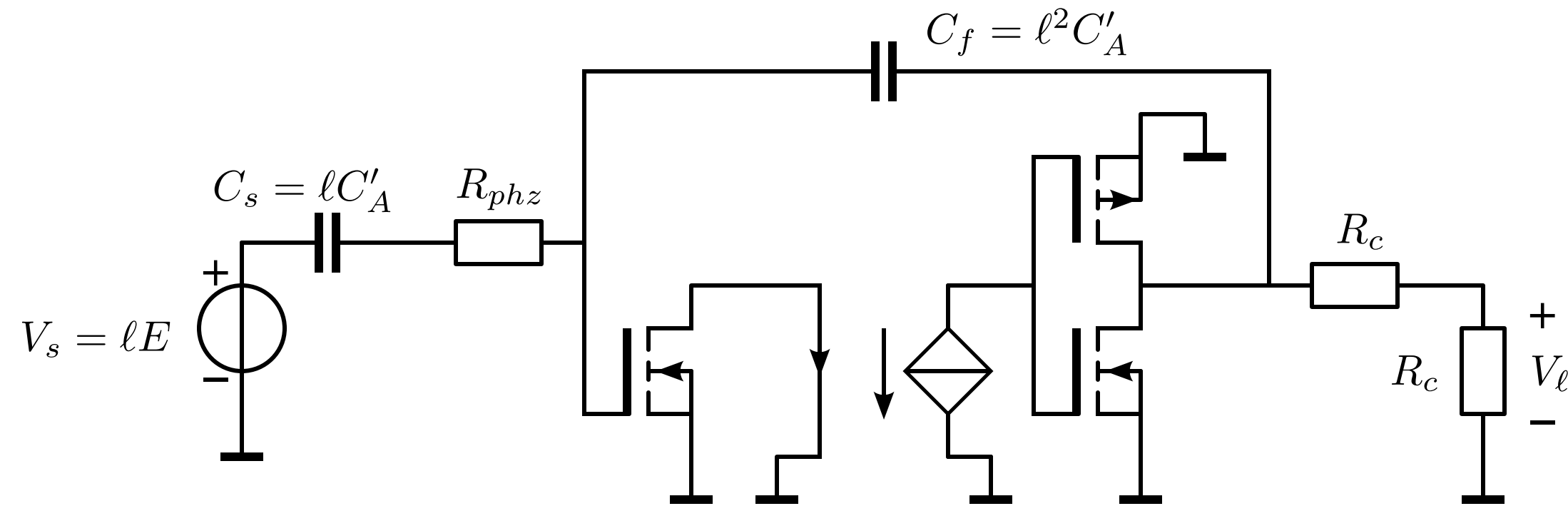

Circuit element values:

$$g_{m_1} = 23\text{m}$$

$$g_{m_2} = 28\text{m}$$

$$C_s = 5\text{p}$$

$$C_{iss1} = 1\text{p}$$


$$C_{iss2} = 1.2\text{p}$$

Achievable MFM bandwidth:

$$B_f = \frac{1}{2\pi} \sqrt{LP_2} = 1.5\text{GHz}$$

Sum of the poles:

# Phantom-zero compensation

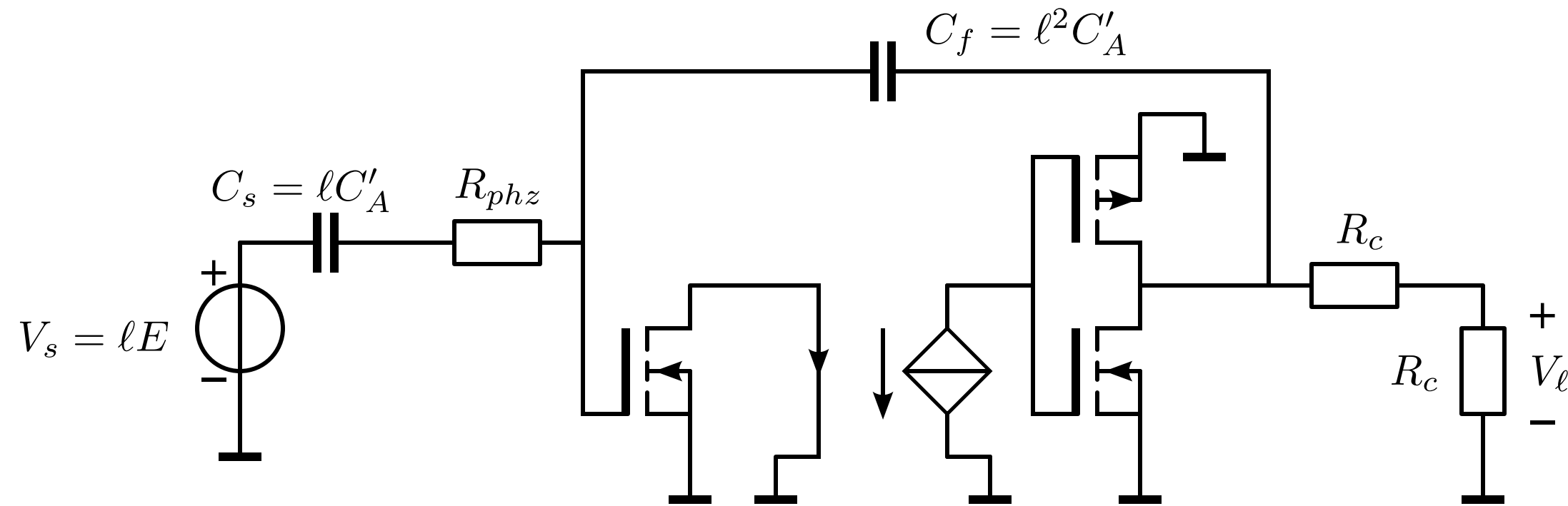

Circuit element values:

$$g_{m_1} = 23\text{m}$$

$$g_{m_2} = 28\text{m}$$

$$C_s = 5\text{p}$$

$$C_{iss1} = 1\text{p}$$

$$C_{iss2} = 1.2\text{p}$$


Achievable MFM bandwidth:

$$B_f = \frac{1}{2\pi} \sqrt{LP_2} = 1.5\text{GHz}$$

Sum of the poles:

$$p_1 = 0, p_2 = -\frac{C_f + C_s + C_{iss1}}{4\pi R_c C_f (C_s + C_{iss1})} = -450\text{MHz}$$

# Phantom-zero compensation

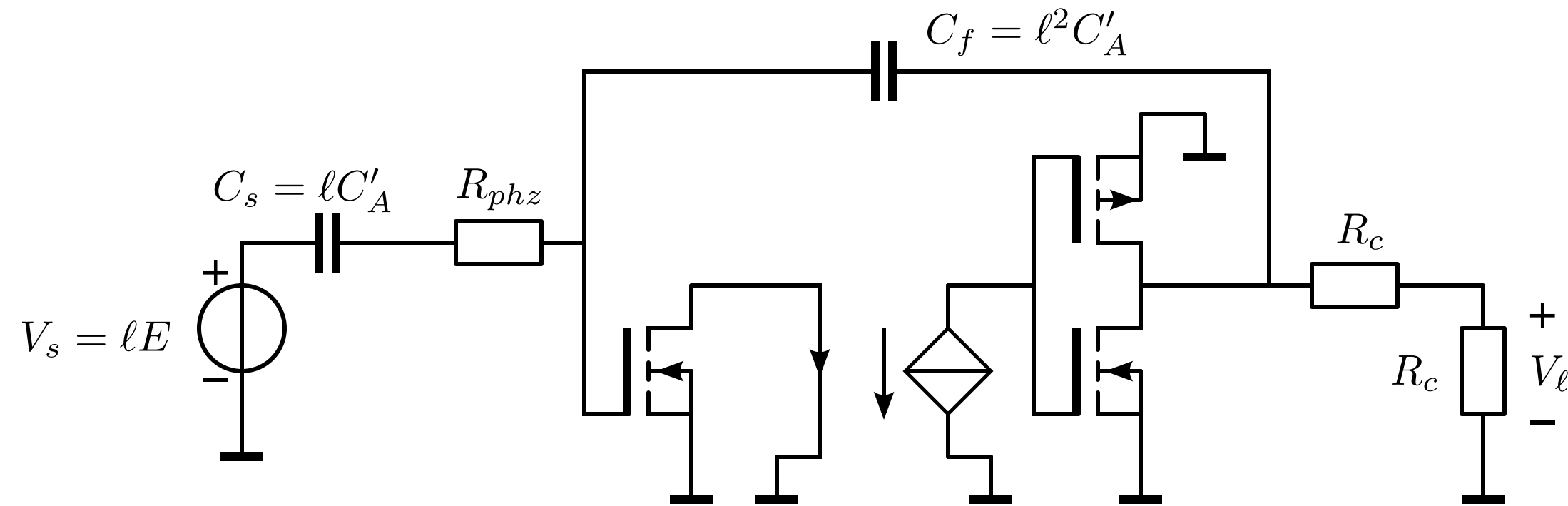

Circuit element values:

$$g_{m_1} = 23\text{m}$$

$$g_{m_2} = 28\text{m}$$

$$C_s = 5\text{p}$$

$$C_{iss1} = 1\text{p}$$

$$C_{iss2} = 1.2\text{p}$$

Achievable MFM bandwidth:


$$B_f = \frac{1}{2\pi} \sqrt{LP_2} = 1.5\text{GHz}$$

Sum of the poles:

$$p_1 = 0, p_2 = -\frac{C_f + C_s + C_{iss1}}{4\pi R_c C_f (C_s + C_{iss1})} = -450\text{MHz}$$

Frequency of the phantom zero

# Phantom-zero compensation

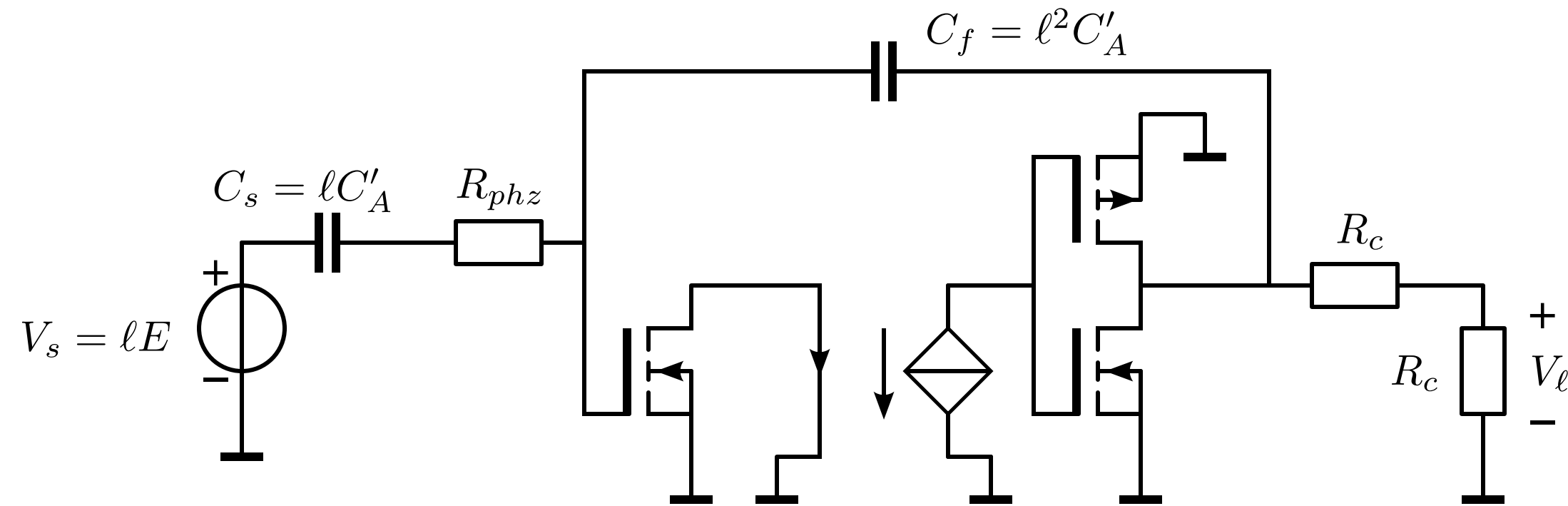

Circuit element values:

$$g_{m_1} = 23\text{m}$$

$$g_{m_2} = 28\text{m}$$

$$C_s = 5\text{p}$$

$$c_{iss1} = 1\text{p}$$

$$c_{iss2} = 1.2\text{p}$$

Achievable MFM bandwidth:

$$B_f = \frac{1}{2\pi} \sqrt{LP_2} = 1.5\text{GHz}$$

Sum of the poles:


$$p_1 = 0, p_2 = -\frac{C_f + C_s + c_{iss1}}{4\pi R_c C_f (C_s + c_{iss1})} = -450\text{MHz}$$

Frequency of the phantom zero

$$z = -\frac{B_f^2}{\sqrt{2}B_f + p_1 + p_2} = -\frac{1}{2\pi R_{phz} C_s} = -1\text{GHz}$$



# Phantom-zero compensation

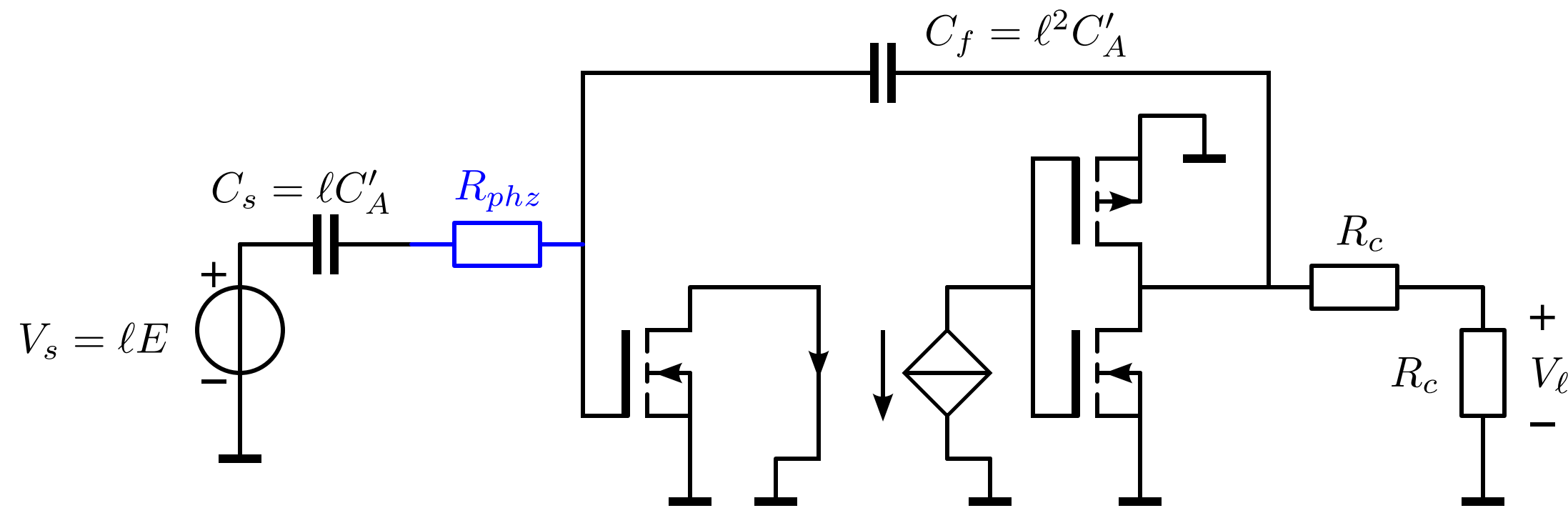

Circuit element values:

$$g_{m_1} = 23\text{m}$$

$$g_{m_2} = 28\text{m}$$

$$C_s = 5\text{p}$$

$$c_{iss1} = 1\text{p}$$

$$c_{iss2} = 1.2\text{p}$$

Achievable MFM bandwidth:

$$B_f = \frac{1}{2\pi} \sqrt{LP_2} = 1.5\text{GHz}$$

Sum of the poles:


$$p_1 = 0, p_2 = -\frac{C_f + C_s + c_{iss1}}{4\pi R_c C_f (C_s + c_{iss1})} = -450\text{MHz}$$

Frequency of the phantom zero

$$z = -\frac{B_f^2}{\sqrt{2}B_f + p_1 + p_2} = -\frac{1}{2\pi R_{phz} C_s} = -1\text{GHz}$$

Value of the compensation resistor

# Phantom-zero compensation

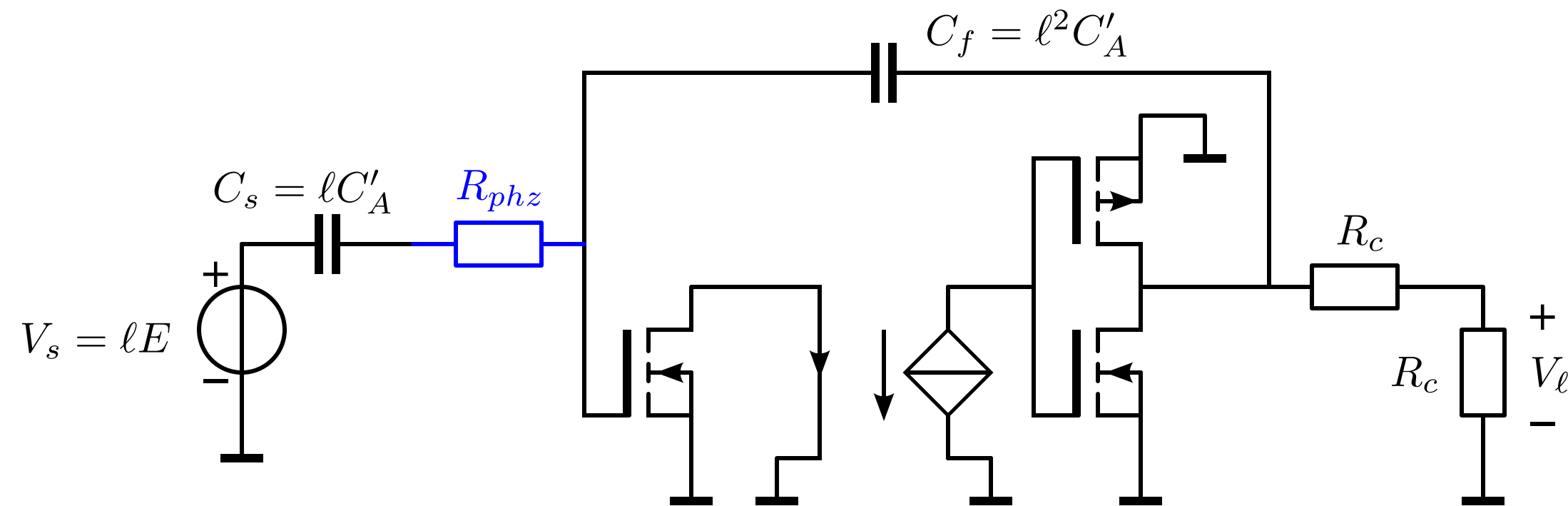

Circuit element values:

$$g_{m1} = 23\text{m}$$

$$g_{m2} = 28\text{m}$$

$$C_s = 5\text{p}$$

$$c_{iss1} = 1\text{p}$$

$$c_{iss2} = 1.2\text{p}$$

Achievable MFM bandwidth:

$$B_f = \frac{1}{2\pi} \sqrt{LP_2} = 1.5\text{GHz}$$

Sum of the poles:

$$p_1 = 0, p_2 = -\frac{C_f + C_s + c_{iss1}}{4\pi R_c C_f (C_s + c_{iss1})} = -450\text{MHz}$$


Frequency of the phantom zero

$$z = -\frac{B_f^2}{\sqrt{2}B_f + p_1 + p_2} = -\frac{1}{2\pi R_{phz} C_s} = -1\text{GHz}$$

Value of the compensation resistor

$$R_{phz} = -\frac{1}{2\pi z C_s} = 30\Omega$$

# Phantom-zero compensation

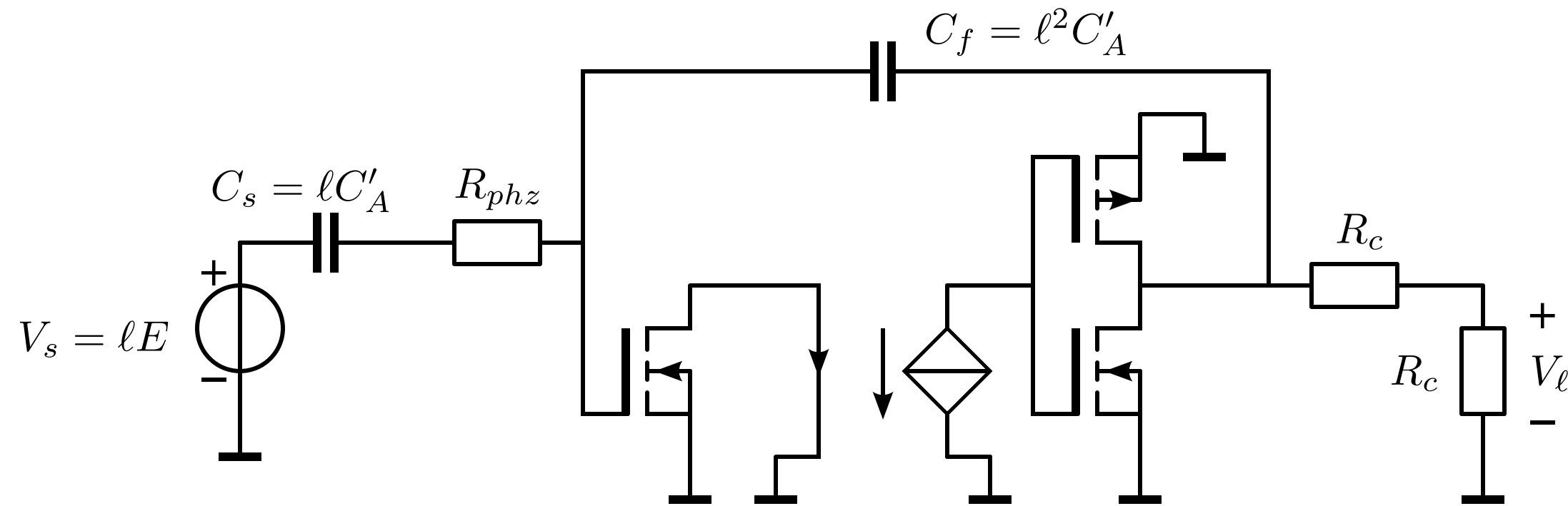

Circuit element values:

$$g_{m1} = 23\text{m}$$

$$g_{m2} = 28\text{m}$$

$$C_s = 5\text{p}$$

$$c_{iss1} = 1\text{p}$$

$$c_{iss2} = 1.2\text{p}$$

Achievable MFM bandwidth:

$$B_f = \frac{1}{2\pi} \sqrt{LP_2} = 1.5\text{GHz}$$

Sum of the poles:

$$p_1 = 0, p_2 = -\frac{C_f + C_s + c_{iss1}}{4\pi R_c C_f (C_s + c_{iss1})} = -450\text{MHz}$$

Frequency of the phantom zero

$$z = -\frac{B_f^2}{\sqrt{2}B_f + p_1 + p_2} = -\frac{1}{2\pi R_{phz} C_s} = -1\text{GHz}$$

Value of the compensation resistor

$$R_{phz} = -\frac{1}{2\pi z C_s} = 30\Omega$$


# **Structured Electronic Design**

## Step 7

Design of the biasing concept  
(ideal bias sources)


*Anton J.M. Montagne*

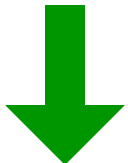Design of independent performance aspects



interaction between design aspects

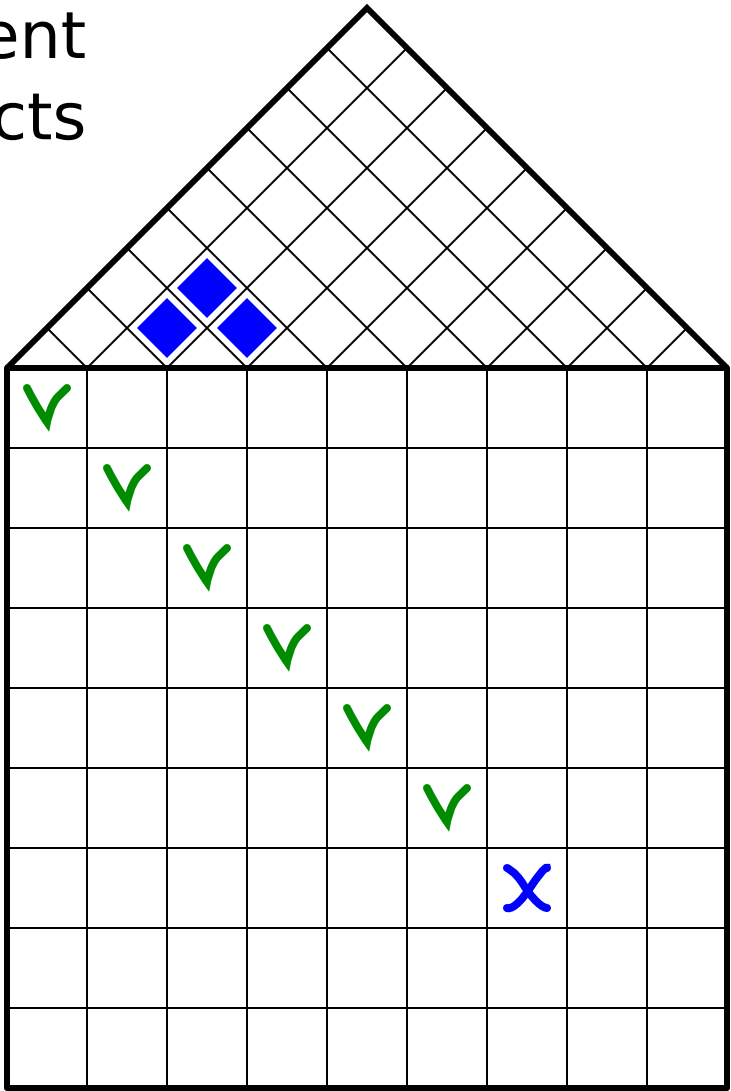Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)




SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure


design aspects

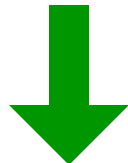Design of independent performance aspects



interaction between design aspects

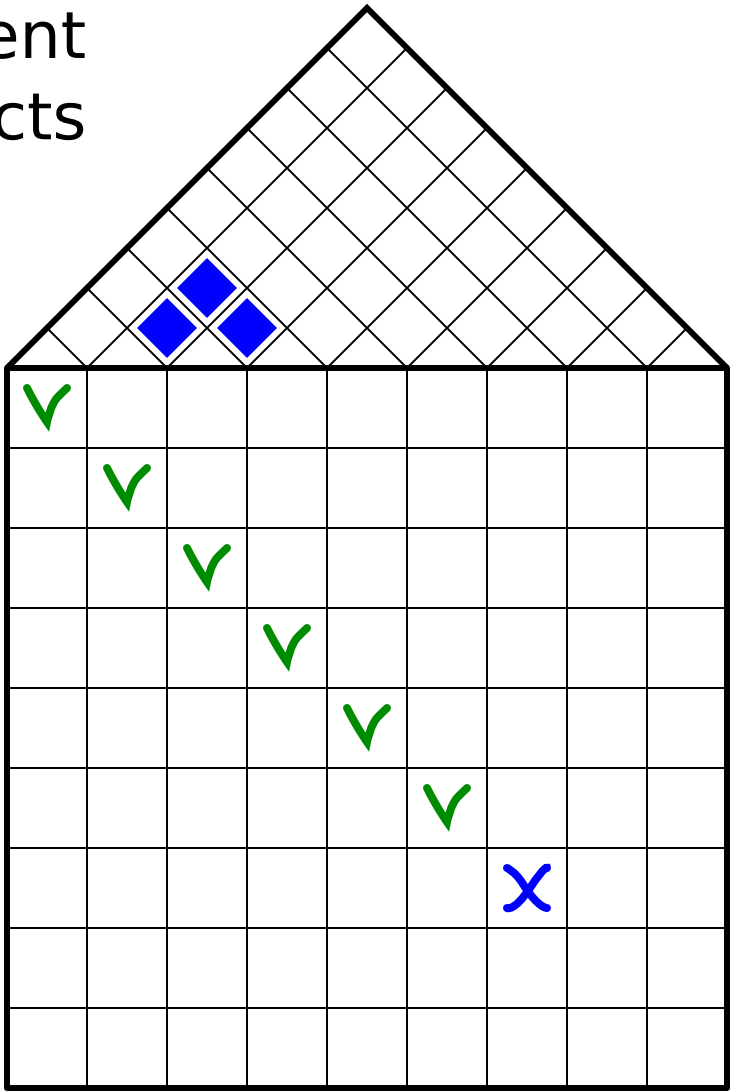*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)




SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice

**Biasing concept**

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure


design aspects

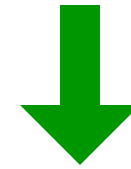Design of independent performance aspects



interaction between design aspects

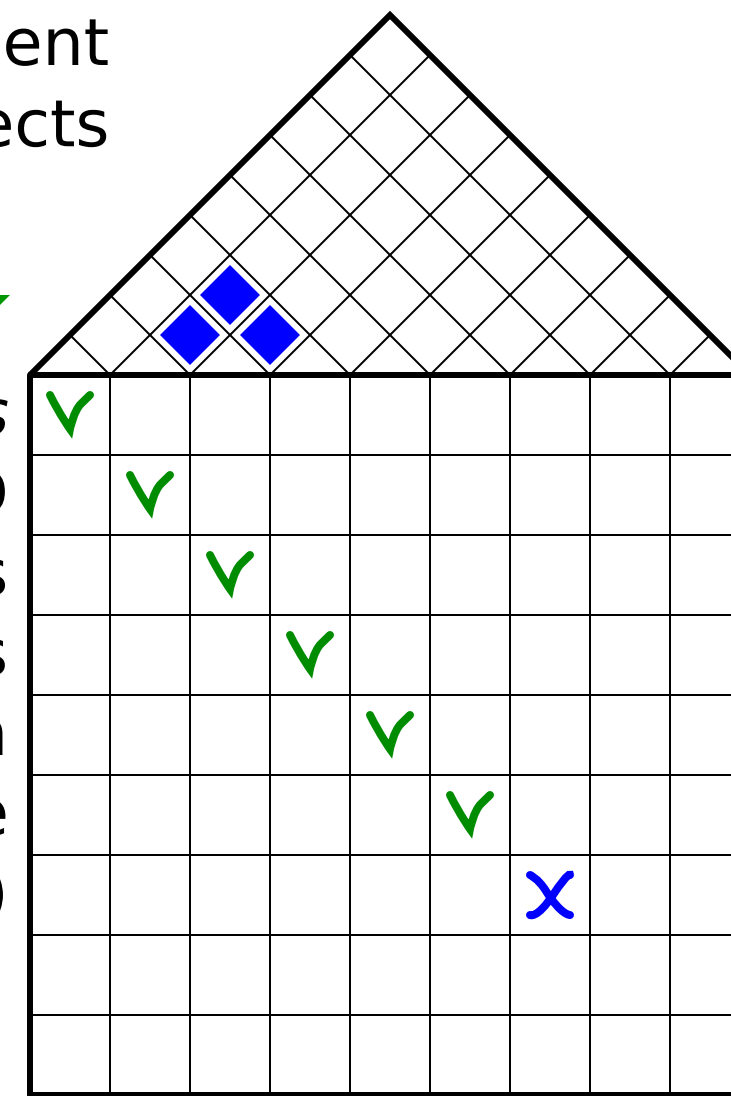*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice


**Biasing concept**

Connect the circuit to the power supply

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure


design aspects

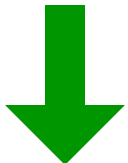Design of independent performance aspects



interaction between design aspects

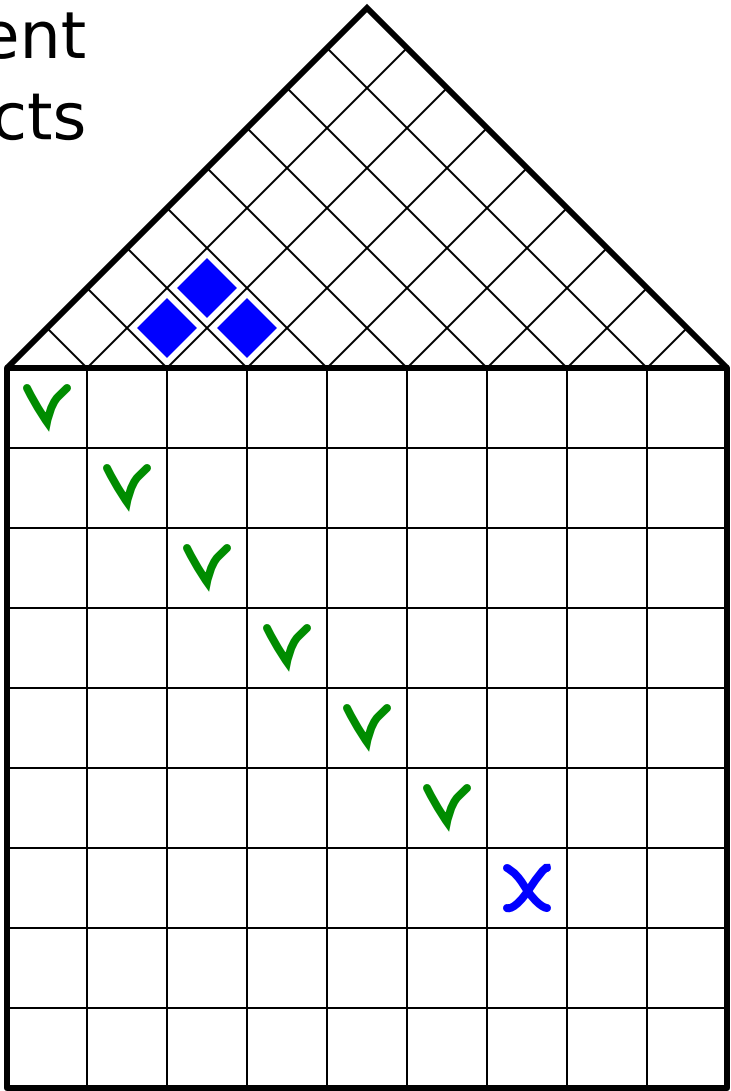*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice

**Biasing concept**


Connect the circuit to the power supply  
 Redirect bias current sources over the power supply

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure

design aspects




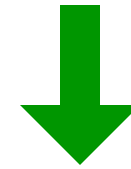Design of independent performance aspects



interaction between design aspects

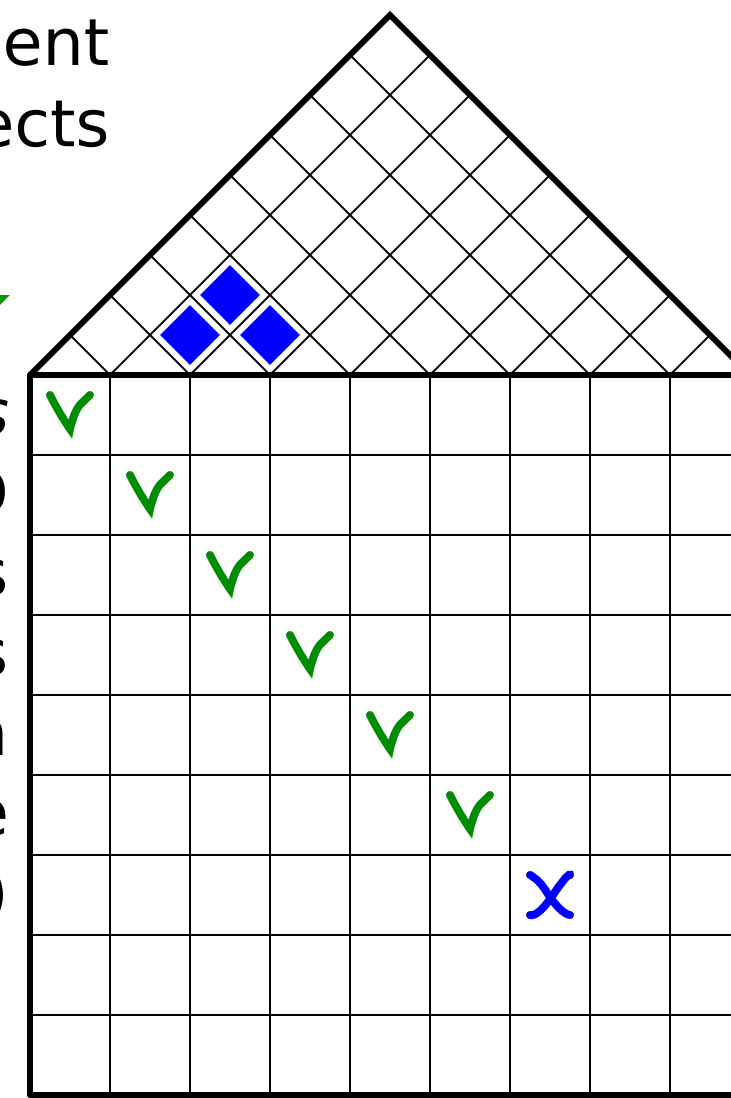*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice


### Biasing concept

- Connect the circuit to the power supply
- Redirect bias current sources over the power supply
- Minimize the number of floating voltage sources

*Function, performance, costs and environment*  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure


design aspects

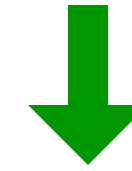Design of independent performance aspects



interaction between design aspects

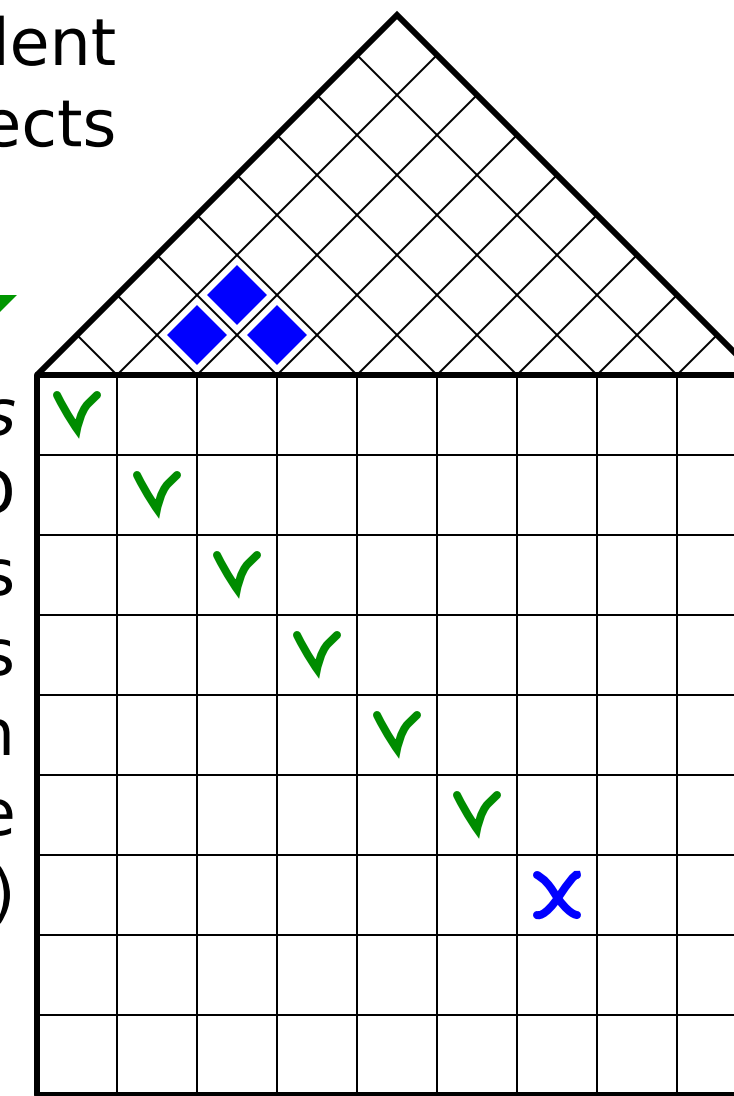*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice


## Biasing concept

- Connect the circuit to the power supply
- Redirect bias current sources over the power supply
- Minimize the number of floating voltage sources
- [Apply error reduction techniques to improve biasing stability](#)

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure


design aspects

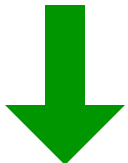Design of independent performance aspects



interaction between design aspects

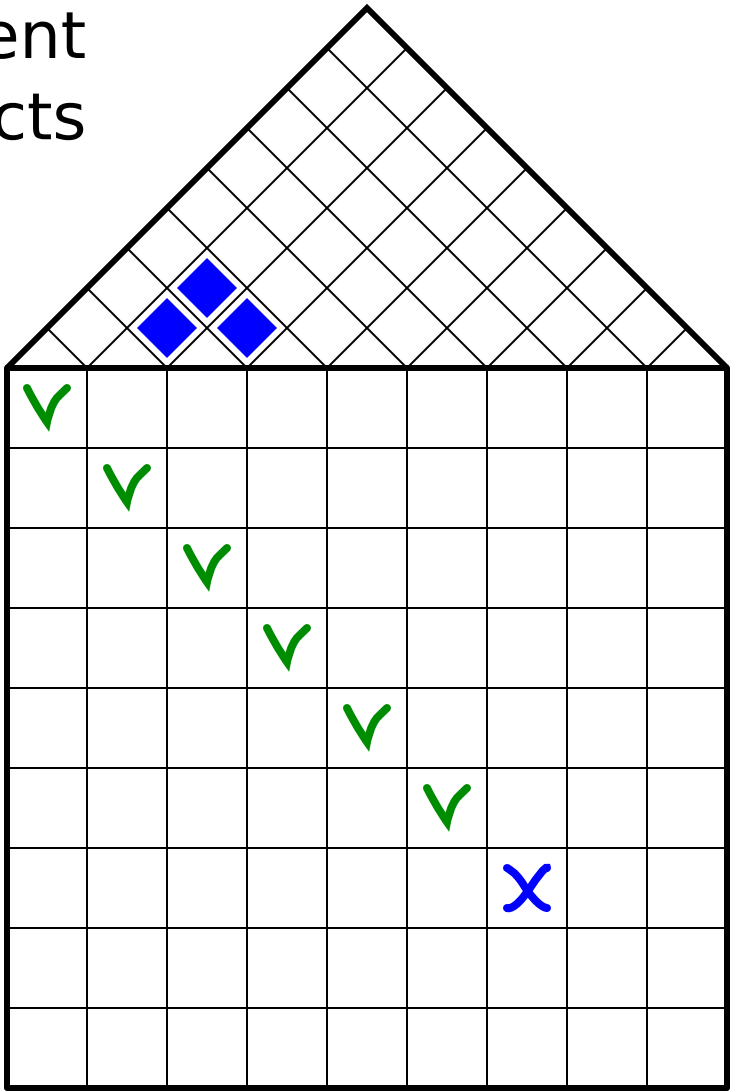*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice

**Biasing concept**


- Connect the circuit to the power supply
- Redirect bias current sources over the power supply
- Minimize the number of floating voltage sources
- Apply error reduction techniques to improve biasing stability

**Design of the active antenna:**

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure


design aspects

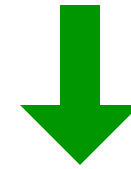Design of independent performance aspects



interaction between design aspects

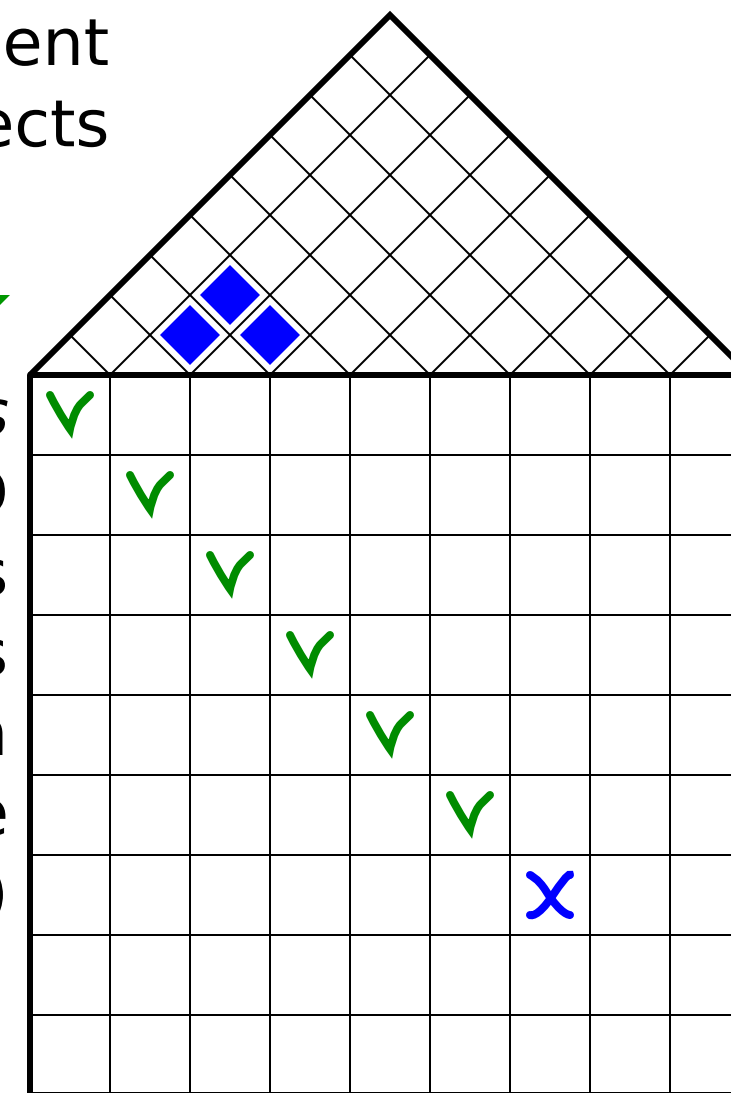*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice

**Biasing concept**

- Connect the circuit to the power supply
- Redirect bias current sources over the power supply
- Minimize the number of floating voltage sources
- Apply error reduction techniques to improve biasing stability


**Design of the active antenna:**

1.8V supply

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure


design aspects

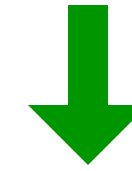Design of independent performance aspects



interaction between design aspects

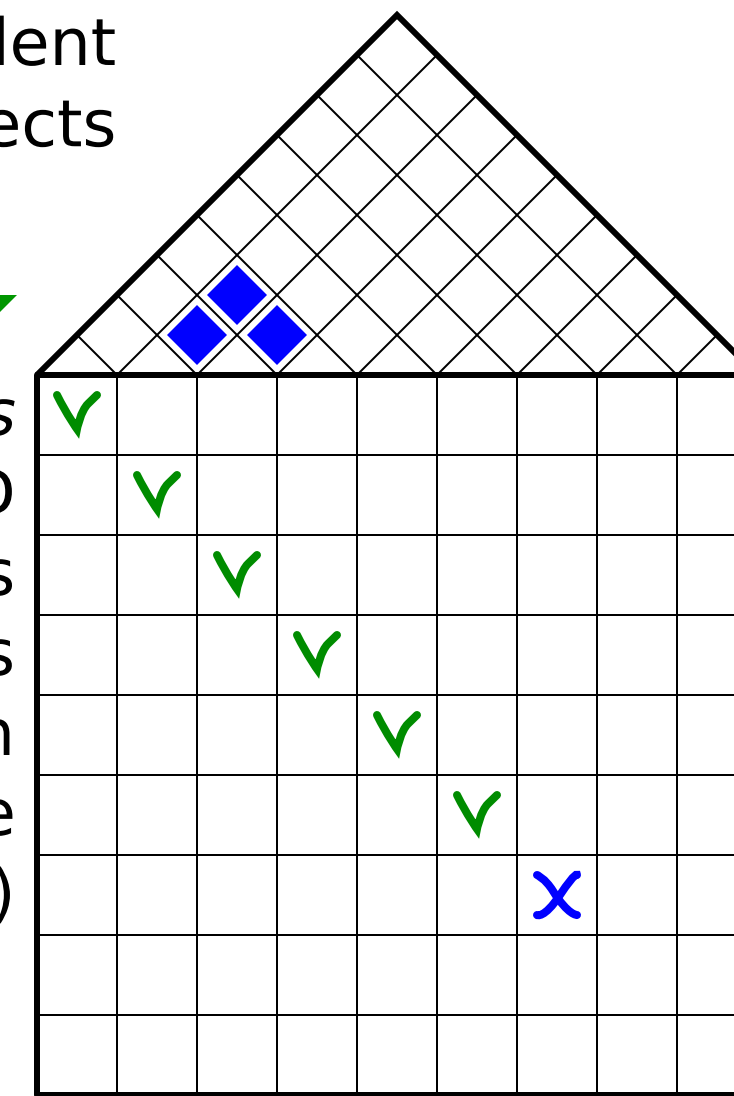*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice

### Biasing concept

- Connect the circuit to the power supply
- Redirect bias current sources over the power supply
- Minimize the number of floating voltage sources
- Apply error reduction techniques to improve biasing stability


### Design of the active antenna:

- 1.8V supply
- Redirected current sources

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure


design aspects

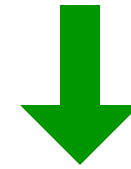Design of independent performance aspects



interaction between design aspects

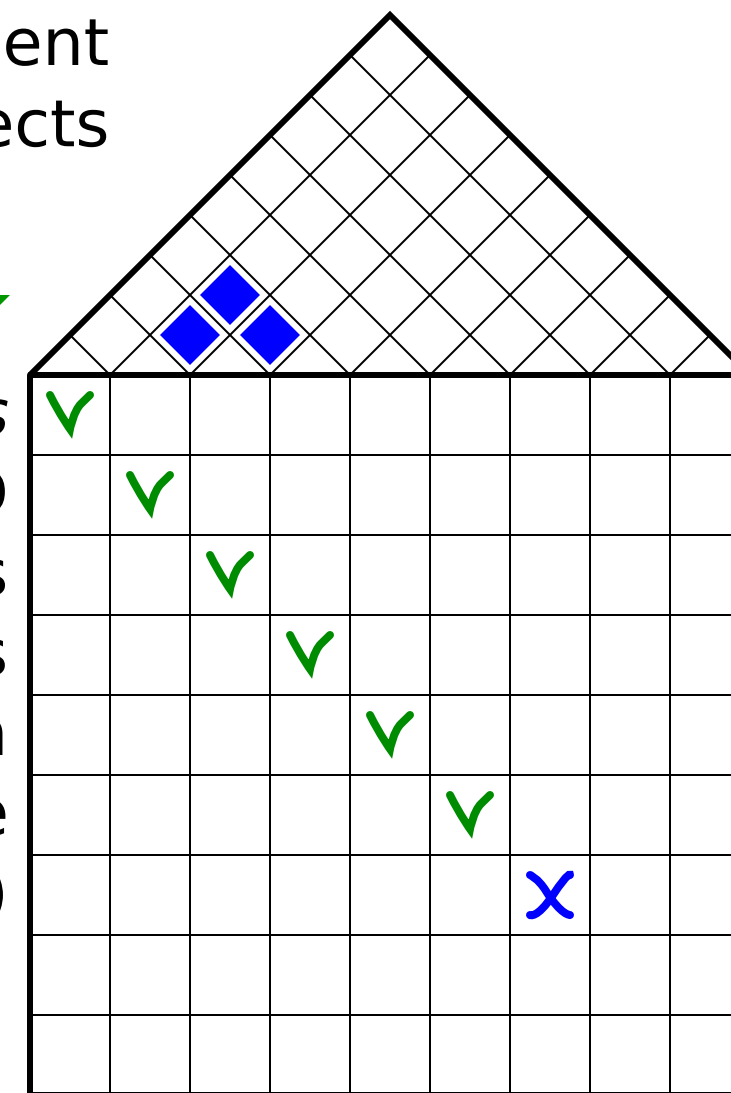*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice

**Biasing concept**

- Connect the circuit to the power supply
- Redirect bias current sources over the power supply
- Minimize the number of floating voltage sources
- Apply error reduction techniques to improve biasing stability


**Design of the active antenna:**

- 1.8V supply
- Redirected current sources
- AC coupling

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure


design aspects

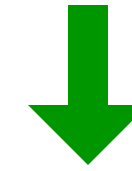Design of independent performance aspects



interaction between design aspects

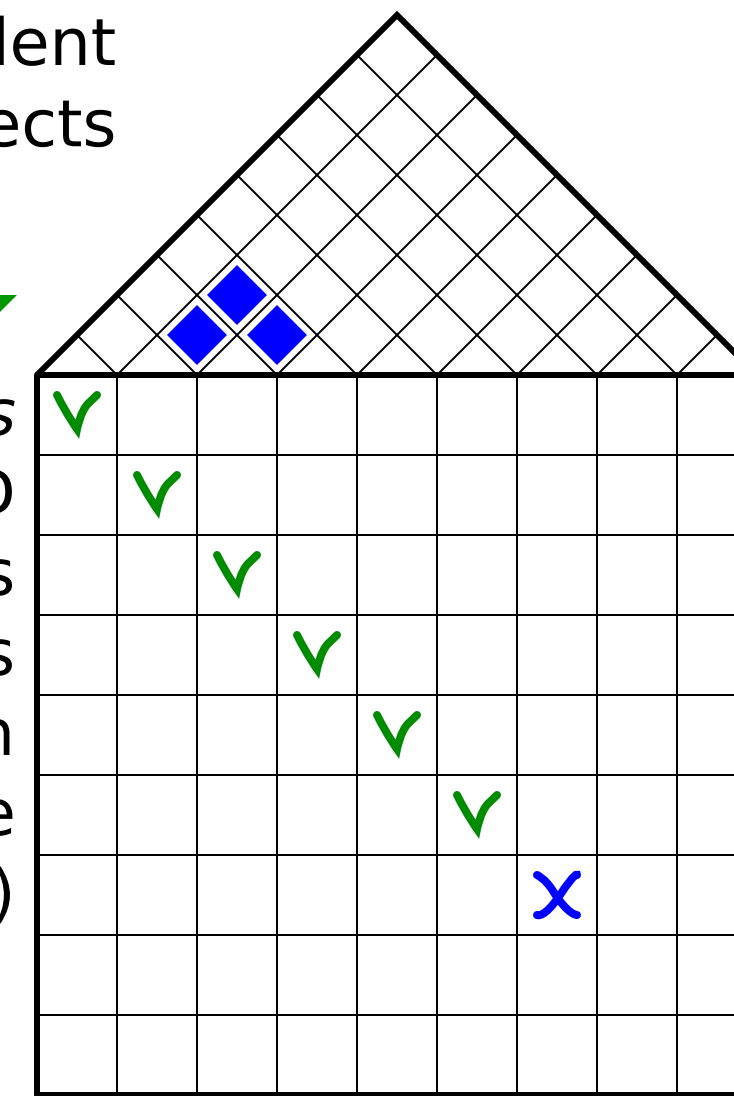Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice

### Biasing concept

- Connect the circuit to the power supply
- Redirect bias current sources over the power supply
- Minimize the number of floating voltage sources
- Apply error reduction techniques to improve biasing stability


### Design of the active antenna:

- 1.8V supply
- Redirected current sources
- AC coupling
- Over-all negative-feedback biasing

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure


design aspects

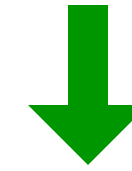Design of independent performance aspects



interaction between design aspects

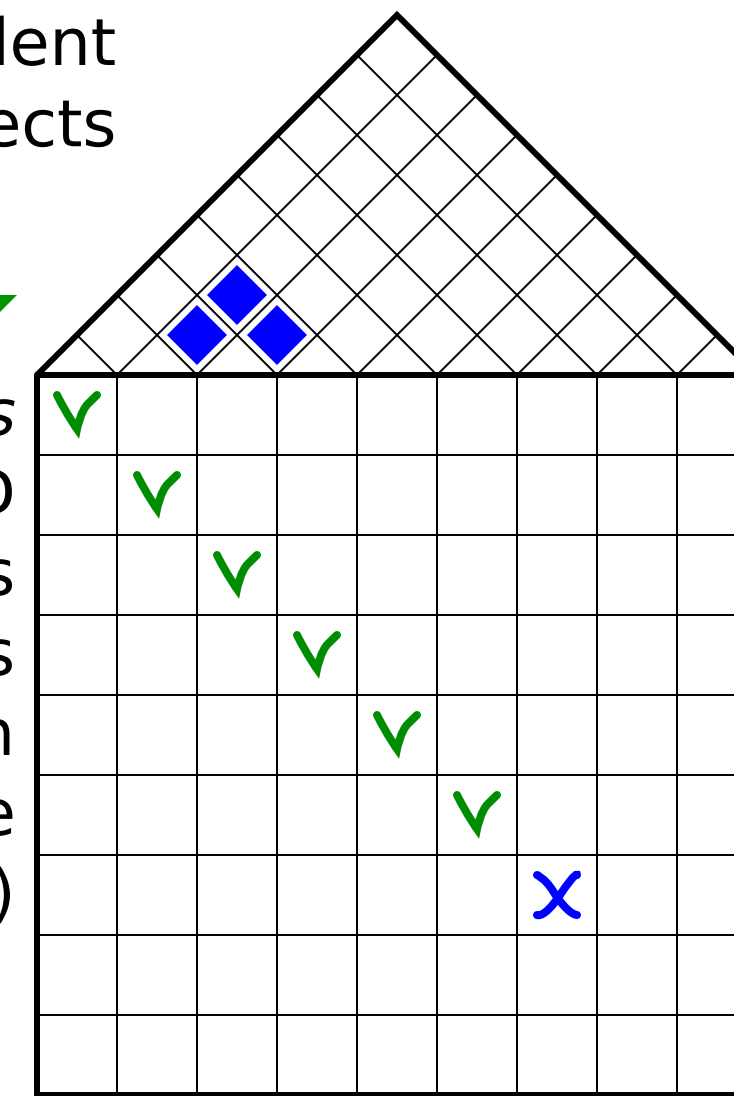*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice

### Biasing concept

- Connect the circuit to the power supply
- Redirect bias current sources over the power supply
- Minimize the number of floating voltage sources
- Apply error reduction techniques to improve biasing stability

### Design of the active antenna:

- 1.8V supply
- Redirected current sources
- AC coupling
- Over-all negative-feedback biasing


Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure

design aspects




# Biasing concept

# Biasing concept

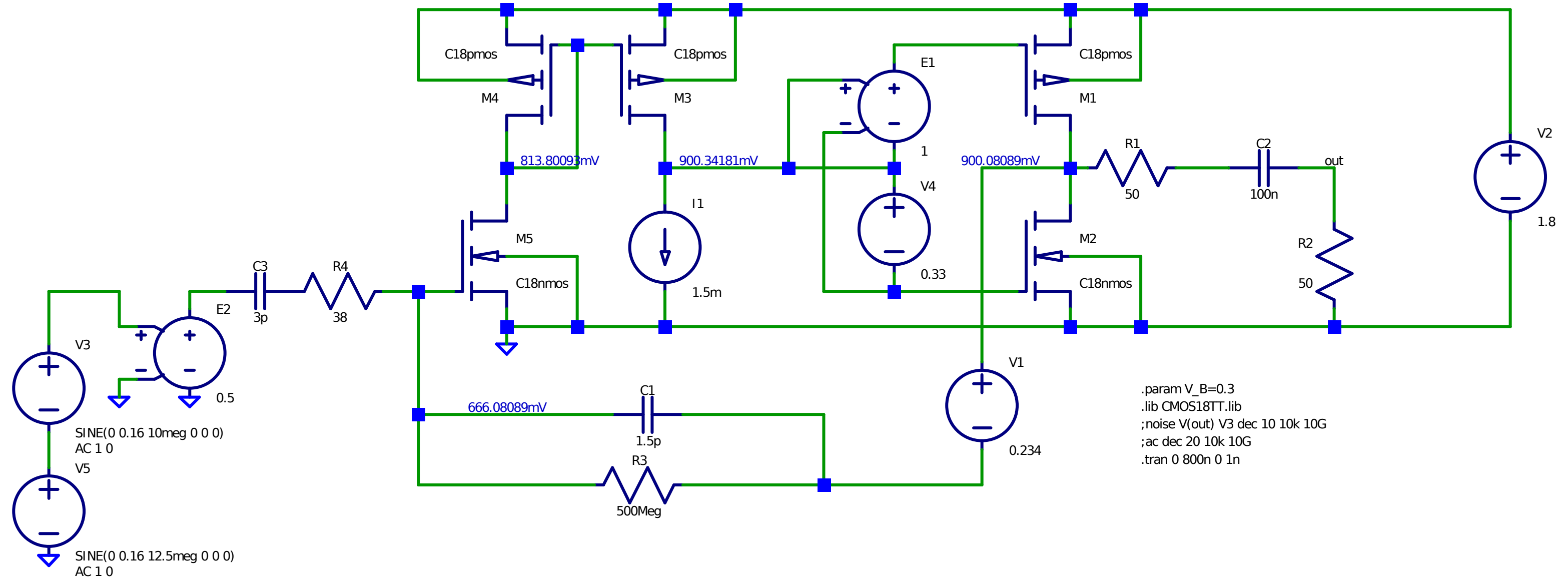


# Biasing concept

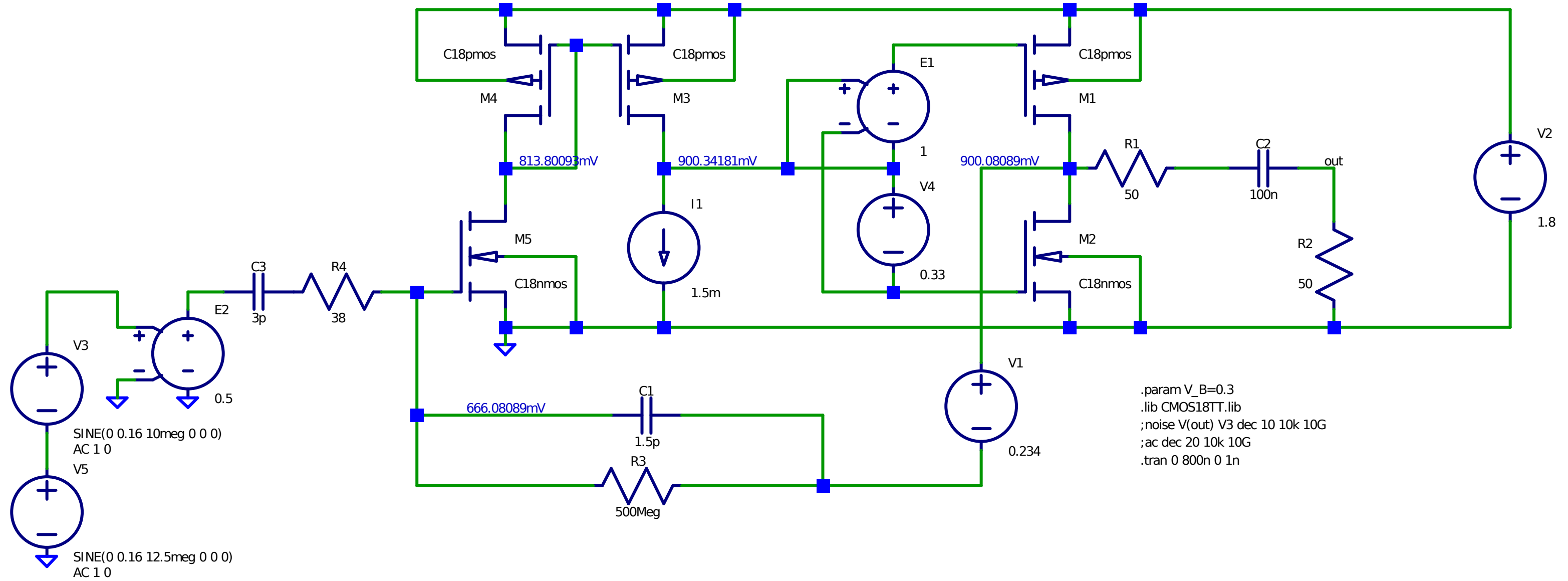

Single supply


# Biassing concept

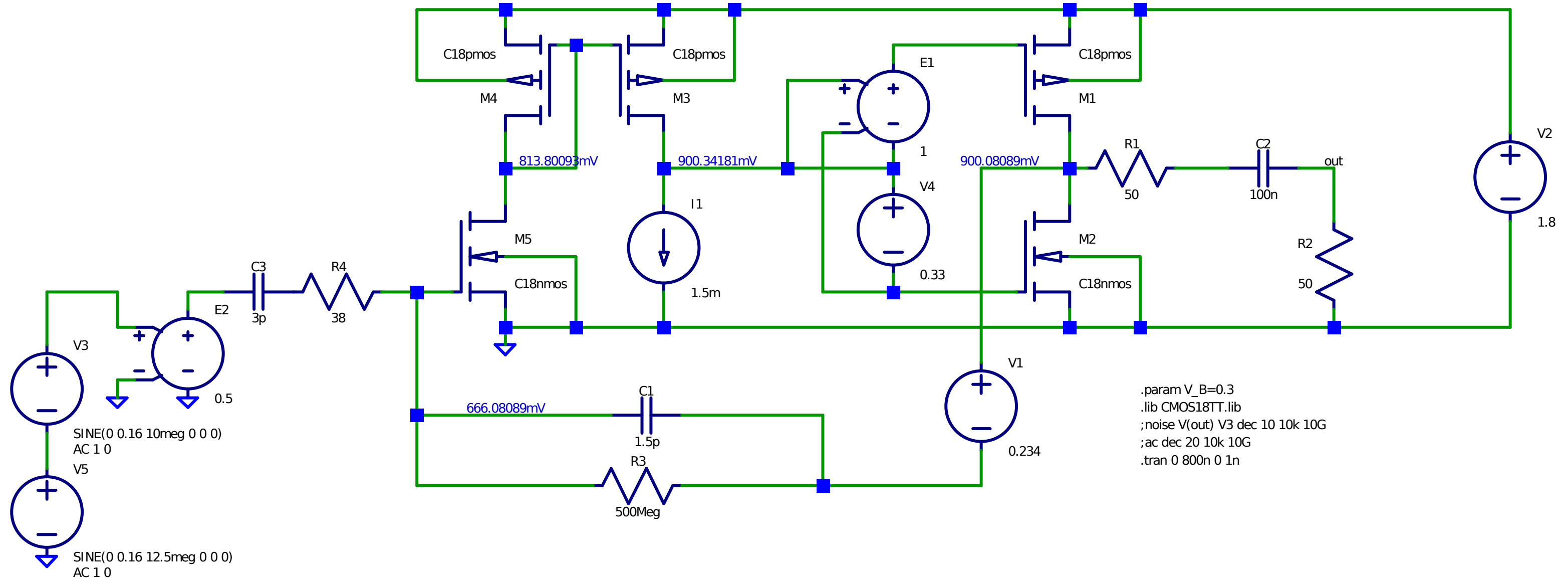

Single supply

Bias current sources redirected via supply and combined

# Biasing concept

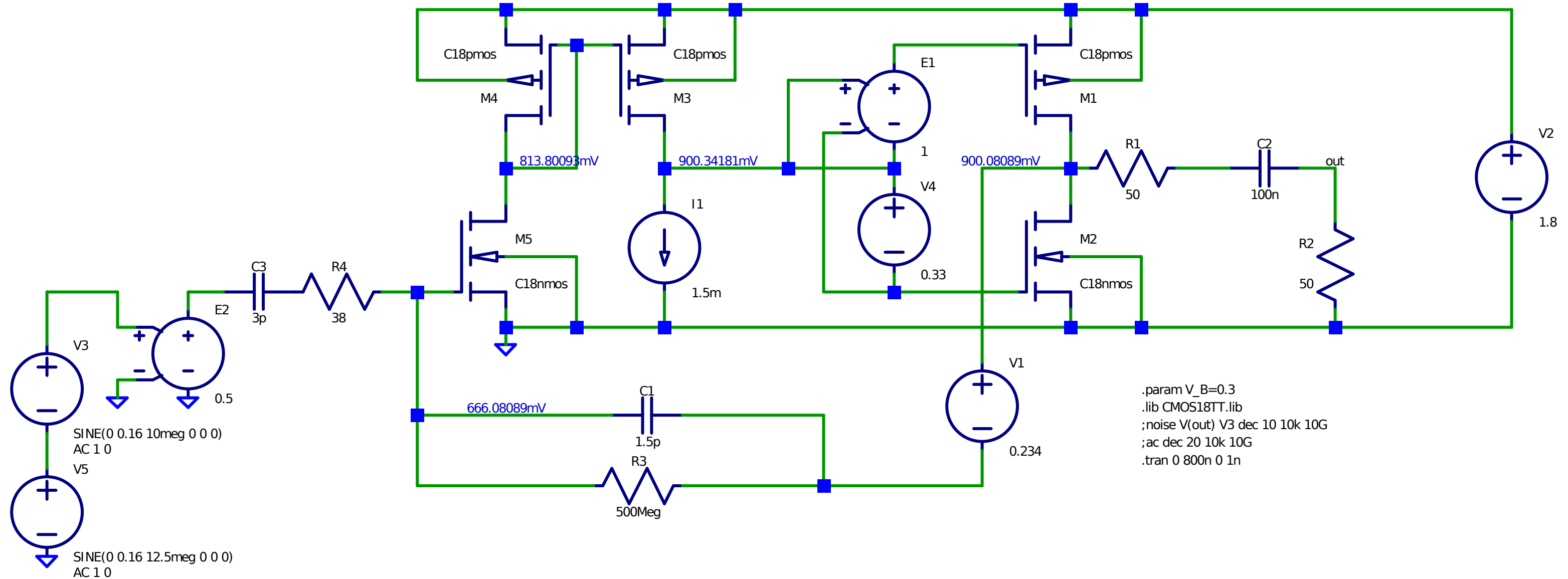


Single supply

Bias current sources redirected via supply and combined

AC coupling and over-all negative feedback biasing

# Biasing concept

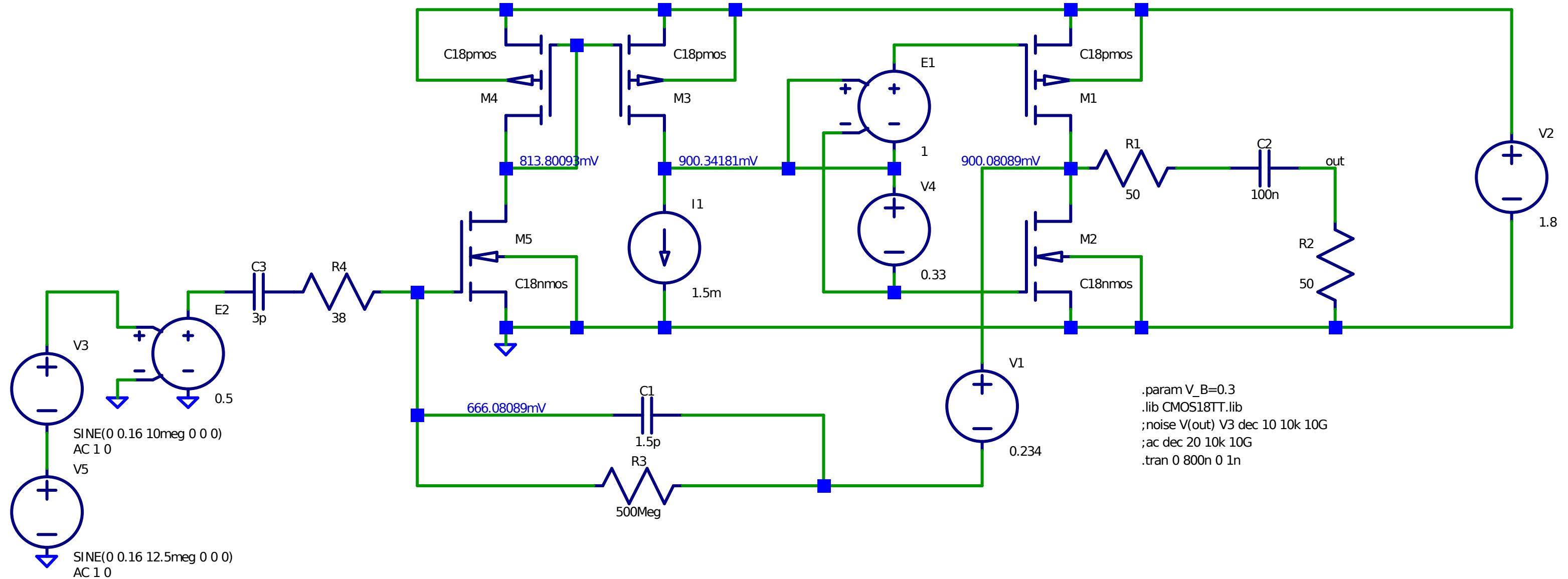


Single supply

Bias current sources redirected via supply and combined  
AC coupling and over-all negative feedback biasing

Two or three remaining floating voltage sources

# Biasing concept

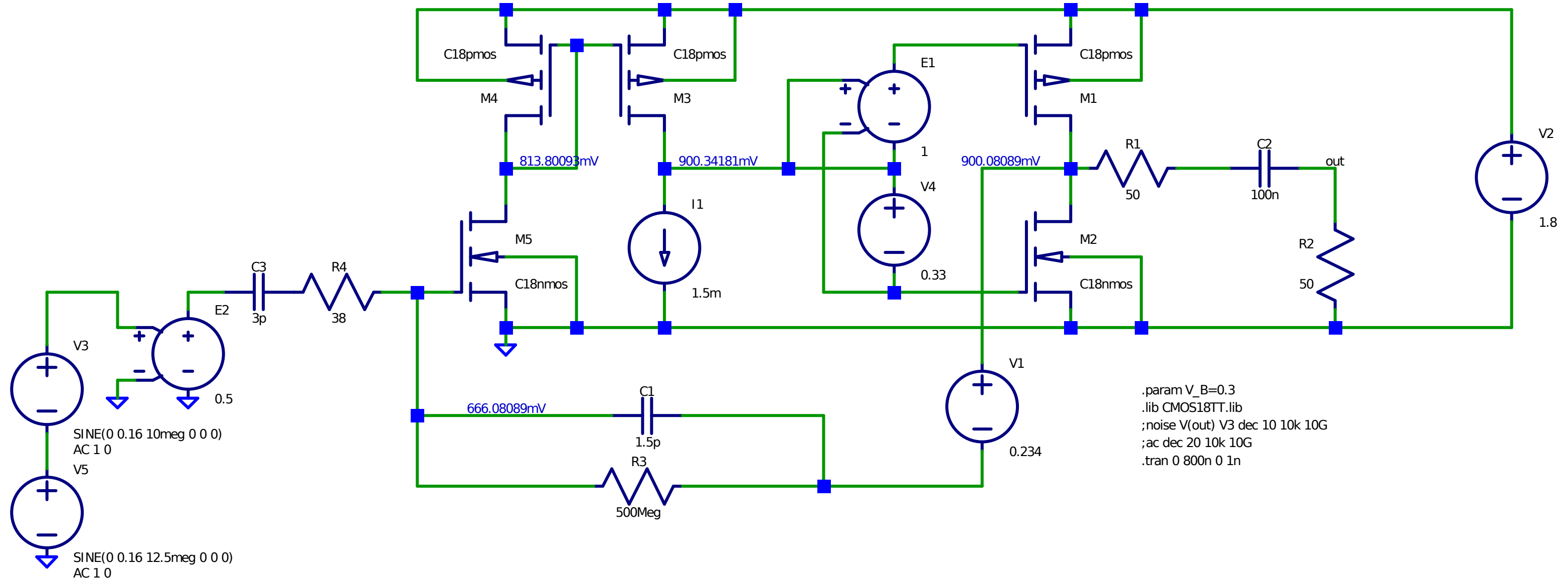

Single supply

Bias current sources redirected via supply and combined

AC coupling and over-all negative feedback biasing

Two or three remaining floating voltage sources

# **Structured Electronic Design**

## Step 8

Design of the sufficiently low weak nonlinearity  
(ideal bias sources)


*Anton J.M. Montagne*



Design of independent performance aspects

interaction between design aspects

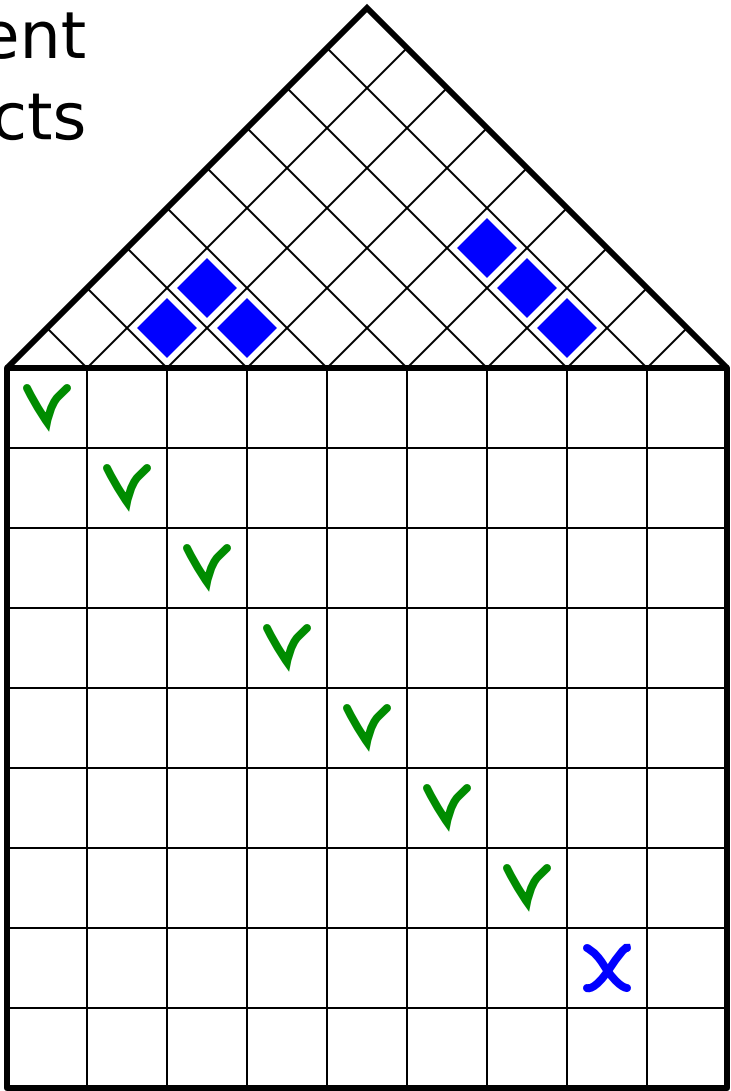- Setting up specifications
- Design of amplifier type: A, B, C, D
- Feasibility of noise (temperature drift) specifications
- Feasibility of static and dynamic drive requirements
- Design of midband accuracy and amplifier bandwidth
- Design of the frequency response
- Design of the biasing (ideal sources)
- Design of sufficiently low weak nonlinearity




- SLiCAP
- SLiCAP
- SLiCAP
- LTspice
- SLiCAP
- SLiCAP
- LTspice
- LTspice


- Function, performance, costs and environment
- Feedback configuration
- Controller input stage
- Controller output stage
- Loop gain poles product
- PZ pattern
- Bias structure
- Differential error to gain ratio

design aspects

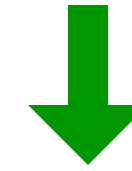
Design of independent performance aspects



interaction between design aspects

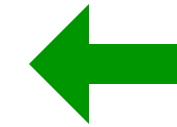

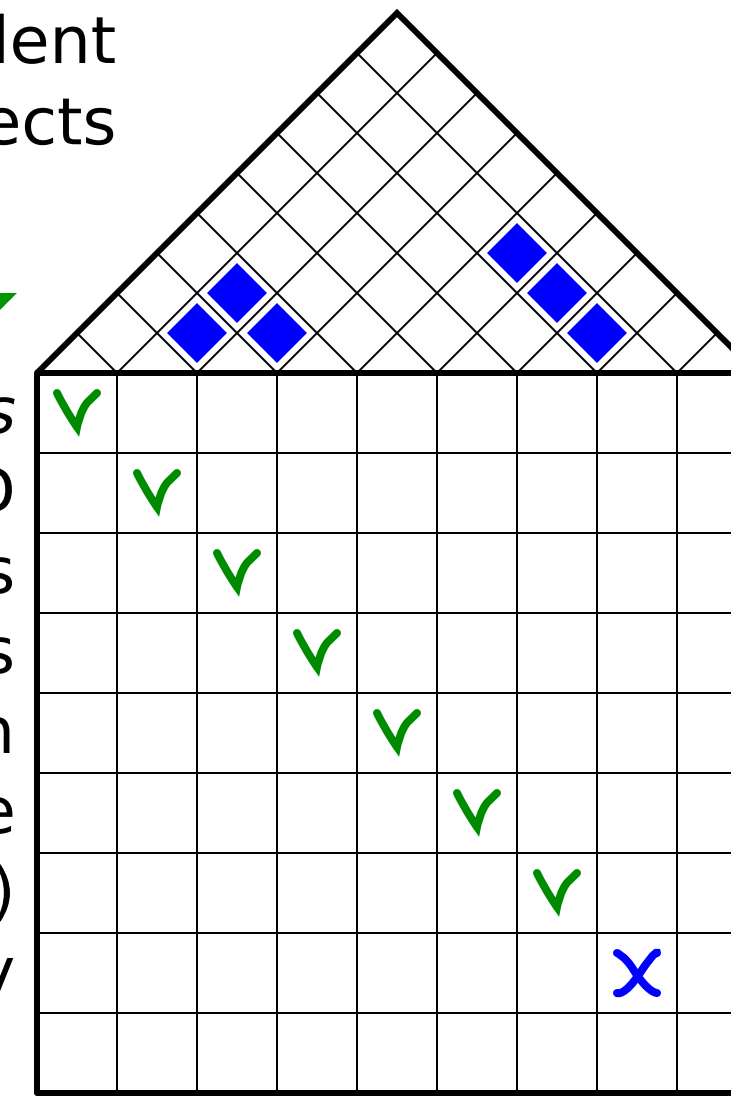
Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)  
 Design of sufficiently low weak nonlinearity



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice

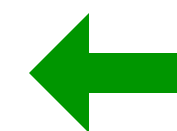
**Differential-error-to-gain ratio**

Function, performance,  
 costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio




design aspects

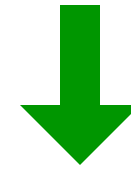Design of independent performance aspects



interaction between design aspects

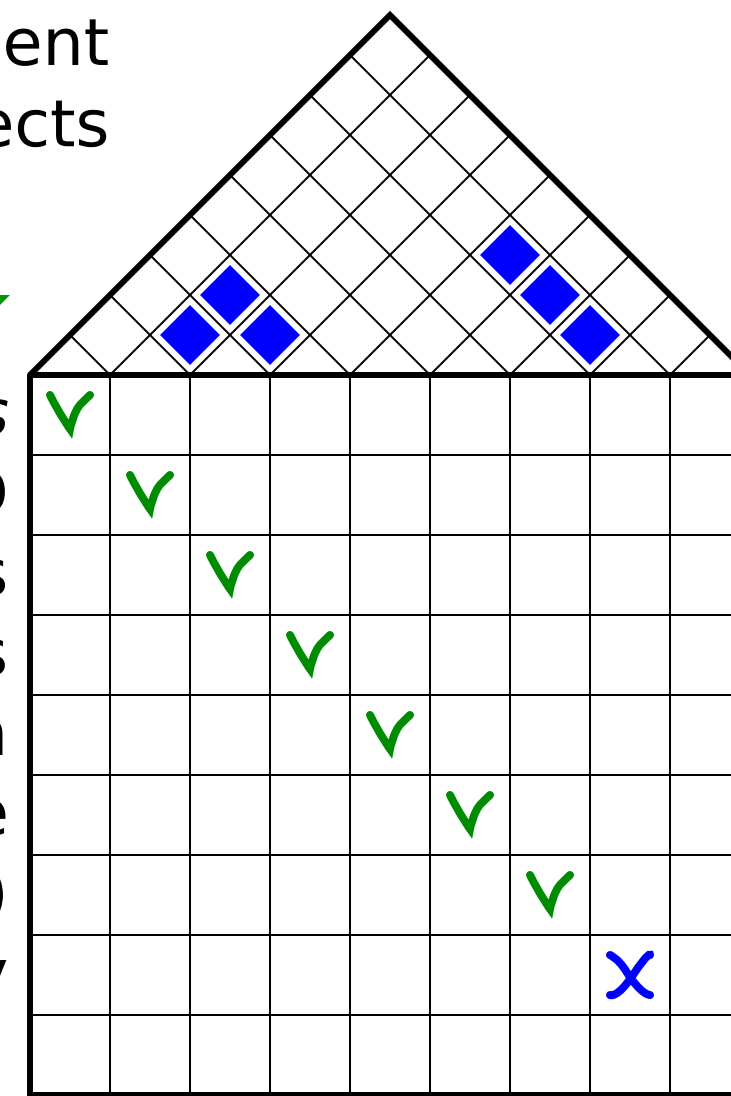*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)  
 Design of sufficiently low weak nonlinearity



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice


### Differential-error-to-gain ratio

Verify the biasing (operating point of all devices)

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio


design aspects

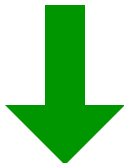Design of independent performance aspects



interaction between design aspects

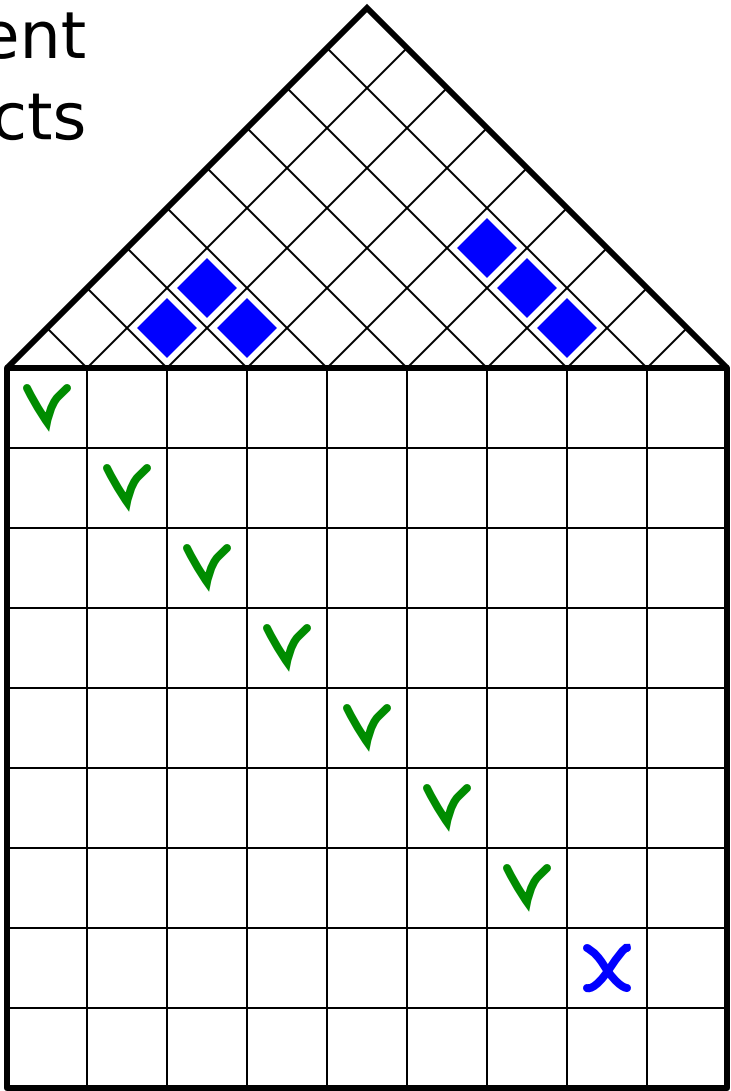*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)  
 Design of sufficiently low weak nonlinearity



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice


**Differential-error-to-gain ratio**

Verify the biasing (operating point of all devices)  
 Verify all performance aspects

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio


design aspects

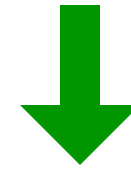Design of independent performance aspects



interaction between design aspects

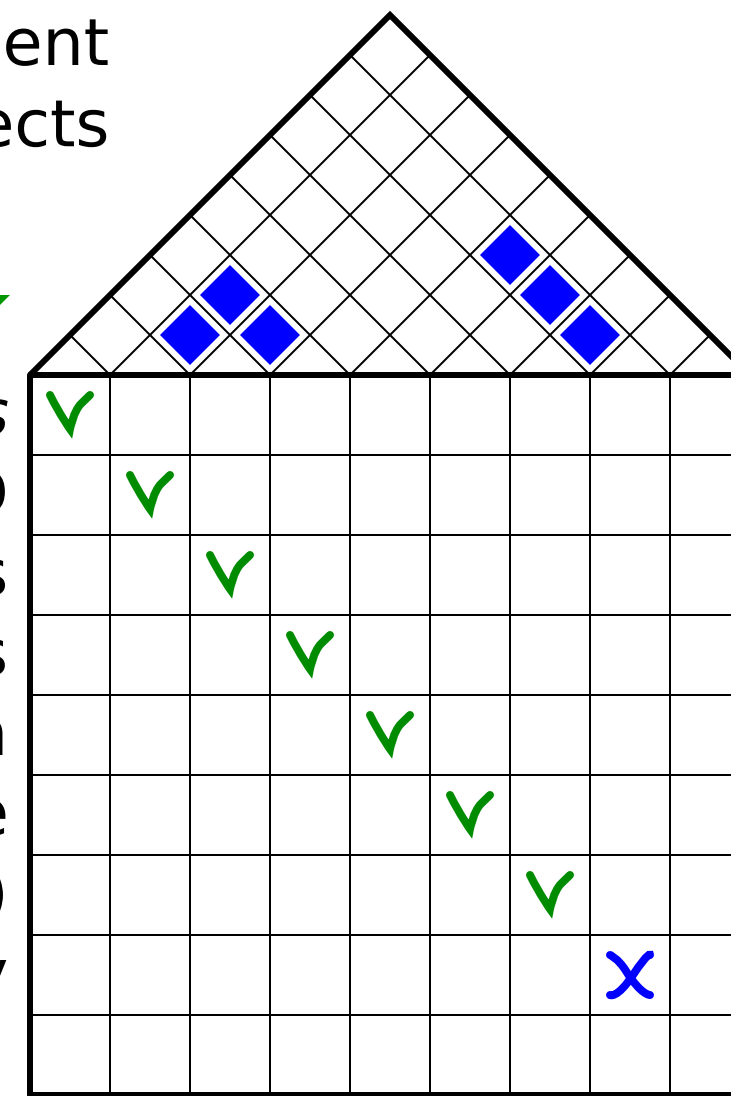*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)  
 Design of sufficiently low weak nonlinearity



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice

### Differential-error-to-gain ratio


Verify the biasing (operating point of all devices)  
 Verify all performance aspects

The weak nonlinearity can be reduced by:


Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio

design aspects

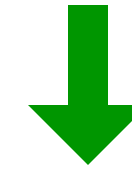
Design of independent performance aspects



interaction between design aspects

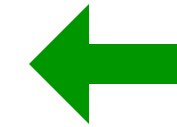

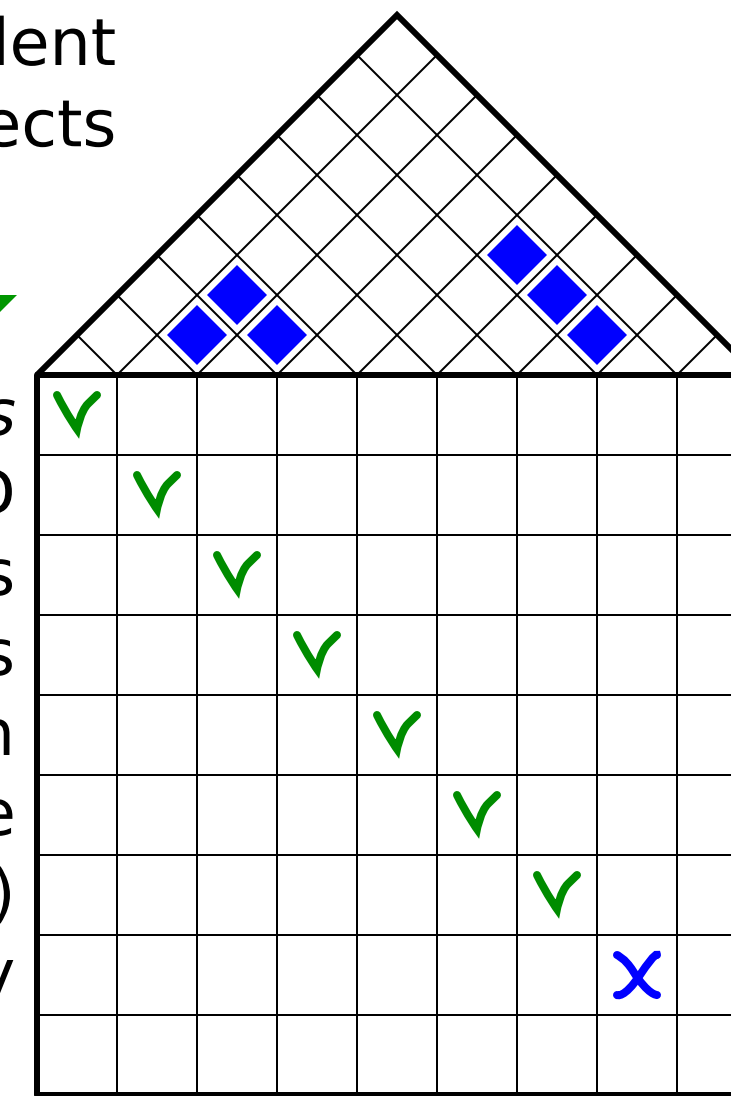*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)  
 Design of sufficiently low weak nonlinearity




SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice

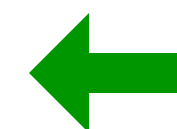**Differential-error-to-gain ratio**


Verify the biasing (operating point of all devices)  
 Verify all performance aspects  
 The weak nonlinearity can be reduced by:  
 Decreasing the differential-error-to-gain ratio per stage

*Function, performance, costs and environment*  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio




design aspects

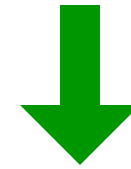Design of independent performance aspects



interaction between design aspects

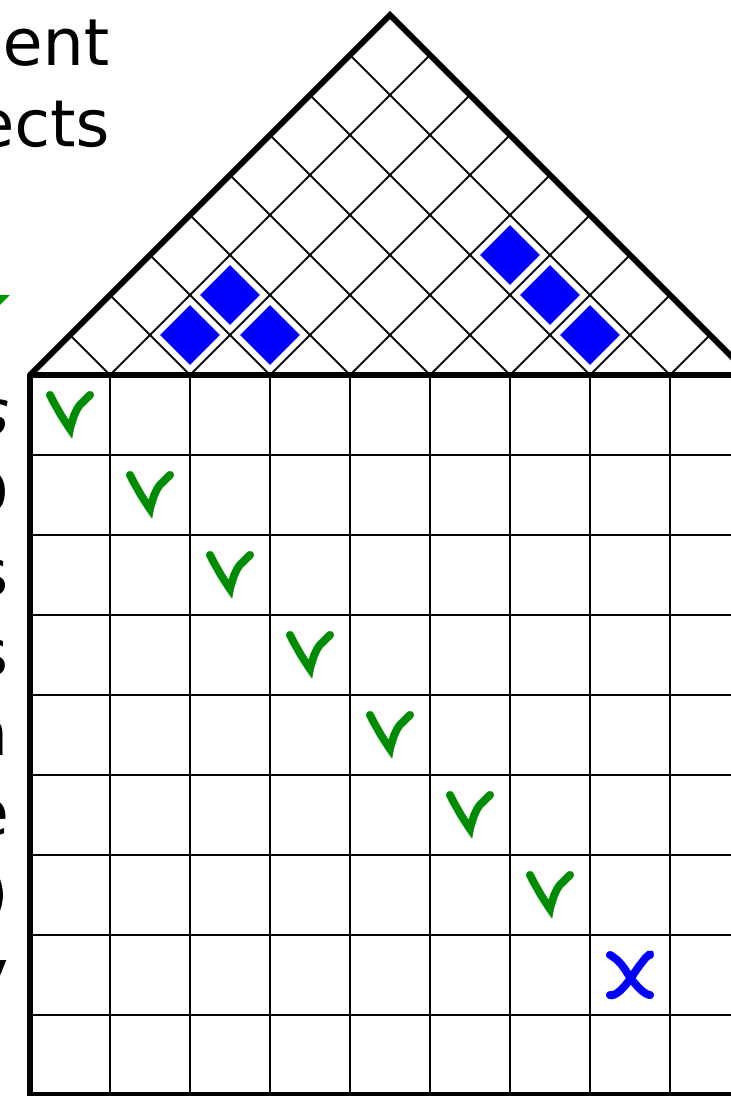*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)  
 Design of sufficiently low weak nonlinearity



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice


### Differential-error-to-gain ratio

- Verify the biasing (operating point of all devices)
- Verify all performance aspects
- The weak nonlinearity can be reduced by:
  - Decreasing the differential-error-to-gain ratio per stage
  - Modify the operating conditions and/or device geometry


Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio

design aspects

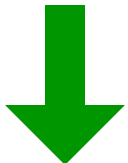
Design of independent performance aspects



interaction between design aspects

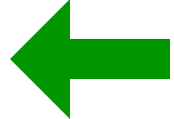

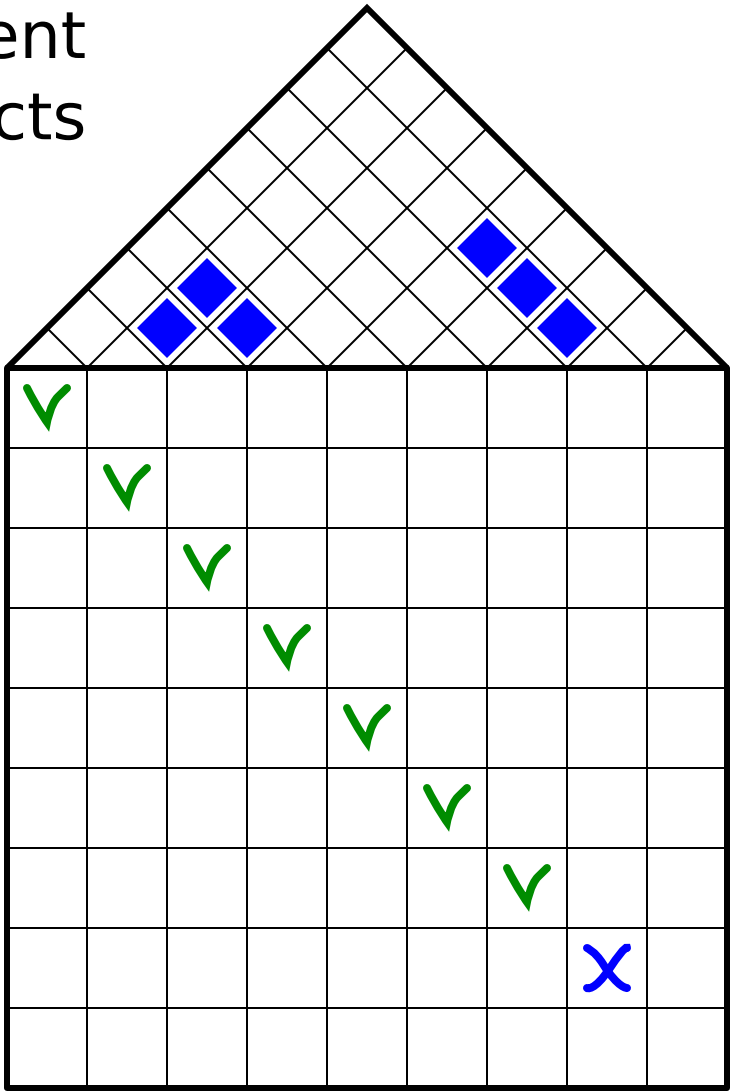Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)  
 Design of sufficiently low weak nonlinearity




SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice

**Differential-error-to-gain ratio**

Verify the biasing (operating point of all devices)  
 Verify all performance aspects  
 The weak nonlinearity can be reduced by:  
 Decreasing the differential-error-to-gain ratio per stage  
 Modify the operating conditions and/or device geometry  
 Increase the number of stages


Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio

design aspects

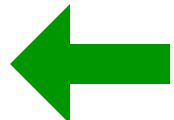




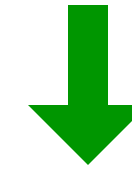
Design of independent performance aspects



interaction between design aspects

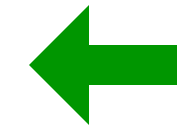

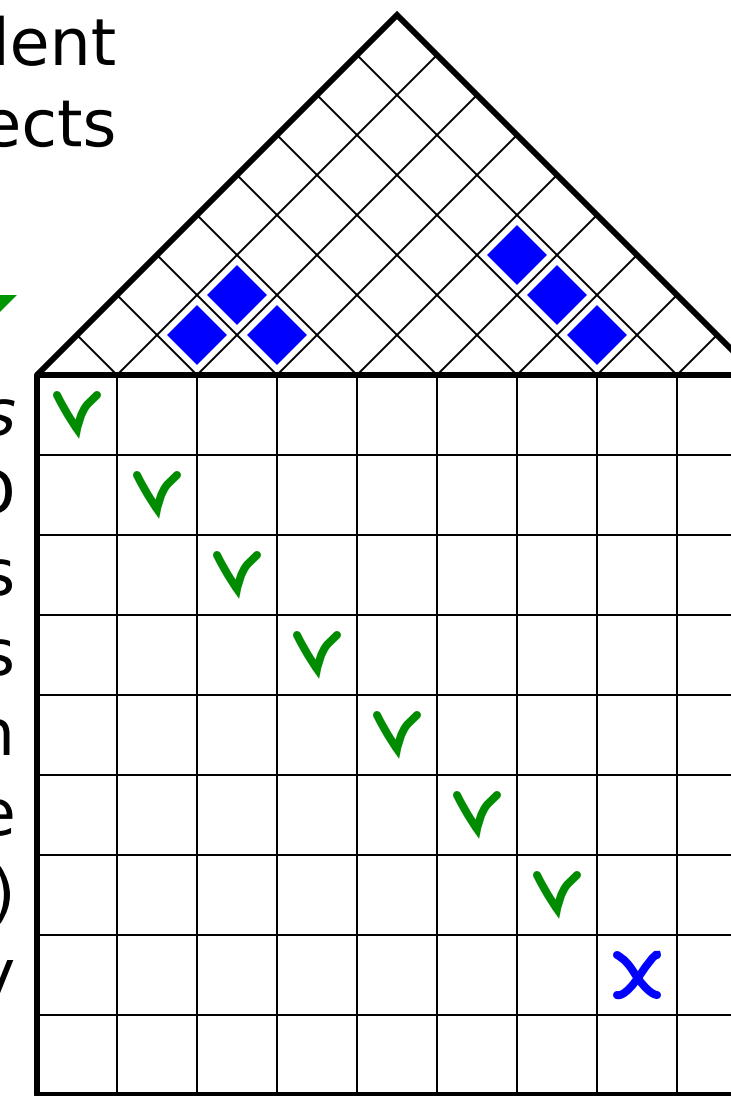*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)  
 Design of sufficiently low weak nonlinearity



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice


**Differential-error-to-gain ratio**

- Verify the biasing (operating point of all devices)
- Verify all performance aspects
- The weak nonlinearity can be reduced by:
  - Decreasing the differential-error-to-gain ratio per stage
  - Modify the operating conditions and/or device geometry
  - Increase the number of stages


**Design of the active antenna:**

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio


design aspects

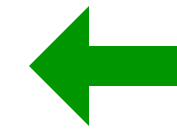

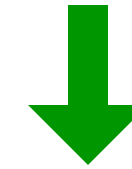
Design of independent performance aspects



interaction between design aspects

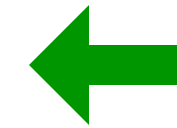

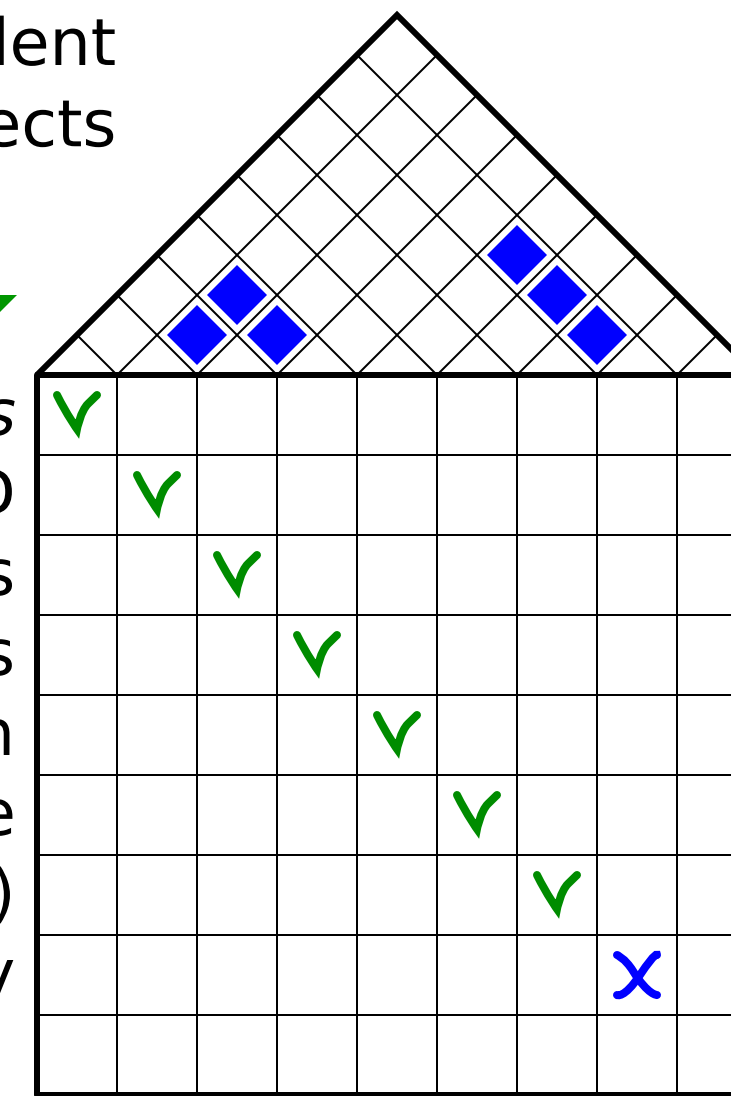*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)  
 Design of sufficiently low weak nonlinearity



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice

### Differential-error-to-gain ratio


- Verify the biasing (operating point of all devices)
- Verify all performance aspects
- The weak nonlinearity can be reduced by:
  - Decreasing the differential-error-to-gain ratio per stage
  - Modify the operating conditions and/or device geometry
  - Increase the number of stages

### Design of the active antenna:


Verification showed sufficiently low distortion

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio


design aspects

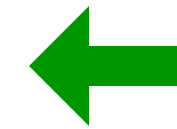

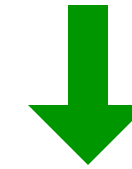
Design of independent performance aspects



interaction between design aspects

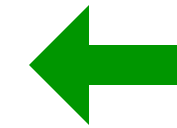

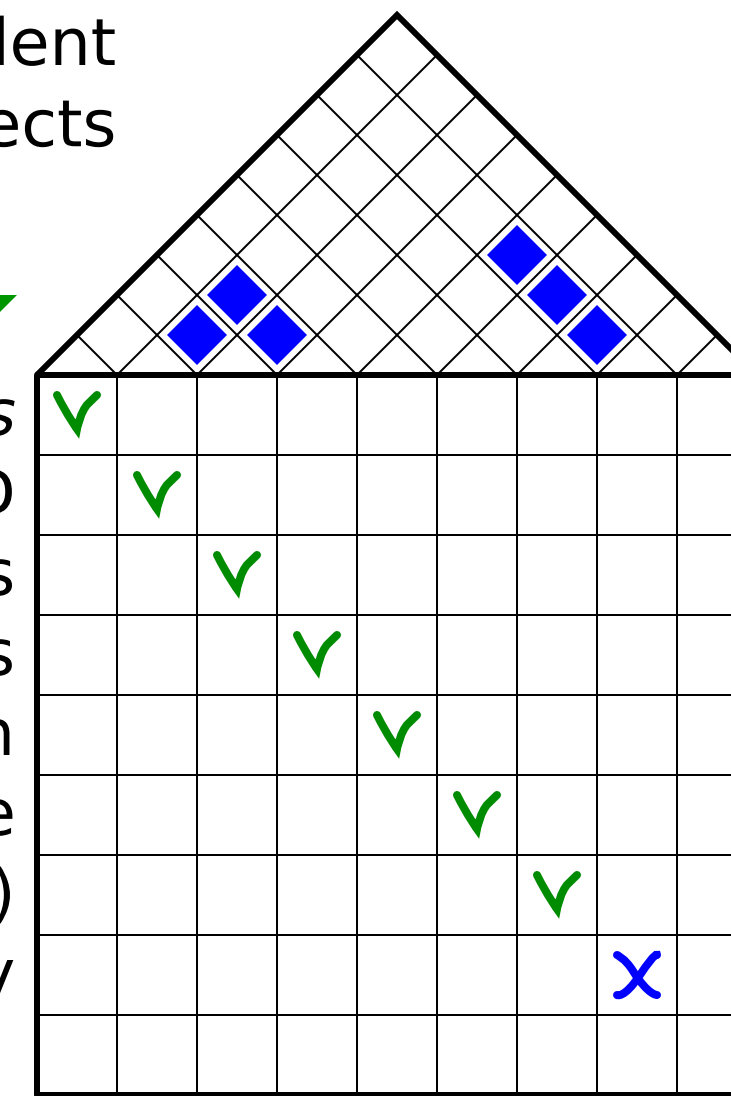*Setting up specifications*  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)  
 Design of sufficiently low weak nonlinearity



SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice


### Differential-error-to-gain ratio

- Verify the biasing (operating point of all devices)
- Verify all performance aspects
- The weak nonlinearity can be reduced by:
  - Decreasing the differential-error-to-gain ratio per stage
  - Modify the operating conditions and/or device geometry
  - Increase the number of stages
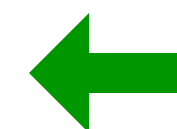
### Design of the active antenna:

Verification showed sufficiently low distortion

Function, performance,  
 costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio




design aspects

# Check performance


# Check performance

## Frequency response

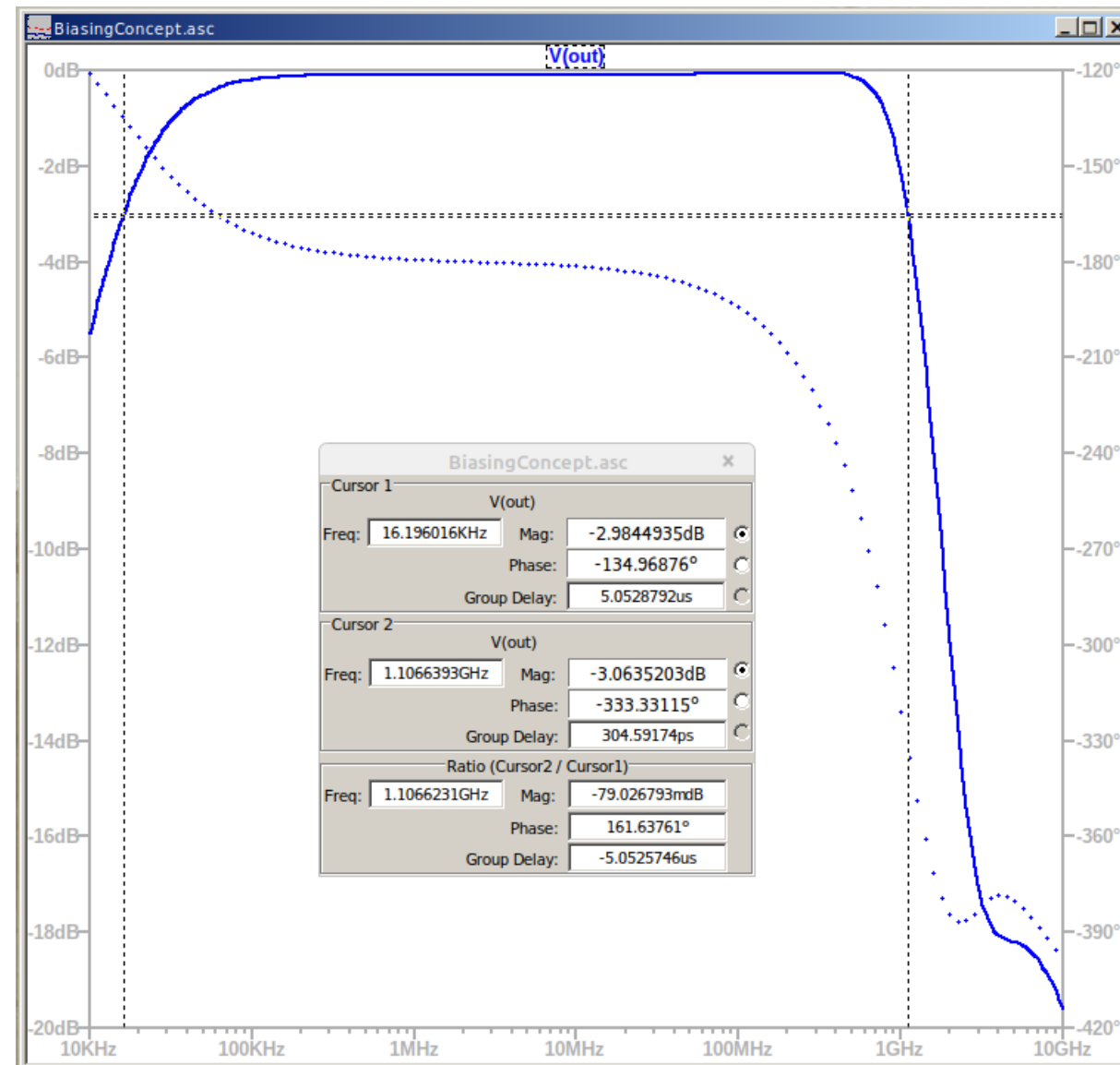


# Check performance

## Antenna referred noise

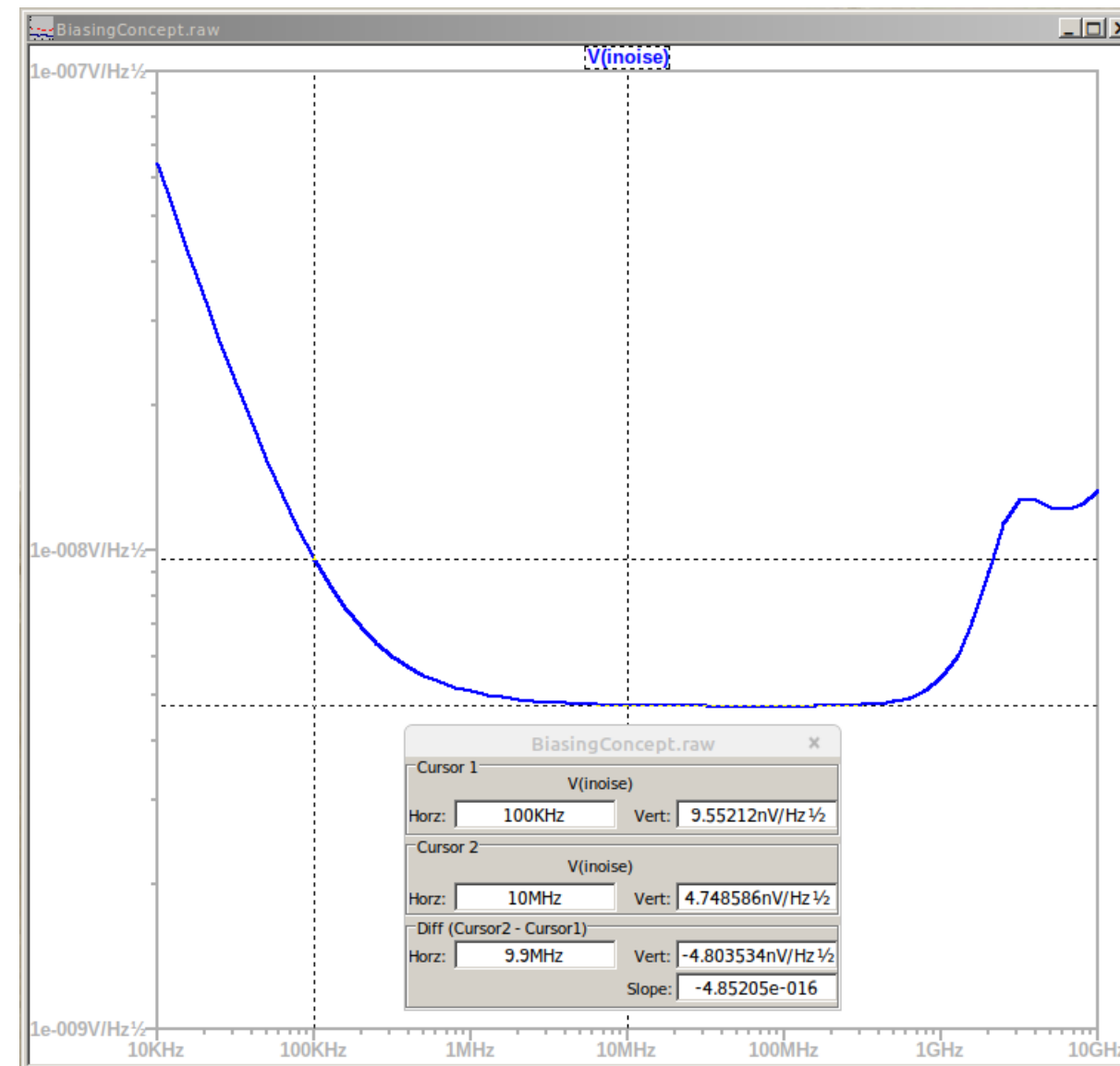


# Check performance

IMD

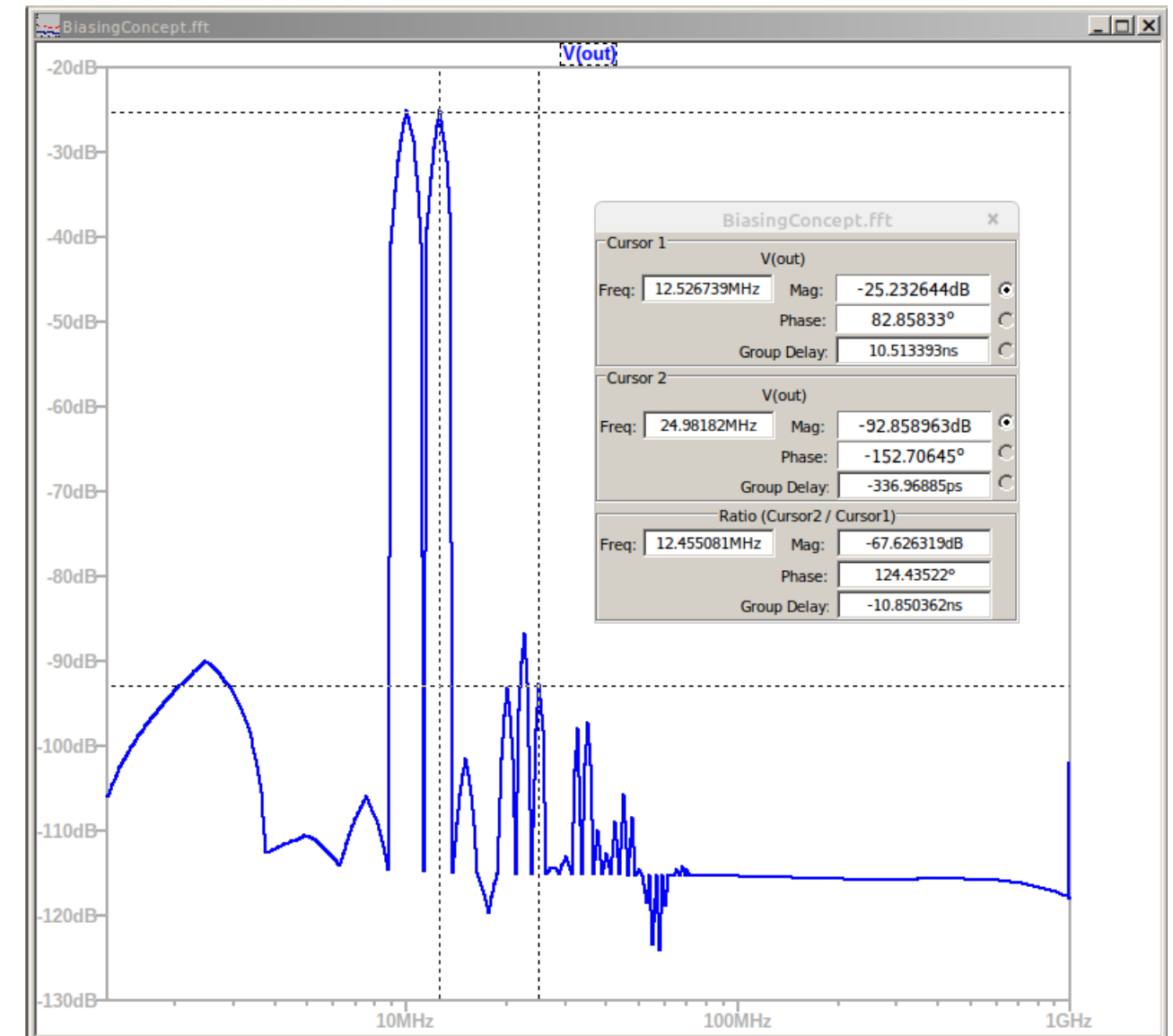


# Check performance


Frequency response

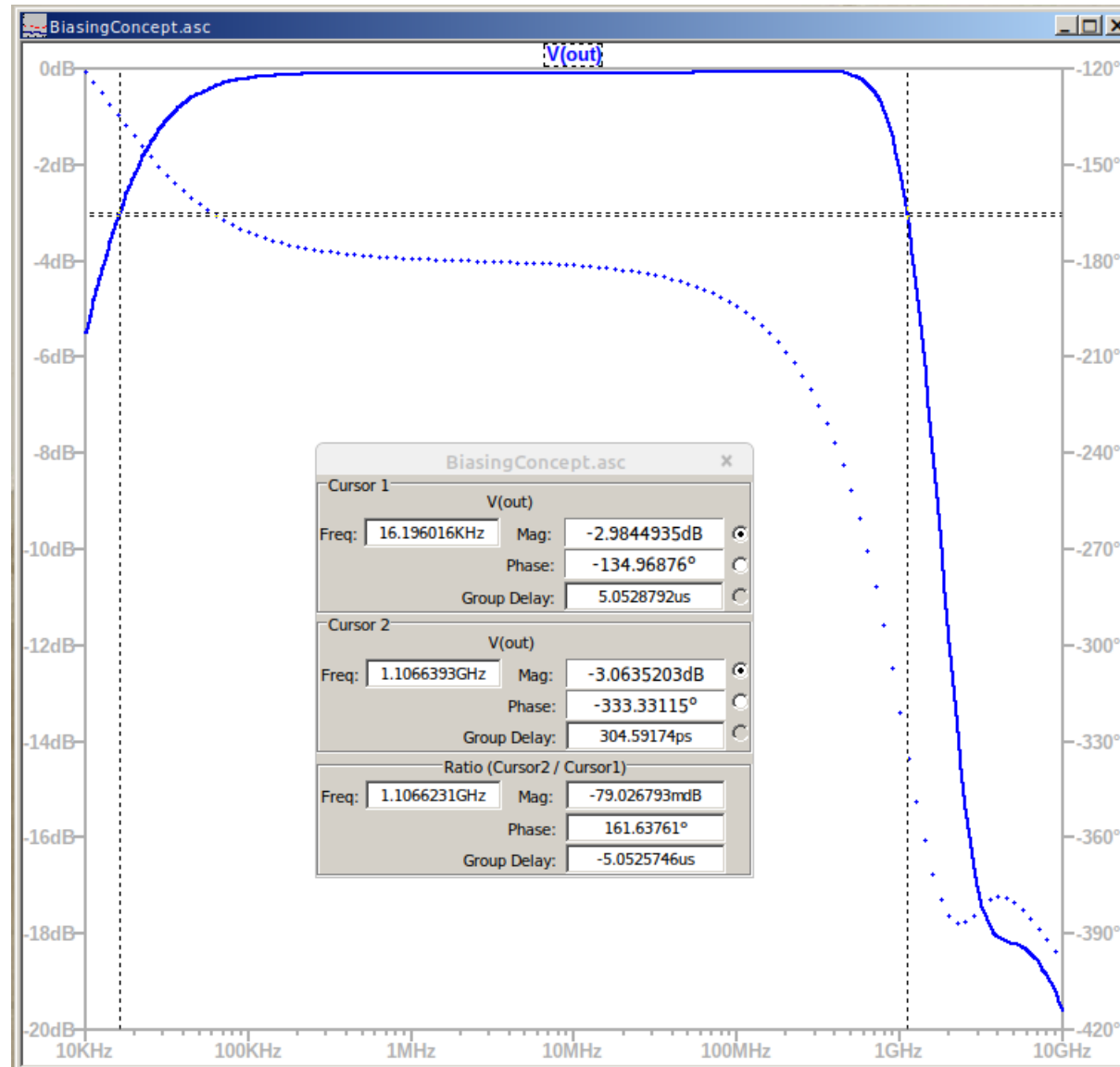

Antenna referred noise

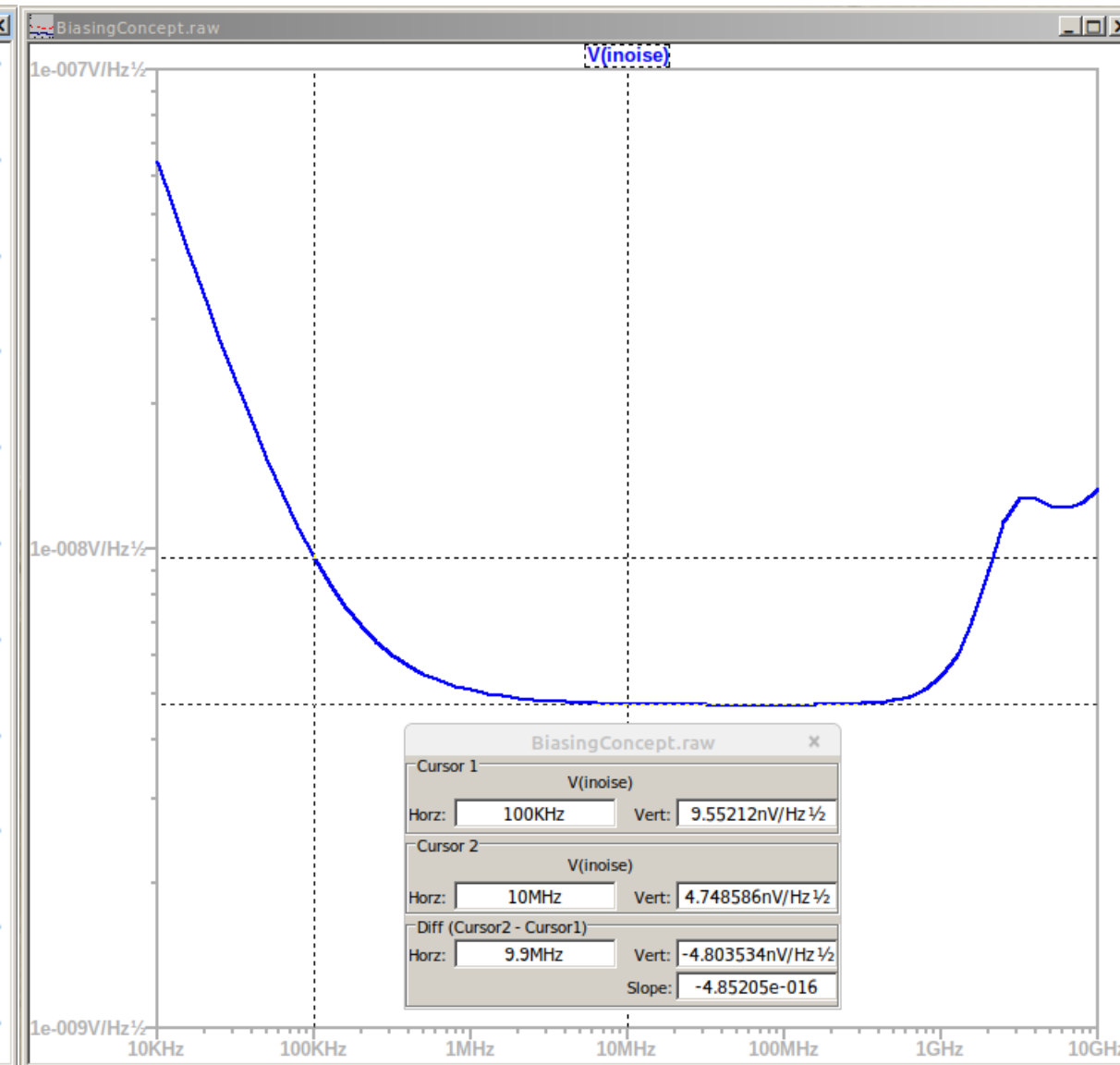

IMD

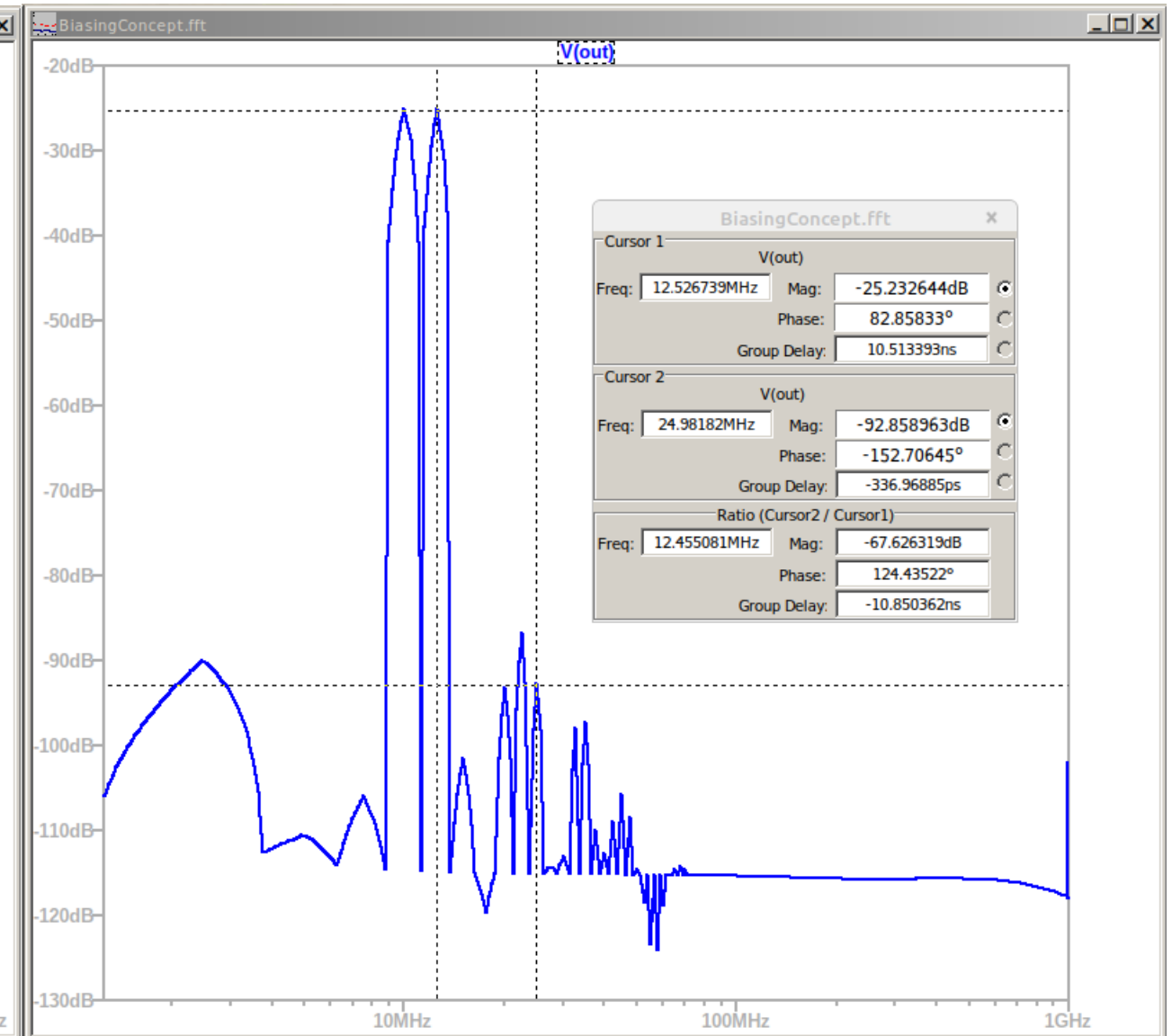




# **Structured Electronic Design**
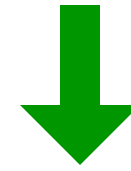
## Step 9 Design of the bias sources

*Anton J.M. Montagne*

Design of independent performance aspects



interaction between design aspects

Setting up specifications  
 Design of amplifier type: A, B, C, D  
 Feasibility of noise (temperature drift) specifications  
 Feasibility of static and dynamic drive requirements  
 Design of midband accuracy and amplifier bandwidth  
 Design of the frequency response  
 Design of the biasing (ideal sources)  
 Design of sufficiently low weak nonlinearity  
*Specification of bias sources*

|   |   |   |   |   |   |   |   |   |
|---|---|---|---|---|---|---|---|---|
|   |   |   |   |   |   |   |   |   |
|   |   |   |   |   |   |   |   |   |
| ✓ |   |   |   |   |   |   |   |   |
|   | ✓ |   |   |   |   |   |   |   |
|   |   | ✓ |   |   |   |   |   |   |
|   |   |   | ✓ |   |   |   |   |   |
|   |   |   |   | ✓ |   |   |   |   |
|   |   |   |   |   | ✓ |   |   |   |
|   |   |   |   |   |   | ✓ |   |   |
|   |   |   |   |   |   |   | ✓ |   |
|   |   |   |   |   |   |   |   | 🏠 |

SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice  
 SLiCAP / LTspice

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio  
*Design of bias sources*

design aspects

Design of independent performance aspects

interaction between design aspects

Same procedure for each bias source

- Setting up specifications
- Design of amplifier type: A, B, C, D
- Feasibility of noise (temperature drift) specifications
- Feasibility of static and dynamic drive requirements
- Design of midband accuracy and amplifier bandwidth
- Design of the frequency response
- Design of the biasing (ideal sources)
- Design of sufficiently low weak nonlinearity
- Specification of bias sources

|   |   |   |   |   |   |   |   |   |  |
|---|---|---|---|---|---|---|---|---|--|
|   |   |   |   |   |   |   |   |   |  |
| ✓ |   |   |   |   |   |   |   |   |  |
|   | ✓ |   |   |   |   |   |   |   |  |
|   |   | ✓ |   |   |   |   |   |   |  |
|   |   |   | ✓ |   |   |   |   |   |  |
|   |   |   |   | ✓ |   |   |   |   |  |
|   |   |   |   |   | ✓ |   |   |   |  |
|   |   |   |   |   |   | ✓ |   |   |  |
|   |   |   |   |   |   |   | ✓ |   |  |
|   |   |   |   |   |   |   |   | 🏠 |  |

SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice  
 SLiCAP / LTspice

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio  
 Design of bias sources

design aspects

Design of independent performance aspects

interaction between design aspects

Same procedure for each bias source

- Setting up specifications
- Design of amplifier type: A, B, C, D
- Feasibility of noise (temperature drift) specifications
- Feasibility of static and dynamic drive requirements
- Design of midband accuracy and amplifier bandwidth
- Design of the frequency response
- Design of the biasing (ideal sources)
- Design of sufficiently low weak nonlinearity
- Specification of bias sources

|   |   |   |   |   |   |   |   |   |  |
|---|---|---|---|---|---|---|---|---|--|
|   |   |   |   |   |   |   |   |   |  |
| ✓ |   |   |   |   |   |   |   |   |  |
|   | ✓ |   |   |   |   |   |   |   |  |
|   |   | ✓ |   |   |   |   |   |   |  |
|   |   |   | ✓ |   |   |   |   |   |  |
|   |   |   |   | ✓ |   |   |   |   |  |
|   |   |   |   |   | ✓ |   |   |   |  |
|   |   |   |   |   |   | ✓ |   |   |  |
|   |   |   |   |   |   |   | ✓ |   |  |
|   |   |   |   |   |   |   |   | 🏠 |  |

SLiCAP  
 SLiCAP  
 SLiCAP  
 LTspice  
 SLiCAP  
 SLiCAP  
 LTspice  
 LTspice  
 SLiCAP / LTspice

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio  
 Design of bias sources

design aspects

Design of independent performance aspects

interaction between design aspects

*Setting up specifications*

Design of amplifier type: A, B, C, D

Feasibility of noise (temperature drift) specifications

Feasibility of static and dynamic drive requirements

Design of midband accuracy and amplifier bandwidth

Design of the frequency response

Design of the biasing (ideal sources)

Design of sufficiently low weak nonlinearity

*Specification of bias sources*


SLiCAP  
SLiCAP  
SLiCAP  
LTspice  
SLiCAP  
SLiCAP  
LTspice  
LTspice  
SLiCAP / LTspice

Same procedure for each bias source

Function, performance, costs and environment  
Feedback configuration  
Controller input stage  
Controller output stage  
Loop gain poles product  
PZ pattern  
Bias structure  
Differential error to gain ratio  
*Design of bias sources*

design aspects

**Design of bias sources**

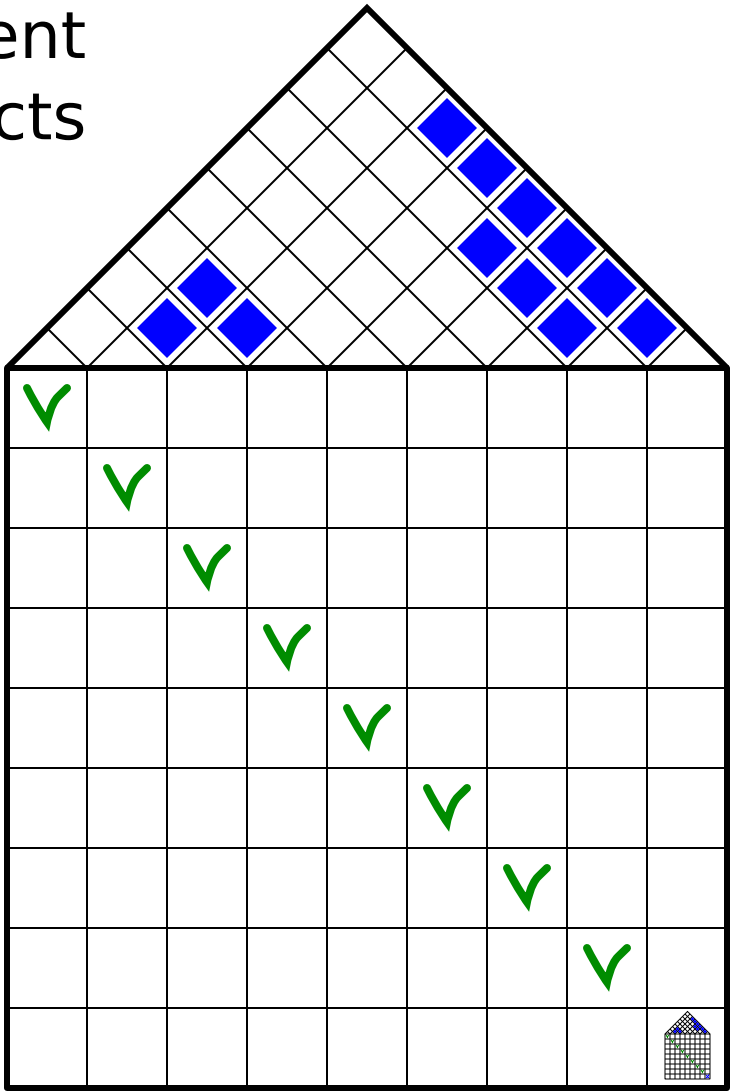

Design of independent performance aspects

interaction between design aspects

Same procedure for each bias source

- Setting up specifications
- Design of amplifier type: A, B, C, D
- Feasibility of noise (temperature drift) specifications
- Feasibility of static and dynamic drive requirements
- Design of midband accuracy and amplifier bandwidth
- Design of the frequency response
- Design of the biasing (ideal sources)
- Design of sufficiently low weak nonlinearity
- Specification of bias sources

|   |   |   |   |   |   |   |   |   |  |
|---|---|---|---|---|---|---|---|---|--|
|   |   |   |   |   |   |   |   |   |  |
| ✓ |   |   |   |   |   |   |   |   |  |
|   | ✓ |   |   |   |   |   |   |   |  |
|   |   | ✓ |   |   |   |   |   |   |  |
|   |   |   | ✓ |   |   |   |   |   |  |
|   |   |   |   | ✓ |   |   |   |   |  |
|   |   |   |   |   | ✓ |   |   |   |  |
|   |   |   |   |   |   | ✓ |   |   |  |
|   |   |   |   |   |   |   | ✓ |   |  |
|   |   |   |   |   |   |   |   | 🏠 |  |

- SLiCAP
- SLiCAP
- SLiCAP
- LTspice
- SLiCAP
- SLiCAP
- LTspice
- LTspice
- SLiCAP / LTspice

- Function, performance, costs and environment
- Feedback configuration
- Controller input stage
- Controller output stage
- Loop gain poles product
- PZ pattern
- Bias structure
- Differential error to gain ratio
- Design of bias sources

design aspects

**Design of bias sources**

Find an operating mechanism:

Design of independent performance aspects

interaction between design aspects

Same procedure for each bias source

- Setting up specifications
- Design of amplifier type: A, B, C, D
- Feasibility of noise (temperature drift) specifications
- Feasibility of static and dynamic drive requirements
- Design of midband accuracy and amplifier bandwidth
- Design of the frequency response
- Design of the biasing (ideal sources)
- Design of sufficiently low weak nonlinearity
- Specification of bias sources

|   |   |   |   |   |   |   |   |   |  |
|---|---|---|---|---|---|---|---|---|--|
|   |   |   |   |   |   |   |   |   |  |
| ✓ |   |   |   |   |   |   |   |   |  |
|   | ✓ |   |   |   |   |   |   |   |  |
|   |   | ✓ |   |   |   |   |   |   |  |
|   |   |   | ✓ |   |   |   |   |   |  |
|   |   |   |   | ✓ |   |   |   |   |  |
|   |   |   |   |   | ✓ |   |   |   |  |
|   |   |   |   |   |   | ✓ |   |   |  |
|   |   |   |   |   |   |   | ✓ |   |  |
|   |   |   |   |   |   |   |   | 🏠 |  |

- SLiCAP
- SLiCAP
- SLiCAP
- LTspice
- SLiCAP
- SLiCAP
- LTspice
- LTspice
- SLiCAP / LTspice

- Function, performance, costs and environment
- Feedback configuration
- Controller input stage
- Controller output stage
- Loop gain poles product
- PZ pattern
- Bias structure
- Differential error to gain ratio
- Design of bias sources

design aspects

**Design of bias sources**

Find an operating mechanism:  
 Element with voltage or current source character

Design of independent performance aspects

interaction between design aspects

Same procedure for each bias source

- Setting up specifications
- Design of amplifier type: A, B, C, D
- Feasibility of noise (temperature drift) specifications
- Feasibility of static and dynamic drive requirements
- Design of midband accuracy and amplifier bandwidth
- Design of the frequency response
- Design of the biasing (ideal sources)
- Design of sufficiently low weak nonlinearity
- Specification of bias sources

|   |   |   |   |   |   |   |   |   |  |
|---|---|---|---|---|---|---|---|---|--|
|   |   |   |   |   |   |   |   |   |  |
| ✓ |   |   |   |   |   |   |   |   |  |
|   | ✓ |   |   |   |   |   |   |   |  |
|   |   | ✓ |   |   |   |   |   |   |  |
|   |   |   | ✓ |   |   |   |   |   |  |
|   |   |   |   | ✓ |   |   |   |   |  |
|   |   |   |   |   | ✓ |   |   |   |  |
|   |   |   |   |   |   | ✓ |   |   |  |
|   |   |   |   |   |   |   | ✓ |   |  |
|   |   |   |   |   |   |   |   | 🏠 |  |

- SLiCAP
- SLiCAP
- SLiCAP
- LTspice
- SLiCAP
- SLiCAP
- LTspice
- LTspice
- SLiCAP / LTspice

- Function, performance, costs and environment
- Feedback configuration
- Controller input stage
- Controller output stage
- Loop gain poles product
- PZ pattern
- Bias structure
- Differential error to gain ratio
- Design of bias sources

design aspects

**Design of bias sources**

Find an operating mechanism:  
 Element with voltage or current source character  
 Study in which way performance aspects can be affected by design



Design of independent performance aspects

interaction between design aspects

Same procedure for each bias source

- Setting up specifications
- Design of amplifier type: A, B, C, D
- Feasibility of noise (temperature drift) specifications
- Feasibility of static and dynamic drive requirements
- Design of midband accuracy and amplifier bandwidth
- Design of the frequency response
- Design of the biasing (ideal sources)
- Design of sufficiently low weak nonlinearity
- Specification of bias sources

|   |   |   |   |   |   |   |   |   |  |
|---|---|---|---|---|---|---|---|---|--|
|   |   |   |   |   |   |   |   |   |  |
| ✓ |   |   |   |   |   |   |   |   |  |
|   | ✓ |   |   |   |   |   |   |   |  |
|   |   | ✓ |   |   |   |   |   |   |  |
|   |   |   | ✓ |   |   |   |   |   |  |
|   |   |   |   | ✓ |   |   |   |   |  |
|   |   |   |   |   | ✓ |   |   |   |  |
|   |   |   |   |   |   | ✓ |   |   |  |
|   |   |   |   |   |   |   | ✓ |   |  |
|   |   |   |   |   |   |   |   | 🏠 |  |

- SLiCAP
- SLiCAP
- SLiCAP
- LTspice
- SLiCAP
- SLiCAP
- LTspice
- LTspice
- SLiCAP / LTspice

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio  
 Design of bias sources

design aspects

**Design of bias sources**

- Find an operating mechanism:
  - Element with voltage or current source character
- Study in which way performance aspects can be affected by design
- If necessary: improve performance versus costs through application of error-reduction techniques

Design of independent performance aspects

interaction between design aspects

Same procedure for each bias source

- Setting up specifications
- Design of amplifier type: A, B, C, D
- Feasibility of noise (temperature drift) specifications
- Feasibility of static and dynamic drive requirements
- Design of midband accuracy and amplifier bandwidth
- Design of the frequency response
- Design of the biasing (ideal sources)
- Design of sufficiently low weak nonlinearity
- Specification of bias sources

|   |   |   |   |   |   |   |   |   |   |
|---|---|---|---|---|---|---|---|---|---|
|   |   |   |   |   |   |   |   |   |   |
| ✓ |   |   |   |   |   |   |   |   |   |
|   | ✓ |   |   |   |   |   |   |   |   |
|   |   | ✓ |   |   |   |   |   |   |   |
|   |   |   | ✓ |   |   |   |   |   |   |
|   |   |   |   | ✓ |   |   |   |   |   |
|   |   |   |   |   | ✓ |   |   |   |   |
|   |   |   |   |   |   | ✓ |   |   |   |
|   |   |   |   |   |   |   | ✓ |   |   |
|   |   |   |   |   |   |   |   | ✓ |   |
|   |   |   |   |   |   |   |   |   | 🏠 |

- SLiCAP
- SLiCAP
- SLiCAP
- LTspice
- SLiCAP
- SLiCAP
- LTspice
- LTspice
- SLiCAP / LTspice

Function, performance, costs and environment  
 Feedback configuration  
 Controller input stage  
 Controller output stage  
 Loop gain poles product  
 PZ pattern  
 Bias structure  
 Differential error to gain ratio  
 Design of bias sources

design aspects

**Design of bias sources**

- Find an operating mechanism:
  - Element with voltage or current source character
- Study in which way performance aspects can be affected by design
- If necessary: improve performance versus costs through application of error-reduction techniques